

Department of Avionics,
Indian Institute of Space Science & Technology, Trivandrum
AV491 – Advanced Sensors and Interface Electronics
Instructor: Anoop C. S., Tutorial – 3

Q. 1. A piezoelectric crystal has an effective mass of 10 g, stiffness of 10^{10} N m^{-1} and damping constant of 200 N s m^{-1} . Electrical capacitance of crystal is 1000 pF and its charge to force sensitivity is $2 \times 10^{-10} \text{ C N}^{-1}$.

- (a) Incorporate the crystal into a Closed-Loop Oscillator System (CLOS) which can oscillate at the crystal parallel resonant frequency.
- (b) Design the specifications of the amplifier that should be used in the CLOS.
- (c) Draw neatly labelled circuits/waveforms/responses of the CLOS system to explain your design methodology.

Q. 2. A piezoelectric transducer has a capacitance of 1200 pF and sensitivity of $100 \text{ pC}/\mu\text{m}$. The connecting cable has a capacitance of 250 pF, while the oscilloscope used for read-out has an input impedance of $2 \text{ M}\Omega // 75 \text{ pF}$.

- (a) Compute the sensitivity ($\text{mV}/\mu\text{m}$) of the transducer alone.
- (b) Compute the high-frequency sensitivity ($\text{mV}/\mu\text{m}$) of the entire measurement system.
- (c) What is the lowest frequency that can be measured with 5 % amplitude error by the entire system?

Q. 3. An input, $x(t)$ is applied to a piezoelectric transducer.

$$x(t) = \begin{cases} At; & 0 < t < T \\ 0; & t > T \end{cases}$$

Solve the differential equation and find the output of the transducer.

Q. 4. A transit time ultrasonic flowmeter is used to measure the velocity of a fluid in a pipe. Transit time during zero flow was found to be 1 ms. When there is a flow, the differential transit-time is found as $87 \mu\text{s}$. The angle between the line connecting the transmitter/receiver and flow direction is 30° .

Find the velocity of the fluid. Velocity of the sound in the fluid is 500 m/s.

Q. 5. Consider the readout circuit of a piezoelectric sensor shown in the figure.

When the piezoelectric sensor generates a charge q_p , the resulting change in voltage V_x is -2 V . Then, find the corresponding change in the voltage V_{out} .

