

Digital Electronics Verilog Lab 6

Submitted By:

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)

PRE-LAB TASK

Question: Write a verilog code for down conversion of the in-built clock of 125 MHz to 10 kHz (nearest possible).

Sol:

Frequency Divider

```
module DFF (clk, reset, D, Q_bar);
```

```
input D, clk, reset;
```

```
output reg Q_bar; Q_bar;
```

```
always @(posedge clk)
```

```
begin
```

```
if(reset)
```

```
begin
```

```
Q_bar <= 0;
```

```
Q_bar <= 1;
```

```
end
```

```
else
```

```
begin
```

```
Q_bar <= D;
```

```
Q_bar <= ~D;
```

```
end
```

```
end
```

```
endmodule
```

```
module divideFreq (clk, reset, In, Out);
```

```
input clk, reset, In;
```

```
output Out;
```

```
wire q1, q2, q3, q4, q5, q6, q7, q8, q9, q10, q11, q12;
```

```
DFF f1 (clk, reset, In, q1);
```

```
DFF f2 (clk, reset, q1, q2);
```

```
DFF f3
```

```
...
```

```
DFF f12 (clk, reset, q11, q12);
```

```
DFF f13 (clk, reset, q12, Out);
```

```
endmodule
```




LAB SHEET

Question No. 1. Integrate VIO and ILA IP cores in problem 1 of the previous lab sheet and visualize input-outputs virtually.

Sol: Moore Machine:

Moore Machine: 0110

 

Code:

```

module detect_0110_Moore(clk,reset,In,Out);
  input clk, reset, In;
  output reg Out;

```

```

  parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100;
  reg[2:0] CurrentState,NextState;

```

```

  always@(posedge clk)
  begin
    if(reset)
      CurrentState = S0;
    else
      CurrentState = NextState;
    end

```

```

  always@(CurrentState, In)
  begin
    case(CurrentState)
    S0:begin
      if(!In) NextState = S1;
      else NextState = S0;
      end
    S1:begin
      if(!In) NextState = S1;
      else NextState = S2;
      end
    S2:begin
      if(!In) NextState = S1;
      else NextState = S3;
      end
    S3:begin
      if(!In) NextState = S4;
      else NextState = S0;
      end
    S4:begin
      if(!In) NextState = S1;
      else NextState = S0;
      end
    default:NextState = S0;
    endcase
  end

```

```

  always@(CurrentState)
  begin
    case(CurrentState)

```

```

S0: Out = 0;
S1: Out = 0;
S2: Out = 0;
S3: Out = 0;
S4: Out = 1;
endcase
end


```

```


endmodule

```

Schematic:

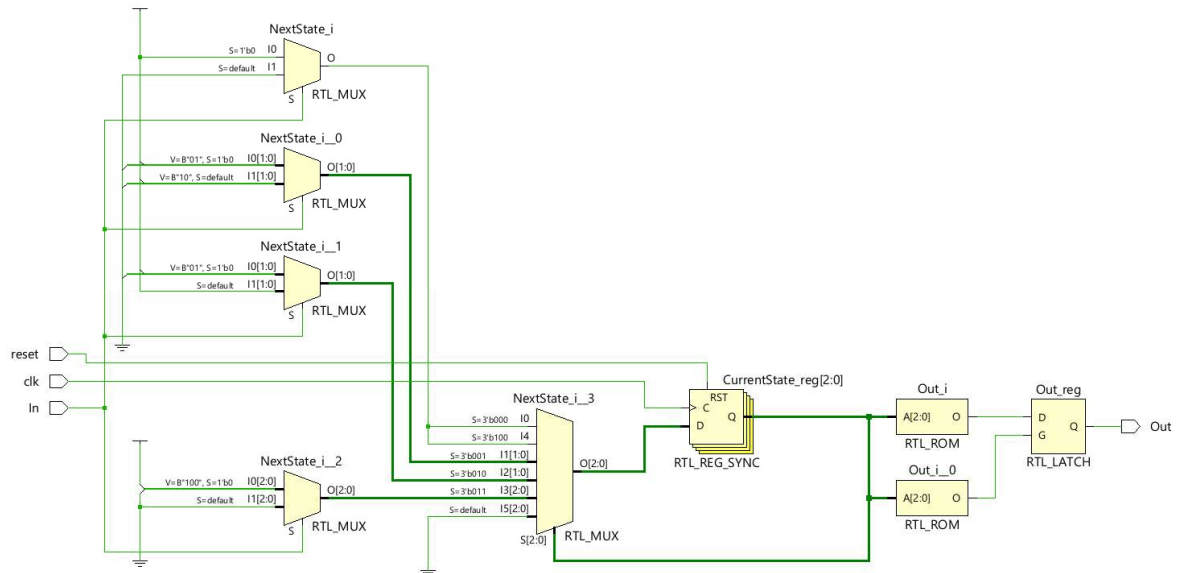


Simulation:

 

Mealy Machine:

Mealy Machine: 0110

 

Code:

```

module detect_0110_Mealy(clk,reset,In,Out);
    input clk, reset, In;
    output reg Out;

    parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011;
    reg[2:0] CurrentState,NextState;

    always@(posedge clk)
    begin
        if(reset)
            CurrentState = S0;
        else
            CurrentState = NextState;
        end

    always@(CurrentState, In)
    begin
        case(CurrentState)
        S0:begin
            if(!In)
                begin
                    NextState = S1;
                    Out = 0;
                end
            else
                begin
                    NextState = S0;
                    Out = 0;
                end
            end
        S1:begin
            if(!In)
                begin
                    NextState = S1;
                    Out = 0;
                end
            else
                begin
                    NextState = S2;
                    Out = 0;
                end
            end
        S2:begin
            if(!In)

```

```


begin
  NextState = S1;
  Out = 0;
end
else
  begin
    NextState = S3;
    Out = 0;
  end
end
S3:begin
  if(!In)
    begin
      NextState = S0;
      Out = 1;
    end
  else
    begin
      NextState = S0;
      Out = 0;
    end
  end
end
default:NextState = S0;
endcase
end

```

Endmodule

endmodule

Schematic:

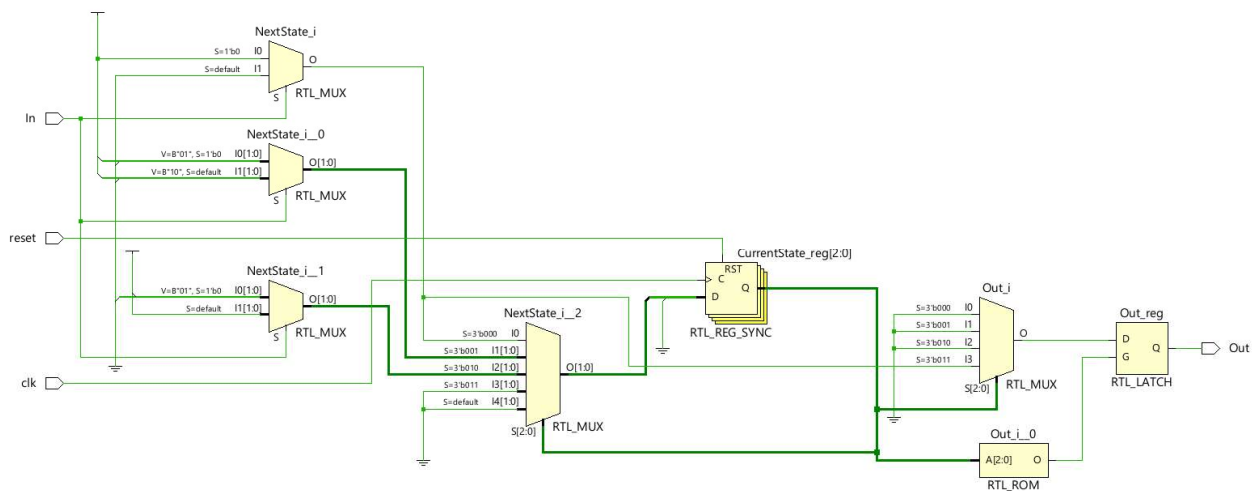

Simulation:



Question No. 2. Design RAM and ROM of size 5*5 to store 8-bits data. Use the design steps from design template shown in the presentation to include enable options for read and write operations, reset, etc. in the code.

Sol: RAM:

Code:


```
module ram(clk,address,data,cs,we,re);
    input clk,cs,we,re;
    input[7:0] address;
    inout[7:0] data;

    reg[7:0] data_out;
    reg[7:0] mem[0:25];
    assign data = (cs && re && !we) ? data_out:8'bz;


    //Memory Write Block when we=1; cs=1; re=0
    always@(posedge clk)
    begin:MEM_WRITE
        if(cs && we && !re) begin
            mem[address] = data;
        end
    end

    //Memory Read Block
    //Read Operation: When we=0; re=1; cs=1
    always@(posedge clk)
    begin:MEM_READ
        if(cs && !we && re) begin
            data_out = mem[address];
        end
    end
endmodule
```

Schematic:

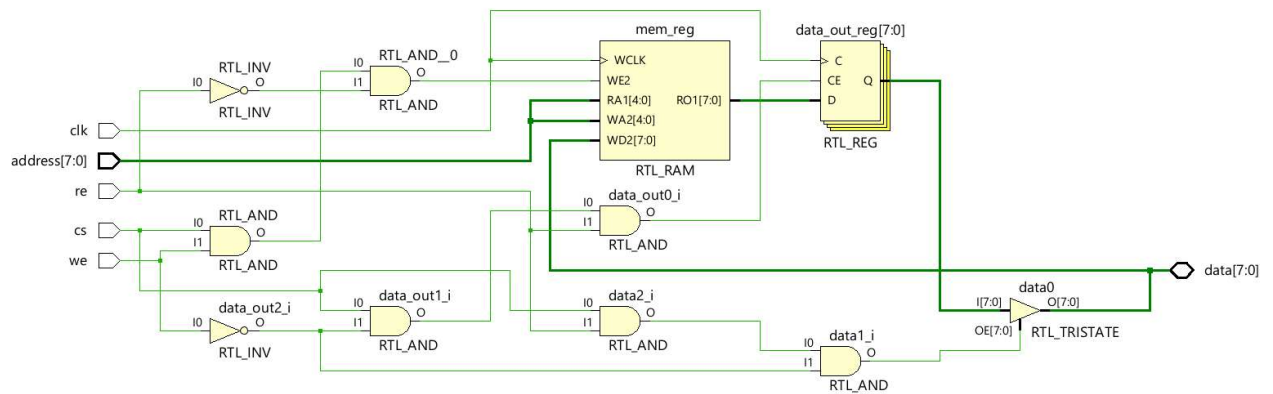

Synthesis:

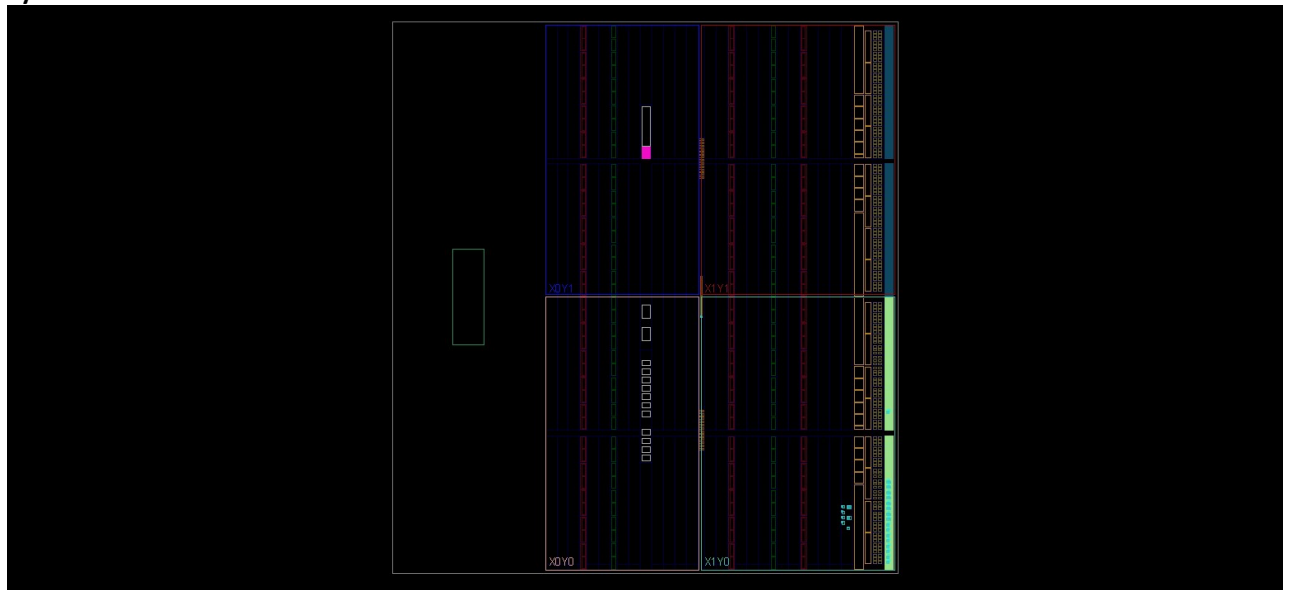

ROM:

Code:

```

module rom(clock,add,dataOut,en);
  input clock,en;
  input[7:0] add;
  output reg [7:0] dataOut;
  reg[7:0] memory[0:25];

  initial
  begin
    dataOut = 25'b0;
  end

  always@(add)
  case(add)
    8'b00000000 : memory[add] = 25'b00000001;
    8'b00000001 : memory[add] = 25'b00000010;
    8'b00000010 : memory[add] = 25'b00000011;
    8'b00000011 : memory[add] = 25'b00000100;
    8'b00000100 : memory[add] = 25'b00000101;
    8'b00000101 : memory[add] = 25'b00000110;
    8'b00000110 : memory[add] = 25'b00000111;
    8'b00000111 : memory[add] = 25'b00001000;
    8'b00001000 : memory[add] = 25'b00001001;
  end

```



```

8'b00001001 : memory[add] = 25'b00001010;
8'b00001010 : memory[add] = 25'b00001011;
8'b00001011 : memory[add] = 25'b00001100;
8'b00001100 : memory[add] = 25'b00001101;
8'b00001101 : memory[add] = 25'b00001110;
8'b00001110 : memory[add] = 25'b00001111;
8'b00001111 : memory[add] = 25'b00010000;

```

```

default: memory[add] = 25'b00000000;

```

```

endcase

```

```

always@(posedge clock)
begin
    if(en) begin
        dataOut <= memory[add];
    end
    else
        dataOut <= dataOut;
    end
end


```


```

endmodule


```

Schematic:

 

 

Synthesis:

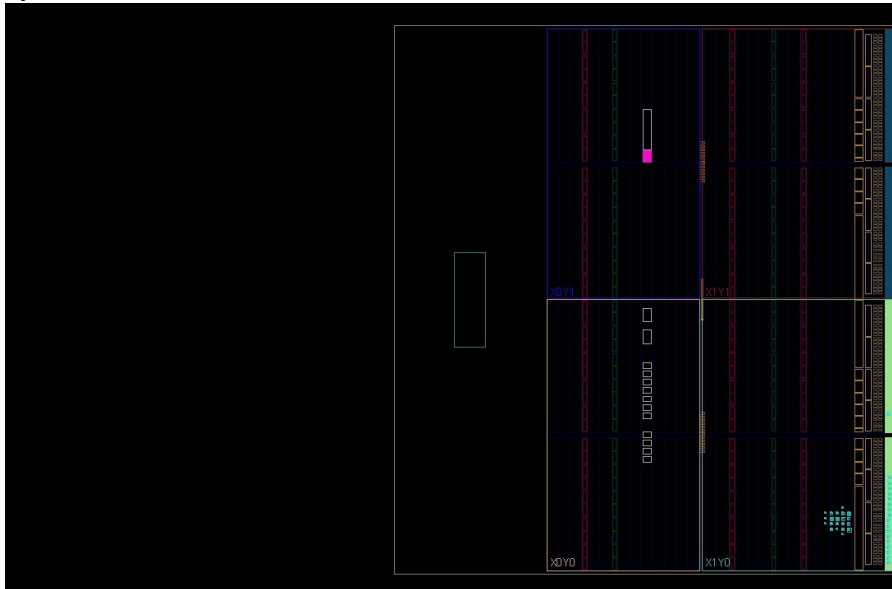

ASSIGNMENT

Question: In problem 2 above, use a text file to feed the data using \$readmemb or \$readmemh commands.

Sol: Code:

```
module memory(inbus, outbus, add, rd_mem, wr_mem);
    input [5:0] add;
    input [7:0] inbus;
    input rd_mem, wr_mem;

    output [7:0] outbus;

    reg [7:0] mem [0:25];

    // mem read data from file
    initial begin
        $readmemb("./memfile.txt", mem, 50, 60);
    end
    //read part

    assign outbus = rd_mem ? mem [add] : 8'bz;
    always @ (wr_mem)
        if (wr_mem == 1) mem [add] <= inbus;
```

endmodule

Schematic:

