

## Digital Electronics Verilog Lab 3

**Submitted By:**

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)

### LAB SHEET

**Question No. 1** Make an one bit comparator circuit through HDL

**Sol: Boolean** expression should be:

**To check if (A=B) :**  $Y = (A \text{ and } B) \text{ or } (\text{not } A \text{ and not } B) = A \text{ xnor } B$


**To check if (A>B) :**  $Y = A \text{ and } (\text{not } B)$

**To check if (A<B) :**  $Y = (\text{not } A) \text{ and } B$


**Code:**

```
module comparator(  
    input A,B,  
    output Yequal, Ygreater, Ylesser);  
    assign Yequal = (A&B)|((~A)&(~B)); //A=B  
    assign Ygreater = A&(~B); //A>B  
    assign Ylesser = (~A)&B; //A<B  
endmodule
```


**Schematic:**

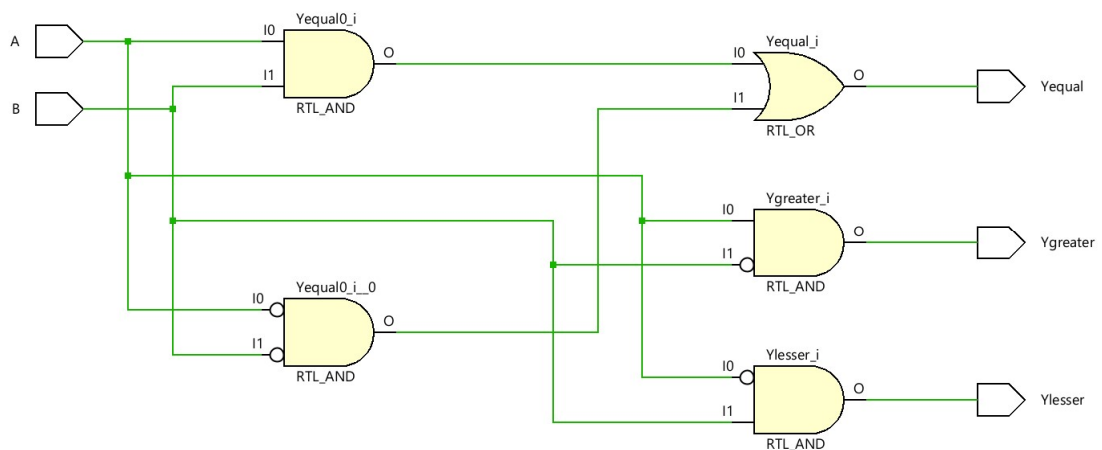

**Simulation:**

 

### Synthesis:

 

**Question No. 2** Make an 4 bit Ripple Carry Adder circuit by module Instantiation technique.

[Hint: Make one full adder circuit and then instantiate (call) it for four times.]

**Sol:** The **boolean** expression for Full Adder:

$$\text{Sum} = A \text{ xor } B \text{ xor } \text{Cin}$$

$$\text{Cout} = (A \text{ and } B) \text{ or } (B \text{ and } \text{Cin}) \text{ or } (\text{Cin} \text{ and } A)$$

**Code:**

```
module fullAdder(Sum,Cout,A,B,Cin);
```

```
input A,B,Cin;
```

```
output Sum,Cout;
```

```
assign Sum = A^B^Cin;
```

```
assign Cout = (A&B) | (B&Cin) | (Cin&A);
```

```
endmodule
```

```
module rippleCarryAddder_4bit(
```

```
input A0,A1,A2,A3,B0,B1,B2,B3,
```

```
input Cin,
```

```
output Sum0,Sum1,Sum2,Sum3,
```

```
output Cout);
```

```
wire C1,C2,C3;
```


```
//Instantiate four 1-bit full adders
```

```
fullAdder f0(Sum0,C1,A0,B0,Cin);
```



```
fullAdder f1(Sum1,C2,A1,B1,C1);
```

```
fullAdder f2(Sum2,C3,A2,B2,C2);
fullAdder f3(Sum3,Cout,A3,B3,C3);
```

**Schematic:**

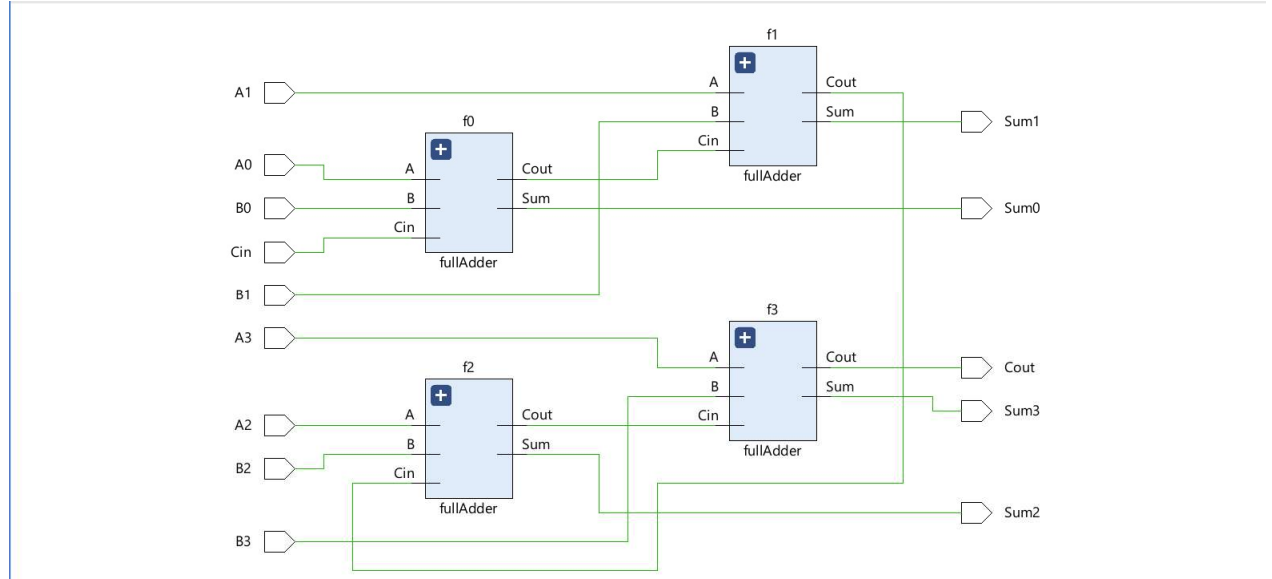


### Simulation:

  

**Synthesis:**



 

**Question No. 3** Make an SR Latch.

[Hint: Latch is level sensitive not an edge sensitive]


**Sol:** SR Latch truth table using NAND Gates:

S	R	Q(t+1)	Q'(t+1)
1	1	Q(t)	Q'(t)
0	1	1	0
1	0	0	1
0	0	Undetermined	Undetermined


**Code:**

```
module srLatch(
    input S, R, prevState,
    output reg nextState, not_nextState);
always@(*)
begin
    if(S==1'b1 & R==1'b1)
    begin
        nextState = prevState;
        not_nextState = ~prevState;
    end
    else if(S==1'b0 & R==1'b1)
    begin
        nextState = 1'b1;
        not_nextState = 1'b0;
    end
    else
    begin
        nextState = 1'b0;
        not_nextState = 1'b1;
    end
end
endmodule
```


**Schematic:**

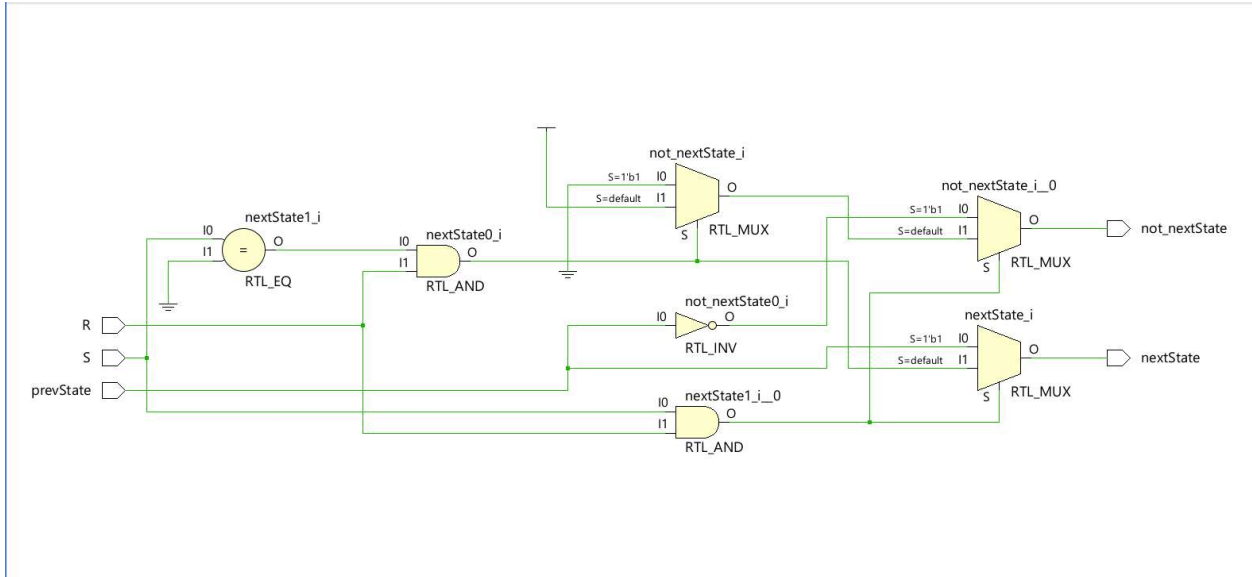

**Simulation:**

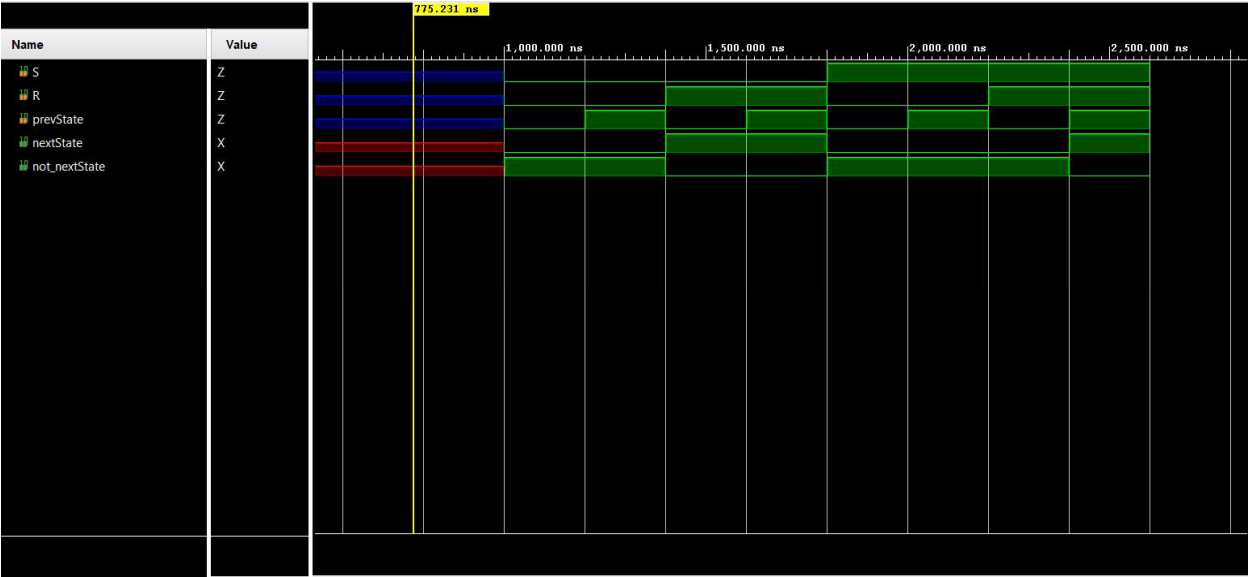

**Synthesis:**

 

**ASSIGNMENT**

**Question No. 1** Make one 3:1 MUX by using 2:1 MUX.

**Sol: Code:**

```
module MUX2_1(F,I0,I1,S);
    input I0,I1,S;
    output F;
    assign F = ((~S)&I0) | (S&I1);
endmodule
```

```
module MUX3_1(A0,A1,A2,S0,S1,Y);
    input A0,A1,A2,S0,S1;
    output Y;
    wire Y1;

    MUX2_1 m1(Y1,A0,A1,S0);
    MUX2_1 m2(Y,Y1,A2,S1);
endmodule
```


**Schematic and Boolean Expression:**

### Verilog Lab Assignment 3

① Make one 3:1 MUX by using 2:1 MUX


Soln:

2:1 MUX:

 


$$Y = \bar{S}A + SB$$

3:1 MUX:

 

$$F = A_0 \bar{S}_1 \bar{S}_0 + A_1 \bar{S}_1 S_0 + A_2 S_1 \bar{S}_0 + A_2 S_1 S_0$$

3:1 MUX using 2:1 MUXs:

 

S <sub>1</sub>	S <sub>0</sub>	F
0	0	A <sub>0</sub>
0	1	A <sub>1</sub>
1	0	A <sub>2</sub>
1	1	A <sub>2</sub>

**Question No. 2** Make 4 bit Carry Look Ahead (CLA) Adder circuit using HDL

**Sol: Code:**

```
module CLA(  
    input A0,B0,A1,B1,A2,B2,A3,B3,Cin,  
    output S0,S1,S2,S3,Cout  
);  
    wire P0,P1,P2,P3;  
    wire G0,G1,G2,G3;  
    wire C1,C2,C3;  
  
    assign P0 = A0^B0;  
    assign P1 = A1^B1;  
    assign P2 = A2^B2;  
    assign P3 = A3^B3;  
  
    assign G0 = A0&B0;  
    assign G1 = A1&B1;  
    assign G2 = A2&B2;  
    assign G3 = A3&B3;  
  
    assign C1 = G0|(P0&Cin);  
    assign C2 = G1|(P1&(G0|(P0&Cin)));  
    assign C3 = G2|(P2&(G1|(P1&(G0|(P0&Cin)))));  
    assign Cout = G3|(P3&(G2|(P2&(G1|(P1&(G0|(P0&Cin))))));  
  
    assign S0 = P0^Cin;  
    assign S1 = P1^C1;  
    assign S2 = P2^C2;  
    assign S3 = P3^C3;  
endmodule
```

**Boolean Expression and Diagram:**

## Carry look ahead adder:

$$S_i = P_i \oplus C_i$$

$$G_{i+1} = G_i + P_i C_i$$

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$C_0 = C_0$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$


$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$S_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

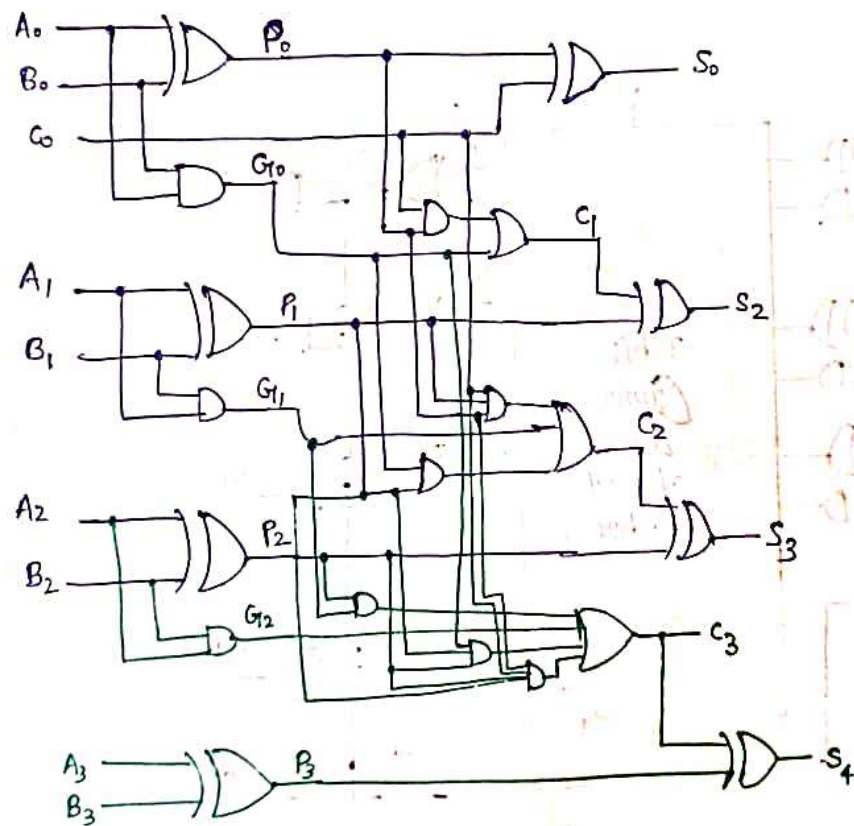

Schematic:



