

LAB 4 Pre-labwork


07-09-2023

SAURABH KUMAR
SC22B146

Realization of Logic Gates using Diodes and Transistor and study the performance metric


① Realizing two input AND, OR, NAND, NOR, NOT, using Diode and Transistor Logic (TTL).

OR Gate

 


A	B	V _{out}
0	0	0
0	1	1
1	0	1
1	1	1

AND Gate

 


A	B	V _{out}
0	0	0
0	1	0
1	0	0
1	1	1

TTL NAND Gate:

 


OR

 

A	B	Vout
0	0	1
0	1	1
1	0	1
1	1	0

✓


NOT Gate:

 

A	Vout
0	1
1	0

✓


NOR Gate:

 


A	B	Vout
0	0	1
0	1	0
1	0	0
1	1	0

Verified
Am

 ② Measuring the propagation delay of a logic using logic circuit.



verified

 

$$\begin{aligned}\text{Propagation delay of one OR Gate} &= \frac{\text{P.D. for entire IC}}{\text{No. of OR gates in an IC}} \\ &= \frac{24 \text{ ns}}{6} \\ &= 4 \text{ ns}\end{aligned}$$

③ 3 input majority logic function using 4 to 1 Mux.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

A	B	F
0	0	0
0	1	C
1	0	C
1	1	1

	$\bar{A}\bar{B}$ I_0	$\bar{A}B$ I_1	$A\bar{B}$ I_2	AB I_3
$\bar{C}(0)$	0	0	0	1
$C(1)$	0	1	1	1
F	0	C	C	1

