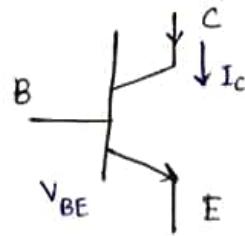


समिक्तीयवैद्युतक्रिया:

ANALOG ELECTRONIC
CIRCUITS


BIPOLAR JUNCTION TRANSISTOR (BJT)



↳ Two terminals control the other two.

Input characteristic:

↳ what happens at B-E decide C-current.

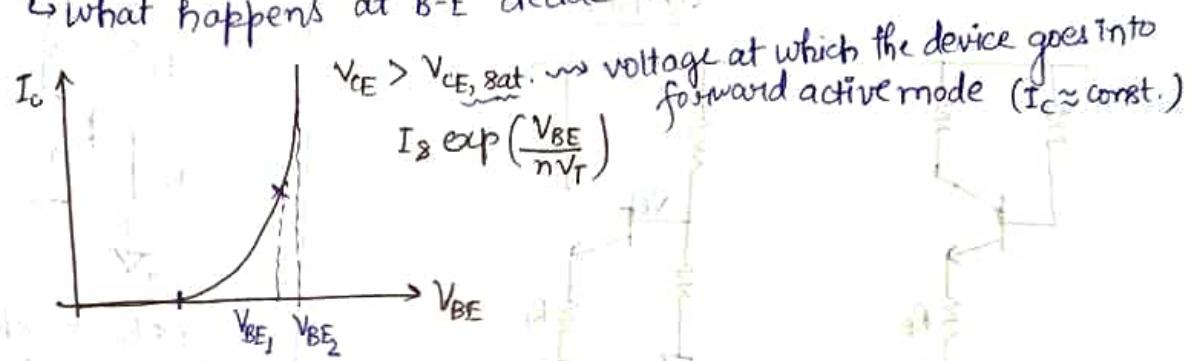


$$I_C = \beta I_B$$

$$\alpha I_E = I_C$$


$$I_E = (\beta + 1) I_B$$

$$I_E = I_B + I_C$$

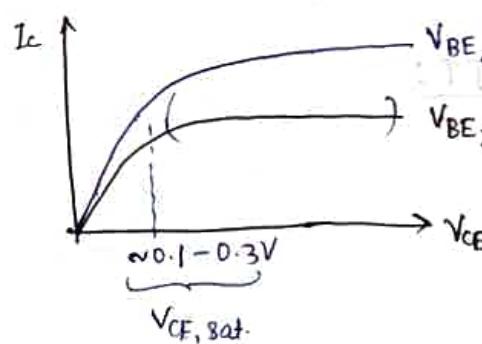


Setup for Input Chart:

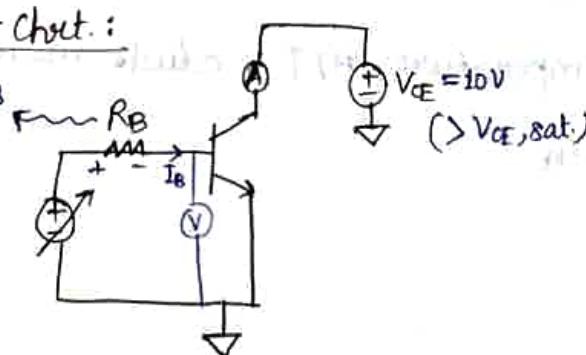
large value of R_B
(to limit I_B ;
otherwise
transistor may
burn)




Setup for Output Chart:

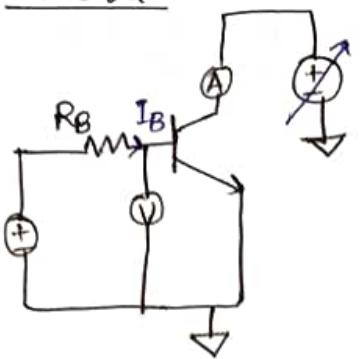

Fixed Bias

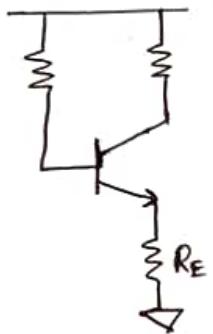

Voltage Divider Bias

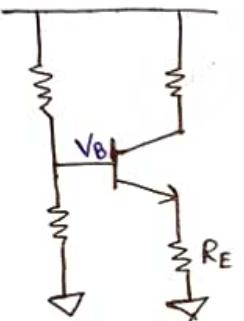


For same ΔV_{BE} , I_c changes by large amount,


$$V_B - V_{BE} - I_E R_E = 0$$

Introducing R_E decreases change in V_{BE} .

What if R_E is not there?

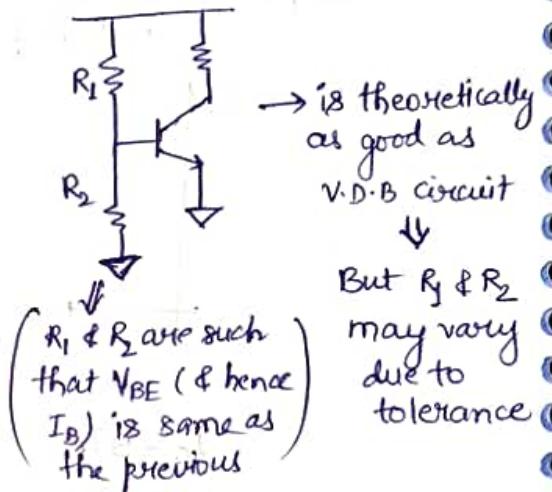

Temperature Dependence of BJT:

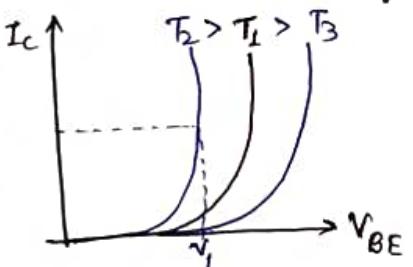

At higher temperature, BJT conducts more current (higher I_c) for same V_{BE} .

"Thermal runaway" Problem:

- Device goes into a vicious cycle where more heating produces more current and more current produces more heating (Joule's heating), which may damage the device.
- As temp. \uparrow , for const. current, $V_{BE} \downarrow$ by $2.1 \text{ mV}/^\circ\text{C}$,
or V_{BE} changes by $-2.1 \text{ mV}/^\circ\text{C}$.


Eg. for 1mA
@ 27°C

$$V_{BE} = 0.695 \text{ V}$$

If internally temp. changes to 37°C ,

$$V_{BE} = 0.695 - 2.1 \text{ mV}/^\circ\text{C} \times 10^\circ\text{C}$$

→ BJT is a temp. sensitive device.

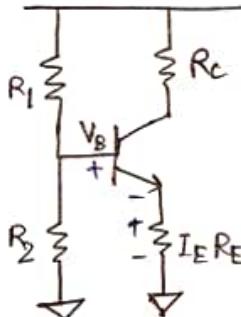

$T \uparrow \Rightarrow I_C, I_E \uparrow \Rightarrow I_E R_E \uparrow \Rightarrow V_{BE} \downarrow$
 (V_E)
 $T \downarrow \Rightarrow V_{BE} \uparrow$

→ Introducing R_E gives control over V_{BE} .

↳ "Negative feedback action"

↳ Thermal bias stabilization/stability



} all b/c of
 R_E

$$\rightarrow V_B - V_{BE} - I_E R_E = 0$$



for ΔT change in temp.,

$\rightarrow R_E \uparrow \rightarrow$ more stable current

I_E changes by $-2.1 \text{ mV} \times \Delta T$,
giving a ΔI_E .

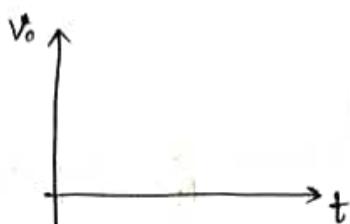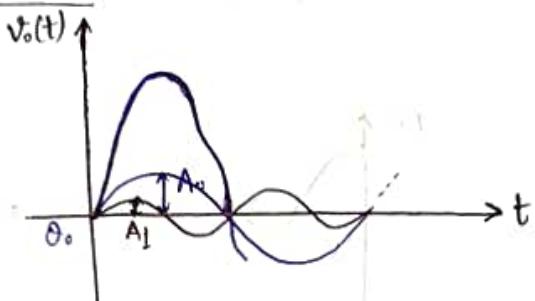FiltersSine waves:

$$v_o(t) = 8\sin(\omega_0 t) \quad \text{generalise} \rightarrow v_o(t) = 8\sin(\omega_0 t - \theta_0) + 8\sin(2\omega_0 t - \theta_1)$$

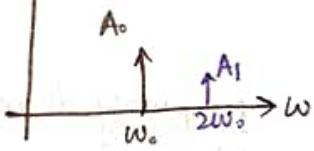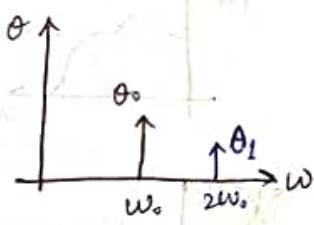w_o: frequency in rad/sec.w.r.t. w:~~versus~~

↳ Frequency domain Representation

Spectrum Analyser


VU meter: measures loudness

$$\rightarrow \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

In frequency domain representation, complex frequency content are


$$j\omega_0, -j\omega_0$$

$$e^{j\omega t} \rightarrow e^{\sigma t + j\omega t} = e^{\sigma t} e^{j\omega t} - e^{-\sigma t} e^{j\omega t}$$

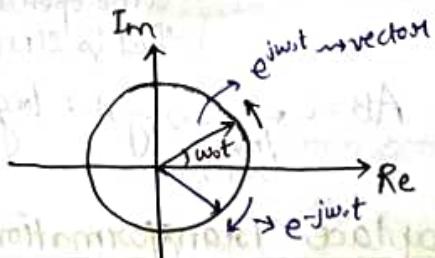
(Assume $\sigma=1$)

$$(A+jB)V \rightarrow (A+B)V$$

$$(A-B)V \rightarrow (A-B)V$$

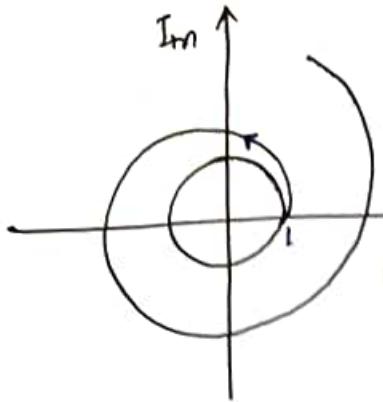



side view:

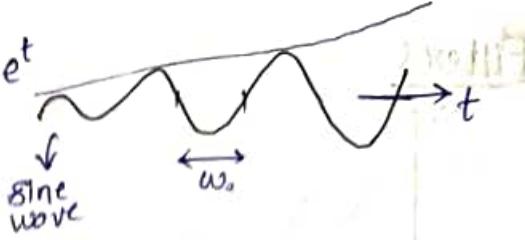

Top view: phase shift
cosine wave


sin & cos are projections of time-varying
 $e^{(\sigma + j\omega)t}$

for $\sigma = -1$

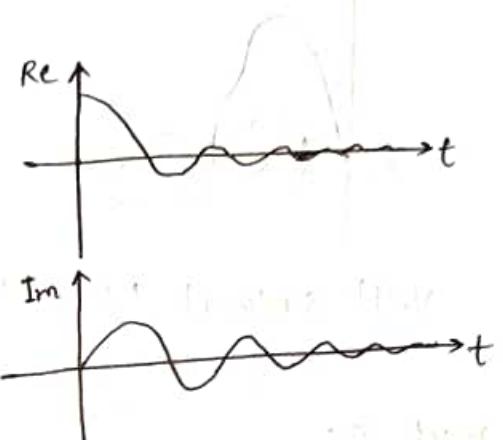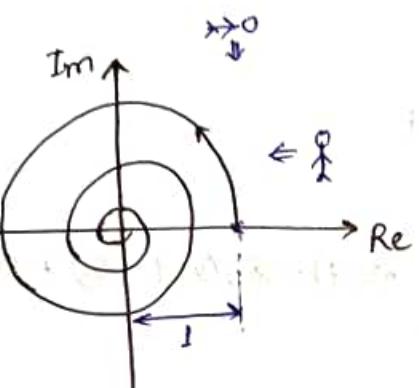

→ Frequency = $\sigma + j\omega$ (now onwards)
= 's': complex frequency

Fourier Series

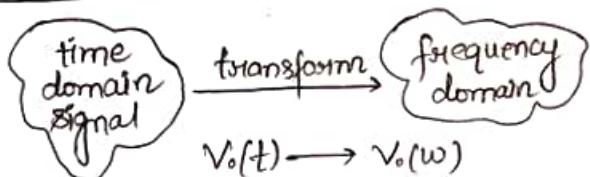

$$\# \log(AB)$$


$$A \xrightarrow{\text{transform}} \log(A)$$

$$B \xrightarrow{\text{transform}} \log(B)$$



↓ some operation
that is simpler

$$AB = C \xleftarrow[\text{inv. transform}]{\log A + \log B}$$


Laplace Transformation

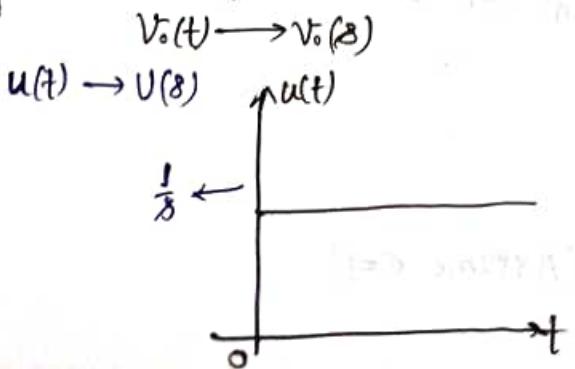

Frequency domain wave / fn:

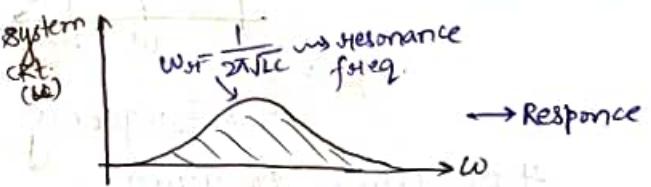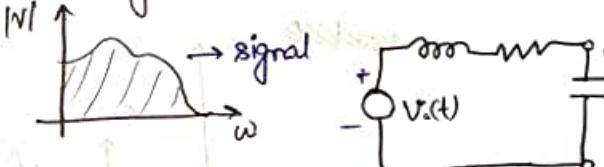
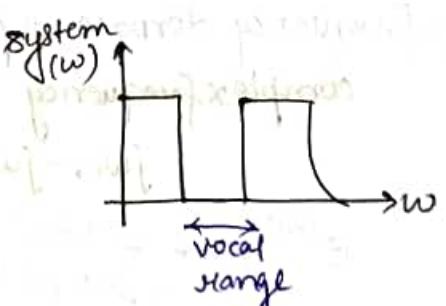
$$\text{out}(w) = \text{input}(w) \times \frac{\text{system}(w)}{\text{filter}}$$




MOSFETs

(Metal Oxide Semiconductor Field Effect Transistor)

→ Transistor → Bipolar Junction Transistor → Junction controls the current through the conductor
 → Field Effect Transistor → Electric field applied controls the transistor current (p-n)

MOSFET


or Cross-section of the device:

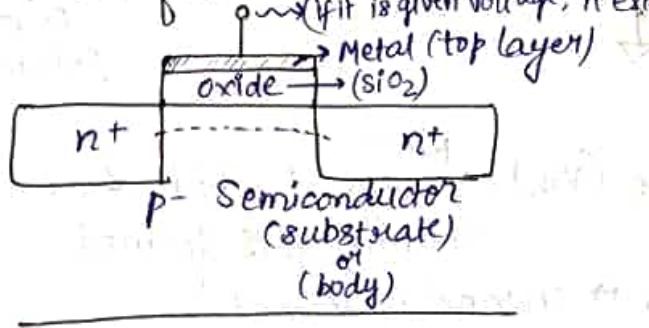


p⁻ → lightly doped
 p⁺ → highly doped

- N-MOS (p⁻ substrate) → Semiconductor is p-doped
- P-MOS (n⁻ substrate) → Semiconductor is n-doped

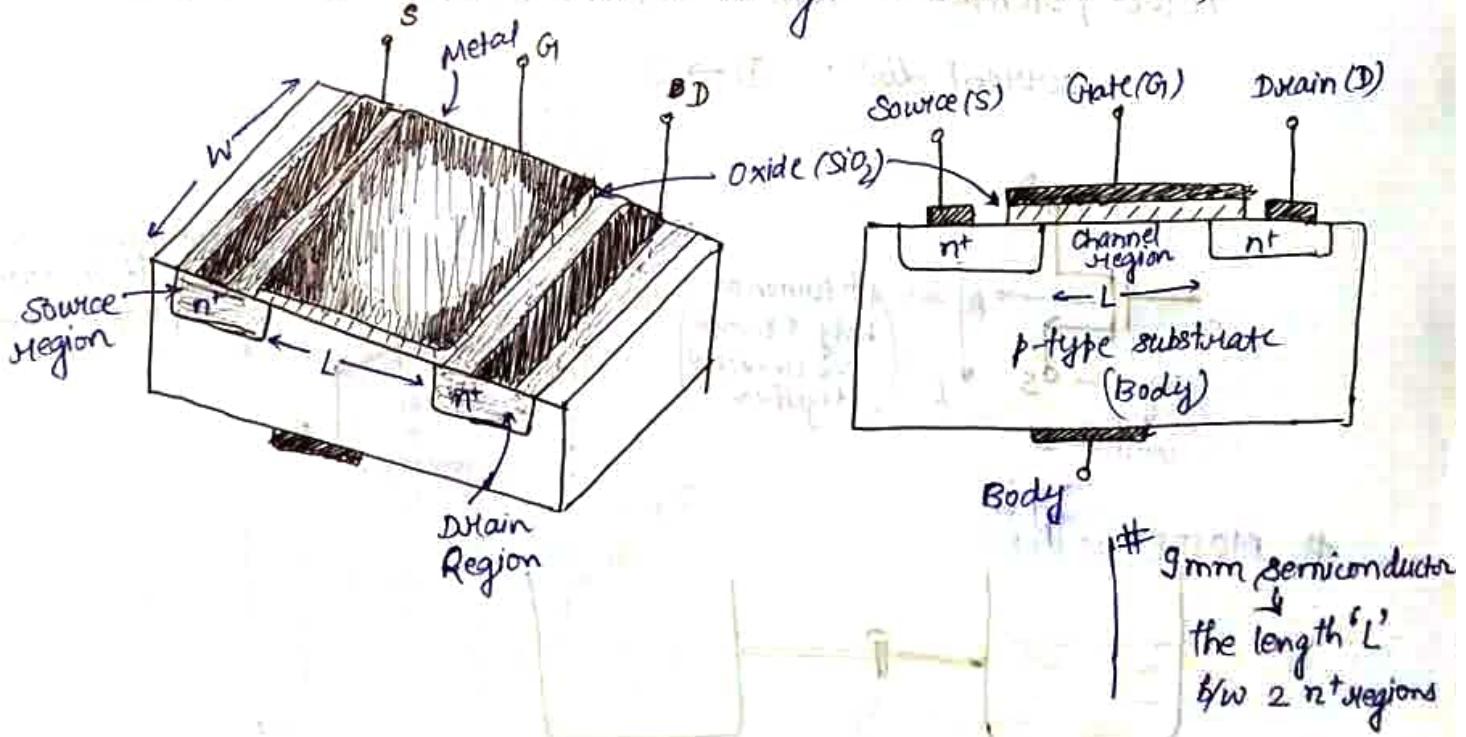↳ 4-terminal device (but we can get 3 terminals also).



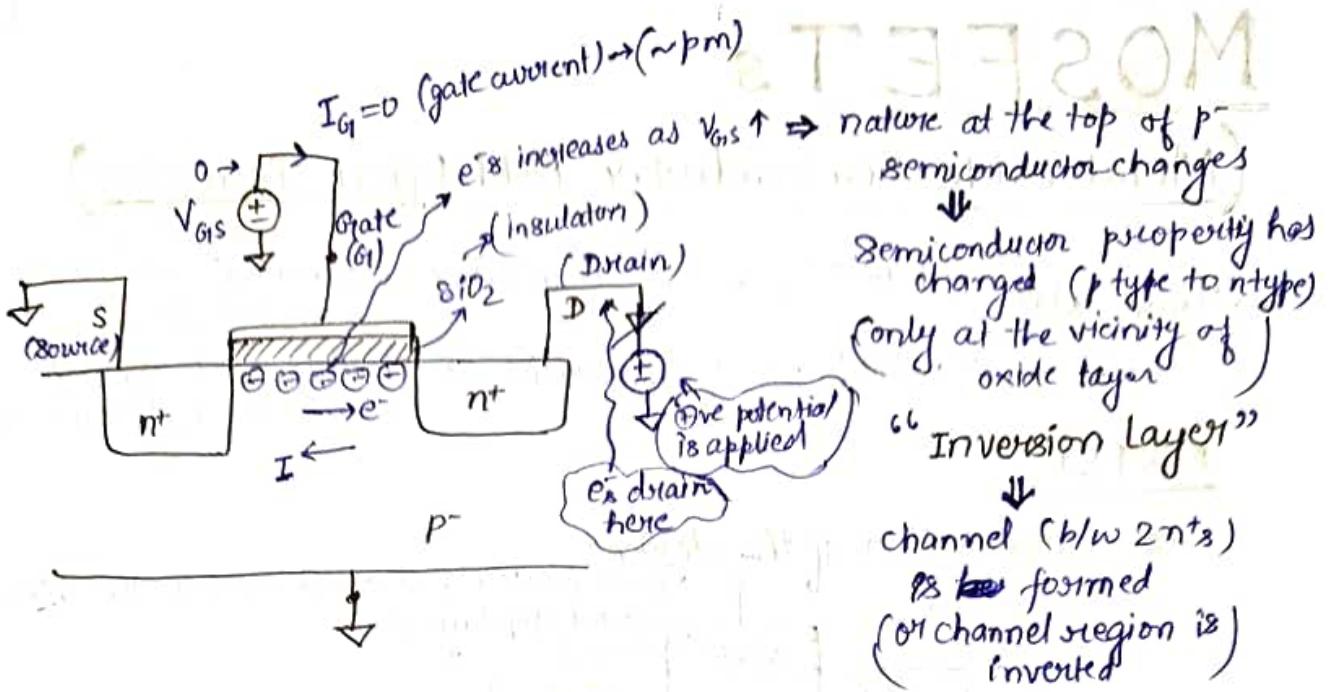$V_G - V_D \geq (V_T + 2V_{DS})$ $WV > 2V$
 All material values assumed $\rightarrow D = 2V + WV \leq 2V$





→ Threshold voltage (V_{Th}): Voltage at which $\frac{\text{Min}}{\text{m}}$ channel gets formed
 $V_{GS} \geq V_{Th} \Rightarrow$ channel is formed

→ MOSFET is a Symmetric device.


↳ can interchange D & S.

→ Higher potential \rightarrow Drain (attracts e^-)
 Lower potential \rightarrow Source (Source e^-)

current dirⁿ: $D \rightarrow S$

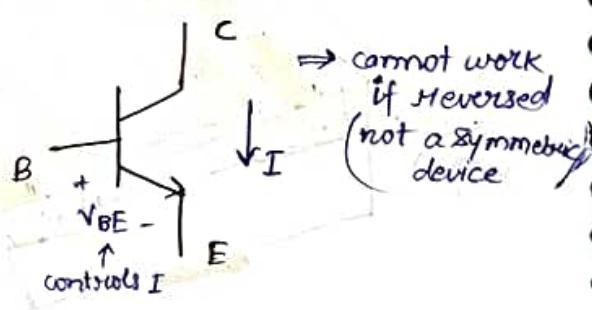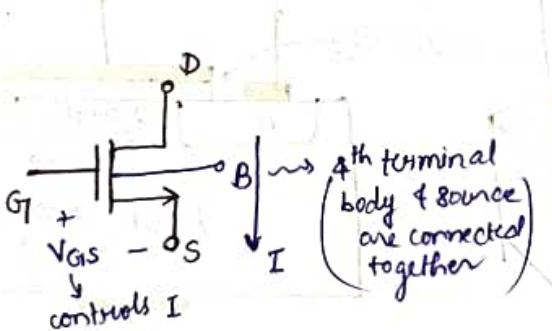

MOSFET is like:

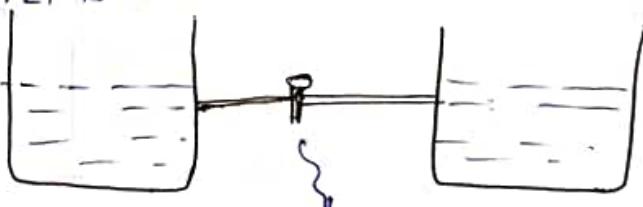


→ For current flow (water flow):

① $V_{GS} < V_{Th}$ (cut-off region) \rightarrow Tap off


② $V_{GS} \geq V_{Th}$ & $V_{DS} = 0$ \rightarrow ~~some~~ water levels in the two tanks.

→ CMOS - complementary MOS

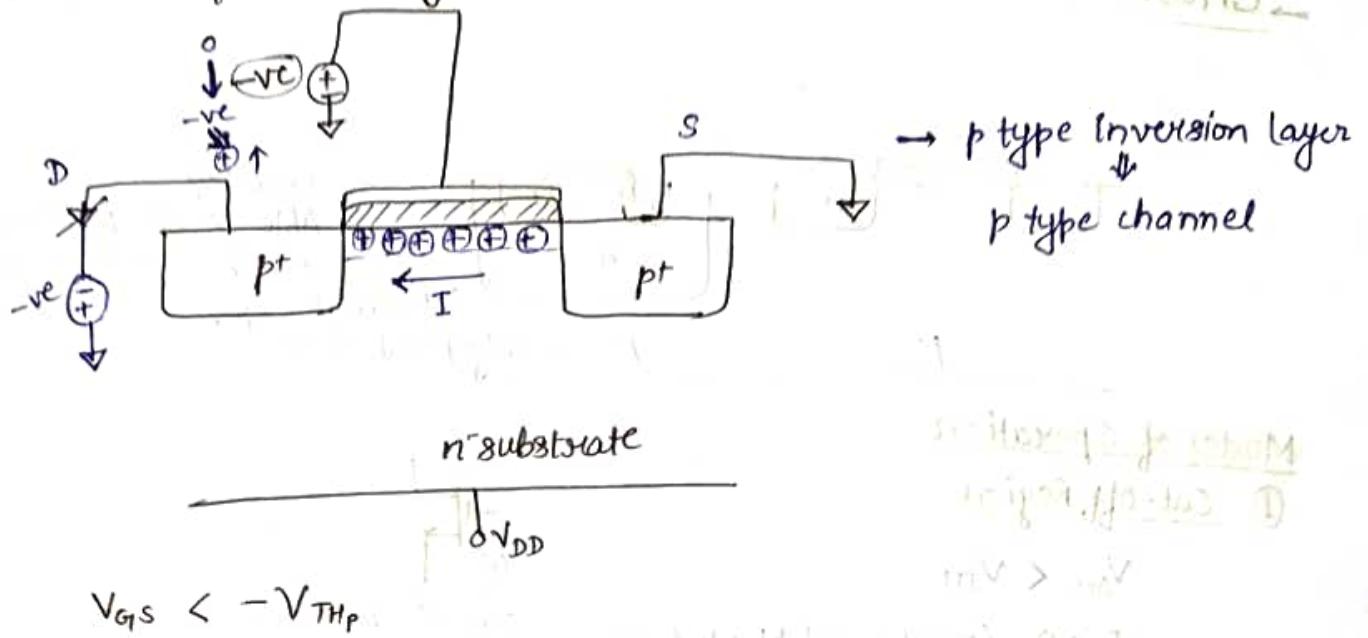

→ p type Inversion layer
↓
p type channel

But, we take +ve voltage.

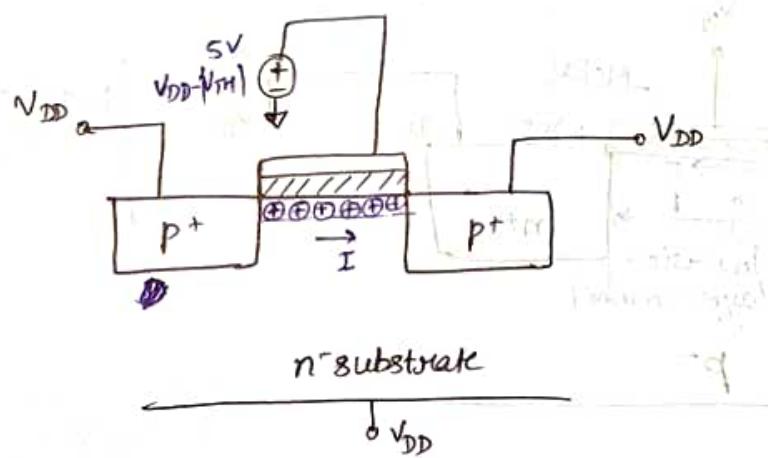

For 'holes' charge carriers:
higher potential → S
lower potential → D

NMOS

$$V_{GS} > V_{TH}$$

PMOS


$$V_{SG} > |V_{TH}|$$

$$S_{SD} > 0$$

$$0 = \alpha V_S + \beta V_D \leq \gamma V_D \quad \text{②}$$

$$\alpha = \alpha I \leq$$

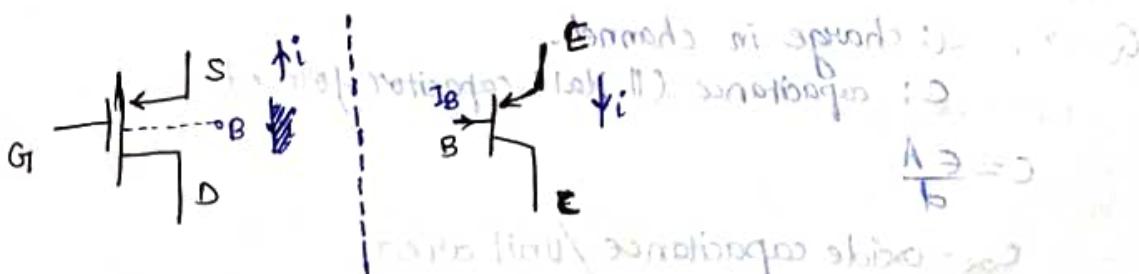
$$\gamma V_D \leq \gamma V \quad \text{③} \quad S < \gamma D \quad \text{④}$$



$$V_{DD} = V_{TH} - 2\alpha V = V$$

$$(V_{TH} - 2\alpha V) \cdot \alpha \cdot 2 = V_0 = \beta$$

→ CMOS:

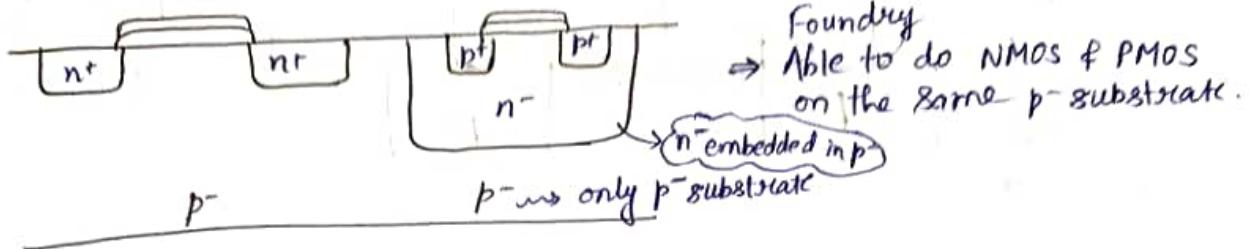


Modes of Operation


① Cut-off Region

$$V_{GS} < V_{TH}$$
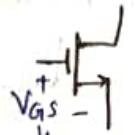
$$I_D = 0 \text{ (no channel b/w D & S)}$$



controls I_D & I_S .

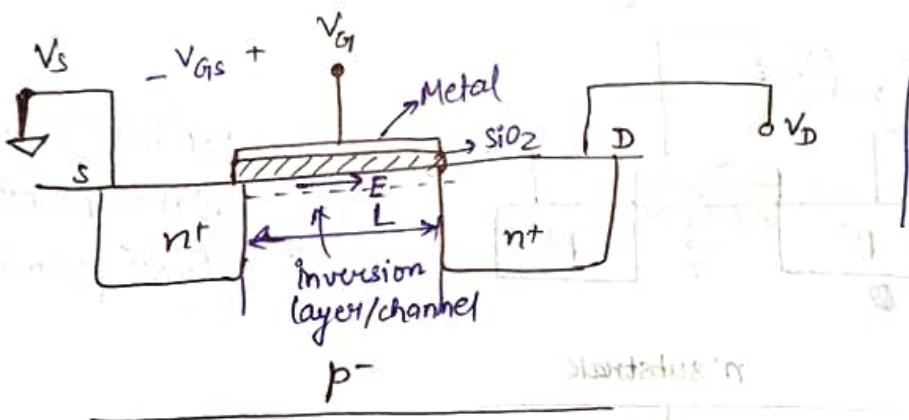

$$\textcircled{2} \quad V_{GS} \geq V_{TH} \text{ & } V_{DS} = 0$$

$$\Rightarrow I_D = 0$$

$$\textcircled{3} \quad V_{DS} > 0 \text{ & } V_{GS} \geq V_{TH}$$

$$I_D = ?$$

$Q = CV$, Q: charge in channel.

C: capacitance (ll. plate capacitor formed)

$$C = \frac{\epsilon A}{d}$$

C_{ox} = oxide capacitance / unit area

$$\therefore C = C_{ox} \cdot WL$$

↳ Total capacitance

$$V = V_{GS} - V_{TH} = V_{OV} : \text{over drive voltage}$$

$$\therefore Q = CV = C_{ox} \cdot WL(V_{GS} - V_{TH})$$

Drain current:

$$I_D = \text{charge / unit length} \times \text{velocity of electron}$$

$$= \frac{Q}{L} \times \mu_n E$$

$$E_{DS} = \frac{V}{L} = \frac{V_{DS}}{L}$$

$\left| \begin{array}{l} \text{drift velocity} = \mu_n E \\ (\nu_{ds}) \\ \text{mobility} \\ \text{electric field} \end{array} \right.$

Electric field in channel
(B/W D & S)


$$\therefore I_D = C_{ox} \cdot W (V_{GS} - V_{TH}) \mu_n \frac{V_{DS}}{2}$$

$$\Rightarrow \boxed{I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH}) V_{DS}} \rightarrow \text{only } V_{GS} \text{ & } V_{DS} \text{ can be controlled}$$

$$-①$$

$$I_D \propto (V_{GS} - V_{TH}) = \nu_{GS}$$

$$I_D \propto V_{DS}$$

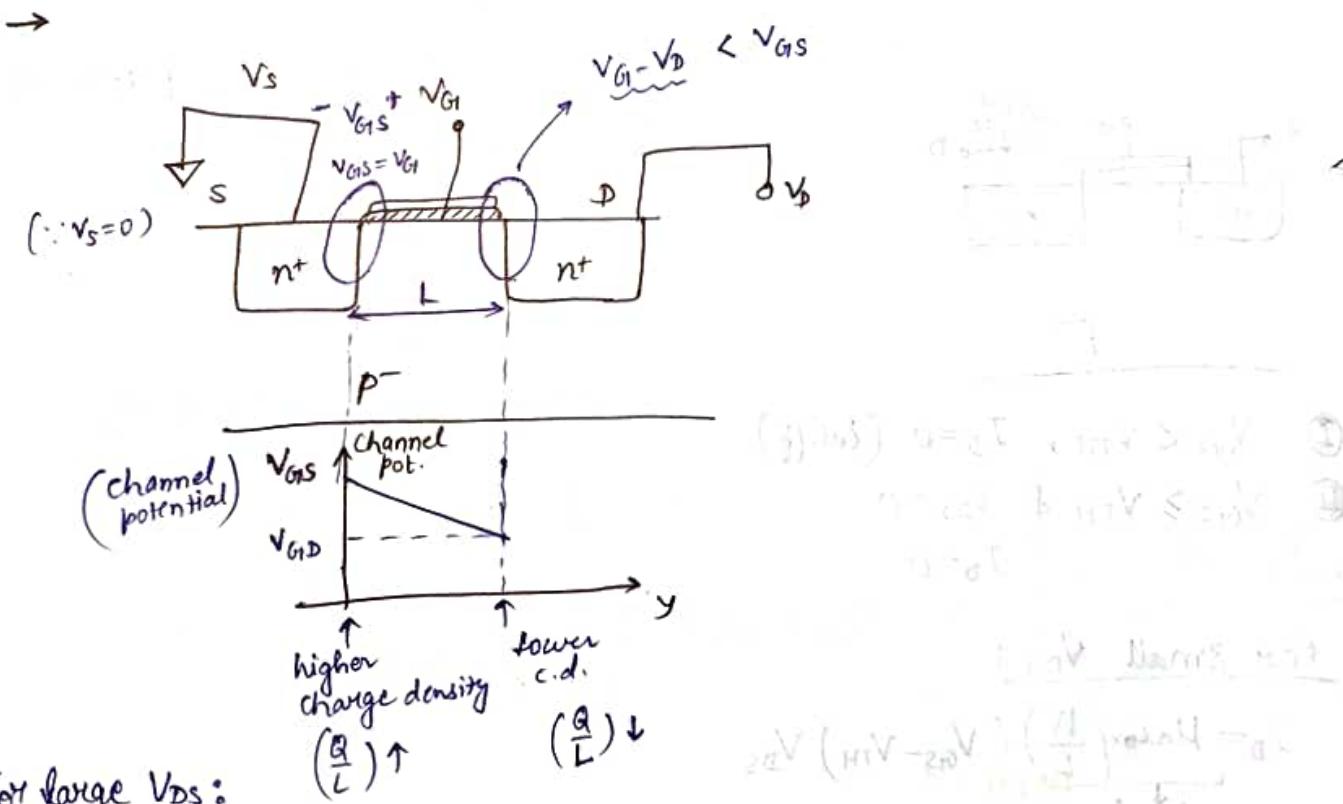

For large V_{DS} :

Average potential $= \frac{(V_{GS} - V_{TH}) + (V_{GD} - V_{TH})}{2}$, where $V_{GD} = V_{GS} - V_{DS}$

$(V_{TH, \text{eff}})$

$$= \frac{(V_{GS} - V_{TH}) + (V_{GS} - V_{DS} - V_{TH})}{2}$$

$$\therefore I_D = C_{ox} \cdot W \left(\frac{(V_{GS} - V_{TH}) + (V_{GS} - V_{DS} - V_{TH})}{2} \right) \mu_n \frac{V_{DS}}{L}$$

$$= \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_{TH}) - \frac{V_{DS}}{2} \right] V_{DS}$$

$$\Rightarrow \boxed{I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]} \quad -②$$

If we keep increasing V_D :

$$V_{GD} \leq V_{TH}$$


$$\Rightarrow V_{GS} - V_{DS} \leq V_{TH}$$

$$\Rightarrow [V_{DS} \geq V_{GS} - V_{TH} = V_{ov}] \rightarrow \text{channel gets pinched off}$$

For $V_{DS} = (V_{GS} - V_{TH})$,

$$I_D = \mu n C_{ox} \left(\frac{W}{L} \right) [(V_{GS} - V_{TH})(V_{GS} - V_{TH}) - \frac{1}{2} (V_{GS} - V_{TH})^2]$$
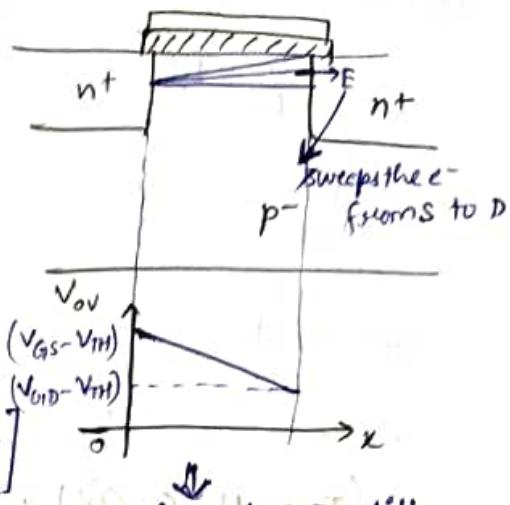
$$\Rightarrow I_D = \frac{1}{2} \mu n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 \quad -③$$




Channel & E still exist.

Similar to BC Reverse biased in ~~an~~ BJT
(current flows despite of reverse bias)

11-08-2023

→

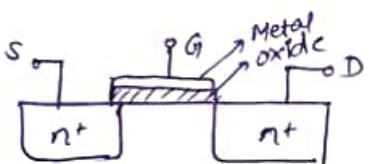

P-

I $V_{GS} < V_{TH}$, $I_D = 0$ (cutoff)

II $V_{GS} \geq V_{TH}$ & $V_{DS} = 0$

$$I_D = 0$$

For small V_{DS} :

$$I_D = \mu n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH}) V_{DS}$$

$$I_D = K_n (V_{GS} - V_{TH}) V_{DS} \quad -①$$


For little larger V_{DS} :

$$I_D = K_n \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad -②$$

For $V_{DS} \geq V_{GS} - V_{TH} = V_{ov}$,

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TH})^2 \quad -③$$

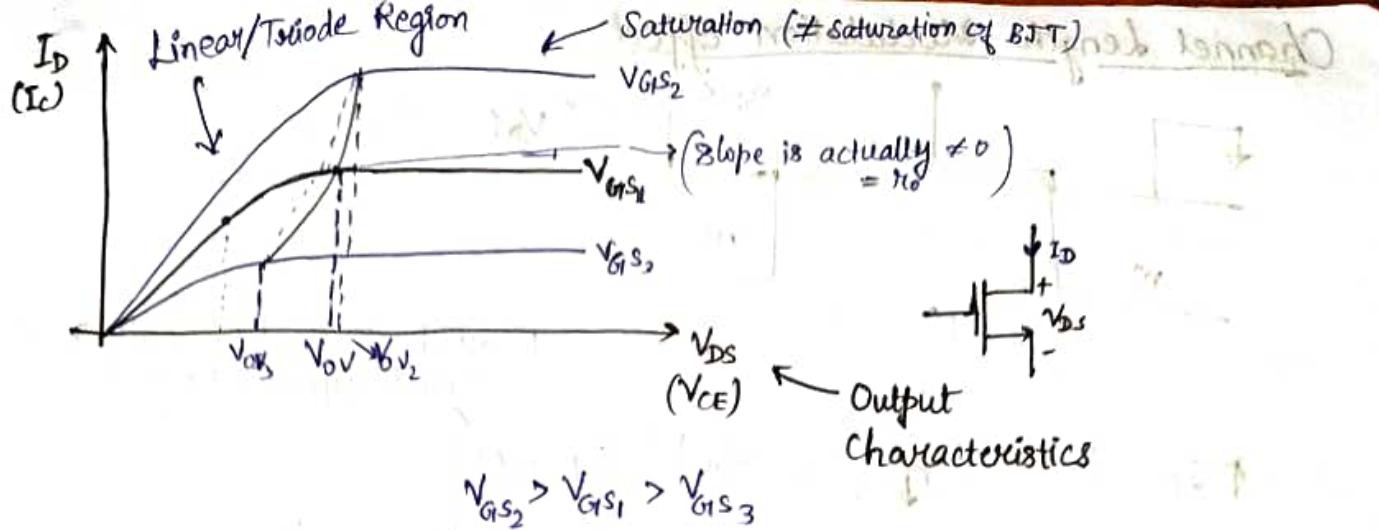
$$\text{Q} = \left[\int_{20V}^{40V} \frac{1}{2} - 20V (40V - 20V) \right] \left(\frac{W}{L} \right) nA = 40 \text{ nA}$$



→ V_{DS} : well-defined point (unlike in BJT) where the device moves from linear to saturation region or vice versa.

Input Characteristics:

<u>BJT</u>	<u>MOSFET</u>
E	S
B	G
C	D

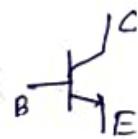


Differences b/w BJT & MOSFET:


Ⓐ $I_G = 0 \text{ vs } I_B \neq 0$

(As gate doesn't get current due to oxide dielectric)

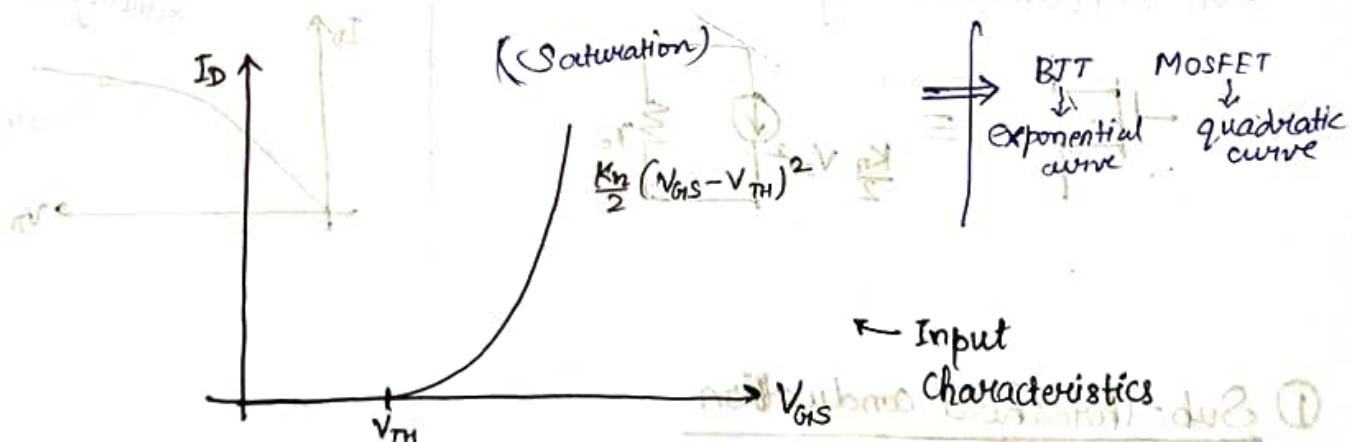
Ⓑ $I_D = I_s \text{ vs } I_E = I_C + I_B$



→ There are no ideal current source.

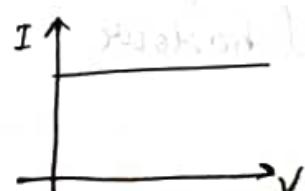

Channel Length Modulation Effect

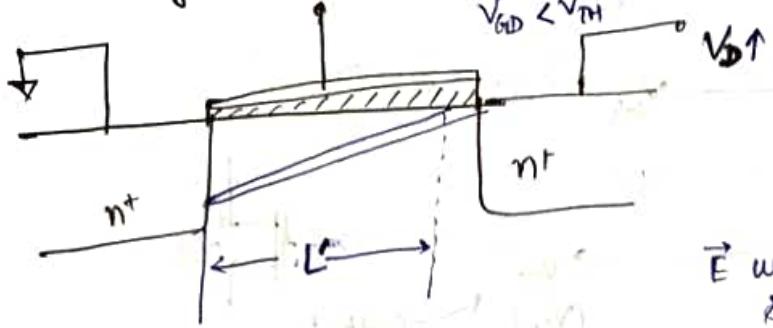

E will be present but only in the small effective region

$$\uparrow I_D = \frac{K_n \cdot C_{ox}}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 \quad (\because L \rightarrow L')$$

→ On increasing V_{GS} , effective channel length decreases.

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}), \quad \lambda : \text{channel length modulation coefficient}$$

\hookrightarrow constant channel length

$$\left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS}=\text{const.}} = \lambda \cdot \frac{K_n}{2} (V_{GS} - V_{TH})^2$$


\hookrightarrow conductance $\approx \lambda I_D$

$$g_{ds} \approx \lambda I_D \quad \rightarrow \text{Output conductance}$$

$$r_o = \frac{1}{g_{ds}} \approx \frac{1}{\lambda I_D} \quad \rightarrow \text{Output impedance}$$

In the saturation region,

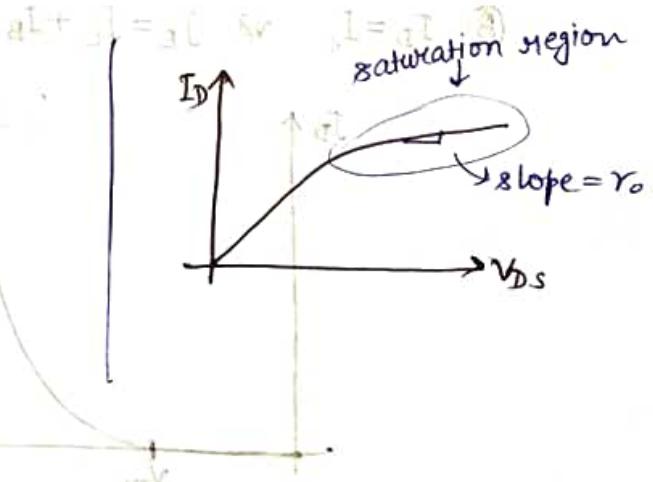
$$-I_D = \frac{K_n}{2} V_{GS}^2 \quad \text{saturation region}$$




① Sub-threshold conduction

↪ Small I_D exists for $V_{GS} < V_{TH}$.

↪ Exponential behaviour.

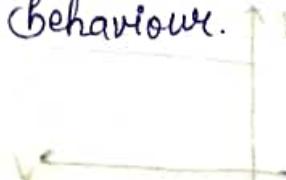

② Body-effect

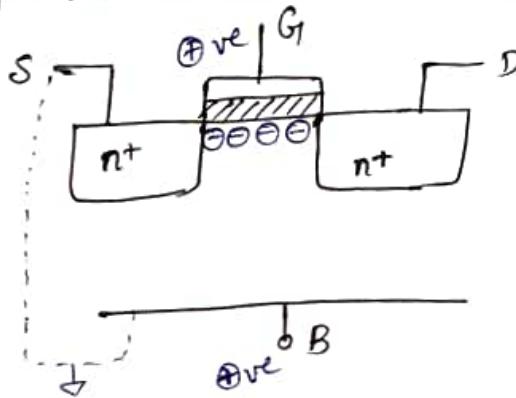

→ Normally, S & B are connected together.
body is grounded.

→ Using body voltage, threshold voltage can be altered.
↳ also called "Back Gate".

20M9



Current of 20M9 is

$$|V_{GS}| \leq 0.2V$$

$$|V_{GS}| - 0.2V = 0.8V \quad (\text{threshold}) = 0.2V$$


$$[0.8V - 0.2V \cdot (0.8V - 0.2V)] \left(\frac{dI}{dV} \right) \approx 0.1A = 0.2$$

$|V_{GS}| - 0.2V \leq 0.2V$ (threshold)

$$[(0.8V - 0.2V) \left(\frac{dI}{dV} \right) \frac{0.2V}{0.2V}] = 0.2$$

$$\left(\frac{dI}{dV} \right) \cdot 0.2V = 0.2$$

$$0.2V \cdot \frac{dI}{dV} = 0.2$$

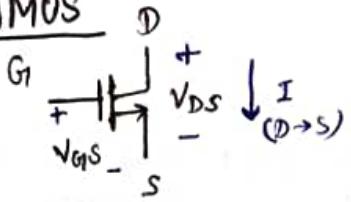NMOS

$$V_{GS} \geq V_{THN}$$


Tsüode:

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{THN}) V_{DS}$$

$$= \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_{THN}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\text{Saturation: } V_{DS} \geq V_{GS} - V_{TH}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{THN})^2 = \frac{k_n}{2} (V_{GS} - V_{THN})^2$$

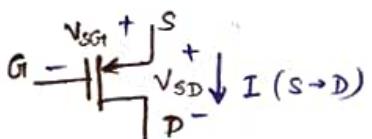PMOS

For PMOS to turn ON,

$$V_{SG} > |V_{THP}|$$

$$I_D = \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{SG} - |V_{THP}|) V_{SD}$$

$$(V_{GS} \xrightarrow{\text{flip}} V_{SG})$$

$$I_D = \mu_p C_{ox} \left(\frac{W}{L} \right) \left[(V_{SG} - |V_{THP}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$$

$$\text{Saturation region: } V_{SD} \geq V_{SG} - |V_{THP}|$$

hole mobility
< e⁻ mobility

$$I_D = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L} \right) (V_{SG} - |V_{THP}|)^2$$


$$k_n = \mu_n C_{ox} \left(\frac{W}{L} \right)$$

or

$$k'_n = \mu_n C_{ox}$$

Enhancement MOSFET

→ Normal MOSFETs.

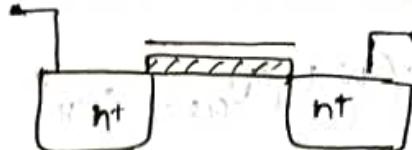



Depletion type MOSFET

→ channel is already embedded.

• Even for $V_{GS} = 0$, channel is already formed.


• To turn off the device,

$$V_{GS} \rightarrow 0\text{Ve.}$$

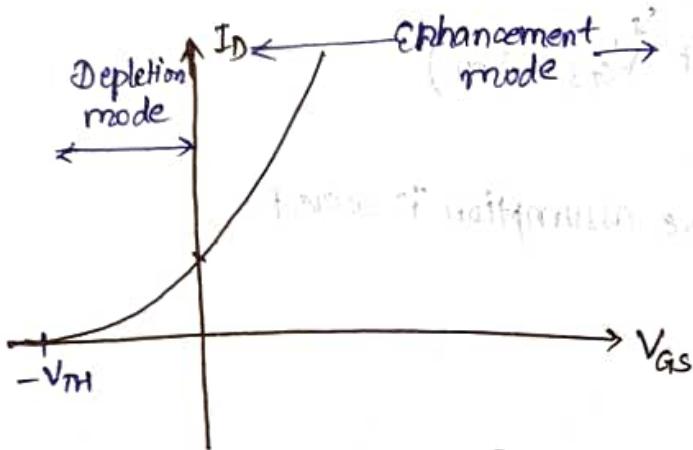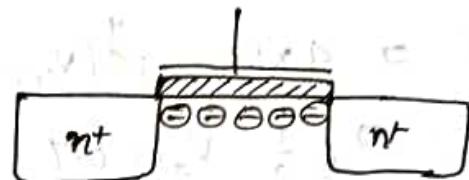

(find R_D & R_S)

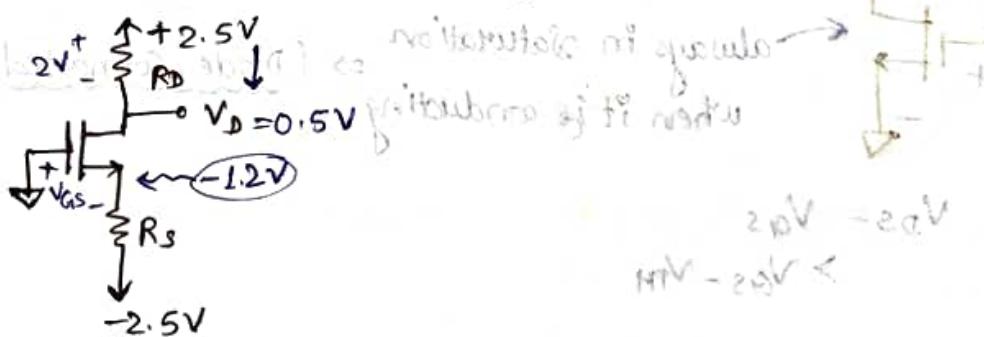Q1 Design the circuit such that you get $I_D = 0.4\text{mA}$, $V_D = +0.5\text{V}$, $V_{TH} = 0.7\text{V}$, $\mu_n C_{ox} = 100 \text{ MA/V}^2$, $W = 32 \mu\text{m}$, $L = 1 \mu\text{m}$, $\lambda = 0$.



Soln: Voltage drop across $R_D = 2.5 - 0.5 = 2\text{V}$

$$R_D I_D = 2\text{V}$$

$$\Rightarrow R_D = \frac{2}{0.4\text{mA}} = 5\text{K}\Omega$$



"resistor between source"

Using $I_D = \frac{MnCox}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$ we form for saturation region:

$$\Rightarrow 0.4 \times 10^{-3} = \frac{100 \times 10^{-6}}{2} \left(\frac{32 \times 10^{-6}}{1 \times 10^{-6}} \right) (V_{GS} - 0.7)^2$$

then check if
 $V_S \geq (V_{GS} - V_{TH})$.

$$\Rightarrow 4 \times 2 = 32 (V_{GS} - 0.7)^2$$

$$\Rightarrow \pm \frac{1}{2} = V_{GS} - 0.7$$

$$\Rightarrow V_{GS} = 0.5 + 0.7 \quad \text{or} \quad V_{GS} = -0.5 + 0.7$$

$$\Rightarrow V_{GS} = 1.2 \text{ V} \quad \text{or} \quad V_{GS} = 0.2 \text{ V}$$

$$\Rightarrow V_{GS} = 1.2 \text{ V} \quad (\text{Neglect } V_{GS} < V_{TH})$$


Here, $V_{DS} = 1.7 \text{ V}$

$$V_{GS} - V_{TH} = 0.5 \quad \left\{ \text{hence, the assumption is correct.} \right.$$

$$\text{Now, } V_G = 0 \Rightarrow V_S = -1.2 \text{ V}$$


$$\frac{V_S + 0.2}{R_S} = I_S = I_D$$
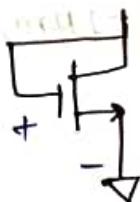
$$\Rightarrow R_S = \frac{1.2 + 0.2}{0.4 \text{ m}} = \frac{1.4}{0.4 \text{ m}} = 3.5 \text{ k}\Omega$$



→ always in saturation when it is conducting \Rightarrow (Diode-Connected Transistor)

$$V_{DS} = V_{GS} \\ > V_{GS} - V_{TH}$$

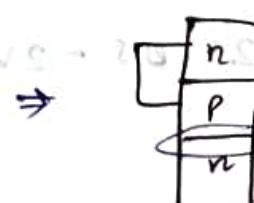


(Diode)

"Diode Connected Transistor"

Q) Find R such that $V_D = 0.7V$.

$$MnCox = 0.4 \text{ m}A/V^2$$
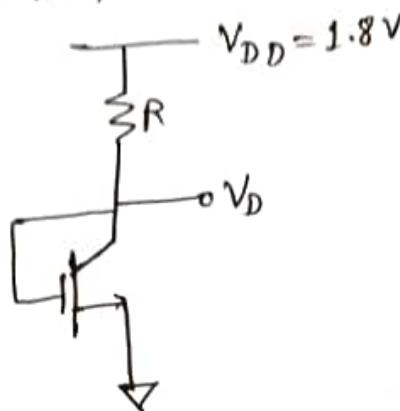
$$\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}, V_{TH} = 0.5 \text{ V}$$



$$\text{Soln: } I_D = \frac{V_{DD} - V_D}{R}$$

$$= \frac{1.8 - 0.7}{R} = \frac{1.1}{R}$$

$$\text{and, } I_D = \frac{MnCox(\frac{W}{L})}{2} (V_{DS} - V_{TH})^2$$

$$\Rightarrow \frac{1.1}{R} = \frac{0.4 \times 10^{-3}}{2} \left(\frac{0.72}{0.18} \right) (0.7 - 0.5)^2$$

$$\Rightarrow \frac{1.1}{R} = 8 \times 10^{-3} (0.04)$$

$$\Rightarrow \frac{1.1}{R} = 3.2 \times 10^{-5} \quad (0.04)^2 = 0.0016 \quad (0.0016) = 0.0016$$


$$\Rightarrow R = \frac{1.1 \times 10^5}{8 \times 4}$$

$$\Rightarrow R = 34.375 \text{ k}\Omega$$

Q1 Determine all node voltages & branch current.

$$V_{TN} = 1V (= V_{TH})$$

$$k_n = 1 \text{ mA/V}^2$$

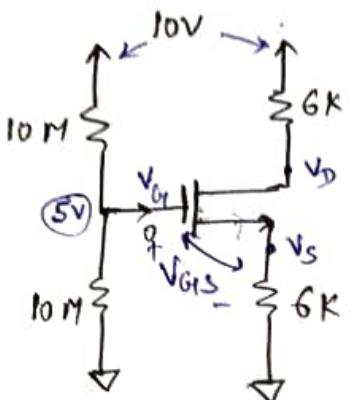

Soln: $V_G = 5V$

$$\text{Using } I_D = \frac{k_n}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$

$$\Rightarrow I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2$$

$$= \frac{1 \times 10^{-3}}{2} (5 - V_S - 1)^2$$

$$\begin{cases} I_D = 0.5 \text{ mA} \\ 5 - I_D R_S - V_{GS} = 0 \end{cases}$$

$$\text{Using } 5 - V_{GS} - I_D R_S = 0$$

$$\Rightarrow 5 = (5 - V_S) + \frac{10^3}{2} (4 - V_S)^2 \cdot 6 \times 10^3$$

$$\Rightarrow V_S = \frac{(16 + V_S^2 - 8V_S)}{2} \cdot 6 \times 10^3$$

$$\Rightarrow 3V_S^2 - 25V_S + 48 = 0$$


$$\Rightarrow V_S = 3, \frac{16}{3}$$

$$\text{As } V_{GS} > V_{TH}, V_S \neq \frac{16}{3}$$

$$\therefore V_S = 3V$$

$$\Rightarrow I_D = \frac{1}{2} (4 - 3)^2 \text{ mA} = 0.5 \text{ mA}$$
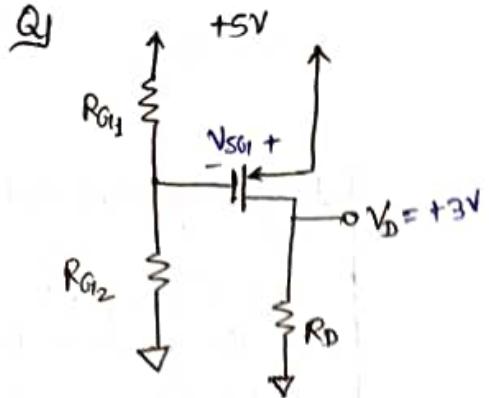
$$V_S = 10 - (6 \times 0.5 \text{ mA}) = 10 - 3 = 7V$$



$$\begin{aligned} I_D &= 0.5 \text{ mA} \\ V_D &= +3 \text{ V} \\ V_{TP} &= -1 \text{ V} \\ k'_p \left(\frac{W}{L}\right) &= 1 \text{ mA/V}^2 \end{aligned}$$

① What is the value of R_D and V_G ?

② What is the largest value of R_D that can be used while keeping the transistor in saturation region?

Soln: ① $R_D = \frac{3V - 0}{0.5 \text{ mA}} = 6 \text{ k}\Omega$.

and,

$$\text{Using } I_D = \frac{k'_p}{2} \left(\frac{W}{L}\right) (V_{SG1} - |V_{TP}|)^2$$

$$\Rightarrow \frac{1}{2} \times 10^{-3} = \frac{1}{2} \times 10^{-3} (V_{SG1} - 1)^2$$

$$\Rightarrow V_{SG1} - 1 = \pm 1$$

$$\Rightarrow V_{SG1} = 2 \quad (\because V_{SG1} \neq 0)$$

and, $V_{SG1} = V_{DD} - V_G$

$$\Rightarrow V_G = 5 - 2 \quad (\because V_{DD} = 5 \text{ V})$$

supply voltage

② For saturation region,

$$V_{DSAT} = V_{SD} \geq V_{SG1} - |V_{TP}|$$

$$5 - V_D \geq 5 - 3 - 1$$

$$\Rightarrow 5 - V_D \geq 1$$



$$\Rightarrow V_D \leq 4$$

$$\therefore R_D = \frac{V_D - 0}{I_D} \quad (\text{since } V_D \leq 4)$$


$$\leq \frac{4}{0.5 \text{ mA}} = 8 \text{ k}\Omega$$

\Rightarrow Largest possible $R_D = 8 \text{ k}\Omega$.
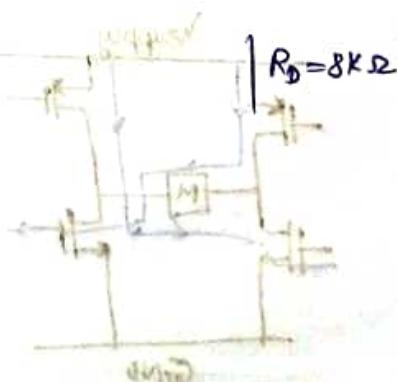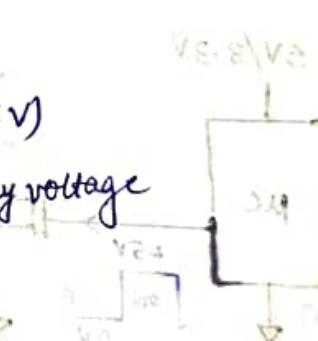
$$\begin{cases} R_D = 6 \text{ k}\Omega \\ V_G = 3 \text{ V} \end{cases}$$



Large Signal Model of MOSFET

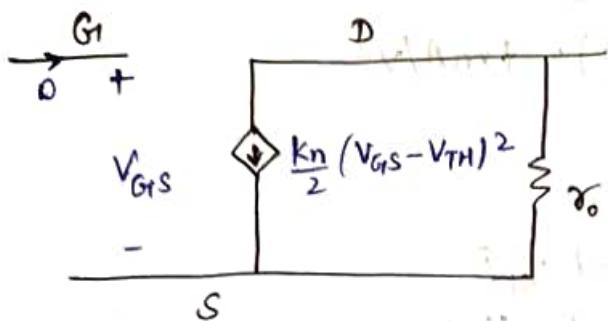


Large Signal Model

↳ can be used for both AC & DC

Small Signal Model

↳ can be only be used for ac


→ MOSFET as Switch:

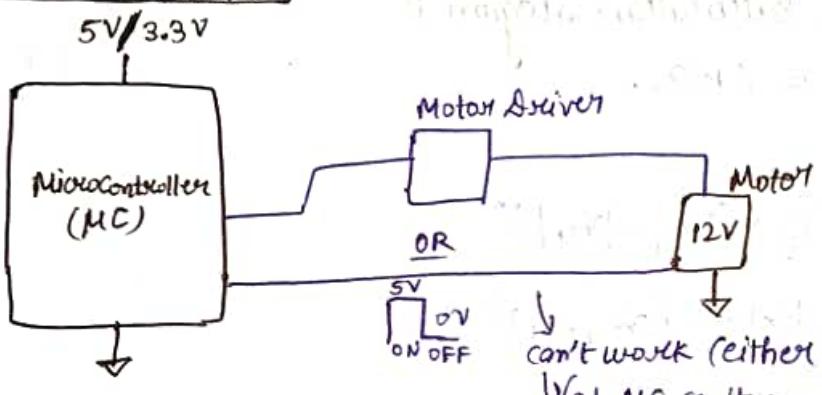


BJT:



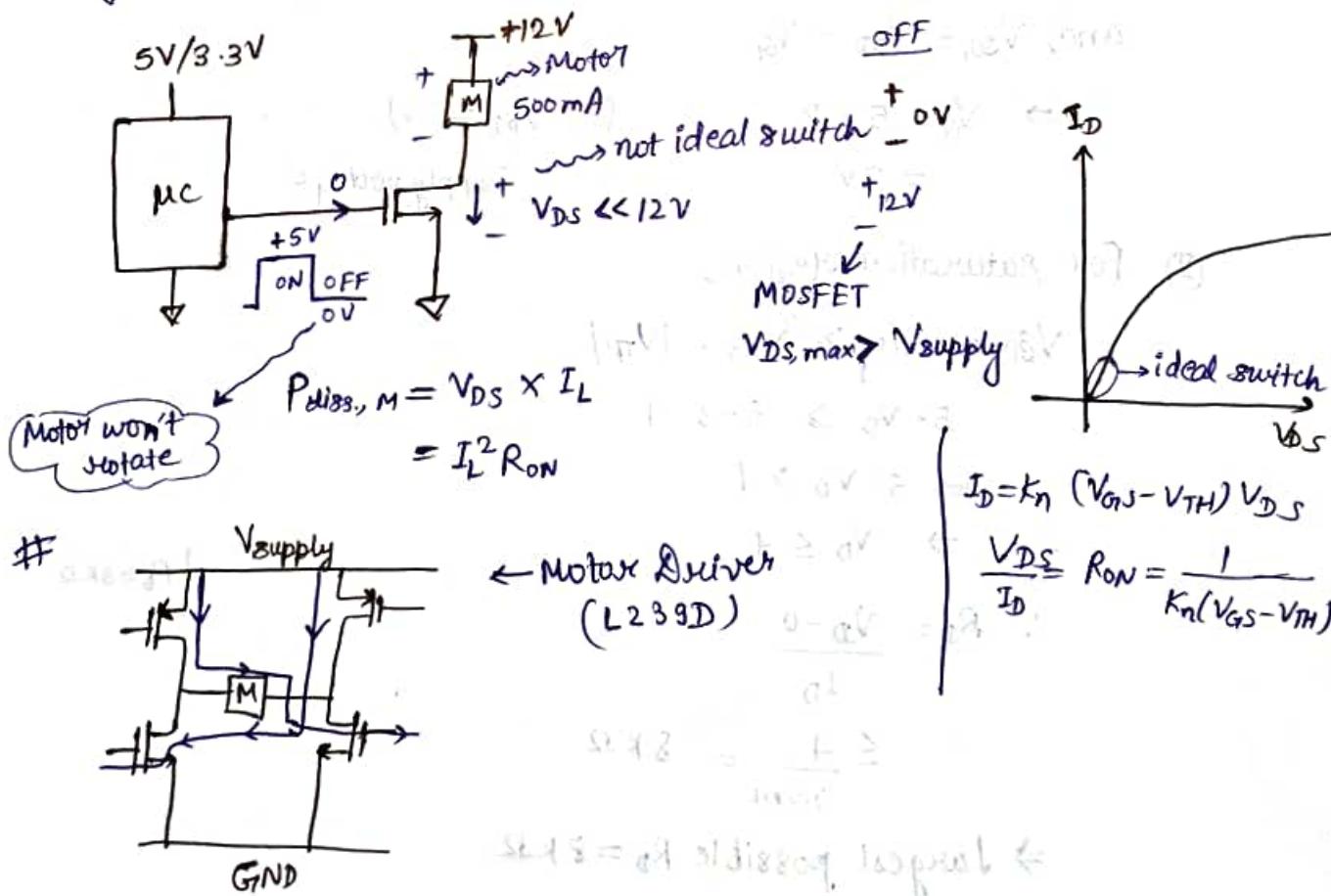We can make it work even without a motor driver.




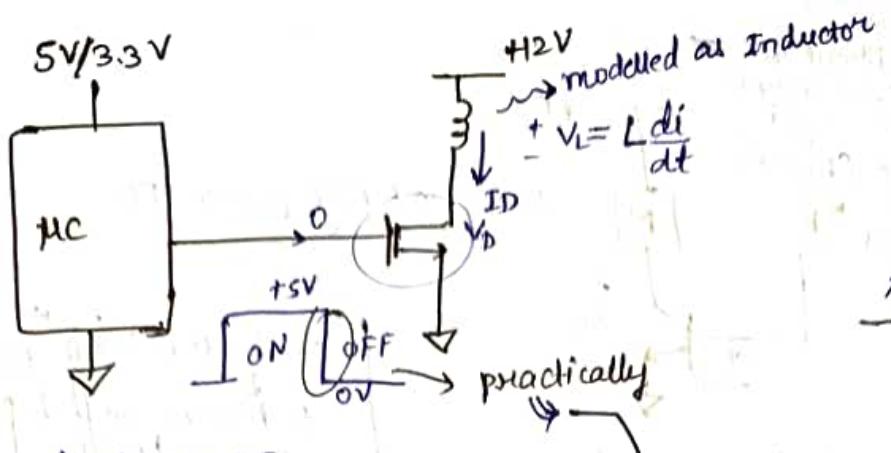

At turn OFF


$\frac{di}{dt} \rightarrow$ large +ve value \rightarrow device may damage

To protect the device,

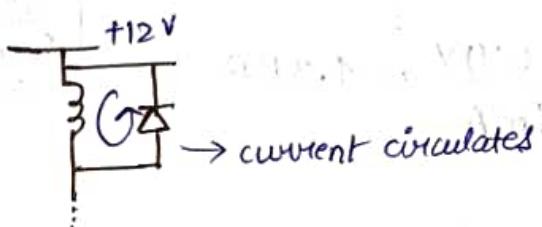

22-08-2023

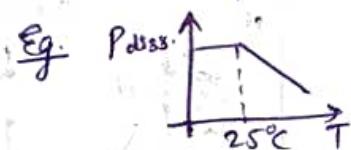
→ With $T \uparrow$, power dissipation derates (\downarrow) (above ambient temp., T_A).



→ Thermal Resistance:

Junction $T = \text{Ambient } T + \text{Thermal resistance}$
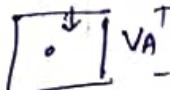
$$\text{Eg. } T_A = 30^\circ\text{C} \quad (\text{Room } T)$$





$$P_{\text{dissipated}} = 10 \text{ mW}$$

$$\text{if } R_{\text{QJA}} = 150 \text{ }^\circ\text{C/W},$$


$$\text{Junction } T = 30^\circ\text{C} + 0.15^\circ\text{C} \\ = 30.15^\circ\text{C.}$$

DATASHEET
= BS170
MOSFET

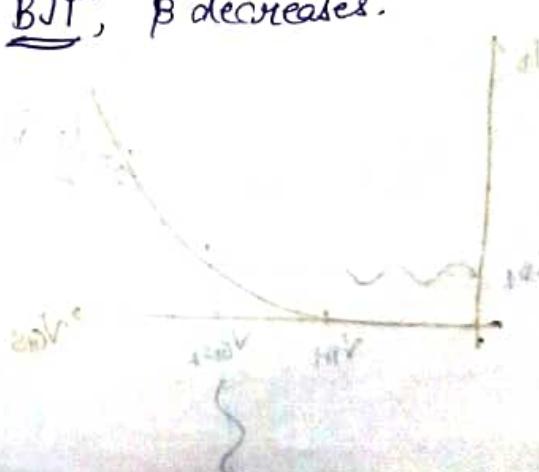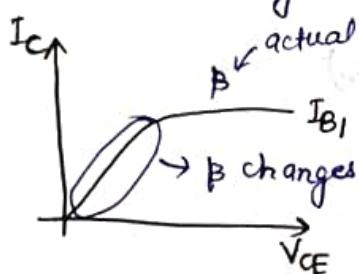→ In the saturation region of BJT, β decreases.



BJT as Switch

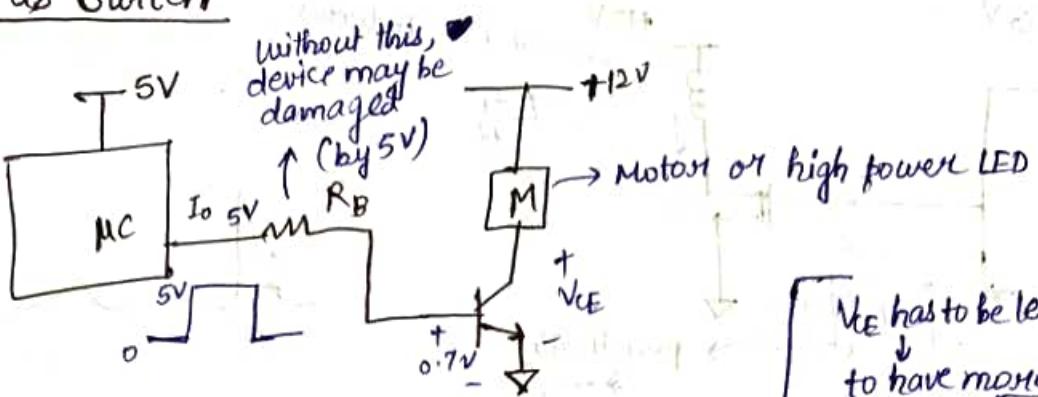

If $I_c = 50\text{mA}$ (say) has to be passed


$$I_B \approx 1\text{mA}$$

$$R_B = ?$$

$$R_B = \frac{(5 - 0.7)\text{V}}{1\text{mA}} = 4.3\text{ k}\Omega$$

V_E has to be less
↓ to have more
voltage for M
↓ for power ↓

V_E

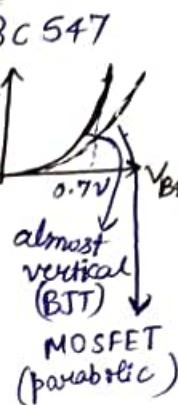

- If $V_{in} = 0\text{V}$, $V_{BE} = 0$; cutoff region (turns OFF)

Small Signal Operation



Condition (approximation): $|V_{ac}| \ll V_B$
 \downarrow dc voltage


$$V_{in} = V_{BE1} + V_{ac}$$

$$\frac{\partial I_c}{\partial V_{BE}} = g_m$$

transconductance

$$I_c = I_{c1} + g_m V_{ac}$$

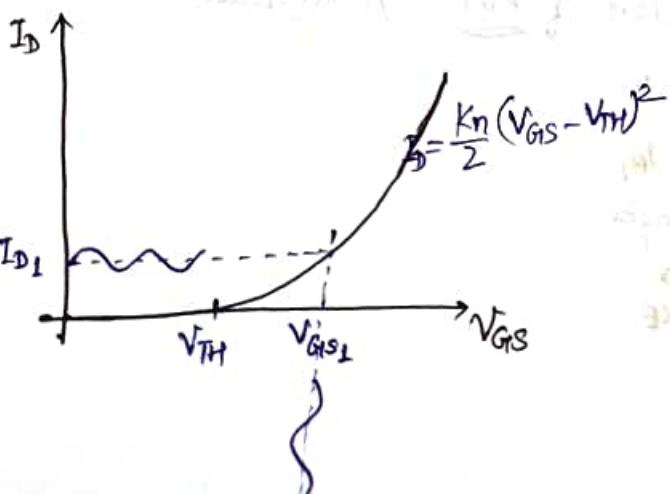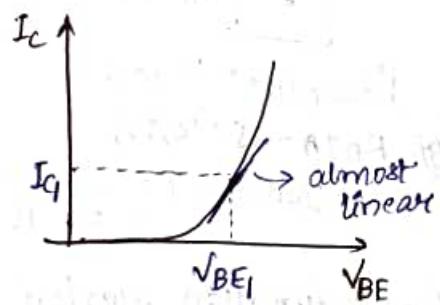

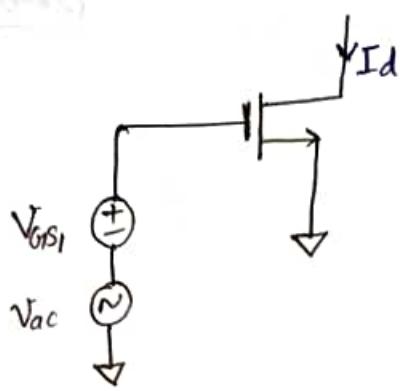

$$V_m = V_{GS} + Vac$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = K_n (V_{GS} - V_{TH})$$

$$I_d = I_{D1} + g_m Vac$$

total current
(ac+dc)

$$[I_D = \frac{K_n}{2} (V_{GS} - V_{TH})^2]$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2 I_D}{(V_{GS} - V_{TH})} = \sqrt{2 I_D K_n}$$


$$\text{As, } g_m = K_n (V_{GS} - V_{TH})$$

$$= \frac{2 I_D}{(V_{GS} - V_{TH})^2} (V_{GS} - V_{TH})$$

$$= \frac{2 I_D}{(V_{GS} - V_{TH})}$$

$$\therefore g_m = K_n \cdot \sqrt{\frac{2 I_D}{K_n}} = \sqrt{2 I_D K_n}$$

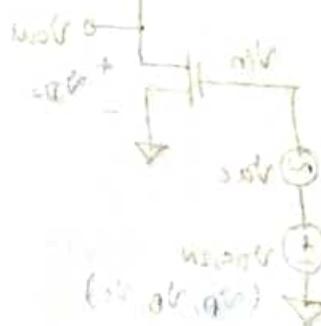using this eqn, we can find the output voltage
as it is the product of current & resistance
which is $I_D \cdot R_D$



$$2V_{GS} - 2V_D = 2V_D$$

$$2(V_{GS} - V_D) + 2V_D = 2V_D$$


$$2(V_{GS} - V_D) \frac{R_D}{R_D + R_F} = 2V_D$$

$$2(V_{GS} - V_D) \frac{R_D}{R_D + R_F} R_F = 2V_D$$

$$2(V_{GS} - V_D) R_F = 2V_D$$


Common Source Amplifier

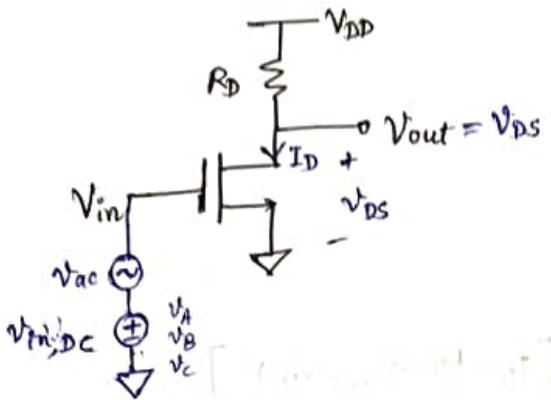↪ Similar to Common Emitter Amplifier of BJT




$$V_{out} = V_{DD} - I_D R_D$$

Voltage Transfer Curve

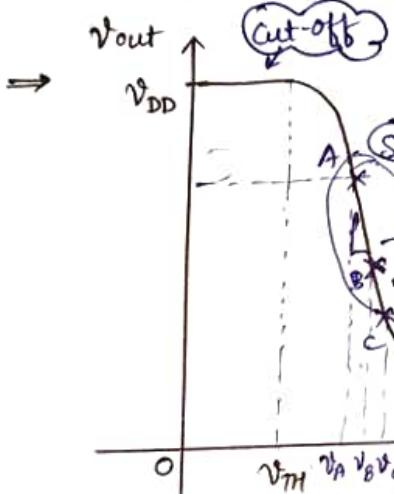

- $V_{in} = 0 \Rightarrow I_D = 0$
↪ cutoff region
 $\Rightarrow V_{out} = V_{DD}$
- For saturation
 $V_{DS} \geq V_{GS} - V_{TH}$
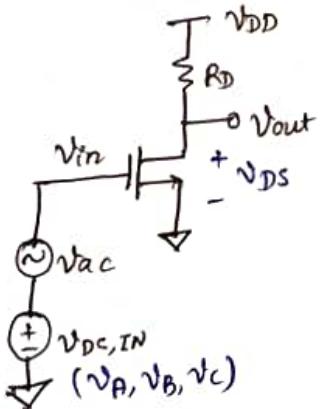
$$\downarrow V_{DS} \geq V_{GS} \uparrow - V_{TH}$$



- Since V_A is near V_{DD} , on high ac wave input, output will be clipped b/c V_{out} cannot be $> V_{DD}$.
- At V_c , since the output cycle is near Triode region & hence that would not be amplified much due to less slope.
- So, the best biasing point is V_B , i.e., middle point V_{DD} and GND ($\frac{V_{DD}}{2}$) for amplification.

$$V_{out} = V_{DD} - I_D R_D$$


$$= V_{DD} - (I_{DC} + g_m V_{ac}) R_D$$

$$\text{where } I_{DC} = \frac{k_n}{2} (V_{DC,IN} - V_{TH})^2$$

$$g_m = k_n (V_{DC,IN} - V_{TH})$$

$$V_{out,DC} = V_{DD} - I_{DC} R_D$$

CE

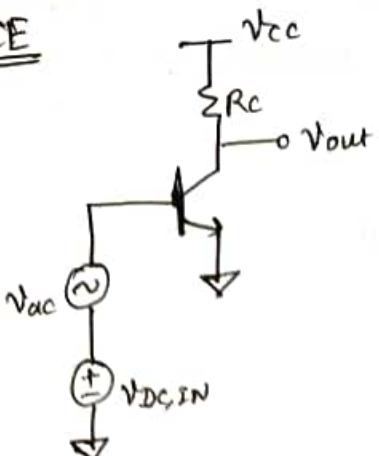

$$V_{out} = V_{cc} - I_c R_c$$

$$= V_{cc} - (I_{DC} + g_m V_{ac}) R_c$$

where,


$$I_{DC} = I_s \exp\left(\frac{V_{DC,IN}}{V_T}\right) \quad \text{and} \quad g_m = \frac{I_c}{V_T}$$

CS: Gain = $-g_m R_D = -g_m \frac{V_{ac} R_D}{V_{ac}}$

$$\left(\text{CS.gain} = \frac{V_{out,dc}}{V_{in}} = -\frac{g_m \cdot V_{ac} \cdot R_D}{V_{ac}} \right)$$

CE: Gain = $-g_m R_c$

Small Signal Model of MOSFET

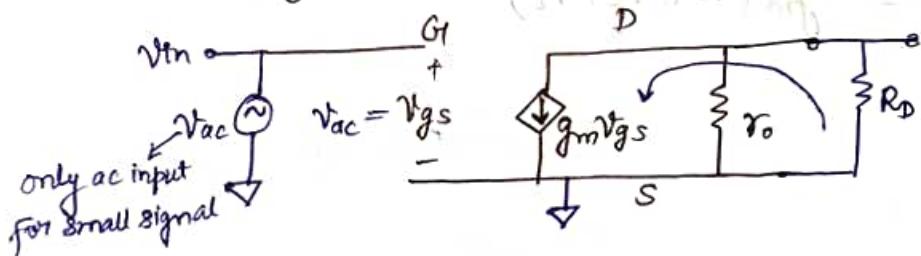


• DC voltages are AC grounds.

$$V_{out} = -g_m V_{gs} (r_o \parallel R_D)$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_D) \approx -g_m R_D \quad (\text{for } R_D \ll r_o)$$


CE:

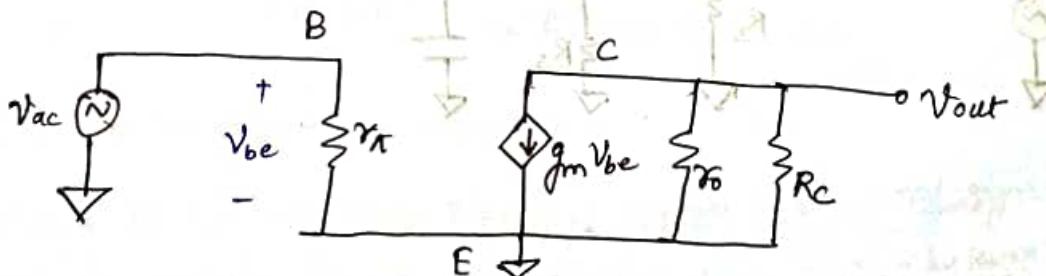


$$V_{out} = -g_m V_{be} (r_o \parallel R_c)$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_c) \approx -g_m R_c$$

Common Emitter Amplifier

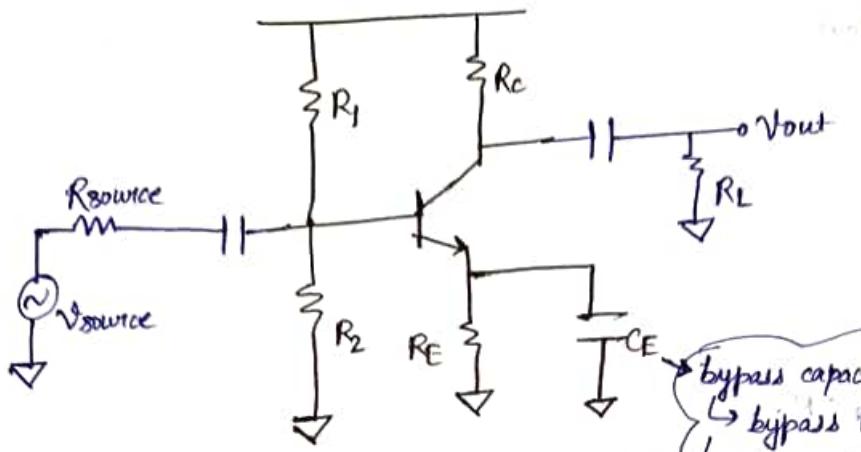

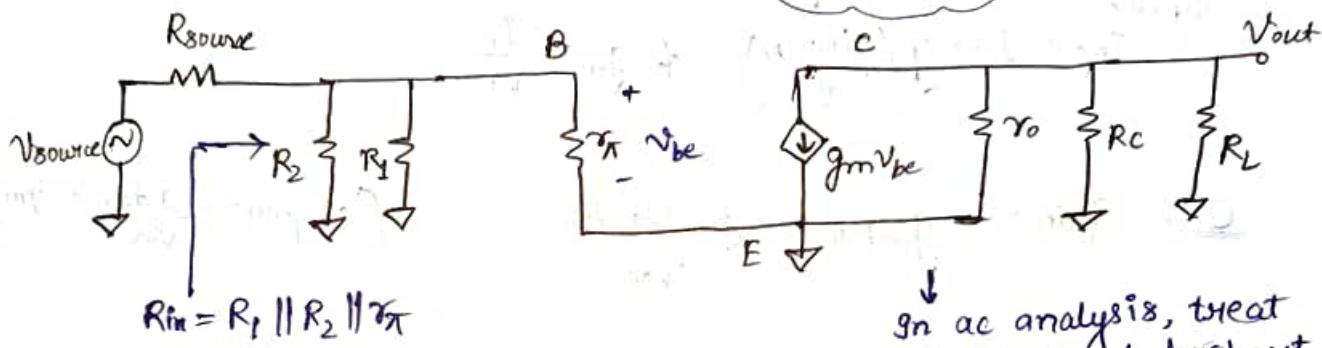bypass capacitor
bypass RE (for AC)
open (for DC)




$$V_{out} = \frac{V_{source} \cdot R_{in}}{R_{in} + R_{source}} \cdot g_m (\gamma_0 \parallel R_C \parallel R_L)$$

↓
In ac analysis, treat capacitors to be short circuited.

$$G_v = \frac{-R_{in}}{R_{in} + R_{source}} \cdot g_m (\gamma_0 \parallel R_C \parallel R_L)$$

CS:

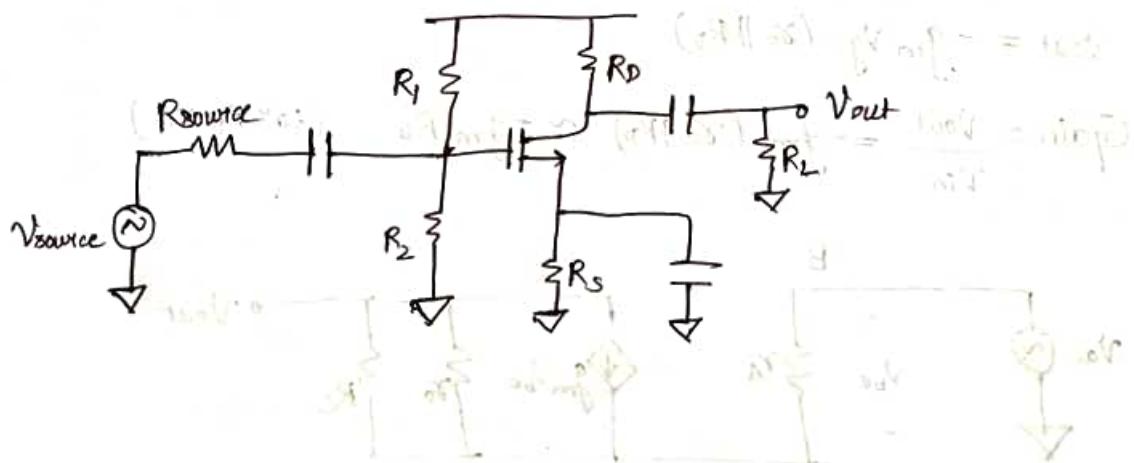
Temp. $\uparrow \rightarrow$ current \downarrow



(with β effect included)
start \Rightarrow (with β effect included) \Rightarrow (without β effect)


Common Source Amplifier with Source Degeneration

1-09-2023

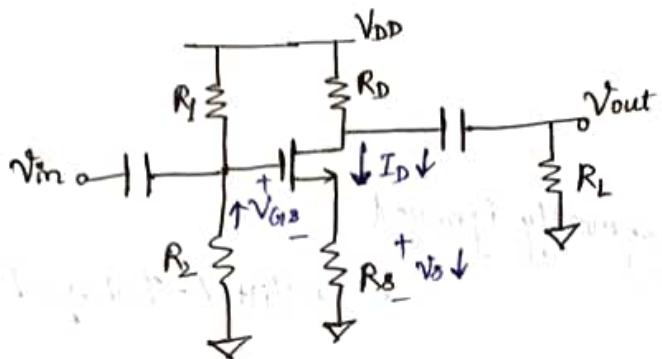

SSM:

$$V_{in} \xrightarrow{G_1} V_{gs}$$

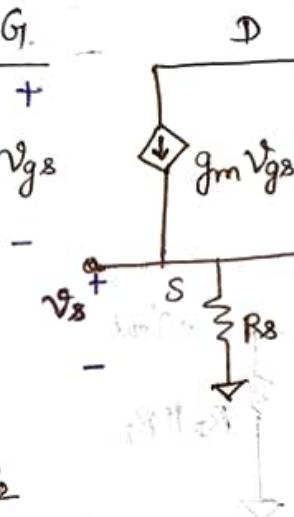

$$R_{in} = R_1 \parallel R_2$$

$$V_{in} = V_{gs} + V_s$$

$$V_s = g_m V_{gs} R_S$$

$$V_{out} = -g_m V_{gs} (R_D \parallel R_L)$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_S}$$

\Rightarrow Reduced by $(1 + g_m R_S)$ wrt if ~~R_S~~ is bypassed.

If R_S is bypassed,

$$A_{CS} = -g_m (R_D \parallel R_L) \Rightarrow$$
 harder to control gain.


$\rightarrow I_D \downarrow \Rightarrow V_S \downarrow \Rightarrow V_{GS} \uparrow \Rightarrow$ Current \uparrow

$\rightarrow R_S$ tries to correct the signal (e.g., in sinusoidal signal) (but cannot do fully), hence decreasing the gain (by factor of $\frac{1}{1 + g_m R_S}$).

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_S} = \frac{-(R_D \parallel R_L)}{g_m + R_S} \approx -\frac{(R_S \parallel R_L)}{R_S} \quad (\because R_S \gg \frac{1}{g_m})$$

T1 ROM to JBLOM-T

for in Transistor

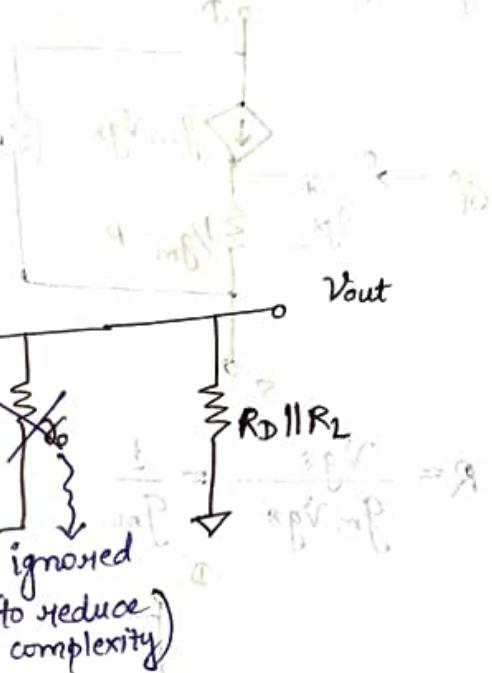


- BJT and MOSFET have opposite behaviour on temperature dependence
- $T \uparrow \Rightarrow$ Mosfet current \downarrow

$$\rightarrow A_v \approx \frac{\text{Total Resistance @ Drain}}{\text{Total Resistance @ Source}}$$



T-Model of MOSFET

↳ Small-Signal Circuit

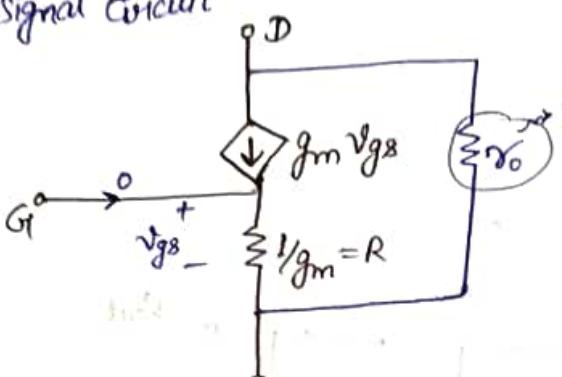

→ Tilted-T shaped
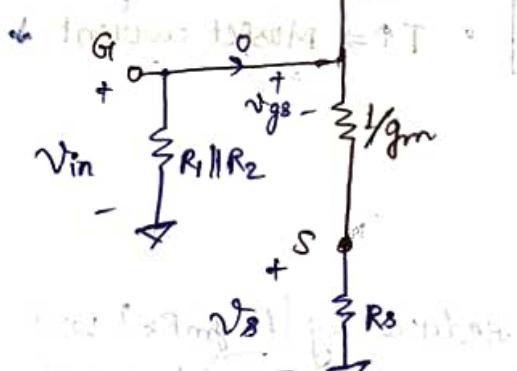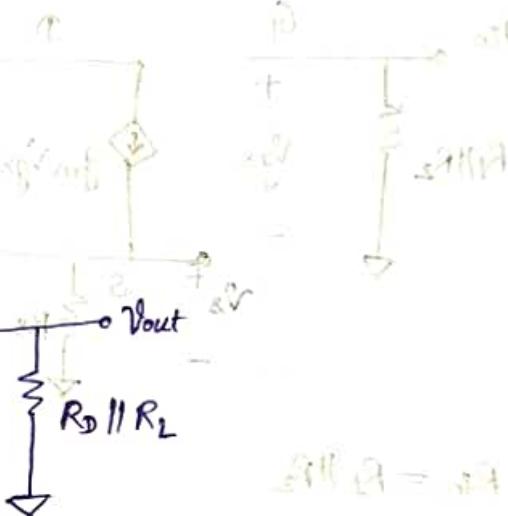
$$R = \frac{v_{gs}}{g_m v_{gs}} = \frac{1}{g_m}$$



$$V_{out} = -g_m v_{gs} (R_D || R_L)$$

$$v_{gs} = \frac{R_S + \frac{1}{g_m} v_{in}}{R_S + \frac{1}{g_m}} v_{in}$$



$$(g_m || g_m) \text{ mfp} = \frac{m}{m + 1}$$

$$\frac{(g_m || g_m) \text{ mfp}}{g_m + \text{mfp}} = \frac{m}{m + 1}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m (R_D || R_L) v_{in}}{1 + g_m R_S}$$

$$\frac{(g_m || g_m)}{g_m} = \frac{(g_m || g_m)}{g_m + \text{mfp}} = \frac{(g_m || g_m) \text{ mfp}}{g_m \text{ mfp} + 1} = \frac{m^2}{m^2 + 1} = m^2$$


CE with Emitter Degeneration

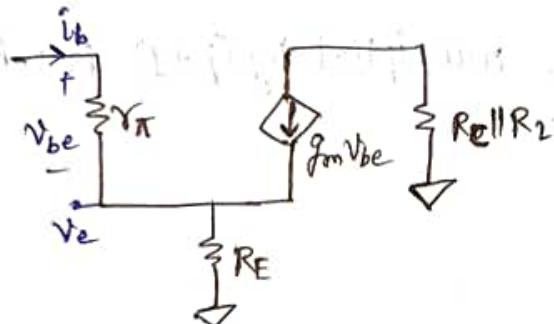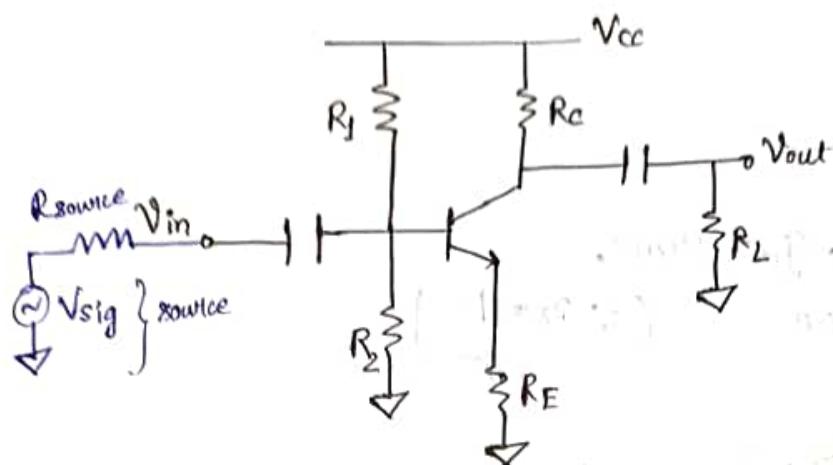

$$V_e = \left(\frac{V_{be}}{r_\pi} + g_m V_{be} \right) R_E$$

$$= \left(\frac{1}{\alpha} + g_m \right) R_E$$

T-Model:

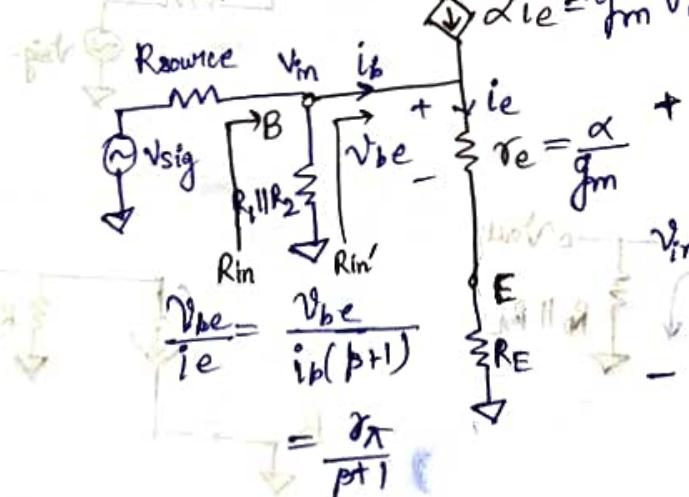

$$A_v = \frac{V_{out}}{V_{in}} \approx -g_m (R_C || R_L)$$

$$\approx -\frac{R_C || R_L}{V_e + R_E}$$

$$i_e = \frac{V_{in}}{r_E + R_E}$$

$$i_b = \frac{i_e}{\beta + 1}$$

$$R_{in} = \frac{V_{in}}{i_b}$$

$$i_b = \frac{V_{in}}{(\beta + 1)(r_E + R_E)}$$

$$V_{out} = -\beta i_b (R_C || R_L)$$

$$\frac{V_{in}}{i_b} = R_{in}' = \frac{i_e(\gamma_e + R_E)}{i_b}$$

$$\Rightarrow R_{in}' = (\beta+1)(\gamma_e + R_E) \\ = \gamma_e + (\beta+1)R_E$$

For $\beta=100$, $R_E=500\Omega$, $g_m=40\text{ms}$,


$$R_{in}' = 2500 + 50500 \quad (\because \gamma_e = \frac{\beta}{g_m})$$

"Impedance Reflection Rule"


Anything we put at emitter, multiplied by $(\beta+1)$ is what appears at the input side.

Common Gate / Common Base



CG:

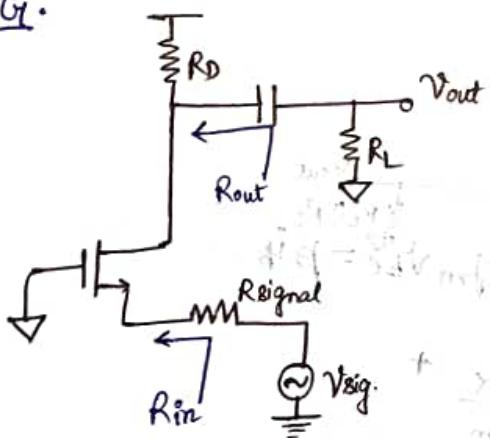

GB:

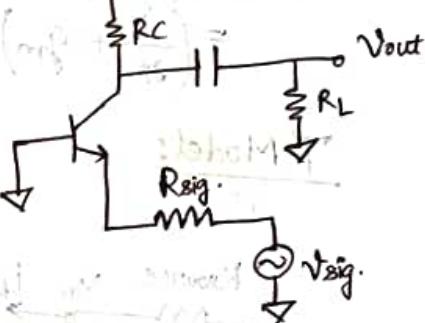

T-Model:

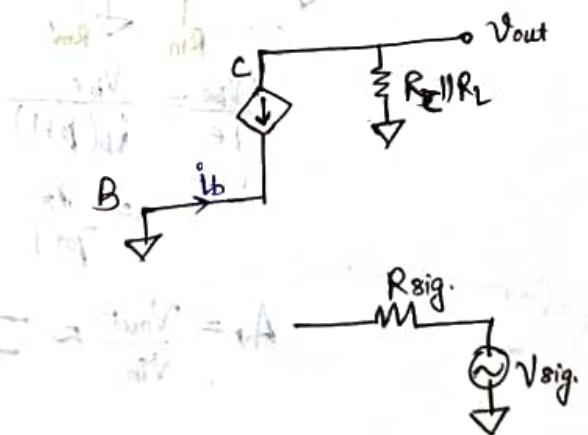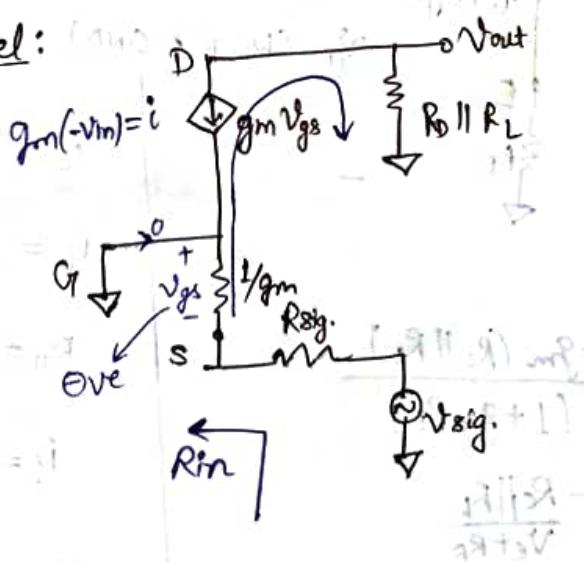

Common Gate

$R_{in} = \frac{1}{g_m}$ \rightarrow very low input impedance (e.g., 25Ω)

$$V_{out} = i (R_D \parallel R_L)$$

$$= \frac{V_{in}}{\frac{1}{g_m}} (R_D \parallel R_L)$$


$$A_v = \frac{V_{out}}{V_{in}} = g_m (R_D \parallel R_L)$$

$$\begin{aligned} G_{vV} &= \frac{V_{out}}{V_{sig.}} = \frac{\frac{1}{g_m} \times g_m (R_D \parallel R_L)}{\frac{1}{g_m} + R_{sig.}} \\ \text{Overall gain} &= \frac{R_D \parallel R_L}{\frac{1}{g_m} + R_{sig.}} \cdot R_{in} \end{aligned}$$

Output Impedance, ($\because R_L \rightarrow$ load impedance)

$$R_{out} = R_D$$

Current Buffer

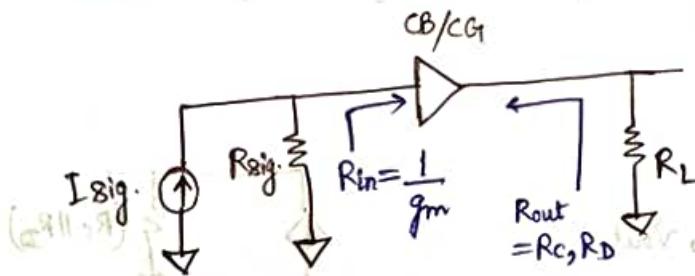

$$I_{in} = \frac{R_{sig}}{R_{sig} + \frac{1}{g_m}} \cdot I_{sig}$$

$$I_{out} = \frac{R_D}{R_D + R_L} \times I_{in}$$


Common Base

$$R_{in} = \frac{V_e}{I_e} = \frac{g_m}{gm} \approx \frac{1}{g_m}$$


$$V_{out} = \frac{V_{in}}{g_m} (R_C \parallel R_L)$$

$$A_v \approx g_m (R_C \parallel R_L)$$

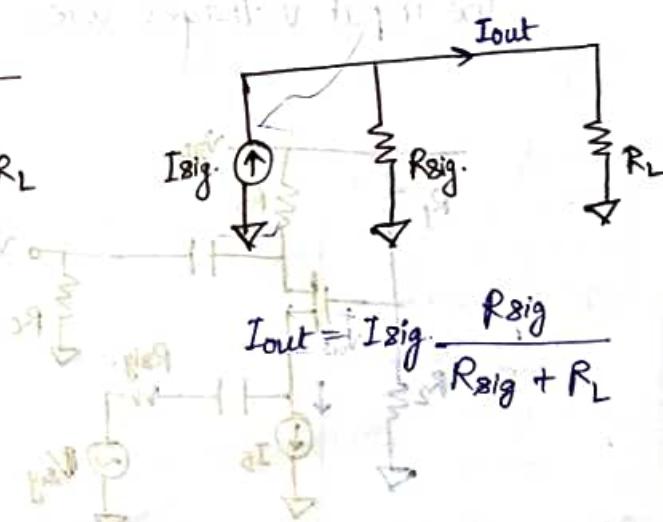Amplifier used with today's transmission line (having low char. impedance, $Z_0 \sim 50-70\Omega$) needs to have low input impedance, i.e., CG/CB amplifier.



CG/CB Amplifier:

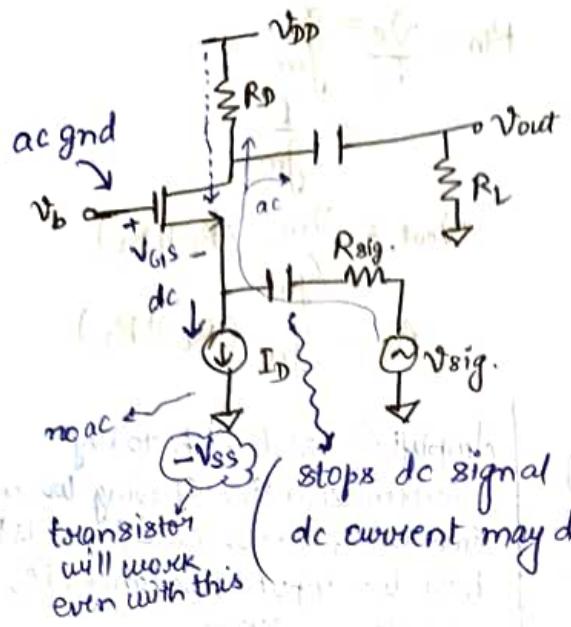


ac coupling → only ac is coupled in the transistors (dc blocked)

Vsig → | → CE → CB → sig
for ac coupling
e.g., in microphone
→ dc has no info.
not required in temperature sensor (which doesn't change much)



Quiescent Condition

→ Current consumption (dc voltages, etc.) of the ~~circuit~~ circuit when no input is provided.

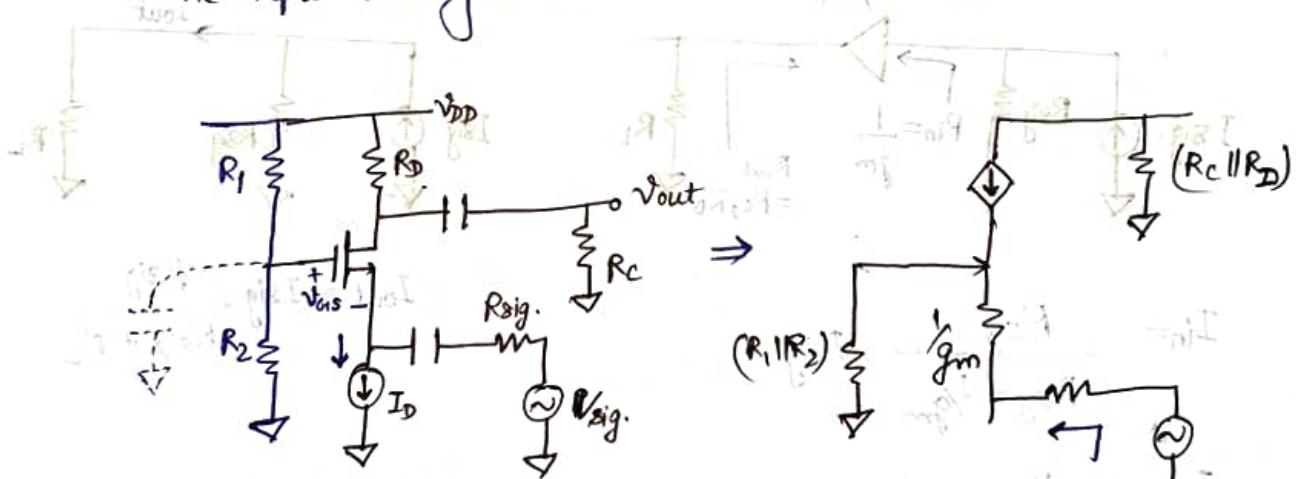→ For the transistor to work, it must be biased (like engine turned ON in a car) (having certain g_m), no matter what the input voltages are.





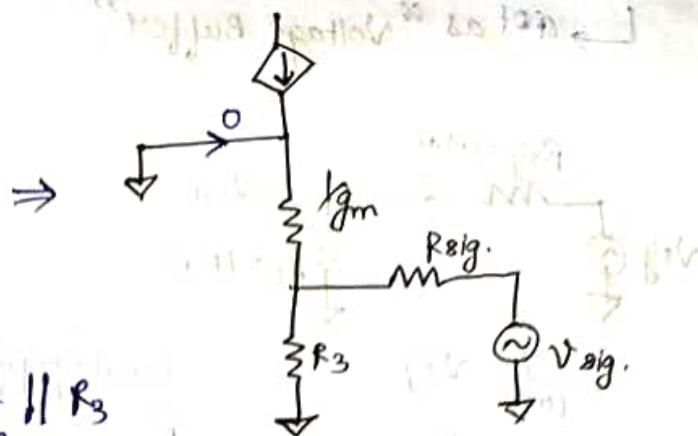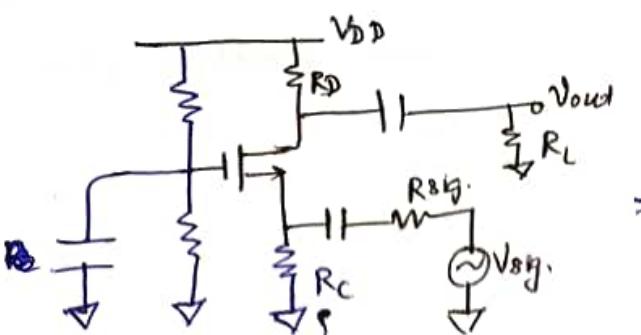For CG amplifier,
 $G \rightarrow$ ac gnd
Transistor won't work.



Instead of current source, a resistor or a saturated transistor up to large value of R can be used (doesn't allow current to change fast)

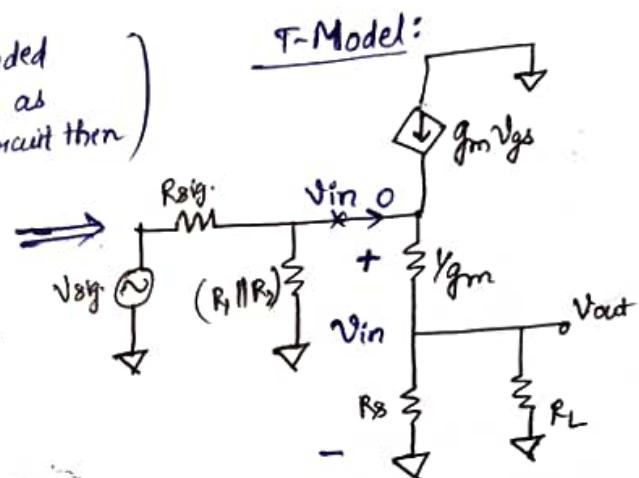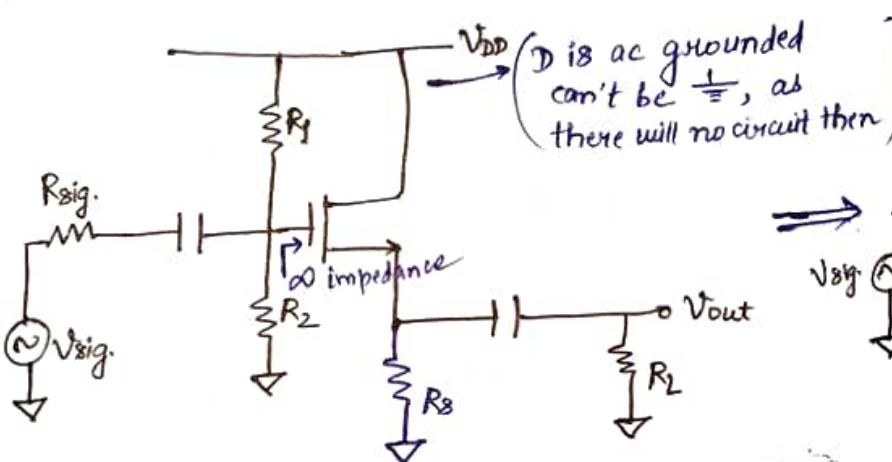Common Drain / Common Collector Amplifier



$$R_{in} = R_1 \parallel R_2$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{R_S \parallel R_L}{R_1 \parallel R_2 + \frac{1}{gm}}$$

$$G_V = \frac{V_{out}}{V_{sig.}}$$

$$= \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig.}} \cdot \frac{R_S \parallel R_L}{R_S \parallel R_L + \frac{1}{gm}}$$

R_{in} calculation:
test current I_T :


 $I_T = \frac{V_T}{R_1 \parallel R_2}$
 $R_{in} = \frac{V_T}{I_T} = R_1 \parallel R_2$

To find R_{out} .


$V_{sig.} = 0$ & find $\frac{V_T}{I_T}$ by connecting V_T @ V_{out} .

$$R_{out} = R_S \parallel \frac{1}{gm} \approx \frac{1}{gm} \quad (\because R_S \gg \frac{1}{gm})$$
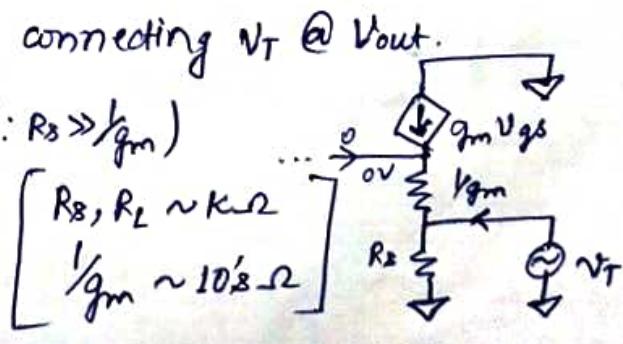
$$A_V = \frac{R_S \parallel R_L}{R_S \parallel R_L + \frac{1}{gm}} \approx 1 \quad (A_V < 1)$$





↪ act as "Voltage Buffer".

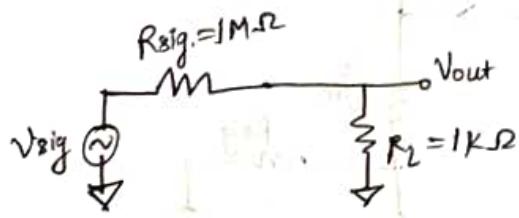


$$\frac{1}{1001} \cdot V_{sig}$$

buffer low impedance
to high imp.

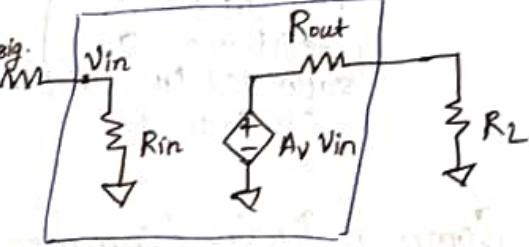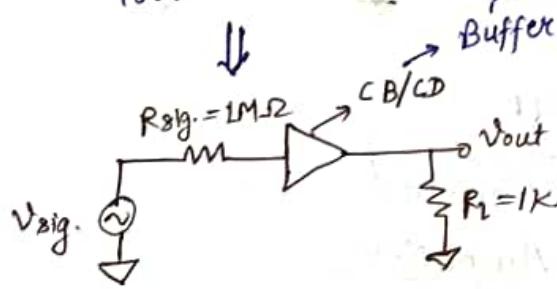


Common Collector (CC):

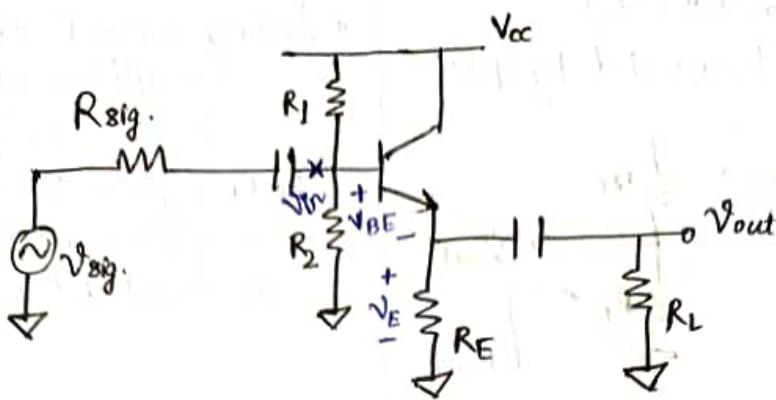

CC:
input = B
output = E

T-Model:

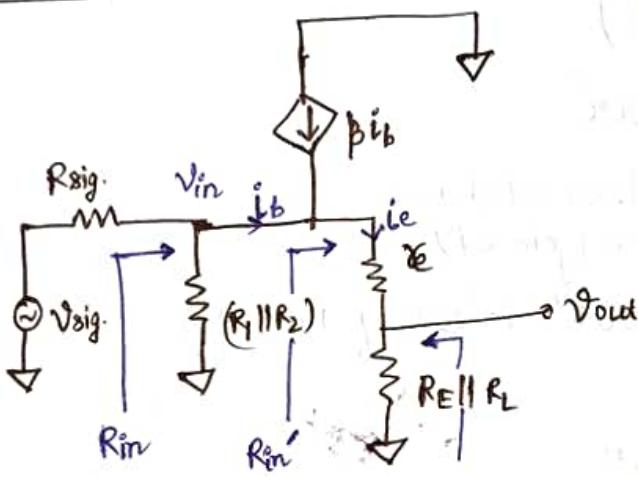

$$Rin' = (\beta + 1)(r_e + R_E \parallel R_L)$$

$$Rin' = \frac{V_{in}}{i_b}$$

$$i_e = \frac{V_{in}}{r_e + (R_E \parallel R_L)}$$

$$i_e = (\beta + 1) i_b$$

... Impedance
Reflection rule

$$V_{out} = V_{in} \frac{R_E \parallel R_L}{r_e + (R_E \parallel R_L)} \quad \text{(voltage divider rule)}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{R_E \parallel R_L}{r_e + (R_E \parallel R_L)}$$

$$Rin = R_1 \parallel R_2 \parallel (\beta + 1)(r_e + (R_E \parallel R_L))$$

≈ 1
 < 1


$$G_v = \frac{V_{out}}{V_{sig}} = \frac{Rin}{Rin + R_{sig}} \frac{R_E \parallel R_L}{r_e + (R_E \parallel R_L)}$$

Set $V_{sig} = 0$

$$Rout \approx r_e \parallel R_E \approx r_e$$

Thevenin Equivalent Circuit:

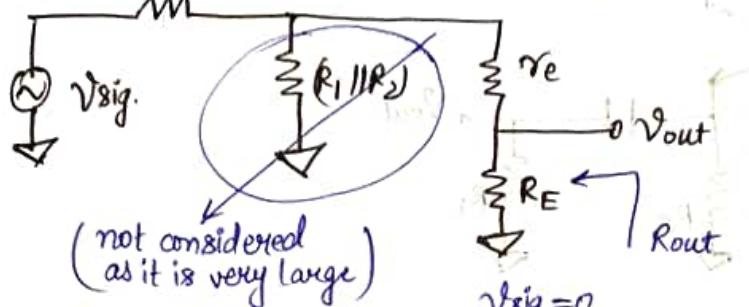(As seen from ~~output~~ Emitter side)
 $R_{sig}/(\beta+1) \rightarrow$ downscaled by $(\beta+1)$



$$R_{out} = R_E \parallel \left(r_e + \frac{R_{sig}}{\beta+1} \right)$$

↳ "Emitter Follower"



→ Emitter follows whatever
is at base (gain ≈ 1)

"Source Follower" in case of MOSFET

In BJT,

- Looking from B-side, everything at E-side is scaled by $(\beta+1)$
- Looking from E-side, everything at B-side is downscaled by $(\beta+1)$.

→ "Diode connected transistor"

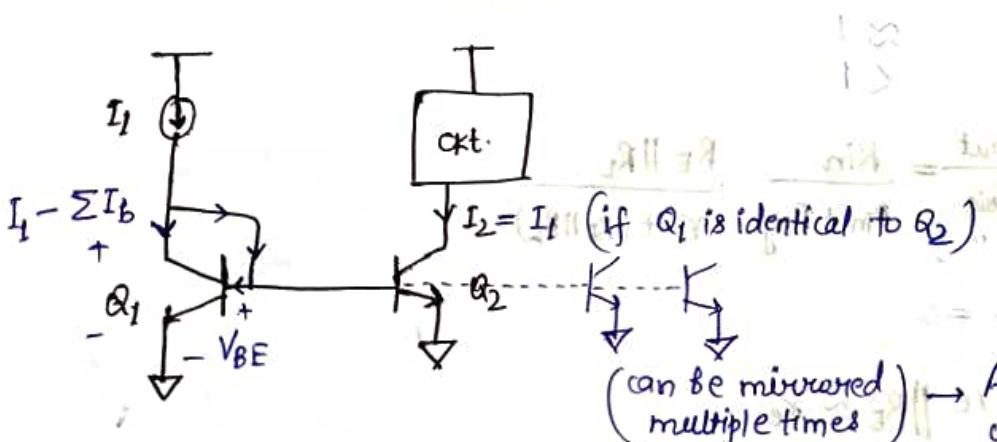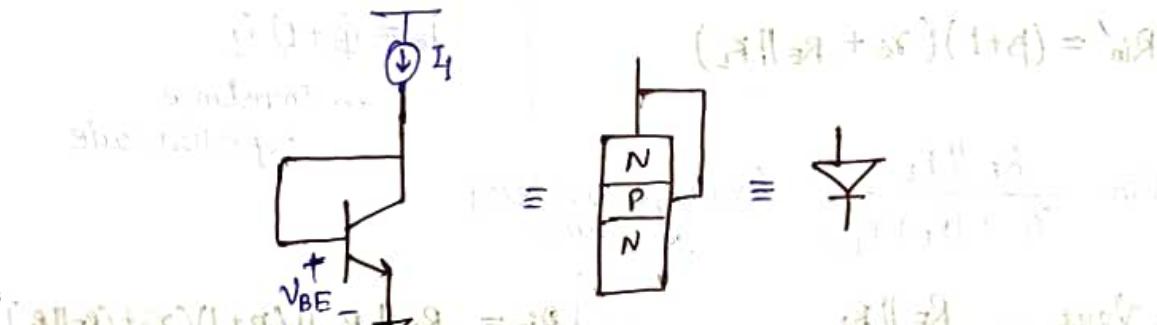

↳ "Current Mirror"


(can be mirrored multiple times) → As BJT needs I_B current getting mirrored is $(I_1 - \sum I_B)$.

no such case in MOSFET


$$V_{CE} = V_{BE} \approx 0.6 - 0.7 \text{ V}$$

$$> 0.3 \text{ V}$$

#

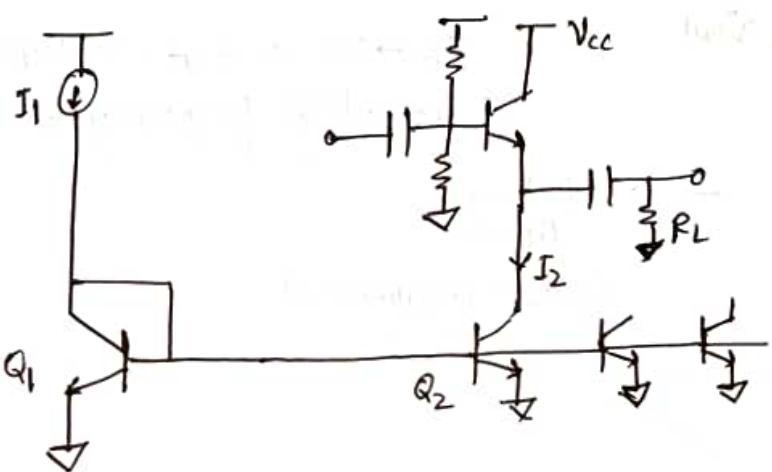


→

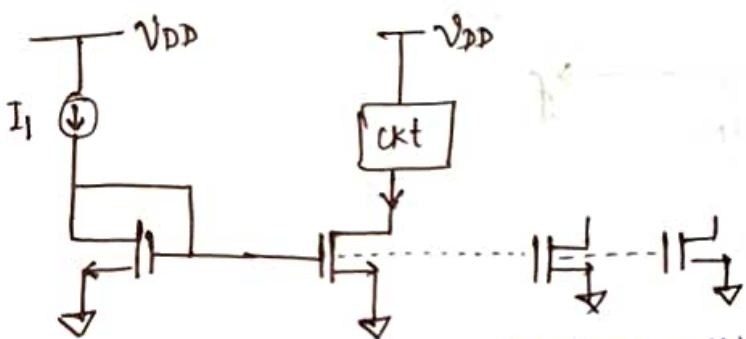

current getting mirrored = I_1 .


FREQUENCY RESPONSE OF AMPLIFIERS

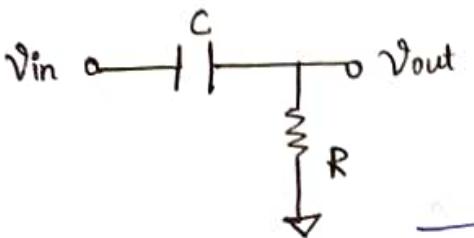

$V_{in} \rightarrow DC \Rightarrow V_{out} = 0$ (open)

$V_{in} \rightarrow high\ frequency \Rightarrow V_{out} = V_{in}$ (short)

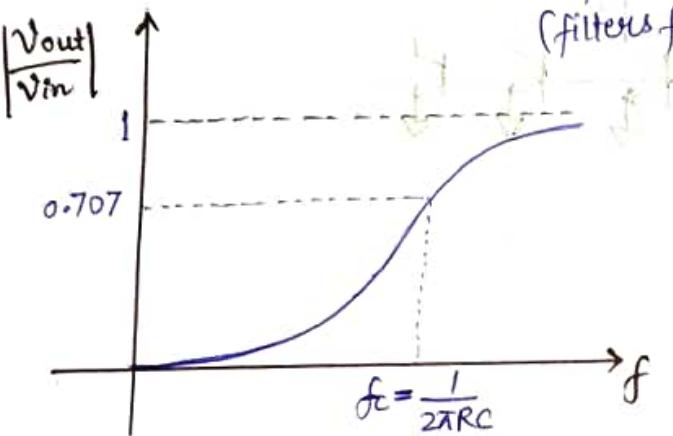→ Electronic filter
(filters frequencies)



$$V_{out} = \frac{R}{R + \frac{1}{j\omega C}} V_{in}$$

$$\frac{V_{out}(j\omega)}{V_{in}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$|\omega = 2\pi f$$

$$|\omega = \frac{1}{RC}$$

↳ High Pass Filter

↳ Passes high frequency

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} \quad \text{when } \omega = \frac{1}{RC}$$

$$\Rightarrow \frac{P_{out}}{P_{in}} = \left| \frac{V_{out}}{V_{in}} \right|^2 = \frac{1}{2}$$

“Bandwidth”

→ Quantity in dB = $10 \log \frac{P_{out}}{P_{in}}$


$$\frac{V_{out}}{V_{in}} = 100$$

$$\frac{P_{out}}{P_{in}} = 10^4$$


$$10 \log 10^4 = 40 \text{ dB}$$

OR

$$20 \log \frac{V_{out}}{V_{in}}$$

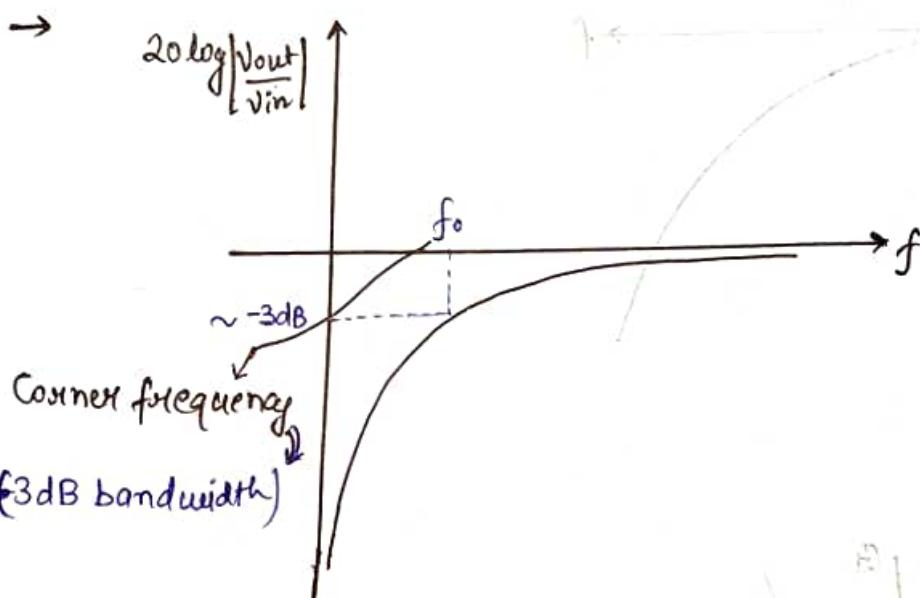


Model:

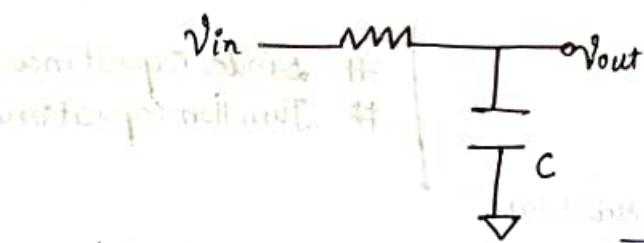

at DC, $V_{out} = V_{in}$

@ $f \gg$, $V_{out} = 0$

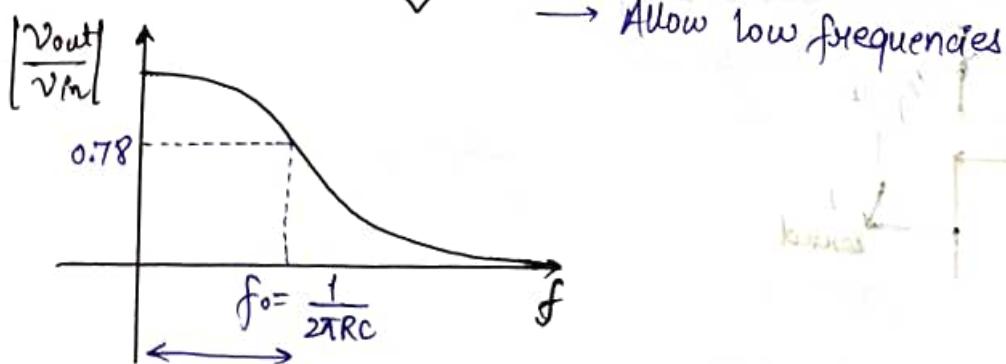


bandwidth: frequency range over which signal is passed.


$$\frac{V_{out}(j\omega)}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$\Rightarrow \left| \frac{V_{out}(j\omega)}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


$$\Rightarrow \left| \frac{V_{out}(j\omega)}{V_{in}} \right| \Big|_{\omega = \frac{1}{RC}} = \frac{1}{\sqrt{2}}$$

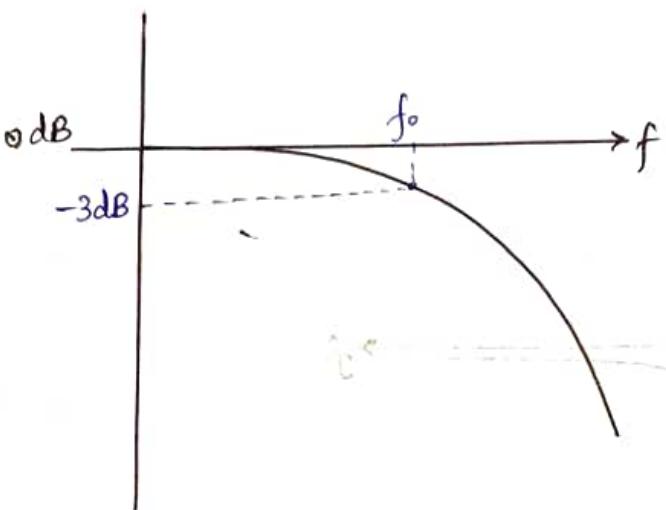


MOSFET:

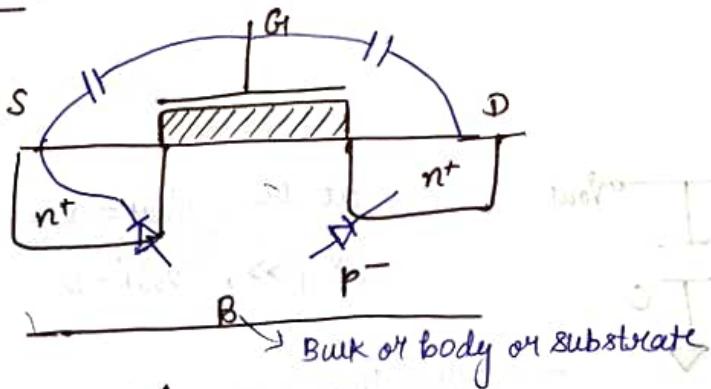

Diode capacitance
Junction capacitance

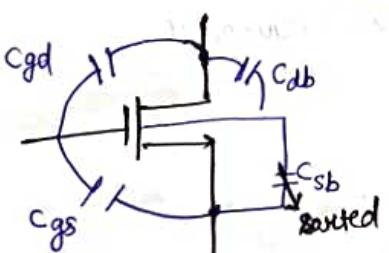


CS:

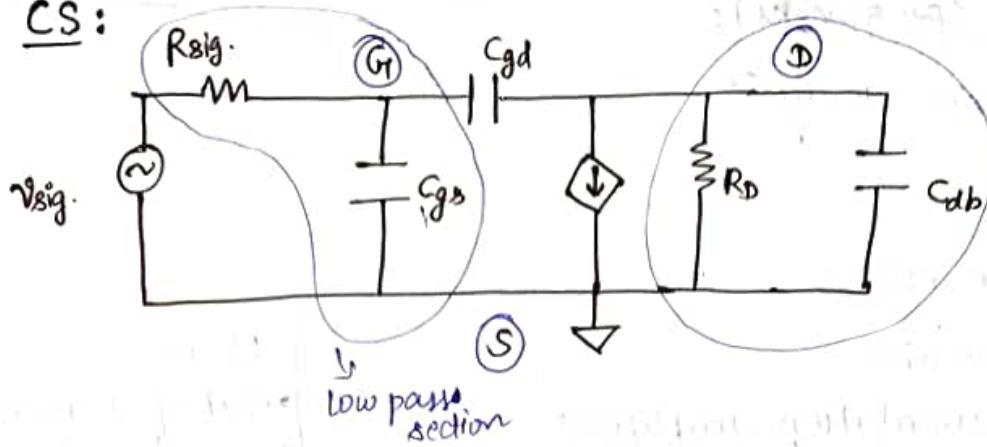


→ Low pass behaviour

- No device has infinite bandwidth

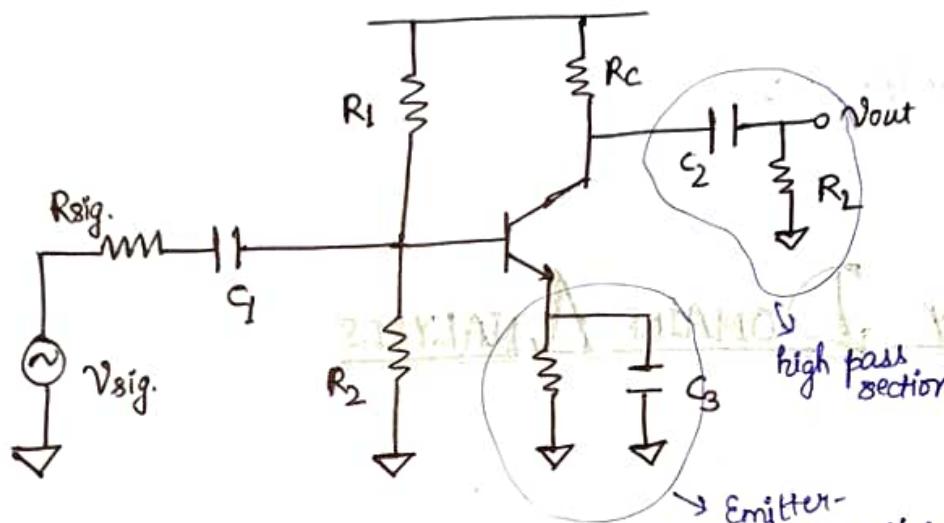

↳ High pass

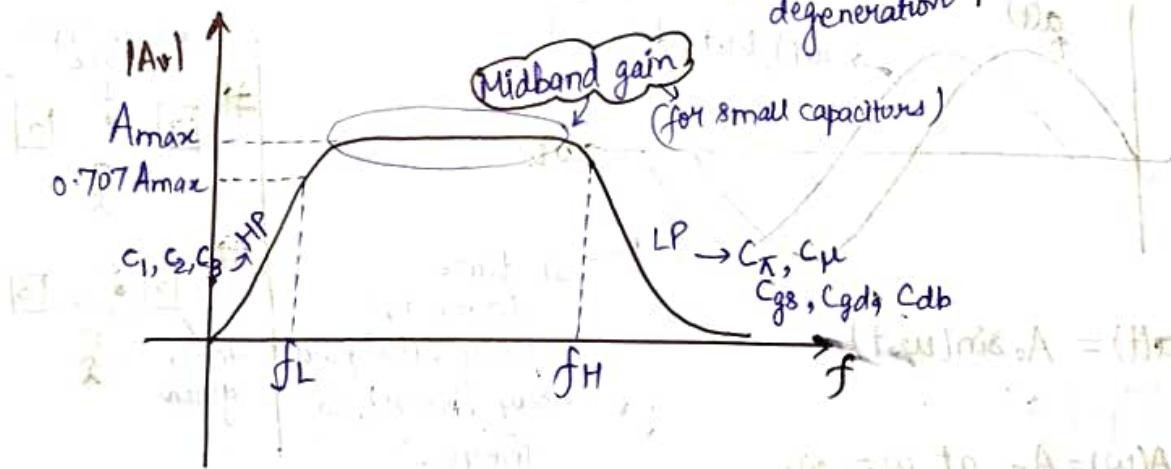

↳ Band of frequency, over which it amplifies as intended
 ↳ "Bandpass" (amplifier functions)

$$f_H - f_L = BW$$

$$\omega_0 = \omega_0 + \omega_0 = \omega_0$$

Topics till Quiz 2 (for 5 weeks):

① Frequency domain analysis

② Opamps

- circuits

- Non-linearities

③ Precision electronics

- Instrumentation amplifiers

④ Filters

- RC


- 1st order

⑤ Oscillators

Book:
 → Art of Electronics
 → Boylestad

FREQUENCY DOMAIN ANALYSIS

Review

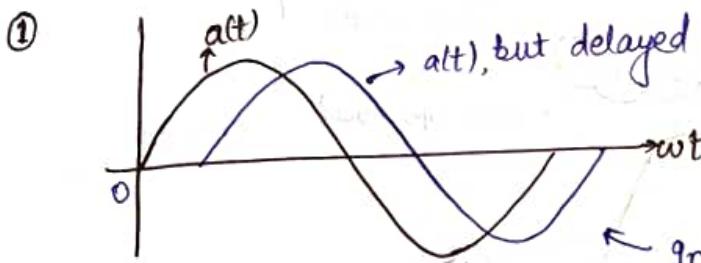

$$a(t) = A_0 \sin(\omega_0 t)$$

or

$$A(\omega) = A_a \text{ at } \omega = \omega_0$$

phase < $\theta_0 = 90^\circ$

source appears to be in middle
 sound system

delay given

② Frequency as complex no.:

$$\omega = \sigma_0 + j\omega_0$$

state of increase/
decay of amplitude

frequency

natural freq.


constitutes damping

$$a(t) = A e^{(\sigma_0 + j\omega_0)t}$$

Frequency domain

both Re & Im part

take only Re part to get time-domain


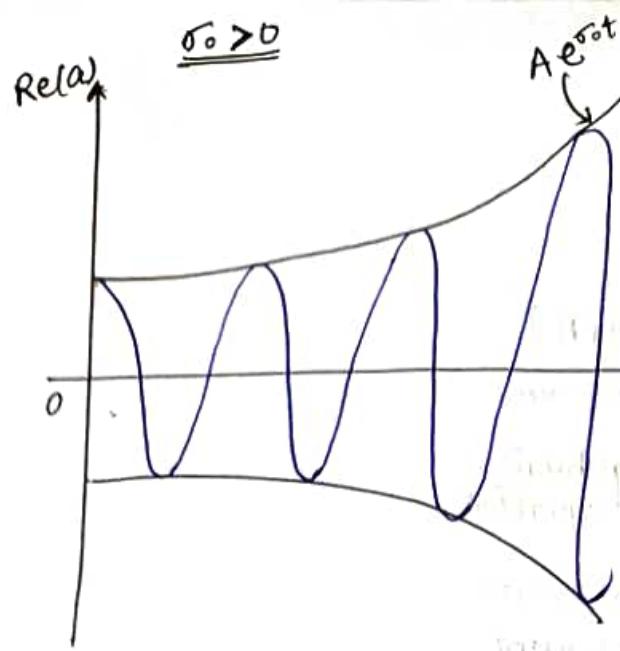


Exponential growth

$\sigma_0 > 0$

t

A

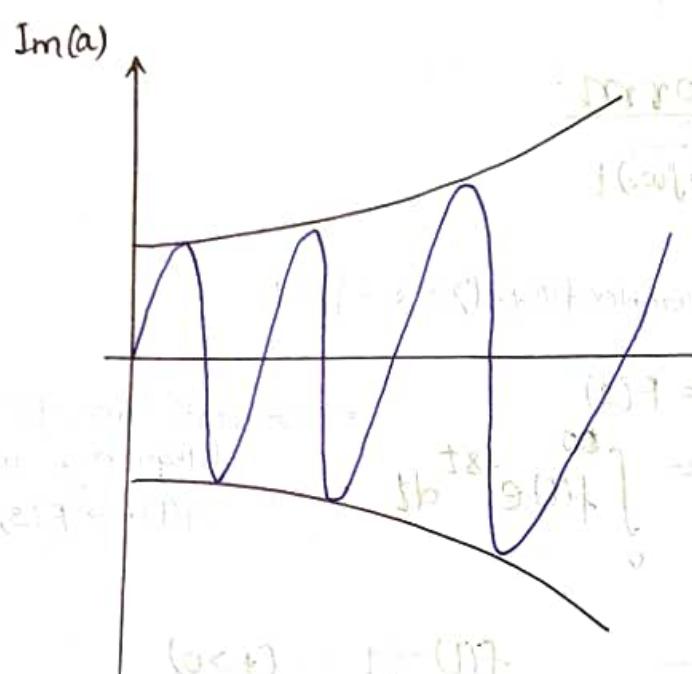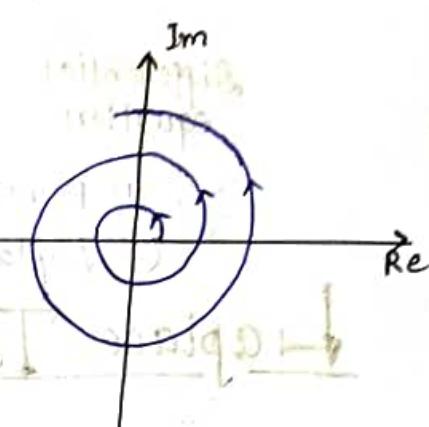


Exponential growth

$\sigma_0 > 0$

$\sigma_0 > 0$



$\sigma_0 > 0$

$\sigma_0 < 0$ (decay)

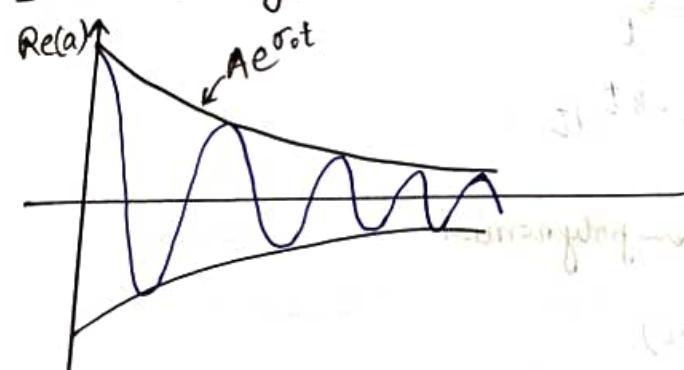

Overlapping Rel(α) & Im(α)


Helix

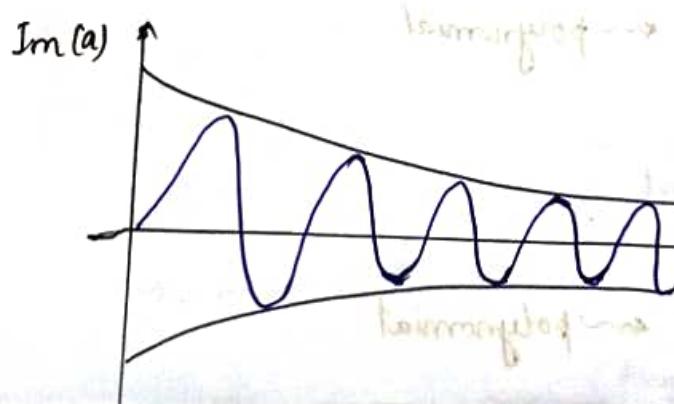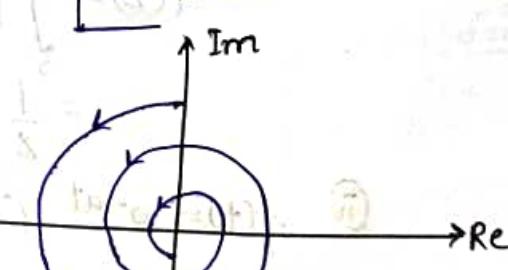

Decay

Decay

Use of Transforms

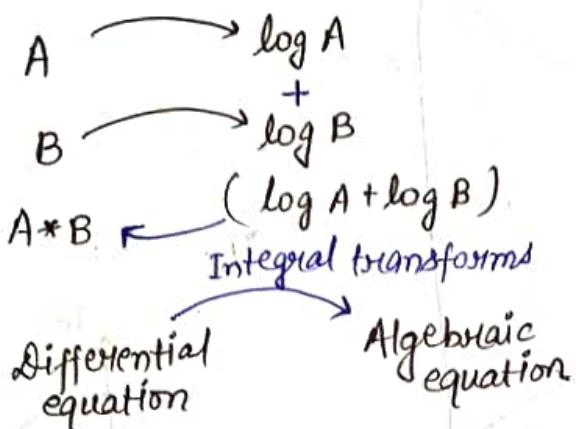


- Eg. ① Fourier transform
② Laplace transform.

Laplace Transform

$$a(t) \longrightarrow A e^{(\sigma_0 + j\omega_0)t} = A e^{\sigma t} \text{ complex freq. } (\sigma = \sigma_0 + j\omega_0)$$
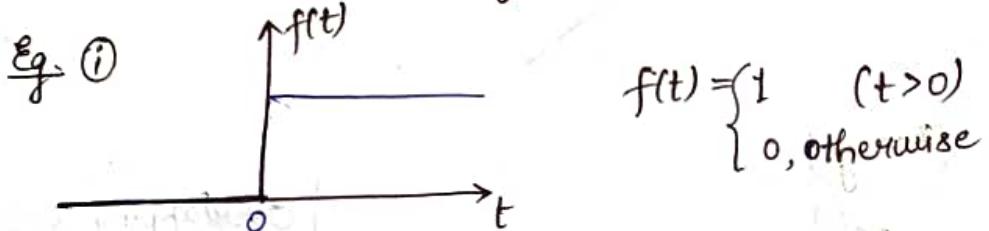
$$f(t) \longrightarrow L[f(t)] = F(s) = \int_0^\infty f(t) e^{-st} dt \quad \begin{matrix} \rightarrow \text{converts time function to} \\ \text{frequency function} \\ f(t) \rightarrow F(s) \end{matrix}$$



$$\begin{aligned} F(s) &= \int_0^\infty 1 \cdot e^{-st} dt \\ &= \frac{1}{s} \text{ en polynomial} \end{aligned}$$

ii) $f(t) = e^{-at} \quad (t > 0)$

$$L[f(t)] = \frac{1}{(s+a)} \text{ en polynomial}$$

iii) $f(t) = \cos \omega_0 t = \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2}$

$$L[f(t)] = \frac{s}{s^2 + \omega_0^2} \text{ en polynomial}$$

$$\mathcal{L}[f(t)] = \frac{\text{Num.}}{\text{Den.}}$$

roots of (Num)
roots of (Den)

For $\frac{1}{s} \rightarrow$ root of den = 0 \rightarrow pole \rightarrow (root of num \rightarrow doesn't exist)

For $\frac{s}{s^2 + \omega_0^2} \rightarrow$ root of num = 0 \rightarrow zero

In amplifiers, we take pole nowhere near to zero.

In oscillators, we take pole = 0.

19-09-2023

Properties of Laplace Transforms

① Linear

$$\begin{aligned} ① \quad f(t) &\longrightarrow F(s) \\ af(t) &\longrightarrow aF(s) \end{aligned}$$


②

$$\begin{aligned} f(t) &\longrightarrow F(s) \\ g(t) &\longrightarrow G(s) \\ a_f(t) + b_g(t) &\longrightarrow aF(s) + bG(s) \end{aligned}$$

$$\text{Eg. } f(t) = 1 \quad (t > 0)$$

$$g(t) = 1 \quad (t > 0)$$
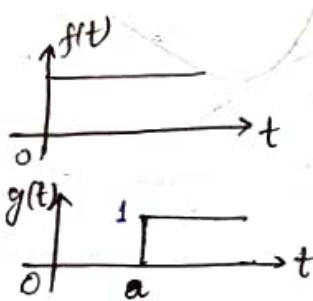
$$\rightarrow F(s) = \frac{\text{Num}(s)}{\text{Den}(s)}$$



roots of Num(s) \rightarrow Zeros of F(s)

roots of Den(s) \rightarrow Poles of F(s).


Representation:
0 \rightarrow Zero
x \rightarrow Pole

$$\text{Eg. } F(s) = \frac{1}{s+a}$$

$$f(t) \quad \text{roots: } s = -a$$

f(t) has a decay related to 'a'.
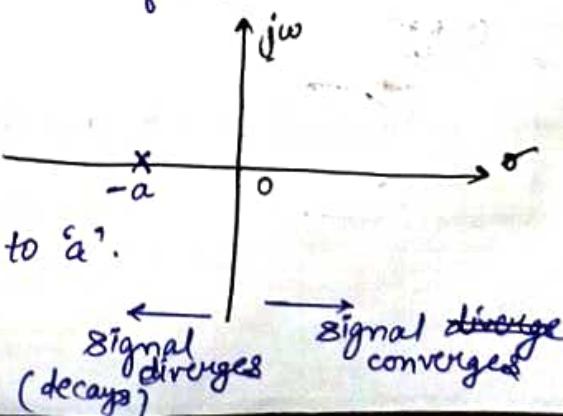
$$\Rightarrow f(t) = e^{-at}, \quad t > 0$$




$$\begin{aligned} s &= -a \\ jw &= 0 \end{aligned}$$

$$\text{Eq } f_1 = e^{-t}$$

$$f_2 = e^{-10t}$$

\curvearrowleft decays faster

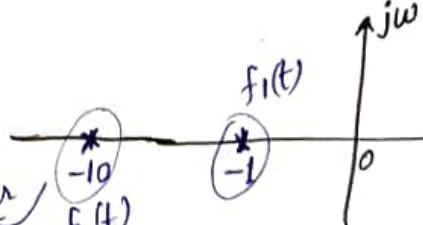

$$\text{rank } N_s = \text{rank } A$$

↓ f





$f \downarrow \rightarrow M$ moves
 $f \uparrow \rightarrow M$ doesn't move

$$\text{Eq: } F(s) = \frac{\omega_0^2}{s^2 + \omega_0^2}$$

$$F(s) = \frac{s}{s^2 + \omega_0^2}$$

$$\text{poles: } s = \pm j\omega_0$$

$$f(t) = \cos \omega_0 t$$

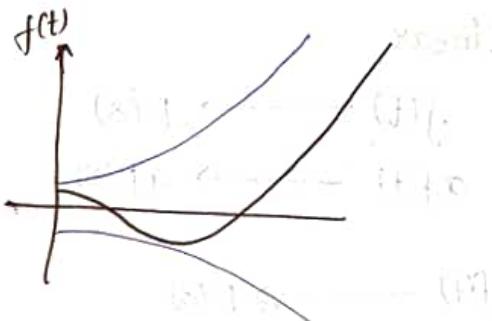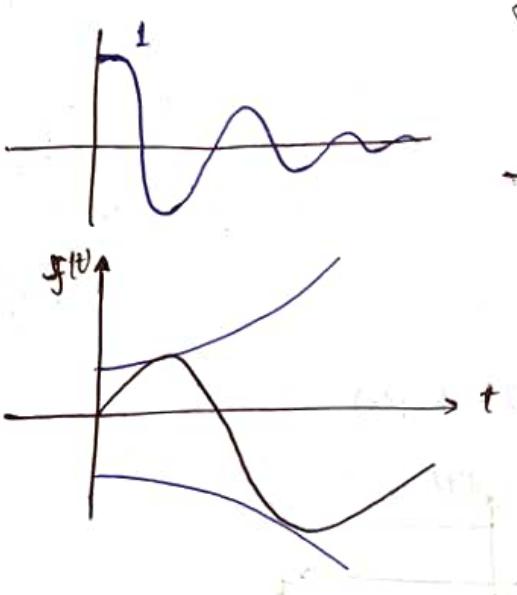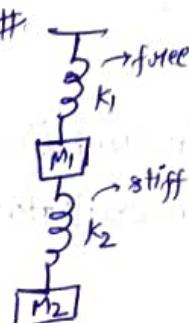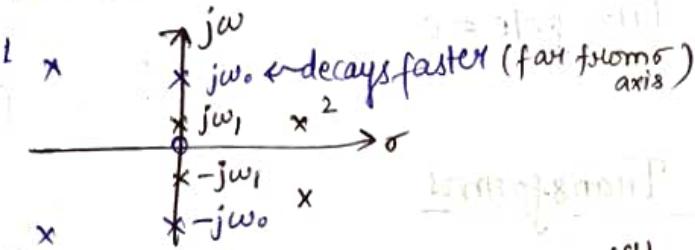

$$f(t) = (A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}) \sin(\omega t)$$

$$f(t) = (B_1 e^{-\alpha t} + B_2 t e^{-\alpha t}) \cos(\omega t)$$

$$\frac{1}{s+8} = 0.17$$

$$s = -8$$



$$f(t) = (C_1 e^{-8t} + C_2 t e^{-8t}) \sin(2t)$$



spontaneous

transient - position

longitudinal

Laplace Transform

$$f(t) \rightarrow F(s)$$

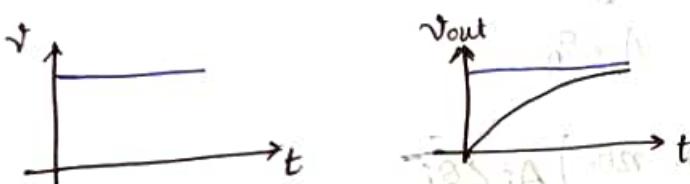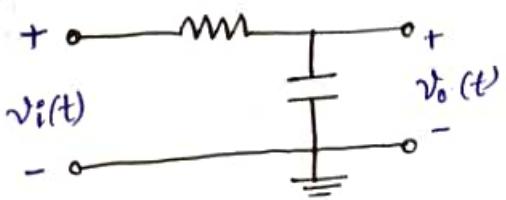


v_i transfer v_{out} function

Transfer function,

$$TF = \frac{V_{out}}{V_{in}} \rightsquigarrow \text{a function in } s\text{-plane}.$$

$$V_{out}(s) = T.F. \times V_{in}(s)$$

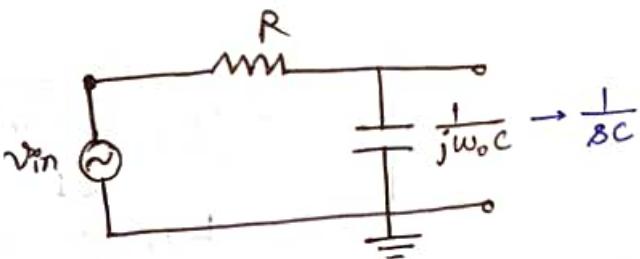

$$V_{in} = A \sin(\omega_0 t)$$

$$V_{out} = V_{in} \times \left(\frac{\frac{1}{j\omega_0 C}}{R + \frac{1}{j\omega_0 C}} \right)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1/8C}{R + 1/8C}$$

$\underbrace{\qquad\qquad\qquad}_{TF}$

$$\rightarrow s = \sigma + j\omega$$

We are interested in the response for a particular frequency @ steady state.

$$\Rightarrow \text{Replace } s = \sigma + j\omega \text{ by } s = j\omega.$$

⇒ If we want to know the response for all ω , replace $s = j\omega$.

$$TF = \frac{1/j\omega C}{R + 1/j\omega C}; \quad FR = \frac{1/j\omega C}{R + 1/j\omega C}$$

Frequency response

Input




$$A_i \angle \theta_i$$

Output

$$A_o \angle \theta_o$$

$$\rightarrow \underbrace{A_o \angle \theta_o}_{@ \omega_0} = \left(\begin{array}{l} \text{complex no.} \\ \text{FR}/\omega_0 \end{array} \right) A_i \angle \theta_i$$

into represent

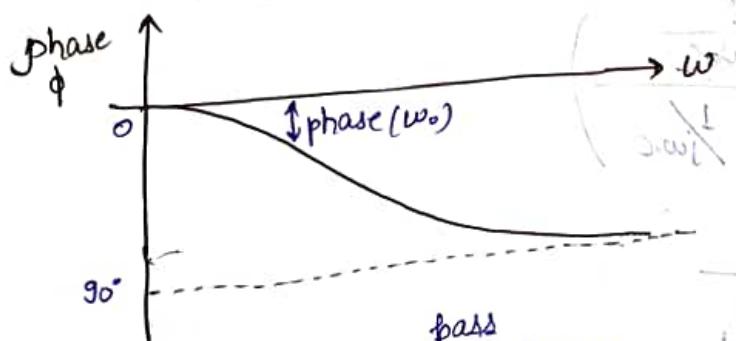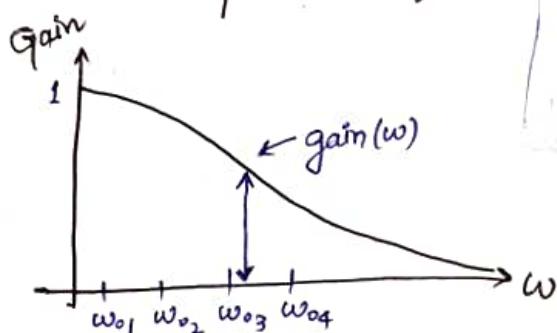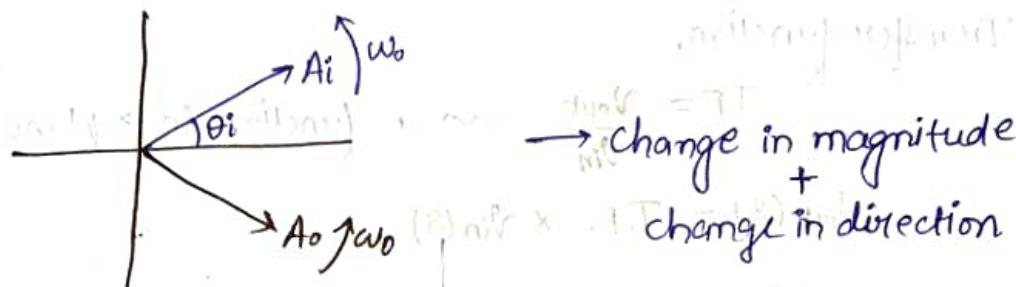

For very small frequency,
 $1/j\omega C \rightarrow$ very large
 ≈ 1

→ phase = 0
 of FR/ω_0



$$FR = \frac{1}{j\omega RC + 1}$$

as $\omega \rightarrow \infty$,
 $|FR| \rightarrow 0$



$$FR = \frac{1}{j\omega RC + 1} \cdot \frac{1-j\omega RC}{1-j\omega RC}$$

$$= \frac{1-j\omega RC}{1+j\omega^2 R^2 C^2}$$

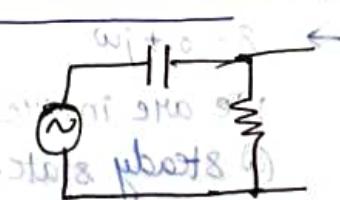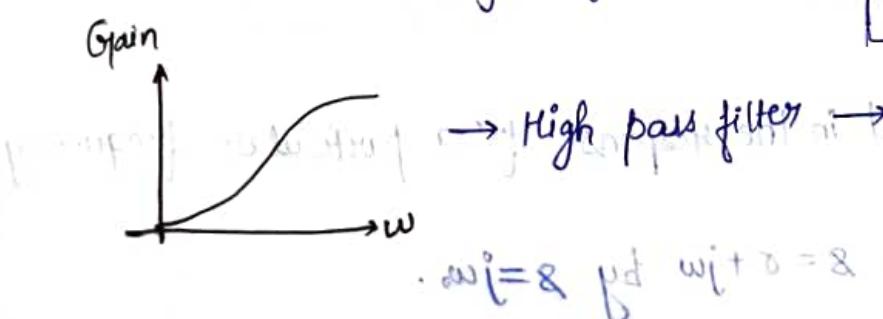
as $\omega \rightarrow \infty$,
 $\text{phase} \geq 90^\circ$



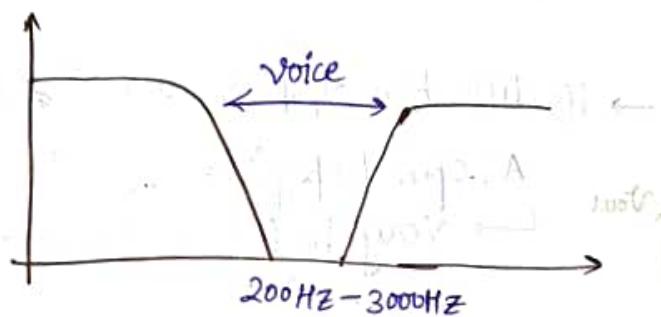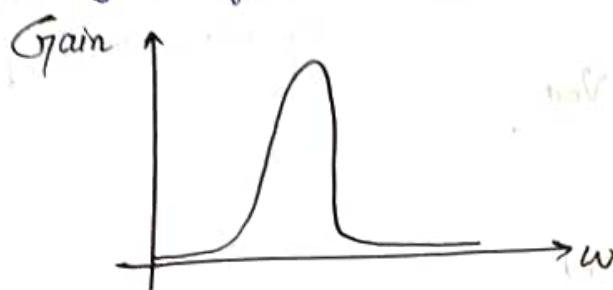
→ Cascading ('cascading one with other')
 ↳ connecting input of high pass filter to the output of low pass filter (or vice versa).



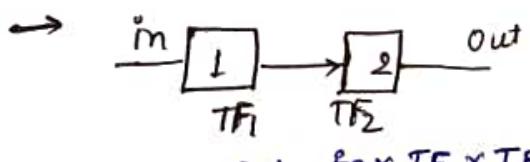
- Analysis → Generating curve from problem
- System design → Generating function from curve
- Synthesis


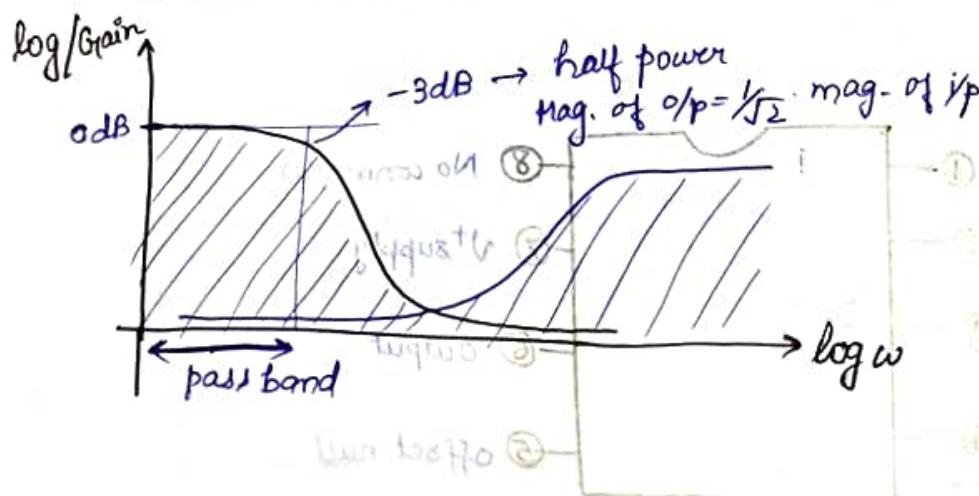
$$\text{Out} = \text{In} \times \text{TF}_1 \times \text{TF}_2$$



OPERATIONAL AMPLIFIER

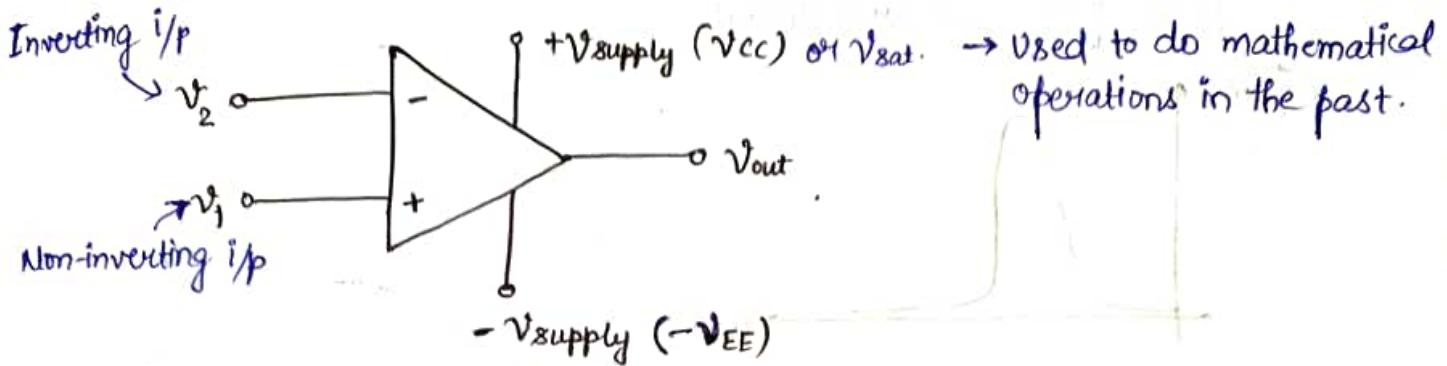


Gain: $10^5 - 10^6$

$$V_{out} = (v_1 - v_2)A \rightarrow \text{if diff. b/w } v_1 \text{ & } v_2 \sim 10^{-5} \text{ V.}$$


A: Open-loop gain

↳ Very high gain of order $10^5 - 10^6$.

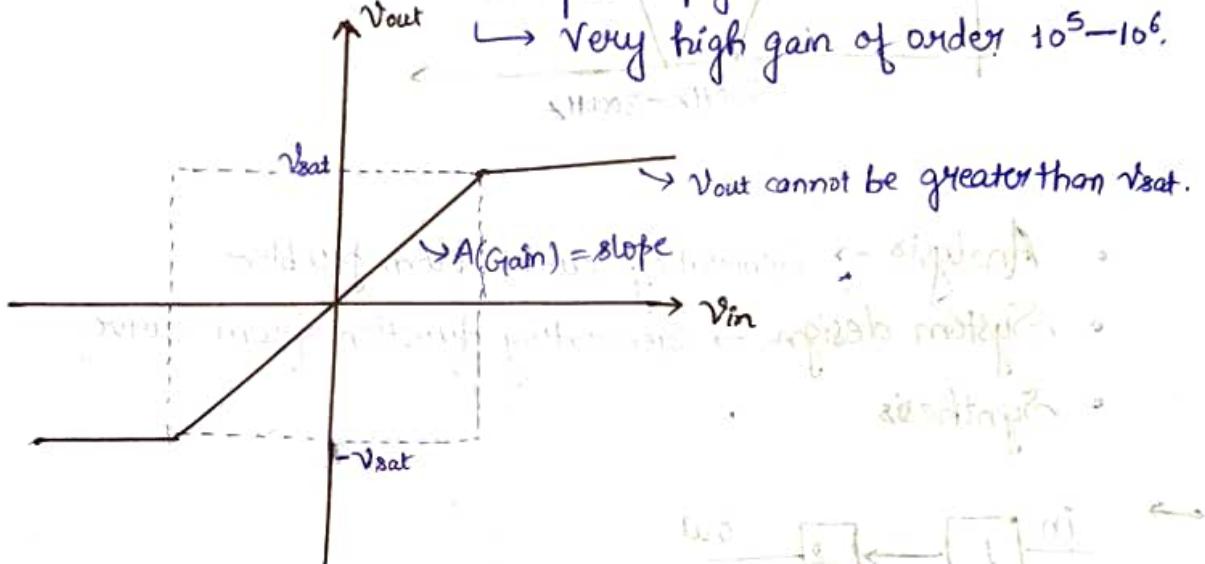


→ Opamps come in ICs.

e.g. LF411

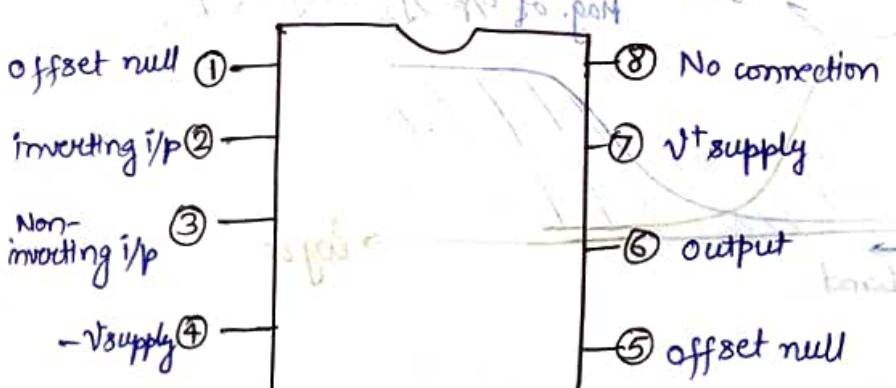

Golden Rules:

① Virtual Ground Rule:

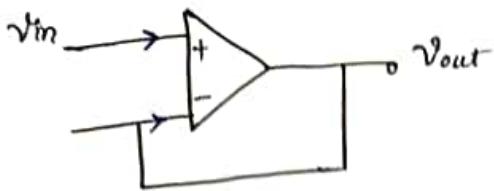


→ Voltage at the inverting terminal is equal to the voltage at the non-inverting terminal.

↳ "Voltage Follower circuit"

Opamps try to make $V_1 = V_2$.

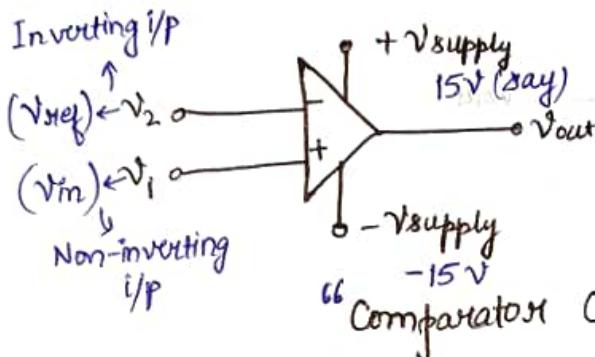② $I_{in} = 0$. (Input draws no current).




If ($V_{ref} > V_{in}$),

$$V_{out} = -V_{sat}$$


If ($V_{ref} < V_{in}$),

$$V_{out} = V_{sat}$$

LM324A

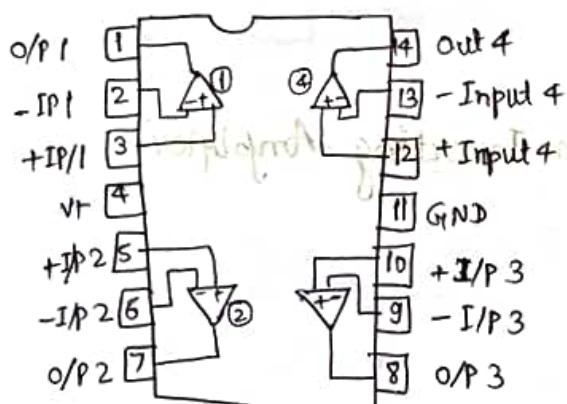

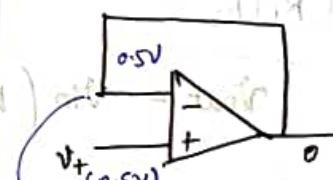
- if ($V_+ > V_-$),
 V_{out} increases very suddenly ($10^6 V/s$)
- if ($V_+ < V_-$),
 V_{out} decreases suddenly



V_- increases until it is 0.5V

→ V_{out} is limited by a range of voltages ($+V_{supply} -- V_{supply}$)
↳ cannot be $> V_{supply}$.


↳ for "Linear Circuits".

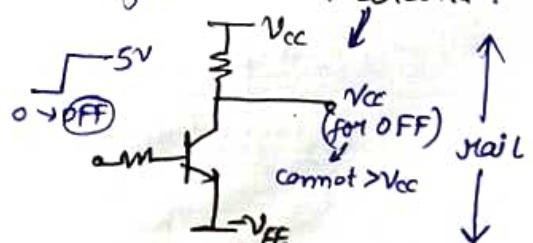

→ Rail-rail operation

→ Opamp is an extreme e.g. of differential amplifier.


Eg.

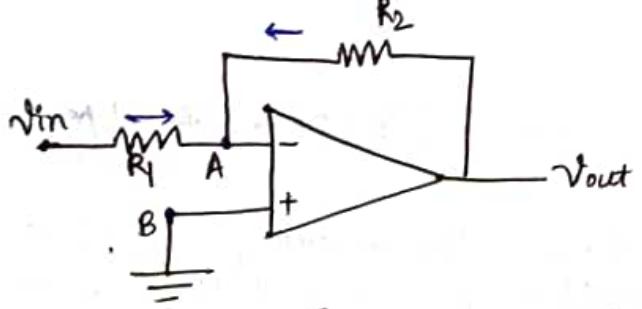

$$\frac{(V_{in} - V_A)}{R_1} + \frac{V_{out} - V_A}{R_2} = 0$$

$$\therefore V_{out} = -V_{in} \left(\frac{R_2}{R_1} \right) \rightarrow \text{"Inverting Amplifier"}$$

Eg.

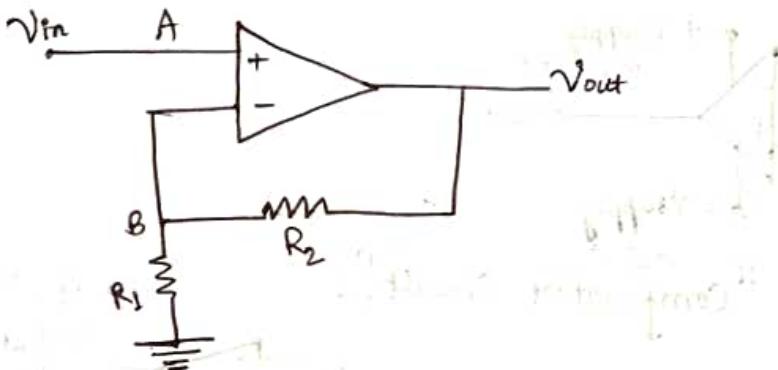

$$V_B = \left(\frac{R_1}{R_1 + R_2} \right) V_{out}; \quad V_A = V_{in}$$

$$\left(\frac{R_1}{R_1 + R_2} \right) V_{out} = V_{in}$$

$$\Rightarrow V_{out} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$$

↳ "Non-Inverting Amplifier"

Golden Rules

$$\textcircled{1} \quad V_{in+} = V_{in-}$$

$$\textcircled{2} \quad I_{in} = 0$$

→ Basic Opamp Circuits:

- ① Inverting amplifier
- ② Non-inverting amplifier
- ③ Voltage follower
- ④ Comparator circuit.


Basic Cautions:

→ Negative feedback


→ Transistor → Active Region

Opamp should work in

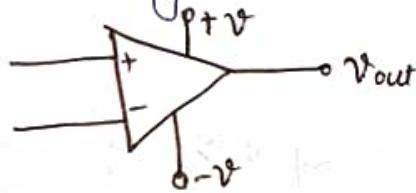→ Do not give voltage more than specified differential input.



Summer/Adder

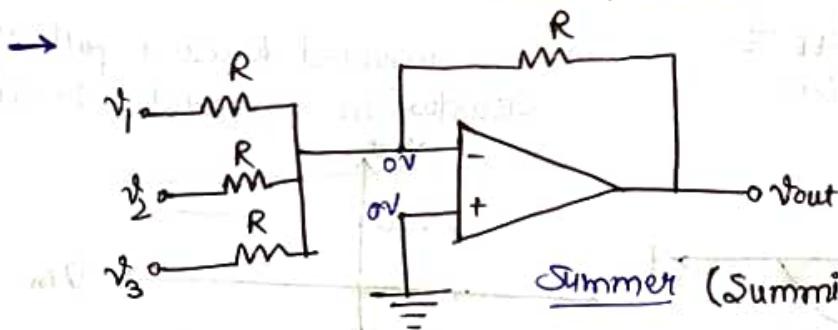


Summer (Summing Amplifier)

$$\frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R} + \frac{V_{out}}{R} = 0$$

$$\Rightarrow V_{out} = -(v_1 + v_2 + v_3)$$

Differential Amplifier

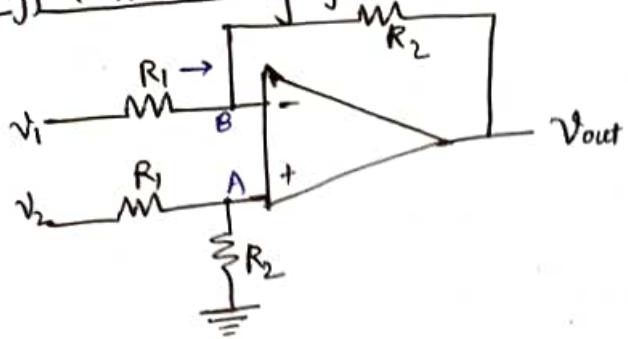


$$V_A - \left(\frac{R_2}{R_1 + R_2} \right) V_B = V_{out} \quad (\text{VGI Rule})$$

KCL at point B :

$$\frac{V_1 - V_B}{R_1} + \frac{V_{out} - V_B}{R_2} = 0$$

$$\Rightarrow V_{out} = (V_2 - V_1) \frac{R_2}{R_1}$$



Comparator Circuit

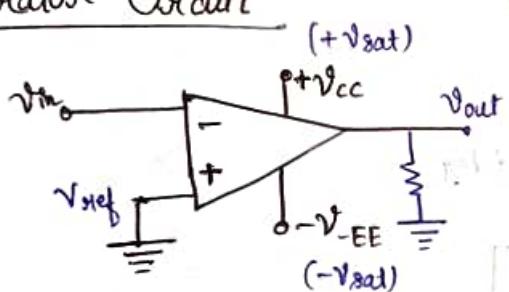


$$\text{If } V_i > V_{ref} \Rightarrow V_{out} = +V_{sat}$$

$$\text{If } V_i < V_{ref} \Rightarrow V_{out} = -V_{sat}$$

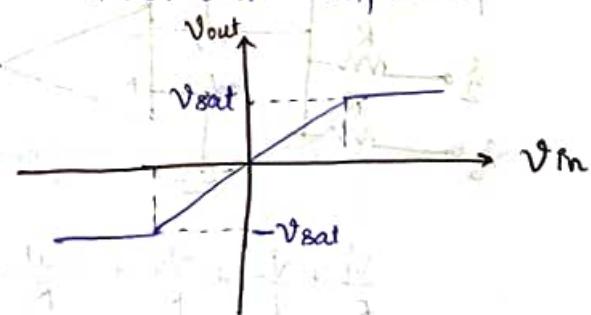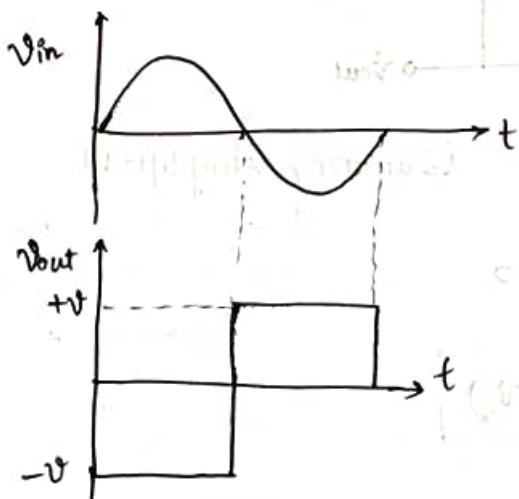→ It is required to use a full-up resistor in comparator circuits.






Voltage Follower Circuit

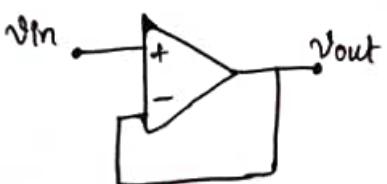

$$V_{out} = V_{in}$$

→ Also called as the buffer.




1/4

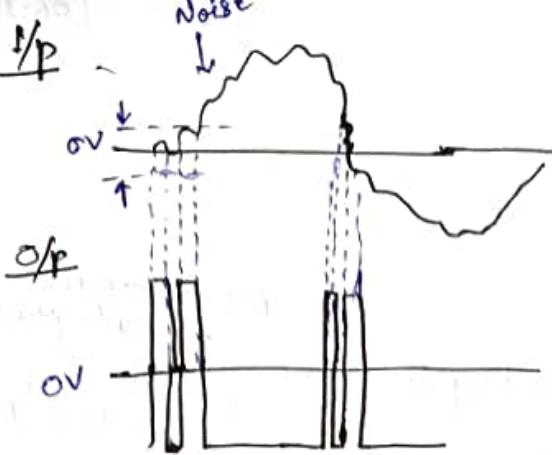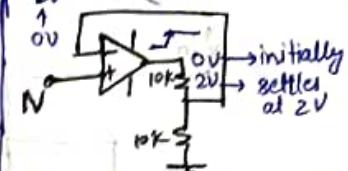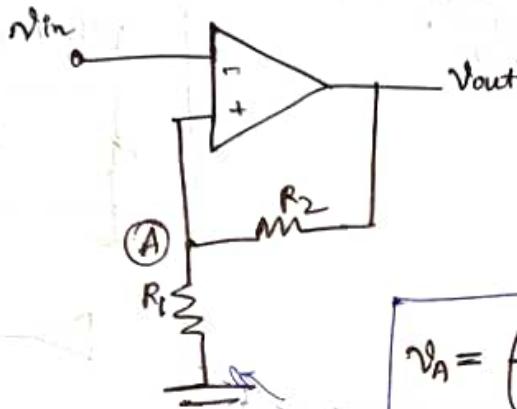Negative feedback $V_{out} \uparrow \Rightarrow (V_+ - V_-) \downarrow$ Increase in V_{out} causes diff. $(V_+ - V_-)$ decrease

→ "Schmitt Trigger Circuit"

$$V_A = \left(\frac{R_1}{R_1 + R_2} \right) V_{out}$$

$$V_H = V_A \\ V_L = -V_A$$

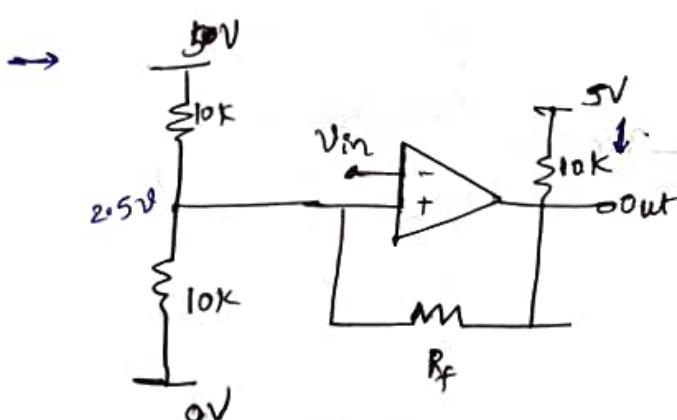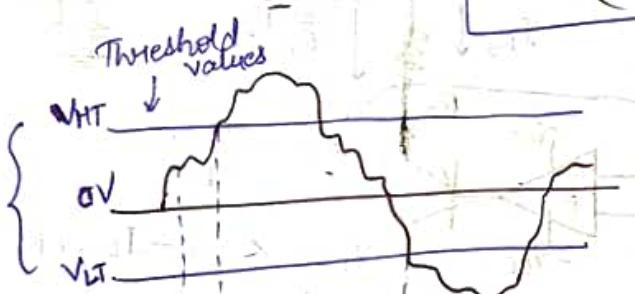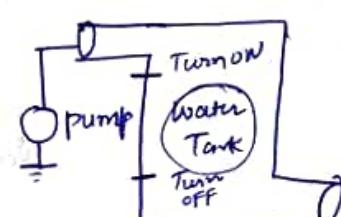

$$V_t(\text{set}) = 2.5V$$

$$V_{in} = 2.4V$$

$$\Rightarrow V_{out} = 5V \text{ (high)}$$

$$V_+(\text{modified}) = \text{Superpose}(2.7V)$$

$$V_{in} \rightarrow 2.8$$


$$V_{out} = 0$$

$$V_+(\text{mod}) = 2.3V$$



Used to
automate
(gains memory)
Responds
only to i/p, not noise


Current Source

Using opamps

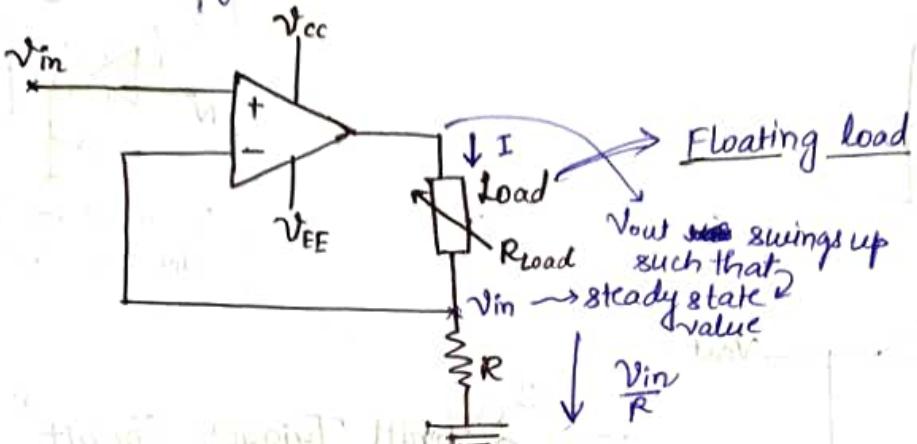
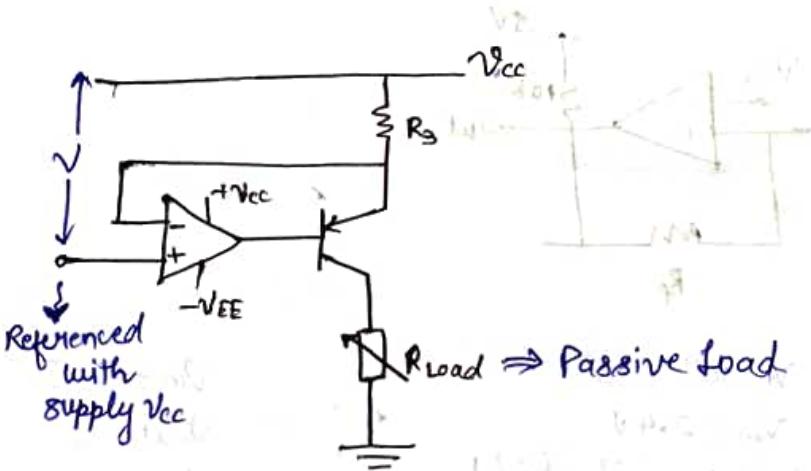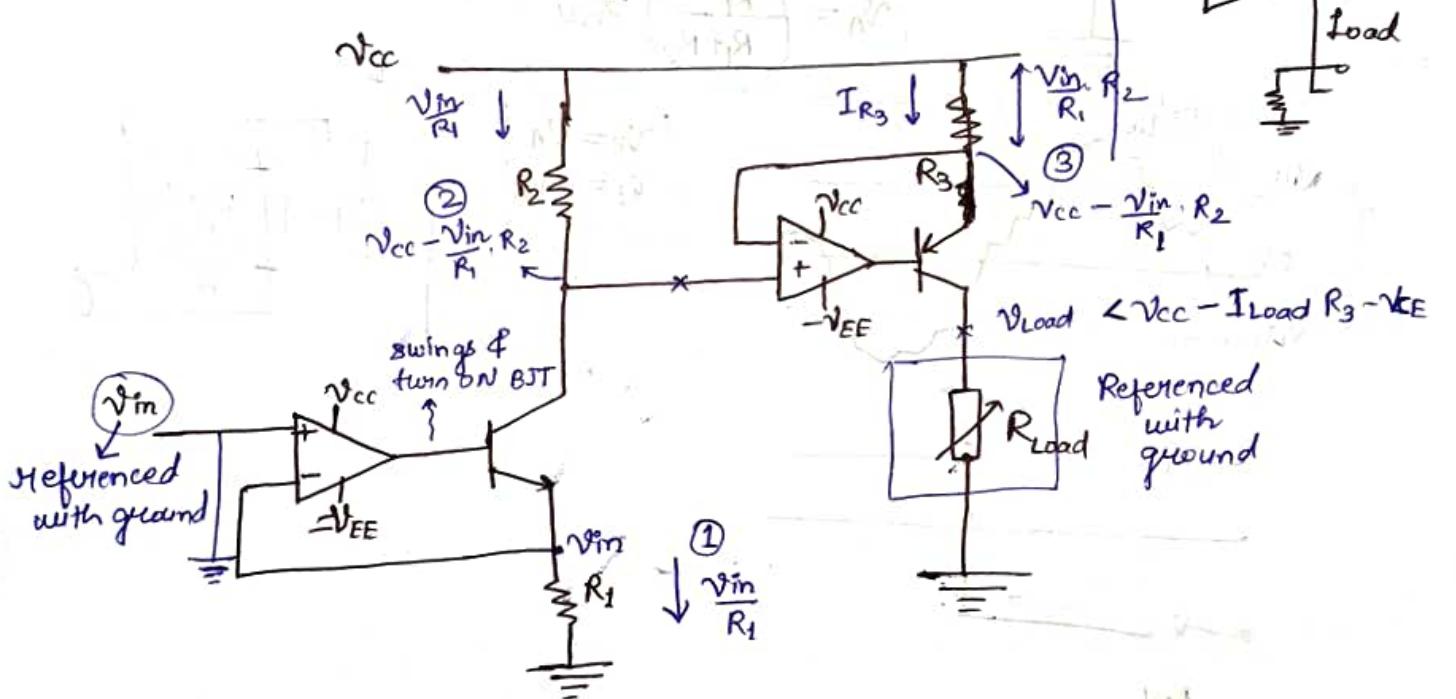
$$I_{\text{Load}} = \frac{V_{\text{in}}}{R}$$




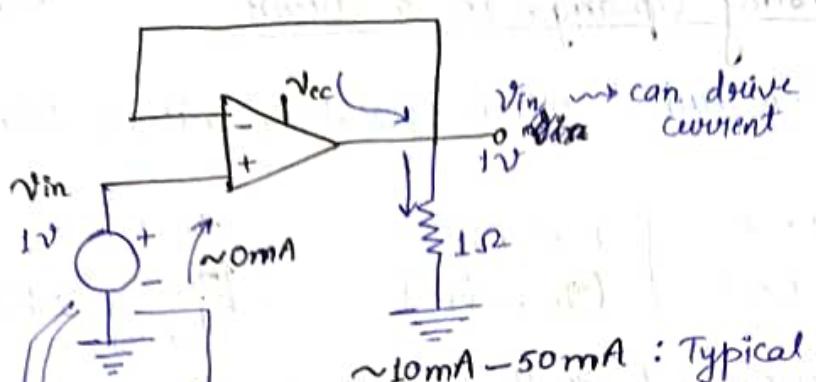

If we try to drive current, voltage will collapse.
Unaffected, whatever we connect at the output

Voltage follower circuit
↓
increases current delivering capability

⇒ Application:

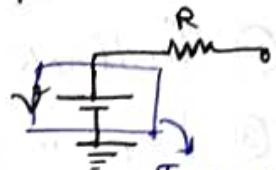

To measure, we give zero current



- Used in circuits with a weak voltage source (not capable of drawing current from the voltage source)
- Current is drawn from the biasing voltage applied.

Power Booster / Voltage Regulator

Control parameters: $R_1, R_2, V_{control}$

- Ratio of $R_1 \& R_2$ [$R_1 + R_2 \rightarrow$ very large $\approx 100\text{ k}\Omega$]
- $V_{control} \rightarrow V_Z$

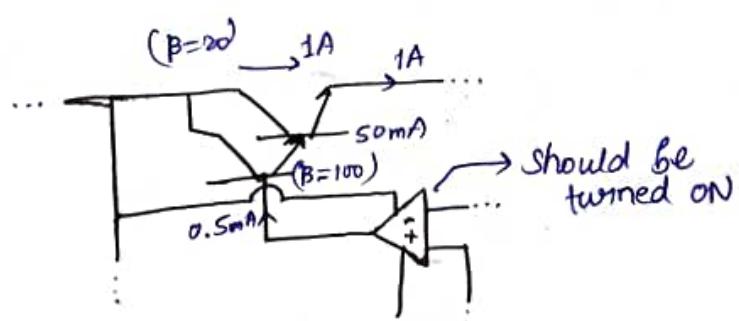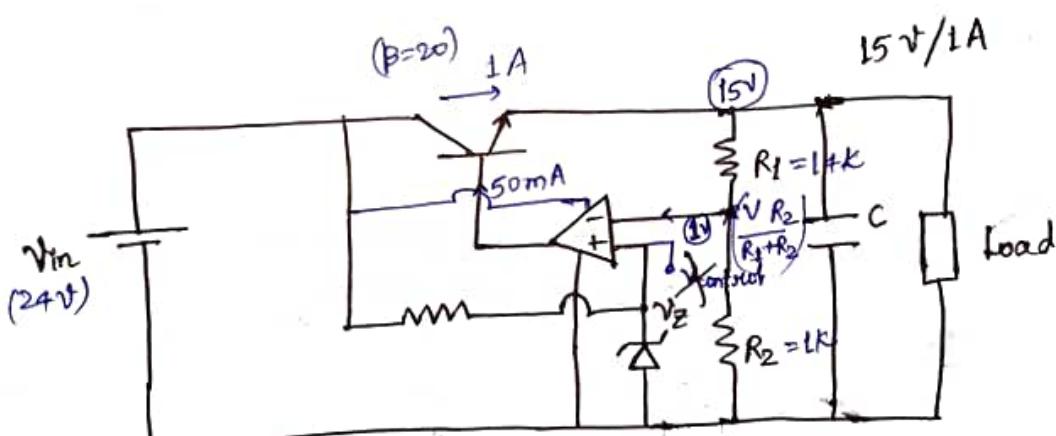$15\text{ V}/1\text{ A}$
Voltage whatever is Load
max. current



If MOSFETs were used
LDO
Low Drop Out Regulator


Darlington pairs are used to make sure opamp is capable of driving the transistor.

Basic Cautions when Using Op-amps in a Circuit

- ① Opamp follows 2 "golden rules" when operating within bias voltages.


Typically: $V_{CC} = -1.5V$ | Rail-Rail

$V_{EE} = +1.5V$ | $(V_{CC}, -V_{EE})$

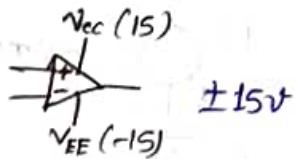

- ② Feedback must be arranged so that it is negative.

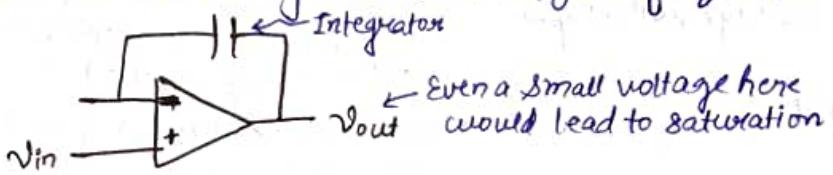- ③ Negative feedback should be present at (zero freq) ac.



- ④ Opamp tries to reduce the differential voltage ($V_{in+} - V_{in-}$).

The circuit should be such that it allows this.




OCs & oscillations
gain & feedback
negative feedback



Departure from Ideal Opamp Characteristics

Ideal Characteristics:

① Input impedance = ∞ .

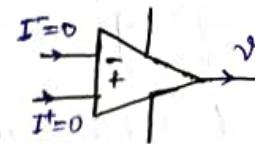


② Output impedance = 0.

↳ Limit on how much current can be drawn

③ Open loop voltage gain = ∞ .

$$\text{gain} = \frac{V_o}{(V_+ - V_-)}$$

④ Common mode voltage gain = 0.

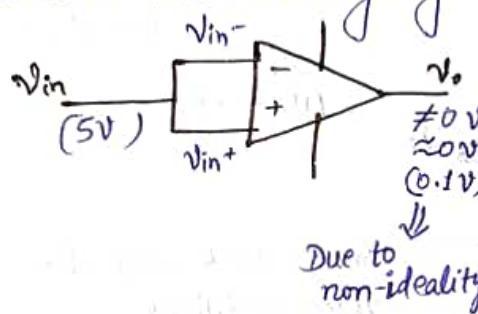

$$\frac{V_o}{V_{in}} = 0$$

$$V_{in-} + V_{in+} = V_{CM}$$

$$A = \frac{V_o}{V_+ - V_-}$$


$$(V_+ \neq V_-)$$

(offset o/p voltage)

⑤ Opamp's output swings instantaneously.

↳ slew rate = 10^6 V/sec . (Rate at which o/p swings)

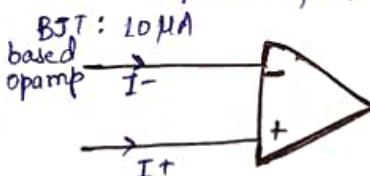
JFET: 10 pA to 10 fA → choose this input current



Input offset current ↳ critical
affects output

① If input current should be low, choose JFET opamps ($I_{in} < 100 \text{ pA}$).

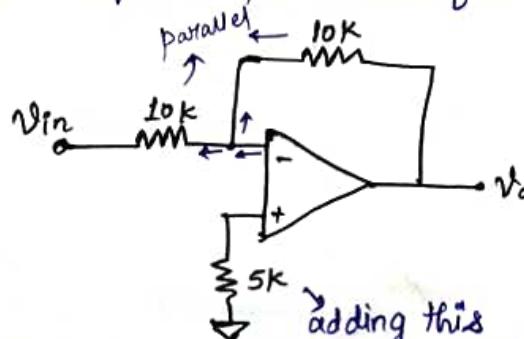② Input offset current will affect the output → Difference in the input current of both terminals of the opamp.
→ Try to make input impedances equal.



→ has little bit resilience towards input offset current.

→ Better than the previous circuit.

adding this resistor provides better resilience for input offset current.

- ③ Input impedance: (If the opamp circuit to be used is sensitive to input impedance)
- JFET opamp (good)
- BJT opamp (not good).


- ④ Common mode input range.

- ⑤ Slew rate

Lower slew rate \rightarrow slow opamp

\Rightarrow low Bandwidth (BW)

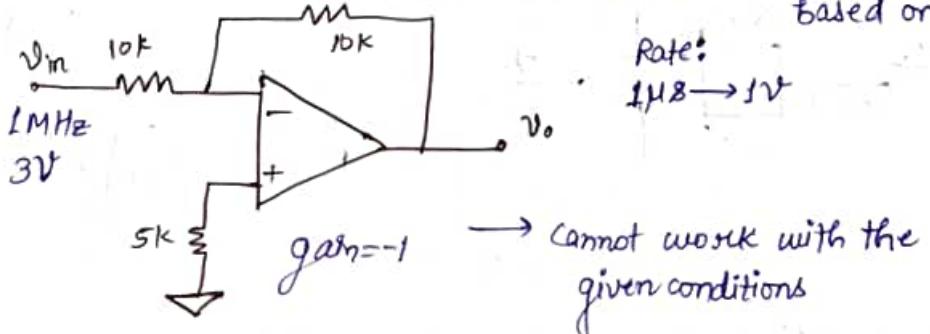\rightarrow opamp should be chosen with adequate bandwidth based on the application.



①

②

③

④

⑤

⑥


⑦

⑧

⑨

⑩

① Input Bias Current

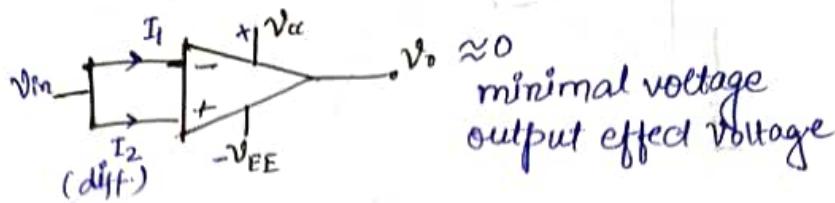


Slew rate: how fast the output swings ($\text{V}/\mu\text{s}$ typically).

$\rightarrow -1\text{V per } \mu\text{s}$.

\rightarrow How fast the output swings.

② CMRR - Common Mode Rejection Ratio

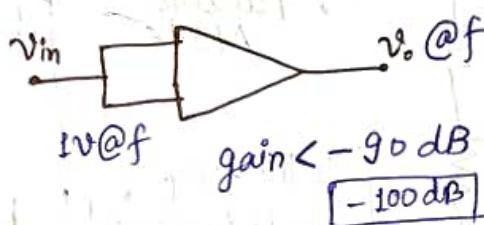

Say, gain $< -100 \text{ dB}$


$$20 \log(x) = -100 \text{ dB}$$

$\Rightarrow x = 10^{-5} \rightarrow$ gain applied to common mode voltage

At the o/p, the effect of CM voltage is reduced by a factor of 10^{-5} .

③ PSRR - Power Supply Rejection Ratio




$\approx -50 \text{ dB}$

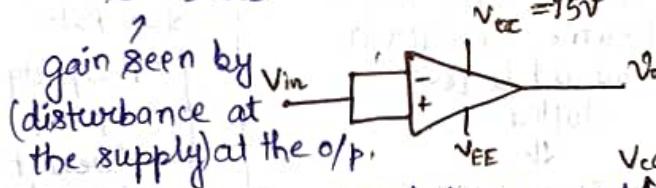

- Having a high PSRR helps in avoiding the transfer of disturbance from the supply to the output.


④ Gain-Bandwidth Product

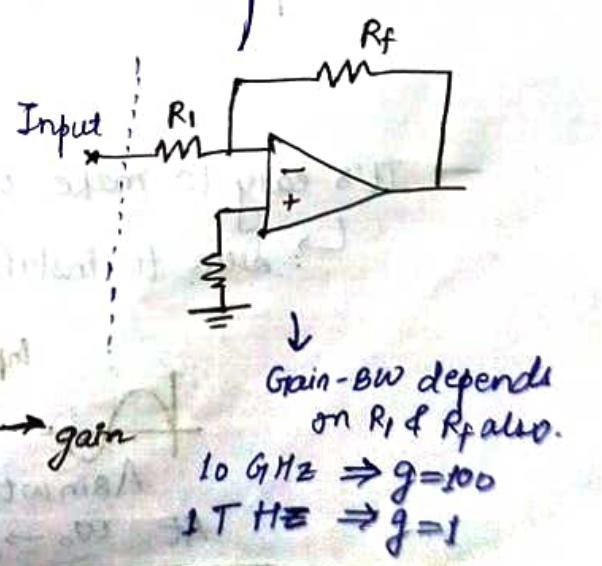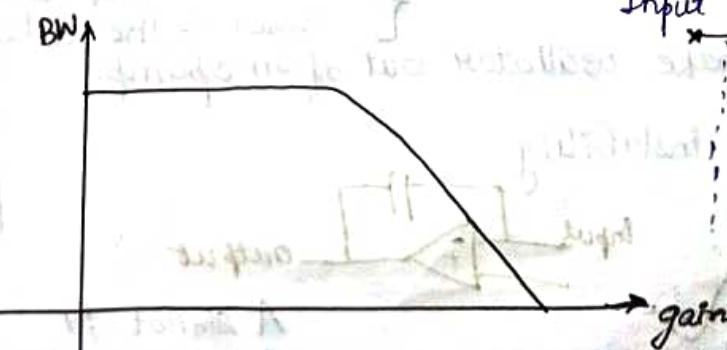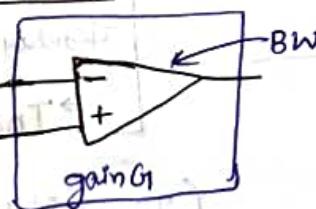→ For higher gain, BW of opamp may not be same when compared to BW for lower gain.



$$10 \text{ GHz} \Rightarrow g=100$$


$$1 \text{ THz} \Rightarrow g=1$$

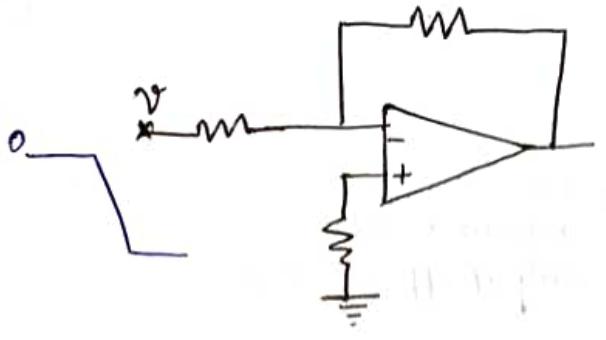

Delayed output voltage
depending upon the
slew rate of the
opamp.

I_p: zero-crossing

O/p: delayed & attenuated

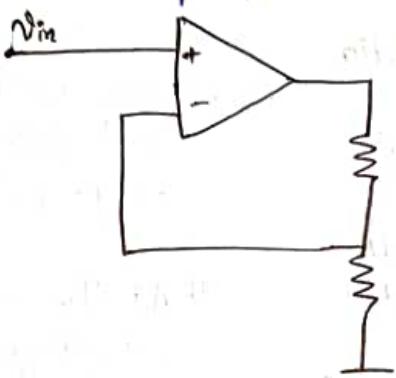


Ways to damage Opamp:

: Failure Mode

→ Give high voltage to
V_{CC} & V_{EE} or
Invert V_{CC} & V_{EE}
voltages

→ Frequency → X
↳ Opamp will
underperform

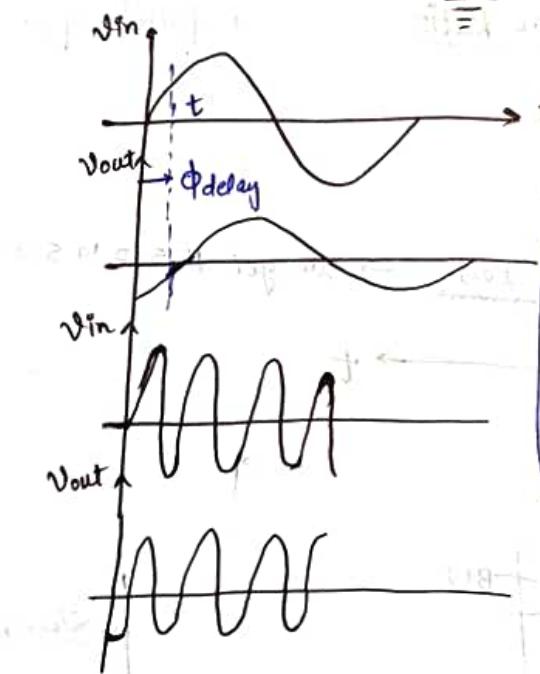Slew Rate
↳ Property of
opamp
→ doesn't
depend on
i/p



If the freq. of
V_{in} is increased
to a specific value,
the o/p would be
delayed by the
same amount if it
would be 180°
shifted

↳ cause circuit to behave
like +ve feedback
even when ckt. is
-ve feedback

→ saturation

Φ_{delay} ≈ 0 : good situation

Φ_{delay} = 180°


↳ Instability of an opamp

{ To avoid this, i/p should not be given
closer to the delay frequency. }

↳ saturation

→ It's easy to make oscillator out of an opamp.

↳ Due to instability.

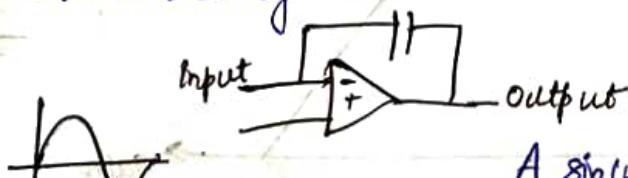

A sin ωt

At $\omega_0 \rightarrow$ particular freq.




$A \sin(\omega t - \phi)$

$A \sin(\omega t - \phi)$

$= -A \sin \omega t \Rightarrow$ Oscillator

[This concept can
be used to make
oscillator]


Q

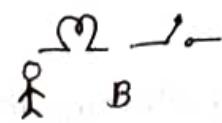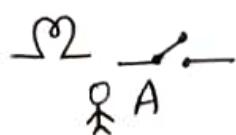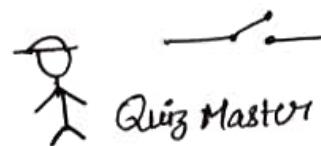

If team A presses switch, its bulb will glow only. Even if B tries to press its switch, there will be no change in state of both the switches, and vice versa.

Quiz Master ~~also~~ has a master switch to reset ~~the~~ both switches.

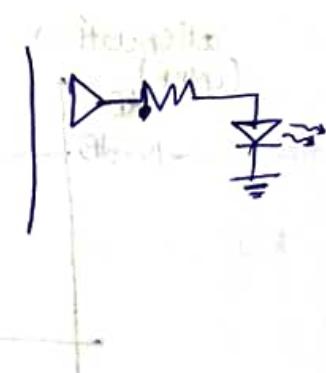Design an opamp-circuit for this functionality.




t_{fall}

99% ②
A1/2E of 0.1%



100% + 10% ③

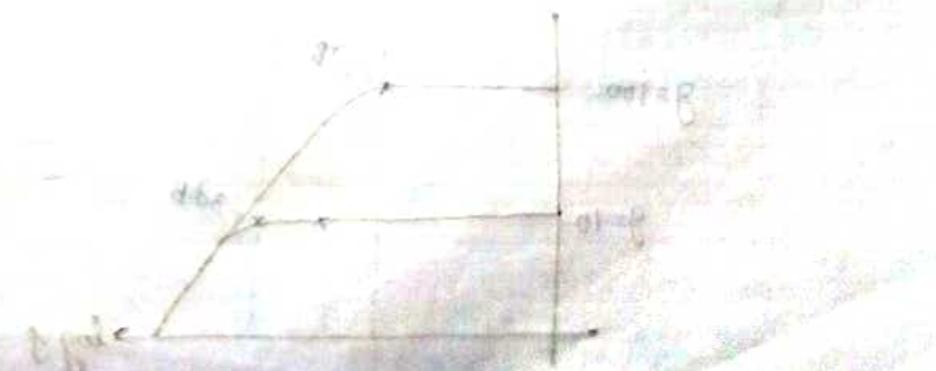



$$CMV = \frac{v_1 + v_2}{2}$$

$$DMV = v_1 - v_2$$

Differential mode

① CMRR is a function of frequency


↓
attenuation
(100 dB)

Common mode

20 dB
↓
decay



$10^2 \rightarrow 10^{-5} V$
CMV output
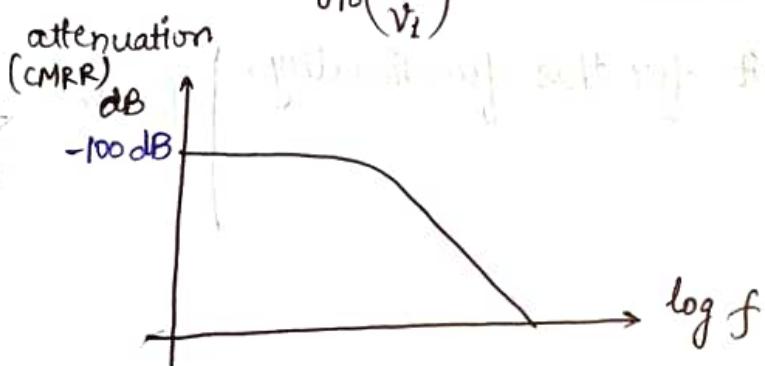
$$20 \log_{10} \left(\frac{V_o}{V_i} \right)$$





② PSRR

↓ 70 to 90 dB

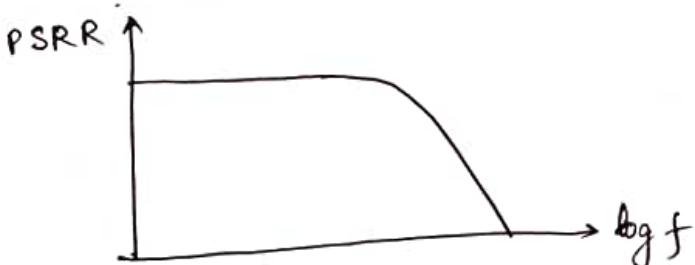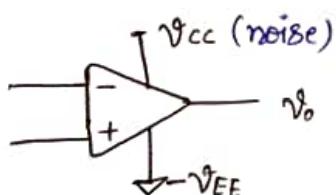

③ Gain-BW Product

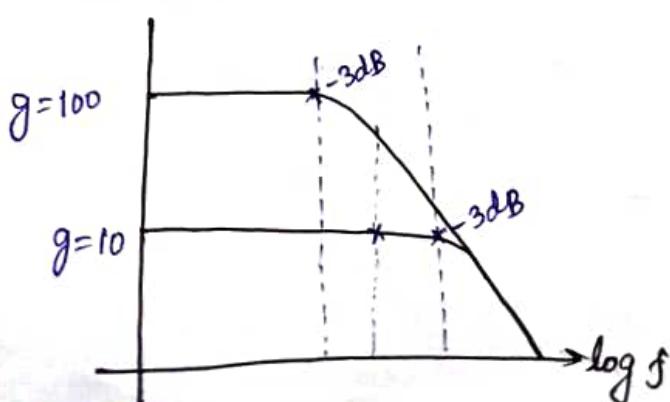

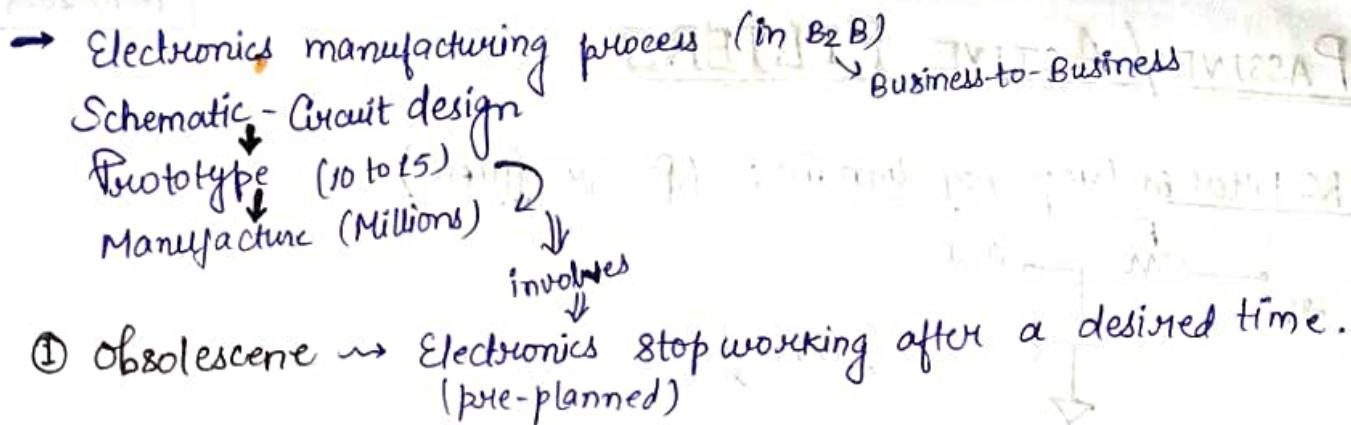


- ① Obsolescence → Electronics stop working after a desired time.
(pre-planned)
- ② Not selling enough
- ③ Lost Schematics
- ④ Manufacturer out of Business.
↳ e.g., LTspice (Linear Technology)

lead time
(typically 52 weeks)

Traitorous Eight

PASSIVE / ACTIVE FILTERS

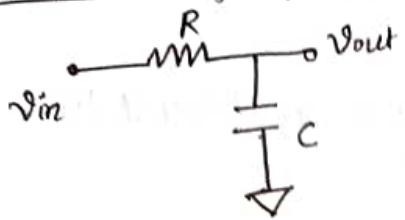RC Filter in frequency domain: (Passive filter)




$$Z_o(s) = \frac{1}{sC}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC} = \frac{1}{1 + s/w_p}$$

$$\omega_p = -\frac{1}{RC}$$

$$\omega_p = |\omega_p| = \frac{1}{RC}$$

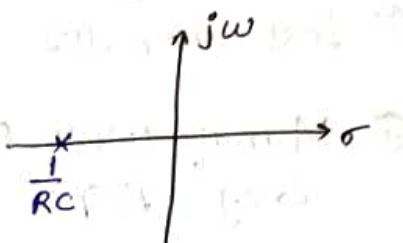

$$H(s) = \frac{1}{1 + sRC} \rightarrow \text{low pass filter}$$

$s = j\omega$ (to look at steady state response)

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$

$$\omega = 0 : \frac{|H(j\omega)|}{1} \quad \frac{20 \log |H(j\omega)|}{0} \quad \frac{\angle H(j\omega)}{0}$$

$$\omega = \frac{1}{RC} : 0.707 \quad -3.01 \quad -45$$

$$\omega = \frac{2}{RC} : 0.447 \quad -6.99 \quad -63$$


$$\omega = \frac{4}{RC} : 0.243 \quad -12.30$$

$$\omega = \frac{6}{RC} : 0.164 \quad -15.66$$

$$\omega = \frac{20}{RC} : 0.05 \quad -26.03 \quad -87$$


$$\omega = \frac{40}{RC} : 0.025 \quad -32.04$$
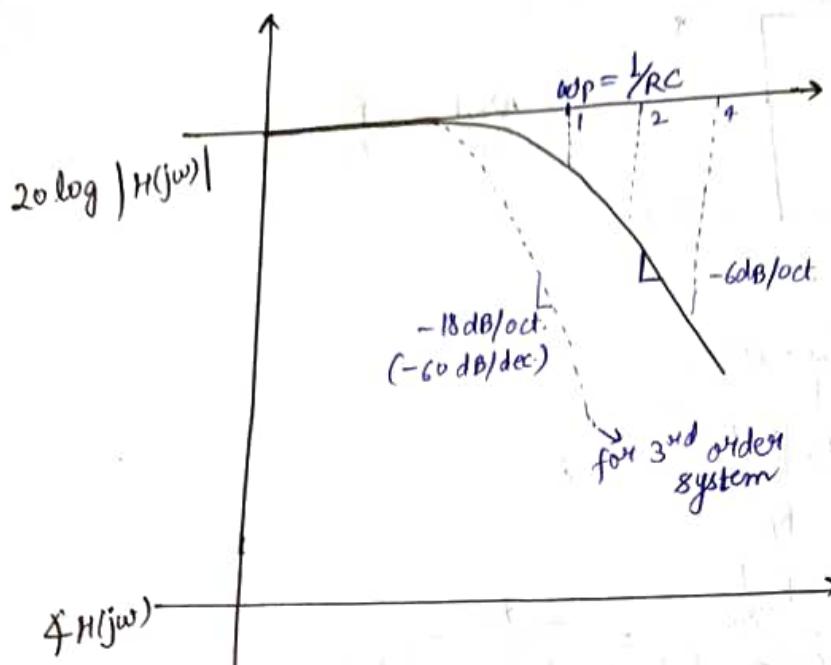
$$\omega = \frac{200}{RC} : 0.005 \quad -46.02 \quad -89.71$$




for doubling of freq ($> f_p$)
 \downarrow pole freq.
decrease of 6dB

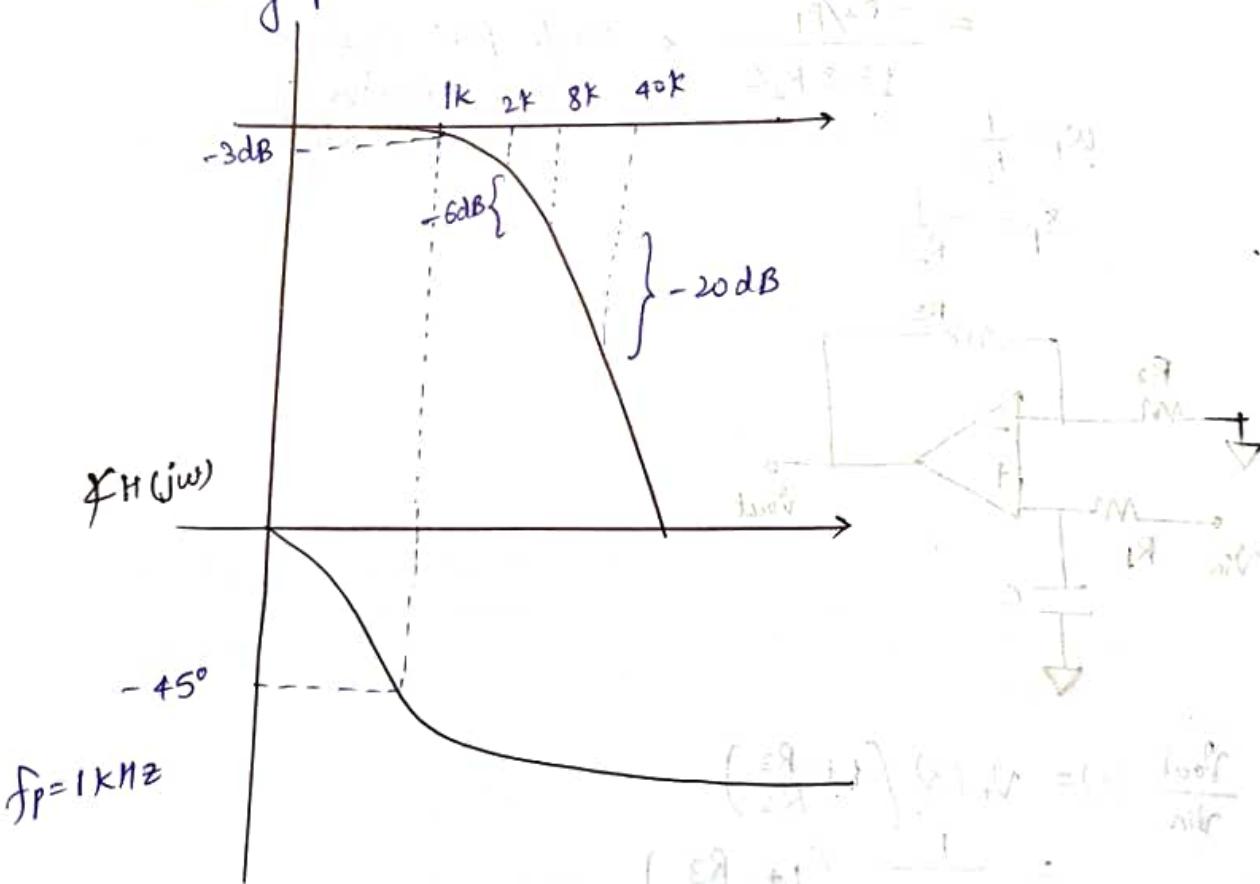$[-6\text{dB/octave}]$
 \downarrow for 1st order system
or
 -20dB/decade.



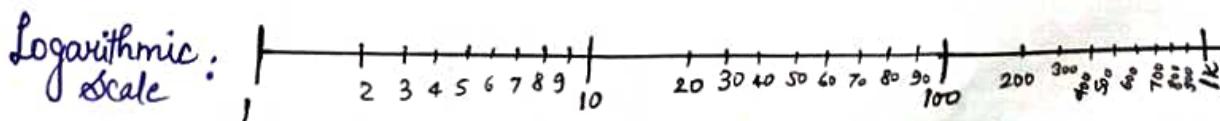\rightarrow To accomodate a large frequency with a good resolution at lower frequencies : Use a semilog graph (logarithmic scale).




on linear scale:

On log scale:

$\sim 20\text{dB/decade}$

Active filters

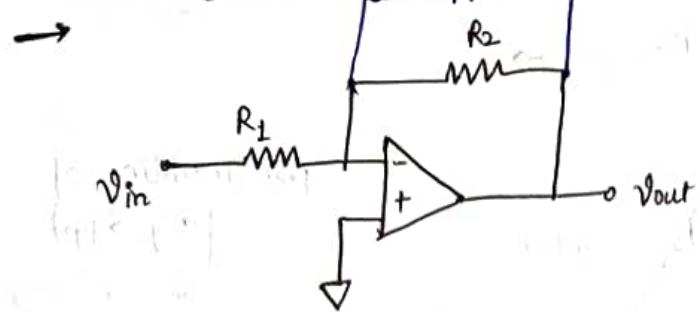

$$\frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$$

After adding the capacitor,

$$\frac{v_{out}}{v_{in}}(s) = -\frac{R_2 \parallel \frac{1}{sC}}{R_1}$$


$$= -\frac{\frac{1}{sC}}{R_1 \left(R_2 + \frac{1}{sC} \right)} = \frac{-\frac{1}{sC}}{R_1 (1 + sR_2C)}$$

$$= \frac{-R_2/R_1}{1 + sR_2C} \quad \leftarrow \text{single pole system}$$

(-6 dB/octave
-20 dB/decade)

$$\omega_p = \frac{1}{R_2 C}$$

$$\delta_p = -\frac{1}{R_2 C}$$

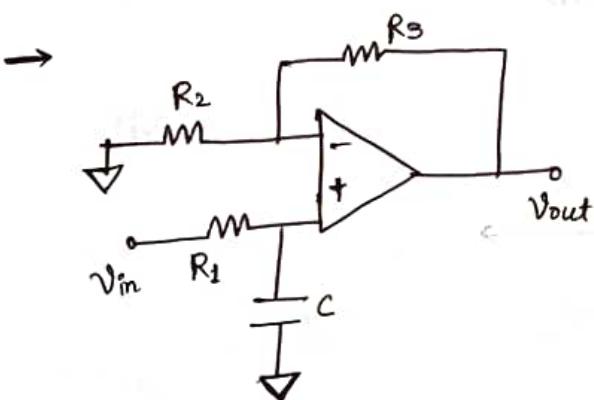


$$\frac{v_{out}}{v_{in}}(s) = V_+(s) \left(1 + \frac{R_3}{R_2} \right)$$

$$= \frac{1}{1 + sR_1C} \left(1 + \frac{R_3}{R_2} \right)$$

Low Pass Filter [Ideal LPF]

$H(s)$: filter transfer function

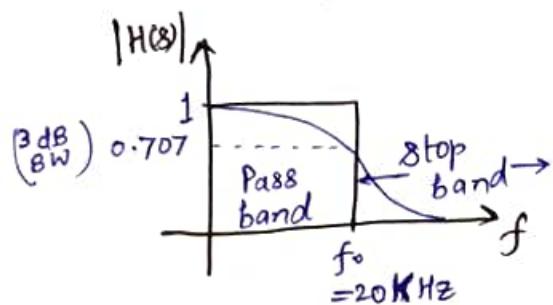

"Brick-wall Response"


↳ cannot be implemented in practice

→ Abrupt change from pass band to stop band, ideally.


$f < f_0 \Rightarrow |H(s)| = 1$ (filter allows the signals to pass through)
 $f > f_0 \Rightarrow |H(s)| = 0$ (filter rejects signals $f > f_0$)

→ Non-idealities:

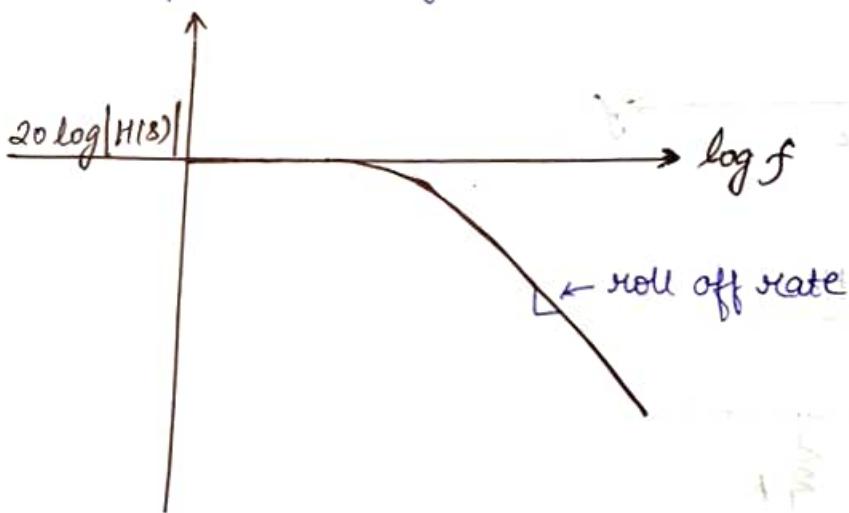
- ① Pass band is not flat
- ② No abrupt transition from pass band to stop band.
(gentle transition)




High Pass Filter (HPF)

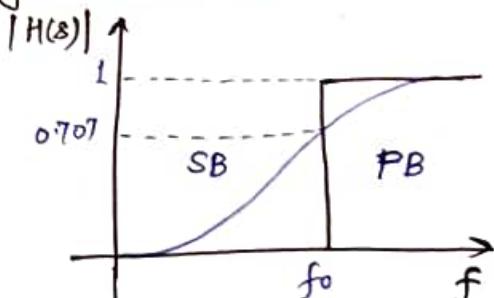


Band Pass filter

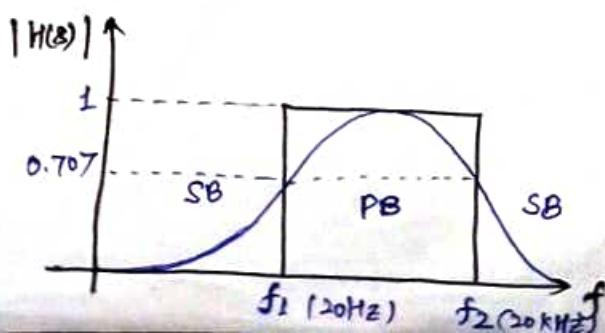


Band stop filter

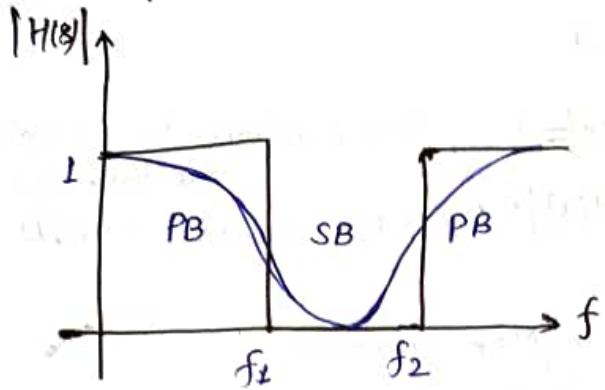

Notch filter

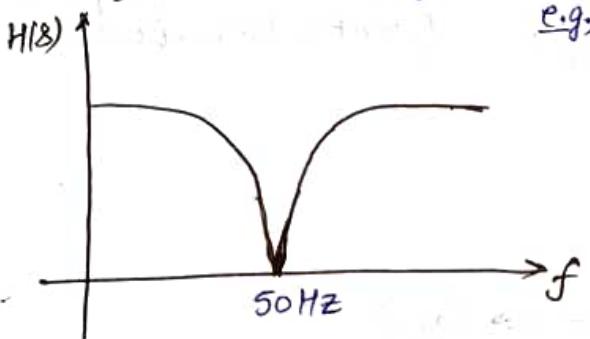

1st order Passive HPF

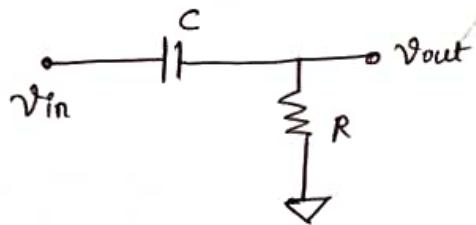

$$\frac{V_{out}}{V_{in}}(s) = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} = H(s)$$

Poles = 1, $\omega_p = -\frac{1}{RC}$

Zeros = 1, $\omega_z = 0$ (DC)

$$|H(s)|_{\omega=0}$$

notch, anti-resonance



$$\text{Eq. } G(s) = 1 + \frac{s}{\omega_z}$$

$$|G(s)| = \sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$$

$$\omega=0 : |G(s)| = 1 \quad \varphi = 0$$

$$\omega=\omega_z : |G(s)| = \sqrt{2} \quad \varphi = +45^\circ$$

$$\omega \uparrow : |G(s)| \uparrow$$

$$20 \log |G(j\omega)|$$

$$+3\text{dB}$$

Pole

zero

$$\text{Slope : } -20\text{dB/dec}$$

$$-6\text{dB/oct}$$

$$\omega=\omega_0 : -3\text{dB}$$

$$\varphi_{\omega=\omega_0} : -45^\circ$$

$$\varphi_{\omega \rightarrow \infty} : -90^\circ$$

$$+20\text{dB/dec}$$

$$+6\text{dB/oct}$$

$$+3\text{dB}$$

$$+45^\circ$$

$$+90^\circ$$

$$+20\text{dB/dec}$$

$$+6\text{dB/octave}$$

$\log f$


$$\omega \rightarrow \infty : \varphi \rightarrow +90^\circ$$

HPF :


$$H(s) = \frac{8RC}{1+8RC}$$

$$\omega_z = 0$$
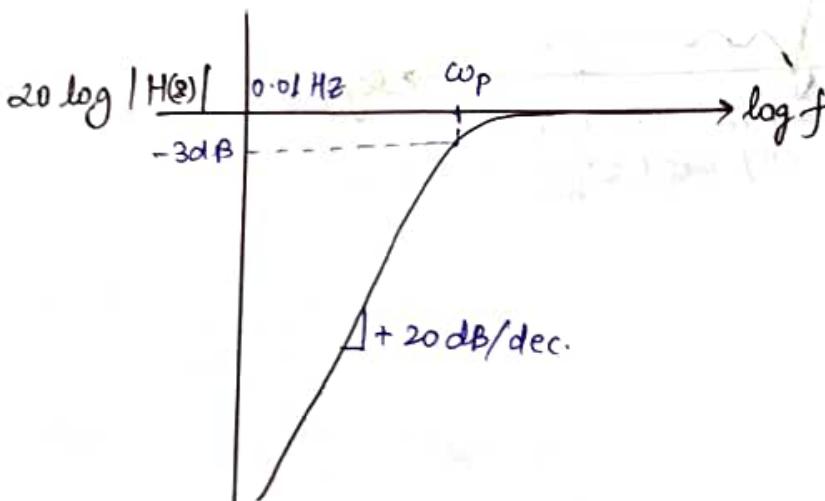
$$\omega_p = \frac{1}{RC} (= 1\text{kHz})$$




Active HPF

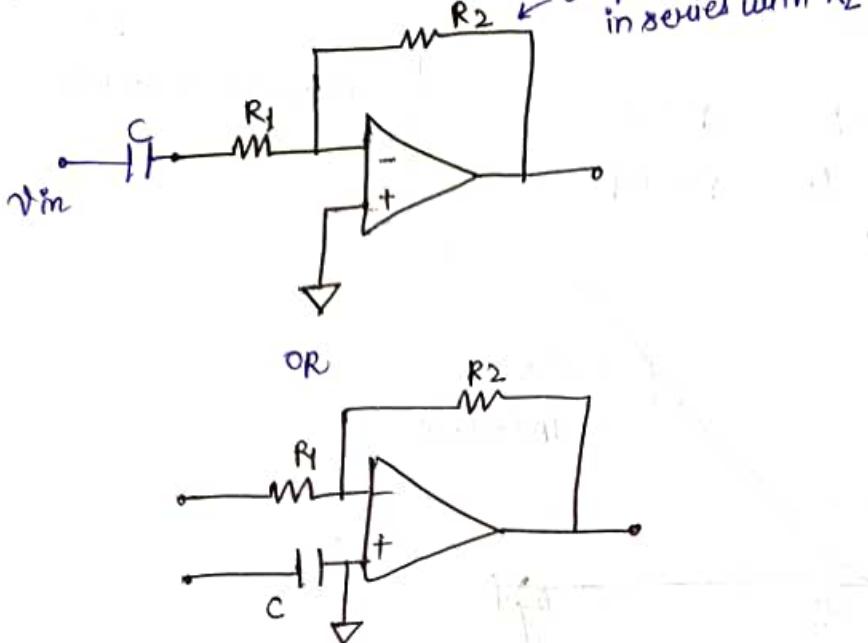

LPH



$$H(s) = \frac{s^2 + ()s + ()}{s^2 + ()s + ()}$$

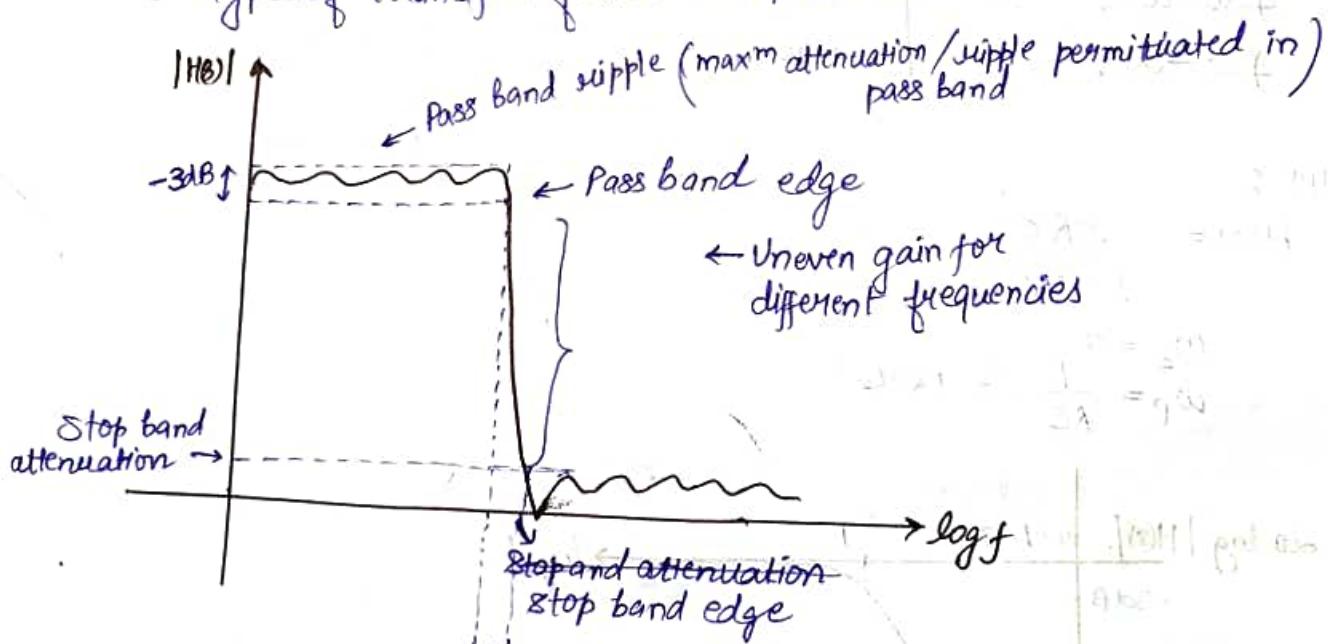- Types of transfer functions: Butterworth




MULTIVIBRATORS

Smith Trigger:

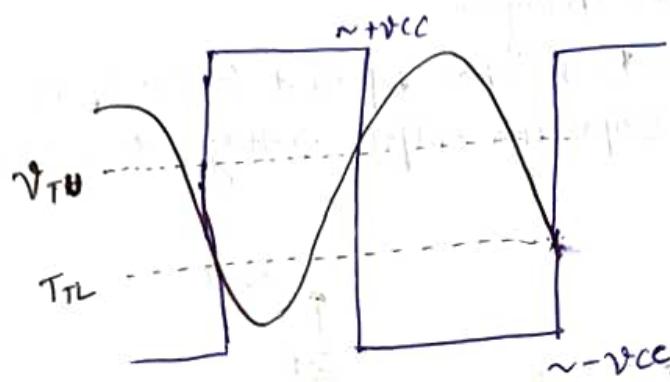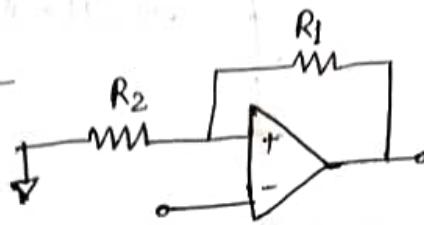

This Smith trigger is called
Bistable multivibrator



Astable Multivibrator:

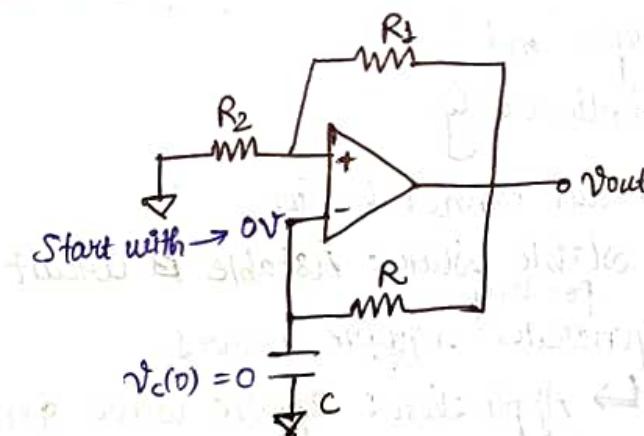

\downarrow
 $V_{out} : +V_{sat}$ or $-V_{sat}$
 ↳ Indetermined
 Start with $V_{out} = +V_{sat}$

$+V_{sat}$: Highest saturation value (close to V_{CC})

$-V_{sat}$: Lowest saturation value

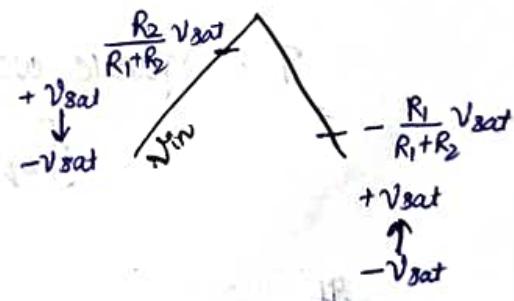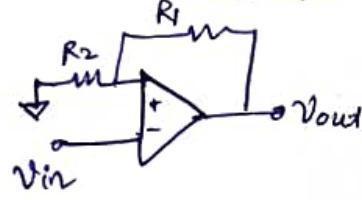



$$V_{TU} = \frac{R_2}{R_1 + R_2} V_{sat.} = \beta V_{sat}$$

$$V_{TL} = -\frac{R_2}{R_1 + R_2} V_{sat.} = -\beta V_{sat}$$

Initially,
 $V_C^{(0)} = 0V$

$$V_{out}(0) = +V_{sat}$$

$$V_+ = +\beta V_{sat}$$

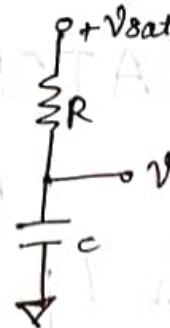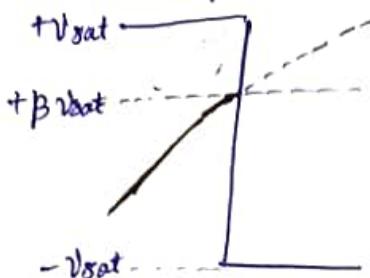



$$V_c(t) = +V_{sat} (1 - e^{-t/RC})$$

$$T = RC$$

→ capacitor charges.

When V_c reaches $+\beta V_{sat}$ ($= V_{TU}$), it trips the output voltage to $-V_{sat}$.

Afterwards,

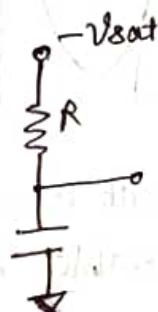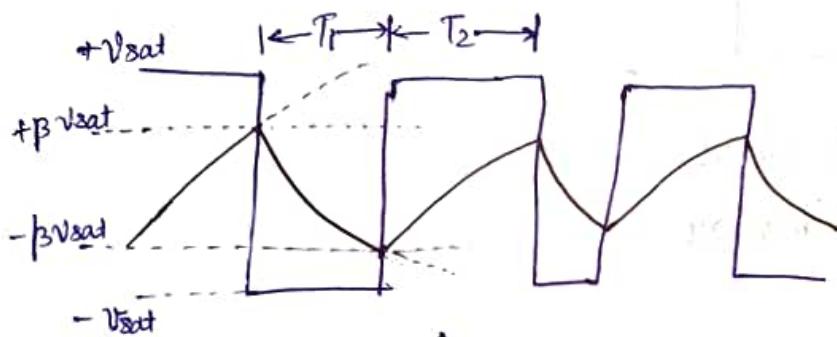

↳ Capacitor discharges

↳ Capacitor charges and discharges continuously.

↳ The circuit cannot be in one stable state: Astable ~~circuit~~ circuit for long

↳ Generates square waves.

↳ Application: square wave generator.

T : Square wave time period = $T_1 + T_2$

$$f_{sq} = \frac{1}{T_1 + T_2}$$

if,

$$V_i = V_{initial}$$

V_f : Voltage at which the capacitor is being charged / discharged.

then,

$$V_c(t) = V_f - (V_f - V_i) e^{-t/RC}$$

↳ Instantaneous.

$$V_c(t) = V_{initial} - \frac{V_f - V_{initial}}{1 + e^{-t/RC}} = V_{initial}$$

$$\text{for } 0 \rightarrow A$$

$$A - (A - 0)e^{-t/RC}$$

$$= A(1 - e^{-t/RC})$$

But, here $V_{initial} \neq 0$.

T₁:

$$V_f = -V_{sat}$$

$$V_i = +\beta V_{sat}$$

The capacitor is ~~atmos~~ actually getting charged towards $-V_{sat}$; in the meanwhile it is getting charged

$$V_c(t) = -V_{sat} - (-V_{sat} - \beta V_{sat}) e^{-t/T_1}$$

$$\text{At } t=T_1, V_c(T_1) = -\beta V_{sat} = -V_{sat} - (-V_{sat} - \beta V_{sat}) e^{-T_1/T_1}$$

$$\Rightarrow -\beta V_{sat} = -V_{sat} + (V_{sat} - \beta V_{sat}) e^{-T_1/T_1}$$

$$\Rightarrow e^{-T_1/T_1} = \frac{V_{sat} - \beta V_{sat}}{V_{sat} + \beta V_{sat}} = \frac{1 - \beta}{1 + \beta}$$

$$\Rightarrow -\frac{T_1}{T_1} = \ln \left(\frac{1 - \beta}{1 + \beta} \right)$$

$$\Rightarrow T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

Similarly,

$$T_2 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

R_1, R_2 should be in range of the current supplying capability of the opamp.



$$T = T_1 + T_2 = 2RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$




$$D = \frac{T_{on}}{T_{on} + T_{off}} \times 100\%$$

Duty cycle

To get triangle wave from square wave:

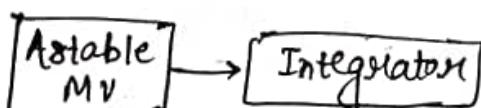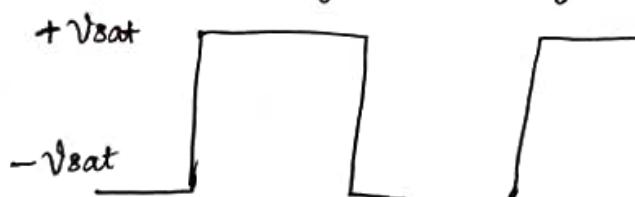

: Add an integrator circuit

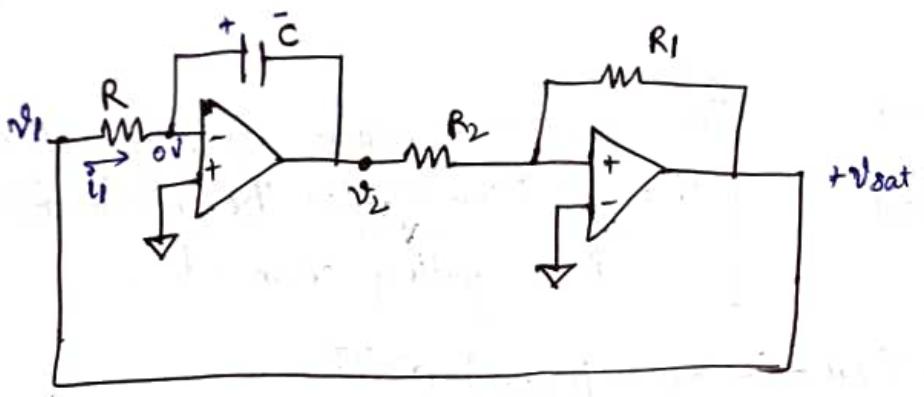


$$i_1 = \frac{v_1}{R}$$

$$v_c(t) = \frac{1}{C} \int i_1 dt$$



$$v_2 = -\frac{1}{C} \int \frac{v_1}{R} dt$$

$$= \frac{1}{RC} \int v_1 dt$$

$$+ \frac{v_{sat}}{RC} \cdot t \quad \left| - \frac{v_{sat}}{RC} \cdot t \right.$$

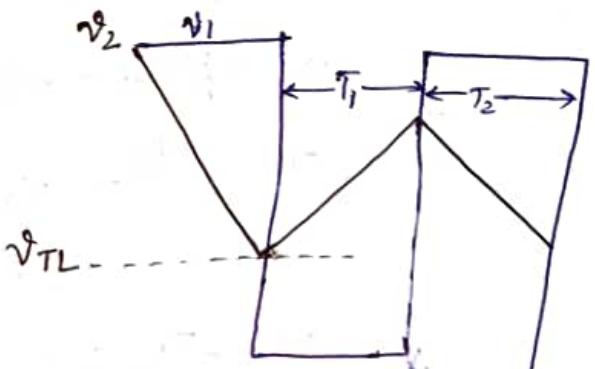

555 Timer IC (NE555)

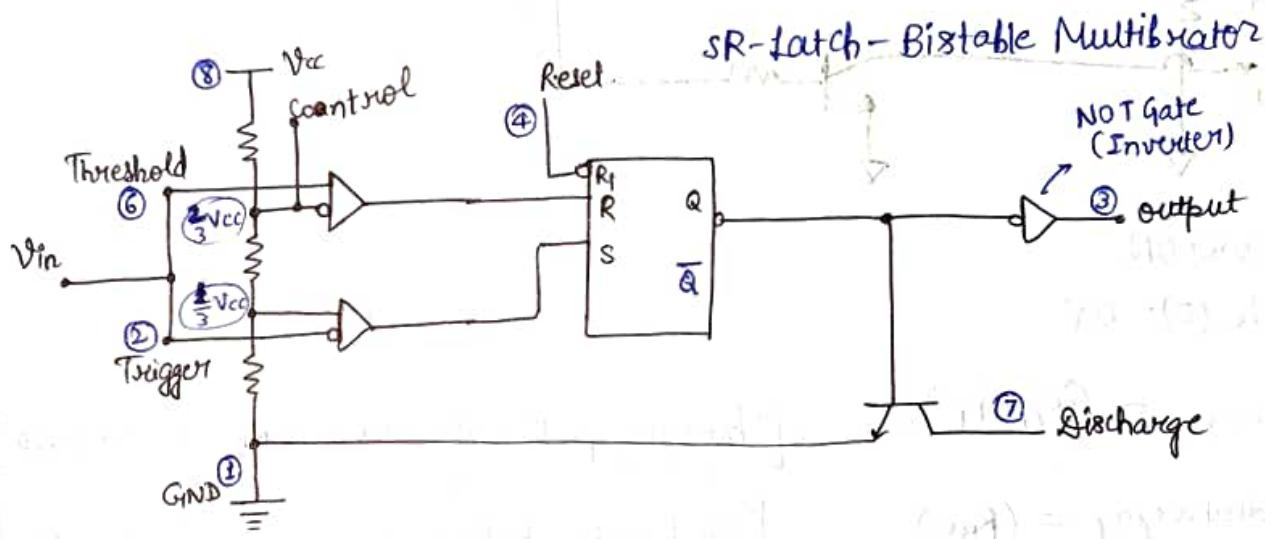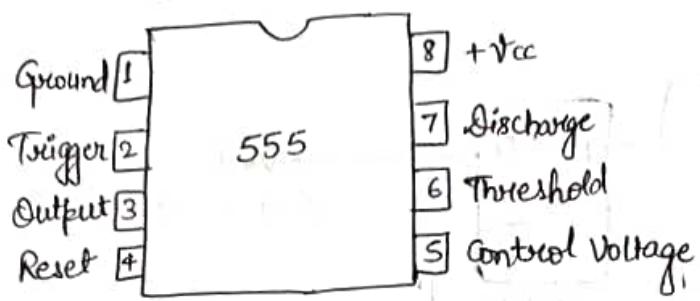

$V_{in} < \frac{1}{3} V_{cc}$: Trigger: ON

$\frac{1}{3} V_{cc} < V_{in} < \frac{2}{3} V_{cc}$: Thresh: OFF, Trig: OFF


$V_{in} > \frac{2}{3} V_{cc}$: Thresh: ON

→ Connect Reset (RESET) to V_{cc}

↳ Used as Enable pin

→ $Q=0, \bar{Q}=1$: Transistor (BJT) : ON

↳ Discharge \rightarrow GND

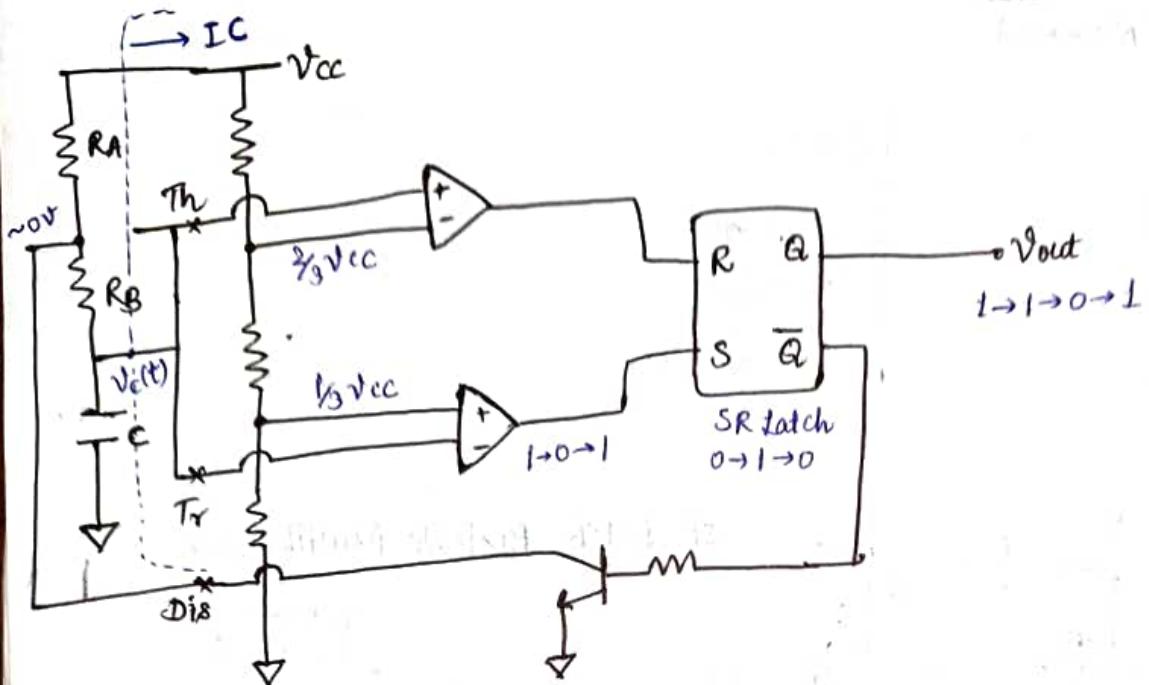


At power ON,

$$V_c(0) = 0V$$

$$T_{\text{charging}} = (R_A + R_B)C \quad [\text{Charging path: } V_{CC} \rightarrow R_A \rightarrow R_B \rightarrow C \rightarrow GND]$$
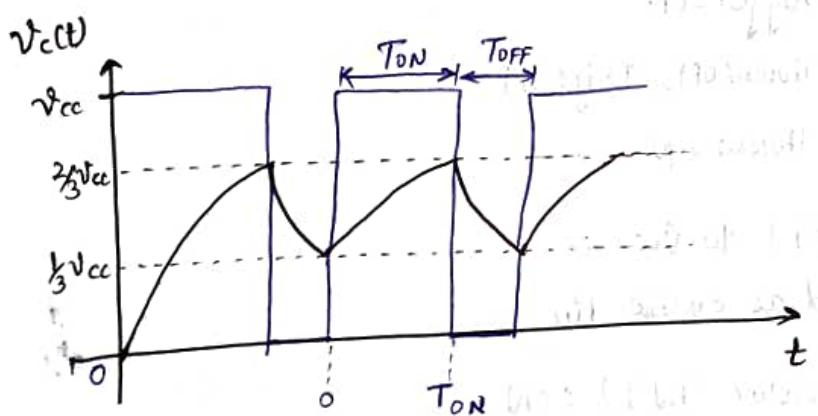
$$T_{\text{discharging}} = (R_B C) \quad [\text{Discharging path: } C \rightarrow R_B \rightarrow GND (\sim 0V)]$$



Charging phase:

$$V_c(t) = V_f - (V_f - V_i) e^{-t/T_{ch}}$$

$$V_c(t) = V_{CC} - (V_{CC} - \frac{1}{3} V_{CC}) e^{-t/T_{ch}}$$

$$\text{At } t = T_{on}, \quad V_c(t) = \frac{2}{3} V_{CC}$$

$$\Rightarrow \frac{2}{3} V_{CC} = V_{CC} - \frac{2}{3} V_{CC} e^{-\frac{T_{on}}{T_{ch}}}$$

$$\Rightarrow \frac{2}{3} V_{cc} e^{-\frac{t_{on}}{T_{ch}}} = \frac{1}{3} V_{cc}$$

$$\Rightarrow \frac{t_{on}}{T_{ch}} = \ln 2$$

$$\Rightarrow T_{on} = T_{ch} \ln 2 \approx 0.69 C (R_A + R_B)$$

$$\text{At } t = T_{off}, V_c(t) = \frac{1}{3} V_{cc},$$

$$V_c(t) = \frac{1}{3} V_{cc} = 0 - \left(0 - \frac{2}{3} V_{cc}\right) e^{-\frac{T_{off}}{T_{ch}}}$$

$$\Rightarrow \frac{V_{cc}}{3} = \frac{2}{3} V_{cc} e^{-\frac{T_{off}}{T_{ch}}}$$

$$\Rightarrow T_{off} = T_{ch} \ln 2 \approx 0.69 C R_B$$


~~Duty cycle, D.C.~~

$$\frac{R_A + R_B}{R_A + 2R_B}$$

$$T = T_{on} + T_{off}$$

$$\Rightarrow T = \frac{1}{f} = 0.69 C (R_A + 2R_B)$$

Monostable Multivibrator (using Opamp)

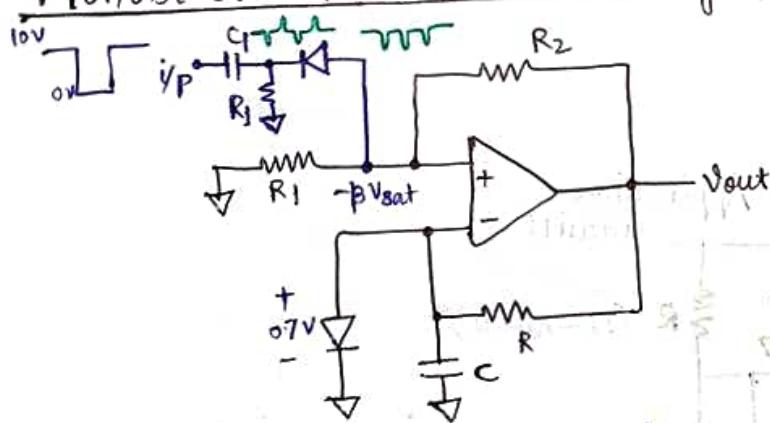

$$\text{Using } V_c(t) = V_f - (V_f - V_i) e^{-t/\tau},$$

Time period,

$$T = RC \ln \left(1 + \frac{R_1}{R_2} \right)$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$\bullet: V_i = 0.7V, V_f = -V_{sat}$$

$$V_c = -\beta V_{sat}$$

$$T_{ch} = RC \ln \left(\frac{V_{cc} + \beta(-V_{cc})}{V_{cc} - V_D} \right)$$



$$\bullet: V_i = 0, V_f = V_{cc}$$

$$V_c(t) = \frac{2}{3} V_{cc}$$


Relaxation Oscillators

Multivibrators

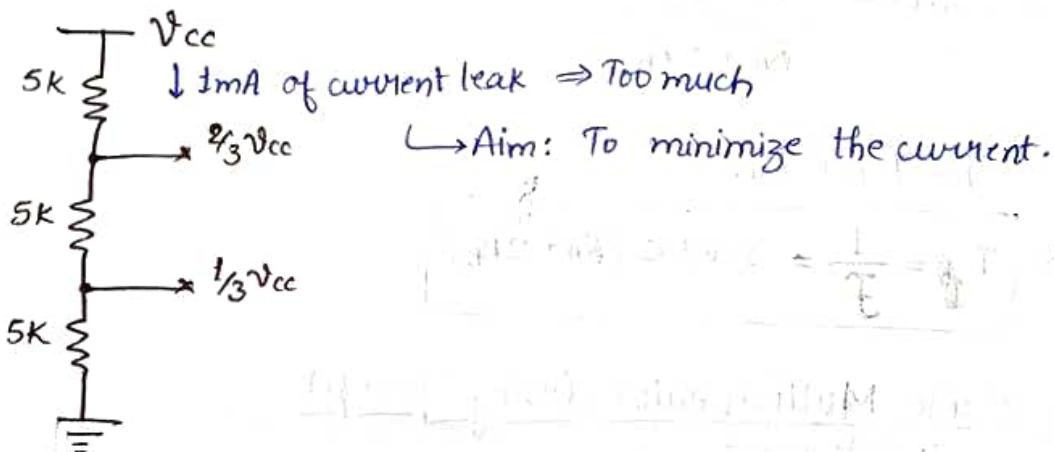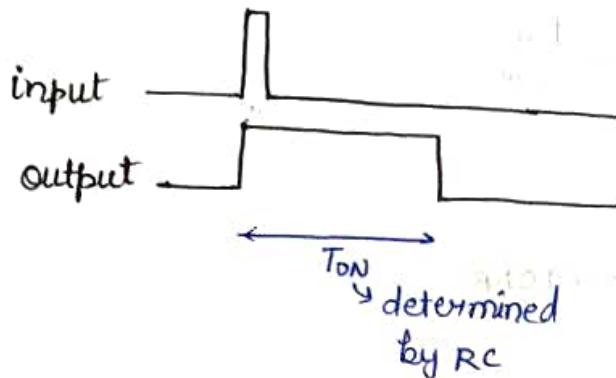- astable
- bi-stable → flip-flop
- mono-stable } 555 IC
- } 555 ICs



Mono-stable Multivibrator

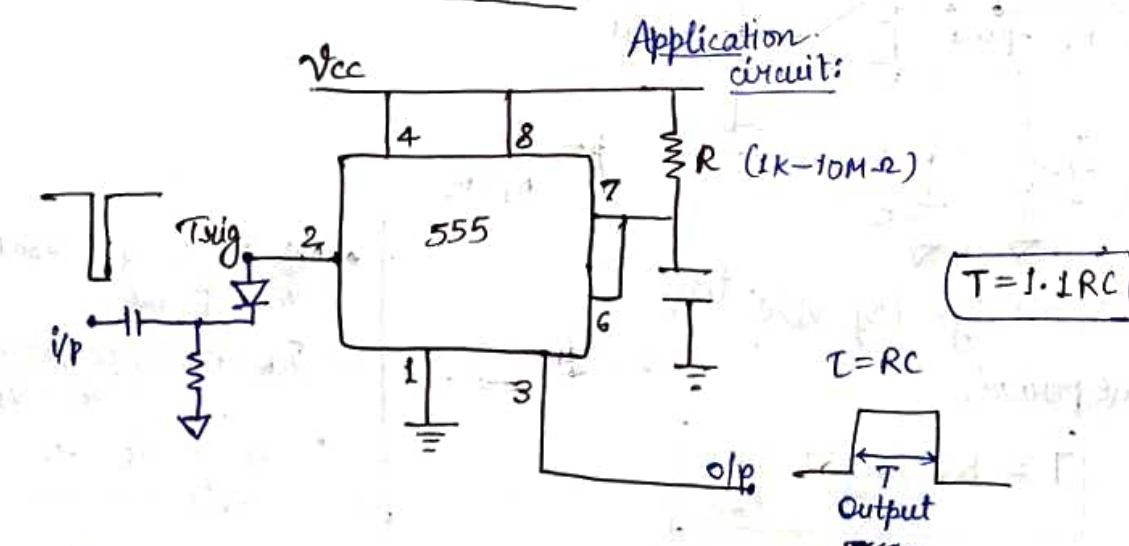

Functional Block: Opens up the internal circuit.

2nd Order Filter

↳ Sallen-Key filter

→ Allows us to use only one opamp.

→ single ended supply.

Generally,

1st order filter $\xrightarrow{\text{use}}$ one opamp

2nd order filter $\xrightarrow{\text{use}}$ 2 opamps

3rd order filter $\xrightarrow{\text{use}}$ 3 opamps.

Review :

* Opamps

- 2 golden rules

• comparators

↳ Schmidt Trigger

• Summer

• Inv., Non-inv. amplifiers

• Differential amplifiers

• Integrator/Differentiator

* Frequency Domain

Plots "jw"

• Stability

$$\frac{A}{BA+1} = \frac{jw^2 R}{m^2}$$

* Non-ideal

• input bias impedance

• output impedance


• G-BW product

• Slew

* Active filters


[Integrator: Modified/limiting case of LPF.]

[Differentiator: Limiting case of HPF.]

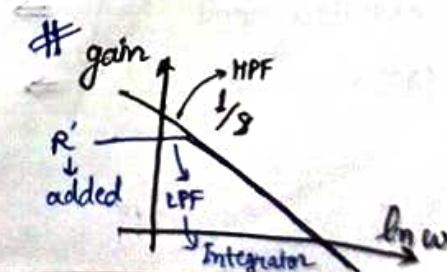

Oscillators



Creates frequency (like sine wave).

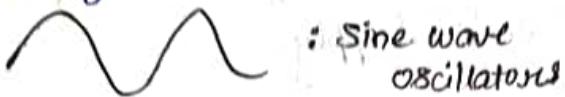

Sine wave oscillator

Relaxation oscillator:

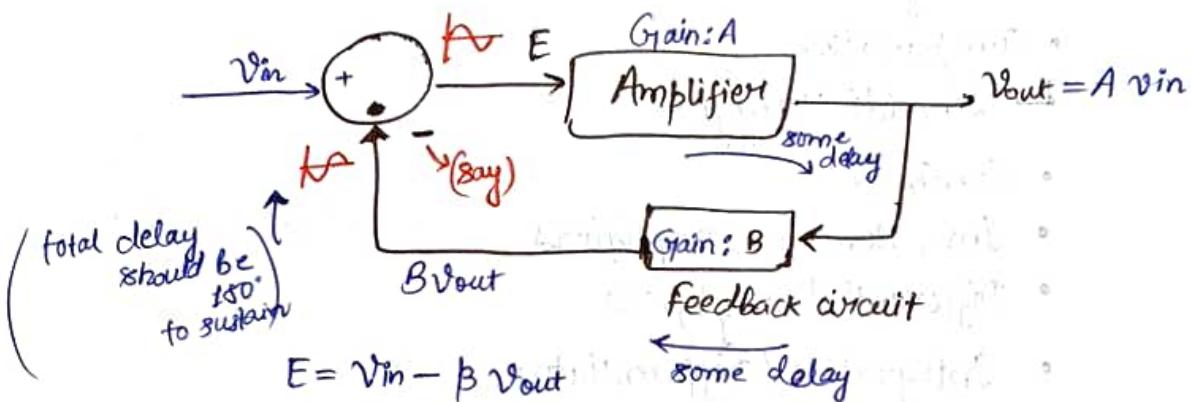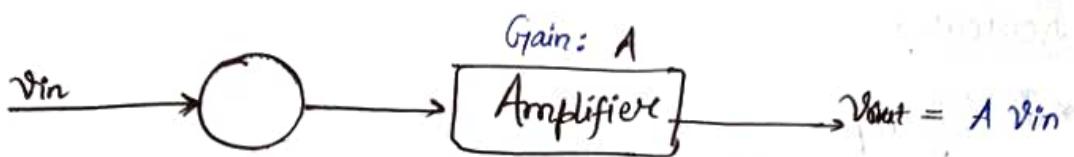- Astable multivibrator
- Bistable multivibrator
- Monostable multivibrator



$$V_{out} = AE = A(V_{in} - \beta V_{out})$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB} \rightarrow \text{Overall gain}$$

→ For V_{out} to exist for $V_{in} = 0$, the circuit should sustain V_{out} even without any input.

$$1 + AB \rightarrow 0$$

$$\Rightarrow AB = -1$$

$$\Rightarrow |AB| = 1$$


→ Phase shift from loop $AB = 180^\circ$

Case-1: $AB < 1$




Getting an oscillator to oscillate is difficult, as getting a particular gain and a phase shift of 180° at the same time can be challenging.


Case-2: $AB = 1$

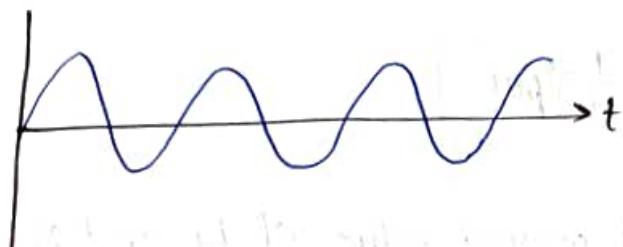

Case-3: $AB > 1$

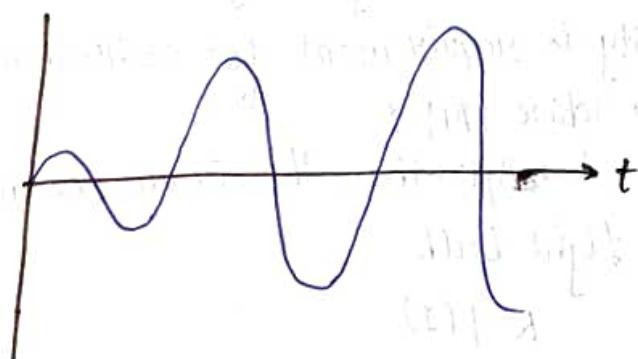

① Wein Bridge Oscillator

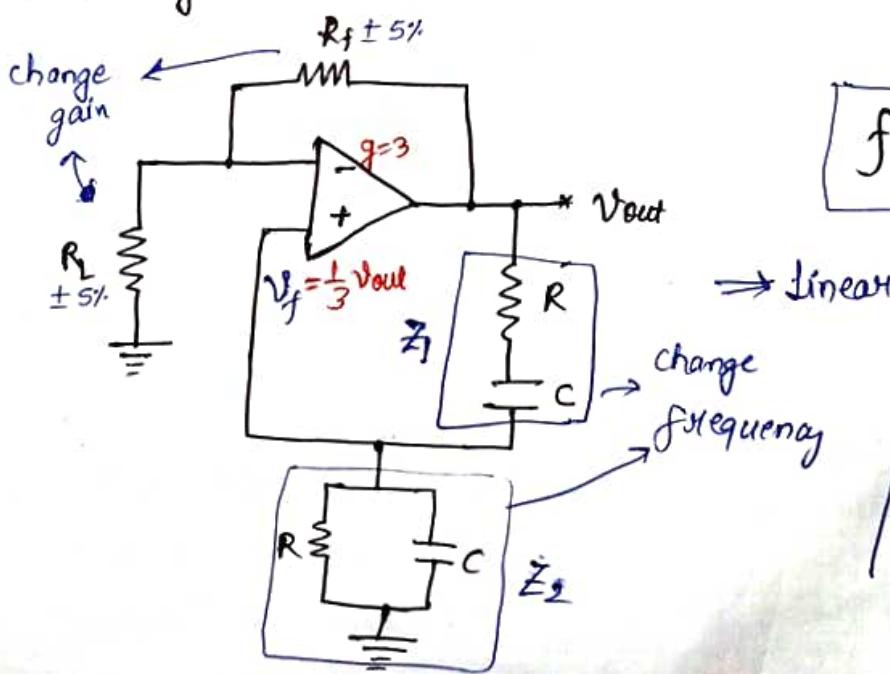

$$f = \frac{1}{2\pi RC}$$

→ Linear
change frequency

To sustain oscillation,
we need non-linear network
↓
to make $(AB)=1$

$$V_f = \frac{j\omega CR}{1 + 3RCj\omega - C^2R^2\omega^2} V_{out}$$

To ensure 0° phase shift at input,

$$1 - C^2R^2\omega^2 = 0$$

$$\Rightarrow \omega = \frac{1}{RC} \Rightarrow \frac{1}{2\pi RC} = f$$

$$\Rightarrow V_f = \frac{1}{3} V_{out}$$

→ It's difficult to get correct value of R_f and R_L while designing

↳ Use some tricks to give $g=3$.

Non-linearity is requirement for oscillation (to sustain):

↳ To achieve $|AB|=1$.

↳ After that, the circuit becomes linear.

① Light bulb

$$R=f(I)$$

② Anti-parallel diodes



Conditions for oscillation

① Feedback Reinforcing Mech.

② $| \text{forward gain} \times \text{feedback gain} | = 1$
or, $|AB| = 1$


③ Phase of feedback signal should be 180° .

Barkhausen Criteria

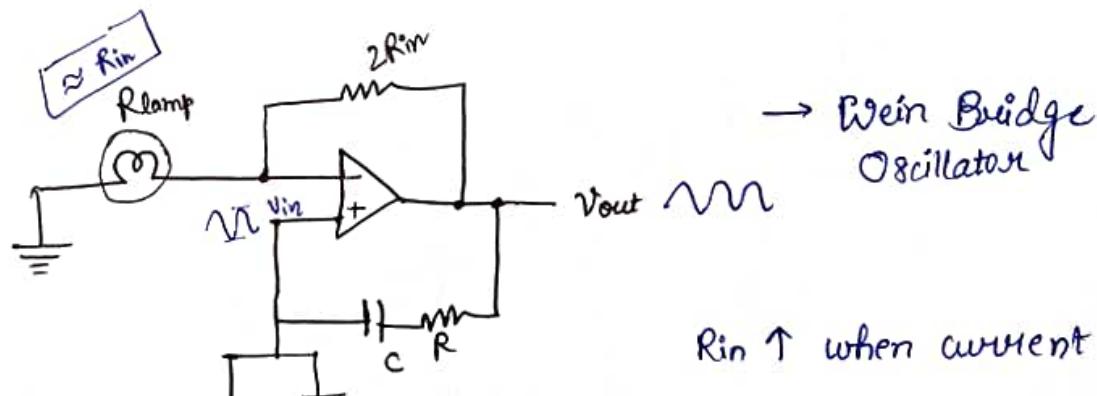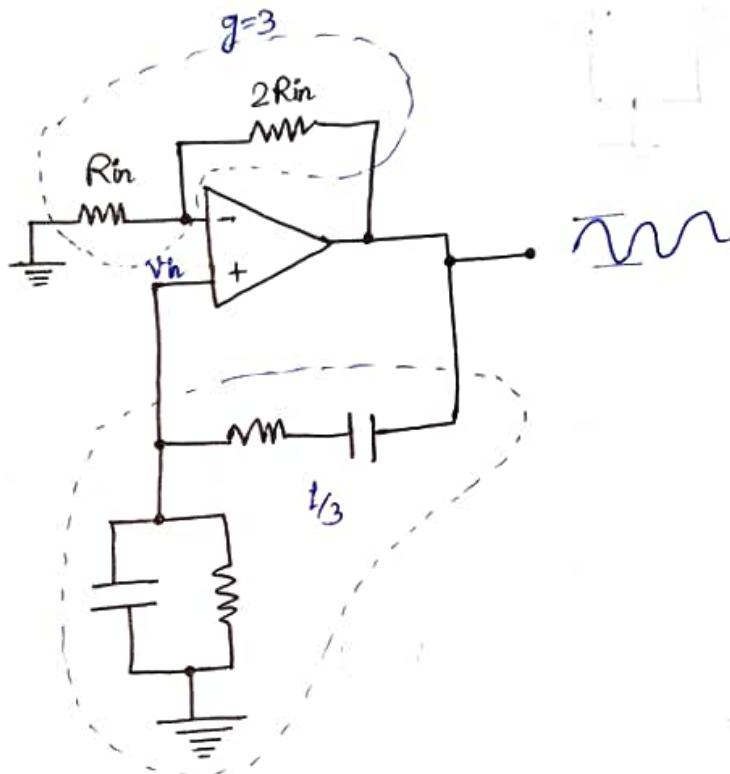

Rin ↑ when current ↑

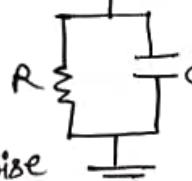Present at all frequencies
by white noise




$$\text{gain} = 1 + \frac{2R_{\text{in}}}{R_{\text{lamp}}}$$

Say $V_{\text{out}} \uparrow$, $V_m \uparrow$, $V_{\text{lamp}} \uparrow$, $I_{\text{lamp}} \uparrow$, $R_{\text{lamp}} \uparrow$, gain ↓, $V_{\text{out}} \downarrow$.

[Make sure than Rin is fixed or has lower thermal coefficient than that of Rlamp.]

II

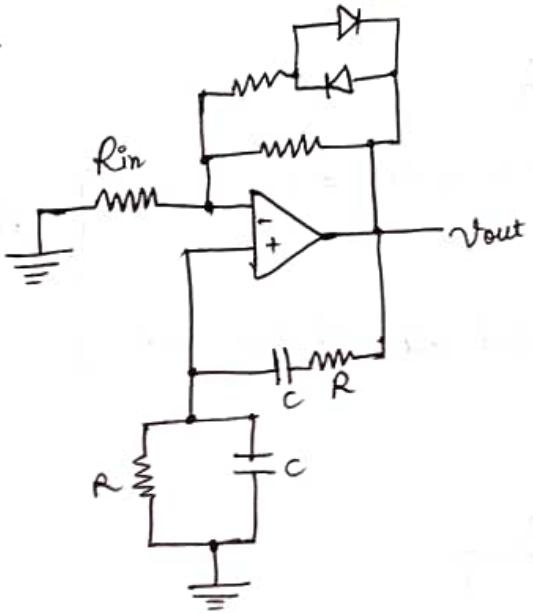


allows $V > 0.7V$.

special mode

mode

terminal voltage ≈ 0

$\frac{V_{out}}{V_{in}} + 1 = \infty$

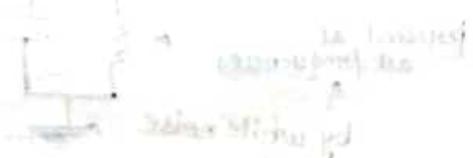

unity-gain buffer
terminal voltage ≈ 0
output voltage $\approx V_{in}$

POWER Amplifiers

Deal with high output power.

For 100 W of output power,

$$100 \text{ W} = \frac{A^2}{2R_L} \Rightarrow P_{\text{RMS}} = \left(\frac{A}{\sqrt{2}}\right)^2 \frac{1}{R_L}$$

$$R_L = 10 \Omega$$

$$\Rightarrow A = \sqrt{2000} \\ = 44.72 \text{ V}$$


$$\Rightarrow I_{\text{max}} = 4.4 \text{ A}$$



$\downarrow 10 \Omega$

- Power amplifiers come with heat sink.
- Have lower β .

Class A amplifier:

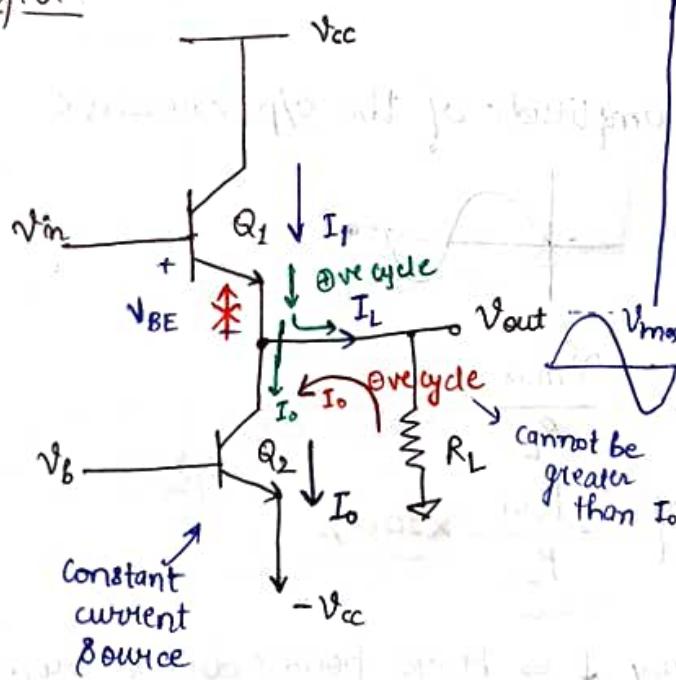

Positive half cycle:


$$V_{\text{in}} \uparrow \Rightarrow V_E(Q_1) \uparrow$$

$$\Rightarrow V_{BE} \uparrow$$

$$\Rightarrow I_1 \uparrow$$

$I_0 \rightarrow \text{constant}$

$$I_L = I_L + I_0$$

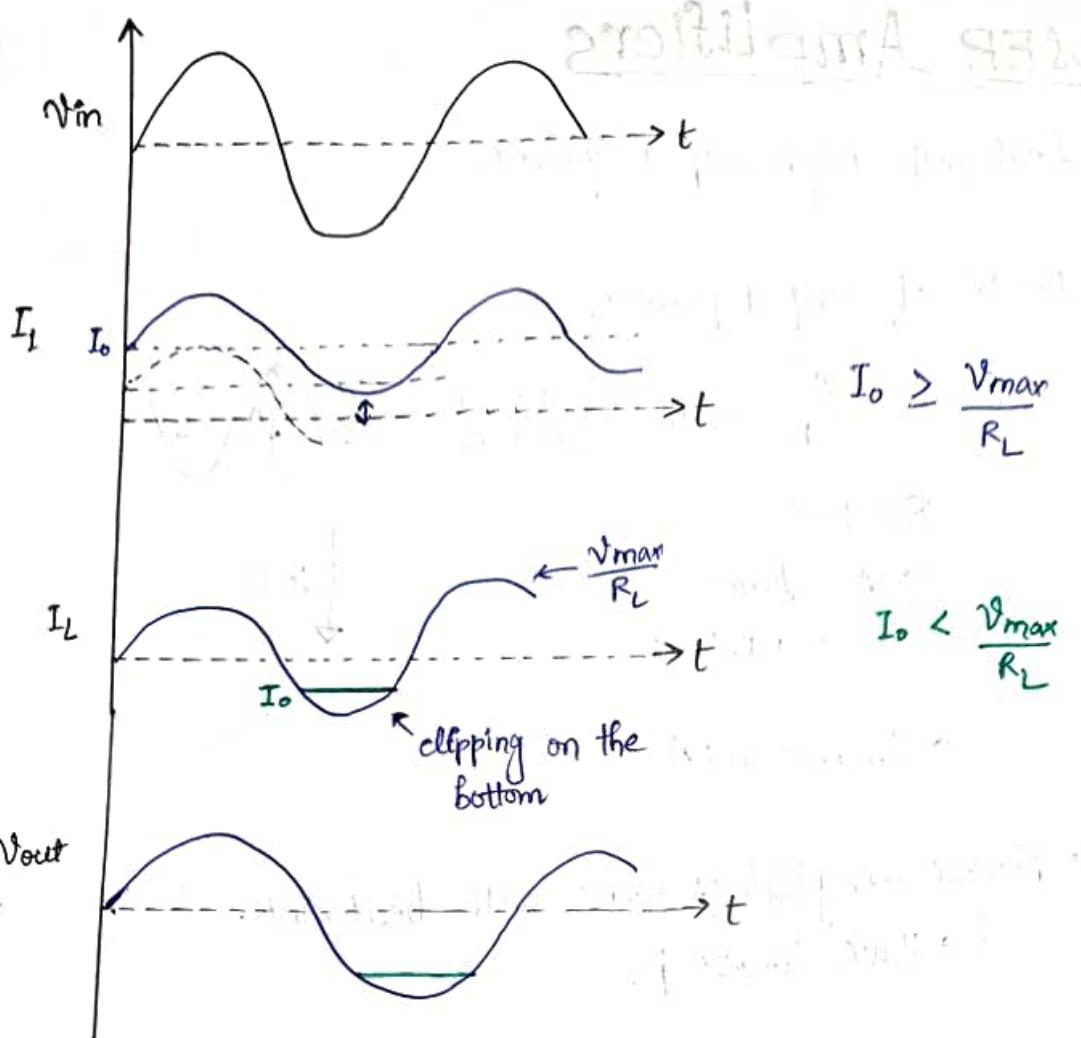

V_{max} : Max amplitude of the o/p sinewave



$$I_{max} = \frac{V_{max}}{R_L}$$

$$\text{Efficiency: } \eta = \frac{P_{out}}{P_{DC}} \times 100\%$$

Efficiency $\downarrow \Rightarrow$ More power drawn from the source.

$$P_{out} = \frac{V_{out}^2}{2R_L}$$

$$P_{DC} = 2 \times V_{cc} \times I_0$$


$$\eta = \frac{V_{out}^2}{2R_L} - \frac{1}{2V_{cc} \times I_0} \times 100\%$$

$$= \frac{1}{4} \cdot \frac{V_{out}^2}{V_{cc} \times I_0 R_L} \times 100\% \Rightarrow \text{Output voltage } \uparrow \Rightarrow \eta \uparrow$$

$$V_{out \max} = I_0 R_L = V_{cc}$$

$\hookrightarrow \eta_{\max} = 25\%$ ($\because I_0 R_L = V_{cc}$)

\hookrightarrow Theoretical limit

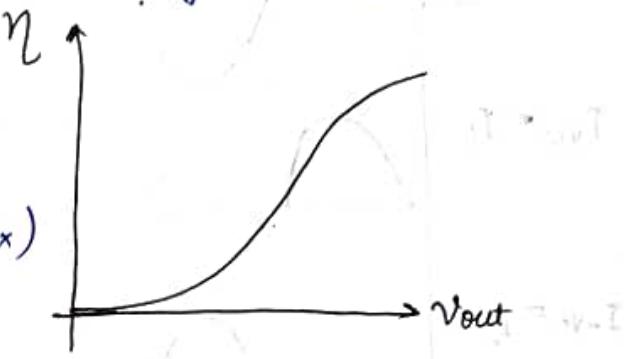


$$\eta_{\max} \rightarrow V_{cc} \downarrow$$

→ Conduction angle = 360° (2π)

\hookrightarrow Duration of sine wave for which each of the transistor is conducting current.

Class B amplifier:

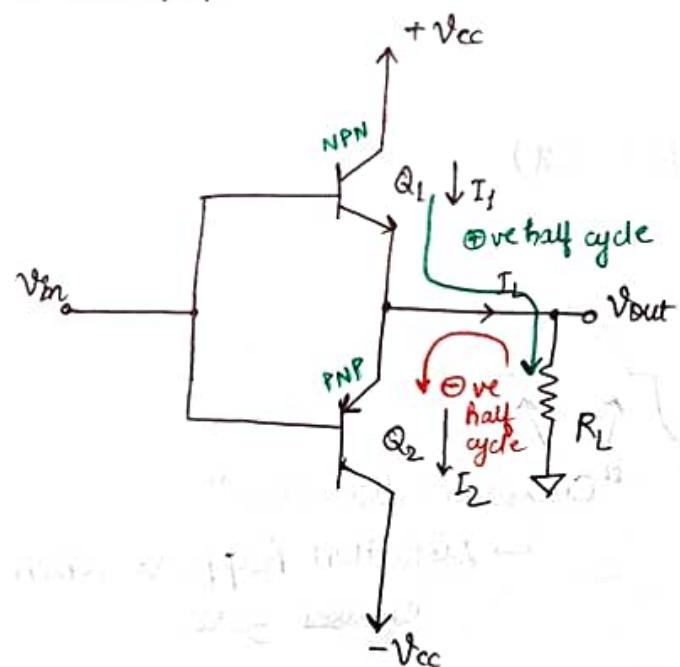


Positive half cycle:


$Q_1 : \text{ON}$

$Q_2 : \text{OFF (pnp)}$

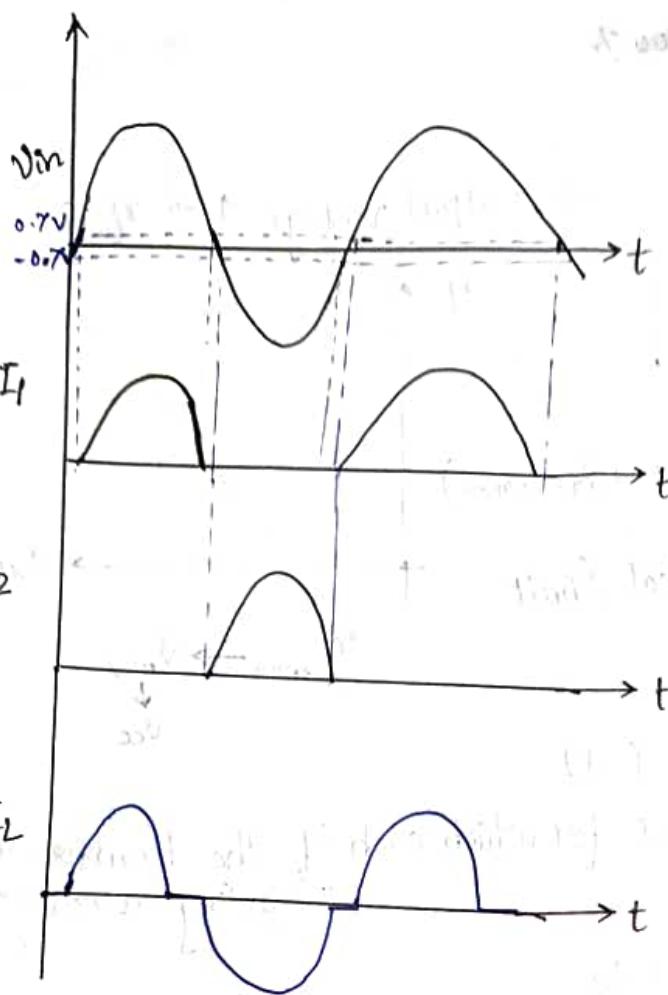To turn ON,
NPN: $V_{BE} > 0.7$
PnP: $V_{BE} < -0.7$



Conduction angle = 180° (π)

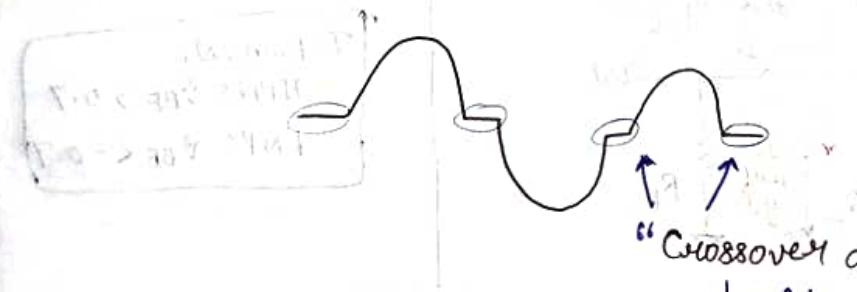

"Crossover distortion"

↳ Distortion happens when V_{in} crosses zero.

$$P_{out} = \frac{V_{out}^2}{2R_L}$$

$$P_{DC} = \frac{2 \times V_{out}}{\pi R_L} \times V_{cc} \quad (\text{using Fourier series})$$

For η_{max} , $V_{out} = V_{cc}$.

$$\eta_{max} = \frac{\pi}{4} \times 100\% \Rightarrow \boxed{\eta_{max} = 78.5\%}$$

Class AB Power Amplifier

→ Conduction angle $> 180^\circ (\pi)$



$< 360^\circ (2\pi)$

→ Small Quiescent current (I_Q)


Class A: $I_Q \geq I_{max}$

Class B: $I_Q = 0$

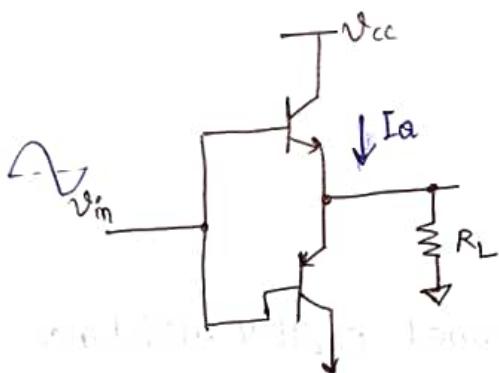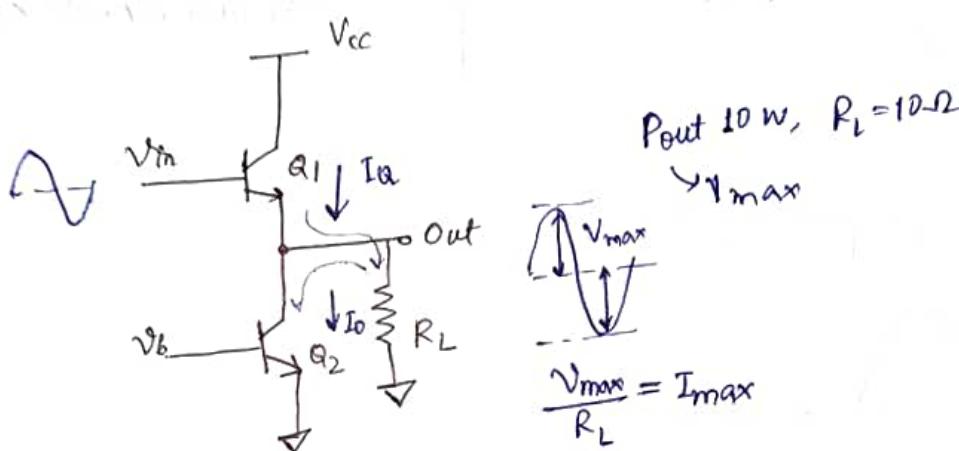
Class AB: $I_Q > 0$ and $I_Q \ll I_{max}$



Class AB PA:

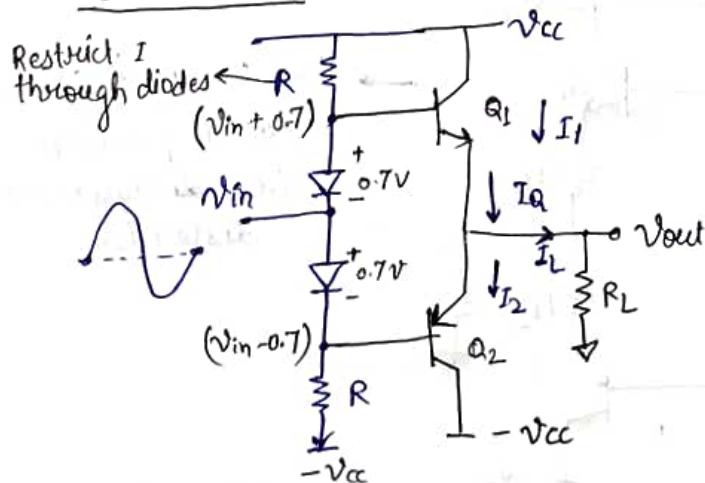

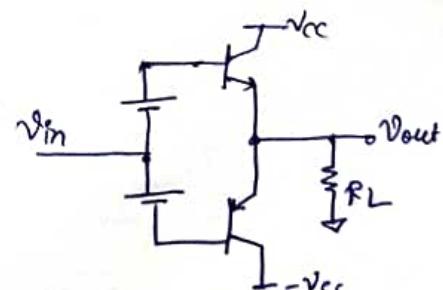When $V_{in}=0$, the transistors should just turn on.




Something like this
But this can't be put into practice

By using this bias, crossover distortion can be avoided, while maintaining a good efficiency.

Choose I_a such that

$I_a \downarrow \rightarrow$ crossover distortion ~~can't be avoided~~

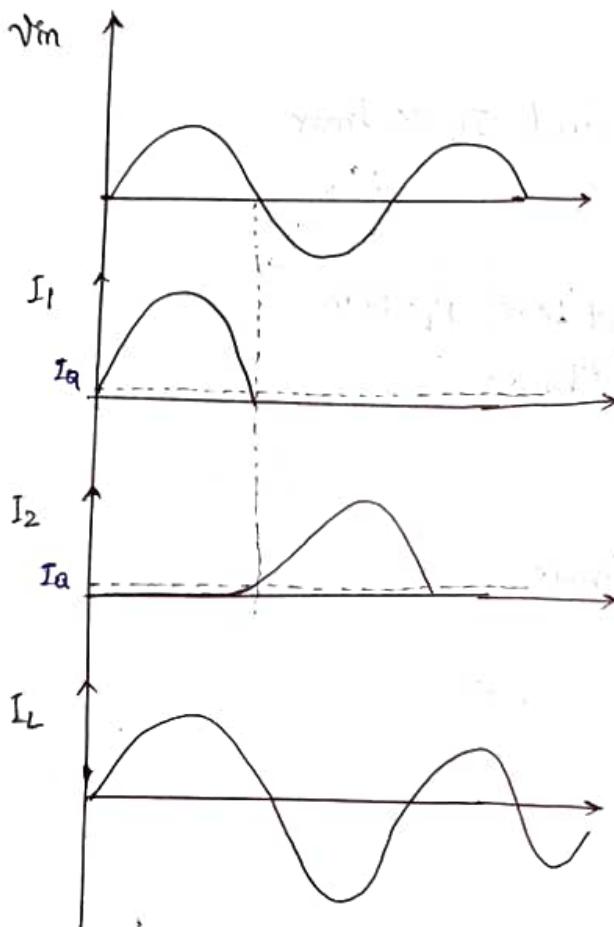
$I_a \uparrow \rightarrow$ Reduce efficiency. \rightarrow maintain efficiency.



class C PA


Conduction Angle $< 180^\circ$

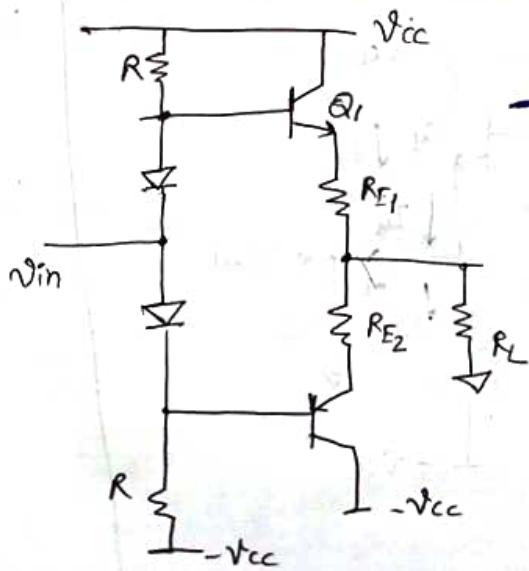→ To avoid thermal runaway problem, connect emitter resistance to both the resistors (these provide thermal stability).



→ But we again get into class B problem, i.e., ~~can't be avoided~~ crossover distortion.

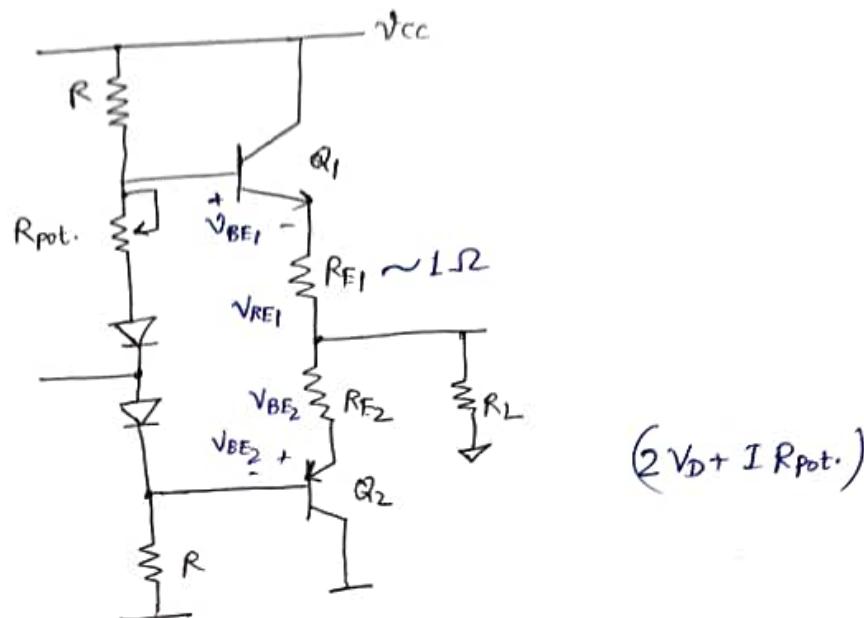Now, connect a potentiometer, as we need more than 2 diode drops.



Short-circuit Protection:

If output is connected to ground by mistake, a large current will flow through both the transistors and will permanently damage them.

To detect the short-circuit, look for the voltage drop across R_E's.

To prevent the short-circuit, reduce the current.

As supply current is difficult to reduce, so add two transistors.

