

# Digital Electronics Verilog Lab 2

**Submitted By:**

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)

## LAB SHEET

**Question No. 1** Design a Three Input majority gate circuit in verilog coding by predefined gates or by Boolean expression.

**Sol: Truth Table:**

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


The reduced **boolean** expression using K-Map should be:

$$F = (A \text{ and } B) \text{ or } (B \text{ and } C) \text{ or } (C \text{ and } A)$$


**Code:**

```
module majorityGate(  
    input A,B,C,  
    output O);  
    assign O = (A&B)|(B&C)|(C&A);  
endmodule
```


**Schematic:**

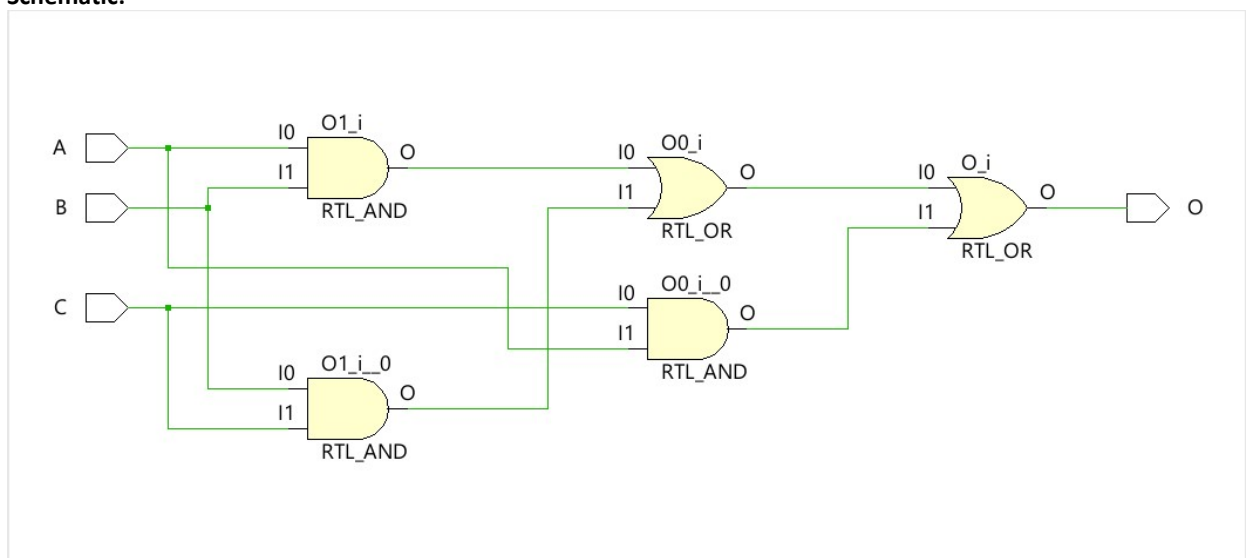

**Simulation:**

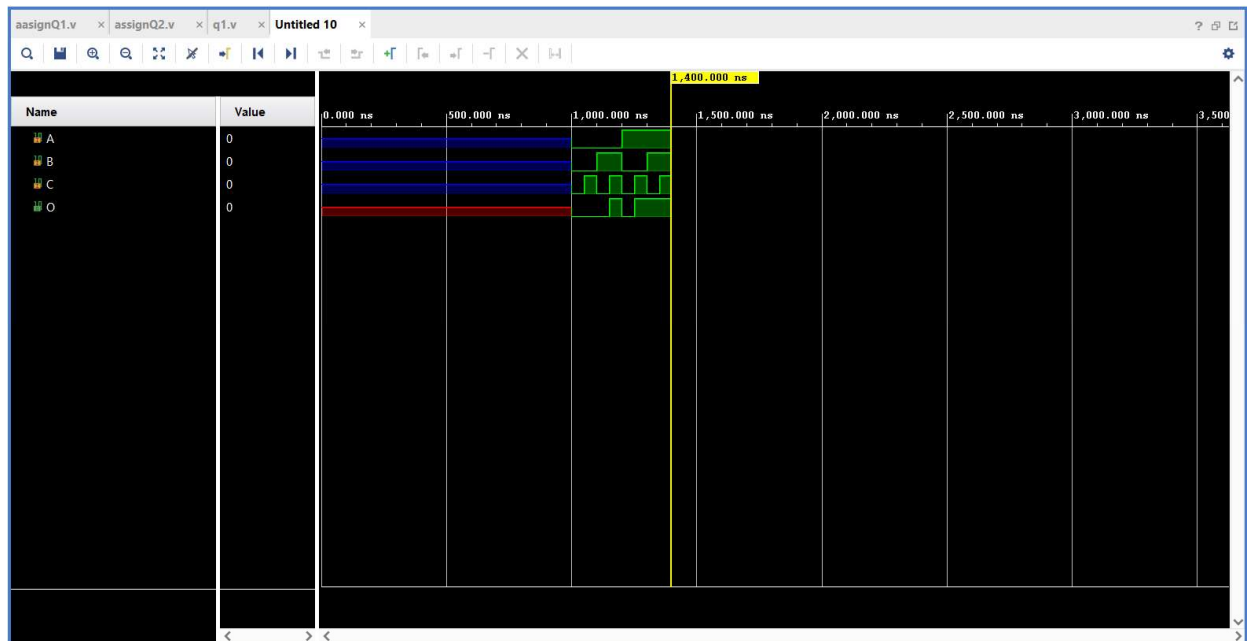

### Synthesis:

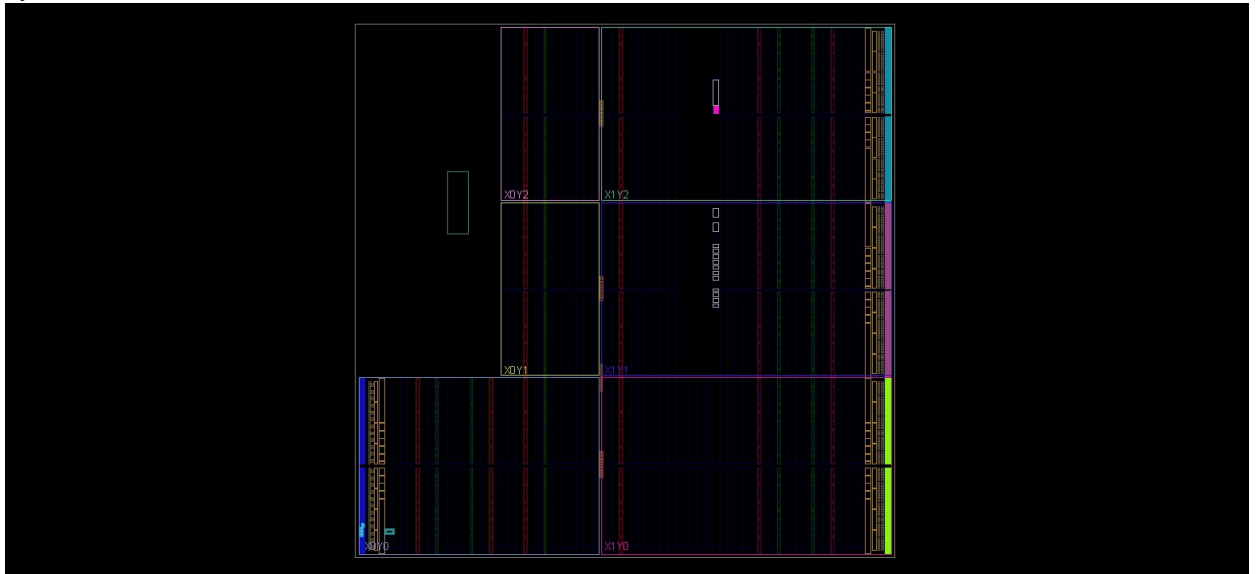

**Question No. 2** Make a BCD to seven segment display circuit.

[You can use behavioural or procedural statement]

[You can arrange the 7 LEDs as your requirement]

Sol: The reduced **boolean** expression should be:

- a = A or C or (B and D) or (not B and not D)
- b = (not B) or ( not C and not D) or (C and D)
- c = B or (not C) or D
- d = (not B and not D) or (C and not D) or (B and not C and D) or (not B and C) or A
- e = (not B and D) or (C and not D)
- f = A or (not C and not D) or (B and not C) or (B or not D)
- g = (not B and C) or (C and not D) or (B and not C) or (B and not C) or A

### Code:


```
module BCDto7Segment(
    input A,B,C,D,
    output a,b,c,d,e,f,g);
    assign a = A|C|(B&D)|((~B)&(~D));
    assign b = (~B)|((~C)&(~D))|(C&D);
    assign c = B|(~C)|D;
    assign d = ((~B)&(~D))|(C&(~D))|(B&(~C)&D)|((~B)&C)|A;
    assign e = ((~B)&D)|((C&(~D)));
```

```


assign f = A/((~C)&(~D))|(B&(~C))|(B&(~D));
assign g = ((~B)&C)|(C&(~D))|(B&(~C))|(B&(~D))/A;
endmodule

```


#### Schematic:

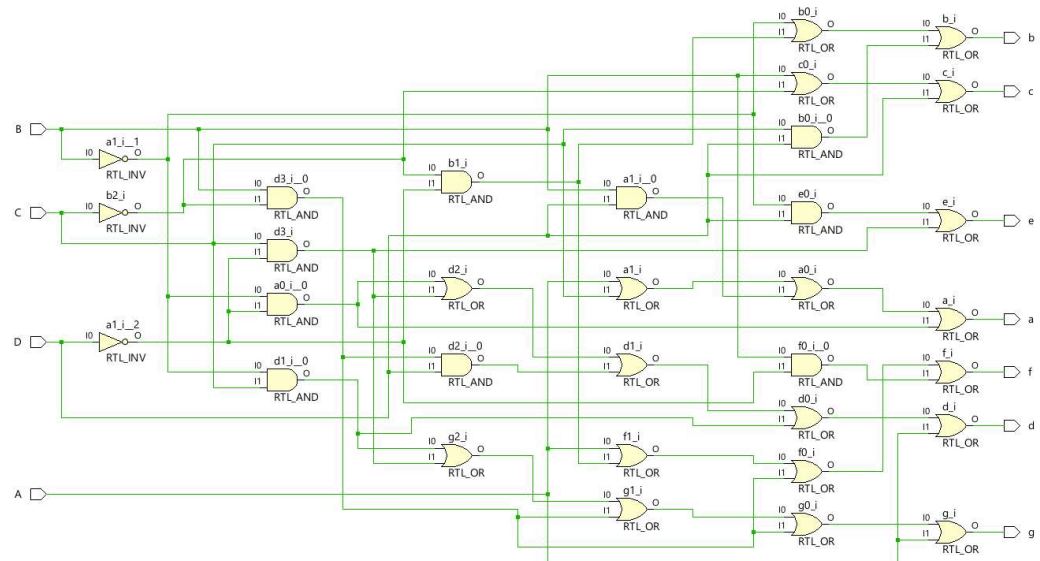

#### Simulation:

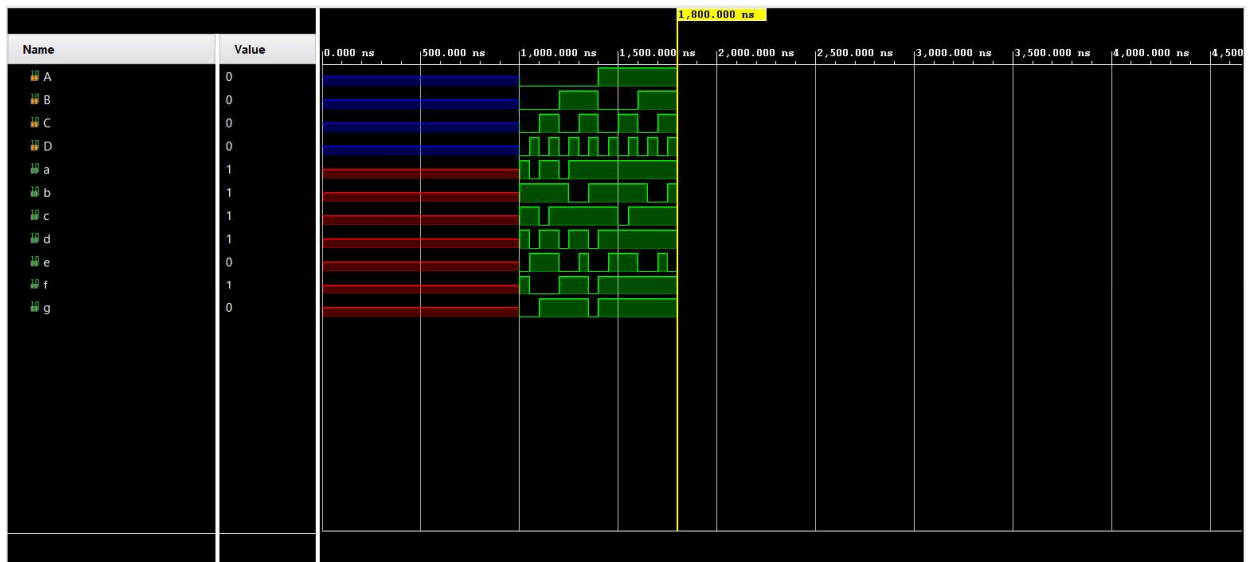

#### Synthesis:

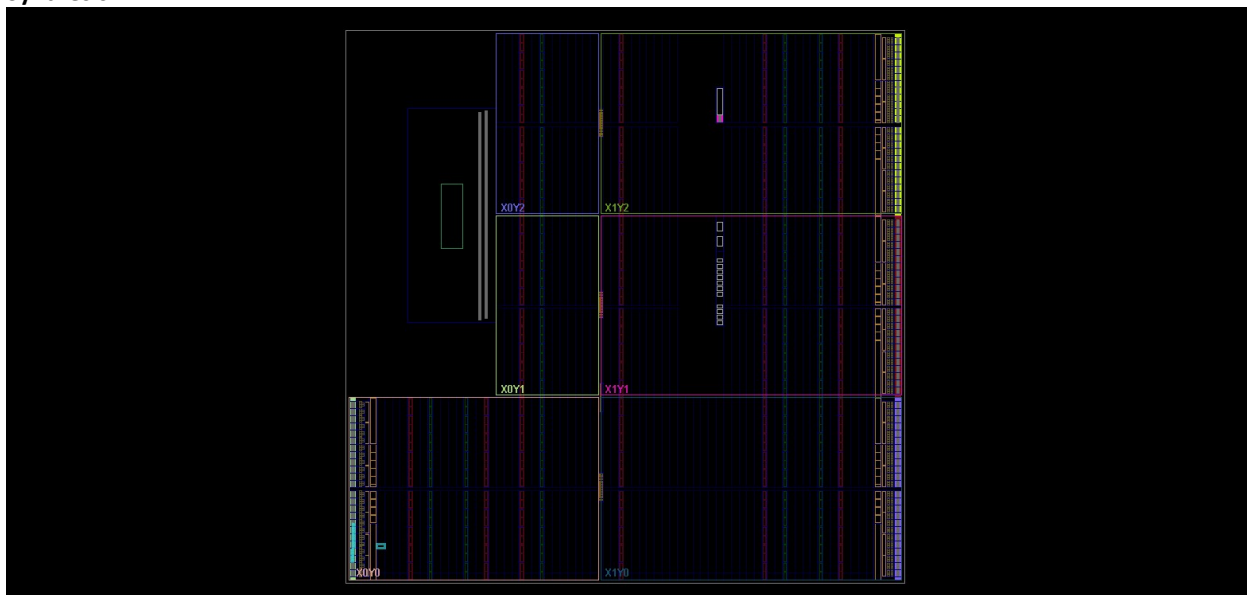

**Question No. 3 (i)** Make one 4:2 Encoder unit.

Sol: The reduced **boolean** expression should be:


$$A = D2 \text{ or } D3$$

$$B = D1 \text{ or } D4$$


**Code:**

```
module encoder(
    input D1,D2,D3,D4,
    output A,B);
    assign A = D2|D3;
    assign B = D1|D4;
endmodule
```


**Schematic:**

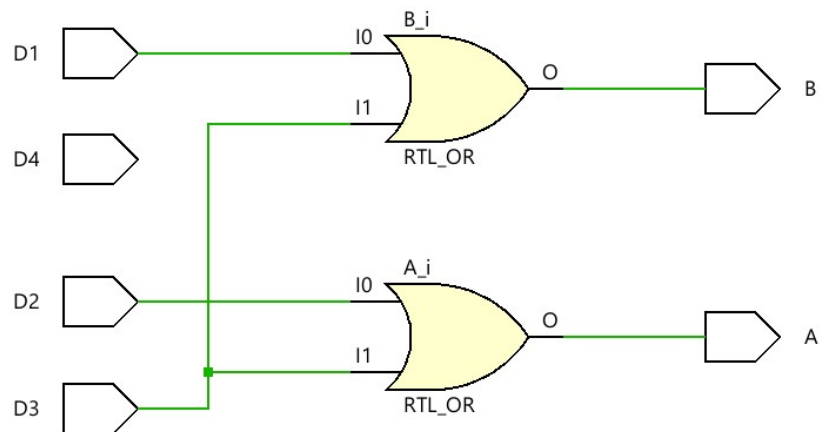


**Simulation:**

 

**Synthesis:**

 

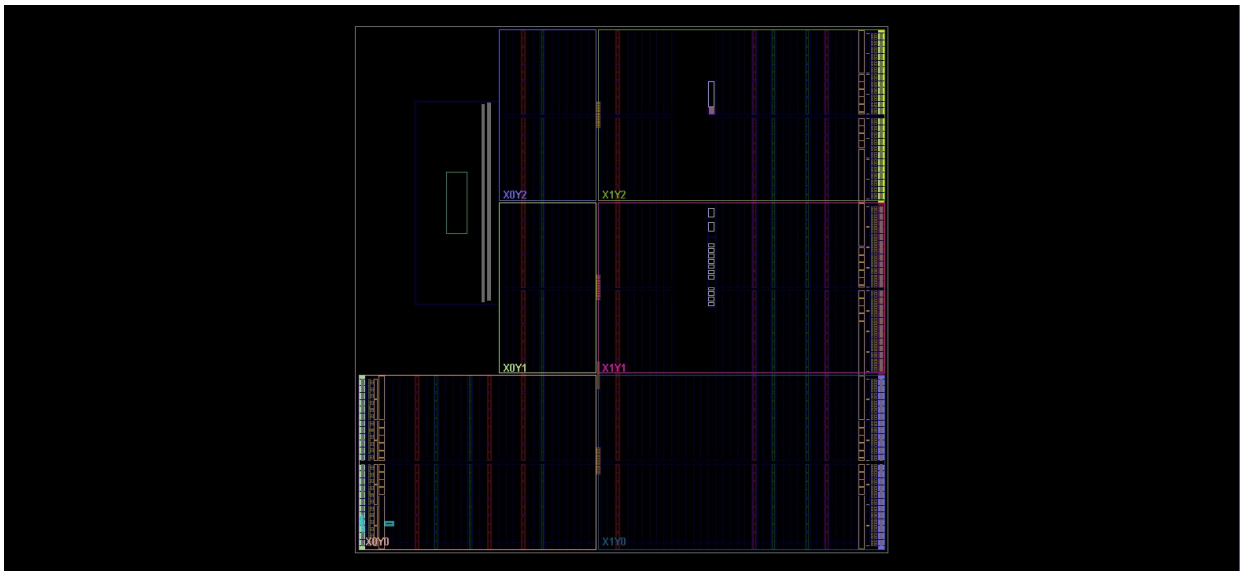

**Question No. 3 (ii)** Make a MUX from that Encoder unit.


Sol: The reduced **boolean** expression should be:

$$F = (\text{not } A \text{ and not } B \text{ and } D1) \text{ or } (\text{not } A \text{ and } B \text{ and } D2) \text{ or } (A \text{ and not } B \text{ and } D3) \text{ or } (A \text{ and } B \text{ and } D4)$$


**Code:**

```
module mux(
    input D1,D2,D3,D4,A,B,
    output F);
    assign F = ((~A)&(~B)&(D1))|((~A)&(B)&(D2))|((A)&(~B)&(D3))|((A)&(B)&(D4));
endmodule
```


**Schematic:**

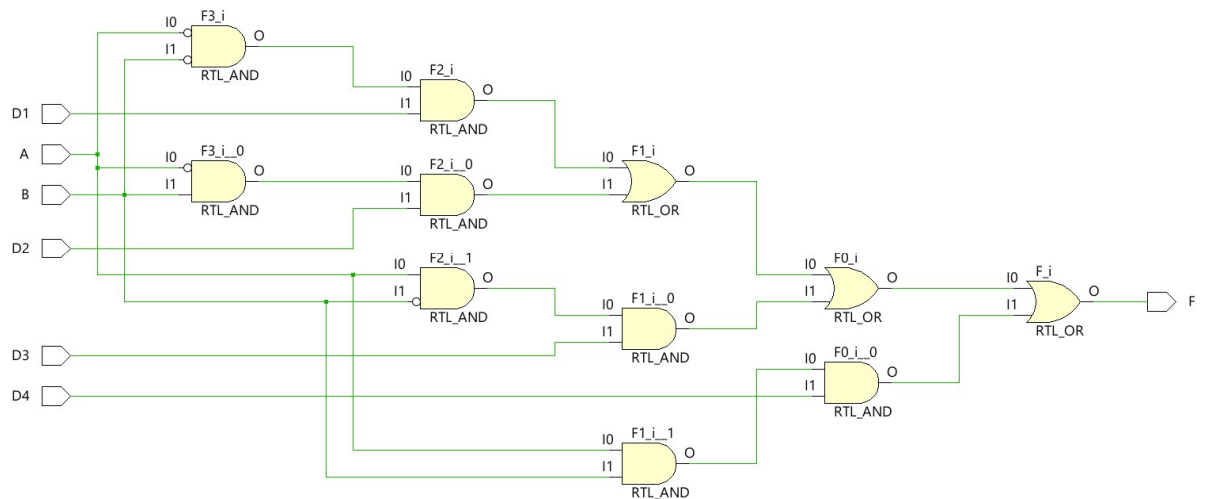

**Simulation:**

 

Synthesis:

 

## ASSIGNMENT

**Question No. 1** Design a Full Adder circuit in verilog by nand gate only.

**Sol: Code:**

```

module aassignQ1(
    input A,B,Cin,
    output S, Cout);
// S = ((A xor B) nand ((A xor B) nand Cin)) nand (Cin nand ((A xor B) nand Cin))
// -wire 1- -wire1- -wire1-
// -----wire2----- -wire2-----
// -----wire3----- -wire4-----
// -----Sum-----
    wire wire1, wire2, wire3, wire4;
    wire w1,w2,w3;
    nand(w1,A,B); //w1 = ~(AB)
    nand(w2,A,w1); //w2 = ~(Aw1)
    nand(w3,B,w1); //w3 = ~(Bw1)

    nand(wire1,w2,w3); //wire1 = A xor B
    nand(wire2,wire1,Cin);
    nand(wire3,wire1,wire2);
    nand(wire4,wire2,Cin);

```

```
nand(S,wire3,wire4);
nand(Cout,w1,wire2);
```


endmodule

**Schematic and Boolean Expression:**

## Verilog Lab Assignment -2

① Design a Full Adder circuit in verilog by nand gate only.

Soln:

 

## Boolean Expression :

By reduction,

$$\begin{aligned} \text{Sum} &= A \oplus B \oplus C_{in} \\ &= \overline{(A \oplus B) \cdot (A \oplus B) C_{in} \cdot C_{in} \cdot (A \oplus B) C_{in}} \\ &\quad \text{where } A \oplus B = \overline{A \cdot \overline{AB}} \cdot \overline{B \cdot \overline{AB}} \end{aligned}$$

$$\begin{aligned} \text{Cout} &= \overline{AB + (A \oplus B) C_{in}} \\ &= \overline{C_{in} (A \oplus B) \cdot AB} \end{aligned}$$

**Question No. 2** Design a 2:1 Mux circuit in verilog by nor gate only.

**Sol: Code:**


```
module muxUsingNor(
    input I0,I1,S,
    output F);

    wire w1,w2,w3,w4,w5;
    nor(w1,I0,I1);
    nor(w2,I0,S);
    nor(w3,S,S);
    nor(w4,w3,I1);
    nor(w5,w1,w2);
    nor(F,w4,w5);
endmodule
```

**Boolean Expression:**

② Design a 2:1 Mux Circuit in Verilog by nor gate only.

Soln:

 

$$F = I_0 \bar{S} + I_1 S$$

$$= (\bar{S} I_0 + S) (\bar{S} I_0 + I_1) \quad [\text{Using } A + BC = (A+B)(A+C)]$$

$$= (\bar{S} + S) (I_0 + S) (\bar{S} + I_1) (I_0 + I_1)$$

$$= (I_0 + S) (\bar{S} + I_1) (I_0 + I_1)$$

$$= (\bar{S} + I_0) (\bar{S} + I_1) (I_0 + I_1)$$

$$\therefore F = (\bar{S} + I_0) (\bar{S} + I_1) + (I_0 + I_1)$$

Schematic:

