


RF Lab 1 Report

Submitted by **Saurabh Kumar**
(SC22B146)


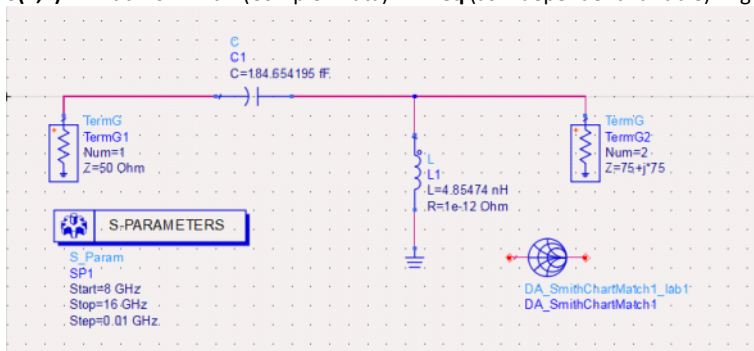
1. Given a load impedance of $75 + j75$, design a 2-element lumped matching port circuit to match with a source impedance of 50 ohms at 12 GHz.

Procedure:

- Place two **TermG** components from Basic Components palette and assign them the values of 50 ohms and $75 + j75$ ohms.
- Place a **Smith Chart Matching Network** from the **Smith Chart Matching** palette.
- Go to **Tools** -> **Smith Chart...** to open **Smith Chart Utility** by selecting the smith chart in the workspace.
- In the **Smith Chart Utility** window, specify the matching frequency (12 GHz), Z0 (50 Ohms), source impedance ($50 + j0$), load impedance ($75 + j75$), Max (1), Type (dB), Trace1 (S11), Trace2 (S11), Min (0), Start Freq (0) and Stop Freq (14.0e9). Optionally lock the source and load impedances.
- Design a two element matching circuit by clicking on the lumped elements (Inductors and Capacitors) with the help of smith chart. Finally, click **Build ADS Circuit**.
- To open the circuit, select the smith chart and click on **Push into Hierarchy** (in the toolbox). Select and copy the relevant circuit and **Pop Out**.
- Then join the circuit with the **TermGs**.
- Now search and place **S_Param** component and set its Start, Stop and Step-size frequencies.
- Click on **Simulate**. A simulation window will open. Then, place a **Rectangular Plot** from the **Palette**. In **Plot Traces & Attributes** window, plot **S(1,1)** --> **Add Vs.** --> **dB (Complex Data)** --> **freq** (as independent variable). A graph will be plotted. Repeat this for **S(1,2)**.



Observations:

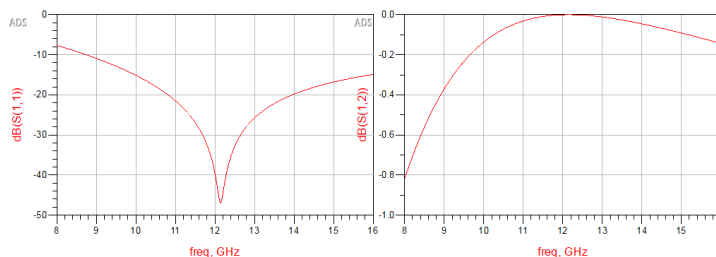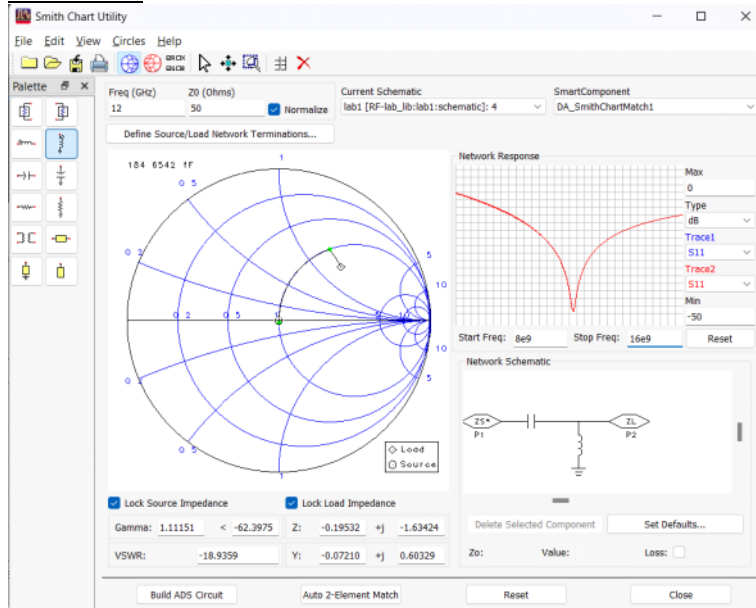





For the matching network, we get the following values for inductance and capacitance:

L = 184.654195 fF (shunt)
C = 4.85474 nH (series)

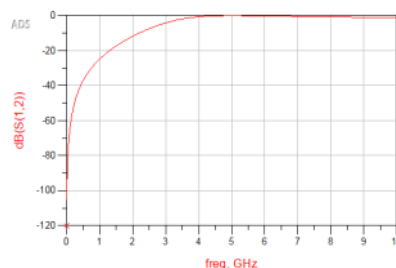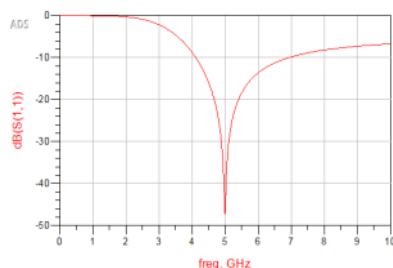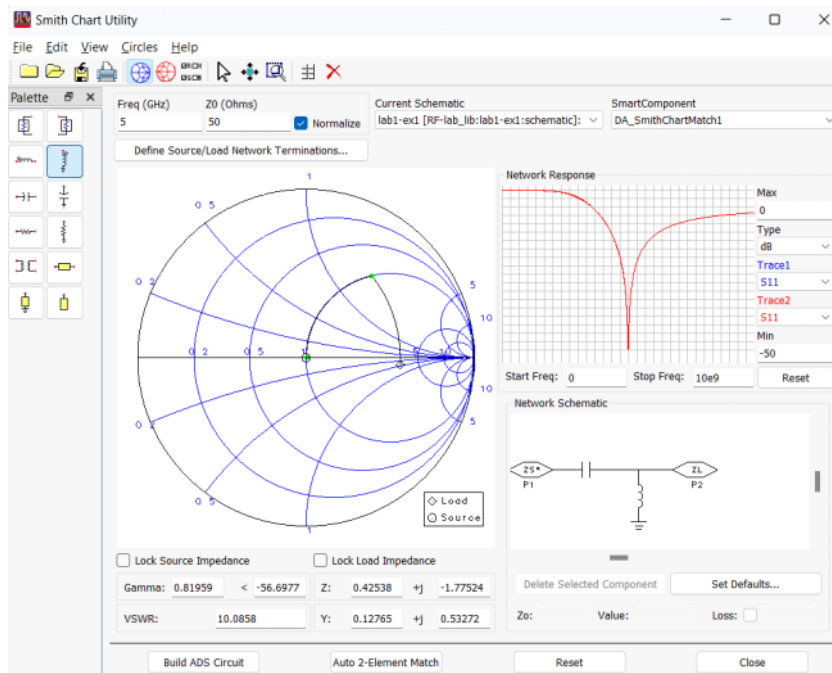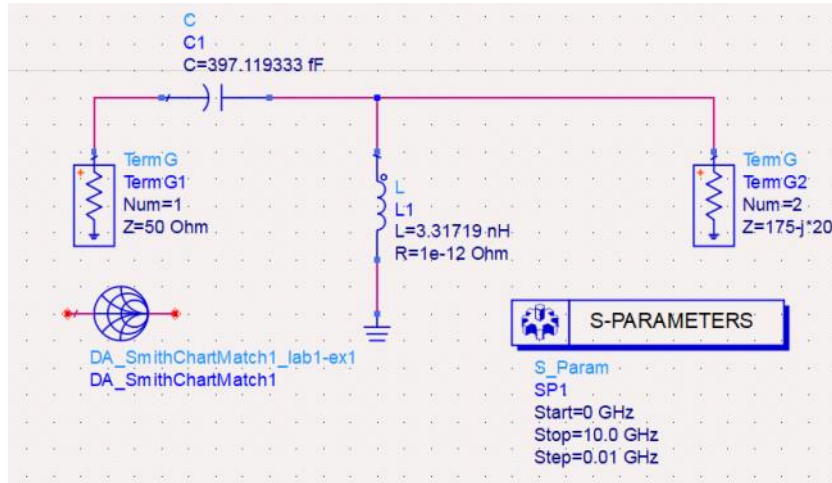2. Design a Lumped element matching circuit to match a 50 Ohm load to a complex load of $175 - j20$ Ohm with an impedance Bandwidth of 5GHz. (The operating frequency is also 5 GHz).

Procedure:

- Place two **TermGs**: 50 ohms and $175 - j20$ ohms.
- Place a **Smith Chart Matching Network** from the **Smith Chart Matching** palette.
- Go to **Tools -> Smith Chart...** to open **Smith Chart Utility** by selecting the smith chart in the workspace.
- In the **Smith Chart Utility** window, specify the matching frequency (5 GHz), Z_0 (50 Ohms), source impedance ($50 + j*0$), load impedance ($175 - j*20$), Max (0), Type (dB), Trace1 (S11), Trace2 (S11), Min (-50), Start Freq (0) and Stop Freq (10.0e9).
- Design a two element matching circuit and click **Build ADS Circuit**.
- Copy and join the circuit with the **TermGs**.
- Now search and place **S_Param** component and set its Start, Stop and Step-size frequencies.
- Click on **Simulate** and plot **S(1,1)** and **S(1,2)** vs frequency.




For the matching network, we get the following values for inductance and capacitance:

L = 3.31719 nH (shunt)
C = 397.119333 fF (series)



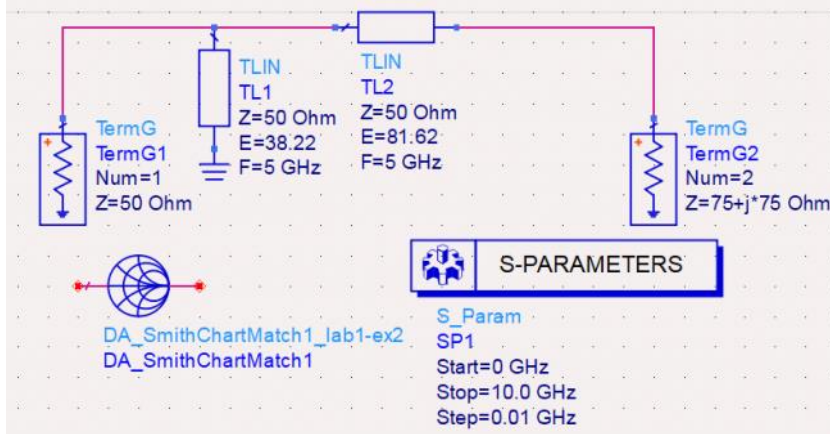
3. Design a Matching circuit using Stubs to match a 50 Ohm source to any complex load of your choice.

Procedure:

- Place two **TermGs**: 50 ohms and $75+j75$ ohms (choice).
- Place a **Smith Chart Matching Network** from the **Smith Chart Matching** palette.
- Go to **Tools -> Smith Chart...** to open **Smith Chart Utility** by selecting the smith chart in the workspace.
- In the **Smith Chart Utility** window, specify the matching frequency (5 GHz), Z_0 (50 Ohms), source impedance ($50+j*0$), load impedance ($75+j*75$), Max (0), Type (dB), Trace1 (S11), Trace2 (S11), Min (-50), Start Freq (0) and Stop Freq (10.0e9).
- Design a two stub element matching circuit and click **Build ADS Circuit**.
- Copy and join the circuit with the **TermGs**.
- Now search and place **S_Param** component and set its Start, Stop and Step-size frequencies.
- Click on **Simulate** and plot **S(1,1)** and **S(1,2)** vs frequency.



Observations:

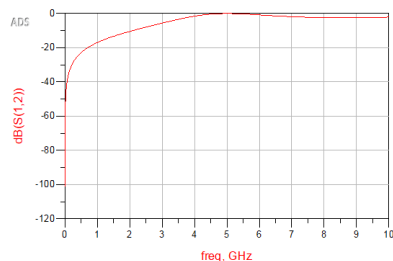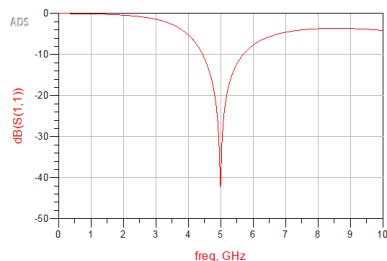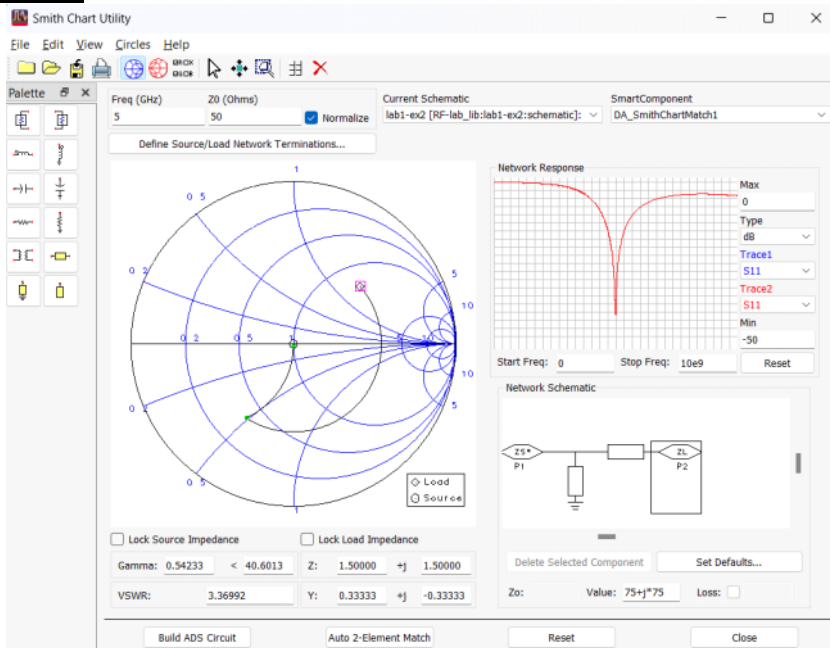

For the matching network, we get the following values for stub impedances:

Short line impedance = 50 Ohm

Line impedance = 50 Ohm