

Analog Electronics

Practice Questions

- 1) The steady-state output (V_{out}), of the circuit shown below, will

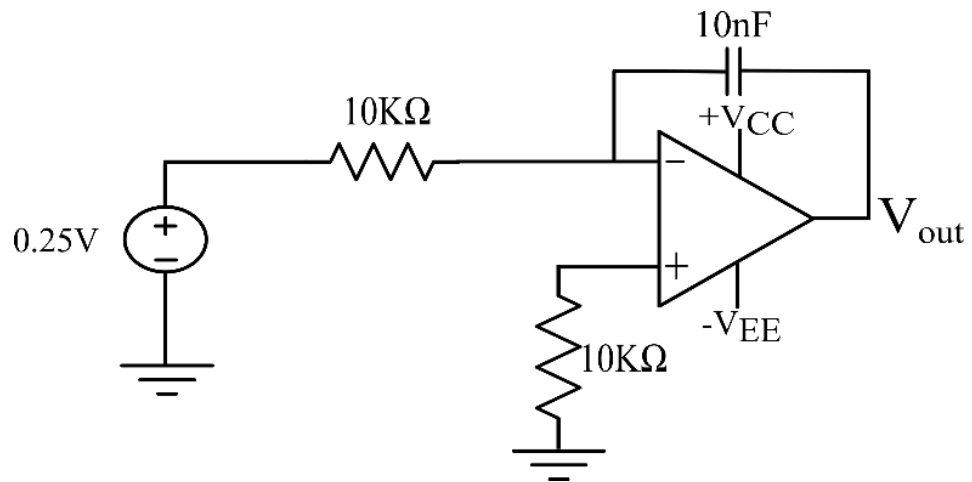


Fig. 1.

- a) Saturate to $+V_{CC}$
- b) Saturate to $-V_{EE}$
- c) 0.25V
- d) -0.25V

- 2) In the circuit shown in Fig.2 , a Silicon transistor Q is used. Then $V_{out} =$ _____

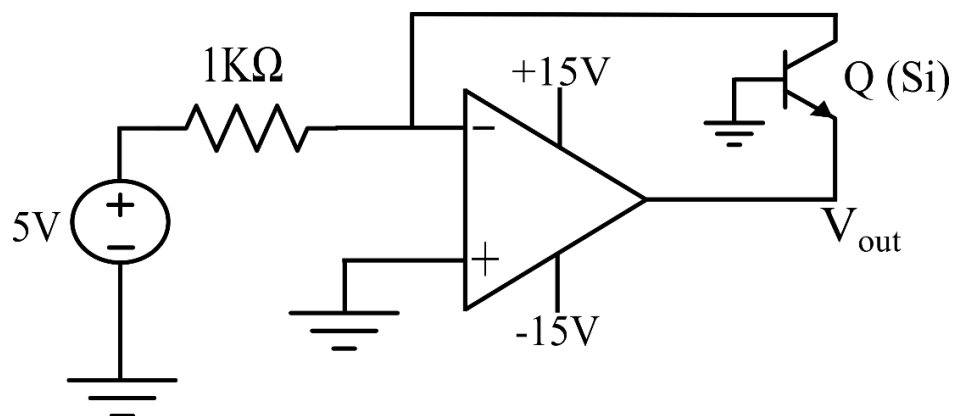


Fig.2

- 3) Out of the four characteristics given below, which of the following a well-designed operational amplifier should possess?

P. High common mode rejection ratio
 Q. High input impedance
 R. Low Power Supply Rejection Ratio
 S. Low output impedance

- a) P, Q & R
 b) Q, R & S
 c) P, Q & S
 d) R & S

- 4) What will be the waveshape and frequency of V_{out} for the following circuit?

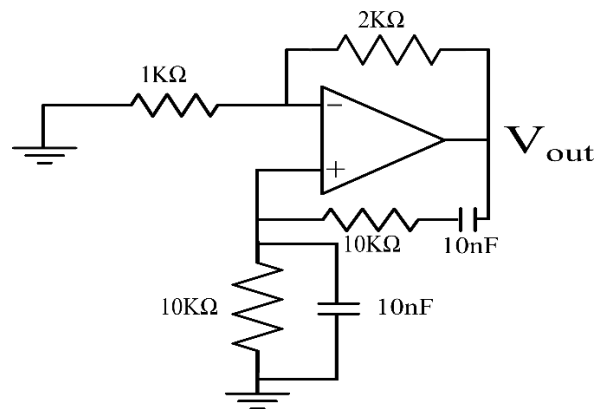


Fig. 3

- 5) The circuit shown in Fig.4 is of an astable multivibrator using the NE555 timer IC. Derive the ratio $\left(\frac{t_H}{t_L}\right)$ where t_H is time duration for which the output is high and t_L is duration for which the output is low. Also find out the frequency of the output signal?

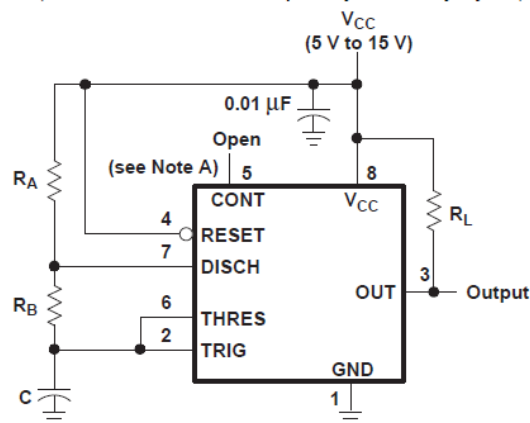


Fig. 4

$$\text{ans} \left(\frac{t_H}{t_L} = \frac{R_A + R_B}{R_B}, f = \frac{1.44}{(R_A + 2R_B)C} \right)$$