

Lab 1 Report: Implementation of Logic circuits

Submitted by:

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)

Aim: Implementation of Logic circuits using Transistor Level Circuit and measuring the performance of the Logic gates

Components Required:

- Digital Circuit board containing LEDs
- Integrated circuits (IC 7400, IC 7402, IC 7404, IC 7408, IC 7432, IC 7486)
- Connecting wires

Circuits Truth Table:

IC 7408:

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

A, B: Input to two pins

0: Low voltage

1: High voltage

IC 7432:

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

IC 7404:

A	Output
0	1
1	0

IC 7400:

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

IC 7402:

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

IC 7486:

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Observations and Conclusions:

Truth table implies the following:

- IC 7408 contains AND Gate.
- IC 7432 contains OR Gate.
- IC 7404 contains NOT Gate.
- IC 7400 contains NAND Gate.
- IC 7402 contains NOR Gate.
- IC 7486 contains XOR Gate.

Gate diagram:

AND:




OR:




NOT:



NAND:

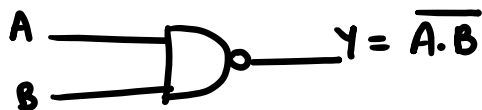

NOR:

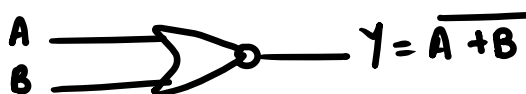

XOR:

