

उपकरणीकरण
मापकरणं च

INSTRUMENTATION
AND MEASUREMENT

INSTRUMENTATION

Measurement concepts

Devices and Circuits for good quality measurement

Analog and digital instruments

Measurement: Process of estimating the value of unknown variable.
measurand

Measurand: temperature, pressure, humidity, displacement
speed, acceleration, force, torque, light intensity.


Industrial scenarios: Automotive, aerospace, biomedical,
process industry, etc.

	Angle/angular displacement (accuracy)	
Automotive	1°	(By steering wheel)
Aerospace	1/360°	(Solar panel in the dorm of sun)
Biomedical	1/60°	(Robotic arm)

Measurand energy form:

- Mechanical (speed, acceleration, force, torque, etc.)
- Optical (light intensity)
- Thermal (temperature)
- Chemical
- Radiation
- Electrical

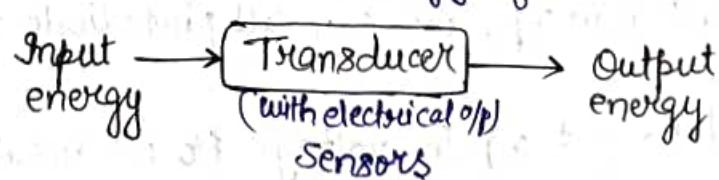Transducer: Converts one energy form into other form.





→ We generally prefer transducers with electrical o/p energy because electrical energy is easy to transmit, amplify, control, display.

INTEGRATION

Sensor: Transducer with electrical output energy

Eg.

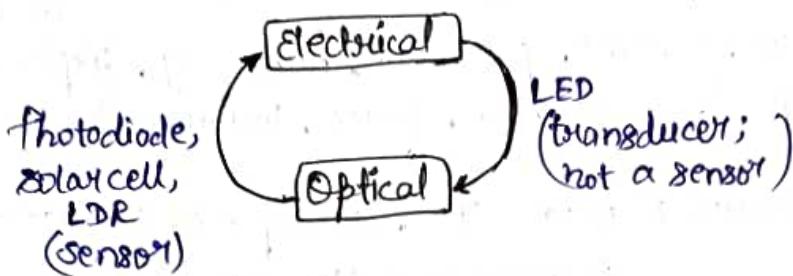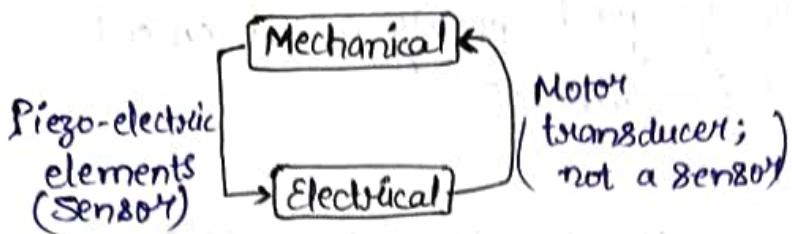

Photodiode:



I_s : Reverse saturation current (due to minority carriers)


L : light intensity

→ More light intensity

→ More photons $L_3 > L_2 > L_1 > L_0$ "Current"

→ More minority carriers

→ more I_s

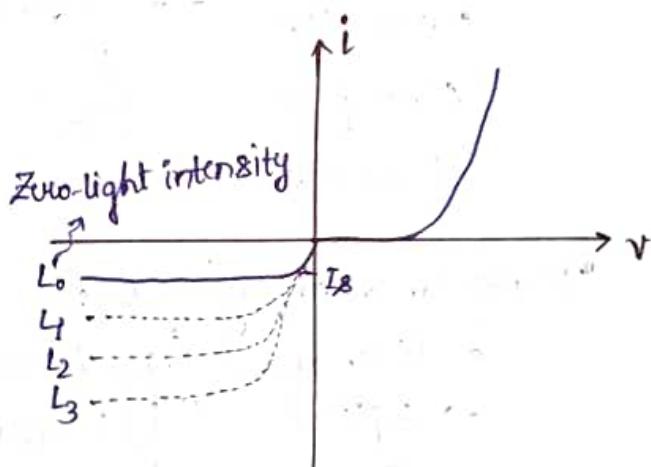

$$I_s \propto L$$

$$\Rightarrow I_s = KL$$


(As current is in o/p)

→ As current is in o/p, we can call photodiode as current-output sensor.

→ We need to get o/p in voltage so we measure most of the times in voltage.


→ we can convert current into voltage using resistor R but it will not work as photo-diode has its internal resistance.

Modelling photodiode:

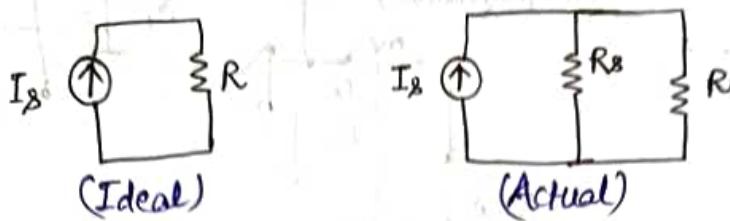

→ Photodiode is not an ideal current source.

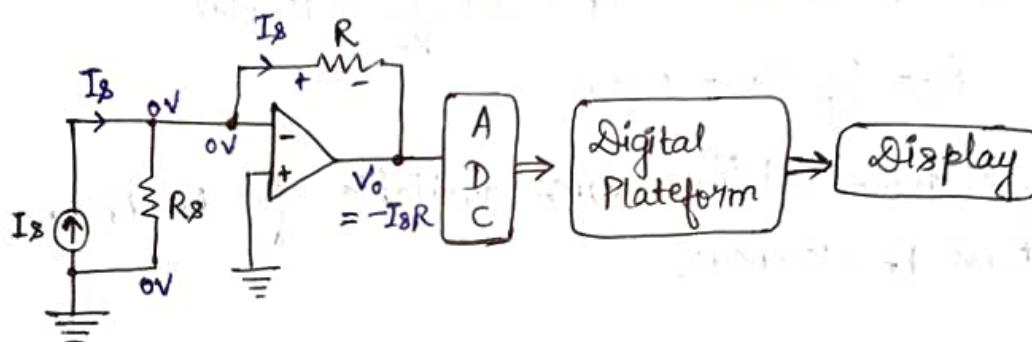→ We will use opamp instead of resistor because internal resistance would not affect o/p voltage in opamp.




$$I_B \propto L$$

$$I_B = kL$$

To get L , divide by R, k .

(in our course)

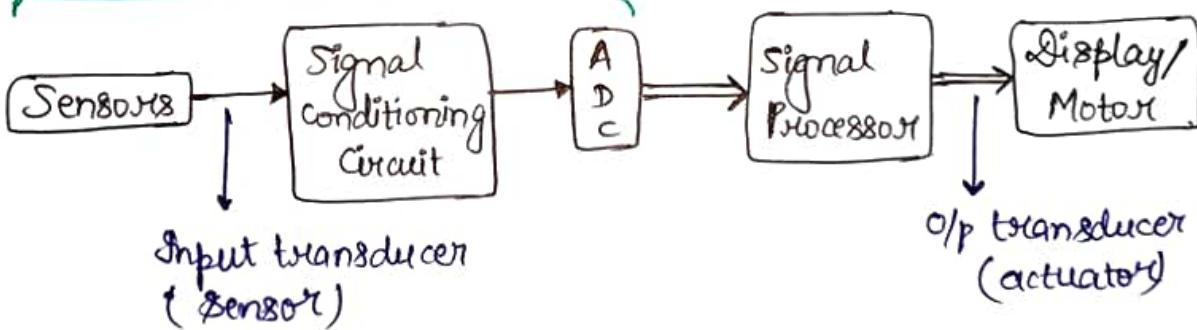


Using T (star) N/w for low current conversion into voltage:

$$I_B = 10nA, V_o = 1V,$$

then we need $R = 100 M\Omega$ by previous formula as $V_o = -I_B R$, but we cannot have such large resistance.

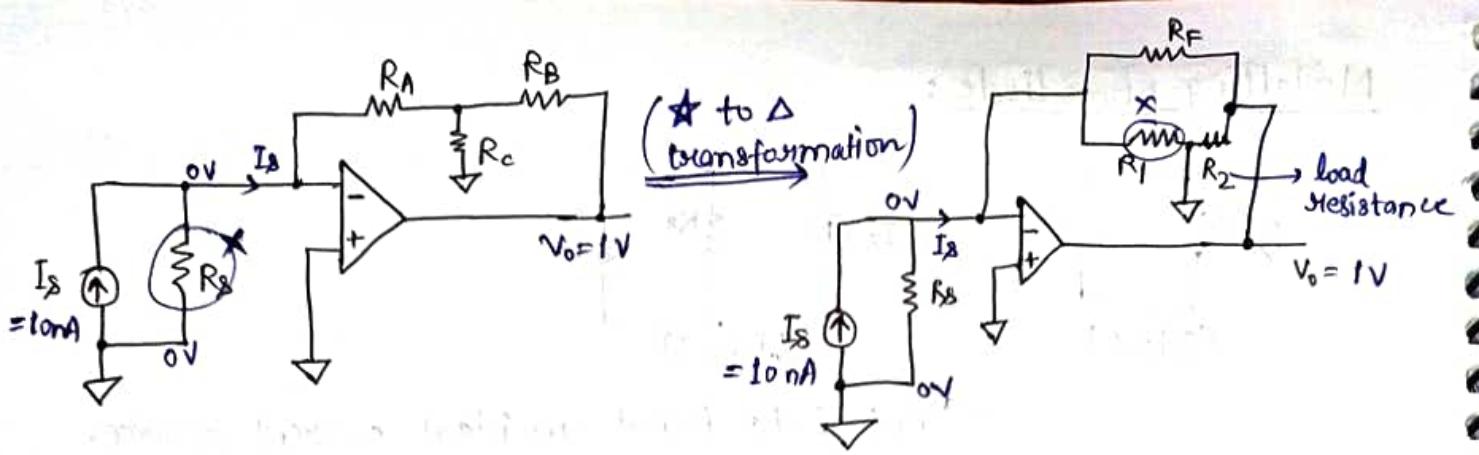The solution of above problem can ~~not~~ be get using T-NW.



$$V_o = -I_S R_F, \quad R_F = R_A + R_B + \frac{R_A R_B}{R_c} = 100 M\Omega$$

$$\text{If } R_A = R_B = 1 M\Omega \Rightarrow R_F = 2 + \frac{1}{R_c} = 100 M\Omega$$

$$R_c = \frac{1}{g_8} M\Omega \approx 10 k\Omega$$

So, we have all the values available for R_A, R_B, R_c and can have $R_F = 100 M\Omega$.

Sensors: Sensors are classified on the basis of o/p:

R : Resistive sensor, e.g., RTD, Thermistor

C : Capacitive sensor, e.g., Level detector, Tactile


L : Inductive sensor, e.g., Proximity sensors

I : Current o/p's, e.g., Photodiodes, Ionospheric probes

V : Voltage o/p's, e.g., Thermo couple

Q : Charge o/p's, e.g., Piezoelectric elements.

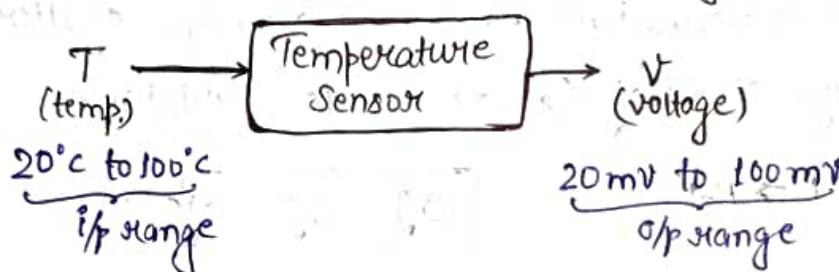Characteristics of Instrumentation System




Input span: Difference b/w i/p and min. i/p values.

$$\text{Here, } \text{i/p span} = 100^\circ\text{C} - 20^\circ\text{C} = 80^\circ\text{C.}$$


Output span: Difference b/w o/p and min. o/p values.

$$\text{Here, o/p span} = 100\text{mV} - 20\text{mV} = 80\text{mV.}$$

Linear Sensor:

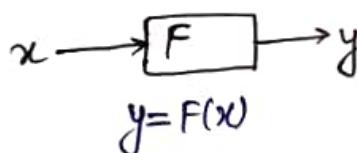

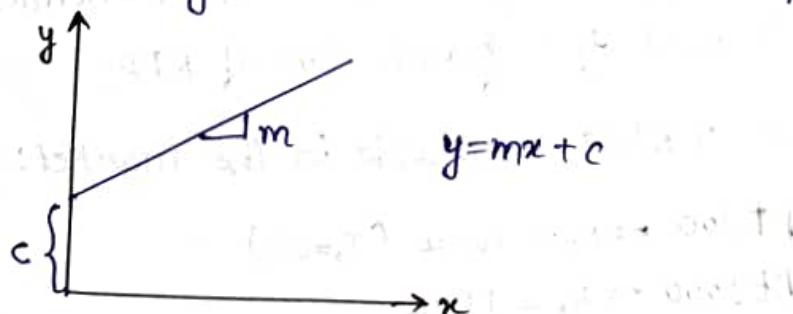We want our system to be linear (need not pass through origin)



↳ Eg.: RTD.

Resistance Temperature Detector (RTD): Gives o/p in resistance form.

$$R_T = R_0 [1 + \alpha(T - T_0)]$$

↓ ↓ ↓
Resistance Nominal Temperature Nominal
@ T resistance @ T_0 coefficient temperature

- R_T has linear relation with T , so RTD is "linear sensor".
- RTDs are generally made of metal.
- $T \uparrow \Rightarrow$ Atoms undergo significant motion from equilibrium position (more vibration) \Rightarrow more charge scattering \Rightarrow less avg. speed of e^- \Rightarrow more resistance.

So, $\boxed{T \uparrow \Rightarrow R \uparrow}$ $\boxed{O \downarrow O \downarrow O \downarrow} \rightarrow \text{metal}$

$$R_T = R_0 [1 + \alpha(T - T_0) + \beta(T - T_0)^2 + \gamma(T - T_0)^3]$$

If we choose correct metals like Pt, then above relation will become almost linear and sensor will also become linear.

~~Ex.~~ (β, γ can be removed by ~~left~~ as per the choice of metals)

For Pt $\Rightarrow \alpha \gg \beta \gg \gamma$

$$\alpha = 0.0039/\text{°C}$$

$$\beta = 5.7 \times 10^{-7}/\text{°C}^2$$

→ We can use copper (high α) but due to chemically inert nature of Pt, it is used for fabrication of RTD.

→ There are 3 RTDs available in the market:


$$\text{Pt 100} \Rightarrow R_0 = 100\Omega \quad (T_0 = 0\text{°C})$$

$$\text{Pt 1000} \Rightarrow R_0 = 1\text{ k}\Omega$$

$$\text{Pt 10000} \Rightarrow R_0 = 10\text{ k}\Omega$$

Optimal working range: $[-100\text{°C}, 600\text{°C}]$.
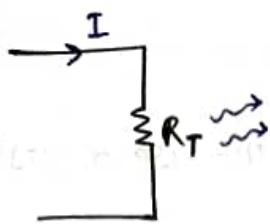
$$R_{600} = 100 [1 + 0.0039 \times 600] = 334\Omega$$



Power

$$\text{dissipation} = I^2 R_T \Rightarrow \text{rise in temp.} \rightarrow \text{self heating}$$

(Should be as minm)
as possible

Self-heating: Local rise in temperature due to power dissipation

Power dissipation factor (P_0): Power required for RTP to raise the temperature by 1°C .

Rise in temperature :


$$\Delta T = \frac{I^2 R_T}{P_0}$$

Non-Linear Sensor

↳ Eg. Thermistor

Thermistor : Thermally sensitive resistor.



↳ made of semiconductor materials.

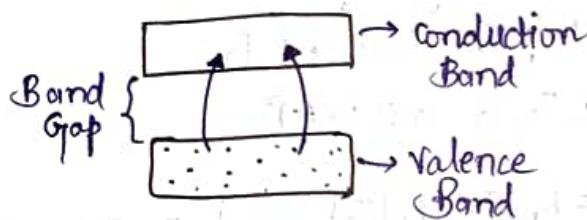

$T \uparrow \Rightarrow$ more free $e^- \Rightarrow R \downarrow$

↳ Also called NTC thermistor.

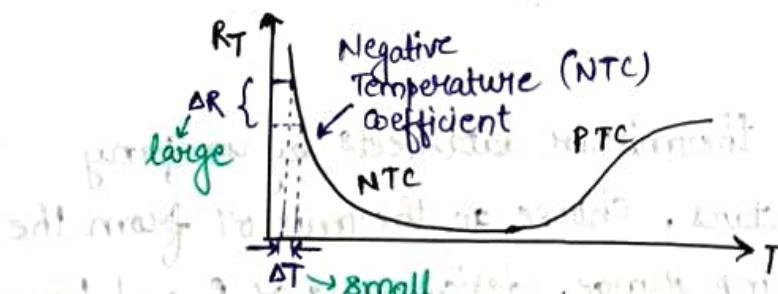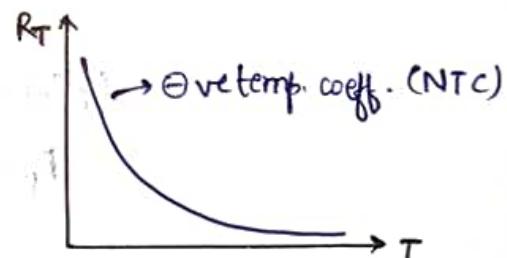↳ On large no. of e^- in conduction band, semiconductor behaves like metal then it becomes PTC thermistor.





↳ We should use thermistor in high attenuation area because we can detect large R change on minute temperature variation.

↳ Not preferred in wide span: $R_T = A e^{\frac{B}{T+C}}$

Improving linearity of thermistor:

→ To increase linearity/reduce non-linearity, we use a resistance R_o in || to thermistor.

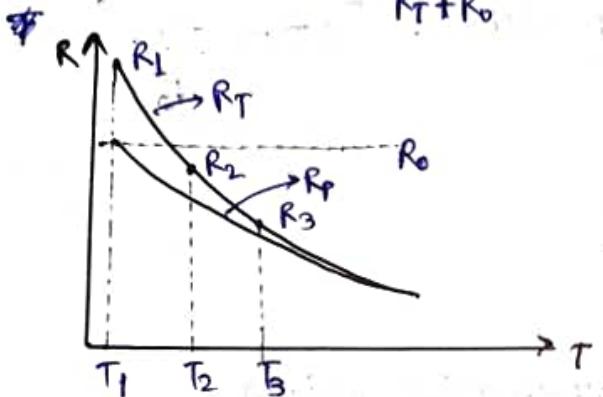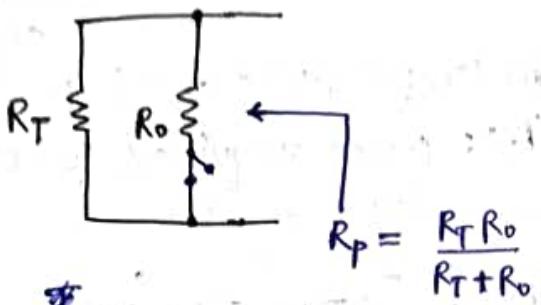

T_1, T_2, T_3 : temp. Range of thermistor

T_2 : middle point b/w T_1 & T_3 .

So, T_1, T_2, T_3 are in A.P.

$$R'(T_2) - R_p(T_1) = R_p(T_3) - R_p(T_2)$$

$$R_p = \frac{R_T R_o}{R_T + R_o}$$

$$R_T @ T_1 = R_1$$

$$R_T @ T_2 = R_2$$

$$R_T @ T_3 = R_3$$

Derive R_o :

$$R_o = \frac{R_2(R_1+R_3) - 2R_1R_3}{R_1+R_3-2R_2}$$

Assignment: Loop up at thermistor datasheets by company

Vishay Semiconductors. Choose an thermistor from the website. Choose temp. range, design value of R_o and linearize the thermistor.

Derivation of R_o :

$$R_p(T_2) - R_p(T_1) = R_p(T_3) - R_p(T_2)$$

$$\Rightarrow 2R_p(T_2) = R_p(T_1) + R_p(T_3)$$

$$As \Rightarrow R_p = \frac{R_T R_o}{R_T + R_o},$$

$$\Rightarrow 2 \frac{R_2 R_o}{R_2 + R_o} = \frac{R_1 R_o}{R_1 + R_o} + \frac{R_3 R_o}{R_3 + R_o}$$


$$\Rightarrow 2 R_2 (R_1 + R_o) (R_3 + R_o) = [R_1 (R_3 + R_o) + R_3 (R_1 + R_o)] (R_2 + R_o)$$

$$\Rightarrow 2 R_1 R_2 R_3 + 2 R_o^2 R_2 + 2 R_o R_2 (R_1 + R_3) = 2 R_1 R_2 R_3 + R_o^2 (R_1 + R_3) \\ + 2 R_o R_1 R_3 + R_o R_2 (R_1 + R_3)$$

$$\Rightarrow 2 R_o R_2 + 2 R_2 (R_1 + R_3) = R_o (R_1 + R_3) + 2 R_1 R_3 + R_2 (R_1 + R_3)$$

$$\Rightarrow R_2 (R_1 + R_3) - 2 R_1 R_3 = R_o (R_1 + R_3) - 2 R_o R_2$$
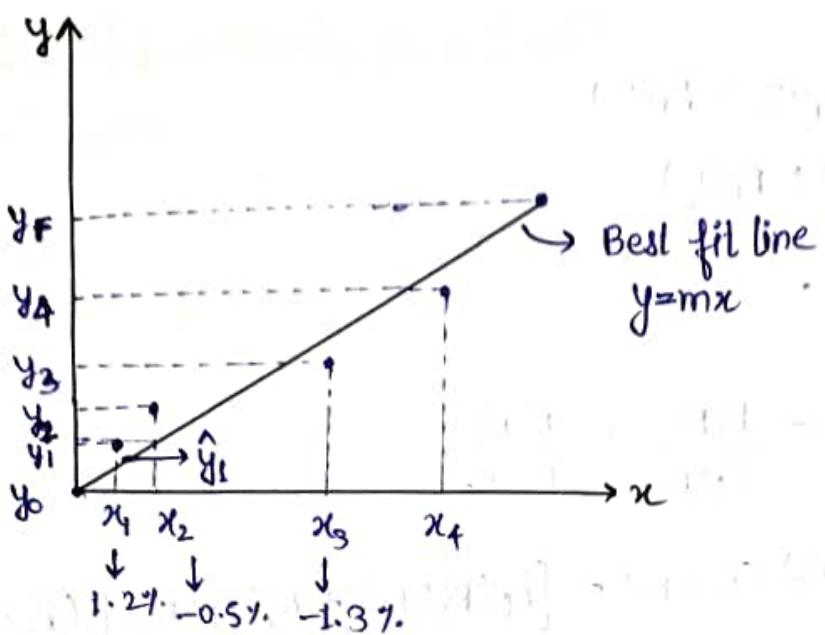
$$\Rightarrow R_o = \frac{R_2 (R_1 + R_3) - 2 R_1 R_3}{R_1 + R_3 - 2 R_2}$$



deviation/non-linearity = $y_i - \hat{y}_i$

y_F : full scale reading

$y_F - y_0$: span (o/p span)

$$\% \text{ non-linearity} / \% \text{ deviation} = \frac{y_i - \hat{y}_i}{y_F - y_0} \times 100\%$$


Sensor non-linearity: Worst-case non-linearity, here = $\pm 1.3\%$.
(maxm deviation)


Sensitivity(s): Rate of change of output wrt. input
= m = slope of characteristic

s = constant, for linear sensor

s = variable, for non-linear sensor.

To measure displacement 'x' of shaft:

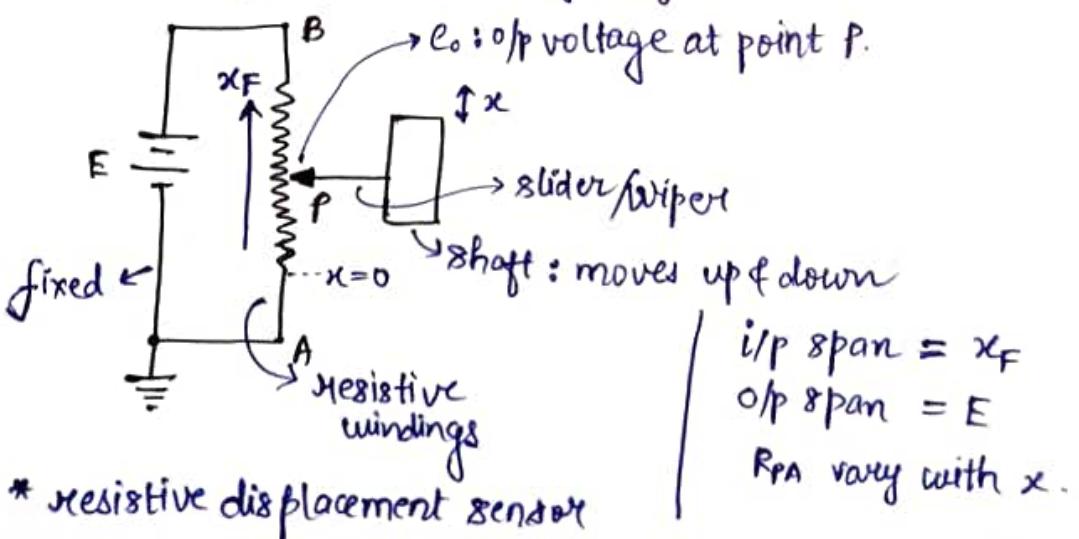

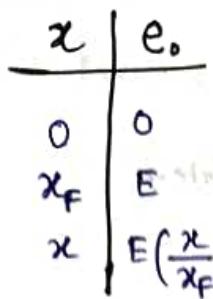


$$e_o = \left(\frac{E}{x_F}\right)x = y = mx \rightarrow \text{linear sensor}$$

$$\delta = \frac{E}{x_F}$$

Let $E = 5V$, $x_F = 10\text{ mm}$.

$$\text{Then, } \delta = \frac{5V}{10\text{ mm}} = 500 \frac{\text{mV}}{\text{mm}} = 500 \frac{\mu\text{V}}{\mu\text{m}} = 500 \frac{\text{nV}}{\text{nm}}$$

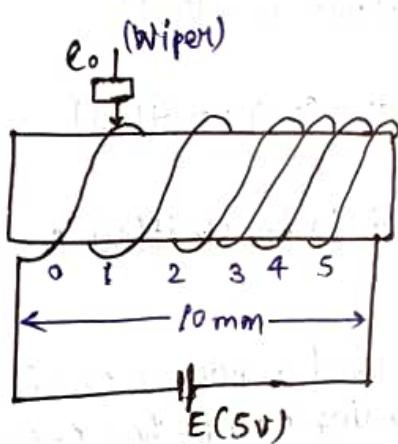Writing the units does not mean we can measure upto these level of displacements.



$$N = 6, x_F = 10\text{ mm}, E = 5V$$

$e_o = 0V$ at $x=0$

$e_o \neq 0V$ at $x=2\text{ mm}$.

When wiper moves by 2 mm, then o/p will change.

$$\text{Input Resolution } (\eta) = 2\text{ mm} = \frac{10\text{ mm}}{6-1} = \frac{x_F}{N-1}$$

Min. ~~value~~ change in the input that can be detected in output.

$$\boxed{\eta = \frac{x_F}{N-1}}$$

$$N \gg 1 \Rightarrow$$

$$\boxed{\eta \approx \frac{x_F}{N}}$$

For a potentiometric displacement sensor.

$$\text{Output Resolution} = Sq = 5 \text{ mV}$$


↪ Minⁿ value of the o/p that the sensor can detect.

Let $N = 1000$, $x_F = 10 \text{ mm}$, $E = 5 \text{ V}$,
then $q = 10 \mu\text{m}$,

$$S = 500 \frac{\mu\text{V}}{\text{mm}}$$

$$\text{o/p resolution} = Sq = 5 \text{ mV}.$$

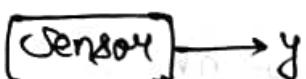The o/p change will come in resolution of 5 mV, like
0, 5 mV, 10 mV, ...



Measured value (MV) \neq True value (TV)

$$\text{Error} = MV - TV \quad (\text{unit: same as output})$$

$$\% \text{ error} = \frac{MV - TV}{\text{ref. value}} \times 100\% \quad (\text{unit: unitless})$$

↪ we want error unit to be unitless so, we can divide by ref. value.

$$\begin{aligned} \text{Ref value} &= TV \\ &= MV \\ &= \text{Span} \end{aligned} \quad \begin{array}{l} \Rightarrow \text{not used as } MV/TV \text{ can become 0 if} \\ \text{reading can be b/w } (-50, 50), \text{ so high} \\ \text{error will come} \end{array}$$

Span is used as ref. value.

$$\% \text{ error} (\text{span}) = 1\% : \text{Class-1 instrument}$$

$$\% \text{ error} (\text{span}) = 5\% : \text{Class-5 instrument}$$

Q Class-1 pressure sensor; Range: 0 to 50 bar.

Find % error when true value (TV) = 10 bar.

$$\text{Soln: } \% \text{ error} = \frac{MV - TV}{50} \times 100\% = 1\% \quad (\text{Span} = 50)$$


$$\Rightarrow MV - TV = 0.5 \text{ bar}$$

$$\text{When } TV = 10 \text{ bar}, \% \text{ error} = \frac{0.5 \text{ bar}}{10 \text{ bar}} \times 100\% = 5\%$$

$$\text{When } TV = 1 \text{ bar}, \% \text{ error} = \frac{0.5 \text{ bar}}{1 \text{ bar}} \times 100\% = 50\%$$

$\Rightarrow 1 \text{ bar} \pm 0.5 \text{ bar}$

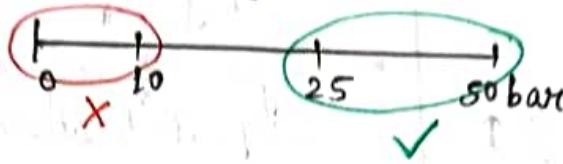To reduce the error, we should operate our sensor in high regimes, not low regimes/levels.




Calibration

15-01-2024


error: 0.1 mm (say)

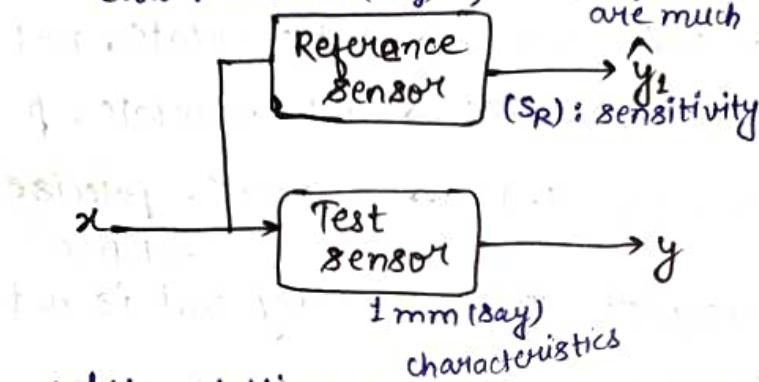similar to test sensor, but performance & specification are much better.



While plotting x - y , y can be found out by looking at the o/p of test sensor ; to know x , we use a reference sensor whose properties are well-known.

$$x_1 = \frac{\hat{y}_1}{S_R}$$

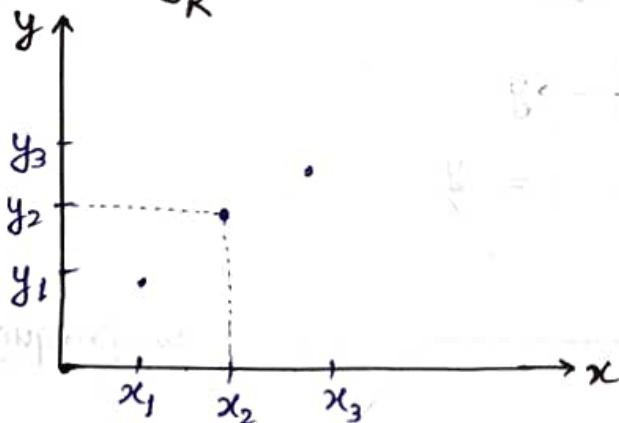

In practice, reference sensor can be costlier and bulky, etc. So, in field, we remove reference sensor, get a value, say y_2 , from test sensor, and predict the i/p, x_2 , using the calibrated data.

Accuracy and Precision

Accuracy

- Closeness to truth (true value).
- Error $\downarrow \Rightarrow$ Accuracy \uparrow

Eg: TV = 5 mm

3 instruments : 5 values each

- Ⓐ: 4.7, 4.6, 4.6, 4.7, 4.8 \rightarrow not accurate, not precise
- Ⓑ: 4.74, 4.74, 4.75, 4.75, 4.76 \rightarrow not accurate, precise
- Ⓒ: 4.99, 5.01, 5.00, 5.01, 4.99 \rightarrow accurate, precise

Relative


\rightarrow Precision is a pre-requisite for accuracy but is not the guarantee for accuracy.

Bandwidth (BW)

\hookrightarrow Useful range of frequencies where the system/sensor ~~works~~ can be used.



$$\text{Sensitivity, } S = \frac{y}{x}$$

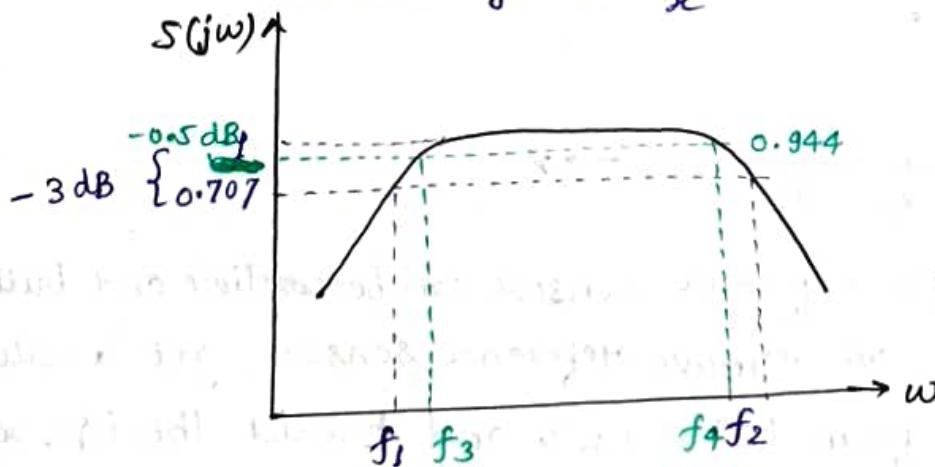

w: frequency of x

$$BW = f_2 - f_1$$

Ideal value of $S = 1$

At f_1, f_2 , actual value of $S = 0.707$

error $\approx -30\%$. ($= -29.3\%$)

↳ Too much error
(Not useful)

So, we use a conservative approach. Take say -0.5 dB , as the frequency.

$$20 \log_{10} S = -0.5$$

$$S = (10)^{-0.5/20} = 0.944$$

At f_3, f_4 , actual value of $S = 0.944$

error $\approx 5\%$.

Measurement Errors

Measuring voltages using 2 voltmeters,

$$V_1 = 10 \text{ V} \pm 0.1 \text{ V} \rightarrow \text{error} = \frac{0.1}{10} \times 100\% = 1\%$$

$$V_2 = 1 \text{ V} \pm 0.1 \text{ V} \rightarrow \text{error} = 10\%$$

$$V_1 + V_2 = 11 \text{ V} \pm 0.2 \text{ V} \rightarrow \text{error} = 1.8\%$$

$$V_1 - V_2 = 9 \text{ V} \pm 0.2 \text{ V} \rightarrow \text{error} = 2.2\%$$

$< 10\%$, so OK!

Now, say

$$V_1 = 10 \text{ V} \pm 0.1 \text{ V} \rightarrow \text{error} = 1\%$$

$$V_2 = 9 \text{ V} \pm 0.1 \text{ V} \rightarrow \text{error} = 1.1\%$$

$$V_1 - V_2 = 1 \text{ V} \pm 0.2 \text{ V} \rightarrow \text{error} = 20\% \quad \} \text{error shoot up!}$$

→ Never take difference b/w two experimental values which are close to each other.

Transformer:

Efficiency, $\eta = 98\%$ or above (typical value)

$$= \frac{P_o}{P_I} \times 100\%, P_o : \text{Output power}$$

$$P_I : \text{Input power}$$

$$\Rightarrow P_o = 0.98 P_I$$

$$\text{Losses} = P_I - P_o$$

$$P_I = 1W \pm 0.01W \quad (\text{say})$$




$$P_o = 0.98W \pm 0.01W$$

$$\text{Losses} = 0.02W \pm 0.02W \rightarrow 100\% \text{ error} \quad \{ \text{Never do this!}$$

To find losses of a transformer, use techniques like short-circuit test, open-circuit test.

16-01-2024


Measurement Errors:

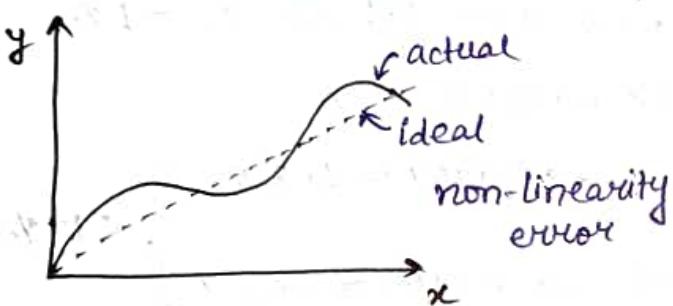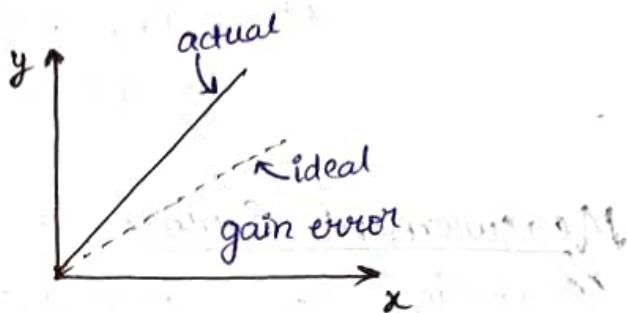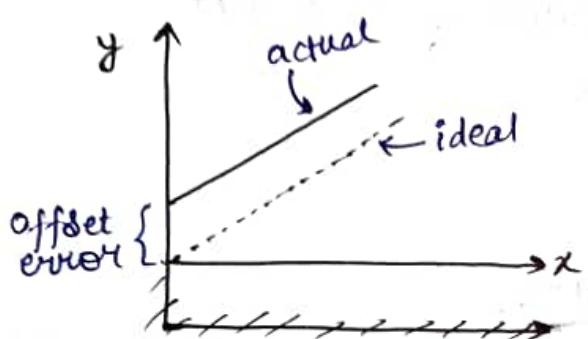

① Identify the error.

② Analyse

③ Compensate

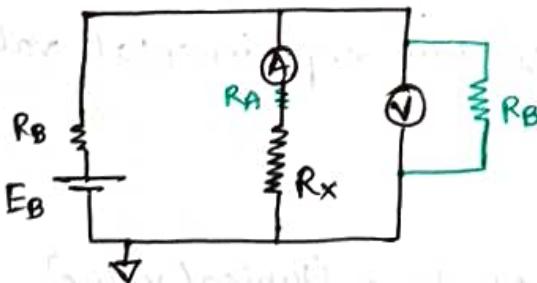

$$\text{M.V.} = \frac{V}{A} = R_x = \text{T.V.}$$

Due to error, $\text{M.V.} = \frac{V}{A} = R_x + R_A$

$$\% \text{ error} = \frac{R_x + R_A - R_x}{R_x} \times 100\% = \frac{R_A}{R_x} \times 100\%$$

↳ does not depend on battery (battery quality can be compromised)


To reduce the error,

$R_A \ll R_x$: High quality ammeter required;

voltmeter quantity can be compromised
(Independent of voltmeter)

↳ suitable for high Rx estimation

To measure low Rx,

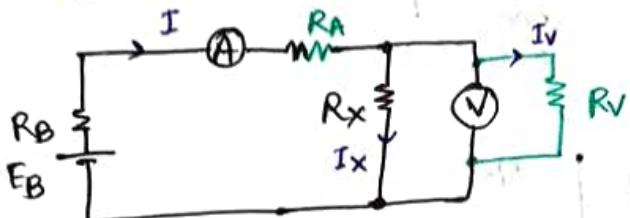

$$M.V. = R_x \parallel R_N$$

$$\% \text{ error} = \frac{\frac{R_x R_V}{R_x + R_V} - R_x}{R_x} \times 100\%$$

$$= \frac{R_x R_V - R_x^2 - R_x R_V}{R_x + R_V} \times 100\%$$

$$= - \frac{R_x}{R_x + R_y} \times 100\%$$


To reduce the error,

$$R_V \gg R_X$$

↳ These setups require both ammeter and voltmeter.

↳ Not suitable for end-user.

To measure the sensor resistance R_x :

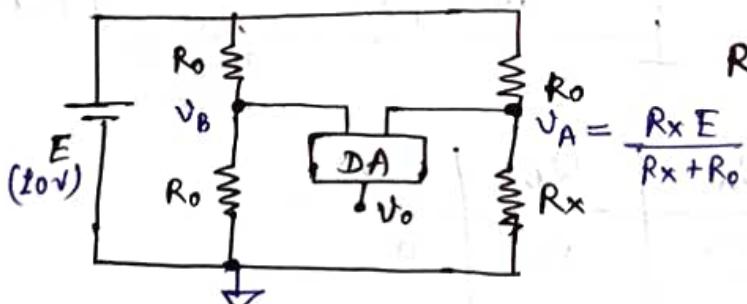

$$R_x = R_0 [1+x]$$

$$\frac{E}{R_0}$$


DA: difference amplifier
gain, $G_1 = 1$
high input impedance

$$\Rightarrow R_0 = 100 \Omega, x \in [0, 0.01]$$

X	v_A	v_B	v_o
0	$E_f/2$	$E_f/2$	0
0.01	$\frac{0.01E}{2.0f}$	$E_f/2$	24.8 mV

Source of error:

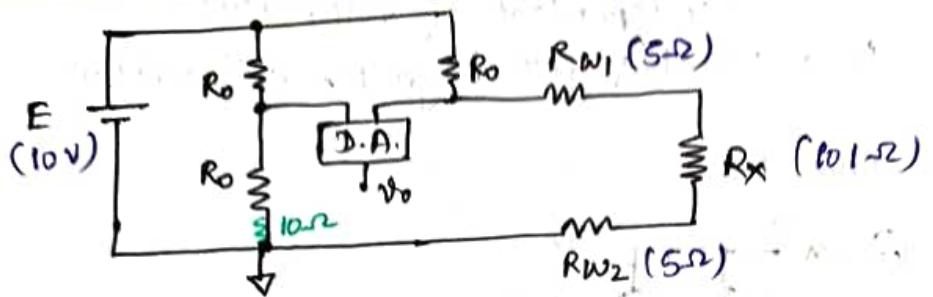Suppose the electronics are at a harsh, hazardous place.
Sensor should be kept far from such places.



X	V _A	V _B	V _O
0	$\frac{110}{210} E$	$E/2$	238 mV
0.01	$\frac{111}{211} E$	$E/2$	261 mV

} Large offset error


Compensation of error:

- ① Subtract 238 mV from DA using microcontroller.
- ② Connect a resistance of 10Ω in series with R_o .

In that way, $V_o (x=0) = 0$

But, these solutions fail miserably b/c R_{W1} & R_{W2} are unknown and changing.



Solution:

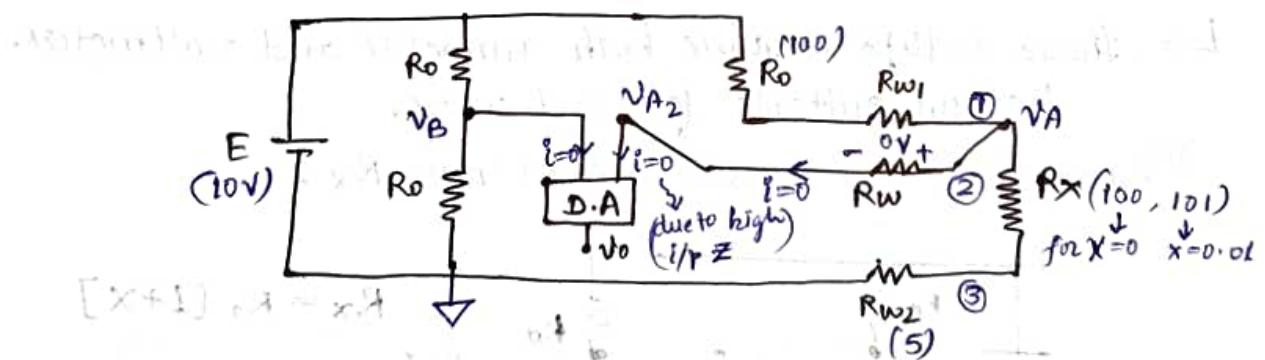

X	V _A	V _B	V _O
0	$\frac{105}{210} E$	$E/2$	0
0.01	$\frac{106}{211} E$	$E/2$	23.7 mV

In scenario where $R_{W1} \neq R_{W2}$, this model will not work.

Resistive Sensors

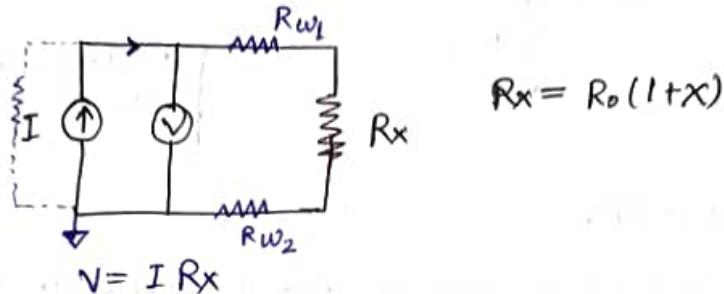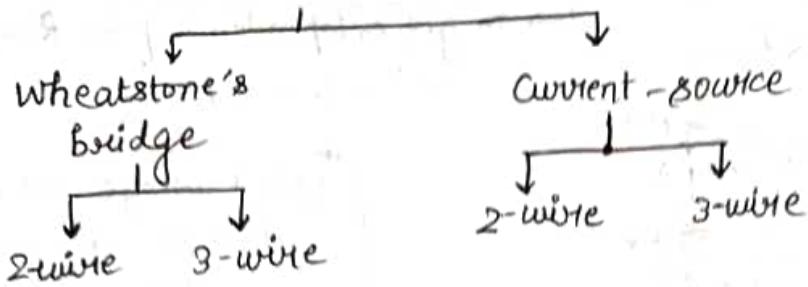

$$R_x = R_0(1+x)$$


When $x=0$, $V_o = IR_0 \rightarrow$ finite offset when $x=0$. : Disadvantage

[In wheatstone bridge circuit, $V_o = 0$ for $x=0$]

↳ preferred in some application

$$V = I(R_x + R_{W1} + R_{W2})$$

Lead-wire compensation:

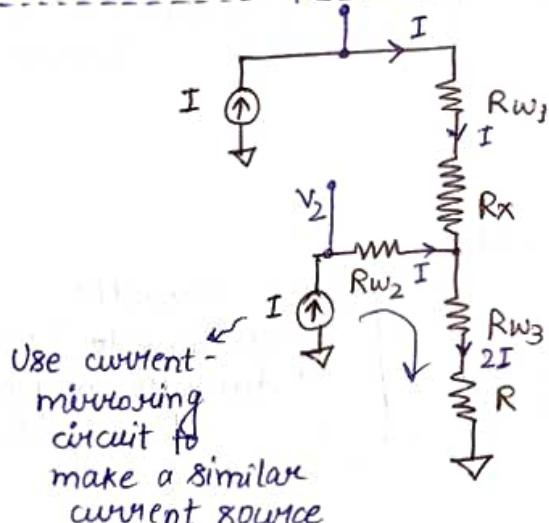

$$V_1 = I(R_x + R_{W1}) + 2I(R_{W3} + R)$$


$$V_2 = IR_{W2} + 2I(R_{W3} + R)$$

$$V_1 - V_2 = I(R_x + R_{W1} - R_{W2})$$

$R_{W1} = R_{W2}$ (lead wires should have same resistances)

$\Rightarrow V_1 - V_2 = IR_x \rightarrow$ Use D.A. to get the difference; not manually.

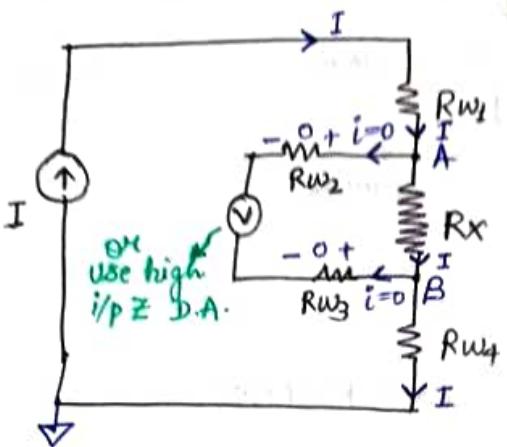4-wire connection: Using only one current source.



→ To get independence from R_{W2} and mismatching.


- # Offset voltage will be there in any current-source method.
- # Electronics will be placed far from the sensor.

$$V = V_{AB} = IR_X$$

Q Is it possible to lead-wire compensation (compensate R_{W1}, R_{W2}, \dots) using 2-wire method?

→ Yes!


Summary:

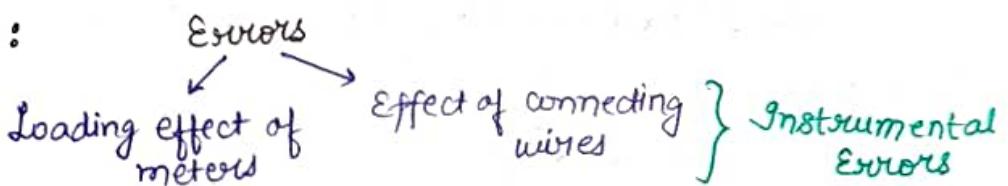

A Instrumental errors

B Environmental Errors

Eg. Measuring current in a wire

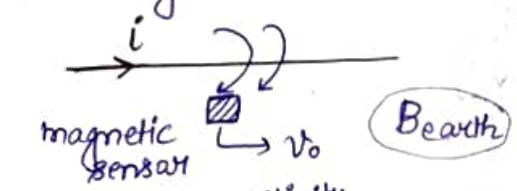

Using ammeter
→ we have to break the wire.
→ Ammeter may burn due to high i.

$$V_o = K_1 B$$

$$B = K_2 i$$


$$\Rightarrow V_o = K_1 K_2 i = K_i + K_1 B_{\text{earth}}, \quad K = K_1 K_2$$

dc ($f=0$)

error due to earth's mag. field

constant ⇒ offset

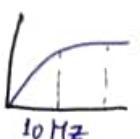To remove the offset error (dc component),
use high-pass filter of $f_c < 50 \text{ Hz}$.



① Observational Errors


- ↳ Human errors due to parallax.
- ↳ Not relevant nowadays as most sensors are digital.

↳ The source of these errors are well-known and can be their effect can be nullified by simple systematic methods.
↓

Systematic Errors


Random Errors (noise): Fluctuations even when all systematic errors are compensated.

- ↳ Erratic, random

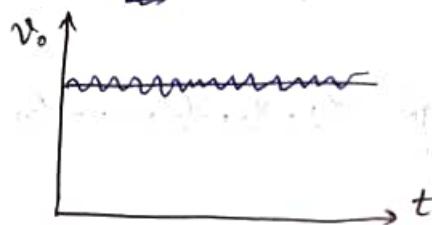

↳ Their source may be known.

Eg.
Analog meter:

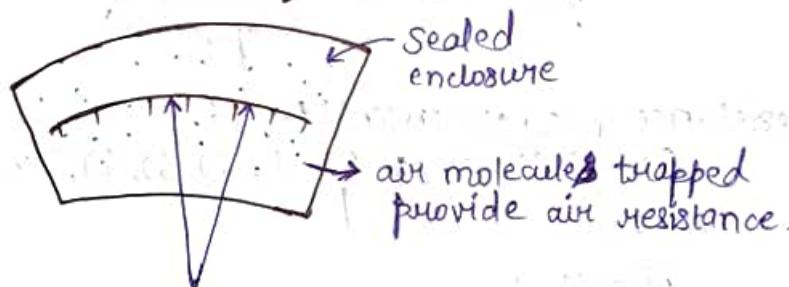

Eg. Thermal noise \Rightarrow depends upon R, T, B

$$V_o = \frac{R}{2\pi f C} \approx 20 \text{nV}$$

↳ Thermal noise \Rightarrow depends upon R, T, B

($R = \rho A L$) and all resistances will form N nodes

Measurement Errors

↓
Systematic Random

↳ Source known

↳ Source may be known or unknown
↳ Difficult to remove.

Random Errors:


- ① Nullify all systematic errors.
- ② Repeated measurements of the physical variable, using same equipment, under the same operating conditions.
- ③ Average of repeated readings.

x : measurand

Take the readings $x_1, x_2, x_3, \dots, x_n$

$$\bar{x} = \frac{1}{n} \sum_{i=1}^n x_i$$

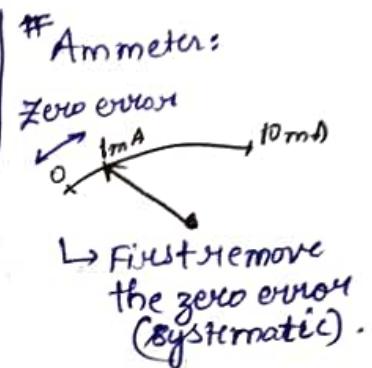$\bar{x} \pm \delta$, δ : measure of dispersion



Eg. Resistance measurements (Ω):

63, 66, 66, 67, 67, 68, 69, 69, 69, 69, 70, 70, 71
 $n=13$

$$\bar{x} = 68.5\Omega$$

- ① Limiting error (L) = 5 \Rightarrow One of the method to specify 80% readings lie b/w $(\bar{x}-L, \bar{x}+L)$.

$$68 \pm 5$$

L : conservative quantity

↳ depends on each and every measurement.

- ② Probable Error (P) = 1 \Rightarrow common in the US.

50% of the readings lie b/w $(\bar{x}-P, \bar{x}+P)$
(at least 50%)

$$\frac{13}{2} \approx 7$$

$$P=1$$

↳ Mathematical treatment is difficult.

↳ More optimistic.

③ Standard Deviation (σ)

$$\textcircled{A} \quad \sigma = \sqrt{\frac{1}{n} \sum_{i=1}^n (x_i - \bar{x})^2} \times$$

$$\textcircled{B} \quad \sigma = \sqrt{\frac{1}{n-1} \sum_{i=1}^n (x_i - \bar{x})^2} \quad \checkmark$$

In most cases, $n \gg 1$.

Eg. $n=1$

$$x_1 = 63$$

$$\bar{x} = 63$$

$$\sigma_A = 0 \quad \times$$

$$\sigma_B = \frac{0}{0} \quad \checkmark \quad [\text{For } n=1, \sigma \text{ should be un-deterministic.}]$$

Eg.

$$R_1 = 68 \pm 3\Omega$$


$$R_2 = 51 \pm 2\Omega$$

$$\begin{matrix} \uparrow \\ \text{avg.} \end{matrix} \quad \begin{matrix} \uparrow \\ \sigma \end{matrix}$$

$$\sigma_{R_1} = 3\Omega$$

$$\sigma_{R_2} = 2\Omega$$

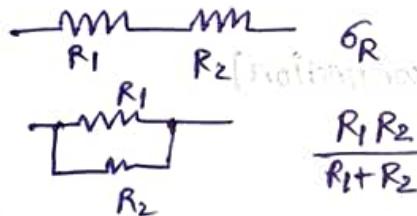Resistors can be combined in any fashion:



Propagation of σ :

Measurands: $u, v \rightarrow$ independent variables

\hookrightarrow value of one doesn't affect the other.

$X = f(u, v)$; Find σ_X when σ_u & σ_v are known.

σ_u :

$$u_1$$

$$u_2$$

$$\vdots$$

$$u_n$$

$$\Delta u_1 = u_1 - \bar{u}$$

$$\Delta u_2 = u_2 - \bar{u}$$

$$\vdots$$

$$\Delta u_n = u_n - \bar{u}$$

$$\sigma_u^2 = \frac{1}{n-1} \sum_{i=1}^n (\Delta u_i)^2$$

$$\sigma_v^2 = \frac{1}{n-1} \sum_{i=1}^n (\Delta v_i)^2$$

$$\text{To find } \sigma_x^2 = \frac{1}{n-1} \sum_{i=1}^n \Delta x_i^2$$

$$\Delta x_i = \left(\frac{\partial f}{\partial u} \right) \Delta u_i + \left(\frac{\partial f}{\partial v} \right) \Delta v_i$$

$$\Rightarrow \sum_{i=1}^n \Delta x_i^2 = \left(\frac{\partial f}{\partial u} \right)^2 \sum_{i=1}^n \Delta u_i^2 + \left(\frac{\partial f}{\partial v} \right)^2 \sum_{i=1}^n \Delta v_i^2 + 2 \frac{\partial f}{\partial u} \cdot \frac{\partial f}{\partial v} \sum_{i=1}^n (\Delta u_i \Delta v_i)$$

[Σ is independent of i]

$\Delta u_i^2 \geq 0$
 Δu_i can be \oplus ve or \ominus ve
 Product of 2 random errors
 summing for large n
 ~ 0

$$\therefore \sigma_x^2 = \left(\frac{\partial f}{\partial u} \right)^2 \sigma_u^2 + \left(\frac{\partial f}{\partial v} \right)^2 \sigma_v^2$$

$$\text{Eg. } X = f(w_1, w_2, w_3, \dots, w_m)$$

$$\sigma_x^2 = \left(\frac{\partial f}{\partial w_1} \right)^2 \sigma_{w_1}^2 + \left(\frac{\partial f}{\partial w_2} \right)^2 \sigma_{w_2}^2 + \dots + \left(\frac{\partial f}{\partial w_m} \right)^2 \sigma_{w_m}^2$$

$$\text{Eg. } R_1 = 68 \pm 3 \Omega \xleftarrow{\sigma_{R_1}}$$

$$R_2 = 51 \pm 2 \Omega \xleftarrow{\sigma_{R_2}}$$

$$R = R_1 + R_2 \quad (\text{Series connection})$$

$$\frac{\partial R}{\partial R_1} = \frac{\partial R}{\partial R_2} = 1$$

$$\sigma_R^2 = \left(\frac{\partial R}{\partial R_1} \right)^2 \sigma_{R_1}^2 + \left(\frac{\partial R}{\partial R_2} \right)^2 \sigma_{R_2}^2$$

$$\sigma_R = \sqrt{13} \Omega$$


$$R = \frac{R_1 R_2}{R_1 + R_2} \quad (\text{Parallel connection})$$

$$\frac{\partial R}{\partial R_1} = \left(\frac{R_2}{R_1 + R_2} \right)^2 = \left(\frac{51}{119} \right)^2$$

$$\frac{\partial R}{\partial R_2} = \left(\frac{R_1}{R_1 + R_2} \right)^2 = \left(\frac{68}{119} \right)^2$$

$$\sigma_R^2 = \left(\frac{\partial R}{\partial R_1} \right)^2 \sigma_{R_1}^2 + \left(\frac{\partial R}{\partial R_2} \right)^2 \sigma_{R_2}^2$$

Eg.

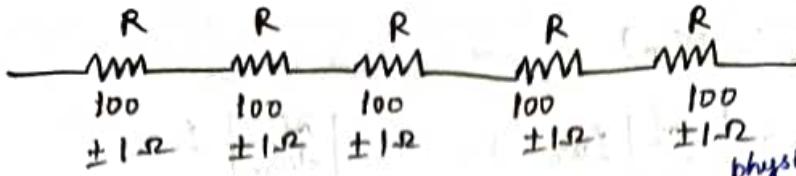

$R_T \neq 5R$ [All R measurements are independent of each other]

$$= R_1 + R_2 + R_3 + R_4 + R_5$$

[In parallel connection,
 $R_T \neq R/5$, $\frac{\partial R}{\partial R_i} \neq \frac{1}{5}$
 $R_T = R_1 \parallel R_2 \parallel R_3 \parallel R_4 \parallel R_5$]

24-01-2024

Propagation of Limiting Errors

$$u \rightarrow u \pm L_u$$

$$v \rightarrow v \pm L_v$$

$$x = f(u, v)$$

$$L_x = ?$$

$$\Delta u_1$$

$$\Delta u_2$$

:

$$\Delta u_n$$

$$L_u = \max(|\Delta u_i|)$$

$$\text{Similarly, } L_v = \max(|\Delta v_i|)$$

$$L_x = \max(|\Delta x_i|)$$

$$\text{As } |\Delta x_i| = \left| \frac{\partial f}{\partial u} \Delta u_i + \frac{\partial f}{\partial v} \Delta v_i \right|$$

$$\Rightarrow |\Delta x_i| \leq \left| \frac{\partial f}{\partial u} \right| |\Delta u_i| + \left| \frac{\partial f}{\partial v} \right| |\Delta v_i|$$

$$|\Delta x_i|_{\max} = \left| \frac{\partial f}{\partial u} \right|_{\max} |\Delta u_i| + \left| \frac{\partial f}{\partial v} \right|_{\max} |\Delta v_i|_{\max} \quad (\text{worst case})$$



$$L_x = \left| \frac{\partial f}{\partial u} \right| L_u + \left| \frac{\partial f}{\partial v} \right| L_v$$

$$\text{Eq. } x = f(w_1, w_2, w_3, \dots, w_m)$$

$$L_x = \left| \frac{\partial f}{\partial w_1} \right| L_{w_1} + \left| \frac{\partial f}{\partial w_2} \right| L_{w_2} + \dots + \left| \frac{\partial f}{\partial w_m} \right| L_{w_m}$$

$$\text{Eq. } R_1 = 68 \pm 3 \Omega \quad L_{R_1}$$

$$R_2 = 51 \pm 2 \Omega \quad L_{R_2}$$

$$R = R_1 + R_2 = 119 \pm L_R \Omega$$

$$L_R = L_{R_1} + L_{R_2} = 5 \Omega$$

$$L_x = \left| \frac{\partial f}{\partial u} \right| L_u + \left| \frac{\partial f}{\partial v} \right| L_v$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$L_R = \left| \frac{\partial R}{\partial R_1} \right| L_{R_1} + \left| \frac{\partial R}{\partial R_2} \right| L_{R_2}$$

How many repeated measurements (n) should we take?

x : measurand

	Case A	Case B
	$n_A = 10$	$n_B = 90$
using different 10 readings	\bar{x}_{A_1} \bar{x}_{A_2} \bar{x}_{A_3} \downarrow More deviation among the means \Downarrow measured using standard deviation among means ($\sigma_{\bar{x}}$)	\bar{x}_{B_1} \bar{x}_{B_2} \bar{x}_{B_3} \downarrow Less deviation among the means

$$\sigma_{\bar{x}} \propto \frac{1}{\sqrt{n}}$$

$$\frac{\sigma_{\bar{x}_B}}{\sigma_{\bar{x}_A}} = \sqrt{\frac{n_A}{n_B}} = \frac{1}{3}$$

$$\Rightarrow \sigma_{\bar{x}_B} = \frac{\sigma_{\bar{x}_A}}{3}$$

→ Precision has improved by a factor of 3.

→ Need 80 more measurements to get precision
⇒ Not enough return

Eg. $n_c = 1,00,000$ \rightarrow Long time
 $\sigma_{\bar{x}_c} = \frac{\sigma_{x_1}}{100}$ Operating conditions need to be the same throughout the time (using same instrument).

$$\rightarrow \text{Mean}, \bar{x} = \frac{1}{N} \sum_{i=1}^N x_i ; \quad \text{S.D., } \sigma = \sqrt{\frac{1}{N-1} \sum_{i=1}^N y_i^2}$$

Grouped Data Approach: Divide raw data into different ranges.

$$\text{Mean, } \bar{x} = \frac{1}{N} \sum_{\text{forall } R} x_R f(x_R)$$

$$\text{S.D., } \sigma = \sqrt{\frac{1}{N-1} \sum_{\text{forall } R} y_R^2 f(x_R)}$$

Sl. No.	Range	x_R	$f(x_R)$	$x_R f(x_R)$
---------	-------	-------	----------	--------------


y_R	$y_R^2 \cdot f(x_R)$
-------	----------------------

x_R : Midpoint of ranges


$f(x_R)$: no. of measurement points in the range that corresponds to x_R

$$y_R = x_R - \bar{x}$$

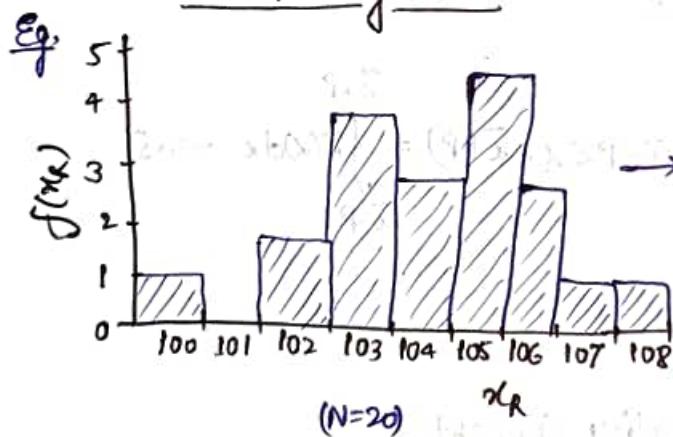Frequency distribution graph or histograms:



Probability Histograms:

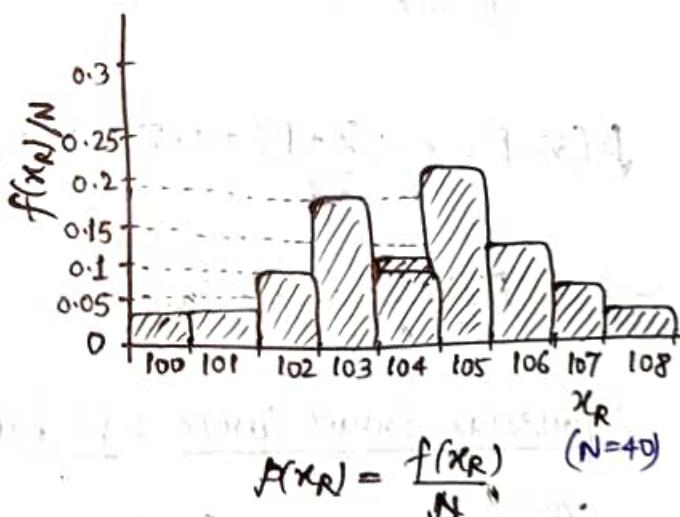


$\rightarrow \Delta x_R$: Width of the interval


Solution: Normalize $f(x_R)$ with respect to Δx_R

$$Z(x_R) = \frac{f(x_R)}{N \Delta x_R} = \frac{P(x_R)}{\Delta x_R}$$

\hookrightarrow Probability Distribution Function

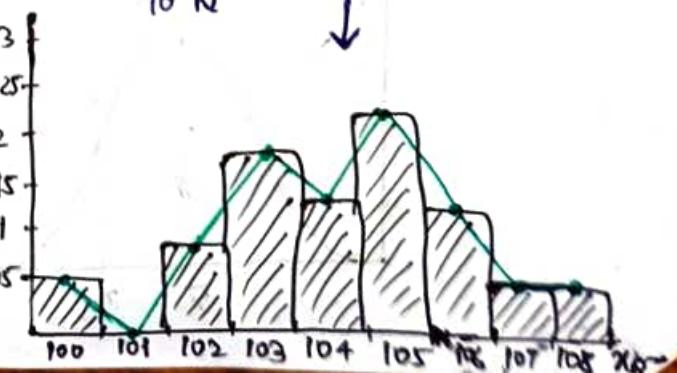Solution: Normalise $f(x_R)$ with respect to N



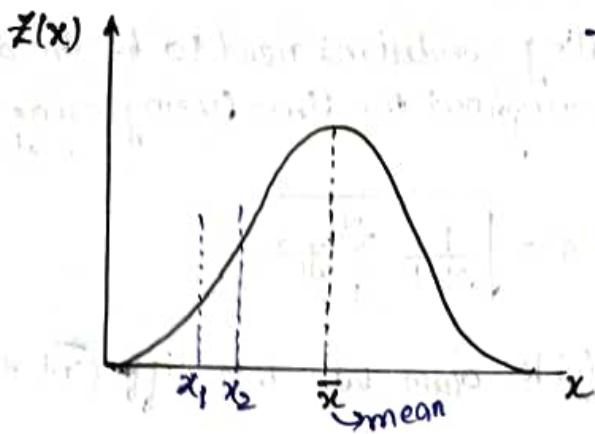

→ In any measurements, the repeated measurements will have highest probability close to mean.

→ Probability of random errors become lesser when we move away from.

→ Even (symmetric) about mean.

$$\beta(x_1 < x < x_2) = \int_{x_1}^{x_2} Z(x) dx$$

$$P(-\infty < x < +\infty) = \int_{-\infty}^{\infty} Z(x) dx = 1$$

P : Probable error

p : probability

$$\bar{x} = \frac{1}{N} \sum_{\text{forall } R} x_R \cdot f(x_R) = \sum_{\text{forall } R} x_R \cdot p(x_R) = \sum_{\text{forall } R} x_R \cdot Z(x_R) \cdot \Delta x_R \approx \int_{-\infty}^{\infty} x \cdot Z(x) dx$$


$$\sigma^2 = \frac{1}{N-1} \sum_{\text{forall } R} (x_R - \bar{x})^2 f(x_R) = \sum_{\text{forall } R} (x_R - \bar{x})^2 \cdot p(x_R)$$

$$= \sum_{\text{forall } R} (x_R - \bar{x})^2 \cdot Z(x_R) \cdot \Delta x_R \approx \int_{-\infty}^{\infty} (x - \bar{x})^2 Z(x) dx$$

$$\beta(\bar{x} - P < x < \bar{x} + P) = 0.5 \Rightarrow p(\bar{x} - P < x < \bar{x} + P) = \int_{\bar{x}-P}^{\bar{x}+P} Z(x) dx = 0.5$$

$$\rightarrow Z(x) = \frac{1}{\sigma \sqrt{2\pi}} e^{-\frac{(x-\bar{x})^2}{2\sigma^2}}$$

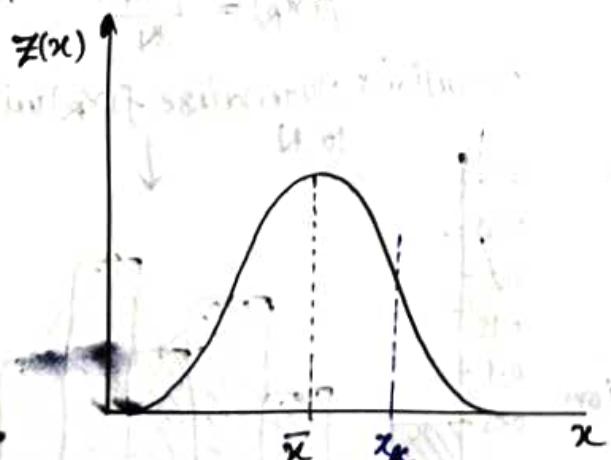Gaussian Error Curve : Probability Concept



$$Z(x) = \frac{1}{\sigma \sqrt{2\pi}} e^{-\frac{(x-\bar{x})^2}{2\sigma^2}}$$

$$P(\bar{x} < x < x_k) = \int_{\bar{x}}^{x_k} z(x) dx = \int_{\bar{x}}^{x_k} \frac{1}{\sigma \sqrt{2\pi}} e^{-\frac{(x-\bar{x})^2}{2\sigma^2}} dx$$

$$y = x - \bar{x}$$

$$y_k = x_k - \bar{x}$$

$$\Rightarrow P(0 < y < y_k) = \int_0^{y_k} \frac{1}{\sigma \sqrt{2\pi}} e^{-\frac{y^2}{2\sigma^2}} dy$$

\downarrow

$$\frac{y}{\sigma} = t$$

$$P(\bar{x} < x < x_k) = P(0 < t < y_k/\sigma) = \int_0^{y_k/\sigma} \frac{1}{\sqrt{2\pi}} e^{-\frac{t^2}{2}} dt$$

Eg.

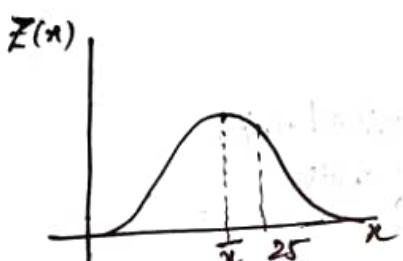


Table gives the integral value for some y_k/σ values.

$$\bar{x} = 21.9 \quad | \quad P(x > 25) = ?$$

$$P = 2.1 \quad | \quad N = 100 \Rightarrow n(x > 25) = ?$$

Soln: $P(\bar{x} - P < x < \bar{x} + P) = 0.5$

$$\Rightarrow P(\bar{x} < x < \bar{x} + P) = 0.25$$

$$\Rightarrow P(0 < y < P) = 0.25$$

$$\Rightarrow P(0 < t < P/\sigma) = 0.25$$

$$P \approx 0.2486 \quad (\text{from the table})$$

$$\Rightarrow P/\sigma = 0.67$$

$$\Rightarrow \sigma = \frac{2.1}{0.67}$$

$$= 3.1$$

$$\therefore P(x > 25) = 0.5 - P(\bar{x} < x < 25)$$

$$= 0.5 - P(0 < y < 25 - 21.9)$$

$$= 0.5 - P(0 < y < 3.1)$$

$$= 0.5 - P(0 < t < \frac{3.1}{3.1})$$

$$= 0.5 - P(0 < t < 1)$$

$$= 0.5 - 0.3413 \quad (\text{from table})$$

$$= 0.1587$$

$$\therefore n(x > 25) \approx 16.$$

Static Characteristics: Measurements when input is constant.

Long Term Performance

↓ to specify

Reliability (R)

↳ Indicator of whether a sensor or instrument has worked with agreed performance (accuracy, error, etc.) levels, over stated period, under specified conditions.

Eg. $A \rightarrow 60S, 40F \xrightarrow{\text{survived}}$ failed
 $B \rightarrow 55S, 45F$

} 100 units of
A & B

$\Rightarrow R_A > R_B$

$$R = \lim_{N \rightarrow \infty} \frac{N_s}{N}, \quad N_s : \text{no. of survived units}$$

N : total no. of units.

$$R_A = 0.6$$

$$R_B = 0.55$$

→ $R=1$: Ideal sensor

$R=0$: Poor sensor

Unreliability (F)

$$F = \frac{N_f}{N}, \quad N_f : \text{No. of failed units}$$

→ ~~R + F~~ $R(t) + F(t) = 1$

Time Independent Parameter:

Failure Rate (λ):

N_s : no. of survived units at time 't'.

ΔN_f units failed in $(t, t+\Delta t)$.

Probability of failure = $\frac{\Delta N_f}{N_s}$

$$\begin{aligned}\lambda &= \frac{1}{\Delta t} \frac{\Delta N_f}{N_s} \quad \rightarrow \text{normalized with time-span} \\ &= \frac{1}{N_s} \left(\frac{\Delta N_f}{\Delta t} \right)\end{aligned}$$

$$\Rightarrow \boxed{\lambda = \frac{1}{N_s} \left(\frac{d N_f}{dt} \right)}$$


$$\rightarrow R = \frac{N_S}{N} = 1 - \frac{N_F}{N}$$

$$\Rightarrow \frac{dR}{dt} = -\left(\frac{1}{N} \frac{dN_F}{dt}\right) \left(\frac{N_S}{N}\right)$$

$$\Rightarrow \frac{dR}{dt} = -\lambda R$$

$$\Rightarrow R = e^{-\int \lambda(t) dt}$$

Bath-tub Curve:

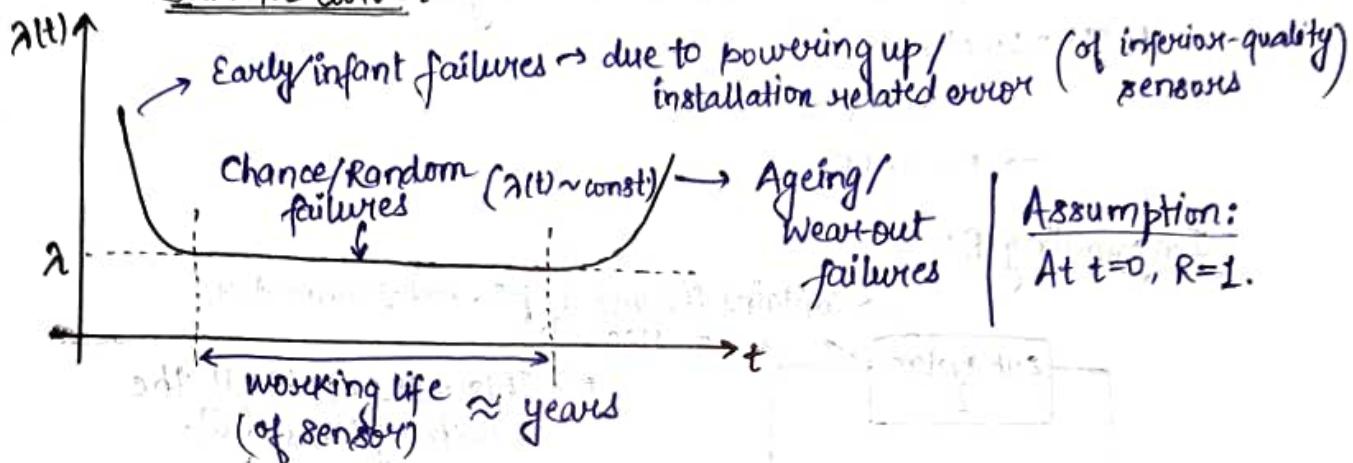

↳ Longer for good sensors

$$\rightarrow \lambda(t) = \lambda : \text{Working life regime}$$

$$R = e^{-\lambda t}$$


Thermistor: $\lambda = 1 \text{ yr}^{-1}$ (say)

$$R(t=0.5 \text{ yr}) = e^{-0.5}$$


$$= 0.61$$

Reliability of Instrumentation System

Instrumentation System:

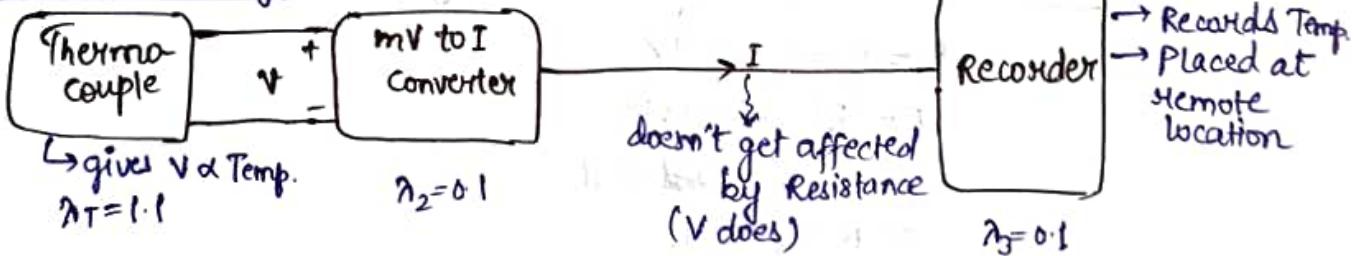

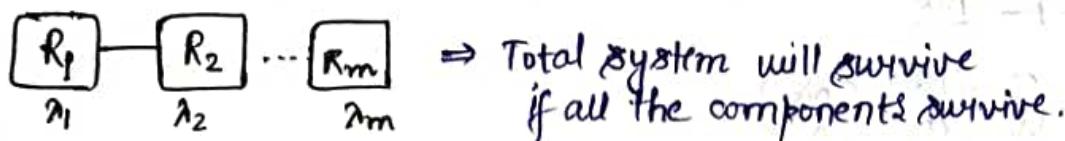Electronics are generally more reliable than sensor components.



$$R = R_1 R_2 R_3 \dots R_m$$

$$\Rightarrow e^{-\lambda t} = e^{-\lambda_1 t} e^{-\lambda_2 t} \dots e^{-\lambda_m t}$$

$$\Rightarrow \lambda = \lambda_1 + \lambda_2 + \lambda_3 + \dots + \lambda_m$$

$\lambda = 1.3$ for the instrumentation system.

$$R(t=0.5 \text{ yrs}) = e^{-0.65}$$


$$= 0.52$$

$$\Rightarrow F = 0.48$$

Improving R:

→ Contains thermo-couple, mv-I converter, & recorder.

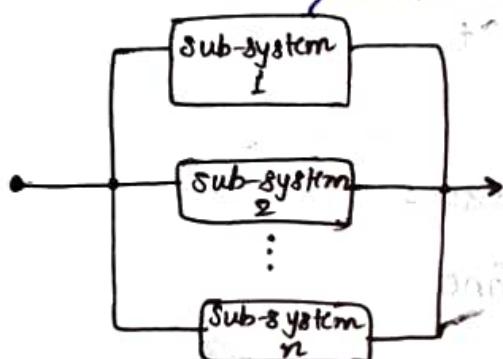⇒ This will fail if all the sub-systems fail.



↓
All are exposed to
same physical
quantity (e.g., T)

$$F = F_1 F_2 \dots F_n$$

For $n=3$: 3 levels of redundancy

$$F_1 = F_2 = F_3 = 0.48$$

$$F = (F_1)^3 = (0.48)^3$$

$$= \cancel{0.11}$$

$$\Rightarrow R = 1 - 0.11 \\ = 0.89$$

Disadvantages:

- Size ↑
- Mass ↑
- Power ↑
- Cost ↑


Improvement:

↳ Bring redundancy to the most critical element.

Here, it is thermo-couple which consumes negligible power.

↳ mV to I converter and Recorder are more reliable.

3 levels of redundancy

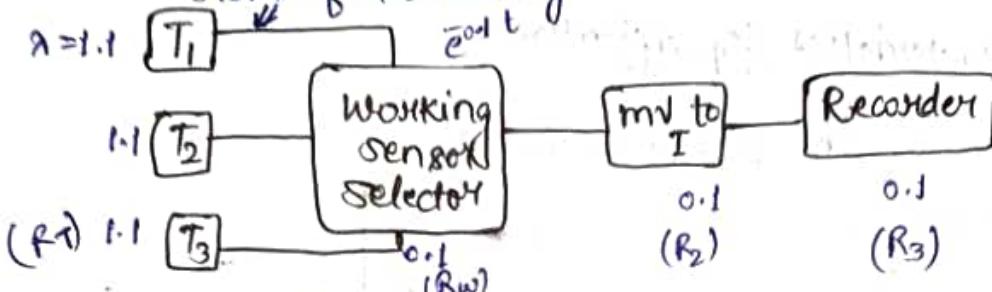

$$R_T = e^{-0.1t}$$

$$F_T = 1 - e^{-0.1t}$$

$$= 1 - e^{-0.55} \quad (t = 0.5 \text{ yrs.})$$

$$= 0.423$$

\nwarrow F_T of individual T \nearrow Thermocouple

$$F_T \text{ of } 3 \text{ } T_s = (0.423)^3 = 0.0757$$

$$R_T \text{ of } 3 \text{ } T_s = 1 - (0.423)^3 \\ = 0.9243$$

05-02-2024

Reliability of complete system,

$$R_w = R_2 = R_3 = e^{-0.05}$$

$$R = R_T R_w R_2 R_3$$

$$= 0.9243 \times (e^{-0.05})^3$$

$$= 0.795$$

52% initially

↓
89% with high cost, high power, high mass

↓ compromise

79% with low cost


Specification

- static characteristics \rightarrow input: constant or slowly changing
- long-term characteristics \rightarrow R , F , α
- dynamic characteristics

Dynamic characteristics / Specification

↪ Performance of the sensor when input is changing.


Potentiometric displacement sensor:

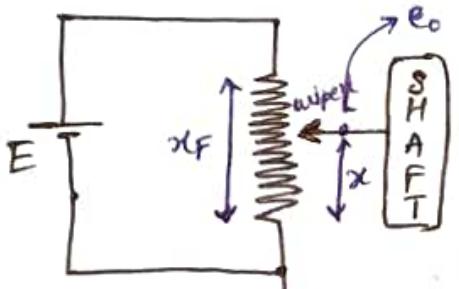

⇒ we measure the displacement of the shaft with ref. windings



$$e_o = \left(\frac{E}{x_F} \right) x = Kx,$$

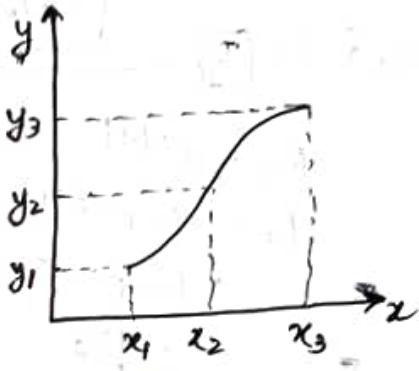where sensitivity $K = \left(\frac{E}{x_F} \right)$.



constant inputs

(if i/p changes suddenly)

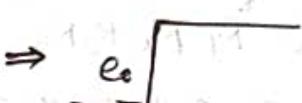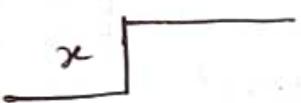

(if i/p changes continuously)



(output faithfully follows the i/p)

↪ Output is same as the input except for the sensitivity, K .


Ideal instrument:

$$y(t) = Kx(t) \rightarrow \text{Zero-order instrument}$$


Practicality: Inertial loading
Frictional loading

} at the wiper.

Eg. Measuring temperature of a liquid

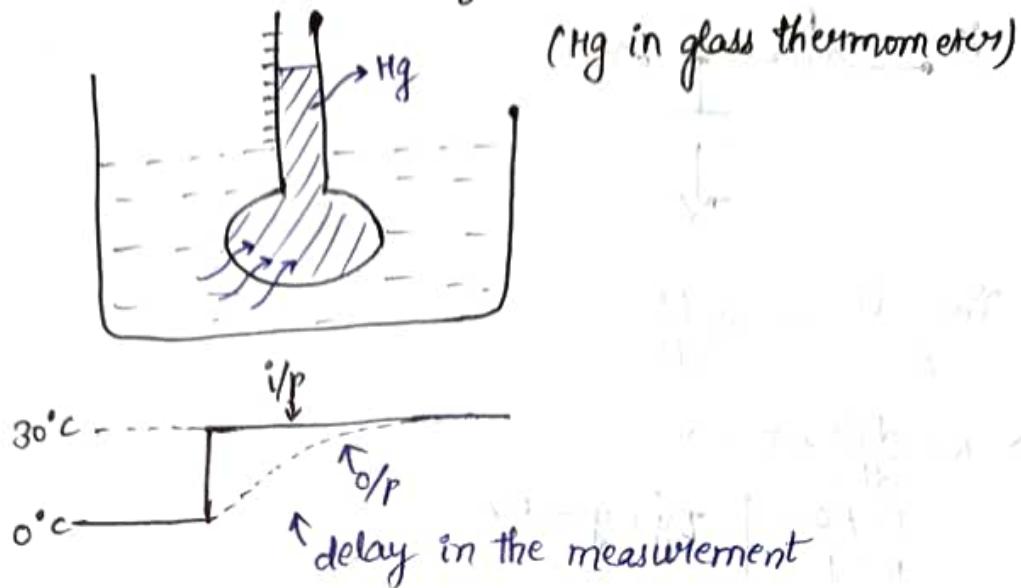

- Transient error
- Steady-state error

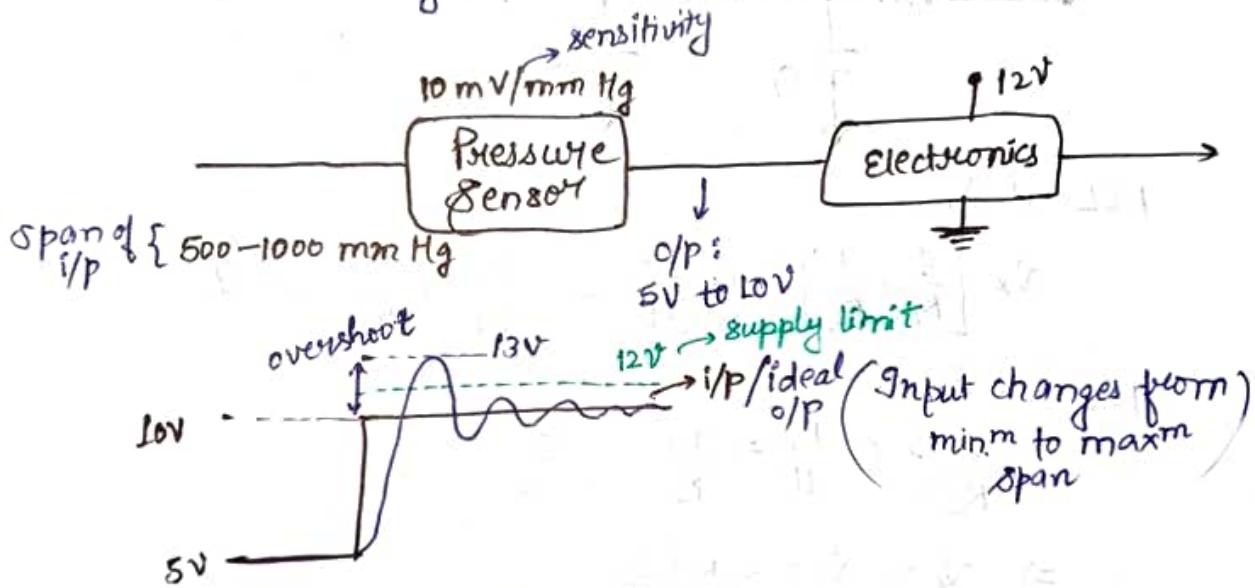

Due to overshoot: • Electronics may get damaged
• Actuator overload.

Solution: Redesign the electronics.


choose the sensor with less overshoot.

$$\rightarrow T \frac{dy}{dt} + y(t) = Kx(t) \rightarrow 1^{\text{st}} \text{ order instrument}$$

T : time-constant

eg Hg in glass thermometer.

Eg: 1st order circuit: Low pass filter

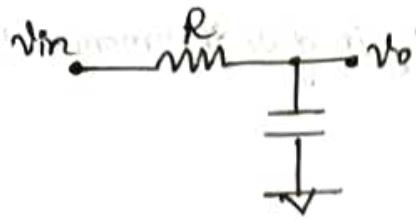


$$\frac{V_{in} - V_0}{R} = C \frac{dV_0}{dt}$$

$$\Rightarrow RC \frac{dV_0}{dt} + V_0 = V_{in}$$

$$\begin{array}{l|l} I = RC & Iy + y = Kx \\ K = 1 & \end{array}$$

Eg: 2nd order circuit

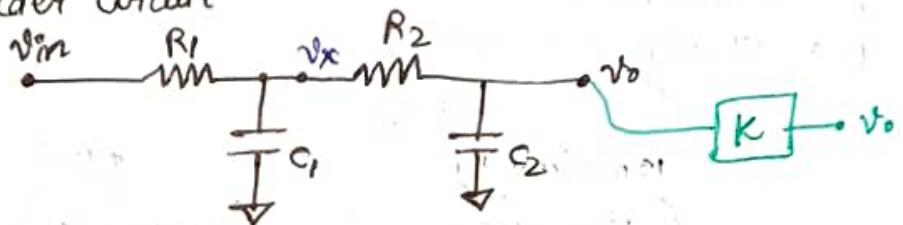

KCL at V_x ,

$$V_x \left[\frac{1}{R_1} + \frac{1}{R_2} \right] + C_1 \frac{dV_x}{dt} = \frac{V_{in}}{R_1} + \frac{V_0}{R_2} \dots \textcircled{1}$$

KCL at V_0 ,

$$\frac{V_0}{R_2} + C_2 \frac{dV_0}{dt} = \frac{V_x}{R_2} \dots \textcircled{2}$$

$$\Rightarrow V_x = V_0 + C_2 R_2 \frac{dV_0}{dt}$$


$$\textcircled{1} \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(V_0 + C_2 R_2 \frac{dV_0}{dt} \right) + C_1 \left(\frac{dV_0}{dt} + C_2 R_2 \frac{d^2 V_0}{dt^2} \right) = \frac{V_{in}}{R_1} + \frac{V_0}{R_2}$$

$$\Rightarrow C_1 C_2 R_2 \frac{d^2 V_0}{dt^2} + \left(C_2 \frac{R_2}{R_1} \frac{dV_0}{dt} + \frac{C_2 dV_0}{dt} + C_1 \frac{dV_0}{dt} \right) + \frac{V_0}{R_1} = \frac{V_{in}}{R_1}$$

$$\Rightarrow \frac{d^2 V_0}{dt^2} + \frac{dV_0}{dt} \left(\frac{C_1 R_1 + R_1 C_2 + C_2 R_2}{R_1 R_2 C_1 C_2} \right) + \frac{V_0}{R_1 R_2 C_1 C_2} = \frac{V_{in}}{R_1 R_2 C_1 C_2}$$

$$\Rightarrow \frac{d^2 V_0}{dt^2} + \left(\frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{R_1 R_2 C_1 C_2} \right) \frac{dV_0}{dt} + \frac{V_0}{R_1 R_2 C_1 C_2} = \frac{V_{in}}{R_1 R_2 C_1 C_2}$$

Second-Order Instrument

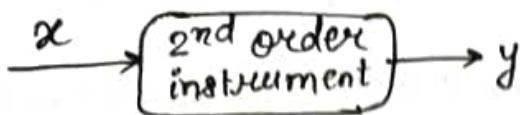

$$\frac{d^2y}{dt^2} + (2\xi\omega_n) \frac{dy}{dt} + \omega_n^2 y = K\omega_n^2 x,$$

where ω_n : natural frequency

ξ : damping ratio


K : sensitivity
unitless quantity

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\xi = \frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{2\sqrt{R_1 R_2 C_1 C_2}}$$

2nd Order sensor

Inertial sensor

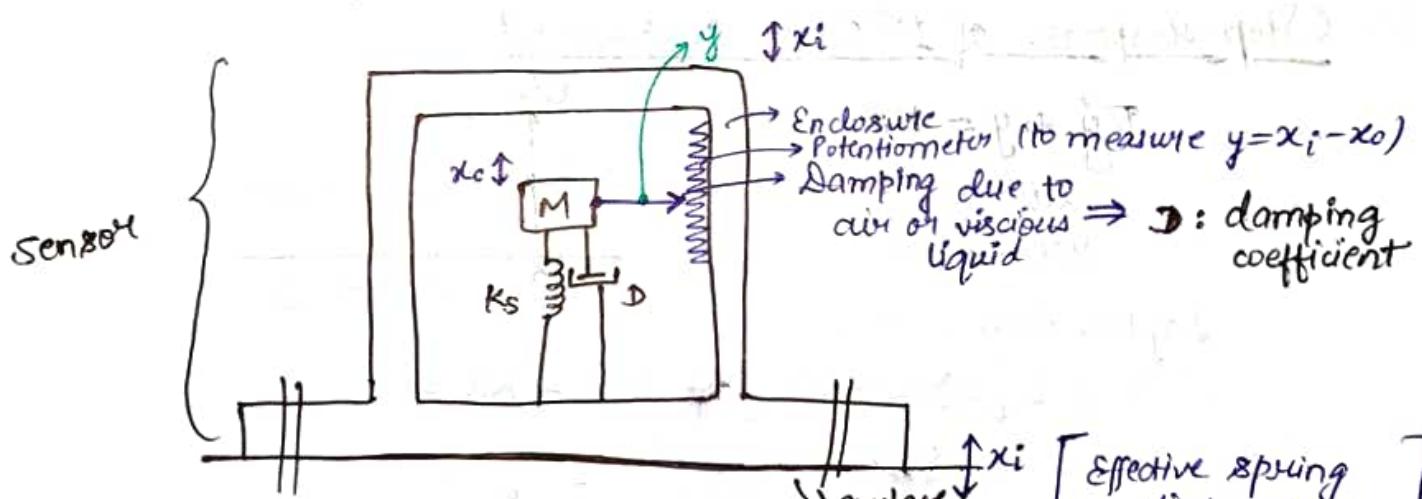

- $a = \ddot{x}_i$ (for some spacecraft)

- $K_s(x_i - x_0) + D \frac{d}{dt}(x_i - x_0) = M \frac{d^2 x_0}{dt^2}$

Take $y = x_i - x_0 \Rightarrow x_0 = x_i - y \Rightarrow$ | Extra variable: x_0


$$\therefore K_s y + D \frac{dy}{dt} = M \frac{d^2}{dt^2} (x_i - y)$$

$$\Rightarrow \boxed{\frac{d^2 y}{dt^2} + \left(\frac{D}{M}\right) \frac{dy}{dt} + \frac{K_s}{M} y = a}$$

- $\omega_n = \sqrt{\frac{K_s}{M}} ; 2\xi\omega_n = \frac{D}{M} \Rightarrow \xi = \frac{D}{2\sqrt{K_s M}} \Rightarrow \xi \propto D$


damping ratio

→

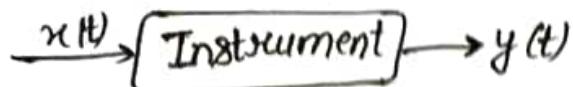

↳ Find the instrument characteristics by observing the output, $y(t)$.


Test Inputs:

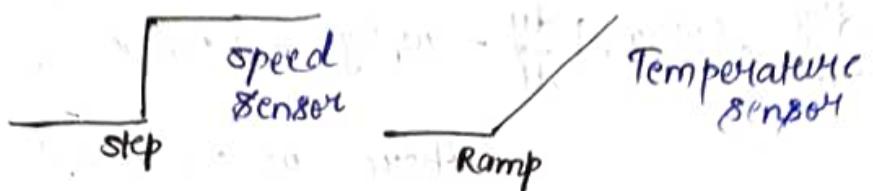

Vibration sensor
Body temperature sensor
(changes sinusoidally)

Impulse

Temp. sensor:

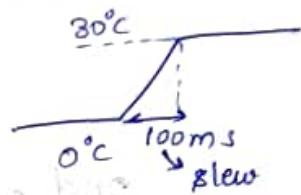

↳ choice of test inputs depend on the instrument types.

Step-response of 1st Order Instrument

$$\tau \dot{y} + y = kx$$

$$x(t) \rightarrow X(s)$$

$$y(t) \rightarrow Y(s)$$

Laplace transform:

$$\mathcal{L}[sY(s) - y(0)] + Y(s) = kX(s)$$

$$\Rightarrow Y(s) = \frac{kX(s)}{\tau s + 1} + \frac{y(0)}{\tau s + 1}$$

$$\text{Take } y(0) = 0.$$


$$\Rightarrow Y(s) = \frac{kX(s)}{\tau s + 1} = \frac{kA}{s(\tau s + 1)} \quad [\because X(s) = A/s]$$

$$= \frac{kA/\tau}{s(s + 1/\tau)}$$

$$\Rightarrow Y(s) = KA \left[\frac{1}{s} - \frac{1}{s + 1/\tau} \right]$$

$$\text{Inverse LT} \Rightarrow y(t) = KA u(t) - KA e^{-t/\tau} u(t)$$
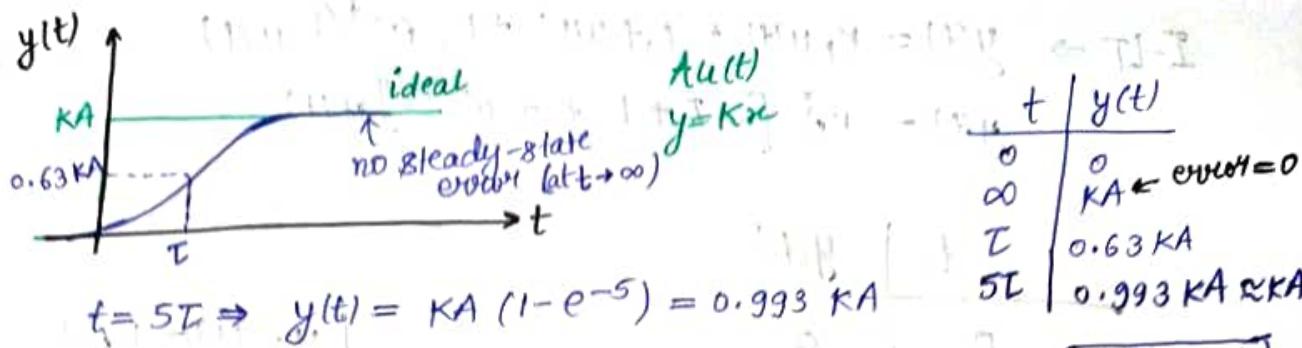
$$\Rightarrow y(t) = KA [1 - e^{-t/\tau}] u(t)$$



07-02-2024


Transient error: ideal o/p (given by zero) error free

$$e(t) = y(t) - y_I(t)$$

$$= -KA e^{-t/T} u(t)$$

$$y_I(t) = KA u(t)$$

$T \downarrow \Rightarrow \frac{t}{T} \uparrow \Rightarrow |e(t)| \downarrow$: T affects the transient error

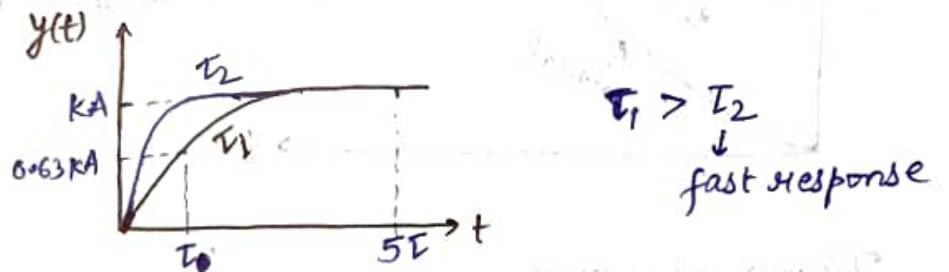


• T helps us to find speed of response (or delay) of the system.

$T \uparrow \Rightarrow \text{Response Speed} \downarrow$

Ramp Response of 1st Order Instrument

$$x(t) = \dot{A}t u(t)$$

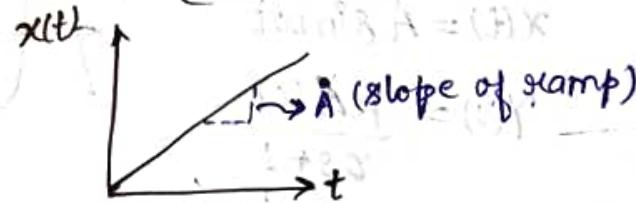

$$Y(s) = \frac{K X(s)}{Ts + 1}$$

$$X(s) = \frac{\dot{A}}{s^2}$$

$$Y(s) = \frac{\dot{A} K / T}{s^2 (s + 1/T)} = \frac{K_1}{s} + \frac{K_2}{s^2} + \frac{K_3}{s + 1/T}$$



$$\Rightarrow K_1 = -KA$$

$$K_2 = KA$$

$$K_3 = KA T$$

$$I-LT \Rightarrow y(t) = K_1 u(t) + K_2 t u(t) + K_3 e^{-t/\tau} u(t)$$
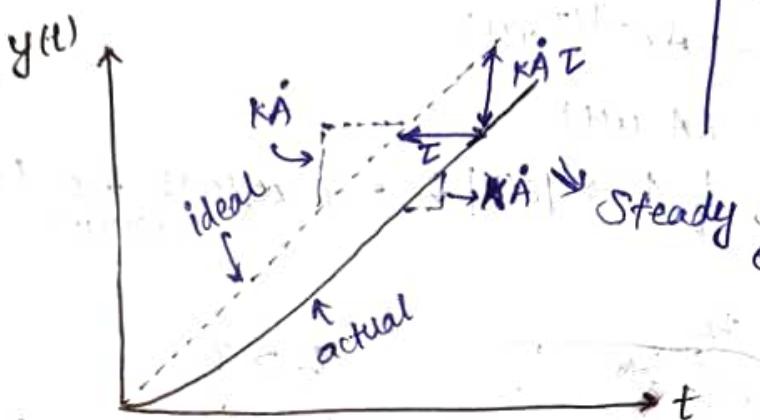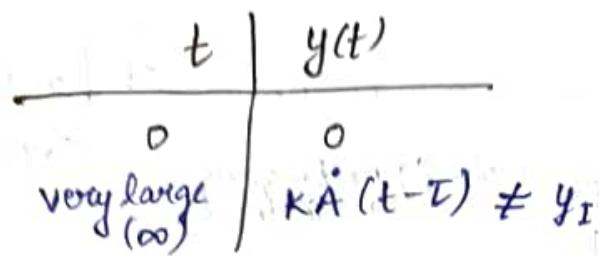
$$y(t) = K \dot{A} [-\tau + t + \tau e^{-t/\tau}] u(t)$$



$$y_I(t) = K \dot{A} t$$

After a long time,
the error has not
died out.

↳ There's steady
state error.

Transient error,

$$e(t) = y(t) - y_I(t)$$

$$= K \dot{A} t - K \dot{A} t e^{-t/\tau}$$

Sine Response of 1st Order Instruments

$$x(t) = A \sin \omega t$$

$$Y(s) = \frac{K X(s)}{\tau s + 1}$$

$$y(t) = \underset{\text{Transient term}}{\cancel{\text{Transient}}} + \underset{\text{Steady-state term}}{\cancel{\text{existing term}}}$$

(as sine is always existing term)

$s = \cancel{\sigma} + j\omega$ determines

$$s = j\omega$$

$$\Rightarrow Y(j\omega) = \frac{K X(j\omega)}{j\omega \tau + 1}$$

freq. response
of sensor

$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)} = \boxed{\frac{K}{j\omega \tau + 1}}$$

$$x(t) = A \sin(\omega t) \rightarrow \boxed{\frac{K}{j\omega T + 1}} \rightarrow y(t)$$

$$y(t) = A |H(j\omega)| \sin(\omega t + \angle H(j\omega))$$


$$\text{error in amplitude} = AK - \frac{AK}{\sqrt{T^2\omega^2+1}}$$

$$\begin{aligned}\text{phase error} &= \angle y(t) - \angle H(j\omega) \\ &= 0 - \angle H(j\omega) \\ &= \tan^{-1}(T\omega)\end{aligned}$$

To reduce the error:

$$wT \ll 1 \Rightarrow \text{accurate measurements}$$

or $T \ll \frac{1}{\omega}$

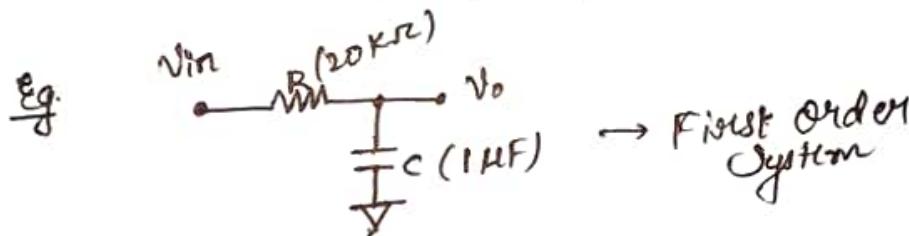

Determine max. frequency that will keep the amplitude error $< 5\%$.

Soln: $\% \text{ error in amplitude} = \frac{AK - \frac{AK}{\sqrt{T^2\omega^2+1}}}{AK} \times 100\% < 5\%$

$$\begin{aligned}\Rightarrow 1 - \frac{1}{\sqrt{T^2\omega^2+1}} &< \frac{5}{100} \\ \Rightarrow \frac{1}{\sqrt{T^2\omega^2+1}} &> \frac{95}{100}\end{aligned}$$

$$\left. \begin{aligned}T &= RC \\ &= (20 \text{ k}\Omega)(1 \mu\text{F}) \\ &= 20 \text{ ms}\end{aligned} \right\}$$

$$\Rightarrow T^2\omega^2 + 1 < \left(\frac{100}{95}\right)^2$$

$$\Rightarrow \omega^2 < \frac{\left(\frac{100}{95}\right)^2 - 1}{(20 \text{ ms})^2}$$

First-Order Instruments


$T, K \rightarrow$ Parameters

Step

Ramp

Sine wave


Pulse:

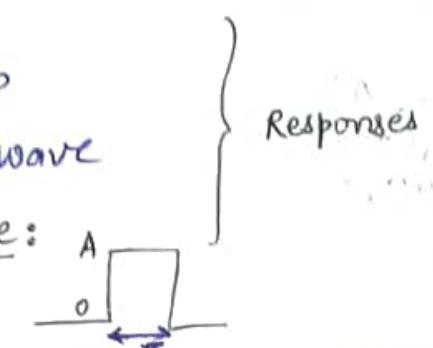

$$y(t) = A u(t) - A u(t-T)$$

Second-Order Instruments

Parameters: ξ, ω_n, K

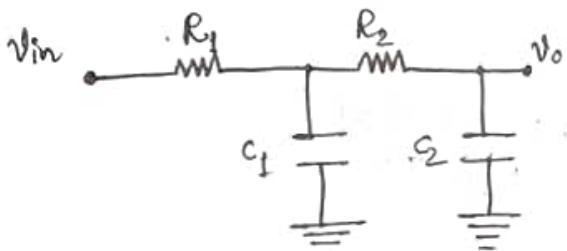

Inertial accelerometer

Step Response:

$$x(t) = A u(t) \Rightarrow X(s) = \frac{A}{s}$$

$$\frac{d^2y}{dt^2} + 2\xi\omega_n \frac{dy}{dt} + \omega_n^2 y = K \omega_n^2 x$$

$$LT \Rightarrow s^2 Y(s) + 2\xi\omega_n s Y(s) + \omega_n^2 Y(s) = K \omega_n^2 X(s)$$

$$\Rightarrow \frac{Y(s)}{X(s)} = \frac{K \omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\Rightarrow Y(s) = \frac{A K \omega_n^2}{s(s^2 + 2\xi\omega_n s + \omega_n^2)} \dots \textcircled{1}$$

Response $y(t)$ depends on the roots of the quadratic $(s^2 + 2\xi\omega_n s + \omega_n^2)$ in the denominator.

$$s^2 + 2\xi\omega_n s + \omega_n^2$$

Case-1: Real, Unequal roots $\Rightarrow \xi > 1$

$$s_1 = [-\xi + \sqrt{\xi^2 - 1}] \omega_n$$

$$s_2 = [-\xi - \sqrt{\xi^2 - 1}] \omega_n$$

Case-2: Real, equal roots $\Rightarrow \xi = 1$

$$s_1 = s_2 = -\omega_n$$

Case-3: Complex roots $\Rightarrow \xi < 1$

$$s_1 = [-\xi + j\sqrt{1-\xi^2}] \omega_n$$

$$s_2 = [-\xi - j\sqrt{1-\xi^2}] \omega_n$$

$$\xi > 1$$

$$Y(s) = \frac{AK\omega_n^2}{s(s-s_1)(s-s_2)} = \frac{K_0}{s} + \frac{K_1}{s-s_1} + \frac{K_2}{s-s_2}$$

$$\Rightarrow K_0 = \frac{AK\omega_n^2}{s_1 s_2} = AK$$


$$K_1 = \frac{AK\omega_n^2}{s_1(s_1-s_2)} = \frac{AK}{[-\xi + j\sqrt{\xi^2-1}] 2\sqrt{\xi^2-1}} = \frac{-AK [\xi + j\sqrt{\xi^2-1}]}{2\sqrt{\xi^2-1}}$$

$$K_2 = \frac{AK\omega_n^2}{s_2(s_2-s_1)} = \frac{+AK}{2\sqrt{\xi^2-1}} [\xi - j\sqrt{\xi^2-1}] \xrightarrow{\text{independent of } \omega_n}$$

$$\therefore y(t) = [K_0 + K_1 e^{s_1 t} + K_2 e^{s_2 t}] u(t)$$

$s_1 < 0, s_2 < 0$ decaying exponential

$$y(t) \Big|_{t \rightarrow \infty} = K_0 = AK \quad (\text{no steady-state error})$$

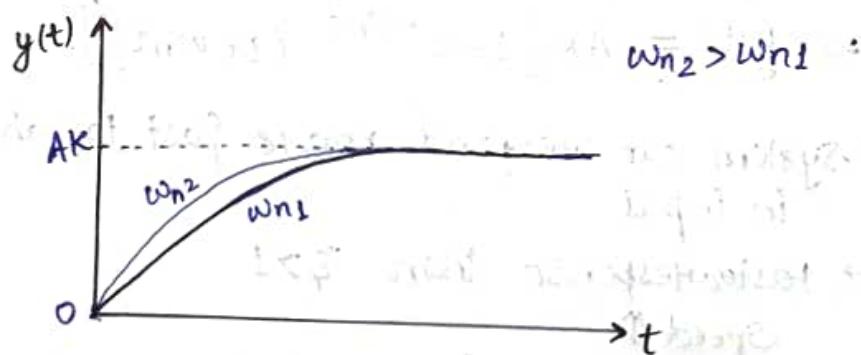

- $\xi = \text{constant}$, ω_n vary

$\omega_n \uparrow \Rightarrow$ Exponential decays faster \Rightarrow Speed \uparrow


ω_n : determines the speed of response or transient error

$\therefore s_1, s_2 \propto \omega_n$

- $\xi \uparrow, \omega_n = \text{constant}$

$\xi \propto \text{damping}$ $\xi \uparrow \Rightarrow \text{speed} \downarrow$

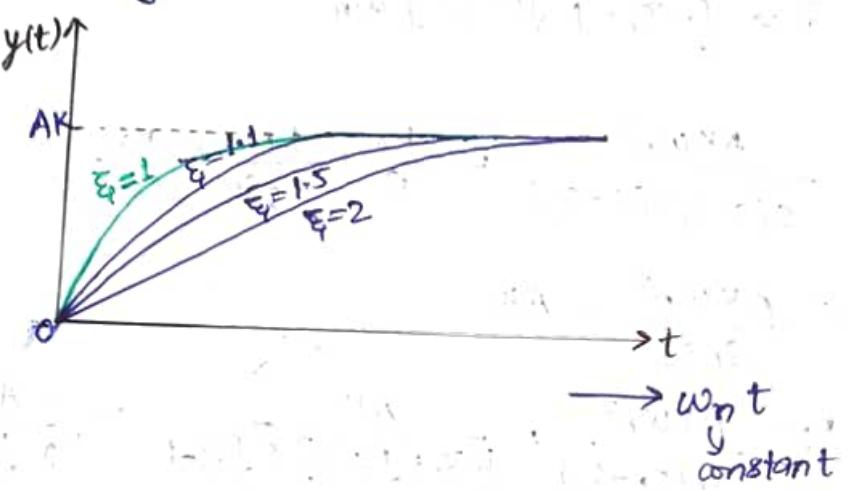- ↳ System does not respond to sharp changes.
- ↳ system becomes slower.



Assignment:

PDF

- Aim
- Code
- Results
- Inferences

Plot $y(t)$ vs. $t/w_n t$ for different ξ

$A=1$
 $K=1$
 w_n

$\xi=1$

$$Y(s) = \frac{AK w_n^2}{s(s+w_n)^2}$$

$$= \frac{K_0}{s} + \frac{K_1}{s+w_n} + \frac{K_2}{(s+w_n)^2}$$

$$\Rightarrow K_0 = AK, K_1 = -AK, K_2 = -AKw_n$$

$$\text{ILT} \Rightarrow y(t) = [K_0 + K_1 e^{-w_n t} + K_2 t e^{-w_n t}] u(t)$$

$$\Rightarrow y(t) = AK [1 - e^{-w_n t} (1 + w_n t)]$$

$\xi=1$: System can respond more fast to abrupt change in input.

↳ Faster response than $\xi > 1$
Speed \uparrow

$\xi < 1$

$$s_1 = [-\xi + j\sqrt{1-\xi^2}] w_n$$

$$s_2 = [-\xi - j\sqrt{1-\xi^2}] w_n$$

$$Y(s) = \frac{AK w_n^2}{s(s-s_1)(s-s_2)} = \frac{K_0}{s} + \frac{K_1}{s-s_1} + \frac{K_2}{s-s_2}$$

$$\Rightarrow K_0 = AK$$

$$K_1 = -\frac{AK [\xi_1 + j\sqrt{1-\xi^2}]}{2j\sqrt{1-\xi^2}}$$

$$K_2 = \frac{AK [\xi_1 - j\sqrt{1-\xi^2}]}{2j\sqrt{1-\xi^2}}$$

$$\therefore y(t) = [K_0 + K_1 e^{s_1 t} + K_2 e^{s_2 t}] u(t)$$

$$\text{let } \xi_1 = \cos \theta.$$

$$K_1 = \frac{-AK e^{j\theta}}{2j \sin \theta}$$

$$K_2 = \frac{AK e^{-j\theta}}{2j \sin \theta}$$

$$\therefore y(t) = AK \left[1 - \frac{1}{2j \sin \theta} [e^{(s_1 t + j\theta)} - e^{(s_2 t - j\theta)}] \right]$$

$$= AK \left[1 - \frac{1}{2j \sin \theta} e^{-\xi w_n t} (e^{j(\underbrace{w_n \sqrt{1-\xi^2} t}_{y}) + \theta} - e^{-j(\underbrace{w_n \sqrt{1-\xi^2} t}_{y} + \theta)}) \right]$$

$$\text{let } \frac{e^{jy} - e^{-jy}}{2j} = \sin y$$


$$\therefore y(t) = AK \left[1 - \frac{e^{-\xi w_n t}}{\sin \theta} \sin(w_n \sqrt{1-\xi^2} t + \theta) \right]$$

$$y(t) = AK \left[1 - \frac{e^{-\xi w_n t}}{\sqrt{1-\xi^2}} \sin(w_n \sqrt{1-\xi^2} t + \cos^{-1}(\xi)) \right]$$


decaying signal
sine wave
decaying sine wave

(for $\xi < 1$)

t	y(t)
0	0
∞	AK

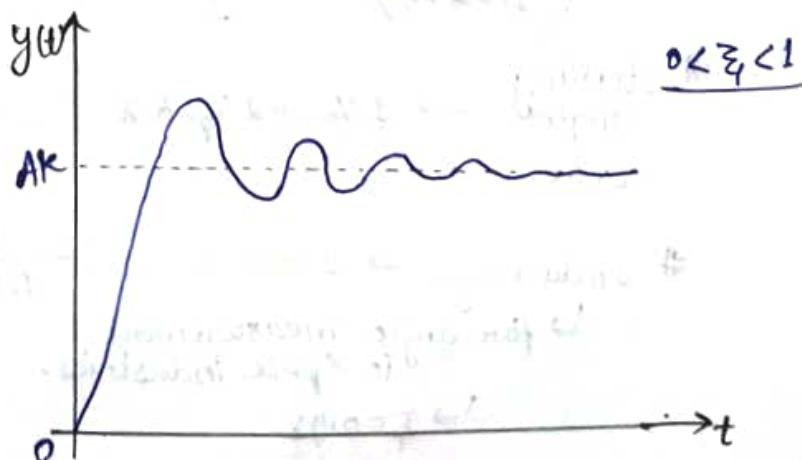

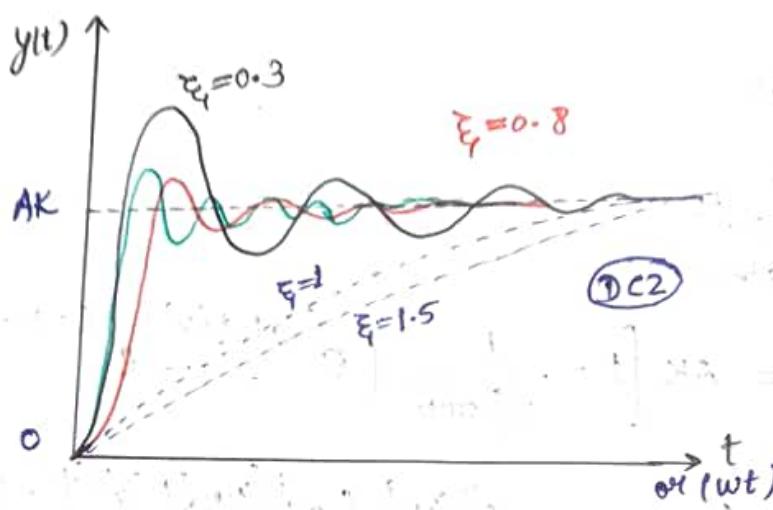- $\xi = \text{constant}$; $\omega_n \uparrow$: Decays faster
Frequency \uparrow
 \Rightarrow Speed \uparrow
- $\omega_n = \text{constant}$, ξ varies \rightarrow Less overshoot



$\xi > 1$: No overshoots, sluggish (Overdamped)

$\xi = 1$: No overshoots, faster than $\xi > 1$ (critically damped)

$\xi < 1$: overshoots, faster (Underdamped)

we would want our system to be slightly underdamped,
i.e., little overshoots.

$$\xi = 0.3 \times \quad \xi = 0.8 \checkmark$$

\rightarrow Ideal value \rightarrow AK

Instrument error $\rightarrow 2\%$ (static error) w.r.t (for all ξ)

$\left(\begin{array}{c} 0.98 \text{ AK} \\ \text{to} \\ 1.02 \text{ AK} \end{array} \right)$ } we want slightly underdamped system.


steering angle $\rightarrow 1\%$ $\Rightarrow \xi = 0.8$
overshoot

Inductosyn $\rightarrow 1 \text{ arc seconds} = \left(\frac{1}{1600}\right)^\circ$

\hookrightarrow for angle measurement
in space industries.

$$\hookrightarrow \xi = 0.98$$

$y(t_p)$ calculation:

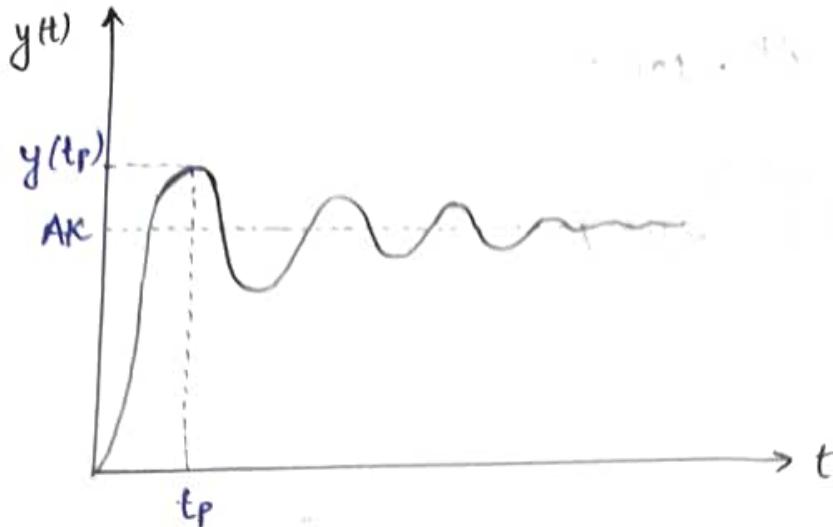

$$\frac{dy}{dt} = 0$$

$$\Rightarrow \frac{d}{dt} \left[e^{-\xi \omega_n t} \sin(\omega_n \sqrt{1-\xi^2} t + \theta) \right] = 0$$

$$\Rightarrow \sin(\omega_n \sqrt{1-\xi^2} t + \theta) e^{-\xi \omega_n t} \times (+\xi \omega_n) \\ + \cos(\omega_n \sqrt{1-\xi^2} t + \theta) \times \underbrace{\omega_n \sqrt{1-\xi^2}}_{\text{constant}} \cdot e^{-\xi \omega_n t} = 0$$

$$\Rightarrow \sin(\omega_n \sqrt{1-\xi^2} t + \beta - \theta) = 0$$

$$\Rightarrow t = \frac{n\pi}{\omega_n \sqrt{1-\xi^2}}$$

$$n=1 \Rightarrow \boxed{t_p = \frac{\pi}{\omega_n \sqrt{1-\xi^2}}}$$

$$y(t_p) = AK \left[1 + \underbrace{\frac{e^{-\xi \omega_n t_p}}{\sqrt{1-\xi^2}} \sin(\underbrace{\omega_n \sqrt{1-\xi^2} t_p + \theta}_{\pi})}_{-8 \sin \theta} \right]$$

$$= AK \left[1 - \frac{e^{-\xi \omega_n t_p}}{\sqrt{1-\xi^2}} \sin \theta \right]$$


$$= AK \left[1 + e^{-\xi \omega_n t_p} \right]$$

$$\therefore \boxed{y(t_p) = AK \left[1 + e^{-\frac{\xi \pi}{\sqrt{1-\xi^2}}} \right]}$$


% overshoot (peak)

$$= \frac{y(t_p) - AK}{AK} \times 100\%$$
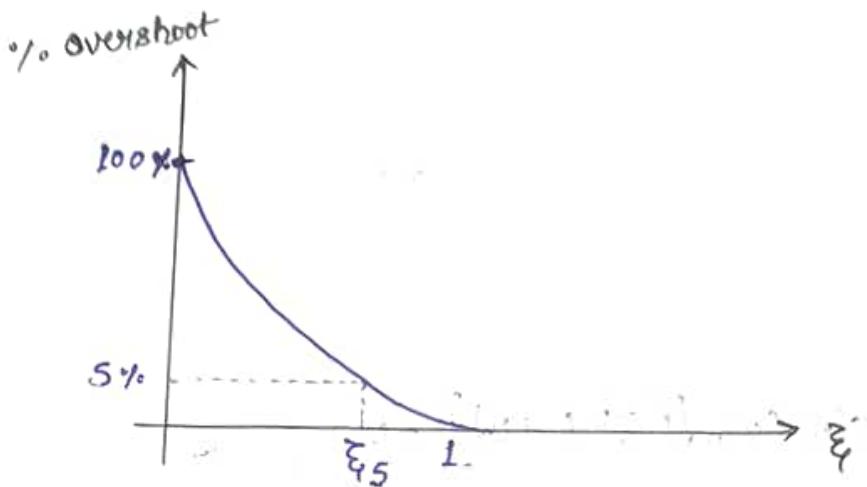
$$= e^{\left(\frac{-\xi\pi}{\sqrt{1-\xi^2}}\right)} \times 100\%$$



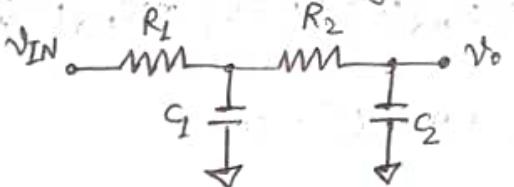Eg: Underdamped 2nd order low pass filter:



$$\xi_p = \frac{R_1 C_1 + R_2 C_2 + \cancel{R_1 C_2}}{2 \sqrt{R_1 R_2 C_1 C_2}} > 1$$

$$AM \geq GM$$

$$\Rightarrow \frac{R_1 C_1 + R_2 C_2}{2} \geq \sqrt{R_1 R_2 C_1 C_2}$$


$$\Rightarrow \frac{R_1 C_1 + R_2 C_2}{2 \sqrt{R_1 R_2 C_1 C_2}} \geq 1$$

$$\Rightarrow \frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{2 \sqrt{R_1 R_2 C_1 C_2}} \geq 1$$

$$\Rightarrow \xi_p > 1$$

$\therefore \xi < 1$ is not possible.

→ Passive RC low pass filter:

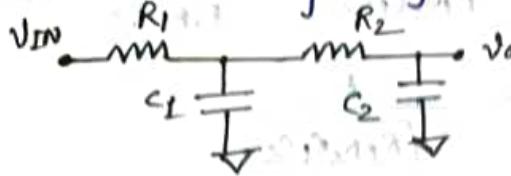


$$\xi = \frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{2\sqrt{R_1 R_2 C_1 C_2}}$$

$$R_1 = R_2 = R \quad \xi = \frac{1}{2}$$

$$C_1 = C_2 = C$$

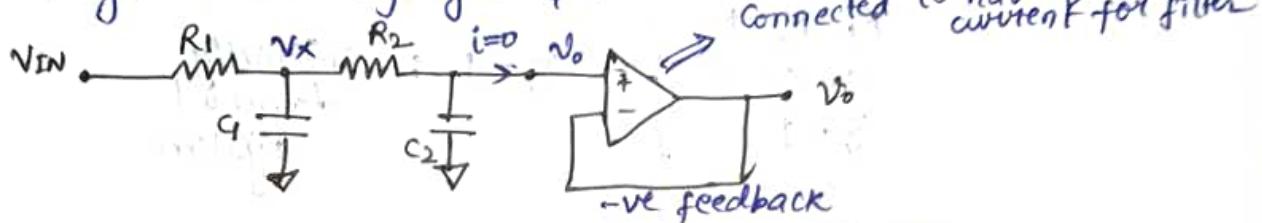
For slight underdamping, $\xi \downarrow$.



→ Slight underdamping are associated with positive feedback.



"Sallen-Key"
Active
LPF

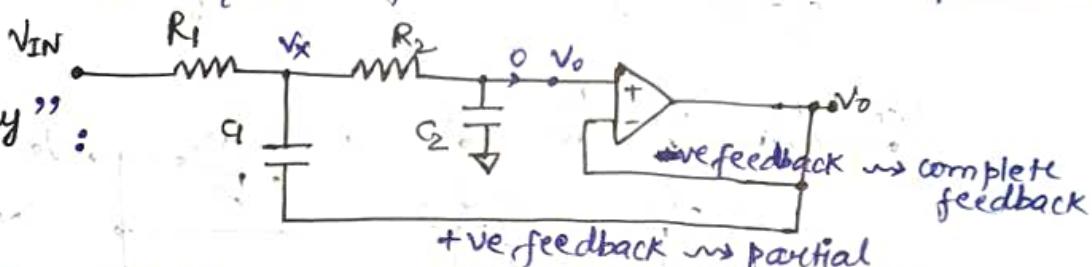

KCL @ V_X:

$$V_X \left[\frac{1}{R_1} + \frac{1}{R_2} \right] + C_1 \frac{dV_X}{dt} = \frac{V_{IN}}{R_1} + \frac{V_O}{R_2} + C_1 \frac{dV_O}{dt} \quad \dots \textcircled{1}$$

KCL @ V_O:

$$\frac{V_O}{R_2} + C_2 \frac{dV_O}{dt} = \frac{V_X}{R_2} \quad \dots \textcircled{2}$$

$$\textcircled{1} \text{ and } \textcircled{2} \Rightarrow \left(V_O + C_2 R_2 \frac{dV_O}{dt} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + C_1 \left[\frac{dV_O}{dt} + C_2 R_2 \frac{d^2 V_O}{dt^2} \right] = \frac{V_{IN}}{R_1} + \frac{V_O}{R_2} + C_1 \frac{dV_O}{dt}$$

$$\Rightarrow \frac{d^2 V_O}{dt^2} + \frac{dV_O}{dt} \left[\frac{1}{R_1 C_1} + \frac{1}{C_2 R_2} \right] + \frac{V_O}{R_1 R_2 C_1 C_2} + \frac{V_O}{C_2 R_2^2} - \frac{V_O}{C_1 C_2 R_2^2} - \frac{V_{IN}}{R_1 R_2 C_1 C_2} = 0$$

$$\Rightarrow \frac{d^2V_o}{dt^2} + \left[\frac{(R_1+R_2)C_2}{R_1 R_2 G_2} \right] \frac{dV_o}{dt} + \frac{V_o}{R_1 R_2 C_1 C_2} = \frac{V_{IN}}{R_1 R_2 G_2} \quad \dots \textcircled{3}$$


$$w_n^2 = \frac{1}{R_1 R_2 G_2 C_2} \Rightarrow w_n = \frac{1}{\sqrt{R_1 R_2 G_2 C_2}}$$

$$2\xi w_n = \frac{(R_1+R_2)G_2}{R_1 R_2 G_2 C_2}$$

$$\Rightarrow \xi = \frac{(R_1+R_2)G_2}{2\sqrt{R_1 R_2 G_2 C_2}}$$

$$\left. \begin{array}{l} R_1 = R_2 = R \\ G = G_2 = C \\ \xi = 1 \end{array} \right\} \Rightarrow \xi = 1 : \text{critically damped system}$$
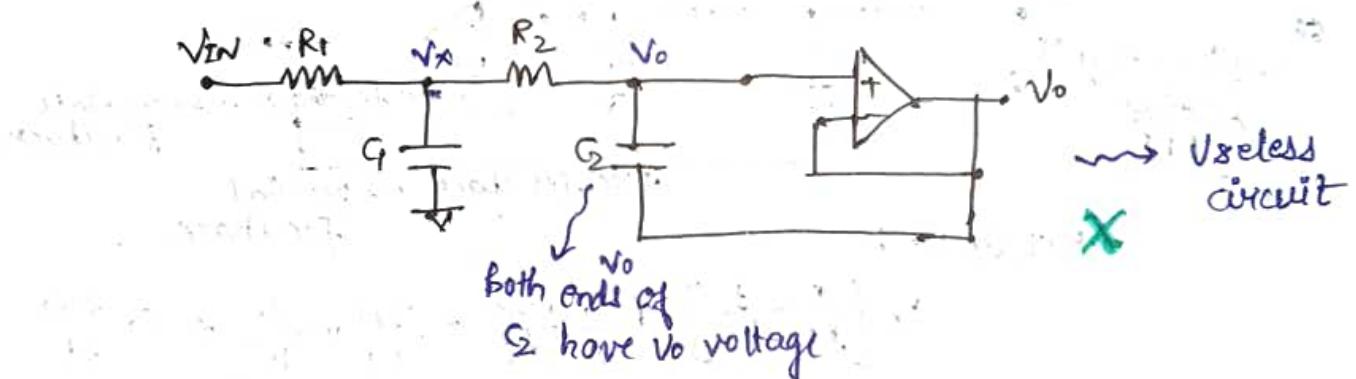
$$\left. \begin{array}{l} R_1 = R_2 = R \\ G = 4C \\ C_2 = C \end{array} \right\} \Rightarrow \xi = 0.5 : \text{underdamped system}$$



Speed of Response of 2nd Order Instruments:

$$\xi < 1 : \quad y(t) = AK \left[1 - \frac{e^{-\xi w_n t}}{\sqrt{1-\xi^2}} \sin(\omega_n \sqrt{1-\xi^2} t + \theta) \right] \quad (\text{slightly underdamped})$$

$$\rightarrow t = \frac{n\pi}{\omega_n \sqrt{1-\xi^2}}$$


$$\rightarrow \% \text{ max overshoot} = e^{\left(\frac{-\xi \pi}{\sqrt{1-\xi^2}} \right)} \times 100\%$$

$$\Rightarrow y(t) = AK \left[1 - \frac{e^{-\xi w_n t}}{\sqrt{1-\xi^2}} (\pm \sin \theta) \right]$$

$$\Rightarrow y(t) = AK \left[1 \pm e^{-\xi \frac{n\pi}{\sqrt{1-\xi^2}}} \right]$$

$$\begin{aligned} \% \text{ overshoot/undershoot} &= \frac{y_{\max} - y(\infty)}{y(\infty)} \times 100\% \\ &= \pm e^{\left(\frac{-\xi w_n t}{\sqrt{1-\xi^2}} \right)} \times 100\% \end{aligned}$$

Setting Time

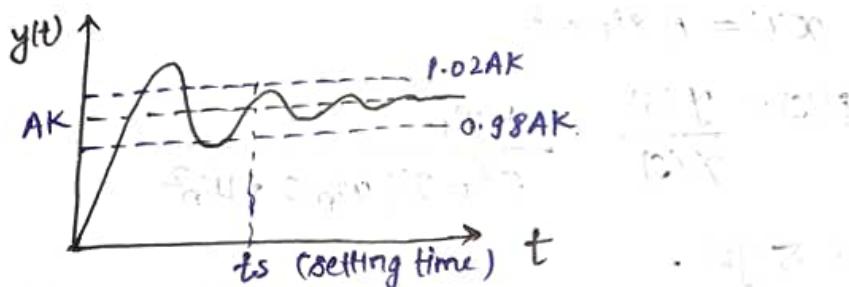

Sensor(s) $\rightarrow 2\%$ error

$$e^{-\frac{\xi n\pi}{\sqrt{1-\xi^2}}} \times 100\% < 2\%.$$


$$-\frac{\xi n\pi}{\sqrt{1-\xi^2}} < -4 \Rightarrow \frac{\xi n\pi}{\sqrt{1-\xi^2}} > 4 \quad \dots ①$$

$$ts > \frac{4}{\xi w_n}$$

General case: $e^{-\frac{\xi n\pi}{\sqrt{1-\xi^2}}} \times 100\% < M\%$

$$\rightarrow ts > \frac{\ln(100/M)}{\xi w_n}$$

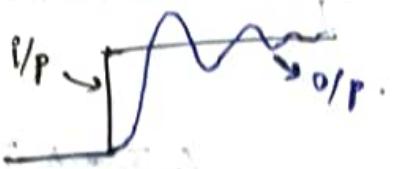DC 4 : Design a sallen-key LPF \rightarrow for typical values of $\xi < 1$.
 Simulate the circuit with step signal.



21-02-2024

Ramp Response of 2nd Order Instruments

$$x(t) = A t$$

Plot $y(t)$, for $\xi > 1, = 1, < 1$.

(DC5)

Derive and obtain the characteristic of $y(t)$ for $\xi > 1, = 1, < 1$ and plot.

Frequency response of 2nd order instruments

$$x(t) = A \sin \omega t$$

$$H(s) = \frac{y(s)}{x(s)} = \frac{k \omega_n^2}{s^2 + 2\xi \omega_n s + \omega_n^2}$$

$$\text{Put } s = j\omega.$$

$$\Rightarrow H(j\omega) = \frac{k \omega_n^2}{\omega_n^2 - \omega^2 + 2\xi \omega_n \omega j}$$

$$y(t) = A |H(j\omega)| \sin(\omega t + \angle H(j\omega))$$

$$\begin{aligned} |H(j\omega)| &= \frac{k \omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + 4\xi^2 \omega^2 \omega_n^2}} \\ &= \frac{k}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_n}\right)^2\right]^2 + 4\xi^2 \left(\frac{\omega}{\omega_n}\right)^2}} \end{aligned}$$


$$|H(j\omega)| \approx k, \text{ for a wide span of } \omega.$$

$$\omega \ll \omega_n \Rightarrow |H(j\omega)| \approx k.$$

- $\omega_n \rightarrow \text{fixed}, \xi \text{ vary.}$


$$|H(j\omega)|_{\omega=\omega_n} = \frac{K}{2\xi}$$

ω	$ H(j\omega) $
0	K
∞	0
ω_n	$K/2\xi$

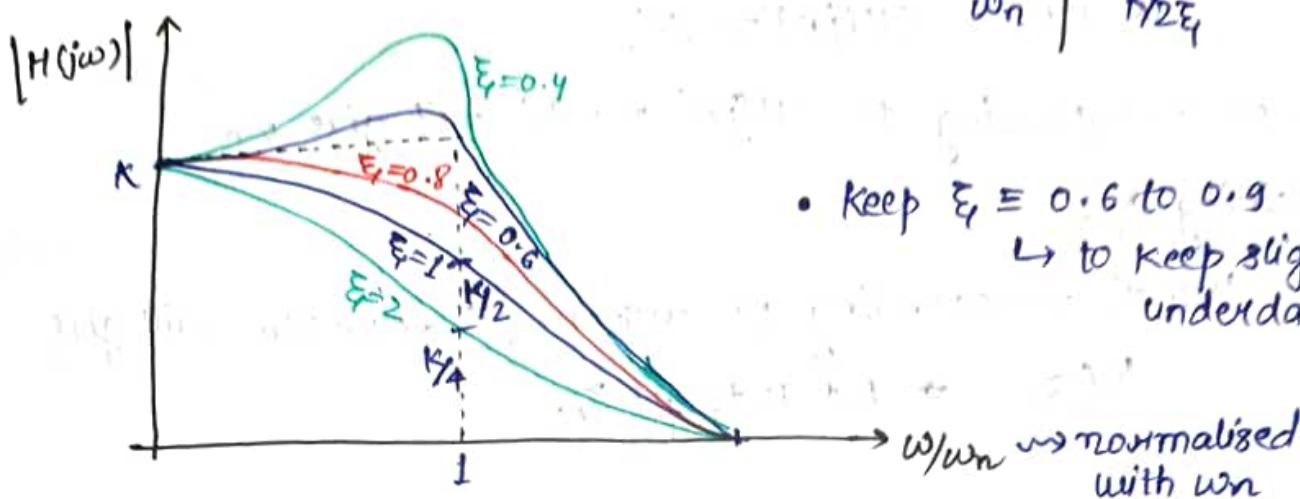


$\xi \downarrow \Rightarrow$ Bandwidth \uparrow

Instrument Identification

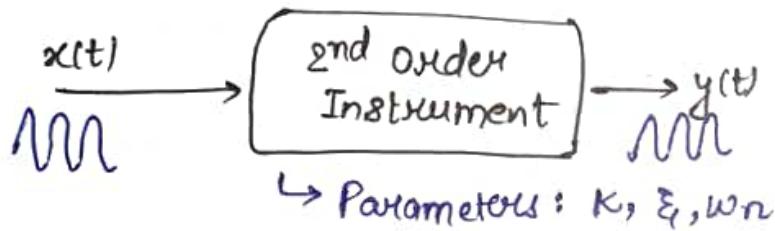

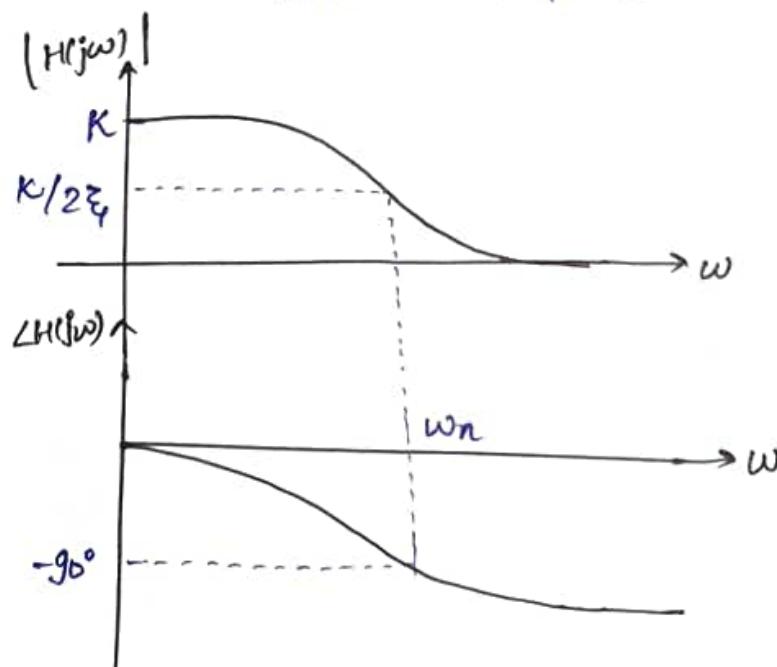→ Obtain the parameters K, ξ, ω_n without looking at the instrument (blackbox) by observing $x(t)$ & $y(t)$.



- Obtaining K:

Output, $y(t)$, corresponding to DC input, $x(t)$, will give K.

Obtaining ω_n :

$$\angle H(j\omega) = -\tan^{-1} \left(\frac{2\xi \omega_n \omega}{\omega_n^2 - \omega^2} \right)$$

$$\omega = \omega_n \Rightarrow \angle H(j\omega) = -90^\circ$$

- ω corresponding to $\angle H(j\omega) = -90^\circ$ will give ω_n .

Obtaining ξ :

$|H(j\omega)|$ corresponding to $\angle H(j\omega) = -90^\circ$ or $\omega = \omega_n$ will give

$$K/2\xi \Rightarrow \text{Put } K \text{ to get } \xi.$$

↓

Stability Test

Considering the Nichols chart

After finding the corner frequency and the peak gain
and the peak angle
(After the procedure)

INSTRUMENTS

- Analog Meters
- Digital Meters

Best possible accuracy

Typical Resolution

Speed

Noise and Errors

Construction

Power Requirements

Information Storage

Application

Analog Meters

0.1 %

$\frac{1}{100}$ th of Full scale

slow (Electro-mechanical principles used)

Human Parallax Errors

(Accuracy can be reduced by operating near full-scale/proper range selection)

Simple, rugged construction, performed well in harsh conditions.

Derives power from

Measurand
(no need of battery)

Not possible

Process control, panel displays

Flowmeters, pressure gauges, Switch-board meters, etc.

low-cost indication & maintenance, good performance in harsh conditions, less training for operators

Digital Meters

0.005 % or better

$\frac{1}{10000}$ th of Full-scale

very fast, depends on clock frequency

Less error-prone


(Accuracy can be reduced by operating near full-scale/proper range selection)

Less rugged instruments, special care is needed for the electronics

Auxiliary power source needed.

Possible (USB, RS232, etc.)

Most Common Analog Meters

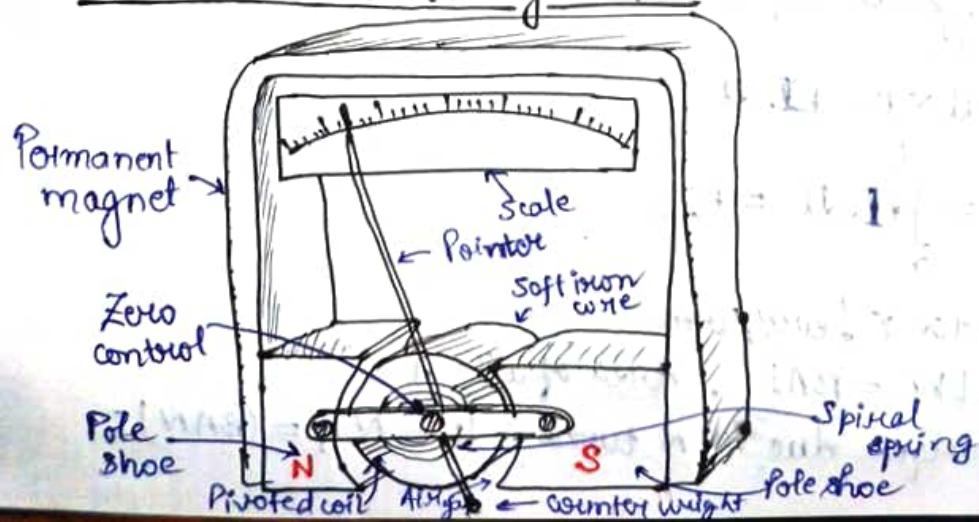

Permanent Magnet Moving Coil (PMMC) Meter

↓
Basic Ammeter
Major Parts:

- Permanent Magnet
- Coil carrying unknown current

Basic Principle: D'Arsonval Movement

Additional Parts:


- Soft Iron Core
- Counter weight
- Zero Control

Shaft iron core: Large relative permeability (μ_r)

↳ helps concentrate the flux into the region of coil.

To remove zero error, move screw to move pointer to zero.

PMMC Meter

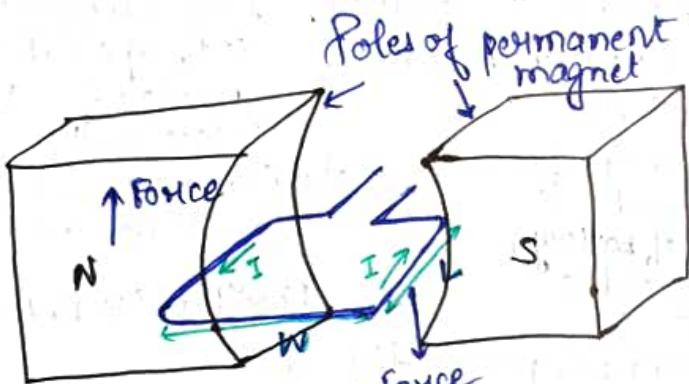

Force (df) on element ds ,

$$df = dq(v \times B)$$

$$Idl = \frac{dq}{dt} \cdot dl = dq \cdot v$$


$$df = I \cdot dl \times B = BI \cdot dl$$

$$\therefore F = \int df = \int BI \cdot dl = BIL$$

Torque = Force \times Lever Arm

$$T_f = BILW = BAI \quad \text{Area of coil} = A$$
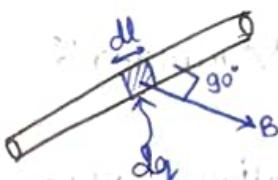
$$\text{Deflecting torque due to } N \text{ turns}, T_b = NT_f = (BAN)I$$




dl : infinitesimal length

dq : Charge flowing through ds in time dt

B : magnetic field provided by magnet

v : velocity of charge carriers

Restoring torque by spring:

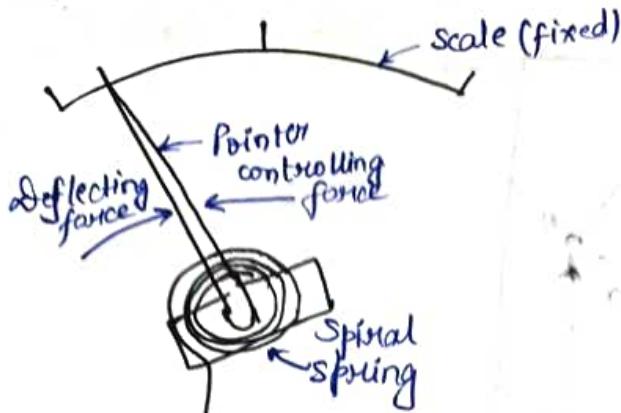

Current, I

Torque due to current,

$$T_I = NT_I = (BAN)I$$

Coil system rotates

Spring to wind-up and introduce a restoring (controlling) torque (say, T_R)

At equilibrium, $T_R = T_I$


$$K_s \cdot \theta = (BAN)I$$

$$\theta = \left(\frac{BAN}{K_s}\right) I = R \times I$$

Deflection of pointer, connected to spring, can be used to measure I

Linear Instrument

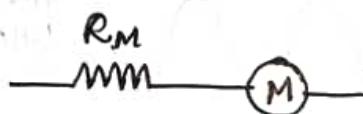Equivalent Electrical Model of PMMC Meter:



R_m : Resistance of coil in the meter


DC Ammeter Using PMMC Principle:

→ Coil has finite resistance:


↪ Basic PMMC meter can only measure limited current (e.g., < 1mA)



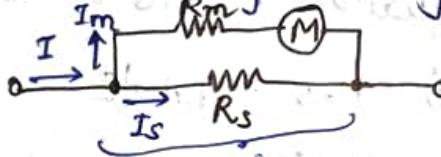→ To measure larger current, place a proper shunt R_s .



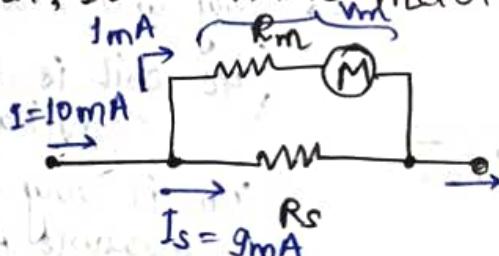Q. Convert a 1mA, 100Ω PMMC meter to an ammeter of 10mA range




$$10\text{mA} = 9\text{mA} \times R_s + 1\text{mA} \times R_m$$

$$1\text{mA} \times R_m = 9\text{mA} \times R_s$$


$$\therefore \Rightarrow R_s = \frac{R_m}{9}$$

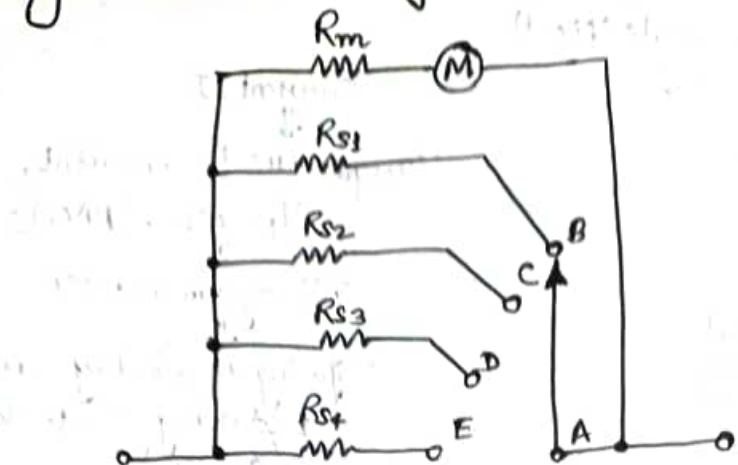Multi-Range Ammeter using PMMC Principle:




Dynamic Characteristics of PMMC Meter

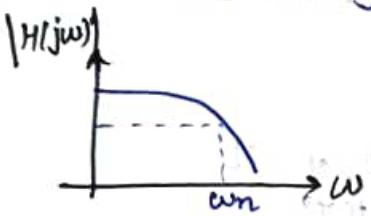→ PMMC meter responds to varying current.



$$i = [1 + 8 \sin \omega t] \text{ mA}$$

$$\omega = 50 \text{ Hz}$$

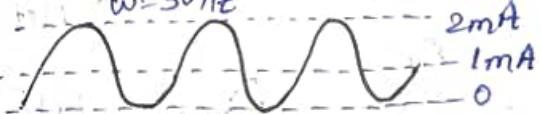

Meter will display average value = 1mA

→ PMMC meter do not respond to AC currents.

↳ settles to DC value of input.

→ Coil system is rotating.

↳ has a moment of inertia, J.

↳ damping coefficient, D.

Steady state equation: $K_s \cdot \theta = (BAN) I$

$$J \ddot{\theta} + D\dot{\theta} + K_s \theta = (BAN) I$$

∴ PMMC meter is a 2nd order instrument.

$$\omega_n = \sqrt{\frac{K_s}{J}} \quad \rightarrow \text{very low value } (< 1 \text{ rad/s})$$

$$\xi_p = \frac{D}{2\sqrt{K_s \cdot J}}$$

[ω_n is very low, so we can't measure AC signals with that]


$\xi > 1$: overdamped PMMC

$\xi = 1$: critically-damped PMMC

$\xi < 1$: underdamped PMMC

ξ, D : can be varied using:

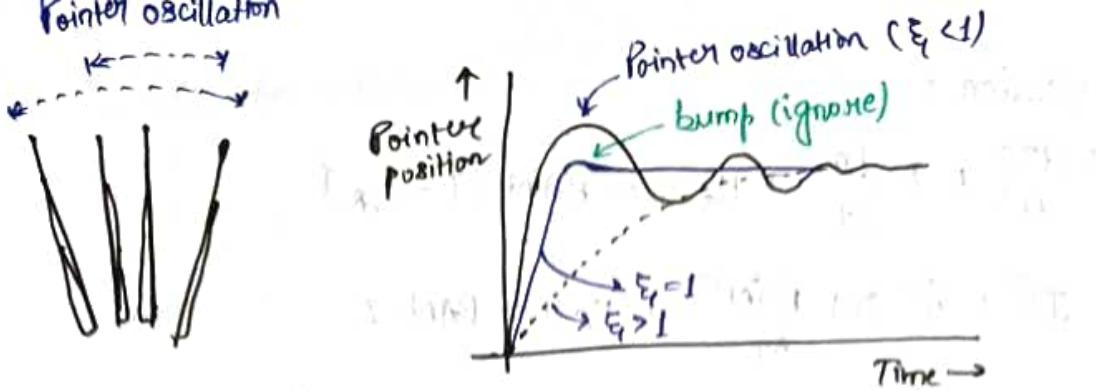- air-damping
- Eddy current damping
- Motional EMF (Air frame)



$\xi < 1$: We don't want overshoot as it may damage the meter (needle crossing maximum deviation).

- ξ close to 1 is preferred.

$$\xi = \frac{D}{2\sqrt{K_s J}}, \quad D, K_s, J : \text{magnetic parameters}$$

\hookrightarrow no control over these

\hookrightarrow To increase damping, use Al coil, causing eddy current which opposes the motion (causing damping).

Induced emf in transient state, [Transient Motional EMF]

$$e_{TR} = B 2 L N V_{TR}, \quad B: \text{magnetic field}$$

V_{TR} : velocity of rotation.

Eliminate V_{TR} : $V_{TR} = \frac{w}{2} \cdot \frac{d\theta}{dt}$

$\therefore e_{TR} = BAN\dot{\theta}$


Current due to e_{TR} , $i_{TR} = \frac{BAN}{R_T} \cdot \frac{d\theta}{dt}$, R_T : total resistance in the coil circuit
 $= R_m + R_E$

$$= \frac{e_{TR}}{(R_m + R_E)}$$

Effective current on meter

$$= I - i_{TR}$$
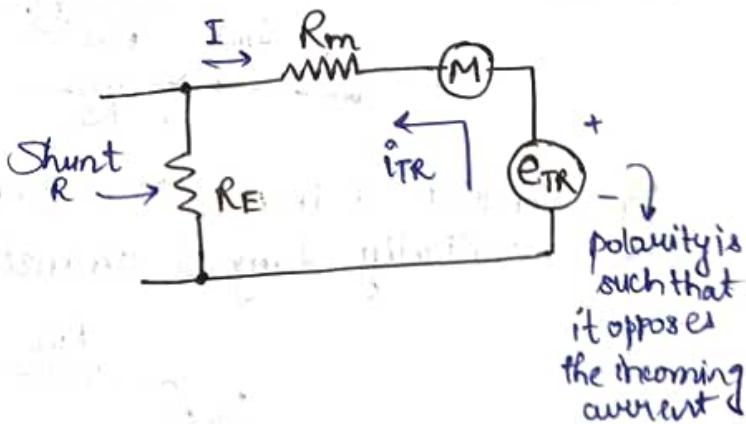
$$\therefore i_{TR} = \frac{BAN}{R_T} \frac{d\theta}{dt}$$



Effective expression:

$$J \frac{d^2\theta}{dt^2} + D \frac{d\theta}{dt} + K_s \cdot \theta = BAN(I - i_{TR})$$

$$\Rightarrow J\ddot{\theta} + \dot{\theta}\left(D + \frac{BAN^2}{RT}\right) + K_S\theta = BAN. I$$

↳ ε_j get affected

↳ we have electrical control over E_g .

$$\xi = \left[D + \frac{B^2 A^2 N^2}{R T} \right]$$


$$= \frac{D + B^2 A^2 N^2}{R M + R E}$$

→ The value of R_E which ensures critical damping : Critical Resistance
 [we can get $\xi = 1$]


$$\xi = 1 \rightarrow R_c = R_E$$

26-02-2024

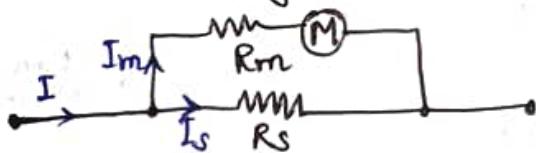Critically Damped DC using Ammeter using PMMC Principle



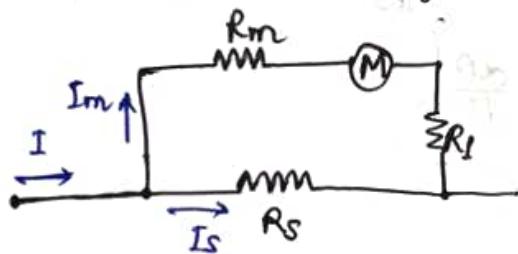Eg. Convert a 1mA, 100Ω PMMC meter with $R_c = 200\Omega$ to a critically damped ammeter of 10mA range.



$$\text{External Resistance, } R_E = R_1 + R_2 = 200 \Omega$$

$$I_m (R_m + R_1) = I_s R_s$$

$$\Rightarrow I_m (100 + R_1) = 9mA \cdot R_s$$

$$\Rightarrow R_s - R_1 = 100\Omega$$


$$\text{Also, } R_E = R_s + R_1 = 200\Omega$$

\hookrightarrow external R.

$$\therefore 10R_s = 300\Omega \Rightarrow R_s = 30\Omega$$

$$\text{and, } R_1 = 200 - 30 = 170\Omega.$$

DC Voltmeter Using PMMC Principle

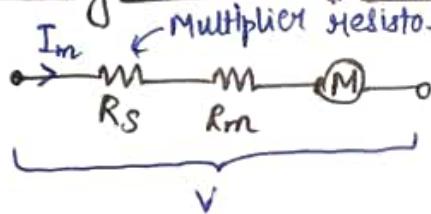

I_{FS} : full-scale current

θ_{FS} : full-scale deflection

Eg. Convert a 1mA, 100Ω PMMC meter to a 10V voltmeter.

$$\frac{10}{R_s + R_m} = 1mA \Rightarrow R_s = 9.9K\Omega$$

For an PMMC meter, output is θ ;
input is I .

We can define our own sensitivity as

$$S = \frac{\theta}{I}$$


Since, PMMC is linear, $S = \frac{\theta_{FS}}{I_{FS}}$

Normalised w.r.t. θ , (since θ is mechanical parameter)

Voltmeter Sensitivity $\left\{ \begin{array}{l} S = \frac{1}{I_{FS}} : \text{Ammeter sensitivity} \\ S = \frac{R_s + R_m}{I_{FS}} : \text{Voltmeter sensitivity} \end{array} \right.$

AC Voltmeter using PMMC Principle

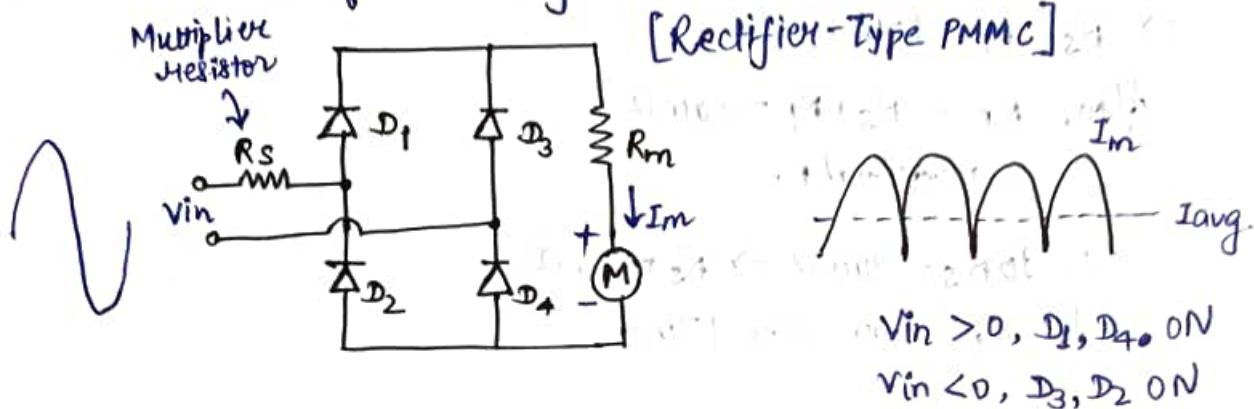→ RMS value of the AC input needs to be measured.



$$I_{avg} = \frac{2}{\pi} I_{peak} \quad (\text{Full wave Rectifier})$$


$$I_{rms} = \frac{I_{peak}}{\sqrt{2}}$$

Eg. Convert a 1mA, 100Ω PMMC meter to a 10V AC voltmeter.

RMS value $\rightarrow 10V$

Peak value $\rightarrow 10\sqrt{2} V$

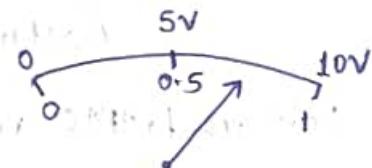Peak current $\rightarrow \frac{10\sqrt{2}}{R_s + R_m}$



$$\text{Now, } \frac{I}{\pi} \left(\frac{10\sqrt{2}}{R_s + R_m} \right) = 1\text{mA}, \quad R_m = 100\Omega \\ = 0.1k\Omega$$

$$\Rightarrow R_s = 8.9k\Omega$$


$$\therefore 10V \xrightarrow{\text{RMS}} 1mA \quad (\text{meter})$$

→ Due to non-ideal behaviour of diode (V_D & R_{on}), there will be error.

→ If we measure a square wave with this, then after rectifier this square wave will convert to DC.

V_{avg} : DC value only.

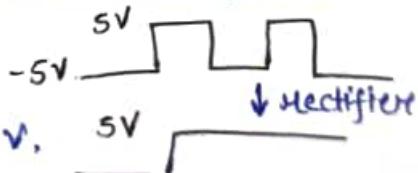So for 5V $\rightarrow V_{avg.}$, here, is 5V.




$$\therefore \frac{5}{8.9+0.1} = \frac{5}{9} = 0.55 \text{ mA} > 0.5 \text{ mA}$$

Disadvantages (Issues) of PMMC:

- Cannot be used for AC measurement without rectifier circuit (Threshold voltage, on resistance of diodes).
- Not a generic solution for AC voltage measure
 - ↳ Solution: Introduce Separate Scale for different inputs.

Modified Principle

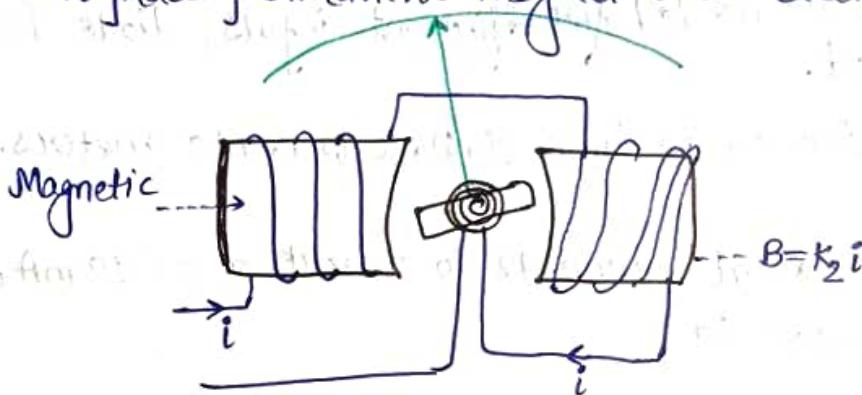↳ Replace permanent magnet with electromagnet.



$$\text{Now, } B = k_2 i$$

$$T_f = (BAN)i$$

$$= (k_2 AN)i^2$$

$$= K_s \cdot \theta$$

$$\boxed{\theta = \left(\frac{k_2 AN}{K_s} \right) i^2}$$

Now, Since i is AC

$$\theta = Ki^2$$



θ will also be ac.

$$\theta_{\text{avg.}} = K \cdot \frac{1}{T} \int i^2 dt \quad , \quad \boxed{K = \frac{k_2 AN}{K_s}}$$

$$\boxed{\theta_{\text{avg.}} = K I_{\text{rms}}^2}$$

In case of DC, $\boxed{\theta = K I^2}$ so, scaling factor is same for AC and DC.

→ Same current is connected to the coil through the spring.

↪ Electrodynamometer Principle (A modified principle)

→ Two coils: One fixed and one movable; both carry unknown current.

→ Gives the square of rms value of any periodic input.

→ Non-linear scale.

→ Have higher current rating compared to PMMC.


→ Calibration can be done for DC and same instrument can be used for AC measurement.

→ No separate scale needed for different inputs, diode bridge not required.

→ Range extension can be done similar to PMMC meters.

Eg. Design suitable shunt networks to convert a 0-10mA, 100Ω electrodynamometer to

Ⓐ 0-1 A DC ammeter.

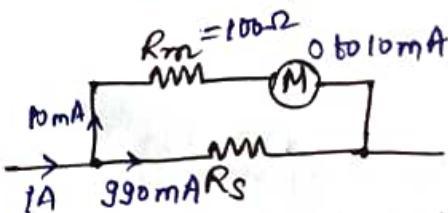

$$10 \times R_m = R_s \times 990 \Rightarrow R_s = \frac{R_m}{99} = \frac{100}{99} \Omega$$

$$\Rightarrow R_s = 1.01 \Omega$$

Ⓑ 0-1 A AC ammeter

↪ No change of shunt R_s, R_s = 1.01 Ω.

Ⓒ 0-100 A AC ammeter

↪ Approx R_s = $\frac{10 \times 100}{100}$ = 10 mΩ.

Factors during High current measurement:


- ① Shunt resistance becomes low.
- ② Large power dissipation ($I_s^2 R_s$ is very high).
- ③ Risk to operator.

Factors during High voltage measurement:


- ① Series resistance becomes very high.
- ② Resistance leakage.
- ③ Large power dissipation.

Solution for high current measurement:

↳ Put a step down transformer.

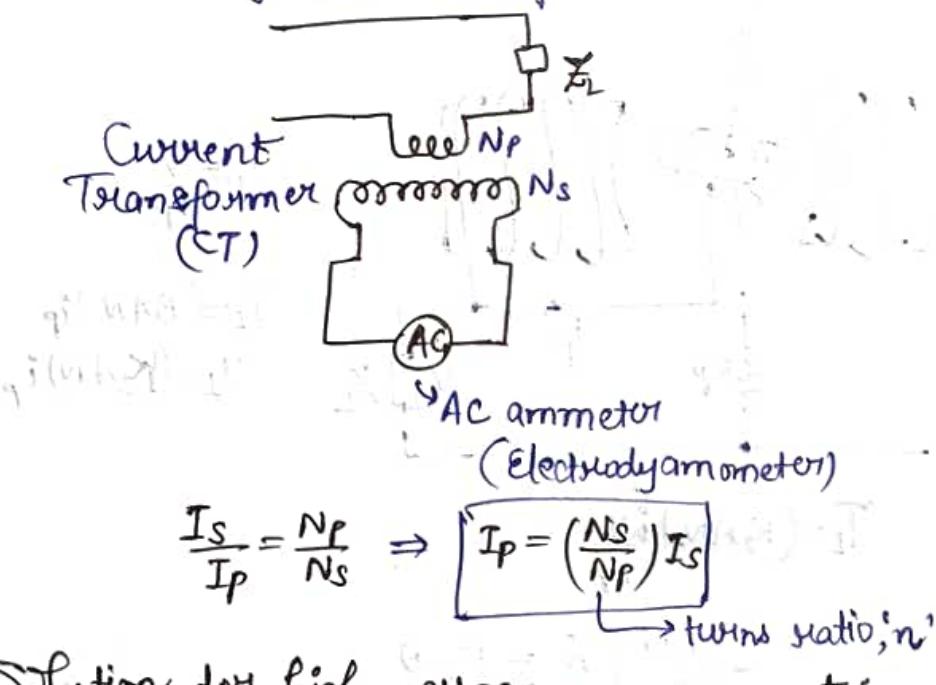

Solution for high voltage measurement:

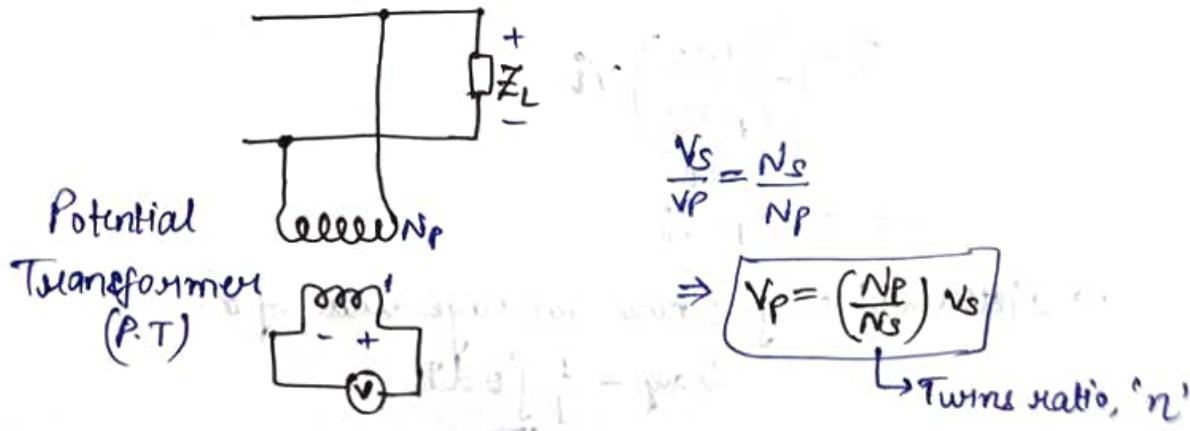


Instrument Transformer

Current Transformer
(C.T.)

Potential Transformer
(P.T.)

Power Measurement:

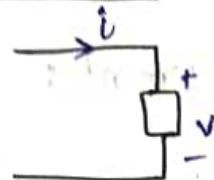


$$P_{avg.} = \frac{1}{T} \int_{T_0}^T v \cdot i dt$$

$$v = V_{rms} \cos \omega t$$

$$i = I_{rms} \cos(\omega t - \phi)$$

$$\therefore P_{avg.} = V_{rms} \cdot I_{rms} \cdot \cos \phi$$

Electrodynamometer for Wattmeter

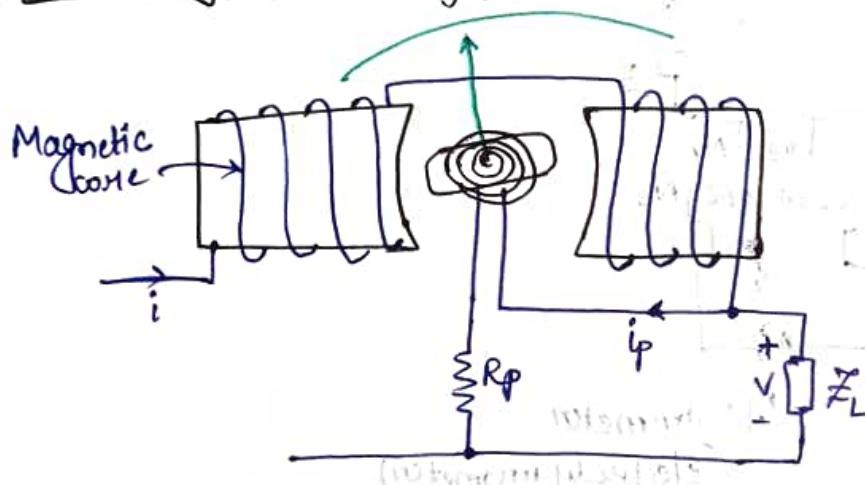

$$i_p = \frac{v}{R_p}$$

$$T_I = (B_1 N) i_p$$

$$T_E = (K_2 A N) i_p$$

$$T_E = \left(\frac{K_2 A N}{R_p} \right) i v$$

$$\theta = \left(\frac{K_2 A N}{R_p \cdot K_s} \right) v i$$

$$\Rightarrow \theta = K_p \cdot v i$$

→ Meter will only show average value of θ .


$$\theta_{avg.} = \frac{1}{T} \int_{T_0}^T \theta dT$$

$$\Theta_{\text{avg.}} = \frac{k_p}{T} \int_{CT} v_i dt$$

$$\therefore \Theta_{\text{avg.}} = k_p \cdot P_{\text{avg}}$$

Fixed coil : Current coil (C) \rightarrow Thick wires

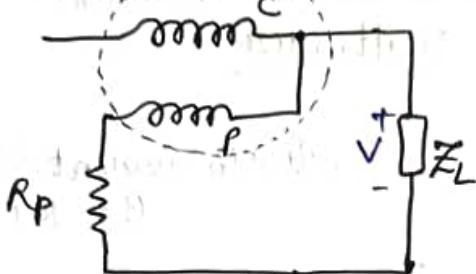Movable coil : Voltage / Pressure coil (P) \rightarrow Thin wires
Wattmeter



\rightarrow Gives average power for periodic inputs.

\rightarrow Calibration can be done for DC and same calibration will hold good for AC measurement.

$$\Theta_{\text{avg.}} = \frac{k_p}{T} \int_{CT} v_p i_c dt, \quad v_p = v, \quad i_c = i + i_p$$

$$= \frac{k_p}{T} \int_{CT} v_i dt + \frac{k_p}{T} \int_{CT} v i_p dt \quad [v = i_p R_p]$$

$$\Rightarrow \Theta_{\text{avg.}} = \Theta_{\text{true}} + \frac{k_p}{T} \int_{CT} v i_p dt$$

$$= \Theta_{\text{true}} + \frac{k_p R_p}{T} \int_{CT} i_p^2 dt$$

the error


$$\therefore \Theta_{\text{avg.}} > \Theta_{\text{true}}$$

Now, to minimize error,

$$i \gg i_p \Rightarrow i \gg \frac{v}{R_p}$$

\hookrightarrow This instrument ~~will~~ is more suited for high current low voltage load.

Now,

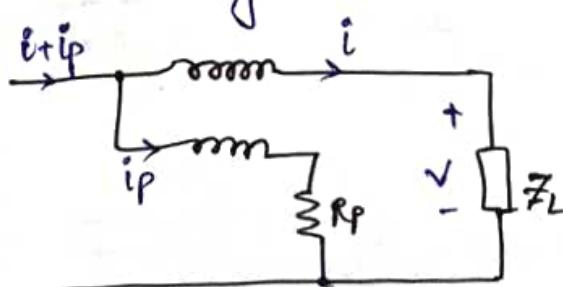

R_C : Resistance of coil

$$\Theta_{avg} = \frac{K_p}{T} \int_{CT} i(v + iR_c) dt$$

$$= \frac{K_p}{T} \int_{CT} v i dt + \frac{K_p}{T} \int_{CT} i^2 R_c dt$$


$$\Rightarrow \Theta_{avg} = \Theta_{true} + \frac{K_p}{T} \int_{CT} i^2 R_c dt$$

$$\therefore \Theta_{avg} > \Theta_{true}$$

To minimise error, $v \gg iR_c$: Suited for high voltage, low current

Universal Wattmeter : Compensated Wattmeter

In current coil,

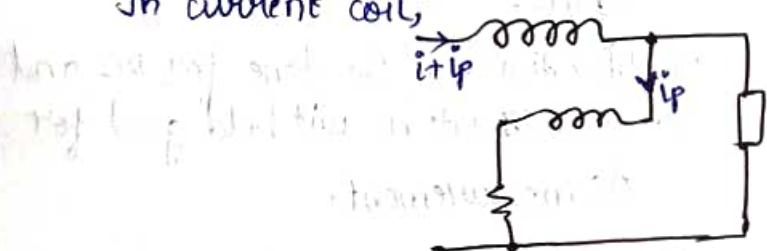

Earlier in current coil,
 $B = K(i + i_p)$

We have to remove the effect of i_p in current coil.

So, we can direct i_p wire into same coil in opposite way.

$$\text{So, net } B = K_p(i + i_p) - K_p i_p$$

$$= K_p i$$

↳ Can be used to detect AC only.

↳ Intrusive measurement.

→ Non-intrusive measurement is using measurement of magnetic field due to current-carrying coil.

Hall Effect Sensors

$$V_H = K_T B_m$$

$$\text{Sensitivity, } K_T = \frac{I}{nq d_H} = 0.625 \frac{\mu\text{V}}{\text{T}}$$

$$= 0.625 \frac{\text{nV}}{\text{mT}} \gg \text{noise}$$

$$I = 1\text{mA}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$n = 10^{27} \text{ m}^{-3}$$

$$d_H = 10 \mu\text{m}$$



Improving K_T :


- $I \uparrow$ (not preferable) \rightarrow more power consumption
 - $n \downarrow$
 - $d_H \downarrow$ (already very low)
- $\Rightarrow n \downarrow$

Take $n = 6 \times 10^{21} \text{ m}^{-3}$ (doped Si)

$$\therefore K_T = 0.1 \frac{\text{mV}}{\text{mT}}$$


$$= 100 \frac{\mu\text{V}}{\text{mT}}$$

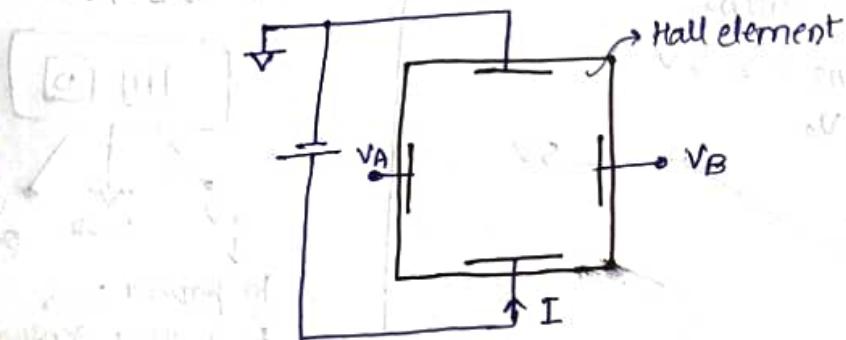Commercially available hall effect sensors are made up of doped semiconductor, and not metal, for this reason.



$$V_H = V_A - V_B$$

Difference amplifier:

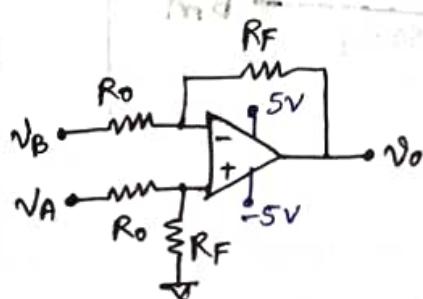


$$V_o = G_{ID} (V_A - V_B) = G_{ID} K_T B_m,$$


where $G_{ID} = \frac{R_F}{R_O} = 100$

$$G_{ID} K_T = 10 \frac{\text{mV}}{\text{mT}}$$


IC:

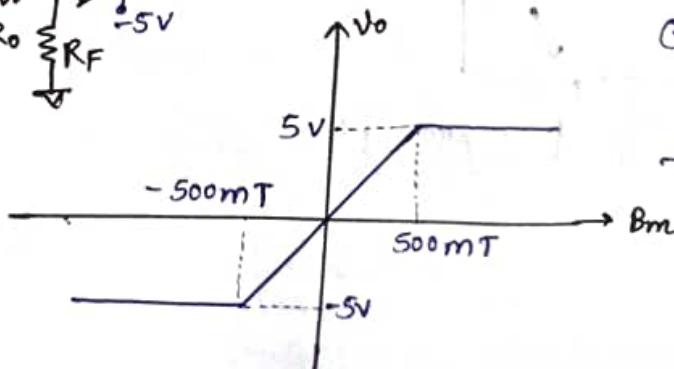

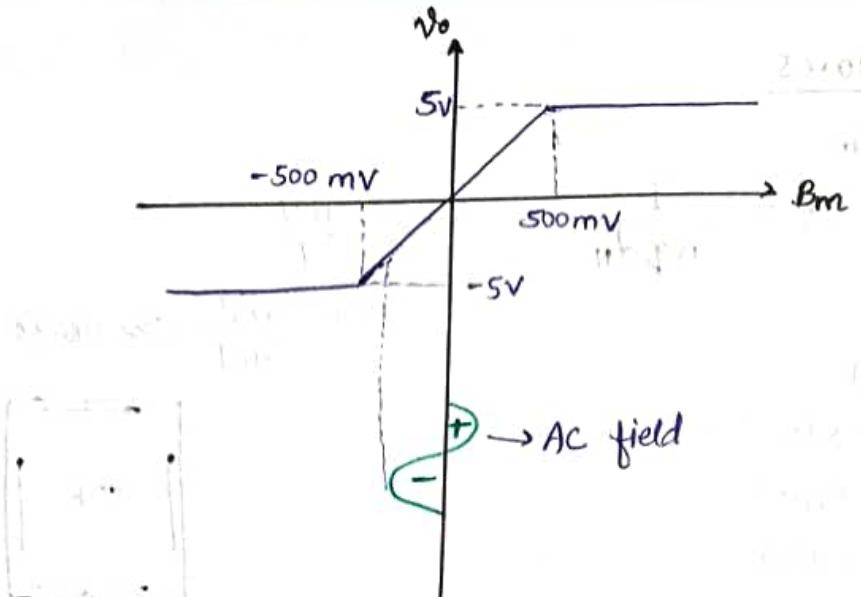→ Limitation due to power supply, not hall effect sensor.



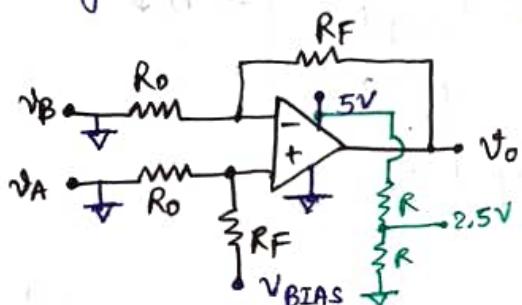- We want only one power supply for the opamp (say, only 5V) while detecting both positive and negative AC fields.





(Superposition principle)

$$V_o = G_{ID} K_T B_m + V_{BIAS} \frac{R_O}{R_O + R_F} \left(\frac{R_O + R_F}{R_O} \right) \text{ gain}$$

$$V_o = G_{ID} K_T B_m + 2.5V$$

Take $V_{BIAS} = 2.5V$

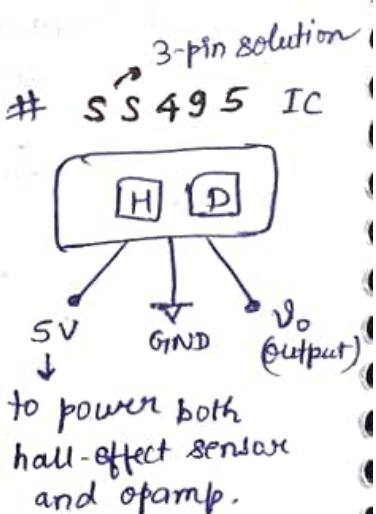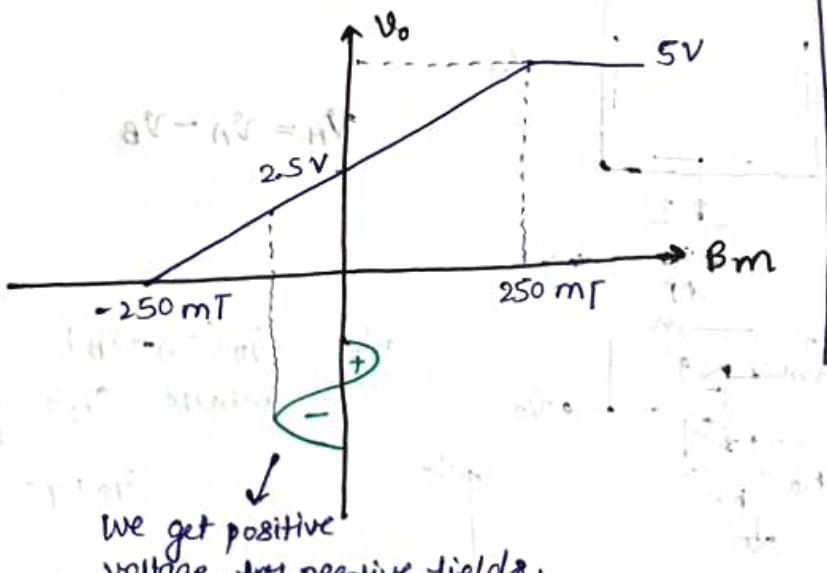


MEASUREMENT CIRCUITS



A: open loop gain of the opamp

$$v_o = A(v_1 - v_2)$$

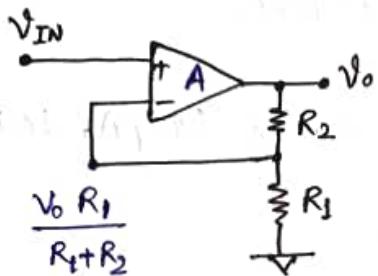

$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_{IN}$$

$$v_o = A \left[v_{IN} - v_o \frac{R_1}{R_1 + R_2} \right]$$


$$= \left[\frac{1 + R_2/R_1}{1 + \frac{1}{A}(1 + R_2/R_1)} \right] v_{IN}$$

$$= \frac{G_o v_{IN}}{1 + \frac{G_o}{A}}, \quad G_o = 1 + \frac{R_2}{R_1}$$

For $G_o \ll A$ or $\frac{G_o}{A} \ll 1$,

$$v_o = G_o v_{IN}$$

$$G_o = 2 \text{ (say)}$$

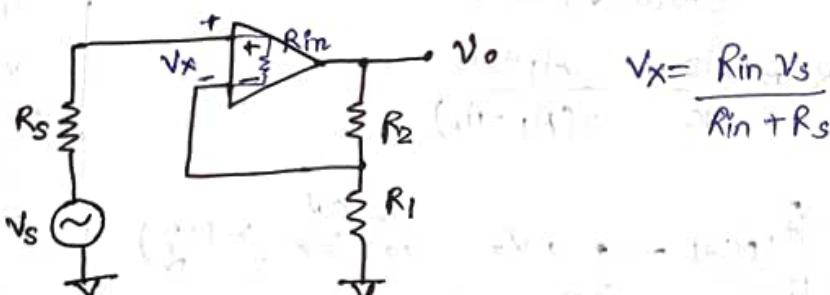

$$v_x = \frac{R_{in} v_s}{R_{in} + R_s}$$

[we want v_s to be directly fed to the opamp for amplification
⇒ $R_{in} \ll \gg$]


$R_s \approx 100 M\Omega$ (very large input impedance)

$R_{in} \gg R_s$ (large input resistance, R_{in})

BJT-based opamp
OP07
LM741

FET-based opamp
TL082
LF356

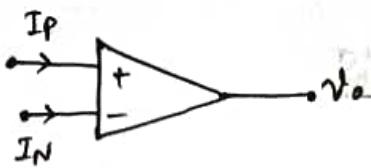FET-based opamp has higher input impedance
⇒ better than BJT-based opamp.



$$\text{Bias current, } I_B = \frac{I_P + I_N}{2}$$


$$\text{Offset current, } I_{OS} = |I_P - I_N|$$

LM741

$$I_B \approx 80\text{nA}$$

$$I_{OS} \approx 3\text{nA}$$

$$I_{OS} < I_B/10$$

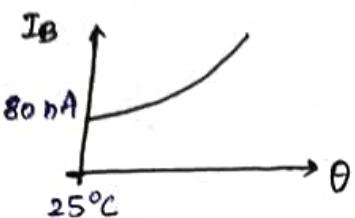


→ Must look for this in the datasheet.

For current measurement in the range (10pA , $10\mu\text{A}$).

Electrometer → e.g., OPA128

$$I_B \approx 100\text{fA}$$

5-03-2024

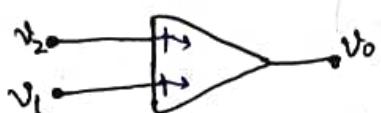

A_D : difference gain (=open loop gain)

$$\text{Ideal: } V_o = A_D (V_1 - V_2)$$

LM741: CMRR $\approx 80\text{dB}$
OP07: CMRR $\approx 120\text{dB}$

Actual:

$$V_o = A_1 V_1 - A_2 V_2$$

$$= A_D (V_1 - V_2) + A_C \left(\underbrace{\frac{V_1 + V_2}{2}}_{V_{CM}} \right)$$

common-mode gain $\underbrace{V_{CM}}$ (common-mode signal)

$$= A_D V_D + A_C V_{CM}$$

Error ↓, A_C ↓

$$\text{CMRR} = \frac{A_D}{A_C} = \frac{A_1 + A_2}{2(A_1 - A_2)}$$


$$V_D = V_1 - V_2$$

$$2V_{CM} = V_1 + V_2$$

$$V_1 = \frac{V_D}{2} + V_{CM}$$

$$V_2 = -\frac{V_D}{2} + V_{CM}$$

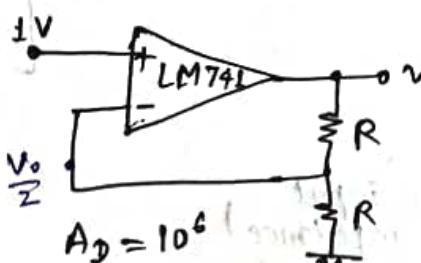Here,
 V_{CM} is common
in both eqn,
that is why it is
called common-
mode signal




$$\text{Ideal } V_o = 2V \left(= \frac{1+R}{R} \right)$$

$$\text{CMRR} = 80\text{dB} \Rightarrow 10^4$$


$$A_C = 10^2$$

$$\begin{aligned} V_D &= 1 - V_o/2 \\ V_{CM} &= \frac{1+V_o/2}{2} \end{aligned} \quad \Rightarrow V_o = 2.0002 \text{ V}$$

$$\text{error} = 200 \mu\text{V}$$

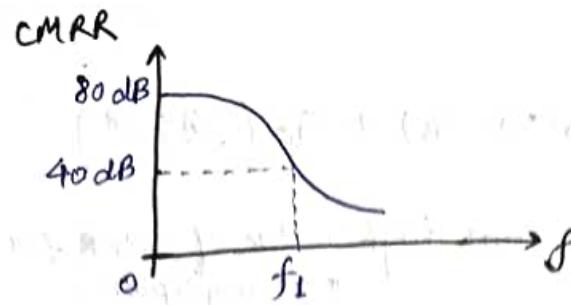

Inverting Amplifier:

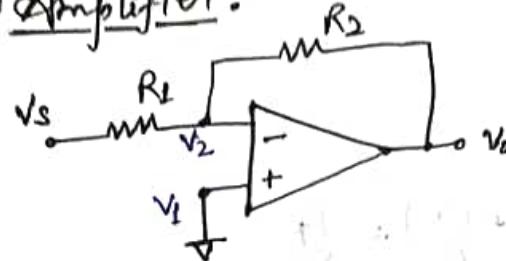


$$V_{CM} = \frac{V_1 + V_2}{2} \approx 0$$

(By virtual short)

$$V_{OOL} \approx 0$$

$\therefore V_0$ is very close to the actual value.

Difference Amplifier

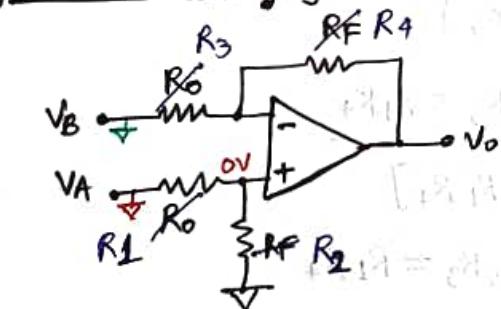

Ideal:

$$V_0 = \frac{RF}{R_0} (V_A - V_B)$$

$$= G_{ID} (V_A - V_B)$$

I88ue:

• we need 2 pairs of matched resistances (R_0, R_F).

t : tolerance

[1% tolerance]

$$t = 0.01$$

$$R_1, R_3 \in [R_0(1-t), R_0(1+t)]$$

$$R_2, R_4 \in [R_F(1-t), R_F(1+t)]$$

What value to 't' we should use?

$$V_0 = \underbrace{\frac{R_2}{R_1 + R_2} \left(1 + \frac{R_F}{R_3} \right)}_{G_1} V_A - \underbrace{\frac{R_F}{R_3}}_{G_2} V_B$$

(By superposition principle)

→ Gain offered to V_A and V_B are different.

Actual:

$$V_o = G_1 V_A - G_2 V_B = G_D (V_A - V_B) + G_C \left(\frac{V_A + V_B}{2} \right)$$

$$CMRR_R = \frac{G_D}{G_C} \quad \rightarrow \text{we want high value of CMRR for our amplifier}$$

↓ due to tolerance

$$= \frac{G_1 + G_2}{2(G_1 - G_2)}$$

$$= \frac{\frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3} \right) + \frac{R_4}{R_3}}{2 \left[\frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3} \right) - \frac{R_4}{R_3} \right]}$$

$$= \frac{R_2(R_3 + R_4) + R_4(R_1 + R_2)}{2 \left[R_2(R_3 + R_4) - R_4(R_1 + R_2) \right]}$$

$$= \frac{R_1 R_4 + R_2 R_3 + 2 R_2 R_4}{2(-R_1 R_4 + R_2 R_3)}$$

$$\therefore CMRR_R = \frac{2 R_2 R_4 + R_2 R_3 + R_1 R_4}{2 \left[R_2 R_3 - R_1 R_4 \right]}$$

$$\max CMRR \Rightarrow R_2 R_3 = R_1 R_4$$

$$\min CMRR \Rightarrow (R_2 R_3 - R_1 R_4) \text{ becomes maxm}$$

$$\Rightarrow \begin{cases} R_2 = R_F(1+t) \\ R_3 = R_o(1+t) \\ R_1 = R_o(1-t) \\ R_4 = R_F(1-t) \end{cases}$$

$$\therefore CMRR_R = \frac{2 R_F^2 (1-t^2) + R_F R_o (1+t)^2 + R_F R_o (1-t^2)}{2 \left[R_F R_o (1+t)^2 - R_F R_o (1-t)^2 \right]}$$

$$= \frac{2 R_F (1-t^2) + R_o [2 + 2t]}{2 R_o [4t]}$$

$$= \frac{R_F (1-t^2) + R_o (1+t)}{4 R_o t}$$

$$G_D = R_F/R_O$$

$$\therefore CMRR_R = \frac{2G_D(1-t^2) + 2(1+t^2)}{2(4t)}$$

$$= \frac{G_D + 1 + t^2(1-G_D)}{4t}$$

Now, as t is tolerance (say, 1% $\Rightarrow 0.01$)

$$\therefore t^2 \ll 1$$

Mence, t^2 term can be neglected.

$$\therefore CMRR_R = \frac{G_D + 1}{4t}$$

$$\text{Eg, } G_D = 10, t = 0.05$$

$$CMRR_R = \frac{11}{0.2} = 55$$

\downarrow

$$20 \log(55)$$

\downarrow

$$34 \text{ dB}$$

Even though tolerance was low, CMRR is limited.

$$\text{For } t = 0.01,$$

$$CMRR_R = \frac{11}{0.04} = 275 \xrightarrow{20 \log 275} 44 \text{ dB.}$$

Issue: Differential amplifier has limited CMRR.

$$CMRR_R \ll CMRR_{\text{opamp}} \quad [\because \text{CMRR of opamp} = 120 \text{ dB}]$$



$\downarrow 10^6$

Assume $CMRR_{\text{OA}}$ is opamp's, resistive network has $CMRR_R$, then total system has CMRR of $CMRR_T$.

$$CMRR_T = f(CMRR_R, CMRR_{\text{OA}})$$

Obtain f :
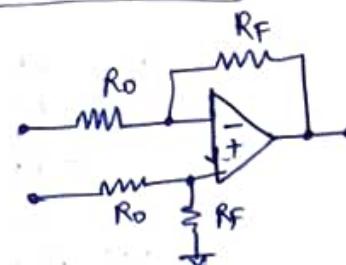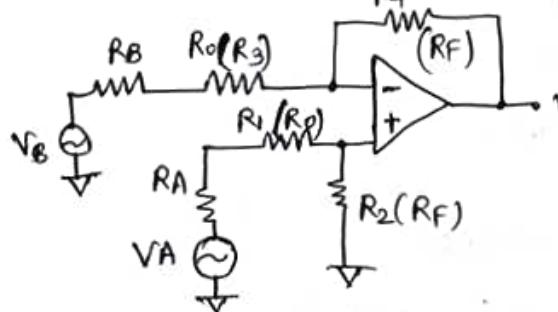
$$CMRR_T = \frac{CMRR_R \cdot CMRR_{\text{OA}}}{CMRR_R + CMRR_{\text{OA}}}$$




Other Issues:

- Effect of i/p resistances: Internal resistances of i/p sources (R_A & R_B) are in series with R_3 & R_1 , hence there is more degradation in CMRR. \Rightarrow Affects gain.

- 2 potentiometers: for gain tuning, we need to change 2 resistors (say, keep 2 rheostats/potentiometers) \Rightarrow Reduce to 1.

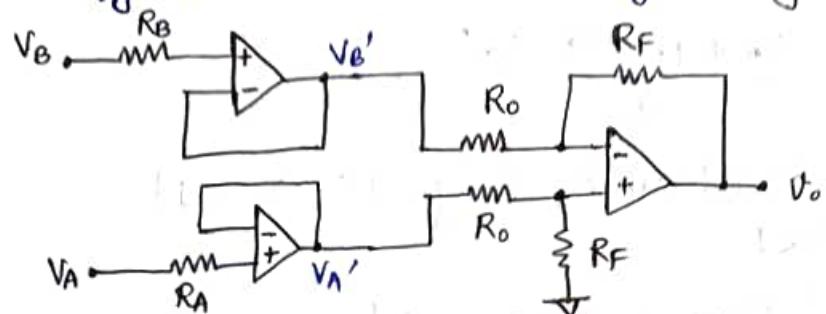
Solution: Nullify effect of R_A and R_B using voltage follower.



Make voltage amplifiers

as non-inverting amplifiers.

$$V_o = \frac{R_F}{R_o} (V_A - V_B)$$

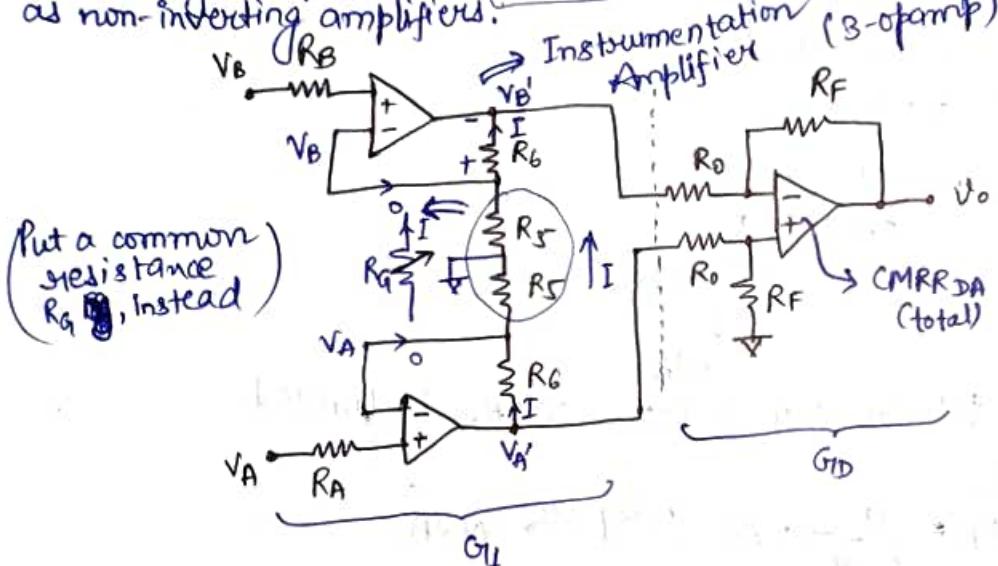

$$V_A' = \left(1 + \frac{R_6}{R_5}\right) V_A$$

$$V_B' = \left(1 + \frac{R_6}{R_5}\right) V_B$$

$$\Rightarrow V_o = \frac{R_F}{R_o} (V_A - V_B) \left(1 + \frac{R_6}{R_5}\right)$$

$$\text{As } I = \frac{V_A - V_B}{R_G}$$

$$V_A' = V_A + IR_G$$

$$V_B' = V_B - IR_G$$

$$\therefore V_o = \frac{R_F}{R_o} (V_A' - V_B')$$

$$= \frac{R_F}{R_o} (V_A - V_B + 2IR_G)$$

$$V_A' - V_B' = (V_A - V_B) \left(1 + \frac{2R_6}{R_G}\right)$$

$$\therefore V_o = \frac{R_F}{R_o} \left[\underbrace{\left(1 + \frac{2R_6}{R_G}\right)}_{G_D} \right] (V_A - V_B)$$

→ Gain tuning can be done through changing R_G .

$G_I = 1 + \frac{2R_6}{R_G}$: gain offered by the 1st stage.

$G_D = \frac{R_F}{R_o}$: gain offered by the 2nd stage.

$$\text{Hence, } V_o = G_D \cdot G_I (V_A - V_B)$$

$$\text{CMRR}_{DA} = \frac{G_D}{G_C}$$

$$V_o = G_D (V_A' - V_B') + G_C \left(\frac{V_A' + V_B'}{2} \right)$$

$$\text{As } V_A' = V_A + IR_6$$

$$V_B' = V_B - IR_6$$

$$\Rightarrow V_A' - V_B' = G_I (V_A - V_B) \quad \} \text{ large gain to difference signal}$$

$$\frac{V_A' + V_B'}{2} = \frac{V_A + V_B}{2} \quad \} \text{ gain of 1 to common mode signal}$$

Hence, our CMRR will be more as preferential gain to difference signal given.


$$\therefore \boxed{V_o = G_D G_I (V_A - V_B) + G_C \left(\frac{V_A + V_B}{2} \right)}$$

CMRR of instrumentation amplifier,

$$\text{CMRR}_{IA} = \left(\frac{G_D}{G_C} \right) G_I$$

$$\Rightarrow \boxed{\text{CMRR}_{IA} = \text{CMRR}_{DA} \times G_I}$$

3 - Opamp Instrumentation Amplifier

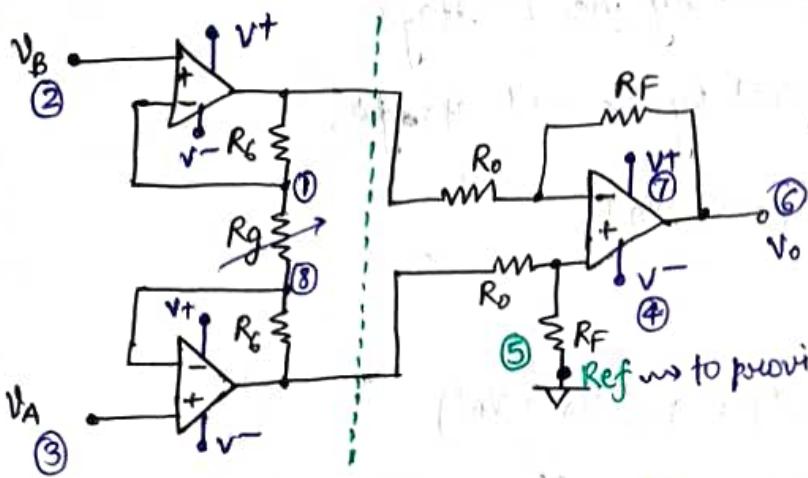

R_g : for tuning


$$G_{IA} = 1 + \frac{2R_F}{R_g}, \quad R_D = \frac{R_D}{R_0}$$

$$G_{IA} = G_I G_D$$

$$CMRR_{IA} = CMRR + 20 \log G_I$$

by Texas Instruments by Analog Devices

↓
ICs: INA 129, AD 620,
INA 101

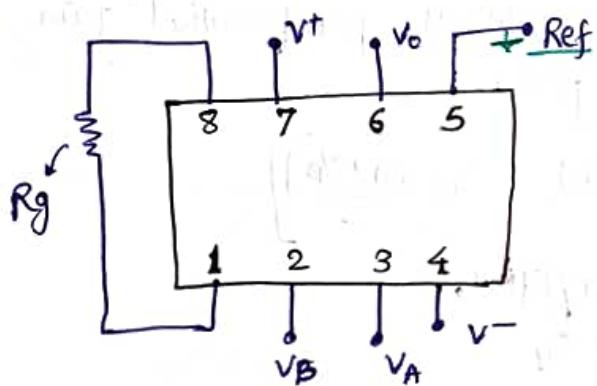

RF, Ro

Laser-Trimmed Devices
↳ Type tolerance
↳ made using MOSFET inside IC.

Laser-trimmed devices:

$$RF = R_0$$

$$\Rightarrow G_D = 1$$

$$G_{IA} = G_I = 1 + \frac{2R_F}{R_g} = 1 + \frac{50K}{R_g}$$


$$R_F = 25K\Omega$$

$$G_{IA} = 10 \Rightarrow R_g = \frac{50K}{9}$$

$$CMRR_{IA} = 80 \text{ dB}$$

$$CMRR_{IA} = 80 + 20 \log(10)$$

$$= 80 + 20 = 100 \text{ dB.}$$

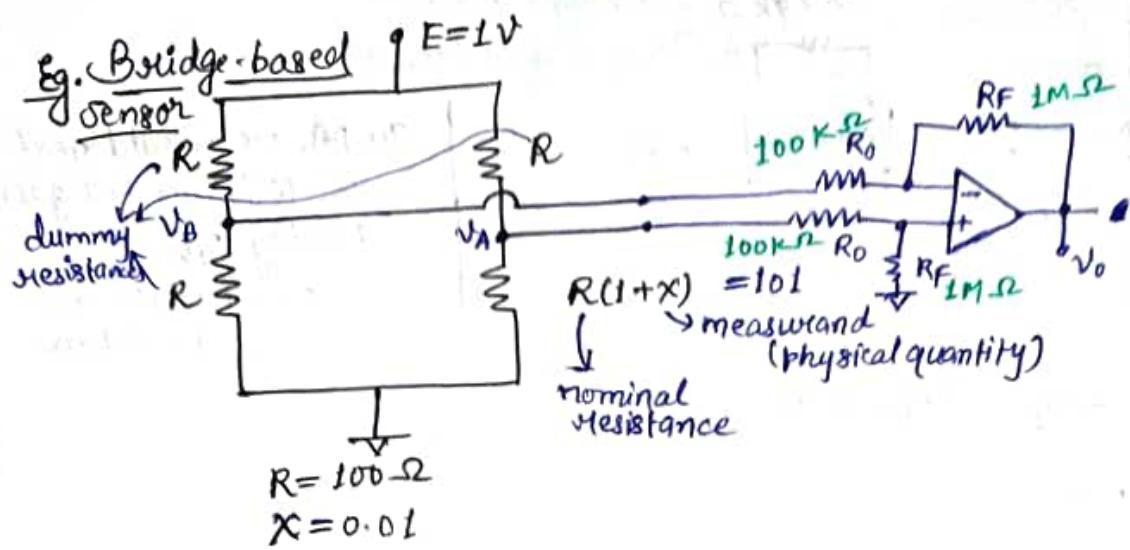

$$V_A = \frac{101}{201} V$$

$$V_B = \frac{1}{2} V$$

$$\Rightarrow V_A - V_B = 2.49 mV$$

$$\therefore V_o = 10(V_A - V_B)$$

$$= 24.9 mV \text{ (Ideal value)}$$

Connecting

difference: $R_F = 10R_0$

Amplifier $t = 0.01$ (1% tolerance)

$$CMRR = \frac{11}{0.04} = 275 = \frac{G_D}{G_C}$$

$$G_C = \frac{10}{275}$$

$$V_o = G_D V_D + G_C V_{CM}$$

$$V_{CM} = \frac{V_A + V_B}{2} \approx 501 mV$$


$$\therefore V_o = 43.1 mV$$

$$\% \text{ error} = \frac{43.1 - 24.9}{24.9} \times 100\%.$$

$$= 73\%$$

↳ very large error for
1% tolerance resistors.

Solution: Use Instrument amplifier.

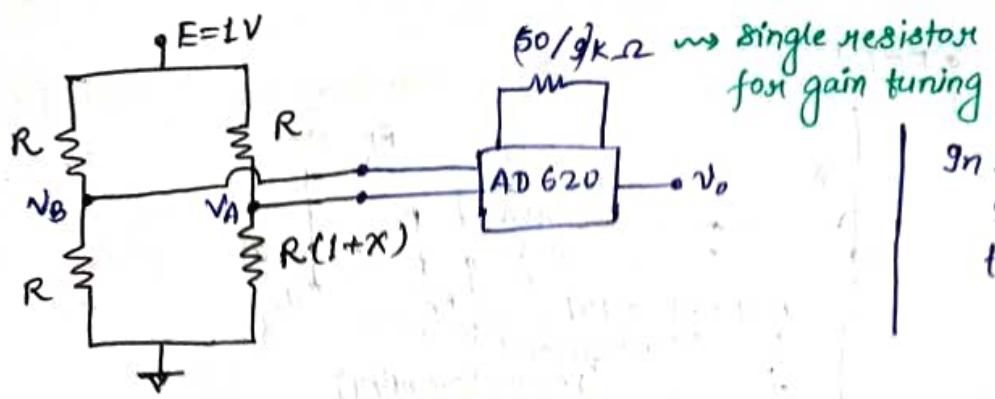

$$G_{IA} = 10 = G_1 \quad (\text{objective})$$

$$R_g = \frac{50}{g} \text{ k}\Omega$$

$$\text{CMRR}_{DA} = 10^4 = \frac{G_D}{G_C} \quad [G_D = 1 \text{ for } R_o = R_F]$$

$$\Rightarrow G_C = 10^{-4}$$

$$\begin{aligned} \therefore V_o &= G_D G_1 (V_A - V_B) + G_C \left(\frac{V_A + V_B}{2} \right) \\ &= (1)(10)(2.49) + 10^{-4}(50) \end{aligned}$$

$$\Rightarrow V_o = 24.95 \text{ mV}$$

$$\% \text{ Error} = \frac{24.95 - 24.9}{24.9} \times 100\% = 0.2\%$$

73% (DA)




0.2% (IA)

Laser trimmed resistor

- ↳ Resistors made from transistors
- ↳ W & L are perfectly chosen.

2-Opamp IA:

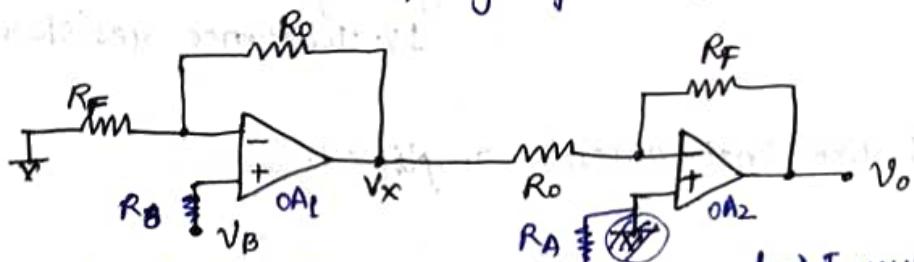- ↳ 1 Resistor for gain tuning
- ↳ High input resistance
- ↳ Lower cost (sacrificing high CMRR)



$$\text{To get: } V_o = G_1 (V_A - V_B)$$

$$V_x = V_B \left[1 + \frac{R_o}{R_F} \right]$$

↳ Inverting amplifier
↳ Feed V_A
↳ to get same gain ~~for~~ (G_1) for V_A as V_B.

$$V_o = -\frac{R_F}{R_o} V_x = -\left(\frac{R_F}{R_o} + 1\right) V_B$$


Feed V_A to 2nd opamp : $V_o = \left(1 + \frac{R_F}{R_o}\right) (V_A - V_B)$

As V_A and V_B are directly fed to opamps, resistances (internal of source) R_A and R_B will not have much effect.

Objective: Achieve single resistance based gain tuning.

R_o : Feedback resistance for OA_1 and input resistance for OA_2 .

R_g \rightarrow affects both R_o

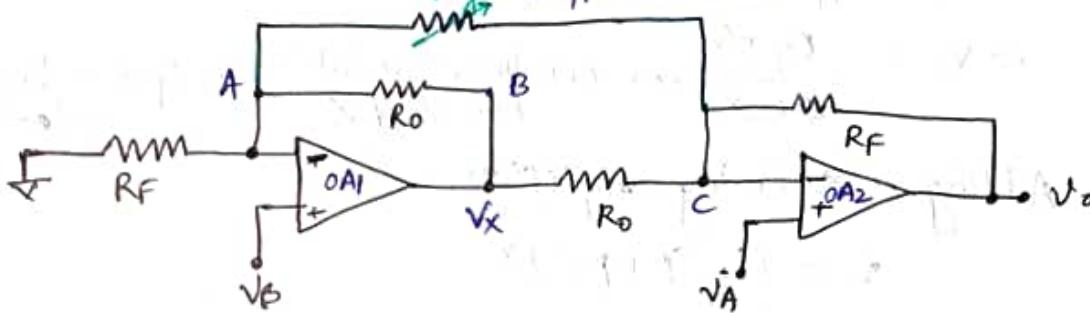

KCL @ V_B :

$$V_B \left[\frac{1}{R_o} + \frac{1}{R_F} + \frac{1}{R_g} \right] = \frac{V_x}{R_o} + \frac{V_A}{R_g} \quad \dots \textcircled{1}$$

KCL @ V_A :

$$V_A \left[\frac{1}{R_o} + \frac{1}{R_F} + \frac{1}{R_g} \right] = \frac{V_B}{R_g} + \frac{V_o}{R_F} + \frac{V_x}{R_o} \quad \dots \textcircled{2}$$

$\textcircled{1} - \textcircled{2}$

$$\Rightarrow (V_B - V_A) \left(\frac{1}{R_o} + \frac{1}{R_F} + \frac{1}{R_g} \right) = \frac{V_A - V_B}{R_g} - \frac{V_o}{R_F} \quad \dots \textcircled{3}$$

$$\Rightarrow V_o = \left(1 + \frac{R_F}{R_o}\right) (V_A - V_B)$$

$$\therefore V_o = (V_A - V_B) \left[\frac{R_F}{R_o} + 1 + \frac{2R_F}{R_g} \right] \xrightarrow{\text{tune}}$$


$$\rightarrow CMRR_{2\text{opamp IA}} < CMRR_{3\text{opamp IA}}$$

\hookrightarrow lower cost

\hookrightarrow As 3opamp IA has spatial amplifiers to amplify difference v.

Now,
 $\frac{2R_F}{2R_o}$ } to be tuned.
 $+ 1R \rightarrow$ where?

Practical Uses: General X.

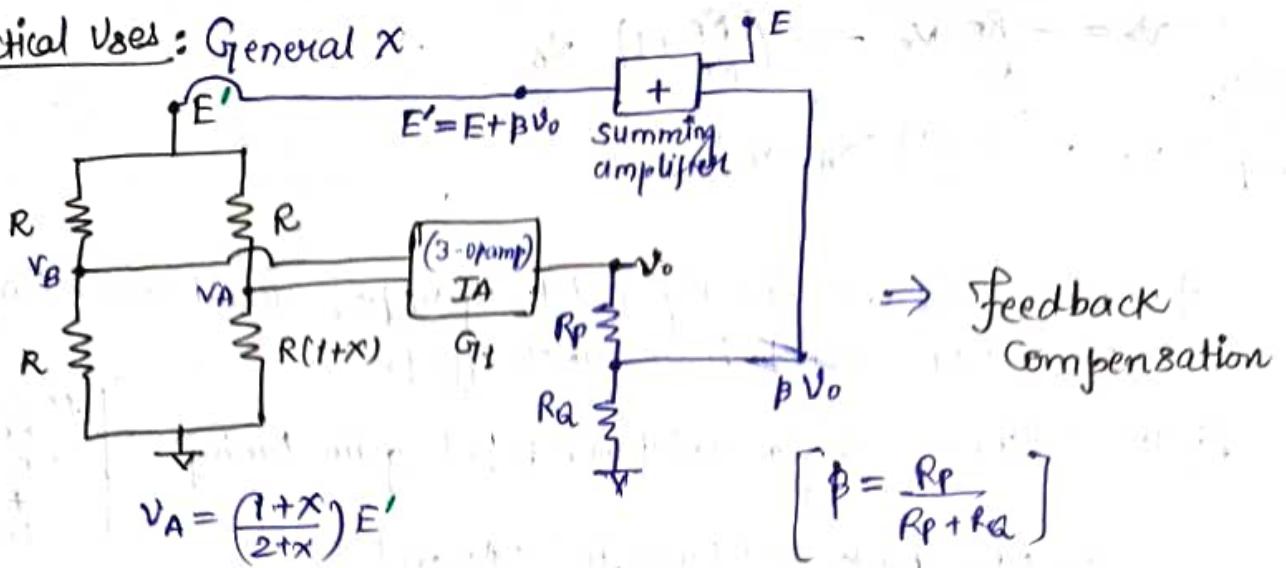

$$\therefore \text{Feedback Compensation}$$

$\Rightarrow V_0 = \frac{G_1 E X}{4+2x} \rightsquigarrow \text{non-linear relation b/w } V_0 \text{ & } x. \Rightarrow \text{Get a linear relationship}$

Adding a summing amplifier,

$$V_0 = \frac{G_1 (E + pV_0)x}{4+2x}$$

$$\Rightarrow (4+2x)V_0 - G_1 \beta x V_0 = G_1 EX$$


$$\Rightarrow V_0 = \frac{G_1 EX}{4+2x(2-G_1\beta)}$$

Take $G_1\beta = 2$. [G_1 and β value can be chosen accordingly.]

$$\therefore V_0 = \frac{G_1 EX}{4} : \text{linear relationship}$$


Application:

①

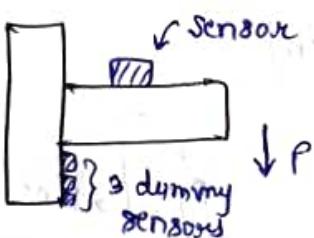


② ECG: Electro Cardio Graphy

To measure
ECG signal
in human body

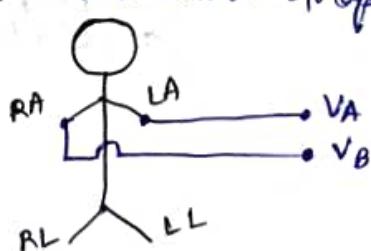

Put electrodes on the body (potential due to ions in body)
one electrode inside body
capacitive coupled
 V_A, V_B .

\rightarrow LA is farthest from RL.

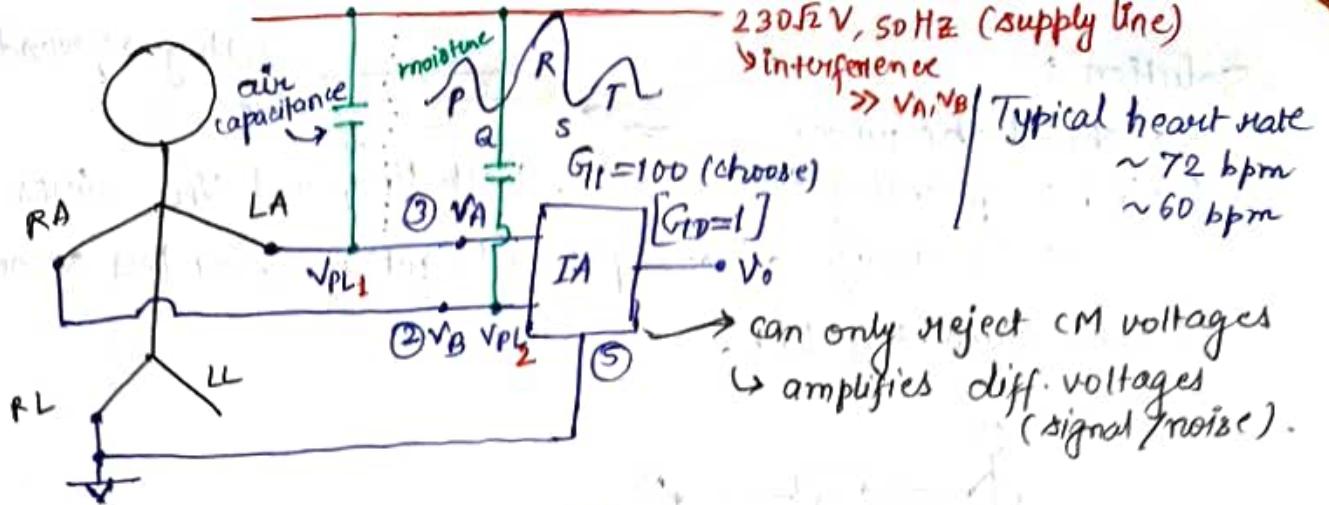

230.52 V, 50 Hz (Supply Line)

↳ Interference

↳ V_A, V_B

Typical heart rate

$\sim 72 \text{ bpm}$

$\sim 60 \text{ bpm}$

$$\begin{aligned} V_A - V_B &\approx 10 \mu\text{V} @ 1 \text{ Hz} \\ \frac{V_A + V_B}{2} &\approx 10 \mu\text{V} @ 1 \text{ Hz} \end{aligned} \quad \left. \begin{array}{l} \text{Typical} \\ \text{order} \end{array} \right\}$$

$$V_o = G_{ID} G_I (V_A - V_B) + G_{IC} \left(\frac{V_A + V_B}{2} \right) + 10^{-4} \times 10 \mu\text{V}$$

~~100V @ 1Hz~~

$$V_o = 1 \text{ mV} @ 1 \text{ Hz} + 10^{-4} \times 10 \mu\text{V}$$

inv @ 1Hz

Practical case:

Due to interference from power supply:

$$\begin{aligned} V_o &= G_{ID} G_I (V_A - V_B) + G_{IC} \left(\frac{V_A - V_B}{2} \right) + G_{IC} V_{PL} \\ &= 1 \text{ mV} + 10^{-4} \times 10 \mu\text{V} + G_{IC} V_{PL} \end{aligned}$$

~~GIC @ 50Hz~~

V_{PL} : induced power-line voltage
 $V_{PL} \approx 10 \text{ mV}$

$$= 1 \text{ mV} + \text{inv} + 1 \mu\text{V}$$

@ 1Hz @ 1Hz @ 50Hz

↳ $\ll 1 \text{ mV}$

Case : $V_{PL1} \neq V_{PL2}$

$$V_{PL1} \approx 10.5 \text{ mV}$$

$$V_{PL2} \approx 9.5 \text{ mV}$$

$$\begin{aligned} \therefore V_o &= G_{ID} G_I (V_A - V_B) + G_{IC} \left(\frac{V_A - V_B}{2} \right) + G_{ID} G_I (V_{PL1} - V_{PL2}) \\ &\quad + G_{IC} \left(\frac{V_{PL1} + V_{PL2}}{2} \right) \end{aligned}$$

amplified the difference (signal/noise)

$$= 1 \text{ mV} + \text{inv} + (100)(1 \text{ mV}) + 10^{-4} (10 \text{ mV})$$

$$= 1 \text{ mV} + \text{inv} + 100 \text{ mV} + 1 \mu\text{V}$$


@ 1Hz @ 1Hz @ 50Hz @ 50Hz

$\gg 1 \text{ mV}$

↳ Too much noise

Solution:

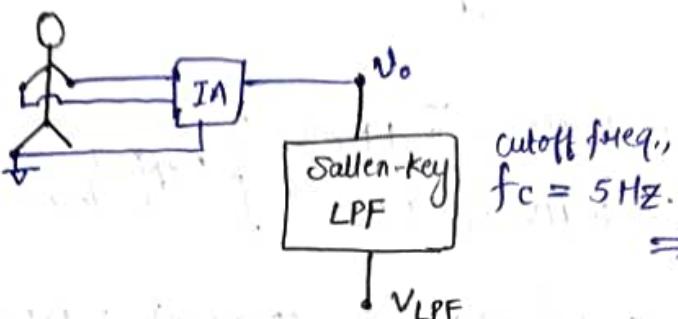- ↪ Shield the wires.
- ↪ (while pointing the circuit), Keep V_{PL_1} and V_{PL_2} wires in as proximity as possible [to get more or less same V_{PL_2}].
- ↪ Use Sallen-Key LPF.



⇒ To reject common mode voltage.

Book:


- Operational Amplifiers by George Clayton & Steve Winder

- Analog Signal Processing by Ramon Pallas-Areny John G. Webster

19-03-2023

Current-Output Instrumentation Amplifier:

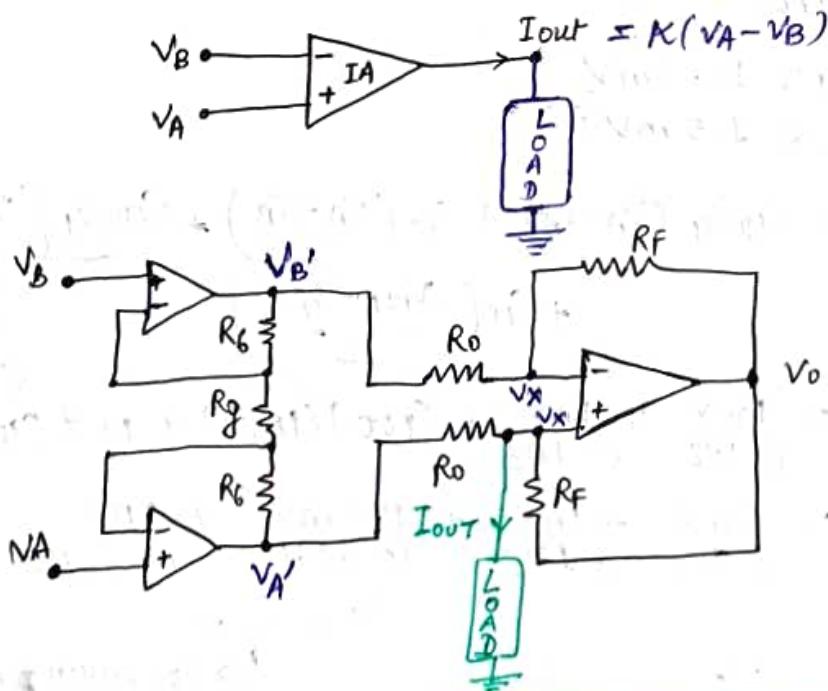For a load at remote location, voltage may get attenuated, so we would want output to be current.



KCL @ +ve terminal of DA:

$$V_x \left[\frac{1}{R_o} + \frac{1}{R_F} \right] + I_{OUT} = \frac{V_o}{R_F} + \frac{V_A'}{R_o} \quad \dots ①$$

KCL @ -ve terminal of DA:


$$V_x \left[\frac{1}{R_o} + \frac{1}{R_F} \right] = \frac{V_o}{R_F} + \frac{V_B'}{R_o} \quad \dots ②$$

① - ②

$$\Rightarrow I_{OUT} = \frac{V_A' - V_B'}{R_o}$$

$$\Rightarrow I_{OUT} = \frac{G_{T_1}(V_A - V_B)}{R_o}, \quad G_{T_1} + \frac{2R_G}{R_g}$$

↳ Doesn't depend on the load.

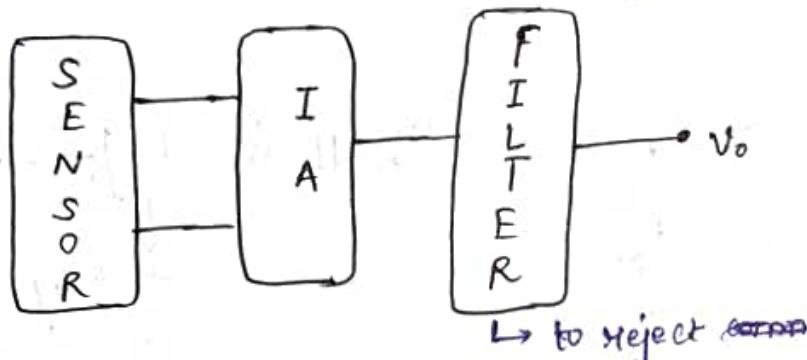

Heart-rate: 60 bpm to 120 bpm
(1Hz to 2Hz)

Interferences: ① Supply: 50 Hz [Powerline]


↳ Solution: LPF; $f_{cL} \approx 5 \text{ Hz}$

② Frequency component of motion artefacts and breathing rate (< 0.5 Hz)

↳ Solution: HPF; $f_{cH} \approx 0.5 \text{ Hz}$.

→ For powerline very-near to the instrument,
use band-reject filter [for further filtering]


LPF:

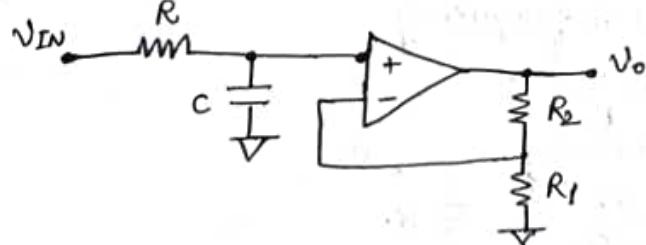

50 Hz


$$G = 1 + R_2/R_1$$
$$f_c = \frac{1}{2\pi R C}$$

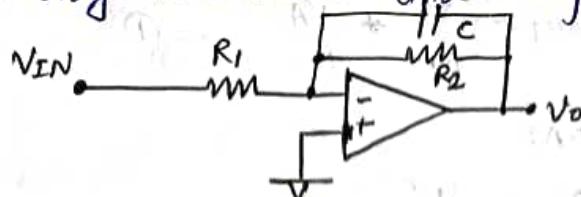Challenge: Use only 2 resistors and a capacitor for the LPF.




$$G = -R_2/R_1$$

$$f_c = \frac{1}{2\pi R_2 C}$$


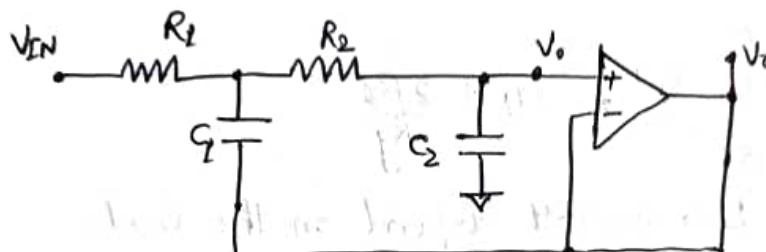


HPF:

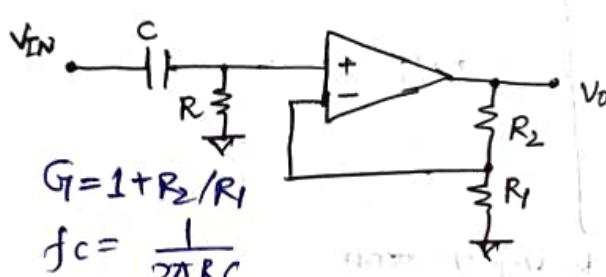

$$G = 1 + R_2/R_1$$


$$f_c = \frac{1}{2\pi R C}$$

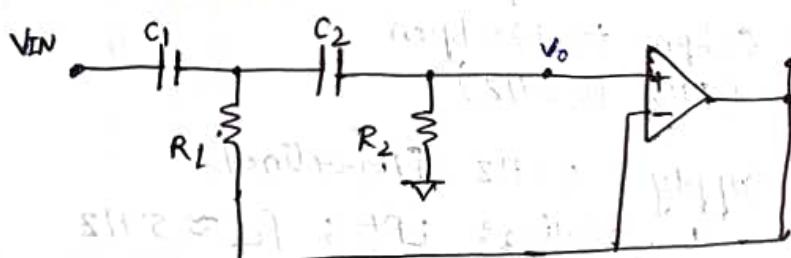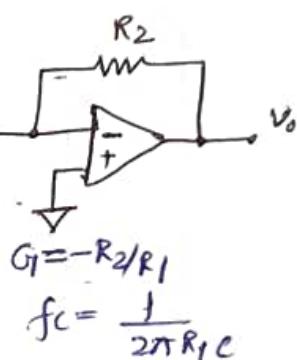

BPF:


↳ LPF + HPF

Band-Reject Filter (BRF):

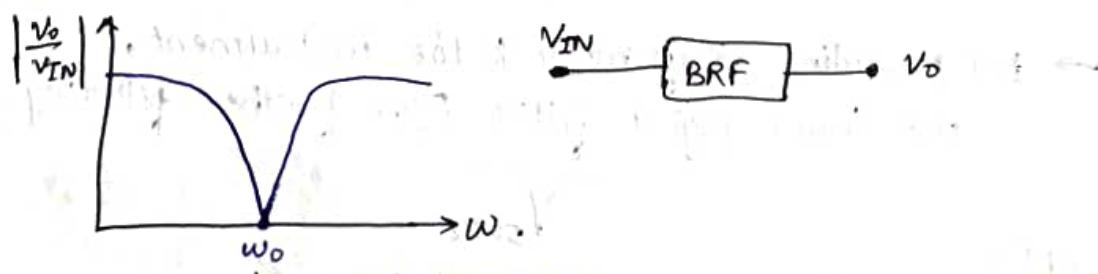

↳ notch frequency

Design BRF using R, L, C:

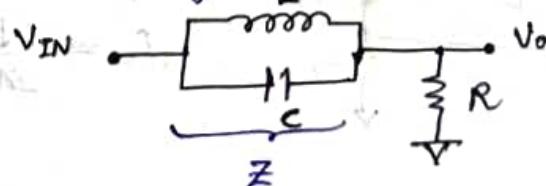

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow Z_{high} \rightarrow V_o = 0$$

$(Z_L \parallel Z_C)$

$$\omega \neq \omega_0 \rightarrow Z_{low} \rightarrow V_o = V_{IN}$$

Analysis:

$$Z = j\omega L \parallel \frac{1}{j\omega C} = \frac{\frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{\frac{1}{j\omega C} (j\omega C)}{-\omega^2 L/C + 1}$$

$$= \frac{j\omega L}{1 - \omega^2 \frac{L}{C}}$$

$$\frac{V_o}{V_{IN}} = \frac{R}{R + Z}$$

$$= \frac{(j\omega)^2 + \frac{1}{L^2 C^2}}{(j\omega)^2 + \frac{j\omega}{RC} + \frac{1}{L^2 C^2}}$$

ω	$ V_o/V_{IN} $
0	1
∞	1
$\omega_0 = \frac{1}{\sqrt{LC}}$	0

Issue: There is a need of inductor which is bulky and costly, and difficult to miniaturize.

$$\frac{V_o}{V_{IN}} = \frac{(j\omega)^2 + \omega_0^2}{(j\omega)^2 + 2\xi\omega_0 j + \omega_0^2}$$


$$\left[\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{LC} = \omega_0^2 \right]$$

$$\left[\xi_{RC} = 2\xi \omega_0 \text{ (say)} \right]$$

For BRF, we don't use ξ , instead we use

Quality factor, $Q = \frac{1}{2\xi}$ \rightarrow more intuitive parameter.
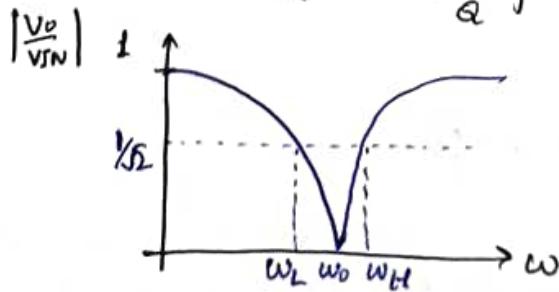
$$\therefore \frac{V_o}{V_{IN}} = \frac{(j\omega)^2 + \omega_0^2}{(j\omega)^2 + \frac{\omega_0^2}{Q} j + \omega_0^2}$$



Bandwidth (BW) :

$$BW = \omega_H - \omega_L \rightarrow \text{rejection BW}$$

BW $\downarrow \Rightarrow$ Specificity \uparrow , Performance \uparrow

To get BW from the equation:

At $\omega = \omega_L, \omega_H$

$$\left| \frac{V_o}{V_{IN}} \right| = \frac{1}{\sqrt{2}} \Rightarrow \text{Get 2 solutions } \omega_L, \omega_H.$$

$$BW = \frac{\omega_0}{Q}$$


$Q \uparrow \Rightarrow BW \downarrow \Rightarrow$ Better the BRF.

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{\omega_0}{Q} = \frac{1}{RC}$$

$$\Rightarrow Q = R \sqrt{\frac{C}{L}}$$

By choosing appropriate values of C and L, we can get good Q.

Inductor-free BRF: (Twin-T notch filter)

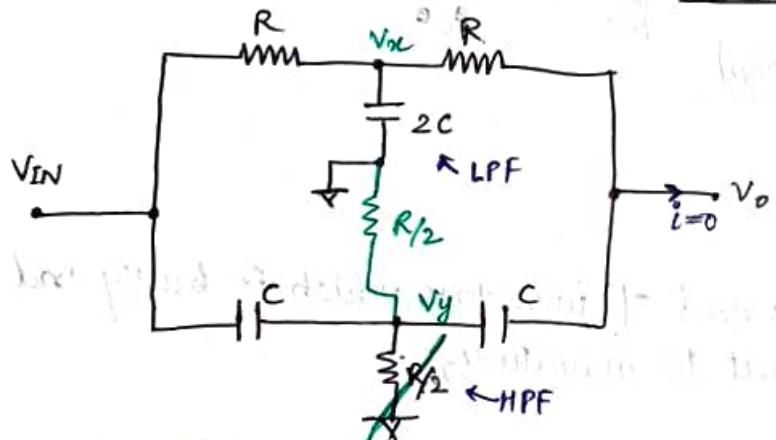

[Adding extra R & C after 2 filters give better band-reject performance by coupling them]

KCL @ V_x :

$$V_x \left[\frac{1}{R} + j\omega 2C \right] = \frac{V_{IN}}{R} + \frac{V_o}{R}$$

$$\Rightarrow 2V_x [1 + j\omega RC] = V_{IN} + V_o \dots \textcircled{1}$$

KCL @ V_y :

$$V_y \left[\frac{1}{R/2} + j\omega 2C \right] = (V_{IN} + V_o) j\omega C$$

$$\Rightarrow 2V_y [1 + j\omega RC] = (V_{IN} + V_o) j\omega C \dots \textcircled{2}$$

$$\textcircled{1}/\textcircled{2} \Rightarrow \frac{V_x}{V_y} = \frac{1}{j\omega CR}$$

$$\Rightarrow V_y = (j\omega CR) V_x \dots \textcircled{3}$$

KCL @ V_o :

$$\frac{V_o}{R} + V_o j\omega C = \frac{V_x}{R} + V_y j\omega C$$

$$\Rightarrow V_o [1 + j\omega CR] = V_x + V_y j\omega CR \quad \dots ④$$

$$③ \text{ and } ④ \Rightarrow V_o [1 + j\omega CR] = V_x + j\omega^2 C^2 R^2$$

$$\Rightarrow V_x = \frac{V_o [1 + j\omega CR]}{1 + (j\omega CR)^2} \quad \dots ⑤$$

$$① \text{ and } ⑤ \Rightarrow 2 \frac{V_o [1 + j\omega CR]}{1 + (j\omega CR)^2} \cdot [1 + j\omega CR] = V_{IN} + V_o$$

$$\Rightarrow 2 \frac{V_o}{V_{IN}} \frac{(1 + j\omega CR)^2}{1 + (j\omega CR)^2} = 1 + \frac{V_o}{V_{IN}}$$

$$\Rightarrow \frac{V_o}{V_{IN}} \left[2 \frac{\frac{1}{R^2 C^2} + (j\omega)^2 + \frac{2j\omega}{RC}}{\frac{1}{R^2 C^2} + (j\omega)^2} - 1 \right] = 1 \quad \rightarrow$$

$$\Rightarrow \frac{V_o}{V_{IN}} = \frac{(j\omega)^2 + \frac{1}{R^2 C^2}}{(j\omega)^2 + 4 \frac{j\omega}{RC} + \frac{1}{R^2 C^2}} \quad \dots ⑥$$

$$\omega_0 = \frac{1}{RC}$$

$$\frac{4}{RC} = \frac{\omega_0}{Q} \Rightarrow Q = \frac{1}{4} : \text{fixed low}$$


Twin-T Active Notch Filter:

Objective: Improve the value of Q , so that ξ_q is lowered.
(of circuit)

-ve feedback is dominating the +ve feedback
(to prevent oscillation)

$$Q = \frac{1}{2\xi_q}$$

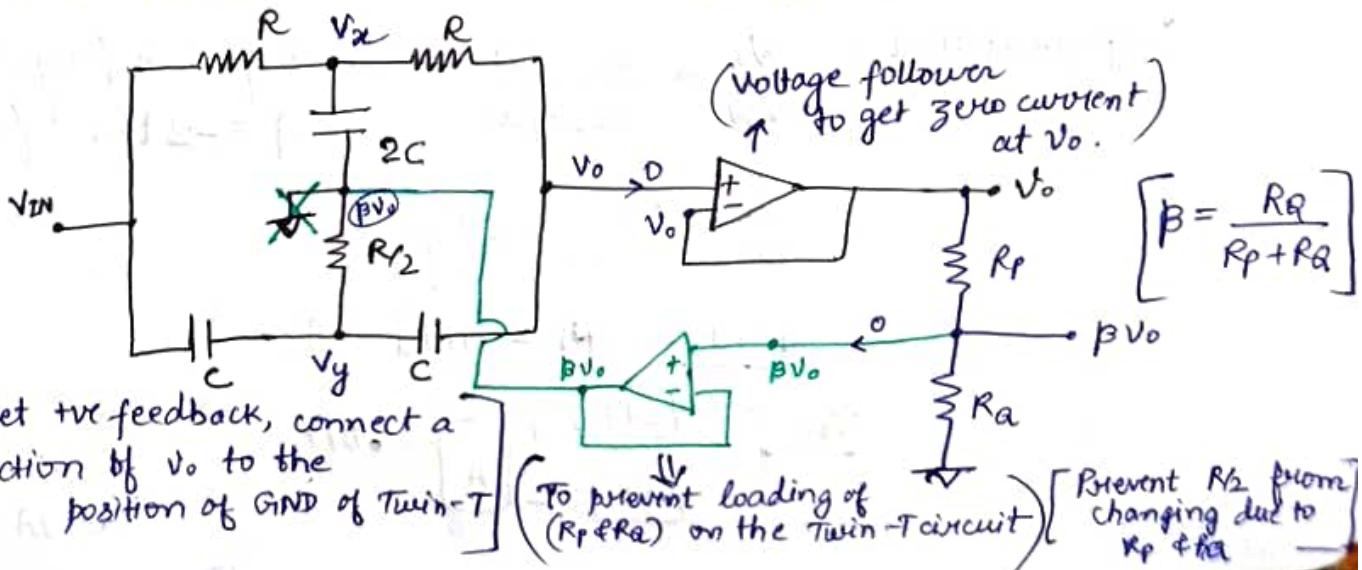$Q \uparrow \Rightarrow \xi_q \downarrow \Rightarrow$ Being some positive feedback in the circuit.



Using KCL at V_x, V_y, V_o ,

$$\frac{V_o}{V_{IN}} = \frac{(j\omega)^2 + \frac{1}{R^2 C^2}}{(j\omega)^2 + \frac{4(1-\beta)}{RC} j\omega + \frac{1}{R^2 C^2}}$$


$$\therefore \omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{4(1-\beta)} : \text{Variable } Q$$

To get $Q=10$,

$$\beta = \frac{39}{40} = \frac{R_Q}{R_P + R_Q} : \text{choose } R_P \text{ & } R_Q \text{ accordingly.}$$

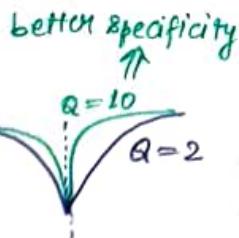→ Negative feedback $>$ Positive feedback : Undamped Response



All-Pass Filter (APF)



$$\left| \frac{V_o}{V_{IN}} \right| = 1$$



$$\phi = \angle \frac{V_o}{V_{IN}}$$

↳ There is a finite value of ϕ (phase). [Used to give phase delay without changing amplitude]

↳ Application :

- time-delay


- synchronization

Implementation : $\frac{V_o}{V_{IN}} = \frac{\omega_0 - j\omega}{\omega_0 + j\omega} \rightarrow \text{obeys both properties}$

$$\phi = -2 \tan^{-1} \left(\frac{\omega}{\omega_0} \right)$$

$$\frac{V_o}{V_{IN}} = \left(\frac{\omega_0}{\omega_0 + j\omega} \right) \frac{(j\omega)}{\omega_0 + j\omega}$$

$$\therefore APF = LPF - HPF \dots ①$$

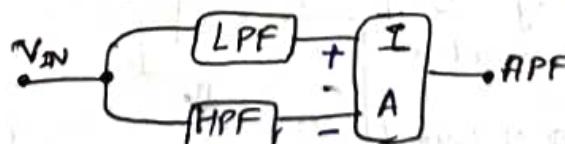

⇒ Issue: Requires 2 filters and an IA.


$$\text{Also, } \text{LPF} + \text{HPF} = 1 \\ \Rightarrow \text{HPF} = 1 - \text{LPF} \dots \textcircled{2} \quad \left[\therefore \frac{\omega_0}{\omega_0 + j\omega} + \frac{j\omega}{\omega_0 + j\omega} = 1 \right]$$

$\textcircled{1}$ and $\textcircled{2}$

$$\Rightarrow \frac{V_o}{V_{IN}} = A_{PF} = 2\text{LPF} - 1$$


$$\Rightarrow V_o = 2\text{LPF}(V_{IN}) - V_{IN}, \dots \textcircled{3}$$

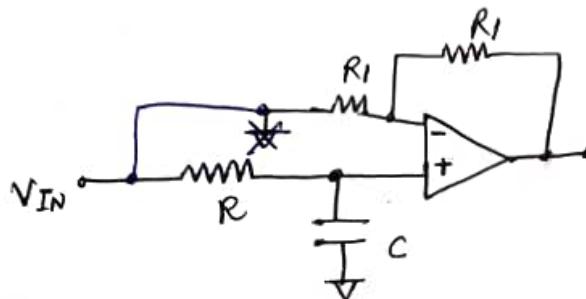\hookrightarrow low-pass-filtered version of V_{IN} amplified by 2 times.



Ques. Generate a stable-controlled magnetic field at the point P.
[Permanent magnet is not ~~possible~~ feasible.]

Solution: V_{8e}

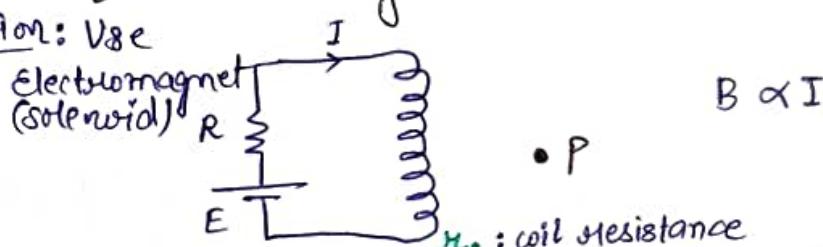

$\bullet P$

μ_c : coil resistance

\hookrightarrow depends on operating temperature and conditions.

$$\text{Ideal: } I = \frac{E}{R}$$

$$\text{Practical: } I = \frac{E}{R + \mu_c} \bullet$$

\hookrightarrow Issue: Becomes uncontrollable due to μ_c .

Solution: $R \gg \mu_c$

$$\therefore I \approx \frac{E}{R}$$

$$\text{For } I = 50\text{mA}, \mu_c = 50\Omega$$

$$R = 100\mu_c = 5\text{k}\Omega \text{ (say)}$$


Issue: $E = IR = 250\text{V}$ (Requires ~~too~~ high E)

Solution: Use current-source.

26-03-2024



Current-Source Circuit

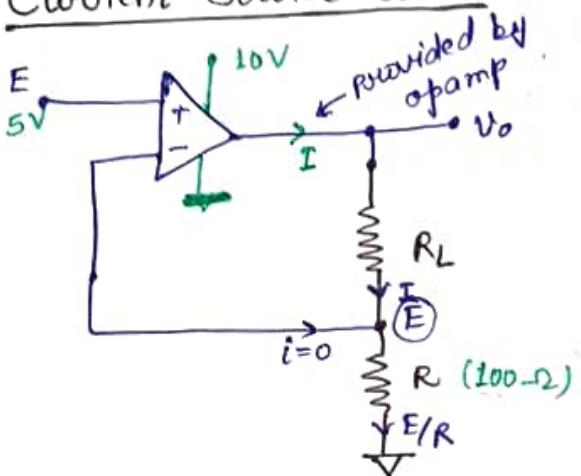

$$I = \frac{E}{R} \quad (\text{provided circuit above forms a closed-path})$$

R_L : Load resistance
(e.g., electromagnet)

R : Extra resistance

To get voltage E with zero current,
connect opamp's input to E point.

To get $I = 50\text{mA}$,

$$\begin{aligned} E &= 5\text{V} \\ R &= 100\text{-}\Omega \end{aligned} \quad \left. \begin{array}{l} \text{Readily available} \\ \text{values.} \end{array} \right.$$


Opamp's output :

$$V_o = \left(1 + \frac{R_L}{R}\right) E$$

$$R_L \in (40, 60)\text{-}\Omega$$

R_L	V_o
50	7.5
40	7
60	8

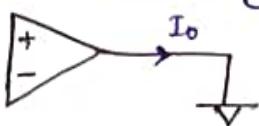Opamp-specification dealing with opamp's output current :




short-circuit
output current

I_o will be maximum when
output is grounded
without any load.

OP07 } $\frac{(I_o)_{\max}}{< 25\text{mA}}$
LM741 }

Issue: We need $I_o = 50mA$, but opamp can only provide $25mA$.
(or sink)

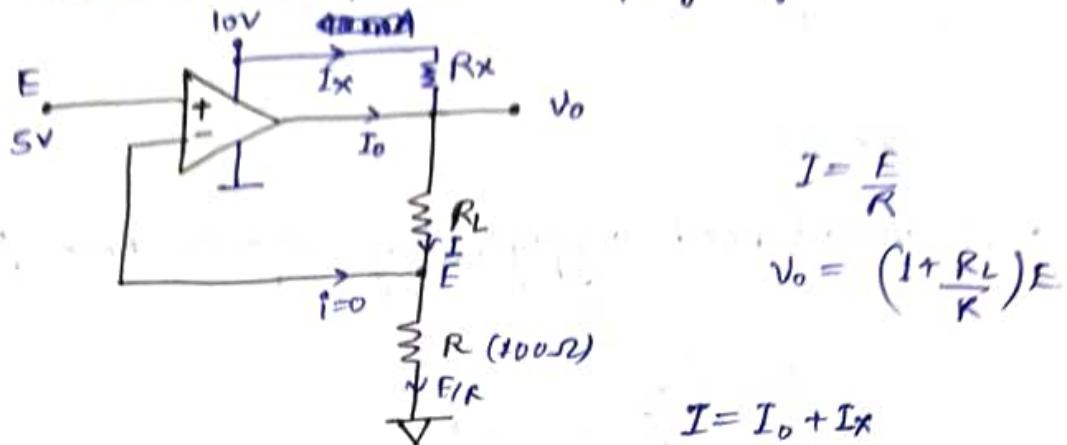Solution: Draw current from the supply of 10V.




R_L	V_o	I_o	I_x
50	7.5	0	50 mA
40	7	-10mA	60 mA
60	8	10mA	40 mA

$$R_L = 50 \Omega, V_o = 7.5 \therefore R_x = \frac{10 - 7.5}{50 \text{ mA}} = 50 \Omega \quad (\because I_x = 50 \text{ mA})$$

Issue: Both ends of load are at finite voltages.

Floating loads:

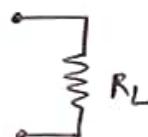

Grounded loads:




(use grounded load when safety is involved.)

Solution:

Howland '8

Current source:

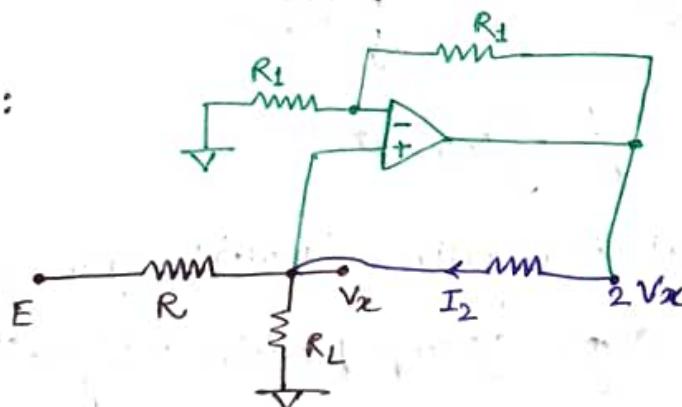

$$I = \frac{E}{R}$$

$$I = \underbrace{\frac{E - V_x}{R}}_{I_1} + \underbrace{\frac{2V_x - V_x}{R}}_{I_2} = \frac{E}{R}$$

$I_2 = V_x / R$
To cancel extra $(-V_x / R)$.

$$I = \frac{E}{R} = \frac{5V}{100\Omega}$$

$$I = 50mA$$

$$R_L = 60\Omega$$


$$V_x = IR_L$$

$$= 3V$$

$$2V_x = 6V$$

Issue: We would need supply voltage of $> 6V$ (here) for proper operation.


Solution:

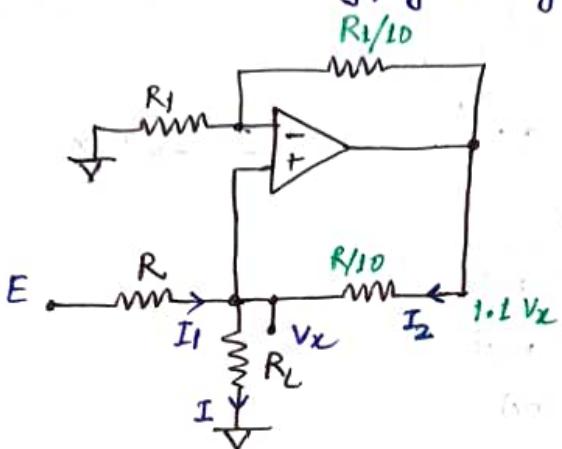

$$I = \underbrace{\frac{E - V_x}{R}}_{I_1} + \underbrace{\frac{1.1 V_x - V_x}{R/10}}_{I_2} = \frac{E}{R}$$

$$1.1 V_x = 3.3V < 5V$$

Integrator

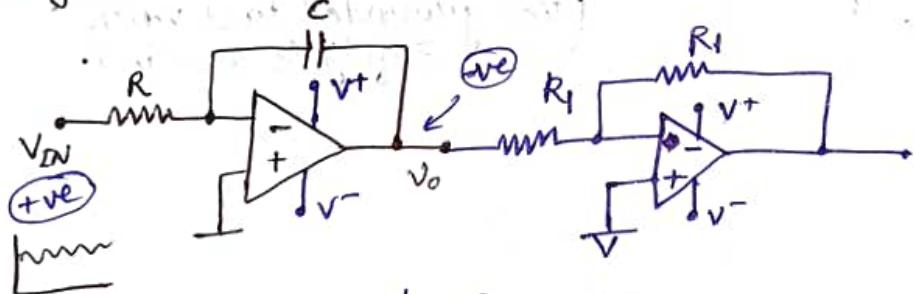


$$V_0 = -\frac{1}{RC} \int V_{IN} dt$$

Issue: Output is negative. [Multiple opamps are not feasible.]

Solution:

Get single opamp positive integrator.

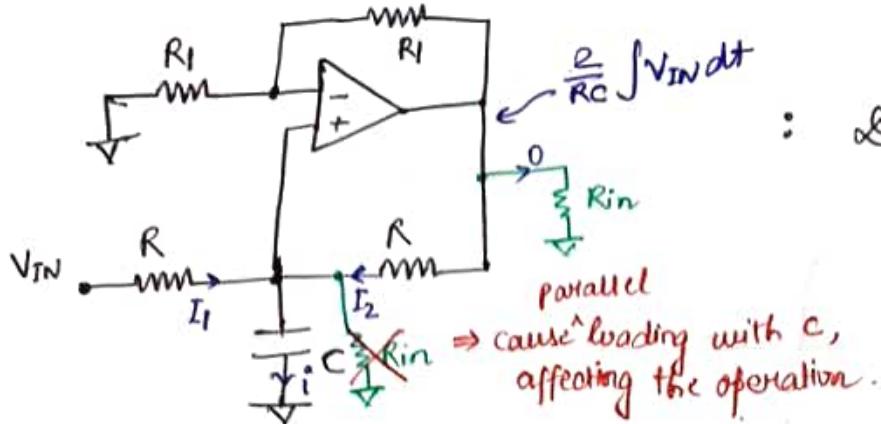


: Deboo's Integrator
 = Howland's Integrator
 (when used as current source)

$$i = \frac{V_{IN}}{R} \quad (= \frac{V_{IN}-V_x}{R} + \frac{2V_x-V_x}{R})$$



$$\therefore V_x = \frac{1}{C} \int i dt = \frac{1}{RC} \int V_{IN} dt$$

27-03-2024



Measure Peak of Signal

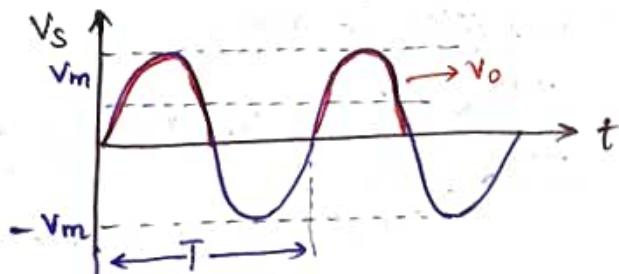

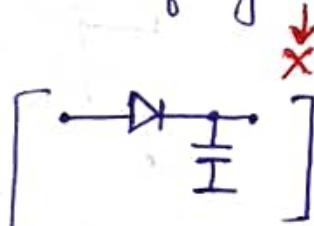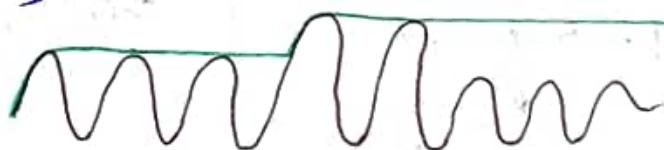→ can only measure the highest value of signal.




Solution:

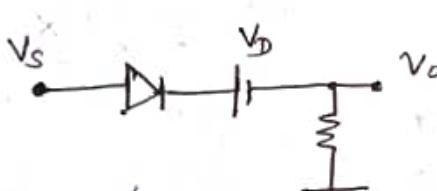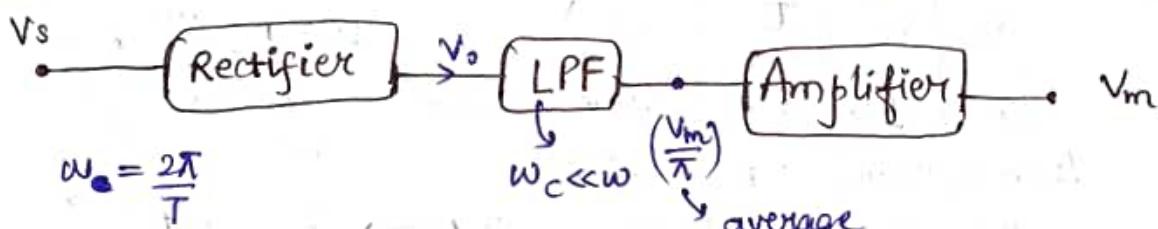

$$V_o = \begin{cases} V_{IN}, & V_{IN} > 0 \\ 0, & V_{IN} \leq 0 \end{cases}$$

$$V_o = \begin{cases} V_{IN} - V_D, & V_{IN} > V_D \\ 0, & \text{elsewhere.} \end{cases}$$

Suppose $V_m = 5V$
 $V_D = 0.7V$.

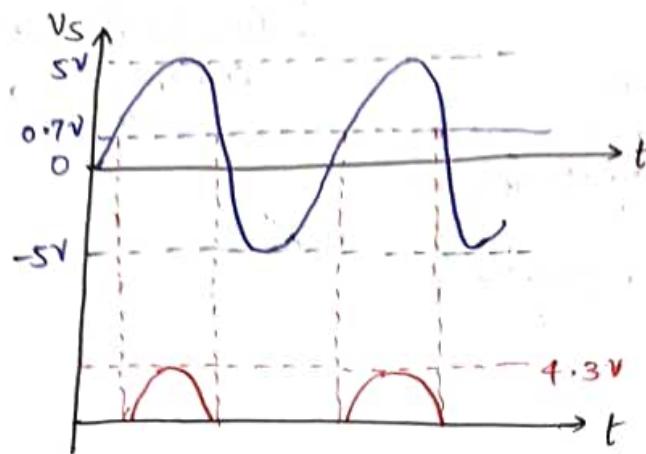

Suppose $V_m = 50mV \rightarrow$ Instrument won't even detect the signal.
 $V_D = 0.7V$


Possible solution : ~~use~~ use amplifier. $\rightarrow X$.

$$0^\circ C \rightarrow V_m = 50mV \xrightarrow{\times 100} 5V \quad \left. \begin{array}{l} \\ \end{array} \right\} V_m \text{ can be } \cancel{\text{anything}} \text{ anything.}$$

$$100^\circ C \rightarrow V_m = 500mV \xrightarrow{\times 100} 50V \quad \begin{array}{l} \\ \end{array}$$


$\rightarrow 50V$ is unhandable.

Precision Rectifier

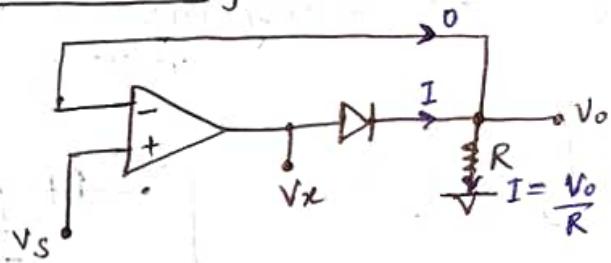

[No fundamental laws should get violated while designing.]

V_S	V_O	D	V_X
1V	1V	F.B.	1.7V
100mV	100mV	F.B.	0.8V
-1V	0	R.B.	$0V - (-10V) \rightarrow$ (saturates)

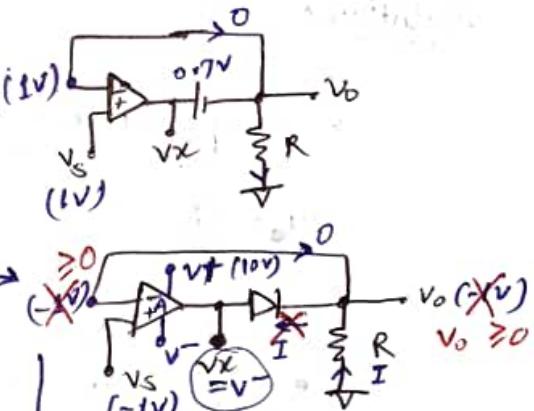

↪ The circuit is independent of cutting voltage of diode.

$$\therefore V_O = \begin{cases} V_S & V_S > 0 \\ 0 & V_S < 0 \end{cases}$$

↪ True Rectifier.


Diode won't allow $I (C \rightarrow A)$.
 \downarrow

I across R would be either \uparrow or 0 .

$$\boxed{V_O \geq 0}$$

$$V_X = A(V_1 - V_2) \rightarrow \text{very large value}$$

(saturates to V_{DD})

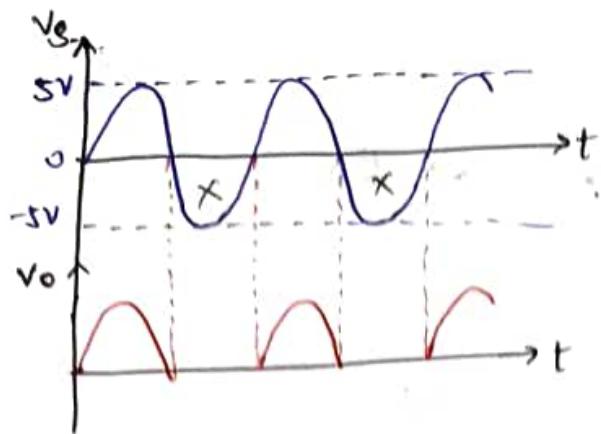


V_s	V_o	D	V_x
> 0	V_s	F.B.	$V_o + V_D$
< 0	0	R.B.	$V^- (= -V_{CC})$

$$V_o \geq 0 \rightarrow F.B.$$

$\Rightarrow V_x \geq V_D \uparrow$

Effect of A (Open Loop Gain):

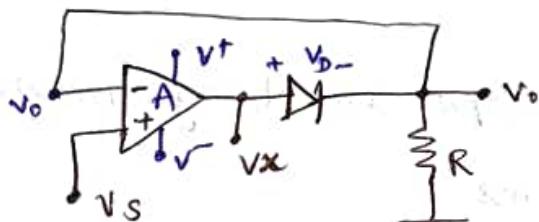

$$V_x = A(V_s - V_o)$$

$$F.B.: V_x = V_o + V_D$$


$$\Rightarrow V_o = \frac{A V_s}{A+1} - \frac{V_D}{A+1} \geq 0 \quad (\text{for F.B.})$$

$$A \gg 1 \Rightarrow V_o \approx V_s$$


$$\Rightarrow V_s \geq \left(\frac{V_D}{A} \right) \rightarrow \text{effective cutting voltage}$$

$$\left\{ \begin{array}{l} V_D = 0.7V \\ A = 10^6 \end{array} \right.$$

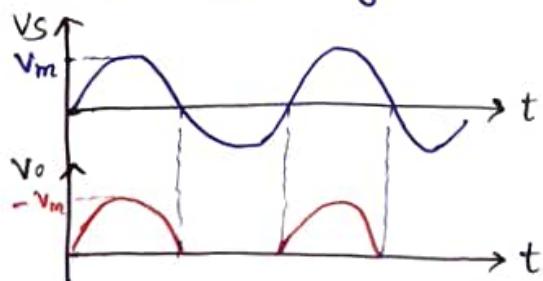\therefore Cutting voltage is reduced from $0.7V$ to $0.7 \mu V$.



Effect of Slew-Rate:

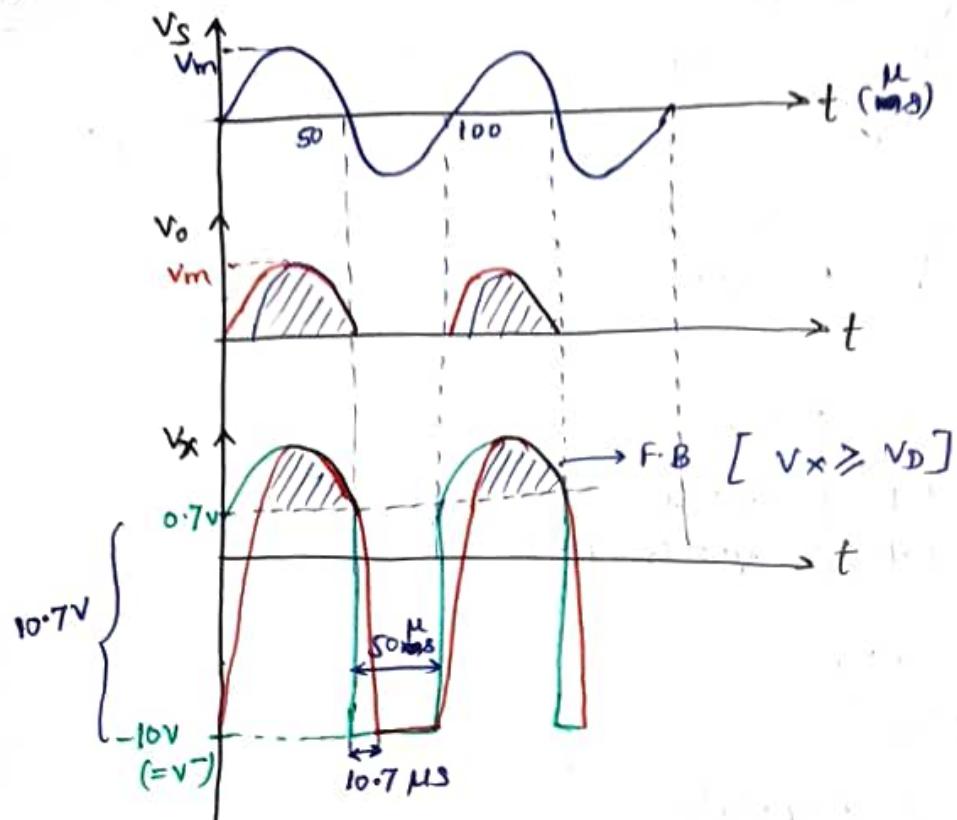

$$SR = 1 \text{ V/}\mu\text{s}$$

\Rightarrow In $1 \mu\text{s}$, opamp output can change maximum by 1V .


$$f = 10 \text{ kHz}, \frac{T}{2} = 50 \text{ }\mu\text{s}$$

$$10.7 \mu\text{s} \leftrightarrow 10.7 \text{V}$$

\rightarrow The precision rectifier works for low frequency signal.

1-04-2024

Precision Rectifier

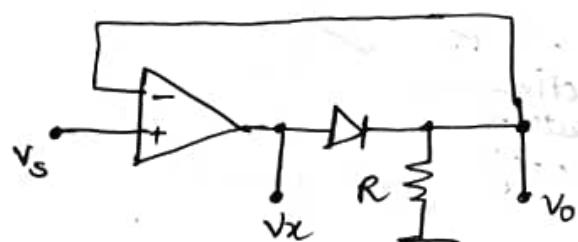


\hookrightarrow Low frequency operation

\hookrightarrow Sharp-transition at v_x .

(10.7V).

Improved Precision Rectifier

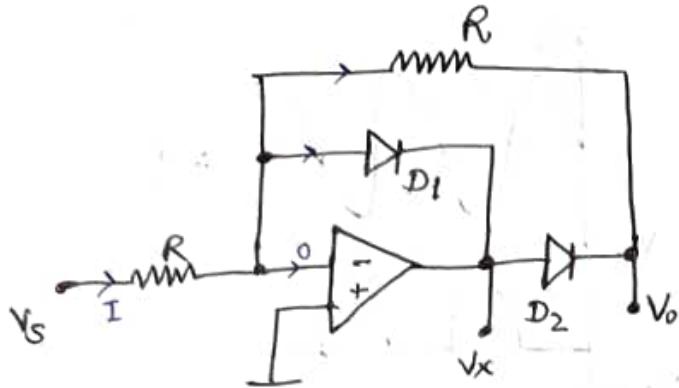

→ Precision Half Wave Rectifier


↳ works even for high frequencies.

$R \gg R_{ON}$
~ $k\Omega$ (diode)


D_2 : helps get half wave rectification

D_1 : helps reduce slew rate

V_s	D_1	D_2	V_o	V_x
> 0	F.B	R.B	0	-0.7 V
< 0	R.B	F.B	$-V_s$	$V_o + 0.7\text{ V}$

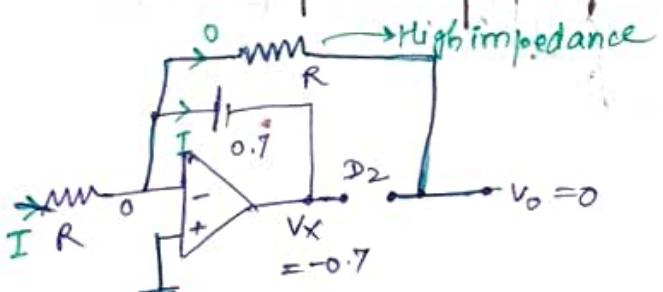

$$I = + \frac{V_s}{R}$$

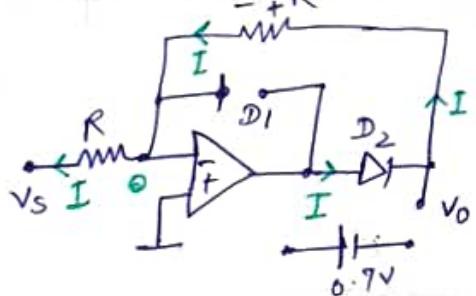


$$I = - \frac{V_s}{R}$$

$$V_o = +IR$$

$$I = - \frac{V_s}{R}$$



$$\therefore V_o = -V_s$$

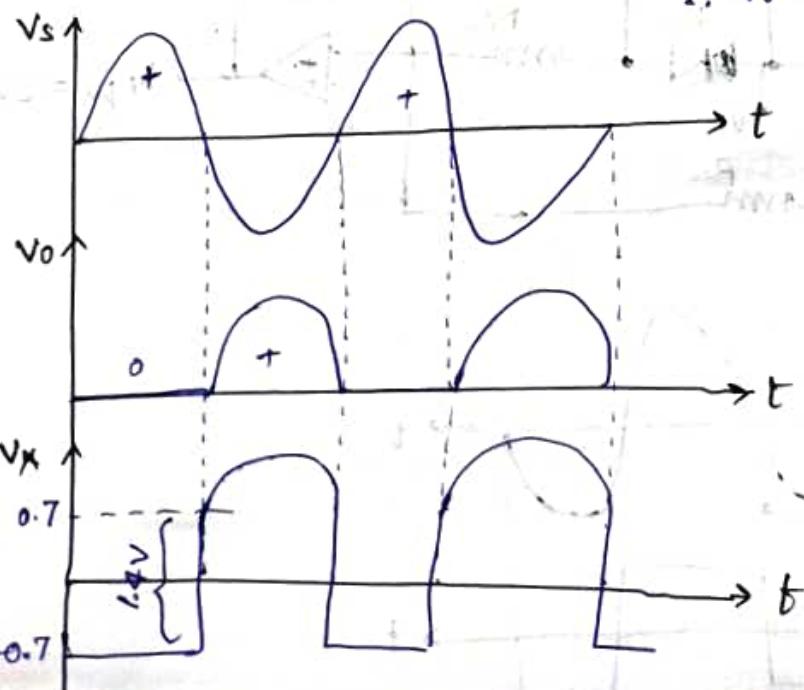

$$\Rightarrow \text{slew rate} = 1.4$$

Precision Full Wave Rectifier



$$V_{FW} = V_s + 2V_o$$

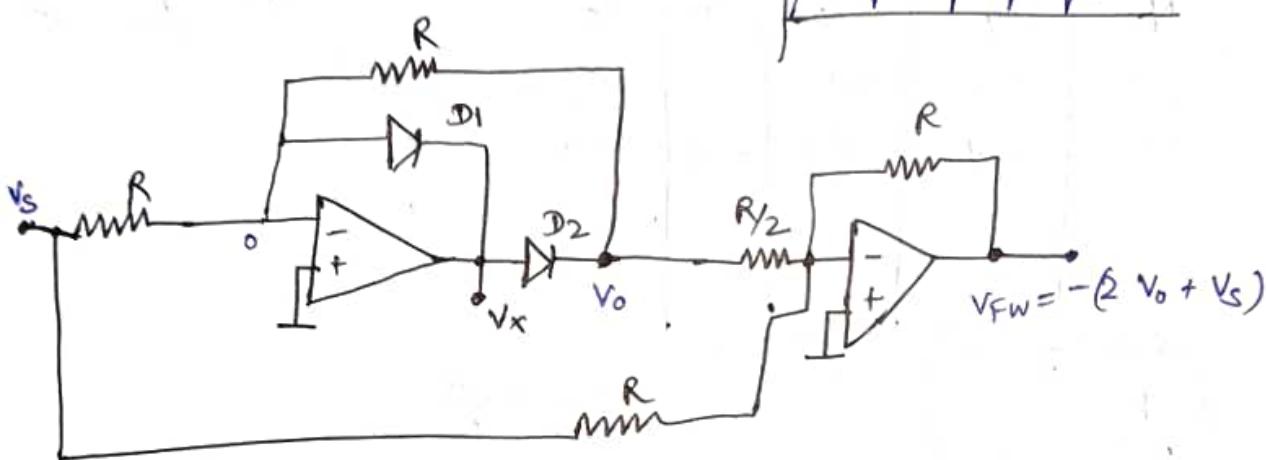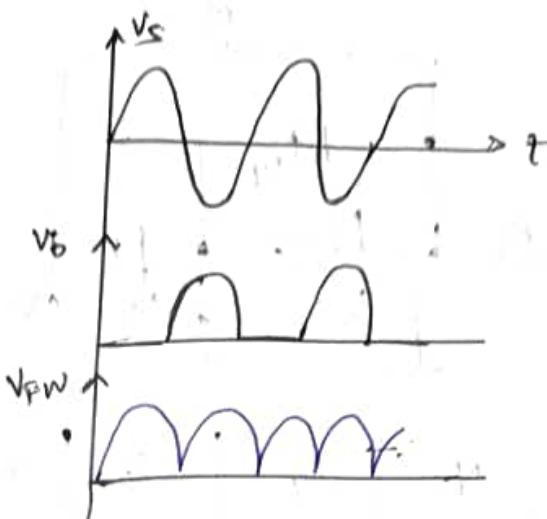

→ Get non-inverted V_{FW} .


[we can't use non-inverting amplifier as it would require
4 resistor components.]

Solution: Invert D_1 and D_2 .

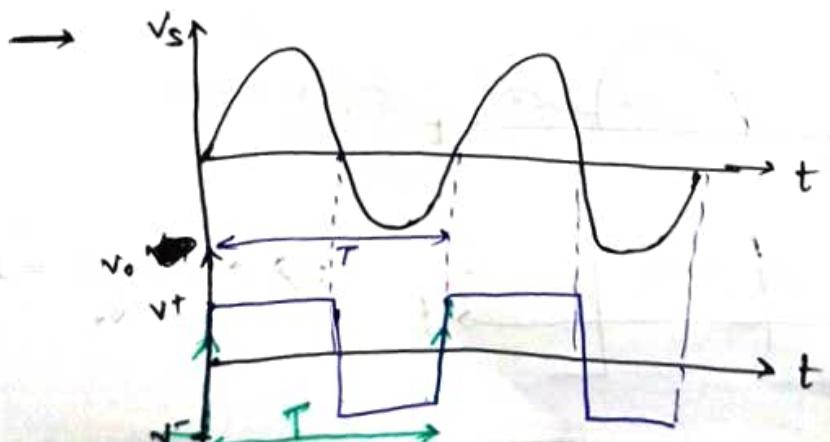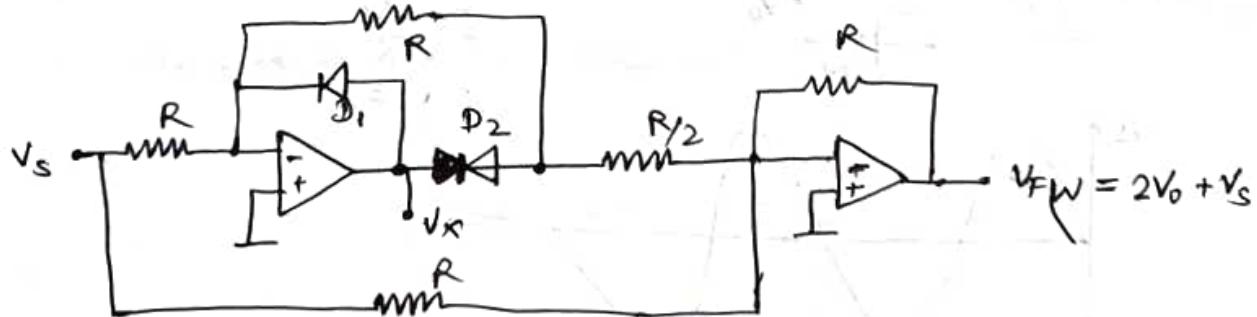

Measure the time period T of the sine signal.

Solution: Convert the signal to pulse.


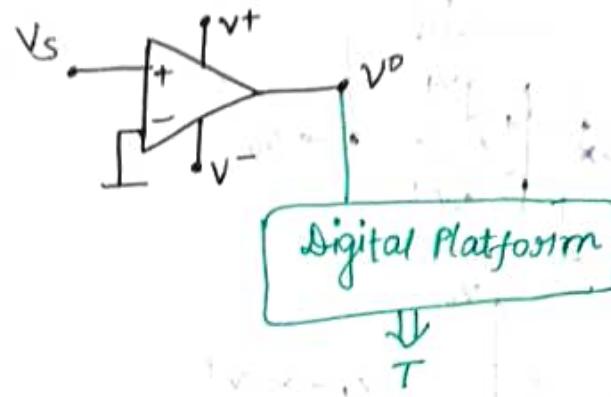


Then, use a digital platform (like microcontroller) to measure the time-difference between two rising pulse.

Issue: There may be noise to V_s which can unnecessarily invert the pulse V_d .

Solution: Use Schmidt Trigger.


2-04-2024

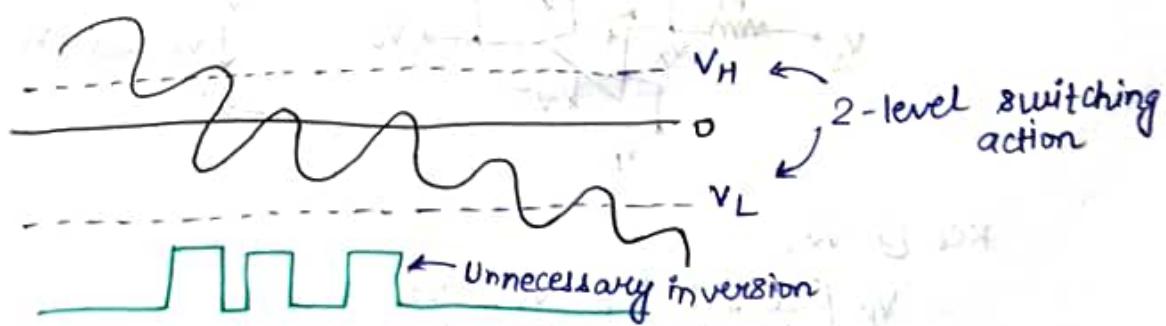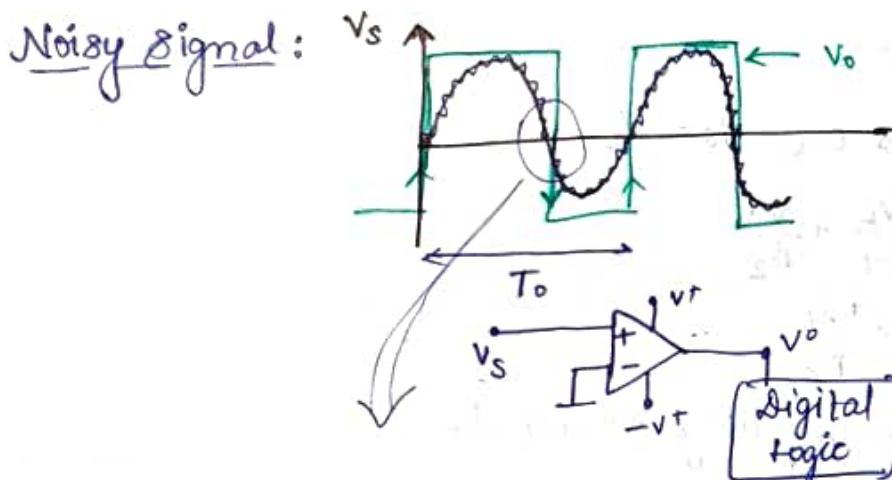

Using 2-level switching action
(Schmidt Trigger)


$$V_S < V_L \Rightarrow V^+ \xrightarrow{V_o} -V^+$$
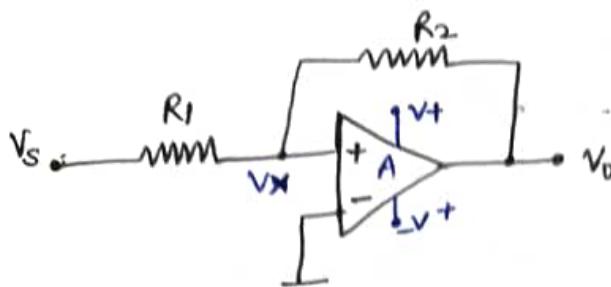
$$V_S > V_H \Rightarrow -V^+ \xrightarrow{V_o} V^+$$



$$V_o = A V_x$$
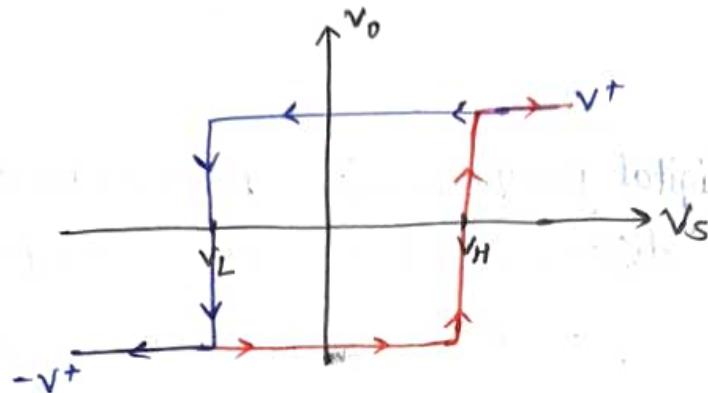
$$\begin{matrix} V^+ & \downarrow & 0^+ \\ \downarrow & & \downarrow \\ V^- & & 0^- \end{matrix}$$



$$|V_L| = V_H$$

KCL @ V_x ,

$$V_x \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_S}{R_1} + \frac{V_o}{R_2}$$

$$V_o = V^+$$


V_x crosses 0 @ $V_S = V_L$.

$$0 = \frac{V_L}{R_1} + \frac{V^+}{R_2}$$

$$V_L = -\frac{V^+ R_1}{R_2}$$

Now, apply V_K to inverting terminal.

($V_K = 1V$, say)

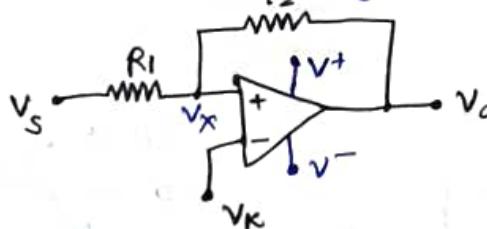

$$\begin{matrix} V^+ & \downarrow & V_K^+ (1.01) \\ \downarrow & & \downarrow \\ V_o & \rightarrow & V_x \\ \downarrow & & \downarrow \\ -V^+ & & V_K^- (0.99) \end{matrix}$$

KCL @ V_x ,

$$V_K \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_S}{R_1} + \frac{V_o}{R_2}$$

$$V_o = V^+$$

V_x crosses V_K @ $V_S = V_L$


$$|V_L| \neq V_H$$

↳ Asymmetrical
Schmidt
Trigger.

$$V_L = -\frac{V^+ R_1}{R_2} + V_K \left(1 + \frac{R_1}{R_2} \right)$$

$$V_H = \frac{V^+ R_1}{R_2} + V_K \left(1 + \frac{R_1}{R_2} \right)$$

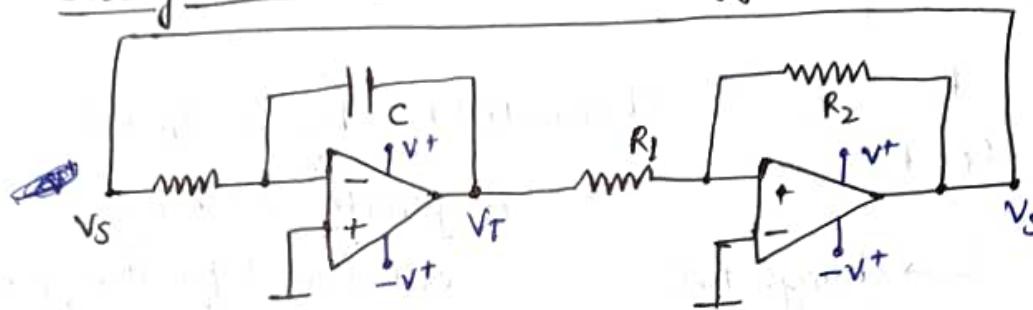→ Integrator with Schmidt-Trigger: [Triangular and square wave generator]




→ Function generator
↓ generates square and triangular waves

→ Capacitor (C) is having some residual voltage, V_{INIT} (initial voltage).

↳ Initial value of V_T :

$$V_T = V_{INIT} - \frac{1}{RC} \int_{V^+}^{V_T} V_S dt \quad | \quad V_L = -V^+ \frac{R_1}{R_2}; V_H = V^+ \frac{R_1}{R_2}$$

$$V_T = V_{INIT} - \frac{1}{RC} V^+ t$$

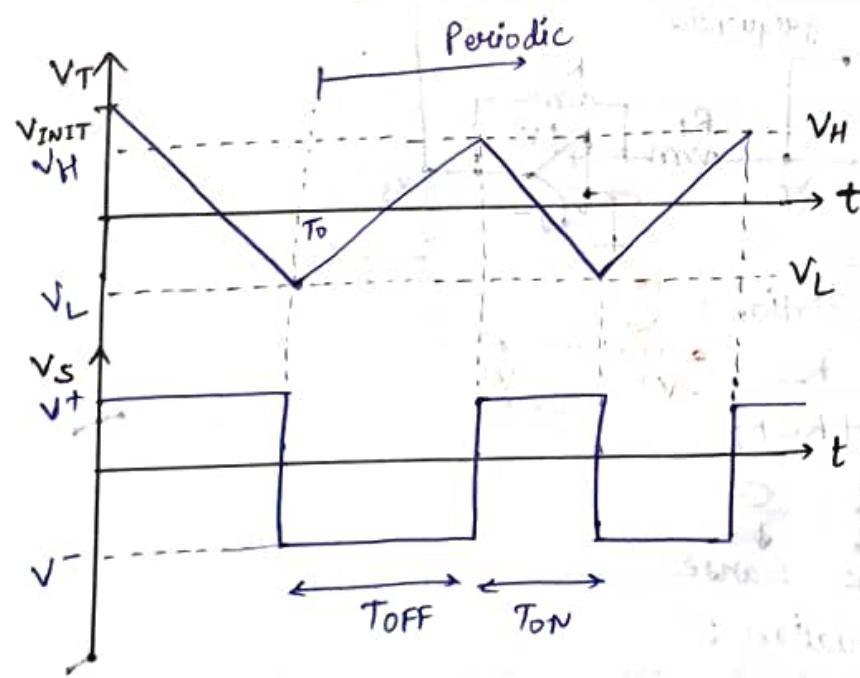

$$T = T_{ON} + T_{OFF}$$

$$f = \frac{1}{T}$$

$$V_T(T_0) = V_L$$

$$V_T = V_L + \frac{V^+}{RC} (t - T_0)$$

$$\left[V_T = V_L + \frac{1}{RC} \int_{T_0}^t V^+ dt \right]$$

~~$$T_{OFF} = (V_H - V_L) / R_C$$~~

$$V_T (T_0 + T_{OFF}) = V_H$$

$$\Rightarrow T_{OFF} = \frac{(V_H - V_L) RC}{V_T}$$

$$T_{OFF} = 2RC \frac{R_1}{R_2} = T_{ON}$$


$$\therefore T = 4RC \frac{R_1}{R_2}$$

$$\Rightarrow f = \frac{R_2}{4R_1 RC}, \text{ changing } R_1 \text{ & } R_2 \text{ changes } V_H \text{ & } V_L$$


Amplitude will change

Not a good function generator.

Change R, C
to change f.

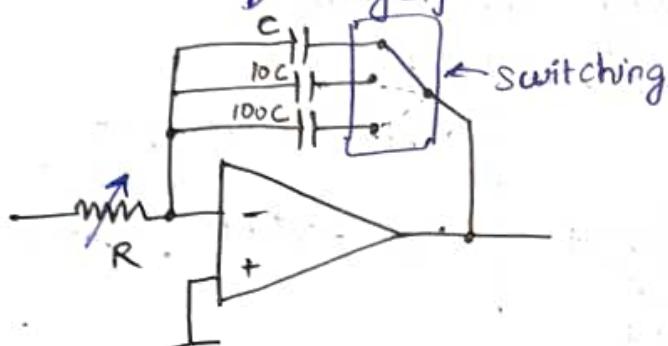

08-04-2024

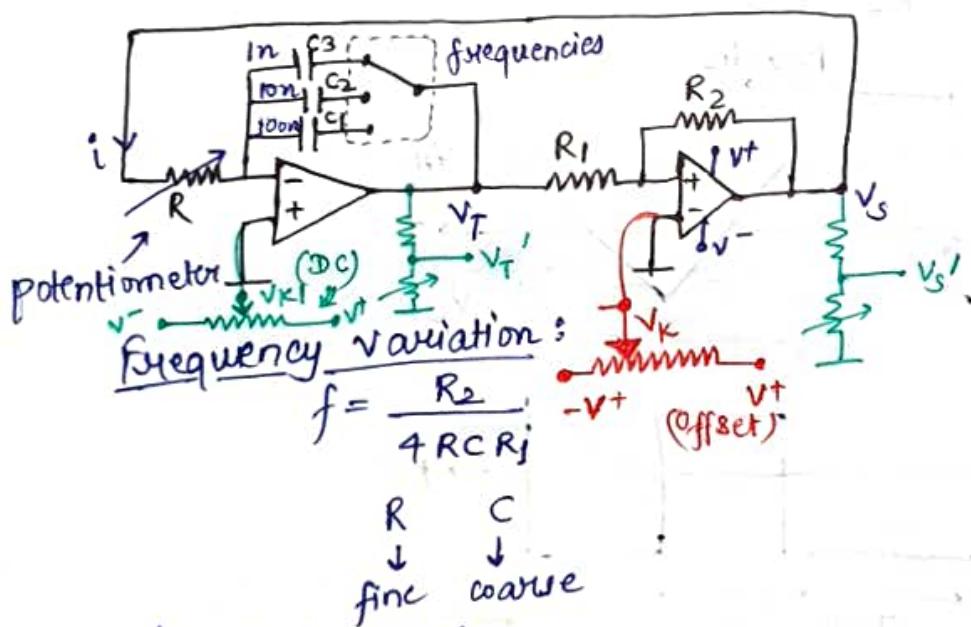

Amplitude variation:

$$V_H = V^+ \frac{R_1}{R_2}$$

→ Cannot be done by changing R_1 , R_2 or V^+
(as there are limitations to supply V^+ , V^-).

→ done using voltage divider → Get V_T' , V_S' .

Offset:

\hookrightarrow To get $V_H \neq |V_L|$

- ↳ To get $V_{H} \neq V_L$
- ↳ Use asymmetrical schmitt trigger \rightarrow Voltage to inverting (V_K) terminal.

Duty-cycle:

$T_{ON} = T_{OFF}$ (for the basic circuit). \Rightarrow Duty cycle = 50%.

$T_{ON} \neq T_{OFF} \rightarrow$ Rate of charging \neq rate of discharging of capacitor.

Add a potential


Charging current,

$$i = \frac{V_s - V_{k1}}{R_1}$$


→ Add a potential to non-inverting terminal of integrator.

$$\text{OFF time: } i_{\text{CHARGE}} = \frac{-V_t - V_{kt}}{R}$$
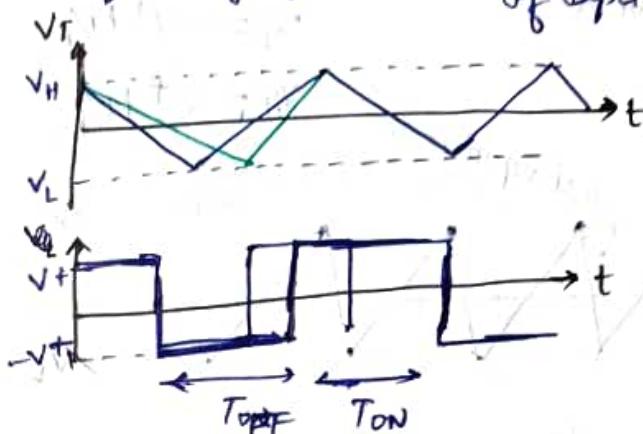
$$\text{ON time} : i_{\text{DISCHARGE}} = \frac{V_t - V_k}{R}$$





Waveform Selection :

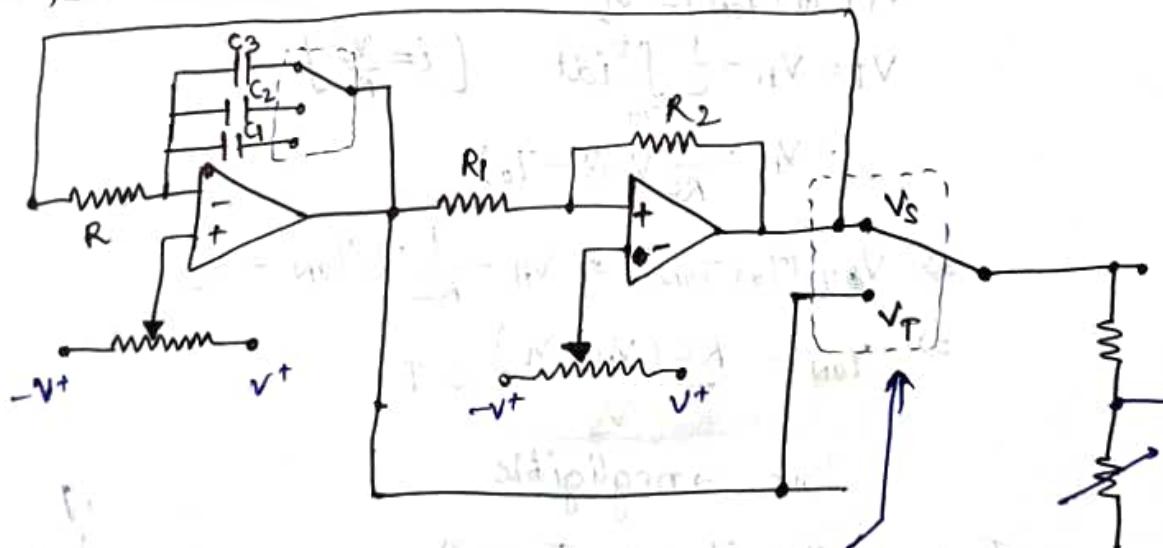

V_s: square wave

\sqrt{T} : Triangular wave

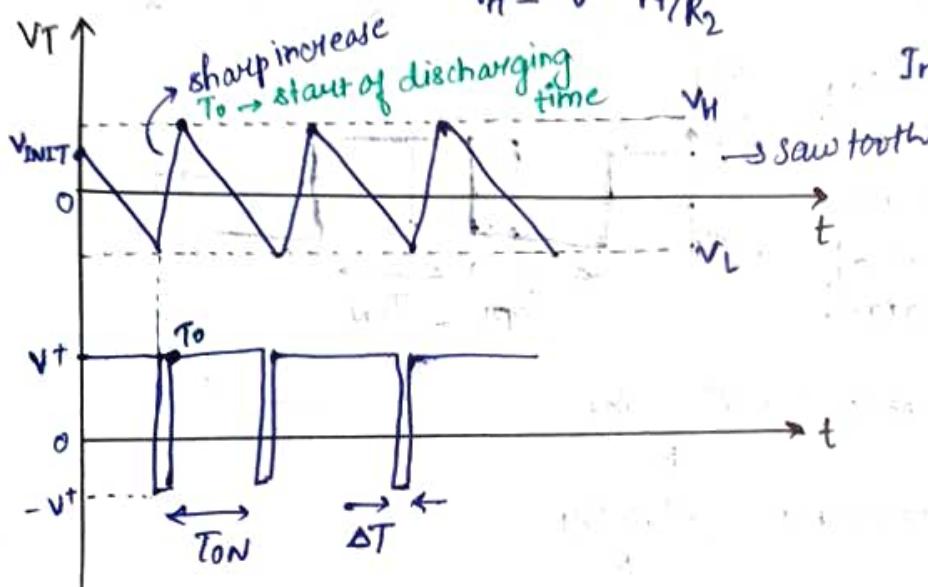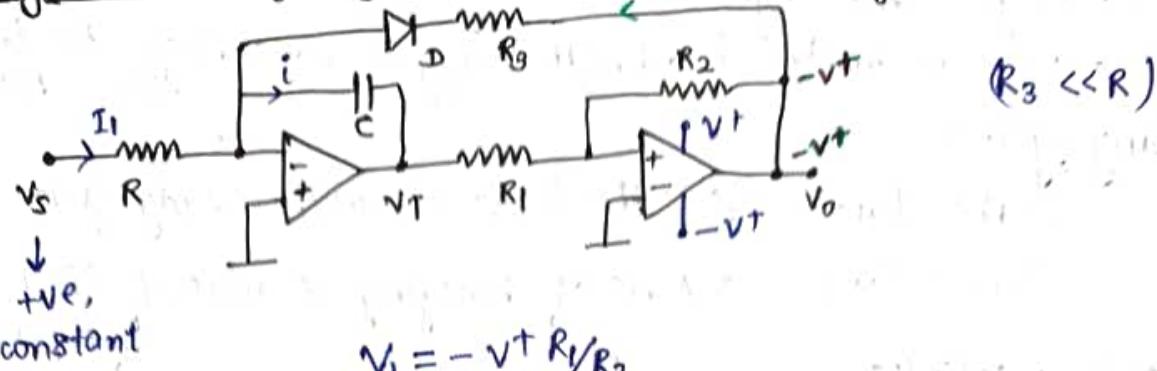Voltage-to-Frequency Converter (Using integrator and schmitt trigger)



Initially: $\underline{\underline{V_T}}$
 $D \Rightarrow R \cdot B.$

$$i = I_1 = \frac{V_s}{R}$$

$$V_T = V_{INIT} - \frac{1}{RC} V_s t$$

(discharge)

$$\underline{\underline{-V_T}}$$

 $D \Rightarrow F \cdot B.$

$$I_2 = -\frac{V_T}{R_3}$$

$$|I_2| \gg |I_1| \quad [R_3 \ll R]$$

$$V_T(T_0) = V_H$$

$$V_T(T_0 + T_{ON}) = V_L$$

$$V_T = V_H - \frac{1}{C} \int_{T_0}^t i dt \quad [i = \frac{V_s}{R}]$$

$$= V_H - \frac{1}{RC} V_s (t - T_0)$$

$$\Rightarrow V_T(T_0 + T_{ON}) = V_H - \frac{1}{RC} V_s T_{ON} = V_L$$

$$\Rightarrow T_{ON} = \frac{RC(V_H - V_L)}{V_s} \approx T$$

$T_{OFF} \rightarrow$ negligible


Time period, $T = T_{ON} + \Delta T \approx T_{ON}$

Fundamental frequency,

$$f = \frac{1}{T} = \frac{V_s}{(2RCV_T + \frac{R_1}{R_2})}$$

$$\Rightarrow f = KV_s$$


↳ Voltage-to-Frequency converter

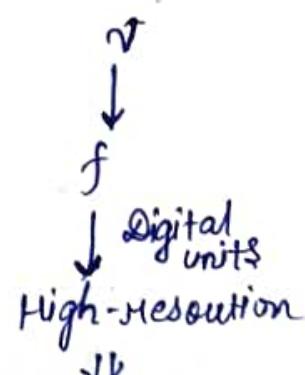

V, I can be measured
with very high resolution

DIGITAL INSTRUMENTATION

Digital Voltmeter

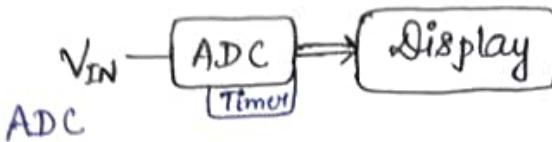


- Speed (samples/sec.) of ADC can be slow.
- Precise and accurate.
- Independent of component non-idealities.

} based on
Time
Measurement
[includes time
module/timer]

Timer

↳ Required for ADC as well as time-measurement of events.


Frequency Meter

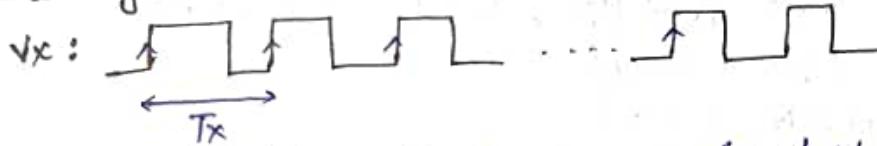

Estimate frequency of unknown signal, V_x :

$$f_x = \frac{1}{T_x}$$

$f_x = ?$

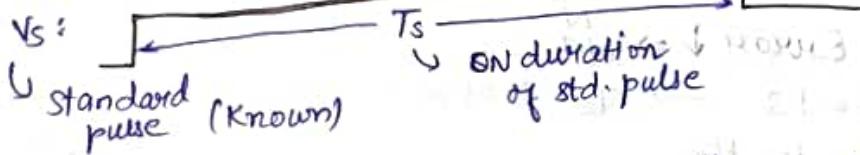

$$T_s = 1 \text{ (say)}$$

$$f_s = 100 \text{ Hz}$$

$$T_x = 0.018$$


$$N = 100 = f_x$$

$$N = \frac{T_s}{T_x} = f_s T_x$$

$N \propto f_x$

Count the no. of pulses of V_x in T_s (i.e. T_x) $\rightarrow N$


Count no. of rise.

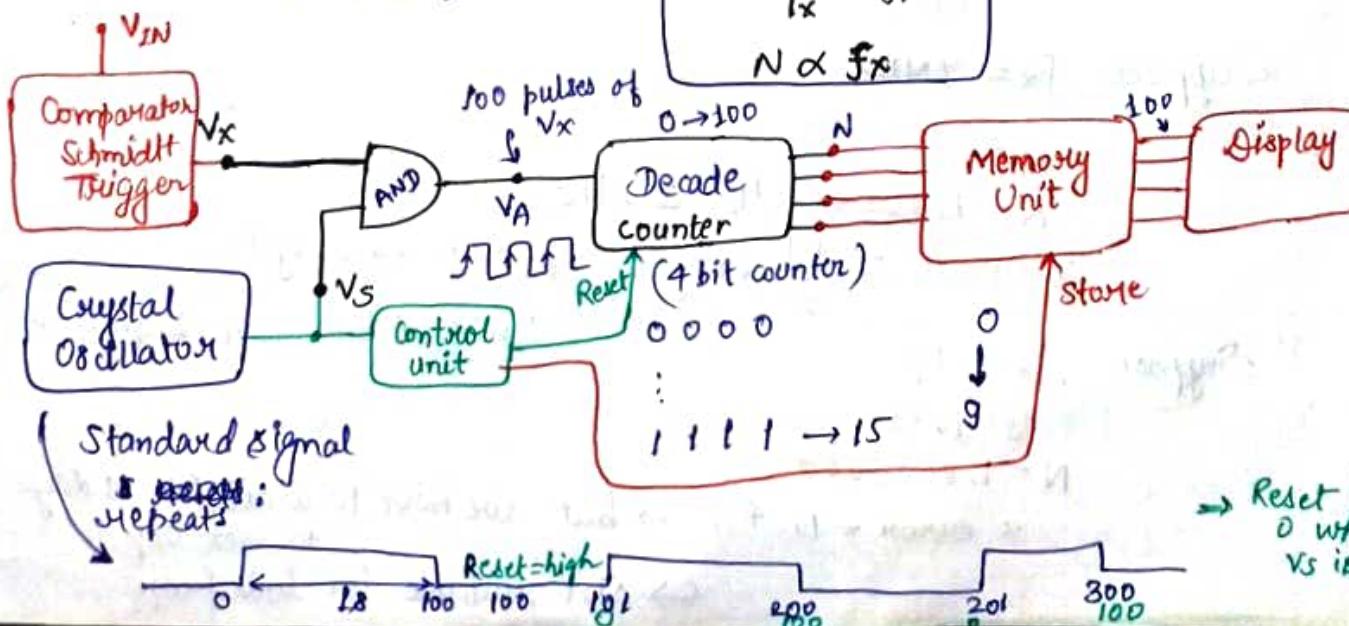

- To get a stable count of 100, (not fluctuating) ⇒ Add a memory unit.
- The input signal can be square / triangle, etc.
↓
Add comparators schmitt trigger to the i/p side.

Sources of Error:

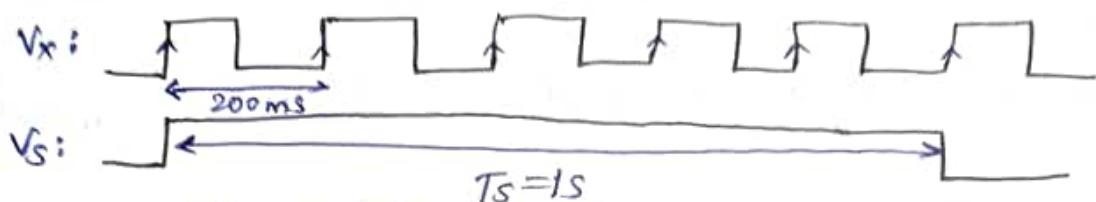Suppose $f_x = 5 \text{ Hz} \Rightarrow N = 5$
 $T_s = 1 \text{ s}$



$N_m = 6$ [There can be a chance that there are 6 transitions]

$$\text{Error}_{\text{in count}} = \Delta N = N_m - N = +1$$

Suppose $f_x = 4.44 \text{ Hz}, T_s = 1 \text{ s} \Rightarrow N = 4.44$ (desired)

$$N_m = 4 \text{ (say)} \\ \Rightarrow \Delta N = -0.44$$

∴ $\Delta N = \pm 1$ (worst case error).

$$\% \text{ error} = \frac{\Delta N}{N} \times 100 \% \\ = \frac{\pm 1}{4} \times 100 \%.$$

Error ↓ $\Rightarrow N \uparrow$

Suppose $T_s = 1 \text{ s} \rightarrow T_s = 1000 \text{ s}$

$$f_x = 100 \text{ Hz} \\ \therefore N = f_x T_s = 100 (\text{Hz}) \pm 1 (\text{Hz}) \rightarrow 100,000 \text{ mHz} \pm 1 \text{ mHz}$$

interpret as mHz
to get 100 Hz
of f_x or display

$$\Rightarrow \text{Error}_{\text{in count}} = \pm 1 \text{ Hz} \rightarrow \pm 1 \text{ mHz}$$

$$\text{Resolution} = 1 \text{ Hz} \text{ (count)} \rightarrow 1 \text{ mHz}$$

Error ↓ $\Rightarrow T_s \uparrow$

Suppose $f_x = 1 \text{ MHz}$

$$T_s = 1 \text{ s}$$

$$N = 1,000,000 \text{ Hz} \pm 1 \text{ Hz}$$

$$\% \text{ error} = \frac{\pm 1}{10^6} \times 100 \% = 10^{-4} \% \rightarrow \text{very low error}$$

if we wait for 1s.
↳ suitable for high freq.

Suppose $f_x = 1 \text{ Hz}$



$$T_s = 10^6 \text{ s}$$

$$N = 1,000,000$$

$$\% \text{ error} = 10^{-4} \% \rightarrow \text{but we have to wait for 11 days}$$

to get o/p
↳ Not suitable for low freq.

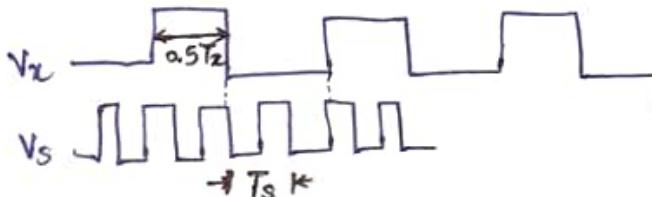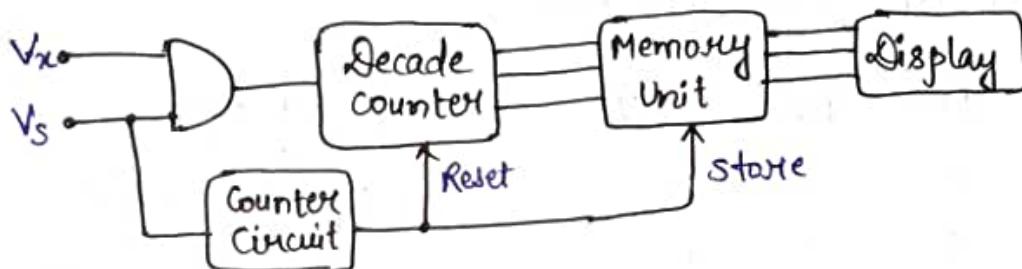Frequency Measurement (Digital Frequency Meters)



$$N = \frac{0.5T_x}{T_s}$$

Eg. $f_x = 1 \text{ Hz}, T_x = 1 \text{ s}$
 $T_s = 0.5 \text{ ms} \Rightarrow N = 1,000,000 (\mu\text{s}) \approx \pm 1 (\mu\text{s})$

% error = $\frac{1}{10^6} \times 100 = 10^{-4}\%$. \rightarrow we have to wait for only $0.5 T_x$ time (not 10^6 s) and have low error.

Frequency, $f_{\text{req.}} = \frac{1}{N}$.

NOW,


$$T_x = 0.98$$

$$N = 9,00,000 (\mu\text{s})$$

$$f_{\text{req.}} = \frac{1}{N}$$




Time Period Mode of Operation : Timer

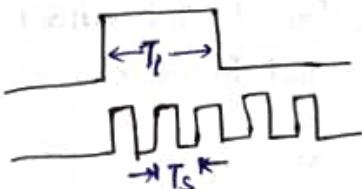

$$N = \frac{T_1}{T_s}$$

$$\Rightarrow T_1 = N T_s$$

Digital Frequency Meter

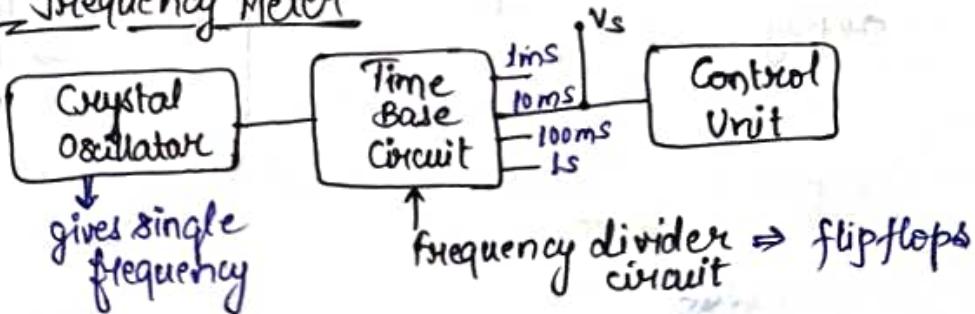


→ Single digit decade counter.

→ n-digit decade counter

↳ cascade single digit meters

T	DC3	DC2	DC1	⇒ 3 full-digit + 1 partial digit
0	0	0	0	0
1	0	0	0	1
2	0	0	0	2
:				
9	0	0	0	9
10	0	0	1	0
11	0	0	1	1
:				
999	0	9	9	9
1000	1	0	0	0
1999	1	9	9	9

↳

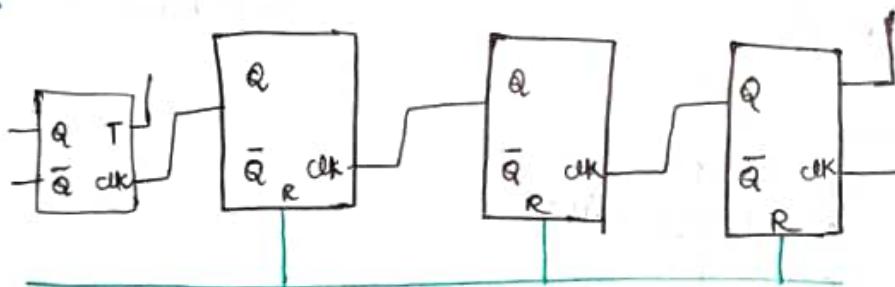

⇒ TFF: doubles the count.

→ Significance of 1/2 digit: To measure 2 resistors of the same batch.
e.g. $1\text{ k}\Omega$

Result: 999.5Ω or 1002.5Ω (due to tolerance)

1/2 digit: $\underline{\underline{9}} \underline{\underline{9}} \underline{\underline{9}}$ ↳ cannot be displayed in 3 digit meter
 $\underline{\underline{1}} \underline{\underline{0}} \underline{\underline{2}}$ ⇒ can be displayed in 3.5 digit meter.

→ LCD or LED is used for display.

[R: $1\text{ k}\Omega$ $2\text{k}\Omega$ $10\text{k}\Omega$ $100\text{k}\Omega$
C: 1nF 10nF 100nF
↳ commonly available values for R & C]

→ May be suitable for project

$$f_x = 500 \text{ Hz}$$

$$T_s = 18$$

$$N = f_x T_s = 500$$

$$\begin{array}{r} \underline{\underline{5\ 0\ 0}} \\ \underline{1\ 9\ 9\ 9} \end{array} \approx 2 \text{ kHz}$$

3.5 meter
(max)

→ 2 kHz

$$\text{Error} = 1 \text{ Hz}$$

$$\text{Resolution} = 1 \text{ Hz}$$

Now,

$$f_x = 5000 \text{ Hz}$$

$$T_s = 10 \text{ ms}$$

$$N = f_x T_s = 500$$

Twin ON the decimal display → $\begin{array}{r} \underline{\underline{5\ 0\ 0}} \\ \underline{1\ 9\ .\ 0\ 0} \end{array} \approx 20 \text{ kHz}$

of 7 segment

→ 2 kHz
→ 20 kHz

Now,

$$f_x = 5000 \text{ Hz}$$

$$T_s = 1 \text{ ms}$$

$$N = 500$$

$$\begin{array}{r} \underline{\underline{5\ 0\ 0}} \\ \underline{1\ 9\ .\ 0\ 0} \end{array} \approx 200 \text{ kHz}$$

16-04-2024

$$f_x = 500 \text{ Hz}$$

$$T_s = 18$$

$$\underline{\underline{5\ 0\ 0}} \text{ Hz}$$

$$\text{error} = \text{resolution} \\ = 1 \text{ Hz}$$

$$f_x = 5 \text{ kHz}$$

$$T_s = 100 \text{ ms}$$

$$\underline{\underline{5\ 0\ 0}} \text{ kHz}$$

$$\text{error} = \text{resolution} \\ = 10 \text{ Hz}$$

$$f_x = 50 \text{ kHz}$$

$$T_s = 10 \text{ ms}$$

$$\underline{\underline{5\ 0\ 0}} \text{ kHz}$$


$$\text{error} = \text{resolution} \\ = 100 \text{ Hz}$$

→ 2K
→ 20K
→ 200K


→ Modern meters have auto-ranging facility.

Digital Voltmeter [Dual Slope ADC]

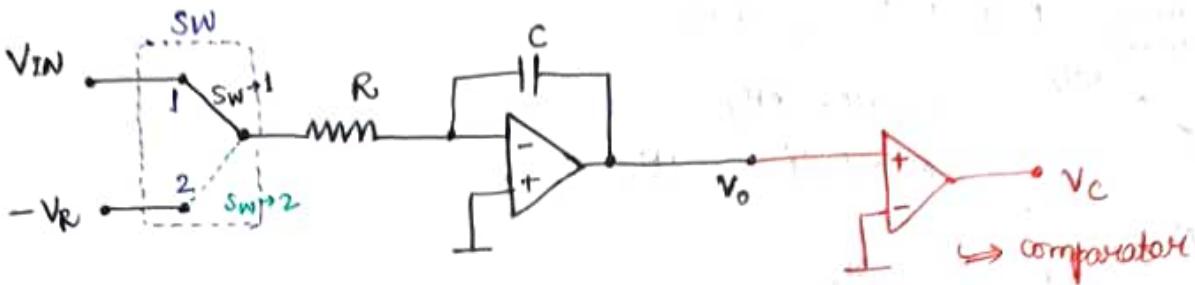ADC should be
 → slow
 → precise
 → independent of circuit


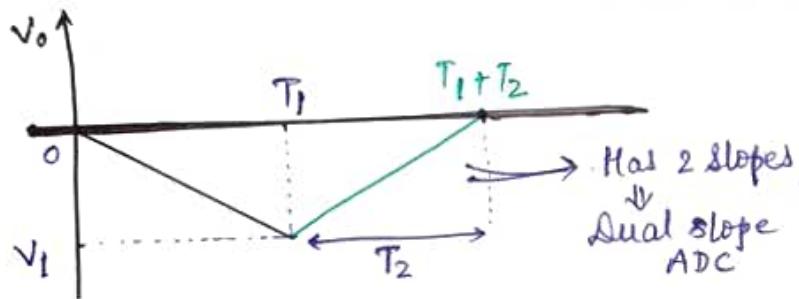
$$V_o = -\frac{1}{RC} \int V_{IN} dt \\ = -\frac{1}{RC} V_{IN} t$$



$$V_I = -\frac{1}{RC} V_{IN} T_1 \dots ③$$

T_1 : integration period (fixed)
 ↳ set before usage

SW → 2

$$\text{Charging: } V_o(t) = V_I + \frac{V_R}{RC} (t - T_1) \dots ①$$

$$V_o(T_1 + T_2) = 0 \dots ②$$

$$① \& ② \Rightarrow V_I + \frac{V_R}{RC} T_2 = 0$$


$$\text{Using } ③ \Rightarrow -\frac{1}{RC} V_{IN} T_1 + \frac{V_R}{RC} T_2 = 0$$

$$\Rightarrow \boxed{\frac{V_{IN}}{V_R} = \frac{T_2}{T_1}}$$

As T_1, V_R : constant $\Rightarrow T_2 \propto V_{IN}$

V_R : reference voltage
 ↳ constant
 T_2 : deintegration time

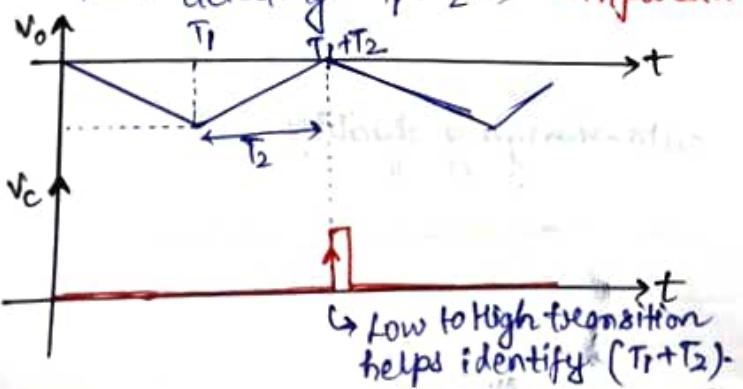For detecting $T_1 + T_2 \Rightarrow$ comparator is required




For T_1 : SW → 1: $V_{SW} \equiv \text{High (H)}$

T_2 : SW → 2: $V_{SW} \equiv \text{Low (L)}$

V_{SW} : control signal

V_C has \int
 ↳ H to L transition

Control and timing unit (CTU) : Timer

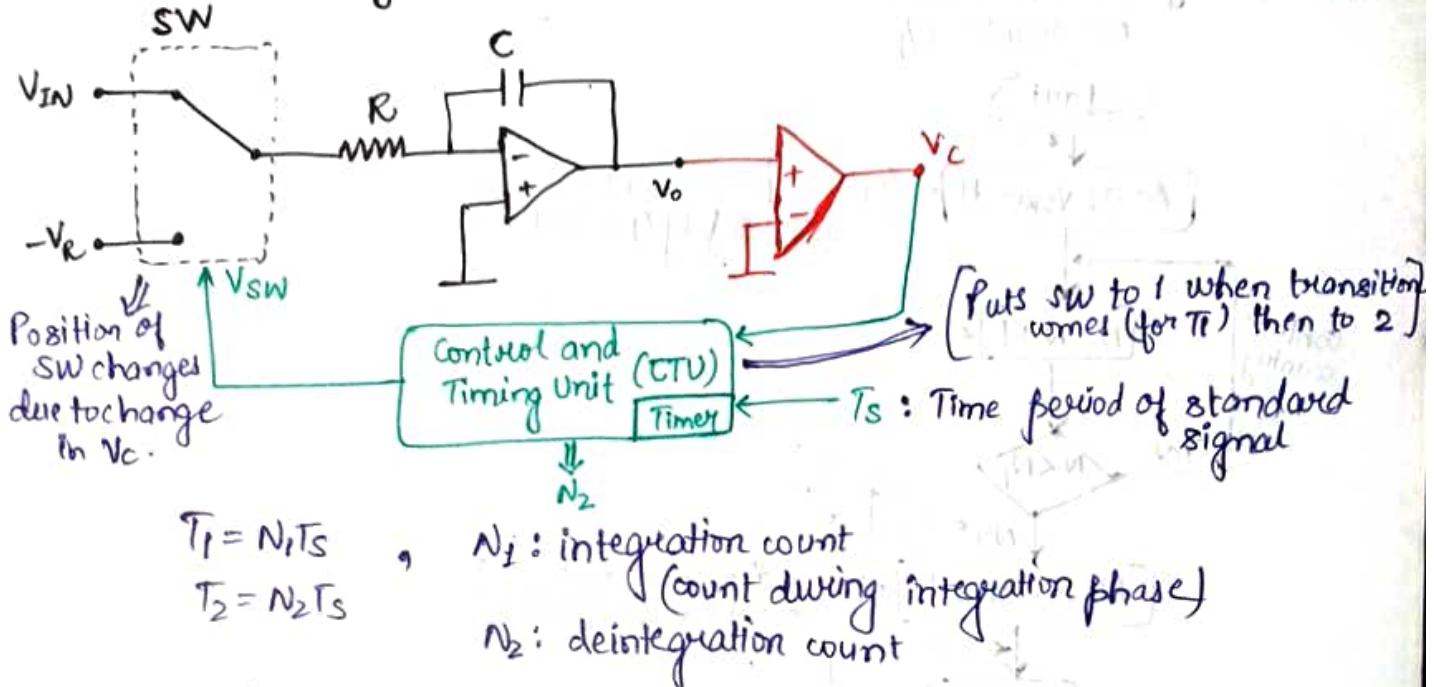

$$T_1 = N_1 T_s$$

$$T_2 = N_2 T_s$$

, N_1 : integration count

(count during integration phase)

N_2 : deintegration count

$$\frac{V_{IN}}{V_R} = \frac{T_2}{T_1} = \frac{N_2}{N_1}$$

As V_R, N_1 : constant $\Rightarrow N_2 \propto V_{IN}$, N_2 : digital count

\hookrightarrow digital indication of I/P voltage

Eg. $N_1 = 2000$

$f_s = 10 \text{ KHz}$, $V_R = 2V$

$$\Rightarrow T_s = 100 \mu\text{s}$$

$$T_1 = 200 \text{ ms}$$

$$\frac{V_{IN}}{V_R} = \frac{T_2}{T_1} = \frac{N_2}{N_1} \Rightarrow \frac{V_{IN}}{2} = \frac{N_2}{2000}$$

$$\Rightarrow N_2 = 1000 V_{IN}$$


\hookrightarrow I/P voltage in unit of (mV)

Suppose after 6 months,


$$T_s = 101 \mu\text{s}$$

$$T_1 = 202 \text{ ms}$$

$N_2 \rightarrow$ remains the same.

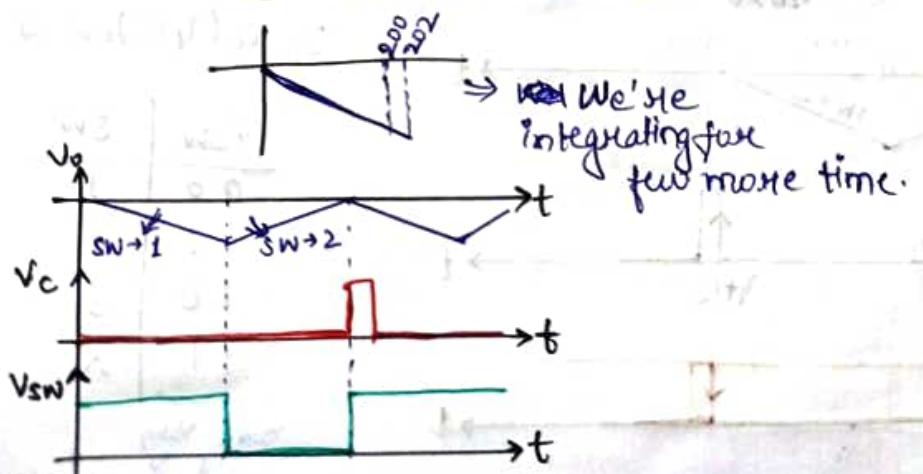


CTU Logic flowchart:

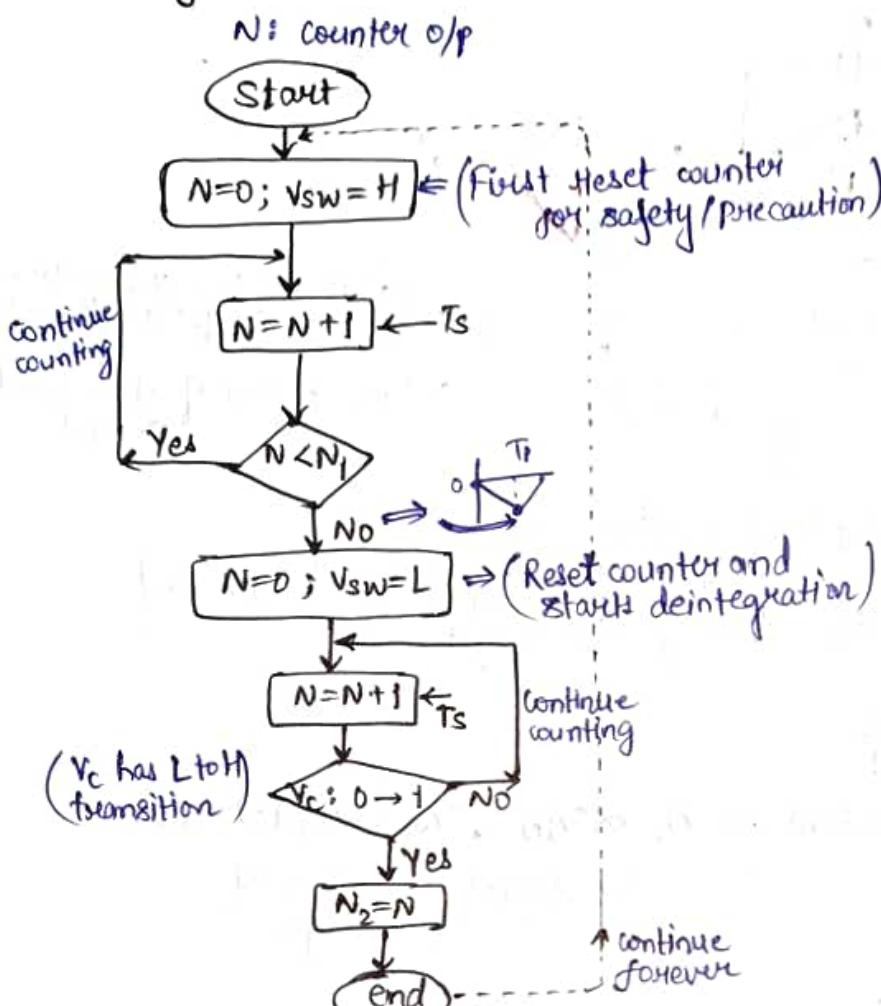


Assumption: Input, $V_{IN} > 0$
 ↳ (Unipolar DC voltmeter)

If $V_{IN} < 0$ also:

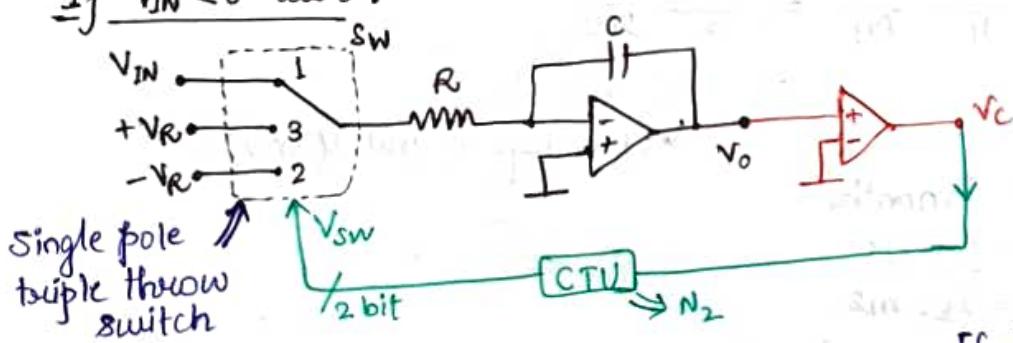

Single pole
triple throw
switch

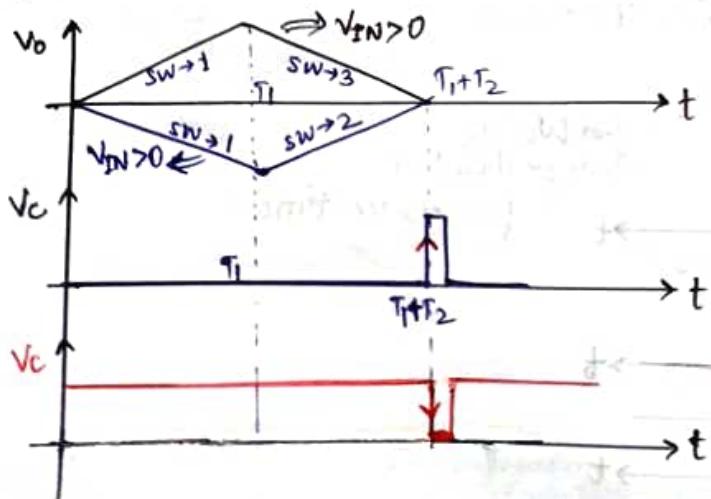

If $V_C(T_1) \equiv \text{High} \Rightarrow SW \rightarrow 3$

If $V_C(T_1) \equiv \text{Low} \Rightarrow SW \rightarrow 2$


V_{SW}	SW
0 0	1
0 1	2
1 0	3
1 1	X

V_{SW1} V_{SW2}
 separate waveforms

$\Rightarrow \frac{V_{IN}}{V_R} = \frac{T_2}{T_1} = \frac{N_2}{N_1} \Rightarrow$ output (N_2) is independent of
 $T_s, R, C, R_{ON}, V_{OS}$
tolerance & drift
don't affect the system


\rightarrow Ideal switches have zero ON resistance.

Practical switches have ON resistance.

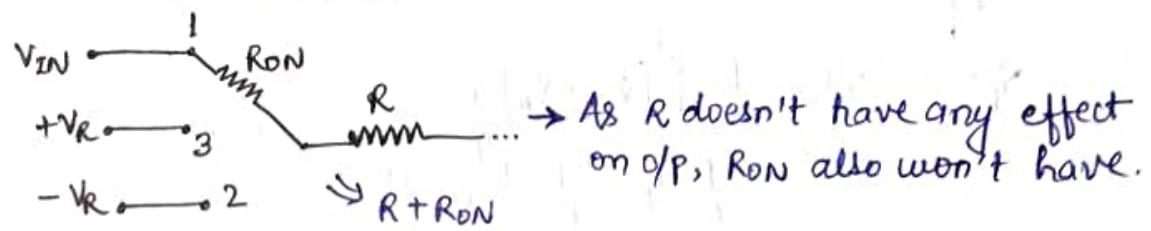

$\rightarrow V_{OS}$: i/p offset voltage of comparator

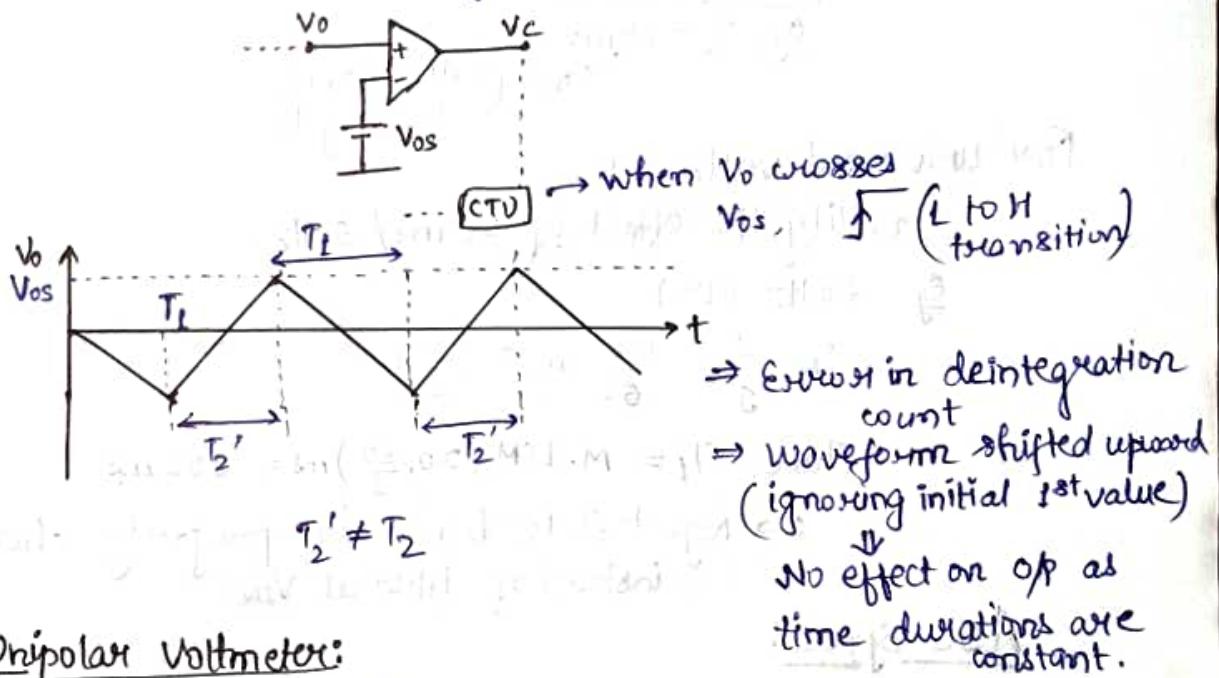
\hookrightarrow modelled as voltage source at +ve terminal.



\rightarrow Unipolar Voltmeter:

Sources of error: Powerline interference

\downarrow can affect i/p signal

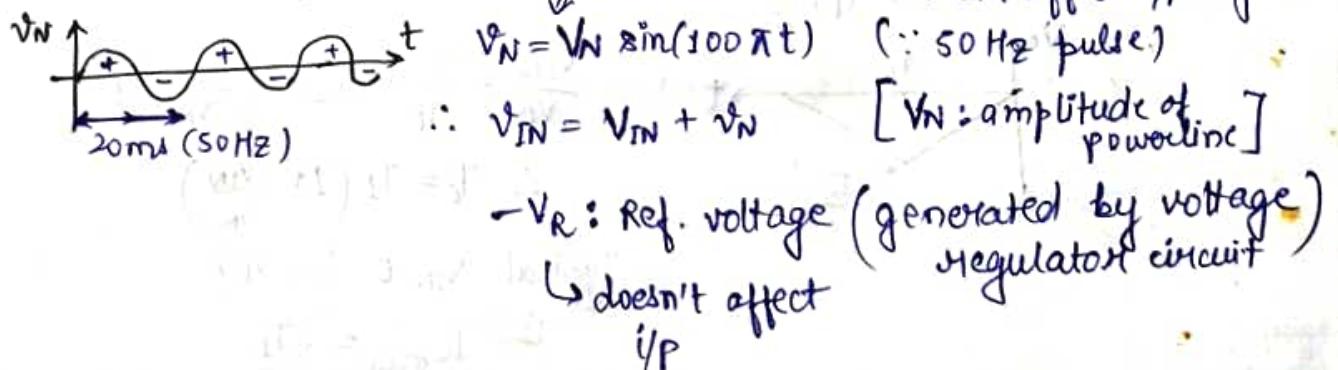

$$V_{IN} = V_{IN} + V_N$$


$(T_2) \rightarrow$ sw at 1 for T_1

$$\therefore -V_R = -V_R$$

$(T_2) \rightarrow$ sw at 2 for T_2

$$V_o = -\frac{1}{RC} \int V_{IN} dt$$
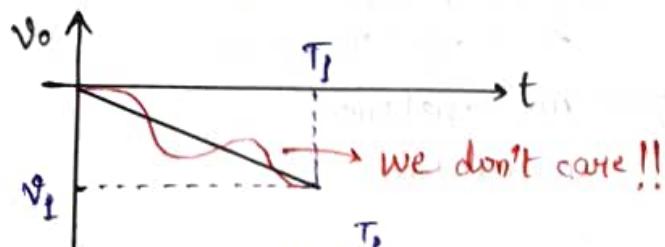
$$\Rightarrow V_o = -\frac{1}{RC} \int (V_{IN} + v_N) dt$$



$[T_1 : \text{integration time}]$

$$\begin{aligned} V_i &= V_o(T_1) = -\frac{1}{RC} \int_0^{T_1} [V_{IN} + v_N] dt \\ &= -\frac{1}{RC} T_1 - \frac{1}{RC} \int_0^{T_1} v_N dt \end{aligned}$$

(for each cycle of v_N)

↪ choose T_1 as integral multiple of 20 ms.

$$T_1 = M(20 \text{ ms}) \rightarrow \text{for Indian condition}$$

e.g., $T_1 = 60 \text{ ms}$
↪ integration vanishes
for 3 cycles.

For universal voltmeter,

nullify the effect of 20 ms / 50 Hz.

e.g. 60 Hz (US)

$$T_N = \frac{1}{f} = \frac{1000}{60} \text{ ms} = \frac{50}{3} \text{ ms}$$


$$\text{Take } T_1 = M \cdot \text{LCM}(20, \frac{50}{3}) \text{ ms} = 100 \text{ ms}$$

↪ Reject disturbance by properly choosing T_1 instead of filter at V_{IN} .

ADC Speed:

Conversion time (T_c) $\downarrow \Rightarrow$ speed \uparrow

$$= T_1 + T_2$$

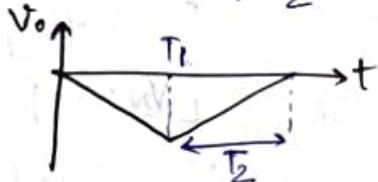

$$\frac{V_{IN}}{V_R} = \frac{T_2}{T_1} \Rightarrow T_2 = \left(\frac{V_{IN}}{V_R}\right) T_1$$

$$\therefore T_c = T_1 \left(1 + \frac{V_{IN}}{V_R}\right)$$

Typical $V_{IN} \in (0, V_R)$


$$\hookrightarrow T_{c\max} = 2T_1$$

we need to provide $2T_1$ to ADC but T_1 has other restriction:

choose lower T_1 and satisfy


$$T_1 = M \cdot \text{LCM}(20, \frac{50}{3})$$

AC Voltmeters

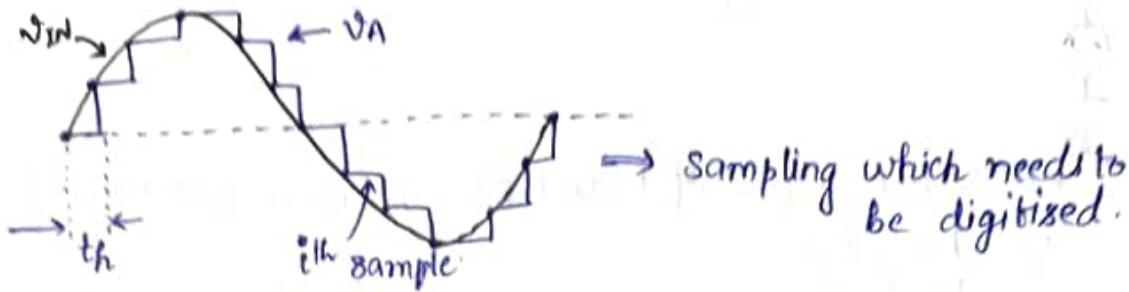

t_h : Hold time

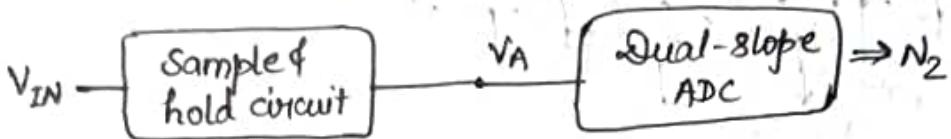
$$t_h \geq 2T_1 \quad [\text{Input should be stable for atleast } '2T_1']$$




ith sample $\rightarrow N_{2i}$

$$\text{RMS value} = \sqrt{\frac{1}{M} \sum_{i=1}^M N_{2i}^2}, \quad M \text{ samples in 1 cycle.}$$

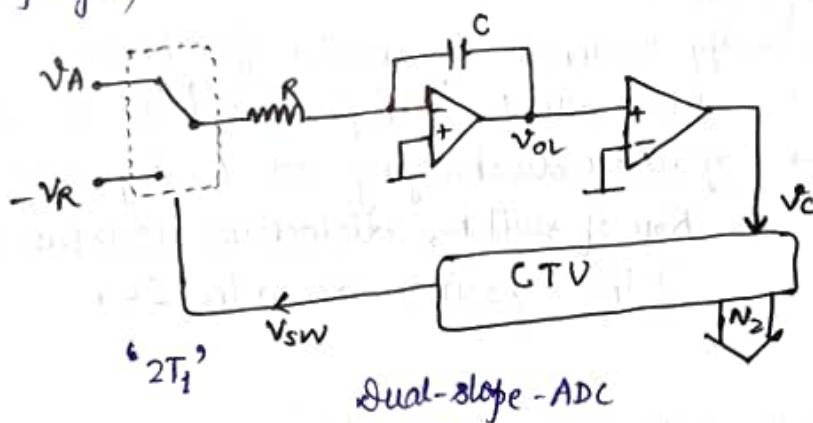
(to be displayed) \hookrightarrow (Approximate formula)




Sample and Hold circuit:

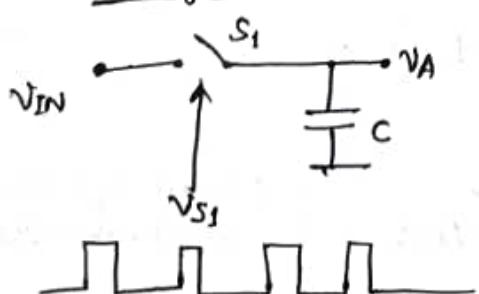

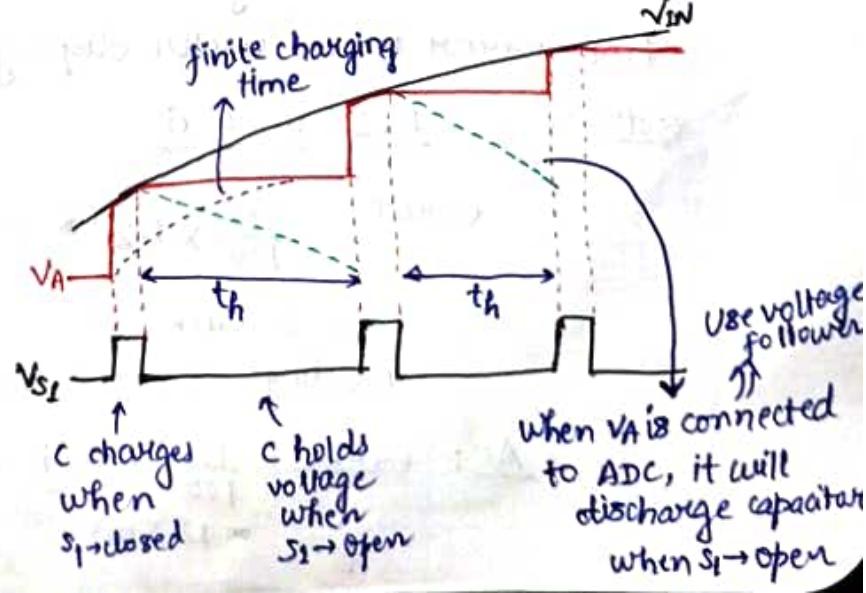
$$V_{S1} = \text{High} \Rightarrow S_1 = \text{closed} \\ = \text{Low} \Rightarrow S_1 = \text{open.}$$



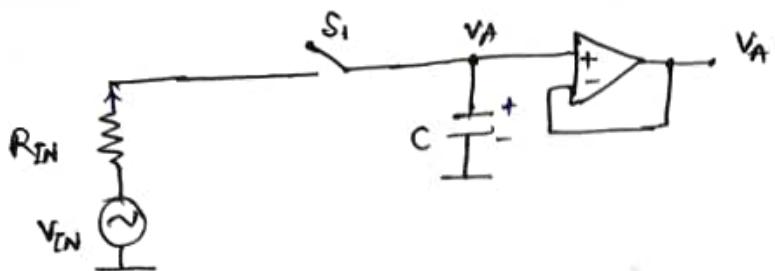

Due to R_{IN} effect of R and C , capacitor will take finite time for charging.

Use one more voltage follower.

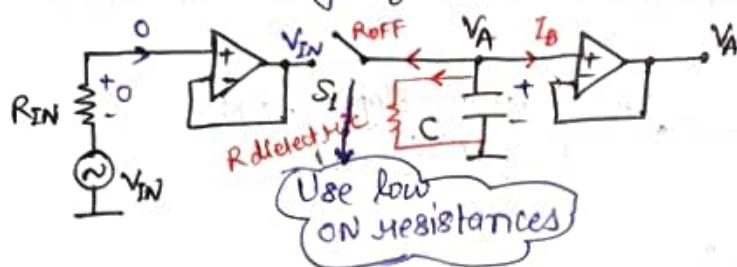

Digital Multimeter (DMM)

Has high errors in AC mode than DC mode

Sources of error:

- Approximate formula for RMS.
- Errors due to sample and hold circuit.
- Capacitor discharging due to input offset current (I_O)
 R_{OFF} of switch, dielectric resistance (R_{dielectric})
 of the capacitor or in the IC.

Eg. 4½ DMM

DC: 0.2% of reading + 2 counts

AC: 1% of reading + 5 counts

Find error when meter displays 1.2 V DC.

Soln: DC: 1.2 0 0 0

$$\text{error} = \frac{0.2}{100} \times 1.2 + 2 \times 0.1 \text{ mV}$$

$$= 2.6 \text{ mV}$$


Reading: $1.2 \text{ V} \pm 2.6 \text{ mV}$

$$\text{AC: error} = \frac{1}{100} \times 1.2 + 5 \times 0.1 \text{ mV}$$

$$= 12.5 \text{ mV}$$

[1 count of error
≡ 0.1 mV error]

Resistance Measurement

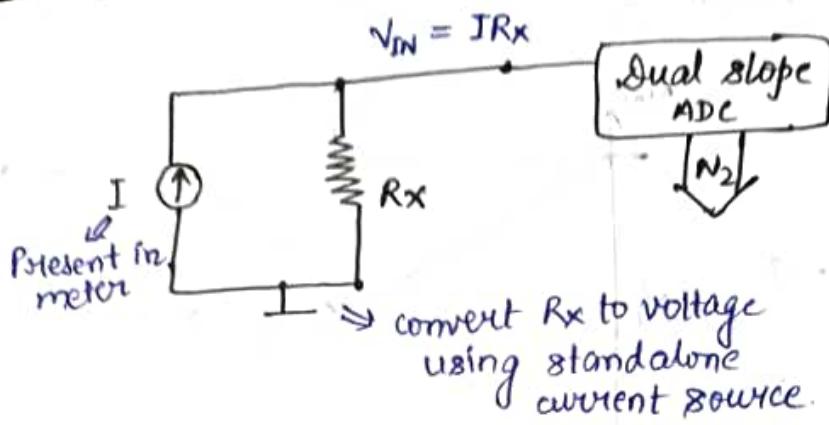

$$\frac{V_{IN}}{V_R} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{IR_x}{V_R} = \frac{N_2}{N_1}$$

$$\Rightarrow N_2 \propto R_x$$

For
 $I = 1\text{mA}$
 $N_1 = 2000$
 $V_R = 2\text{V}$

$$\frac{1\text{mA}}{2} R_x = \frac{N_2}{2000}$$


$$\Rightarrow N_2 = R_x (2)$$

↳ N_2 is representing the resistance in the units of ohm.

- Demerits:
- One grounded current source is needed.
 - One separate ADC is needed.
 - The circuit is cascaded, adding up the errors.

Solution: Use R_x as the input resistance of ADC, instead.

Resistance to Digital converter:

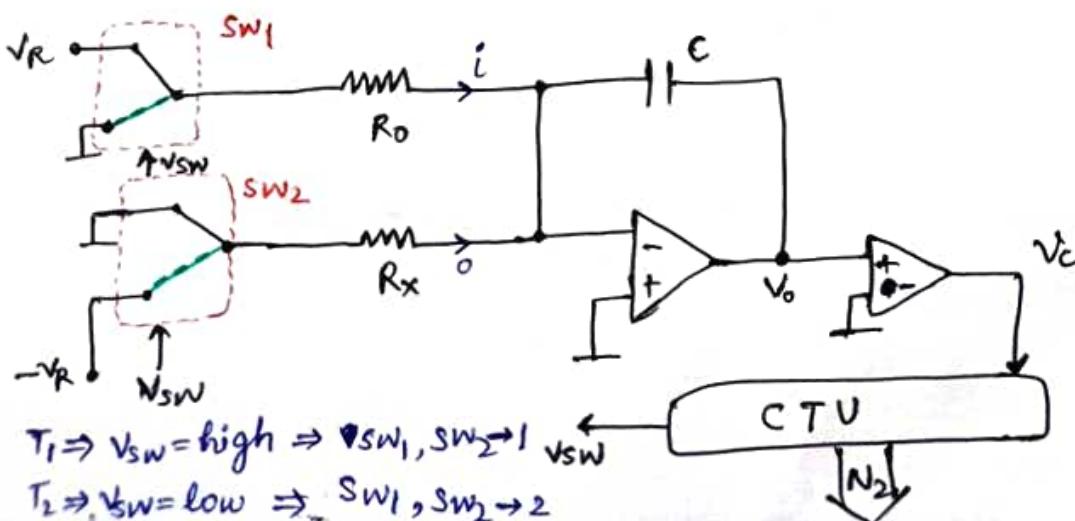

$T_1 \Rightarrow V_{SW} = \text{high} \Rightarrow SW_1, SW_2 \rightarrow 1$

$T_2 \Rightarrow V_{SW} = \text{low} \Rightarrow SW_1, SW_2 \rightarrow 2$

During T₁

R_x is inactive.


$$i = \frac{V_R}{R_o}$$

$$V_{oi} = -\frac{1}{R_o C} V_R t$$

$$\Rightarrow V_i = -\frac{1}{R_o C} V_R T_1 \quad \text{--- ①}$$



transistor M₁ on transistor M₂

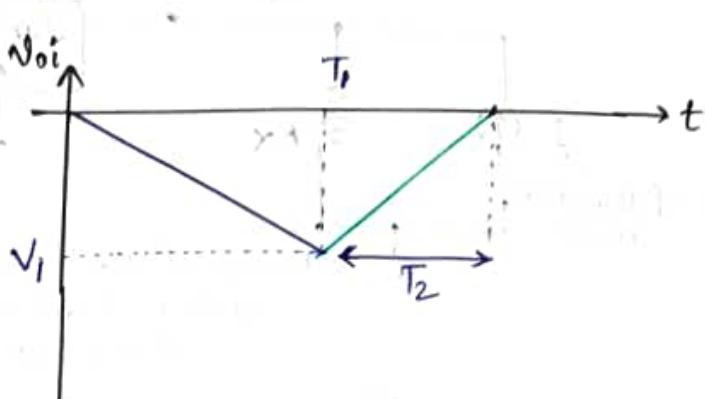

During T₂

R_o is inactive

$$i = -\frac{V_R}{R_x}$$

$$V_o = V_i + \frac{V_R}{R_x C} (+ - T_1) \quad \text{--- ②}$$

$$V_o (T_1 + T_2) = 0 \quad \text{--- ③}$$



$$\text{①, ② + ③} \Rightarrow V_o = -\frac{1}{R_o C} V_R T_1 + \frac{V_R}{R_x C} T_2 = 0$$

$$\Rightarrow \boxed{\frac{T_2}{T_1} = \frac{R_x}{R_o} = \frac{N_2}{N_1}}$$

Capacitance to Digital converter



Generic dual-slope ADC

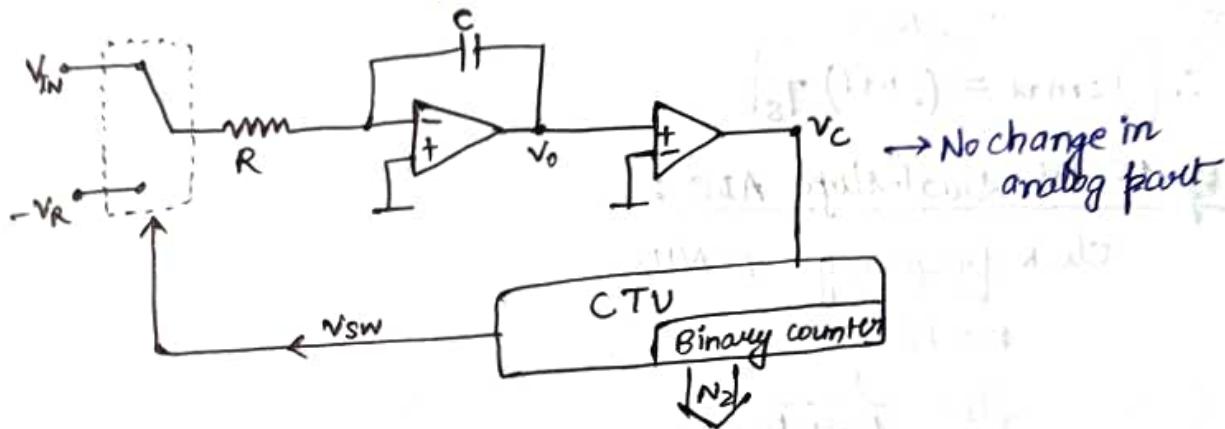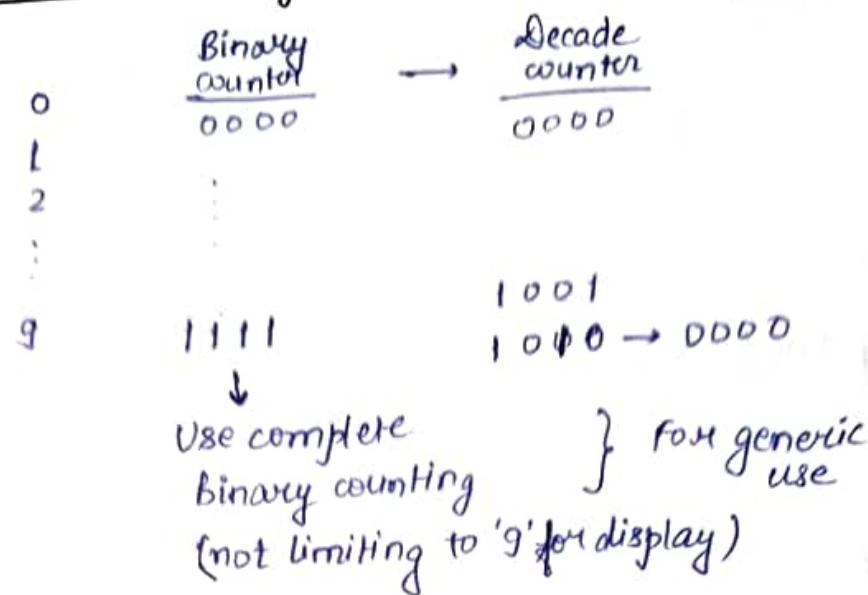

3-bit dual-slope ADC:

v_{IN}	DOUT
(0,1)	0 0 0
(1,2)	0 0 1
(2,3)	0 1 0
(3,4)	0 1 1
(4,5)	1 0 0
(5,6)	1 0 1
(6,7)	1 1 0
(7,8)	1 1 1

$$V_R = 8V$$

$$V_{IN} \in (0, 8)$$

$$\text{Resolution} = 1V = \frac{8V}{2^3}$$

$$n\text{-bit ADC : Resolution} = \frac{V_R}{2^n}$$

↑ Unipolar ADC

Bipolar ADC:

$$V_{IN} \in (-V_R, V_R)$$

$$\text{Resolution} = \frac{2V_R}{2^n}$$

$$= \frac{V_R}{2^{n-1}}$$

For $N_1 = 8$, $= 2^3 \checkmark$ [Unipolar]

$$\frac{V_{IN}}{V_R} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{V_{IN}}{8} = \frac{N_2}{8}$$

$$\Rightarrow N_2 = V_{IN} \checkmark$$

n-bit ADC: [Unipolar]

$$N_1 = 2^n$$

$$T_1 = N_1 T_s$$

$$T_{cmax} = 2 T_1$$

$$= 2 N_1 T_s$$

$$\therefore \boxed{T_{cmax} = (2^{n+1}) T_s}$$

Eg 16-bit Dual-slope ADC:


$$\text{Clock frequency} = 10 \text{ MHz}$$

$$n = 16$$


$$T_s = \frac{1}{10 \times 10^6}$$

$$\therefore T_{cmax} = 2^{17} \times 10^{-7} = 13 \text{ ms}$$

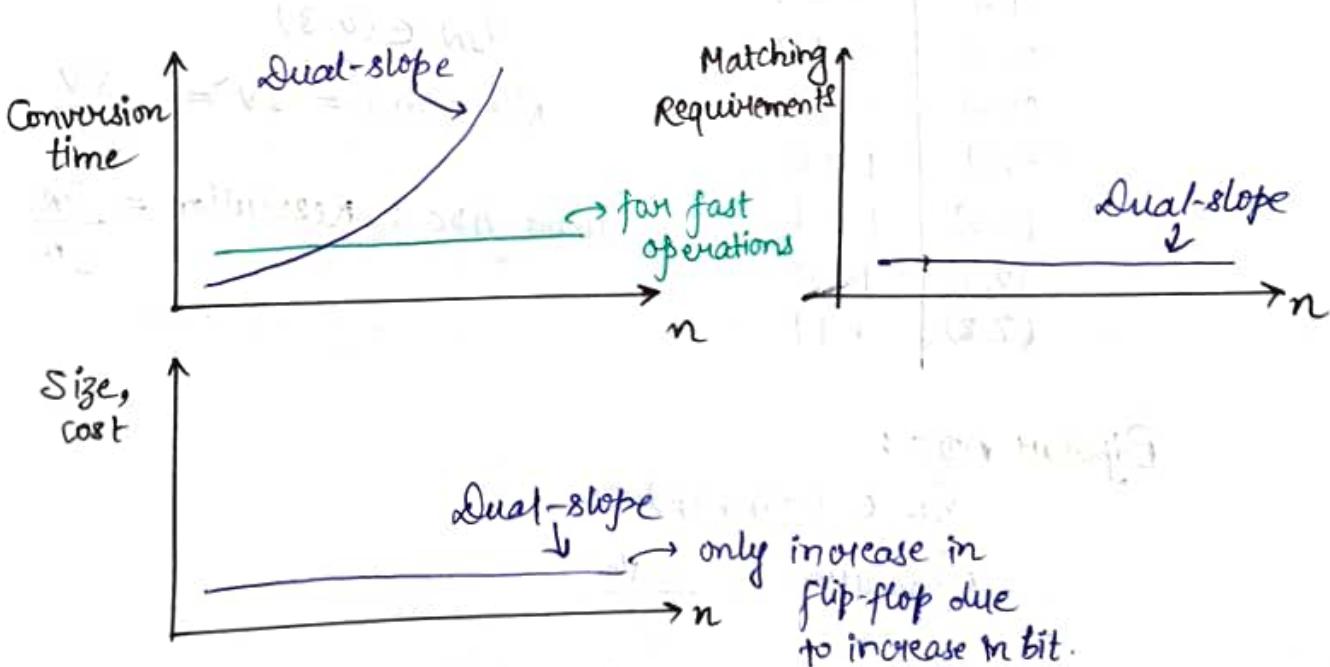
$$\therefore \text{no. of conversions/sec.} = \frac{1}{13 \text{ ms}} \approx 76.$$



Flash ADC:

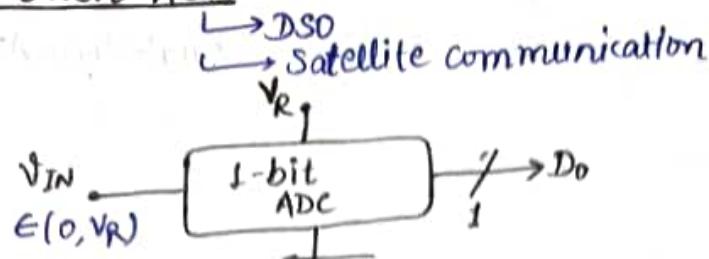


V_{IN}	D_0
$(0, V_R/2)$	0
$(V_R/2, V_R)$	1

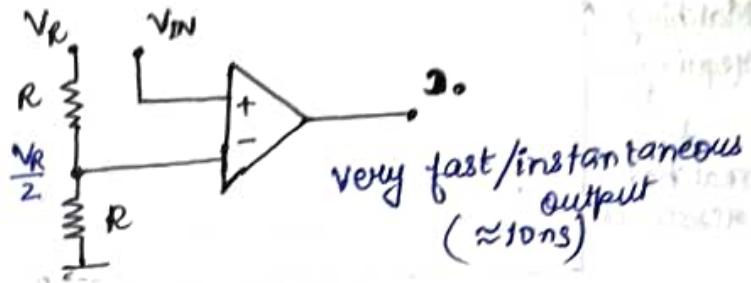

2-bit Flash ADC:

V_{IN}	D_1	D_0	C_3	C_2	C_1	$C_2 \bar{C}_1$	D_1	D_0
$(0, V_R/4)$	0	0	0	0	0	1	0	0
$(V_R/4, V_R/2)$	0	1	0	0	1	1	1	0
$(V_R/2, 3/4 V_R)$	1	0	0	1	1	0	0	0
$(3/4 V_R, V_R)$	1	1	1	1	1	0	0	0

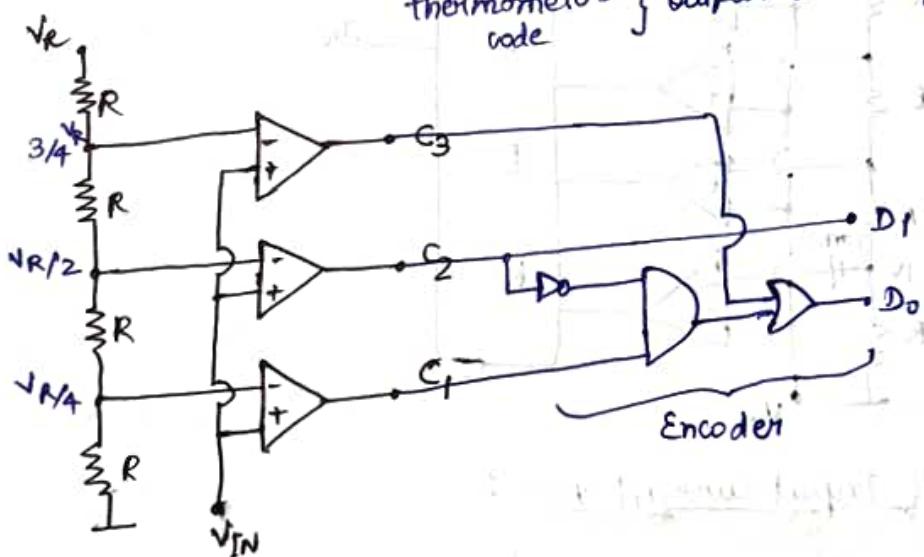
thermometer code } outputs become progressively high



$$D_1 = C_2$$

$$D_0 = C_3 + C_2 \bar{C}_1$$

Flash ADC:


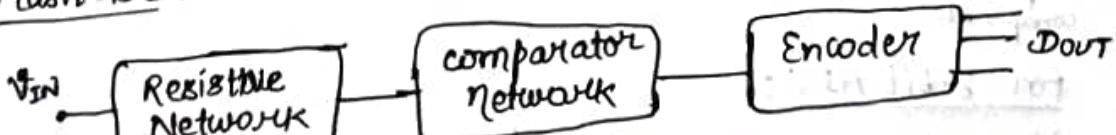


2 bit Flash \rightarrow 4R, 3 comparators


n-bit Flash ADC \rightarrow $2^n R$, $(2^n - 1)$ comparators

$\hookrightarrow n \leq 8$ (available)

Conversion time

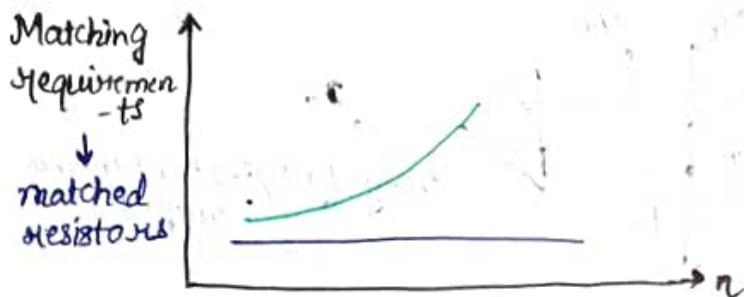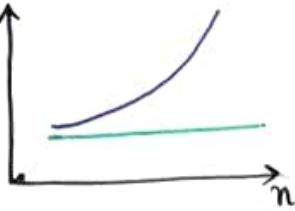

3-bit ADC: $V_R = 8V$

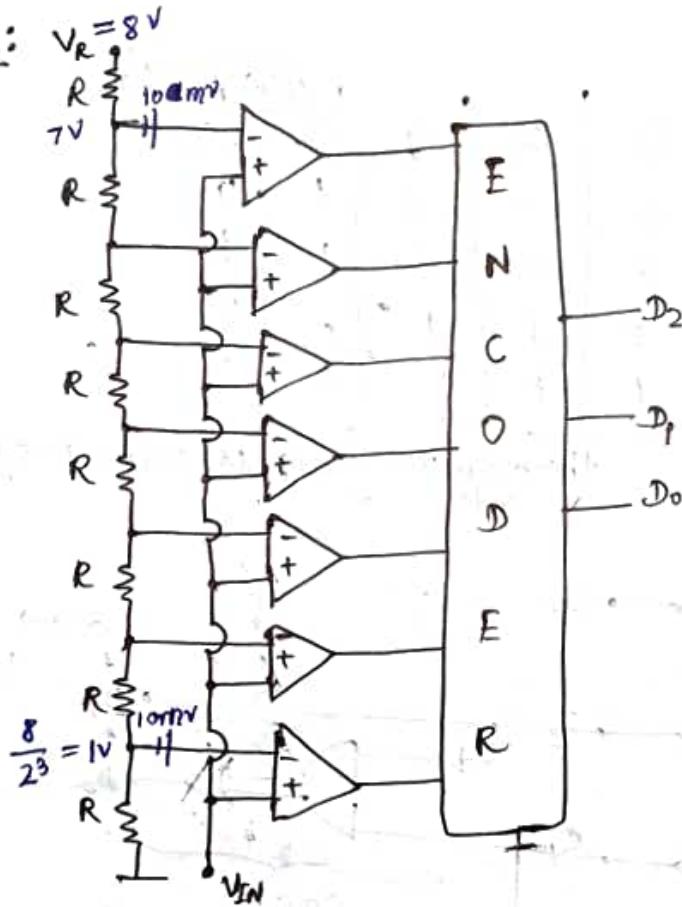

Effect of Input Current Bias:

Suppose $V_{OS} = 10mV \rightarrow$ doesn't affect Dual-slope ADC

for bottommost, $1V + 10mV = 1.01V$ [Error $= 1\%$] } Error is highest
comparator
for topmost: $7V + 10mV = 7.01V$ [Error $< 1\%$] } for bottommost
comparator

for 8-bit ADC:

bottommost: $\frac{8}{2^8} = 31mV$ $\xrightarrow{\text{offset}} 41mV$
[Error $= \frac{10}{31} \times 100\% \rightarrow$ very large]


DAC (Digital to Analog Converter)

↪ Present within ADC

: DAC fid-8

2-bit DAC: (NR)

D_1	D_0	V_o
0	0	0
0	1	$-V_R/4$
1	0	$-V_R/2$
1	1	$-3/4 V_R$

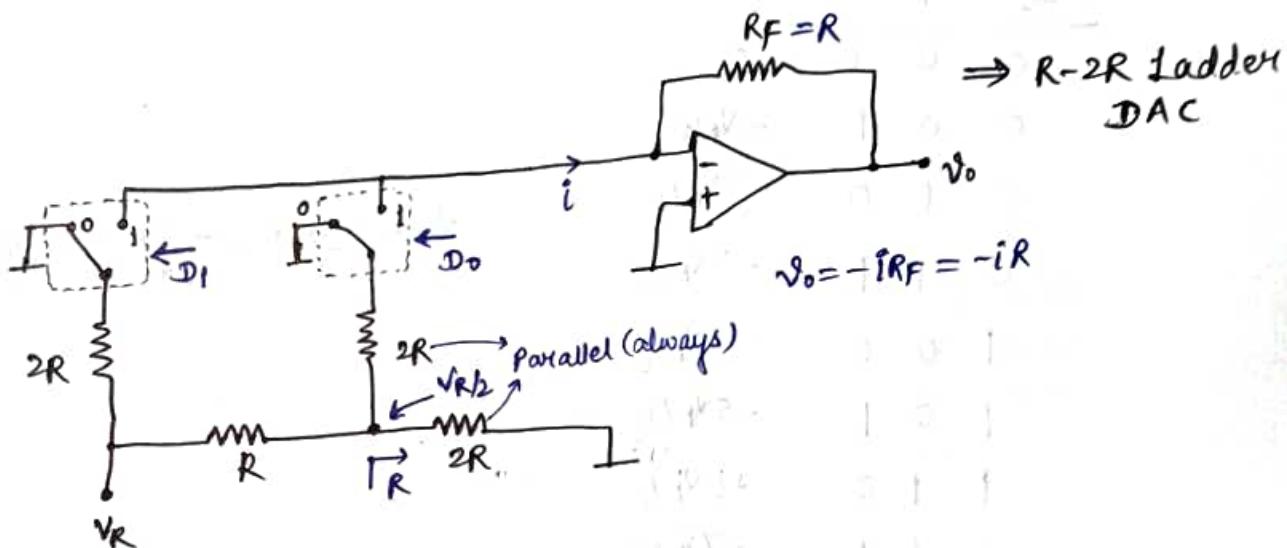

$$D_1 = 0, D_0 = 0 : i = 0$$

$$D_0 = 0, D_1 = 1 : i = \frac{V_R/2}{2R} = \frac{V_R}{4R}$$


$$V_o = -\frac{V_R R_F}{4R} = -\frac{V_R}{4}$$

$$D_0 = 1, D_1 = 0 : i = \frac{V_R}{2R}, V_o = -\frac{V_R}{2}$$

$$D_0 = D_1 = 1 : V_o = -\frac{V_R}{4} - \frac{V_R}{2} = -\frac{3}{4} V_R$$

: DAC scales linearly
with input digital code

3-bit DAC :

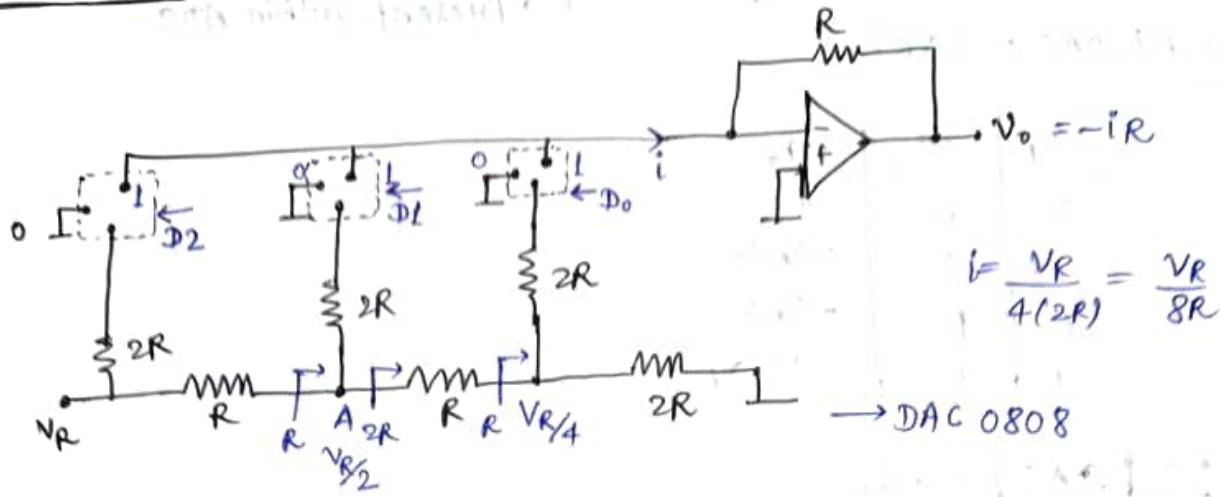

D ₂	D ₁	D ₀	V _o
0	0	0	0
0	0	1	-V _R /8
0	1	0	-2V _R /8
0	1	1	-3V _R /8
1	0	0	-4V _R /8
1	0	1	-5V _R /8
1	1	0	-6V _R /8
1	1	1	-7V _R /8

$$I = \frac{V_R}{4(2R)} = \frac{V_R}{8R}$$

→ DAC 0808

$$V_o = -\frac{V_R}{8}D_0 - \frac{V_R}{4}D_1 - \frac{V_R}{2}D_2$$

4-bit DAC:

$$V_o = -\frac{V_R}{16}D_0 - \frac{V_R}{8}D_1 - \frac{V_R}{4}D_2 - \frac{V_R}{2}D_3$$



n-bit DAC:

$$V_o = -\frac{V_R}{2^n}D_0 - \frac{V_R}{2^{n-1}}D_1 - \dots - \frac{V_R}{4}D_{n-2} - \frac{V_R}{2}D_{n-1}$$

→ Dual slope ADC: $(2^n - 1)T_s$

Flashes Instantaneous

4 bit SAR ADC

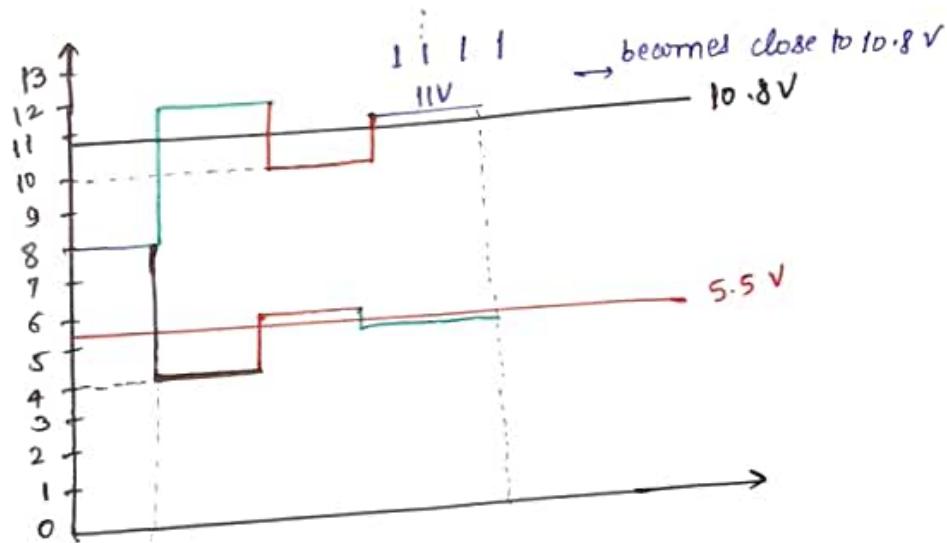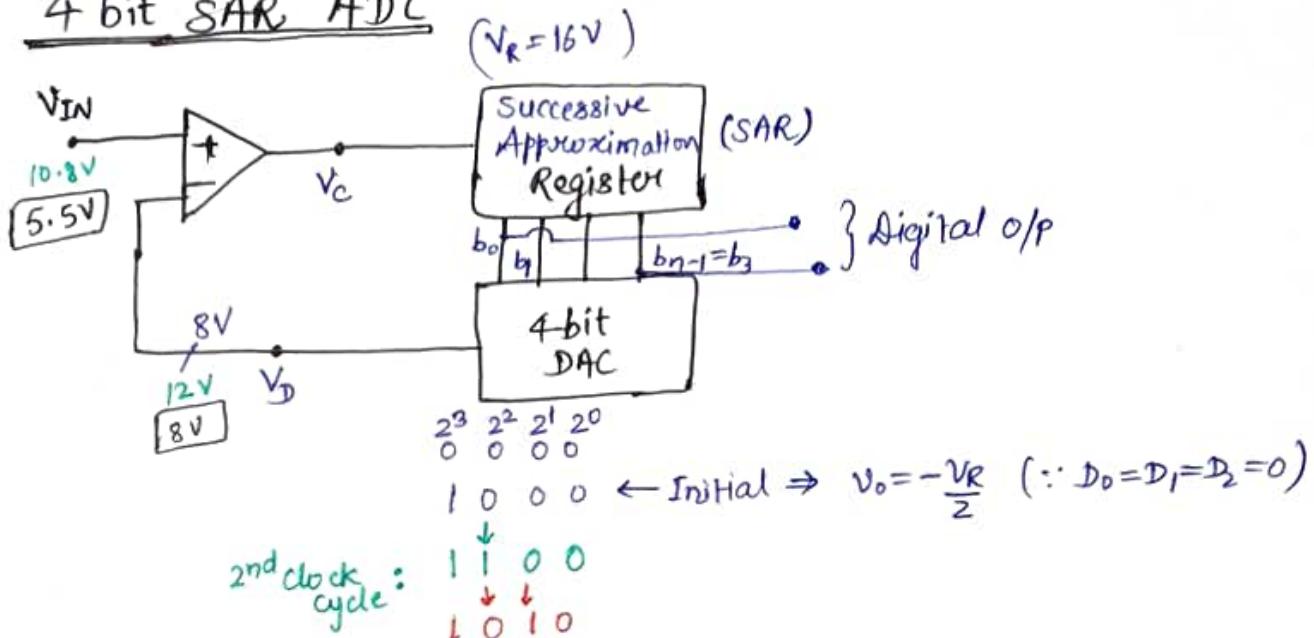

1	0	0	0
0	1	0	0
0	1	1	0
0	1	0	1