

Instrumentation Lab-3Experiment-1SAURABH KUMAR
SC22B146Aim:


- ① Reference current generation unit.
- ② Current measurement technique 1 - Transimpedance Amplifier.
- ③ Current measurement technique 2 - Current Integrator.

Component and Equipments Required:

- ① Voltage Regulator IC - 7805
- ② Opamp IC - 0707
- ③ Switch IC - CD4053
- ④ Resistors
- ⑤ Capacitors
- ⑥ DC power supply
- ⑦ Digital storage oscilloscope
- ⑧ Multimeter
- ⑨ Function generator.

Theory:


Measurement of currents in sub-micro ampere ranges are usually done using Opamp current-to-voltage converter circuits. Opamps are generated operated in voltage amplifier configuration with a passive component (either resistor, capacitor or semiconductor) as the feedback element. Conventional opamp current-to-voltage converter circuits are the transimpedance amplifiers and current generator amplifier having a resistor and capacitor in negative feedback, respectively.

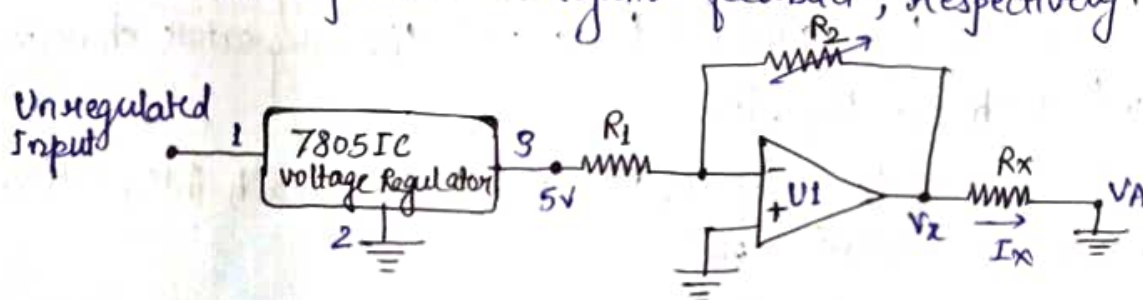circuit for current generation

Generated current, I_x , is given by

$$I_x = -\frac{5R_2}{R_1 R_x} \quad [R_2 \text{ is varied to change } I_x]$$

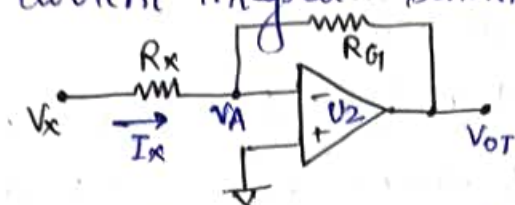This generated current must be sensed using the transimpedance amplifier and current integrator schemes.




Transimpedance Amplifier

The point V_A of the generation circuit is connected to the inverting terminal of opamp U_2 of the transimpedance amplifier. The zero potential required at point for the flow of I_x is achieved using the virtual short condition of the inverting amplifier.

The output of the circuit, V_{OT} , is given by

$$V_{OT} = -I_x R_{G1}$$

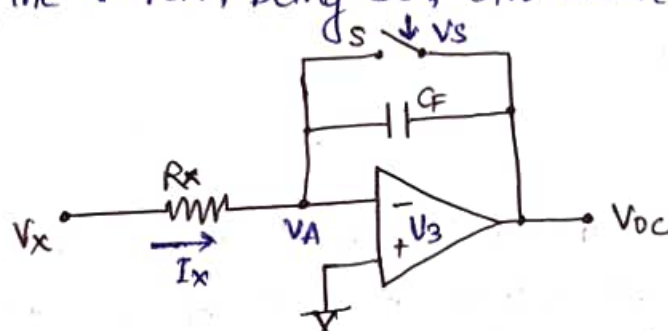The output of the TIA, being DC, can be measured using a multimeter.



Current integrator amplifier

Integrator is periodically discharged by using switch S . Switch S is implemented using the CD4053 multiplexer IC. The generation of switch control signal V_s is generated using the function generator. The duty cycle of V_s needs to be adjusted to adjust the integrator charging time, T_c , and discharge time, T_d .

The peak value of the output, V_{OC} at the end of each integration cycle is given by the relation :

$$V_{OC} = \frac{-I_x T_c}{C_F}$$

Required Details:

- ① Details of the ICs used with their corresponding pin details.
- ② Procedure of experiment.
- ③ Tabular column of experimental results, V_{OT} and V_{OC} , for current range (100 nA, 1 μ A), each heading separated by 50 nA with error and non-linearity.
- ④ Waveforms of V_s and V_{OC} .
- ⑤ Plotted output characteristics of TIA and current integrator.
- ⑥ Inferences.

2. 在 $\triangle ABC$ 中, $\angle A = 60^\circ$, $\angle B = 45^\circ$, $AB = 2$, 求 AC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 60^\circ$, $\angle B = 45^\circ$, $AB = 2$.

由正弦定理得: $\frac{AC}{\sin B} = \frac{AB}{\sin C}$, 即 $\frac{AC}{\sin 45^\circ} = \frac{2}{\sin 75^\circ}$.

∴ $AC = \frac{2 \sin 45^\circ}{\sin 75^\circ} = \frac{2 \times \frac{\sqrt{2}}{2}}{\frac{\sqrt{6} + \sqrt{2}}{4}} = \frac{4\sqrt{2}}{\sqrt{6} + \sqrt{2}} = 2\sqrt{3} - 2$.

∴ AC 的长为 $2\sqrt{3} - 2$.

3. 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$, 求 AC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$.

由正弦定理得: $\frac{AC}{\sin B} = \frac{AB}{\sin C}$, 即 $\frac{AC}{\sin 30^\circ} = \frac{2}{\sin 30^\circ}$.

∴ $AC = 2$.

4. 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$, 求 BC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$.

由正弦定理得: $\frac{BC}{\sin A} = \frac{AB}{\sin C}$, 即 $\frac{BC}{\sin 120^\circ} = \frac{2}{\sin 30^\circ}$.

∴ $BC = \frac{2 \sin 120^\circ}{\sin 30^\circ} = \frac{2 \times \frac{\sqrt{3}}{2}}{\frac{1}{2}} = 2\sqrt{3}$.

∴ BC 的长为 $2\sqrt{3}$.

5. 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$, 求 AC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$.

由正弦定理得: $\frac{AC}{\sin B} = \frac{AB}{\sin C}$, 即 $\frac{AC}{\sin 30^\circ} = \frac{2}{\sin 30^\circ}$.

∴ $AC = 2$.

6. 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$, 求 BC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$.

由正弦定理得: $\frac{BC}{\sin A} = \frac{AB}{\sin C}$, 即 $\frac{BC}{\sin 120^\circ} = \frac{2}{\sin 30^\circ}$.

∴ $BC = \frac{2 \sin 120^\circ}{\sin 30^\circ} = \frac{2 \times \frac{\sqrt{3}}{2}}{\frac{1}{2}} = 2\sqrt{3}$.

∴ BC 的长为 $2\sqrt{3}$.

7. 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$, 求 AC 的长.

解: 在 $\triangle ABC$ 中, $\angle A = 120^\circ$, $\angle B = 30^\circ$, $AB = 2$.

由正弦定理得: $\frac{AC}{\sin B} = \frac{AB}{\sin C}$, 即 $\frac{AC}{\sin 30^\circ} = \frac{2}{\sin 30^\circ}$.


∴ $AC = 2$.

Experiment Simulation Result:

1) R3: 4 k ohms

I: 200 nA

V_{out}: 199.98 mV

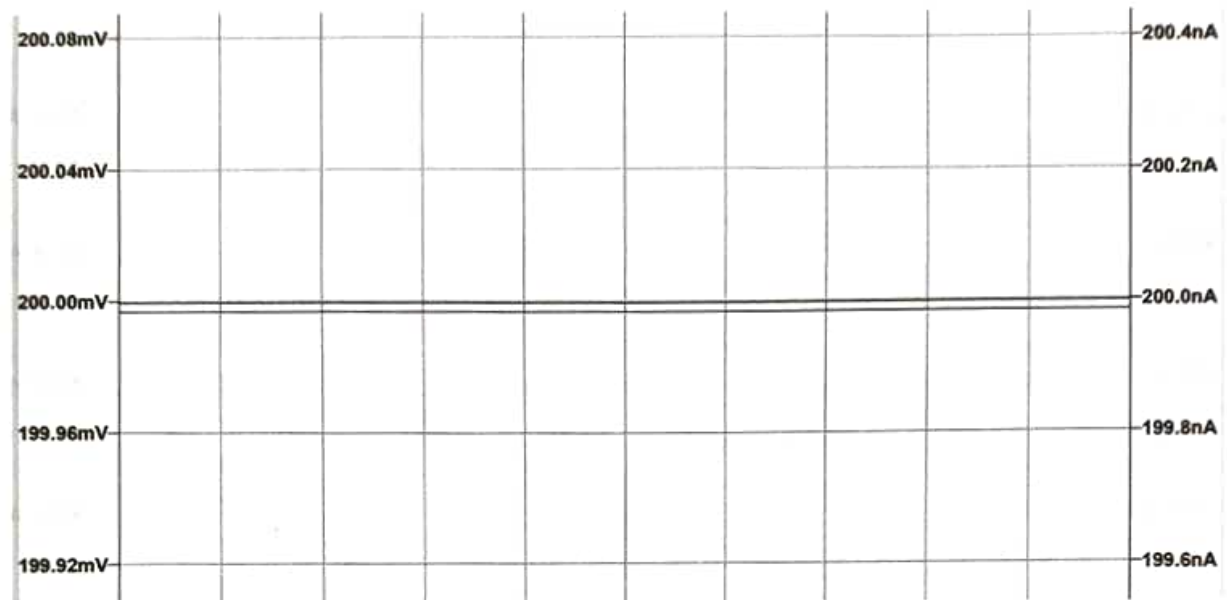


2) R3: 6 k ohms

I: 300 nA


V_{out}: 299.97 mV



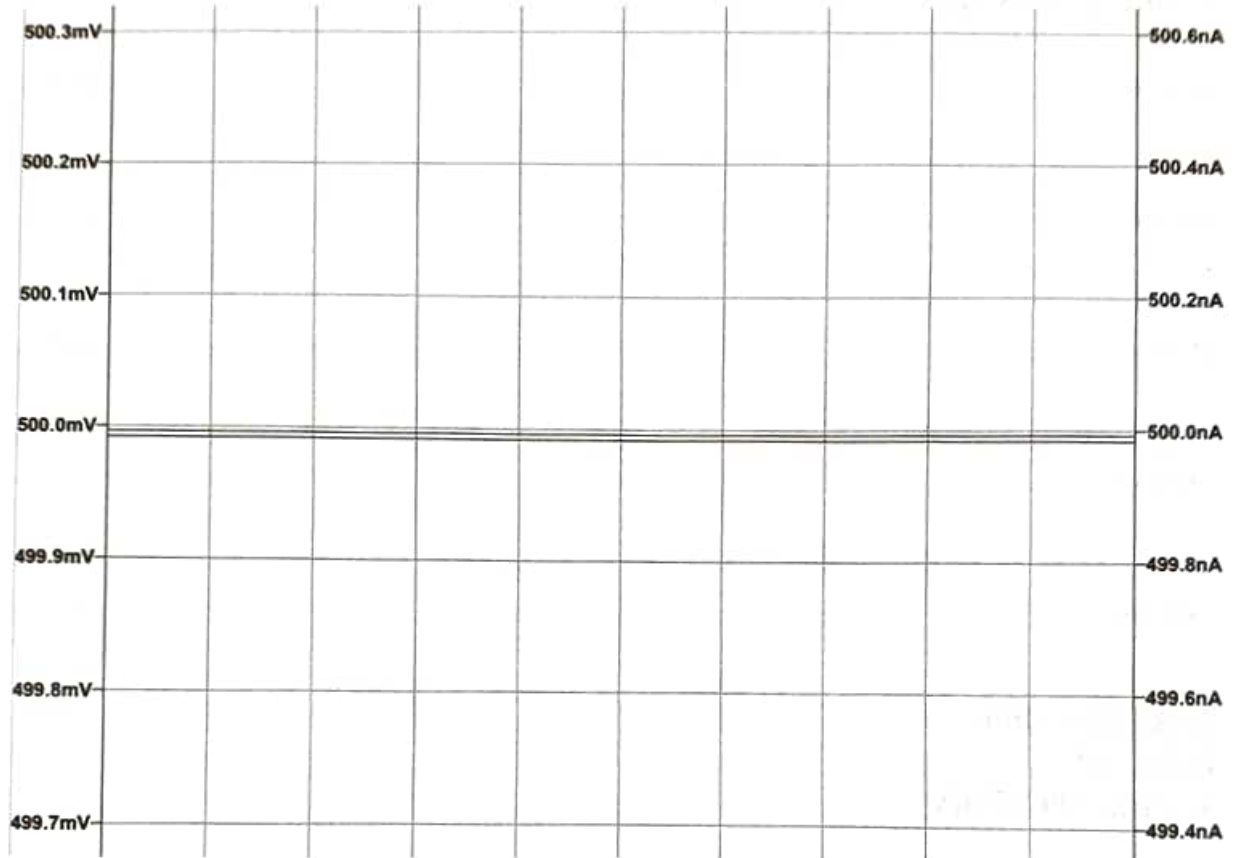3) **R3:** 10 k ohms
I: 500 nA
V_{out}: 499.97 mV




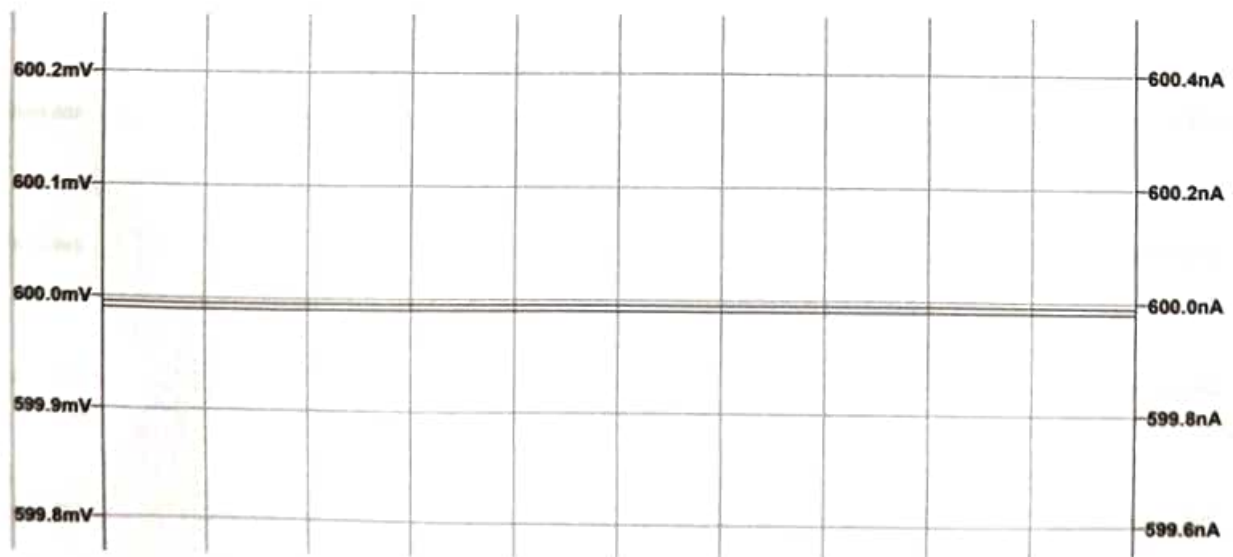4) **R3:** 12 k ohms
I: 600 nA
V_{out}: 599.98 mV




Experiment Simulation:

Transimpedance Amplifier (TIA) Circuit:

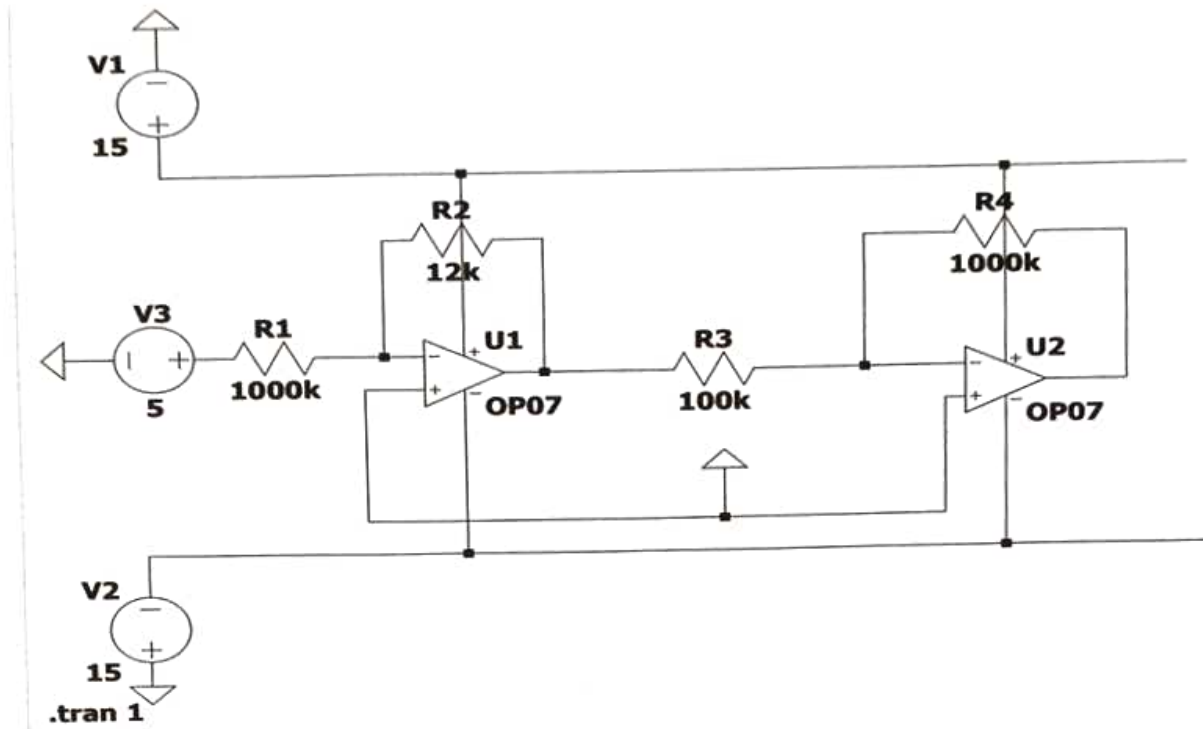

Integrator Circuit:

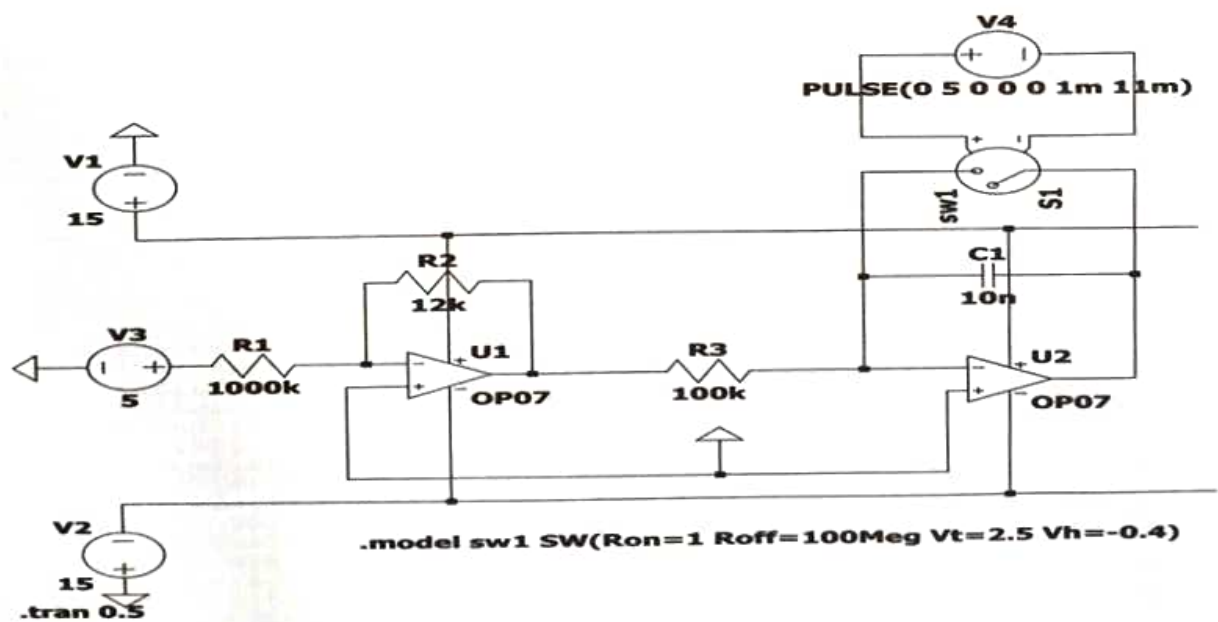

$$T(\mathbf{z}) = \mathbf{z}^T \mathbf{A} \mathbf{z} + \mathbf{b}^T \mathbf{z} + c$$

$$T(\mathbf{z}) = \mathbf{z}^T \mathbf{A} \mathbf{z} + \mathbf{b}^T \mathbf{z} + c$$

$$T(\mathbf{z}) = \mathbf{z}^T \mathbf{A} \mathbf{z} + \mathbf{b}^T \mathbf{z} + c$$

$$T(\mathbf{z}) = \mathbf{z}^T \mathbf{A} \mathbf{z} + \mathbf{b}^T \mathbf{z} + c$$


Results

[NOTE: Unregulated input voltage = $+V_{cc} = 10\text{ V}$]

Reference Current Generator

Resistance R_2 (k Ω)	Measured Current I_x (nA)	Expected I_x (nA)	Error (nA)	%Error	Best-fit I_x (nA)	%Non- linearity (%)
2	89	100	-11	-11	88.383	0.056090909
3	134	150	-16	-10.667	133.442	0.050727273
4	180	200	-20	-10	178.501	0.136272727
5	224	250	-26	-10.4	223.56	0.04
6	269	300	-31	-10.333	268.618	0.034727273
7	314	350	-36	-10.286	313.677	0.029363636
8	359	400	-41	-10.25	358.736	0.024
9	403	450	-47	-10.444	403.794	-0.07218182
10	448	500	-52	-10.4	448.853	-0.07754545
11	493	550	-57	-10.364	493.912	-0.08290909
12	537	600	-63	-10.5	538.971	-0.17918182
13	582	650	-68	-10.462	584.029	-0.18445455
14	628	700	-72	-10.286	629.088	-0.09890909
15	673	750	-77	-10.267	674.147	-0.10427273
16	720	800	-80	-10	719.206	0.072181818
17	765	850	-85	-10	764.264	0.066909091
18	810	900	-90	-10	809.323	0.061545455
19	855	950	-95	-10	854.382	0.056181818
20	900	1000	-100	-10	899.44	0.050909091
21	945	1050	-105	-10	944.499	0.045545455
22	989	1100	-111	-10.091	989.558	-0.05072727
23	1036	1150	-114	-9.913	1034.617	0.125727273

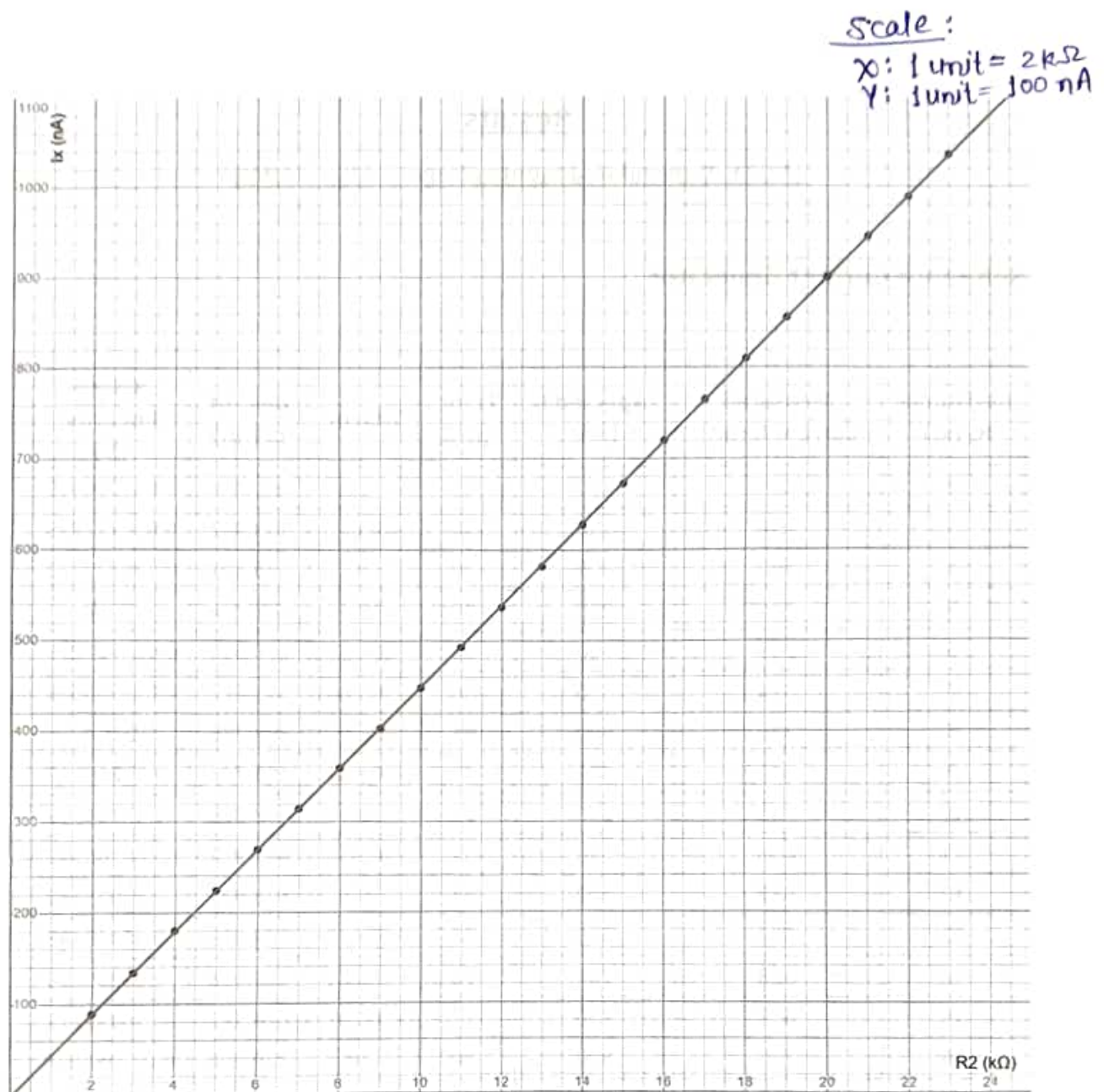Line of best fit: $y = mx + b$; $m = 45.0587$, $b = -1.73405$



Plot: I_x vs R_2 for Reference Current Generator with Line of Best Fit

Current Measurement through Transimpedance Amplifier


Resistance R_2 (k Ω)	Output Voltage V_{OT} (mV)	Measured Current $ I_x $ (nA)	Expected $ I_x $ (nA)	Error (nA)	%Error (%)	Best-fit I_x (nA)	%Non- linearity (%)
2	95	95	100	-5	-5	94.569	0.035916667
3	145	145	150	-5	-3.3333	144.164	0.069666667
4	194	194	200	-6	-3	193.759	0.020083333
5	244	244	250	-6	-2.4	243.355	0.05375
6	293	293	300	-7	-2.3333	292.95	0.004166667
7	343	343	350	-7	-2	342.545	0.037916667
8	392	392	400	-8	-2	392.14	-0.011666667
9	442	442	450	-8	-1.7778	441.735	0.022083333
10	492	492	500	-8	-1.6	491.33	0.055833333
11	540	540	550	-10	-1.8182	540.925	-0.077083333
12	590	590	600	-10	-1.6667	590.521	-0.043416667
13	639	639	650	-11	-1.6923	640.116	-0.093
14	689	689	700	-11	-1.5714	689.711	-0.05925
15	738	738	750	-12	-1.6	739.306	-0.108833333
16	788	788	800	-12	-1.5	788.901	-0.075083333
17	838	838	850	-12	-1.4118	838.496	-0.041333333
18	887	887	900	-13	-1.4444	888.091	-0.090916667
19	937	937	950	-13	-1.3684	937.687	-0.05725
20	986	986	1000	-14	-1.4	987.282	-0.106833333
21	1039	1039	1050	-11	-1.0476	1036.88	0.176916667
22	1088	1088	1100	-12	-1.0909	1086.47	0.127333333
23	1138	1138	1150	-12	-1.0435	1136.07	0.161083333

Line of best fit: $y = mx + b$; $m = 49.5951$, $b = -4.62112$

Scale:

X: 1 unit = $2\text{ k}\Omega$

Y: 1 unit = 100 nA

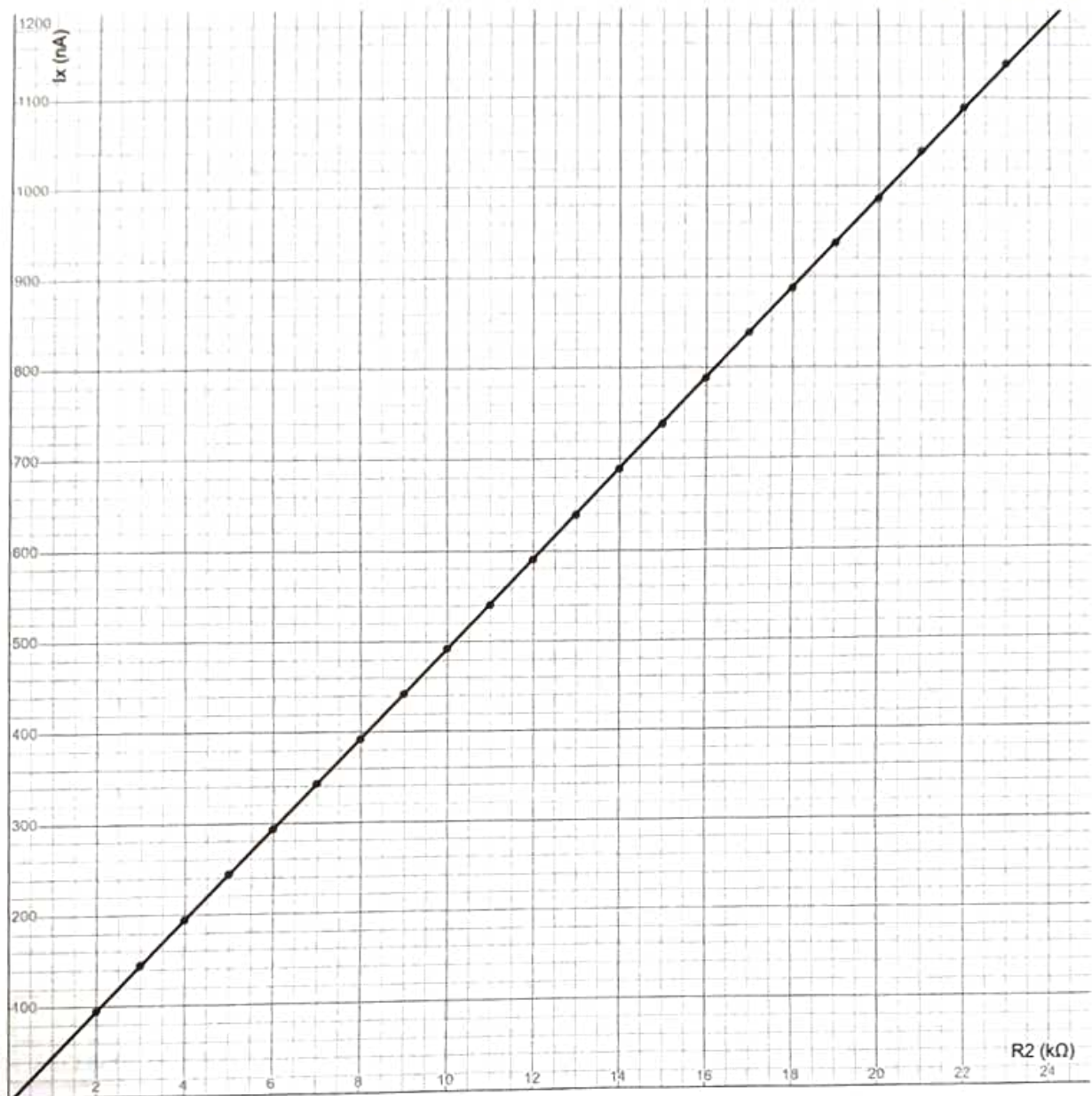

Plot: I_x vs R_2 for TIA with Line of Best Fit

Current Measurement through Current Integrator


Resistance R_2 (k Ω)	Output Voltage V_{OC} (mVpp)	Measured Current $ I_x $ (nA)	Expected $ I_x $ (nA)	Error (nA)	%Error (%)	Best-fit I_x (nA)	%Non- linearity (%)
2	112.5	112.5	100	12.5	12.5	121.137	-0.71975
3	160	160	150	10	6.6667	176.414	-1.36783333
4	230	230	200	30	15	231.691	-0.14091667
5	320	320	250	70	28	286.968	2.75266667
6	360	360	300	60	20	342.245	1.479583333
7	382.5	382.5	350	32.5	9.2857	397.522	-1.25183333
8	437.5	437.5	400	37.5	9.375	452.799	-1.27491667
9	532	532	450	82	18.222	508.076	1.99366667
10	587.5	587.5	500	87.5	17.5	563.353	2.01225
11	627.5	627.5	550	77.5	14.091	618.63	0.73916667
12	660	660	600	60	10	673.907	-1.15891667
13	715	715	650	65	10	729.184	-1.182
14	730	730	700	30	4.2857	784.461	-4.53841667
15	830	830	750	80	10.667	839.738	-0.8115
16	892.5	892.5	800	92.5	11.563	895.015	-0.20958333
17	970	970	850	120	14.118	950.292	1.642333333
18	1030	1030	900	130	14.444	1005.569	2.035916667

Line of best fit: $y = mx + b$; $m = 55.277$, $b = 10.5833$

Scale:

X: 1 unit = 2 k Ω

Y: 1 unit = 100 nA

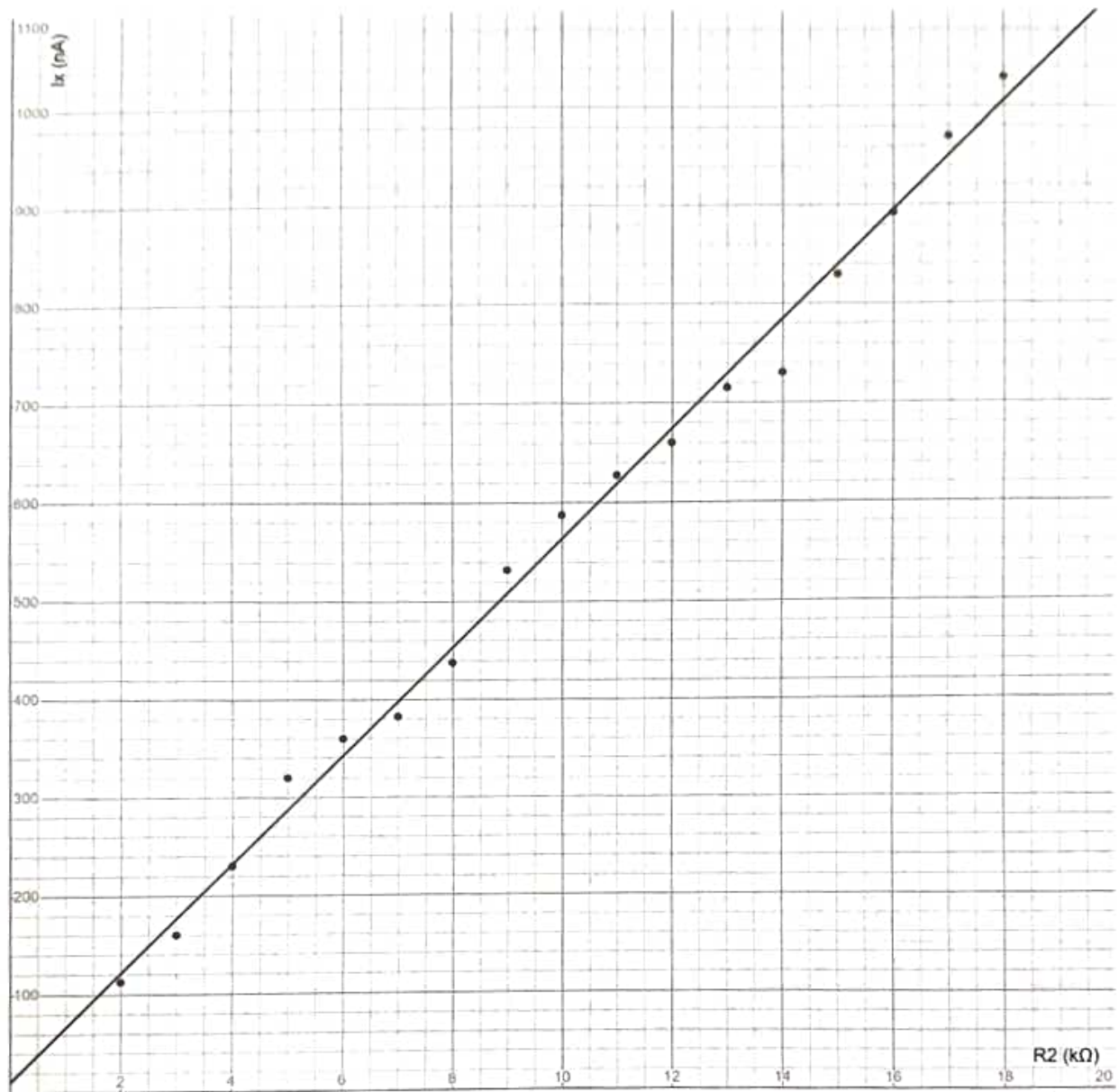

Plot: I_x vs R_2 for Current Integrator with Line of Best Fit