

## Basic Electrical Engineering : Assignment No.2

1. In the circuit shown in Fig.1:
  - (a) Evaluate the complex power absorbed by the impedances  $Z_1$  and  $Z_2$ .
  - (b) Prove that Kirchhoff's voltage law is valid.

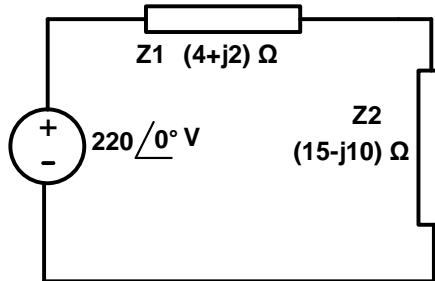


Fig.1

2. In the circuit shown in Fig.2, the  $60 \Omega$  resistor consumes an active power of  $240\text{ W}$ . Find the voltage ' $V$ ' of the AC source and the complex power of each branch of the circuit. What is the complex power delivered by the source? Assume that the current through the  $60 \Omega$  resistor has no phase shift.

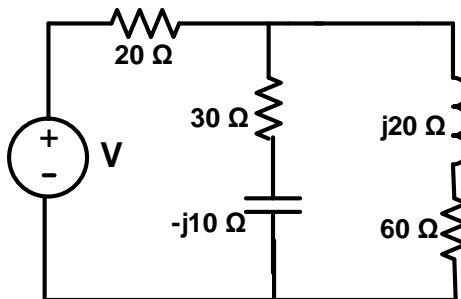


Fig.2

3. In the circuit shown in Fig.3:
  - (a) Determine the power factor as seen by the source.
  - (b) Prove that the complex power supplied by the source is equal to the total complex power absorbed by the circuit.

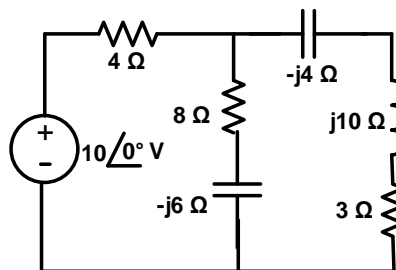


Fig.3