

Digital Electronics Verilog Lab 5

Submitted By:

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)


LAB SHEET

Question No. 1 Design a state machine for detecting sequence "0110" using Moore and Mealy state machine

Sol: Moore Machine:

State Diagram:

Moore Machine: 0110

 

Code:

```
module detect_0110_Moore(clk,reset,In,Out);
```

```
    input clk, reset, In;
```

```
    output reg Out;
```

```
    parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100;
```

```
    reg[2:0] CurrentState,NextState;
```

```
    always@(posedge clk)
```

```
    begin
```

```
        if(reset)
```

```
            CurrentState = S0;
```

```
        else
```

```
            CurrentState = NextState;
```

```
    end
```

```
    always@(CurrentState, In)
```

```
    begin
```

```
        case(CurrentState)
```

```
        S0:begin
```

```
            if(!In) NextState = S1;
```

```
            else NextState = S0;
```

```

end
S1:begin
  if(!In) NextState = S1;
  else NextState = S2;
end
S2:begin
  if(!In) NextState = S1;
  else NextState = S3;
end
S3:begin
  if(!In) NextState = S4;
  else NextState = S0;
end
S4:begin
  if(!In) NextState = S1;
  else NextState = S0;
end
default:NextState = S0;
endcase
end

```


```

always@(CurrentState)
begin
  case(CurrentState)
  S0: Out = 0;
  S1: Out = 0;
  S2: Out = 0;
  S3: Out = 0;
  S4: Out = 1;
  endcase
end

```


endmodule

Schematic:

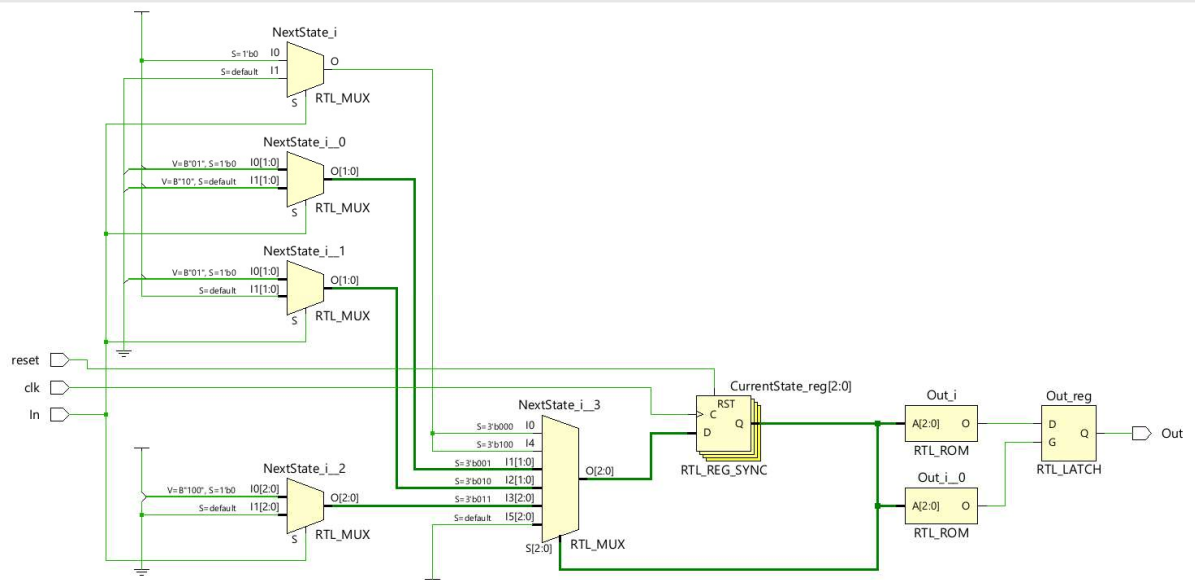


Simulation using TestBench:

Input Given: 01100100011011010

 


Synthesis:

 

Mealy Machine:

State Diagram:

 

Code:

```

module detect_0110_Mealy(clk,reset,in,Out);
  input clk, reset, in;

```

```

output reg Out;

parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011;
reg[2:0] CurrentState,NextState;

always@(posedge clk)
begin
if(reset)
    CurrentState = S0;
else
    CurrentState = NextState;
end

always@(CurrentState, In)
begin
case(CurrentState)
S0:begin
    if(!In)
        begin
            NextState = S1;
            Out = 0;
        end
    else
        begin
            NextState = S0;
            Out = 0;
        end
    end
S1:begin
    if(!In)
        begin
            NextState = S1;
            Out = 0;
        end
    else
        begin
            NextState = S2;
            Out = 0;
        end
    end
S2:begin
    if(!In)
        begin
            NextState = S1;
            Out = 0;
        end
    else
        begin
            NextState = S3;
            Out = 0;
        end
    end
S3:begin
    if(!In)
        begin
            NextState = S0;
            Out = 1;
        end
    else
        begin
            NextState = S0;
            Out = 0;
        end
    end
end

```

```

        end
    end
    default:NextState = S0;
endcase
end

```

```

Endmodule


```

```

endmodule

```

Schematic:

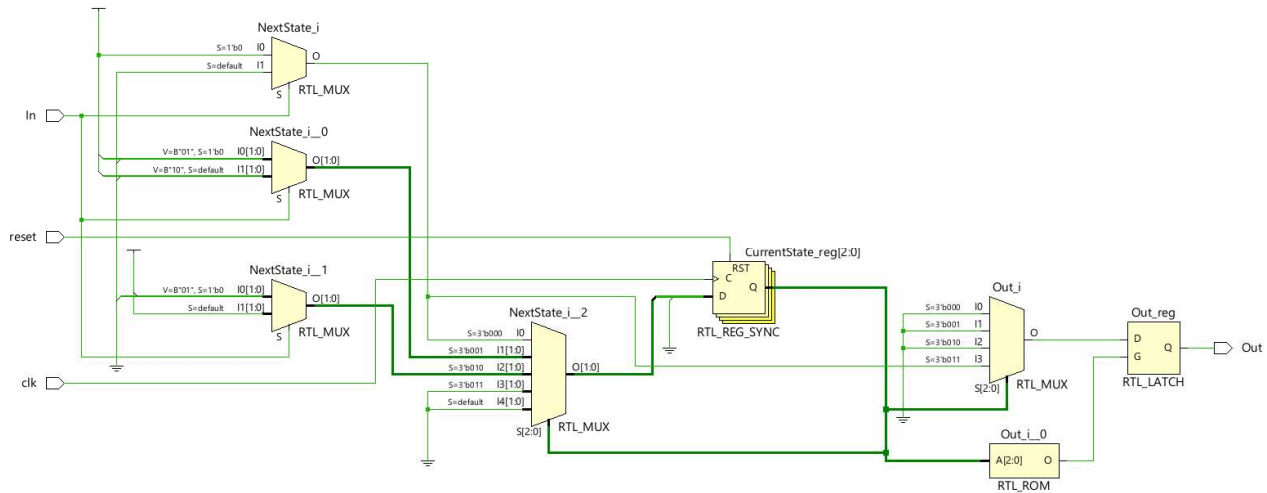


Simulation using TestBench:

Input Given: 01100100011011010



Synthesis:

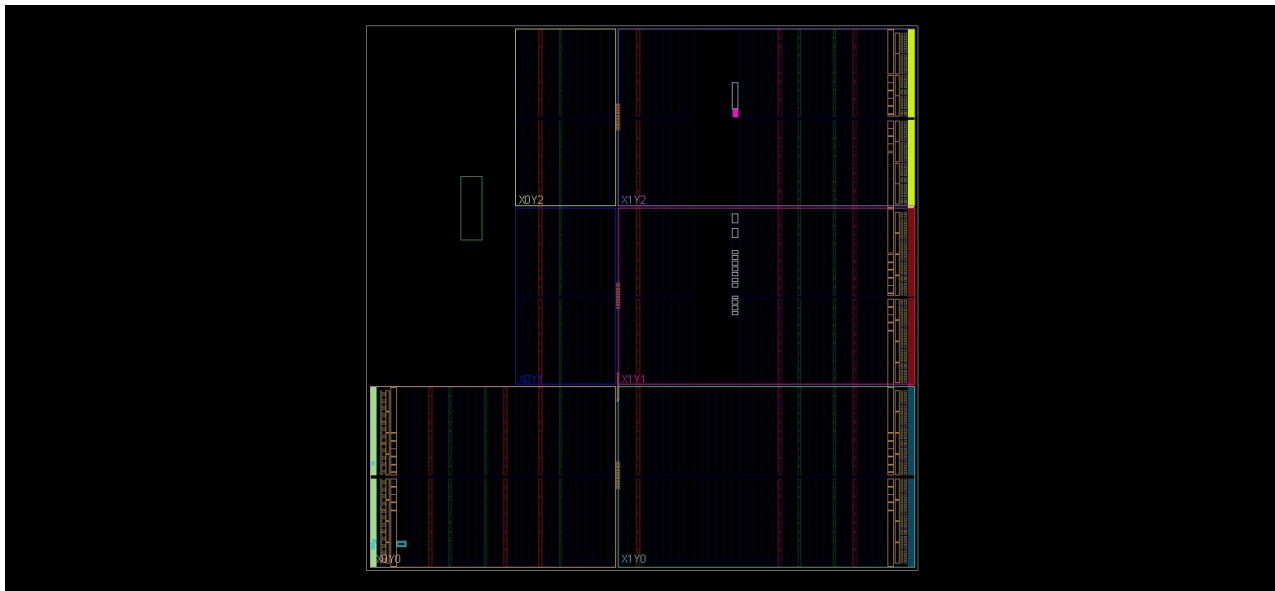

Question No. 2 Design a 4-bit Johnson counter and implement on FPGA.


Sol: Implementation using D Flip Flop (DFF Code):

```
module DFF(clk,reset,D,Q,Qbar);
    input D,clk,reset;
    output reg Q, Qbar;
```

```
    always@(posedge clk)
    begin
        if(reset)
            begin
                Q <= 0;
                Qbar <= 1;
            end
        else
            begin
                Q <= D;
                Qbar <= ~D;
            end
        end
    end
```

```
end
endmodule
```

4-bit Johnson counter

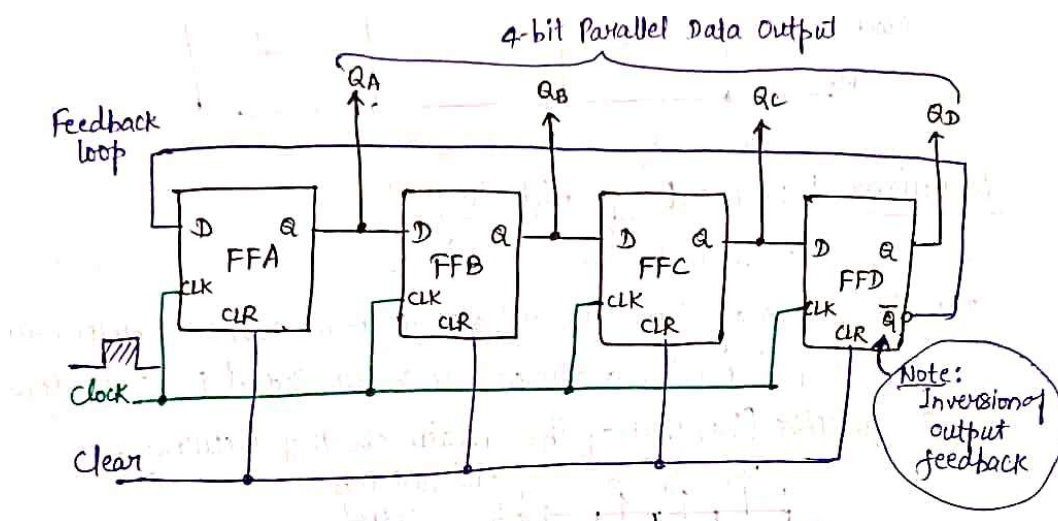

Code:


```

module JohnsonCount(clk,clear,Out,QA,QB,QC,QD,QAbar,QBbar,QCbar,QDbar);
    input clk,clear;
    output Out;
    output QA,QB,QC,QD,QAbar,QBbar,QCbar,QDbar;
    wire qa,qb,qc,qd;


    assign QA = qa, QB = qb, QC = qc, QD = qd;
    assign Out = (QAbar & QDbar);
    DFF reg1(clk,clear,QDbar,qa,QAbar);
    DFF reg2(clk,clear,qa,qb,QBbar);
    DFF reg3(clk,clear,qb,qc,QCbar);
    DFF reg4(clk,clear,qc,qd,QDbar);
endmodule

```


Schematic:

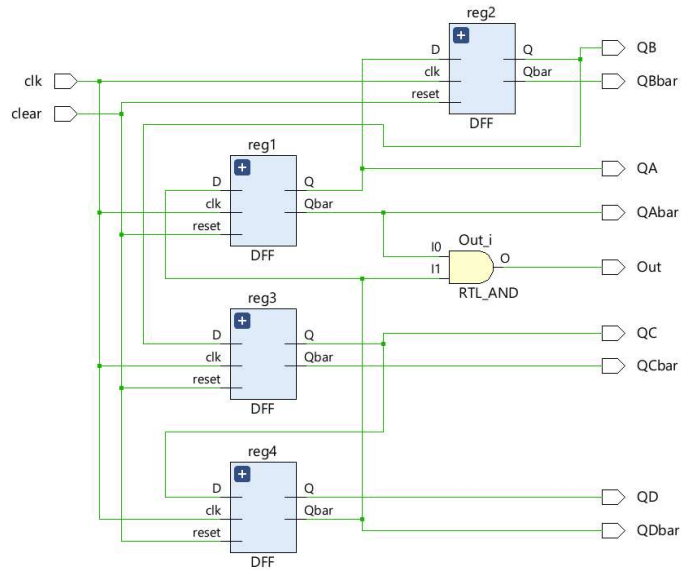

Simulation using TestBench:

 


Synthesis:

 

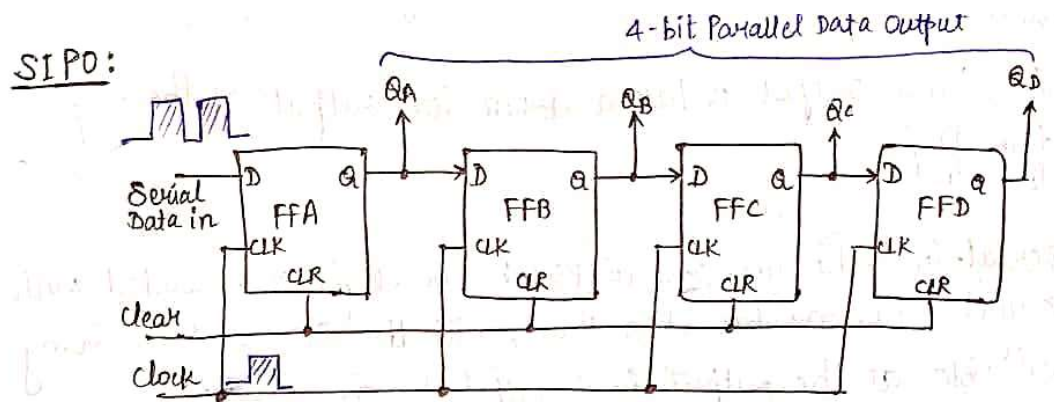Question No. 3 Design a 4-bit serial-in-parallel-out shift register and implement on FPGA

Sol: 4-bit Serial-in parallel-out (SIPO) shift register:




Code:

```
module SIPO(clk,clear,In,QA,QB,QC,QD,QAbar,QBbar,QCbar,QDbar);
    input clk,clear,In;
    output QA,QB,QC,QD,QAbar,QBbar,QCbar,QDbar;
    wire qa,qb,qc,qd;


    assign QA = qa, QB = qb, QC = qc, QD = qd;
    DFF reg1(clk,clear,In,qa,QAbar);
    DFF reg2(clk,clear,qa,qb,QBbar);
    DFF reg3(clk,clear,qb,qc,QCbar);
    DFF reg4(clk,clear,qc,qd,QDbar);
endmodule
```

Schematic:

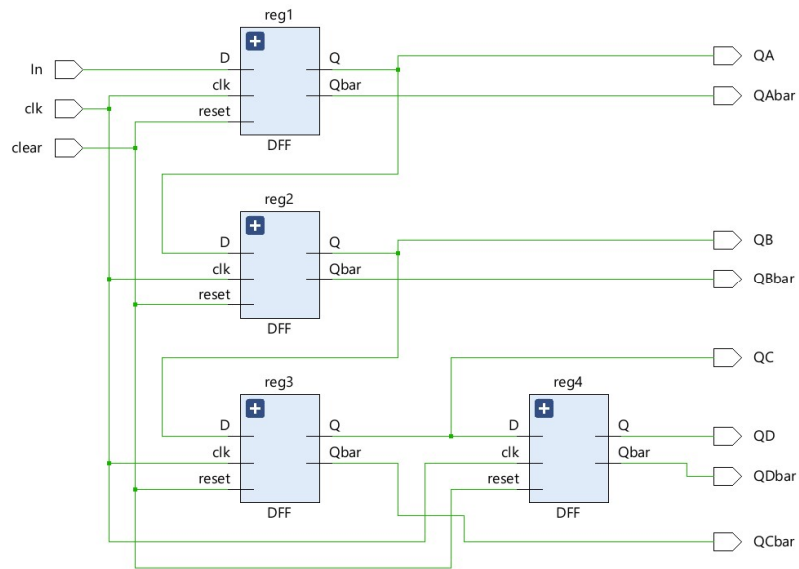

Simulation using TestBench:

Input Given: 01100100011011010

 

Synthesis:

