

Instrumentation Lab-3All-Pass Filter and Phase  
Detector Schemes

19-03-2023

SAURABH KUMAR  
Sc22B146Aim :

- ① Design and implement an all-pass filter and verify its response.
- ② Detect phase difference between two signals using a phase detector circuit.

Components and Equipments Required :

- ① DC power supply.
- ② Function generator.
- ③ Digital Storage Oscilloscope.
- ④ Opamp IC OP07
- ⑤ Comparator IC LM311
- ⑥ XOR IC 7486
- ⑦ Resistors
- ⑧ Capacitors

Theory :

An all-pass filter is that which passes all frequency components of the input signal without attenuation but provides predictable phase shifts for different frequencies of the input signals.


The phase angle  $\phi$  is given by

$$\phi = 2 \tan^{-1} (2\pi f CR)$$

Phase detector circuit is used to detect phase difference between two sinusoidal signals. It consists of two comparators followed by an XOR gate and a low pass filter.

The low-pass filter cut-off frequency should be less than 5 Hz.  
The output voltage is given by

$$V_{avg} = \frac{V_m \theta}{\pi}$$

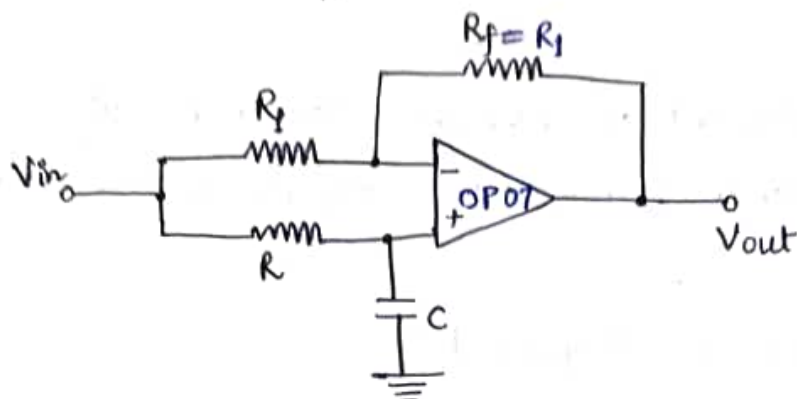

### Procedure:

#### Part A:


- ① Design the all-phase circuit such that it can offer a phase difference of  $90^\circ$  to a sine wave input of frequency 500 Hz.
- ② Implement the above circuit in a breadboard. Note the actual phase delay b/w the input and output waves.
- ③ Suitably change the design of the circuit (variable resistor) so that the phase delay can be changed to  $30^\circ$ ,  $60^\circ$ ,  $120^\circ$  and  $150^\circ$ .  
Plot the actual vs. calculated reading and find the error.

#### Part B:

- ① Design the phase detector circuit for input sine waves of frequency 500 Hz.
- ② Implement the comparators (using LM311 IC) and ensure the compatibility of their output is compatible with TTL standard. Observe the plot of comparators outputs for typical inputs.
- ③ Include the XOR gate and filter circuit in the breadboard. Vary the phase delays ( $\theta$ ) between  $V_1$  and  $V_2$  in steps of  $15^\circ$  and measure the output signal of the filter ( $V_{avg}$ ) for each case using a digital multimeter.

[Use that all-pass filter circuit implemented in part ① to obtain] ③  
multiple phase delays.


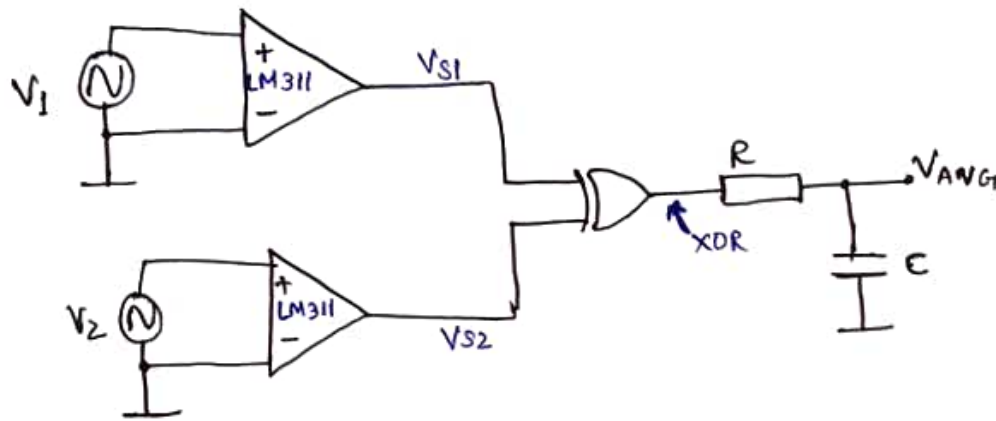
- ⊕ Plot the output signal,  $V_{avg}$ , with  $\theta$  and determine the error.  
Calculate the non-linearity of the phase detector with respect to the best-fit straight line.








## Experimental Simulations:

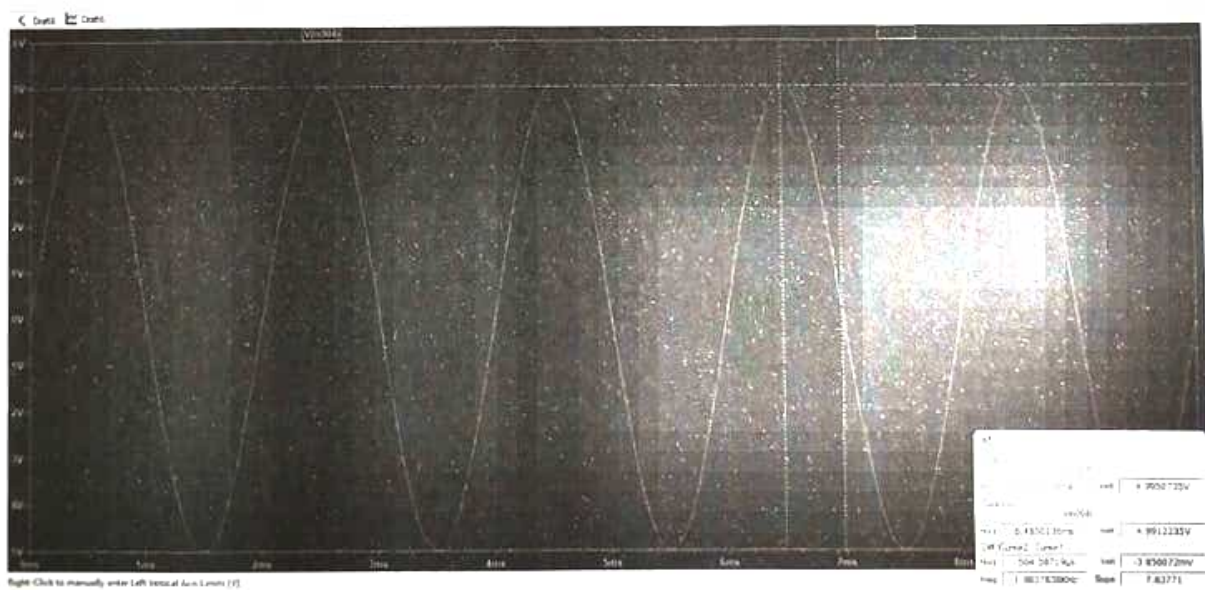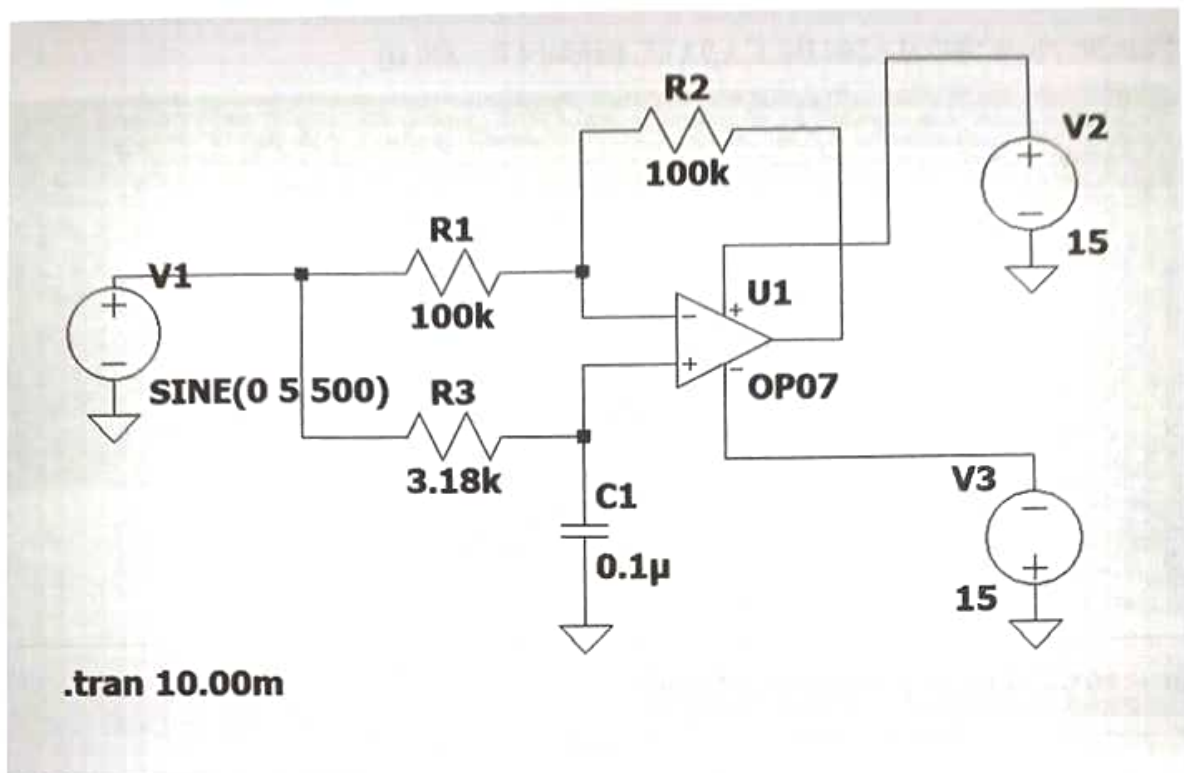

Change in time ( $\Delta t$ ) = 504.08  $\mu s \Rightarrow \varphi = \omega \Delta t = 90.699^\circ$   
 Expected value =  $90^\circ$ ; error = 0.0493%

**Plot: 30° Phase Shift ( $f = 500 \text{ Hz}$ ,  $C = 0.1 \mu\text{F}$ , standard  $R = 820 \Omega$ )**

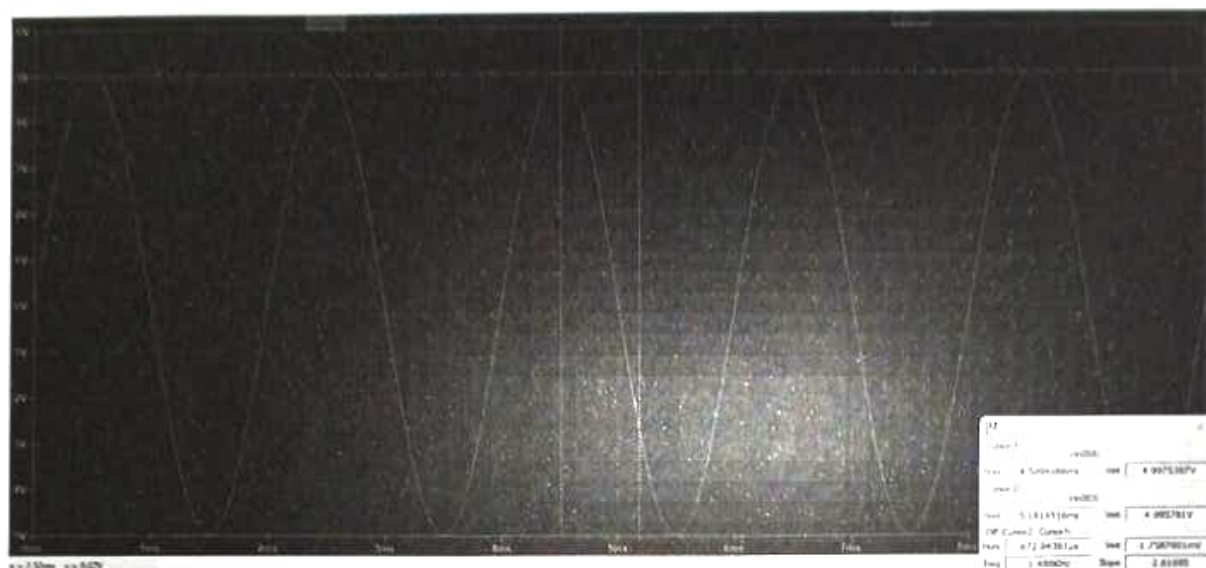**Plot: 120° Phase Shift ( $f = 500 \text{ Hz}$ ,  $C = 0.1 \mu\text{F}$ , standard  $R = 5.6 \text{ k}\Omega$ )**




**Plot: 120° Phase Shift ( $f = 500 \text{ Hz}$ ,  $C = 0.1 \mu\text{F}$ , standard  $R = 5.6 \text{ k}\Omega$ )**

$$\Delta t = 672.0430 \mu\text{s} \Rightarrow \varphi = \omega \Delta t = 0.6709547\pi \text{ rad} = 120.96^\circ$$

Expected value @  $5.6 \text{ k}\Omega = 120.771289^\circ$ ; error (expected value) = 0.163%

Error (desired value) = 0.6432%

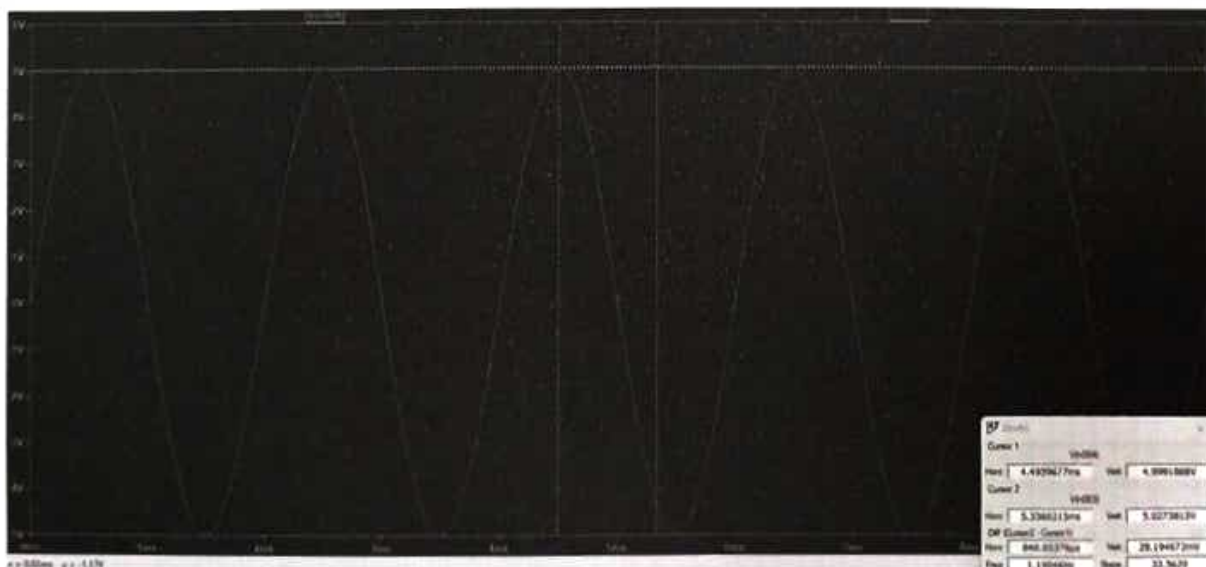**Plot: 150° Phase Shift ( $f = 500 \text{ Hz}$ ,  $C = 0.1 \mu\text{F}$ , standard  $R = 12 \text{ k}\Omega$ )**




**Plot: 150° Phase Shift ( $f = 500 \text{ Hz}$ ,  $C = 0.1 \mu\text{F}$ ,  $R = 12 \text{ k}\Omega$ )**


$$\Delta t = 840.0536 \mu\text{s} \Rightarrow \varphi = \omega \Delta t = 151.209^\circ$$

Expected value @  $12 \text{ k}\Omega = 150.288^\circ$ ; error (expected value) = 0.6132%

Error (desired value) = 1.2897%

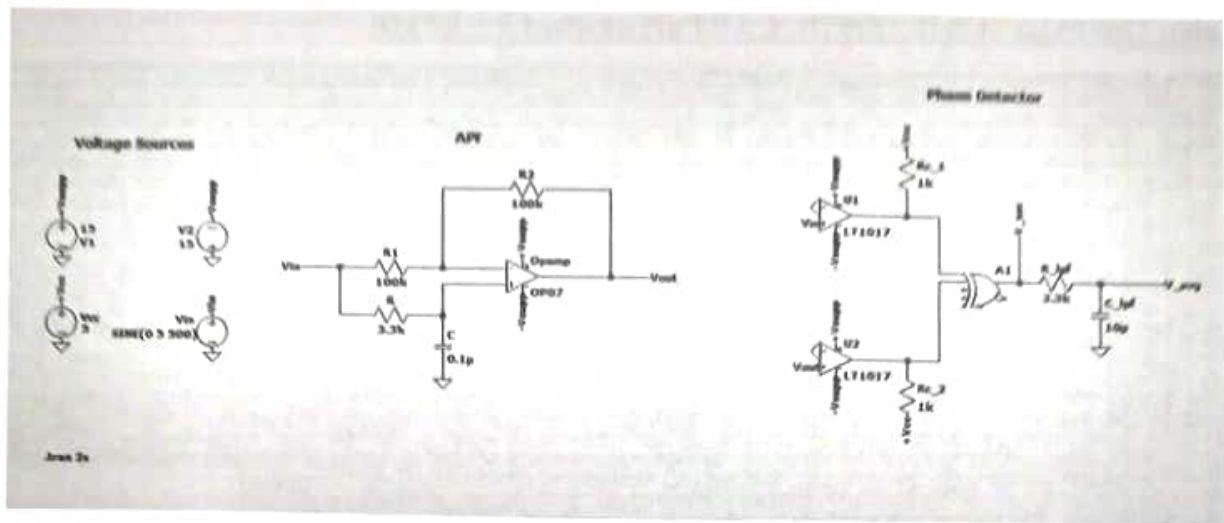

$$\Phi = 90^\circ$$

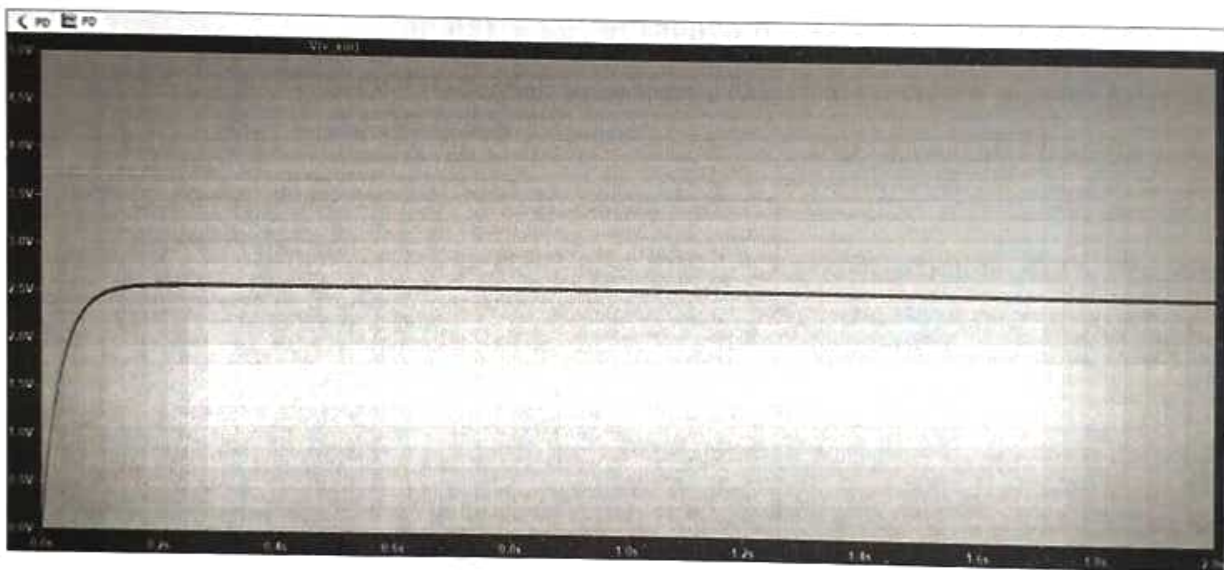


Plot: v\_xor (green) and v\_avg (blue) for 90° phase shift

Plot: Close-up of XOR output (v\_xor) for 90° phase shift

Logic HIGH of XOR,  $V_H = 5\text{ V}$



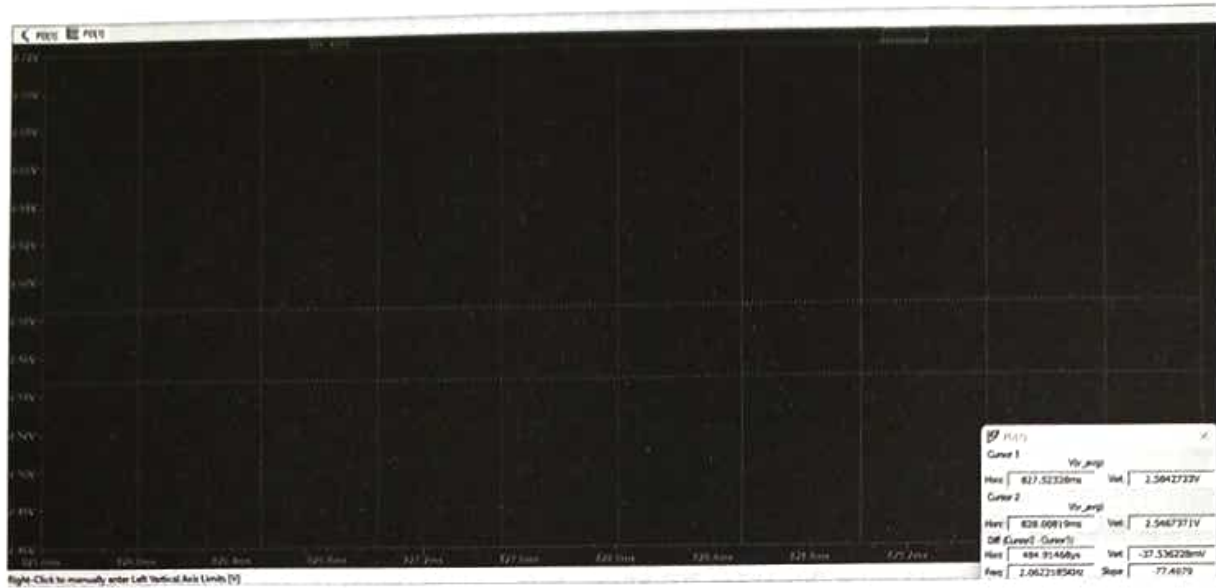

**Plot: Close-up of low-pass filter average output (v\_avg) for 90° phase shift**

$$V_{avg} = \frac{2.5842 + 2.546}{2} = 2.5655 \text{ V} \approx 2.5656 \text{ V}$$

Then,

$$V_{avg} = \frac{V_H \phi}{\pi} \Rightarrow \phi = \frac{V_{avg} \pi}{V_H} = 0.5131 \pi \text{ rad} = 92.36^\circ$$


Expected value @ APF R = 3.3 kΩ = 92.066° (calculated) / 92.4137° (APF o/p)

So, error (calculated value) = 0.3194%;


Error (APF o/p) = -0.0580%; and

Error (desired value) = 2.6223%

$$\Phi = 30^\circ$$

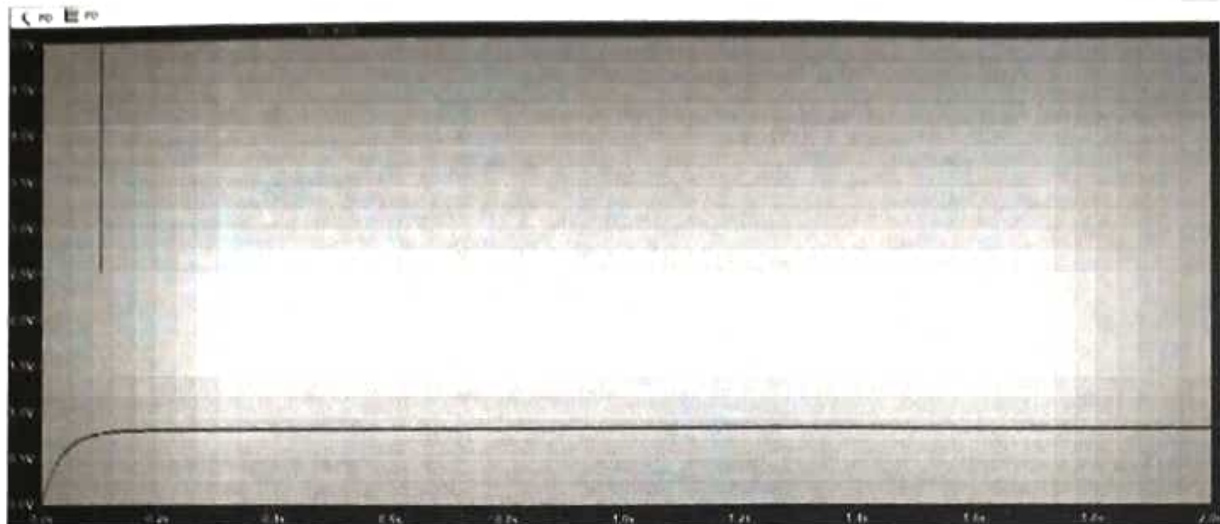

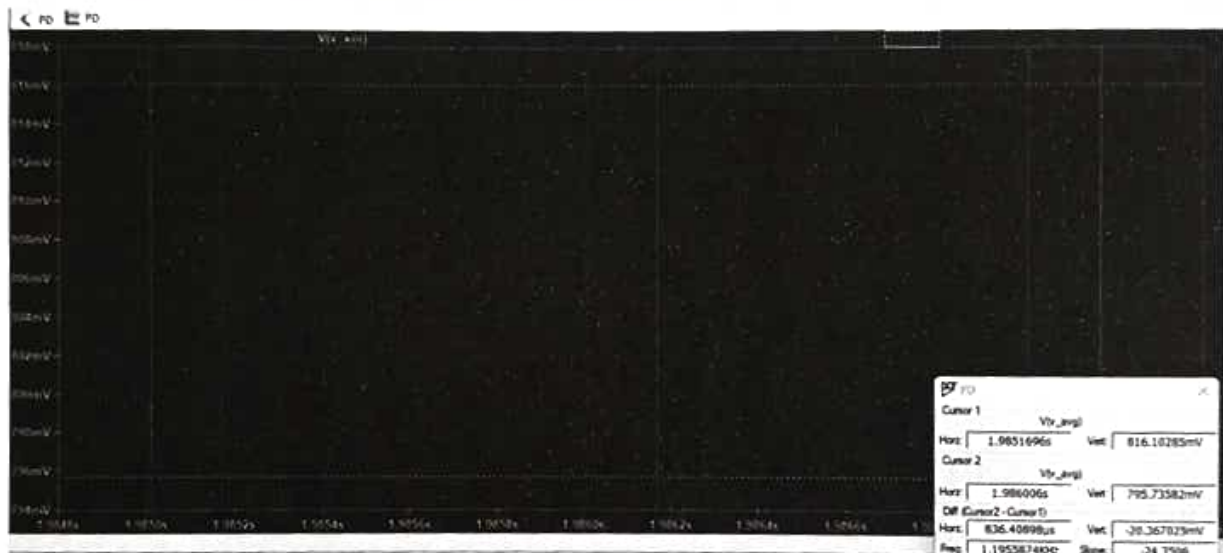Plot: v\_xor (green) and v\_avg (blue) for 30° phase shift



Plot: Close-up of low-pass filter average output (v\_avg) for 30° phase shift

$$V_{avg} = \frac{816.10285 + 795.7352}{2} = 805.919025 \text{ mV}$$


Then,

$$V_{avg} = \frac{V_H \phi}{\pi} \Rightarrow \phi = \frac{V_{avg} \pi}{V_H} = 0.1612 \pi \text{ rad} = 29.0131^\circ$$


Expected value @ APF R = 820  $\Omega$  = 28.892° (calculated) / 29.1386° (APF o/p)

So, error (calculated value) = 0.4191%;

$\Phi = 60^\circ$

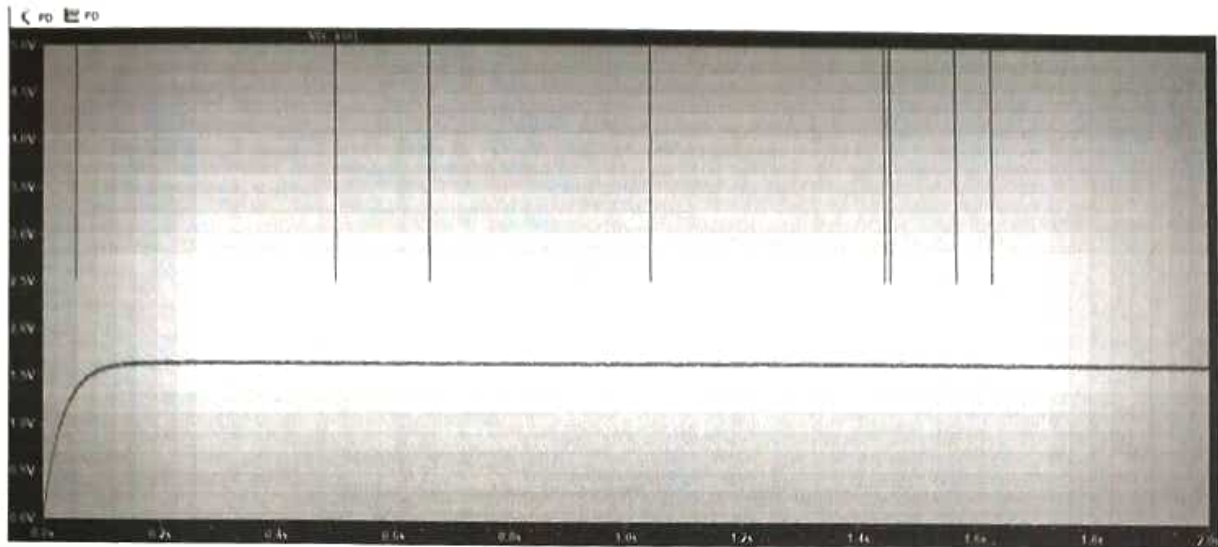

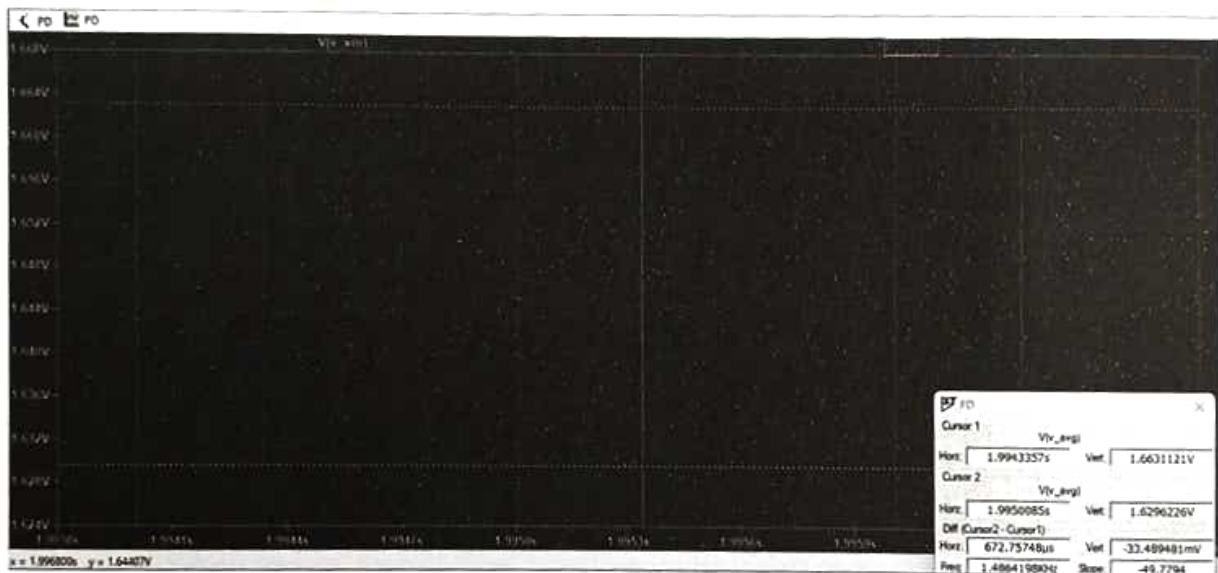**Plot:  $v_{xor}$  (green) and  $v_{avg}$  (blue) for  $60^\circ$  phase shift**



**Plot: Close-up of low-pass filter average output ( $v_{avg}$ ) for  $60^\circ$  phase shift**

$$V_{avg} = \frac{1.6631121 + 1.6296226}{2} = 1.64636735 \text{ V}$$


Then,

$$V_{avg} = \frac{V_H \phi}{\pi} \Rightarrow \phi = \frac{V_{avg} \pi}{V_H} = 0.3293 \pi \text{ rad} = 59.2692^\circ$$


Expected value @ APF R = 1.8 k $\Omega$  = 58.975° (calculated) / 59.1652° (APF o/p)

So, error (calculated value) = 0.4989%;

$\Phi = 120^\circ$

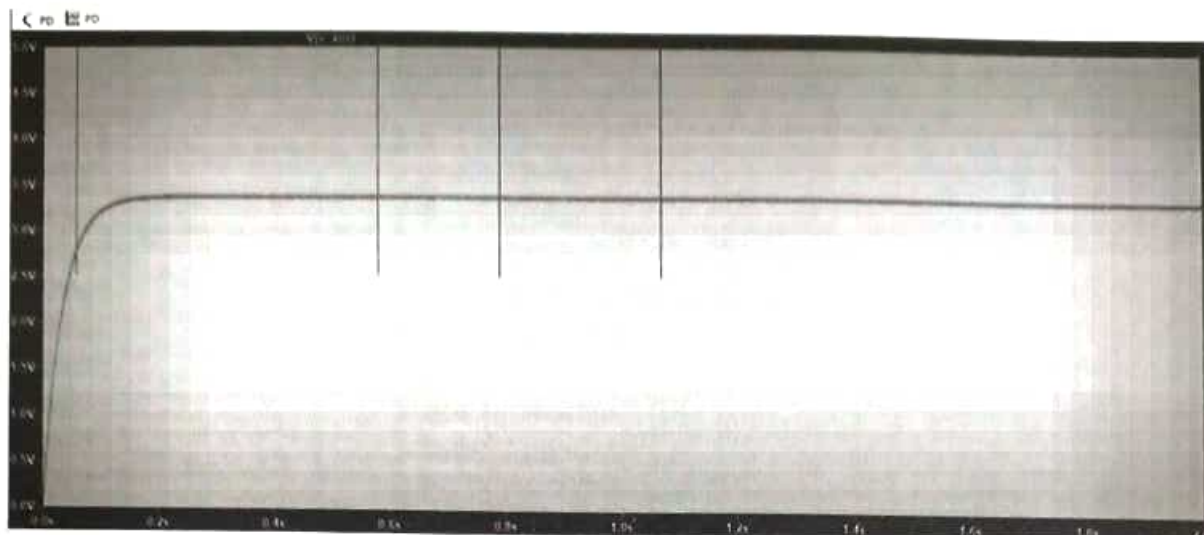

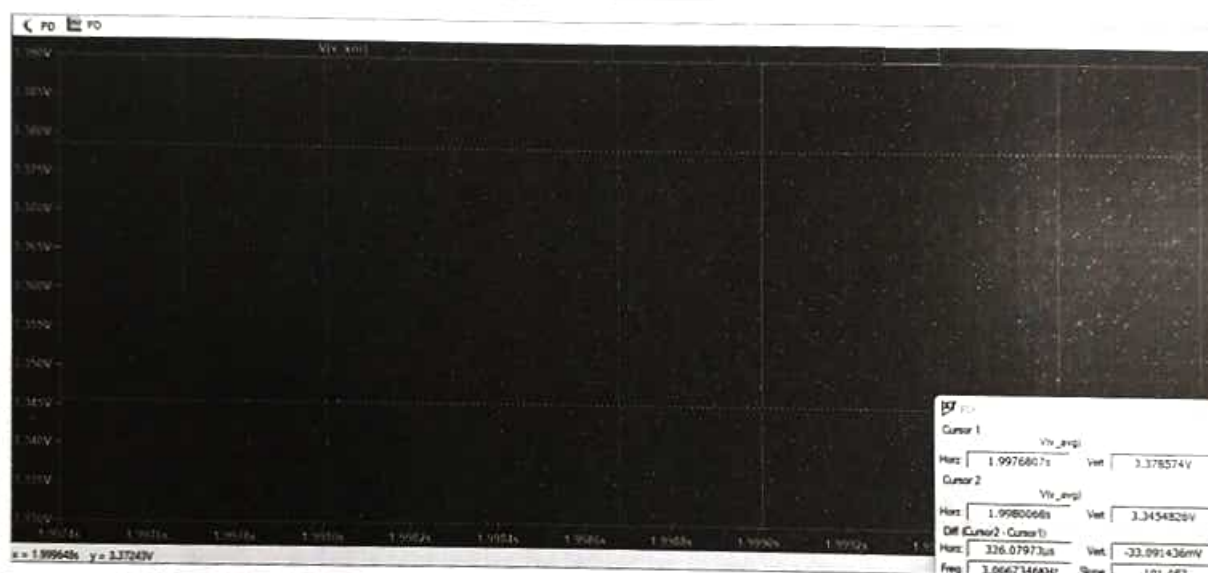Plot: v\_xor (green) and v\_avg (blue) for 120° phase shift



Plot: Close-up of low-pass filter average output (v\_avg) for 120° phase shift

$$V_{avg} = \frac{3.378574 + 3.3454826}{2} = 3.3620283 \text{ V}$$

Then,

$$V_{avg} = \frac{V_H \phi}{\pi} \Rightarrow \phi = \frac{V_{avg} \pi}{V_H} = 0.67240566 \pi \text{ rad} = 121.0330^\circ$$

Expected value @ APF R = 5.6 kΩ = 120.771289° (calculated) / 120.771846° (APF o/p)


So, error (calculated value) = 0.2167%;

Error (APF o/p) = 0.2163%; and


Error (desired value) = 0.8808%

$\Phi = 150^\circ$



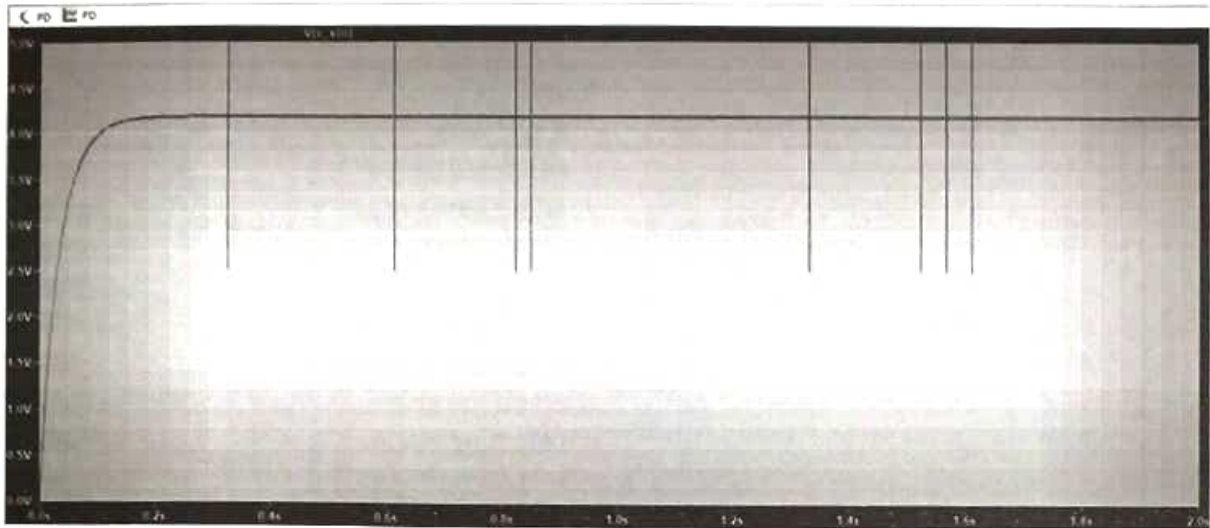

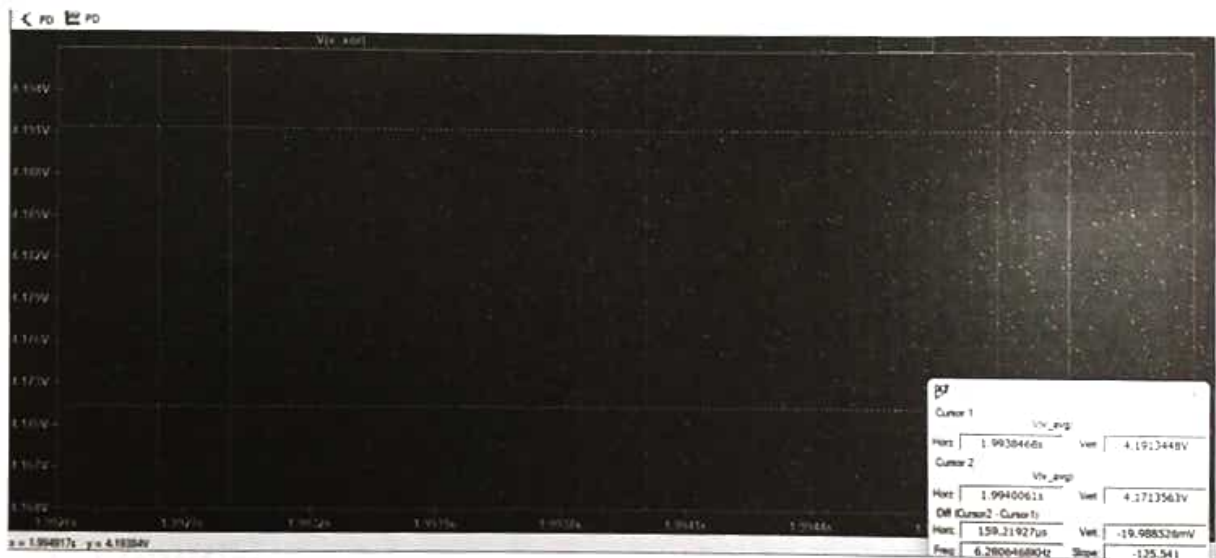Plot: v xor (green) and v avg (blue) for 150° phase shift



Plot: Close-up of low-pass filter average output (v\_avg) for 150° phase shift

$$V_{avg} = \frac{4.1913448 + 4.1713563}{2} = 4.18135055 \text{ V}$$

Then,

$$V_{avg} = \frac{V_H \phi}{\pi} \Rightarrow \phi = \frac{V_{avg} \pi}{V_H} = 0.8363 \pi \text{ rad} = 150.5286^\circ$$


Expected value @ APF R = 3.3 kΩ = 150.288° (calculated) / 151.9481° (APF o/p)

So, error (calculated value) = 0.1601%;

Error (APF o/p) = -0.9342%; and

Error (desired value) = 0.3524%

**Non-linearity of Phase Detector:**

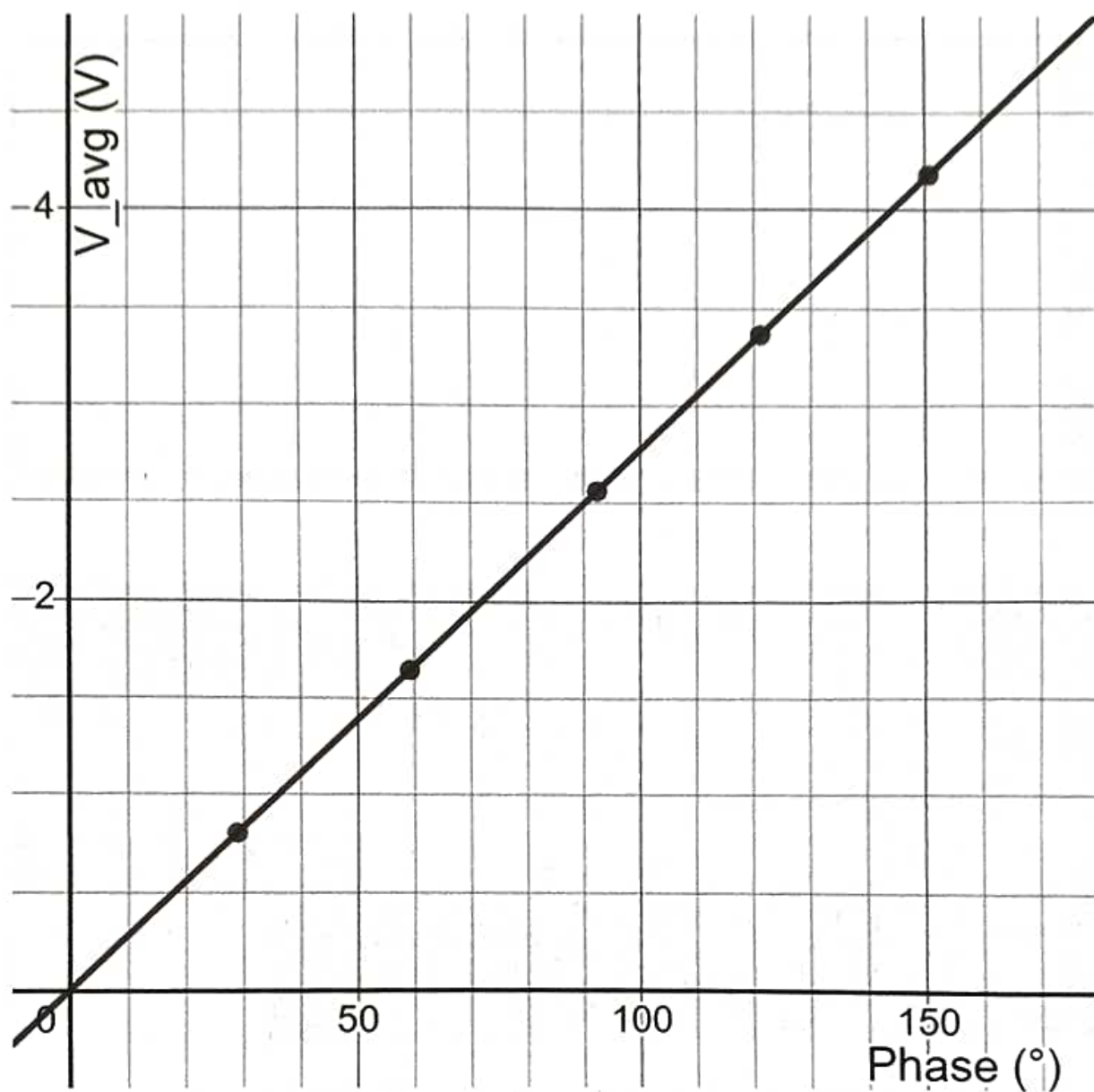

Plot: V\_avg (V) vs Phase (°)


[Best-fit parameters:  $m = 0.027778$ ,  $b = -0.00000719472$ ;  $y = mx + b$ ]

The simulated phase detector has negligible non-linearity.


Results: All Pass Filter  
Phase Shift

SC22B146 (15)


Phase shift =  $30^\circ$

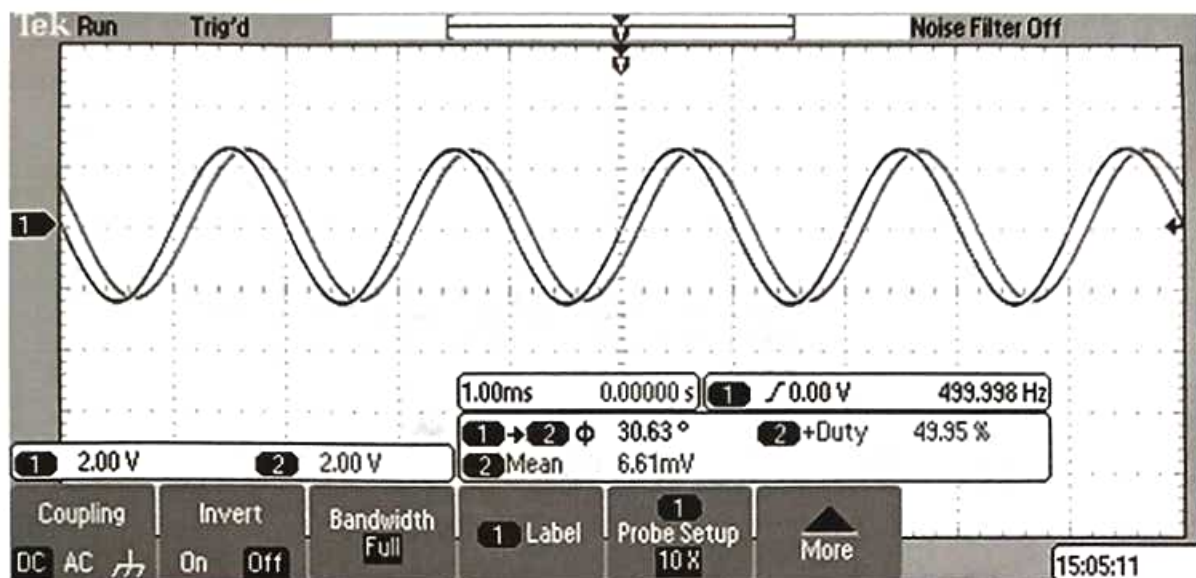


Phase shift =  $60^\circ$

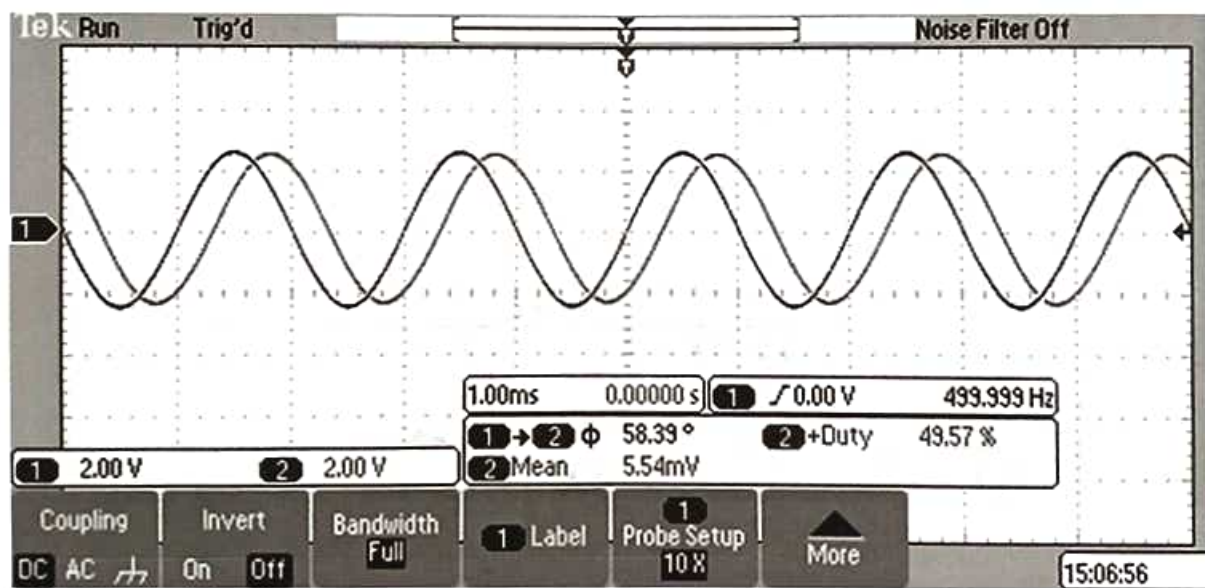

Phase shift =  $90^\circ$

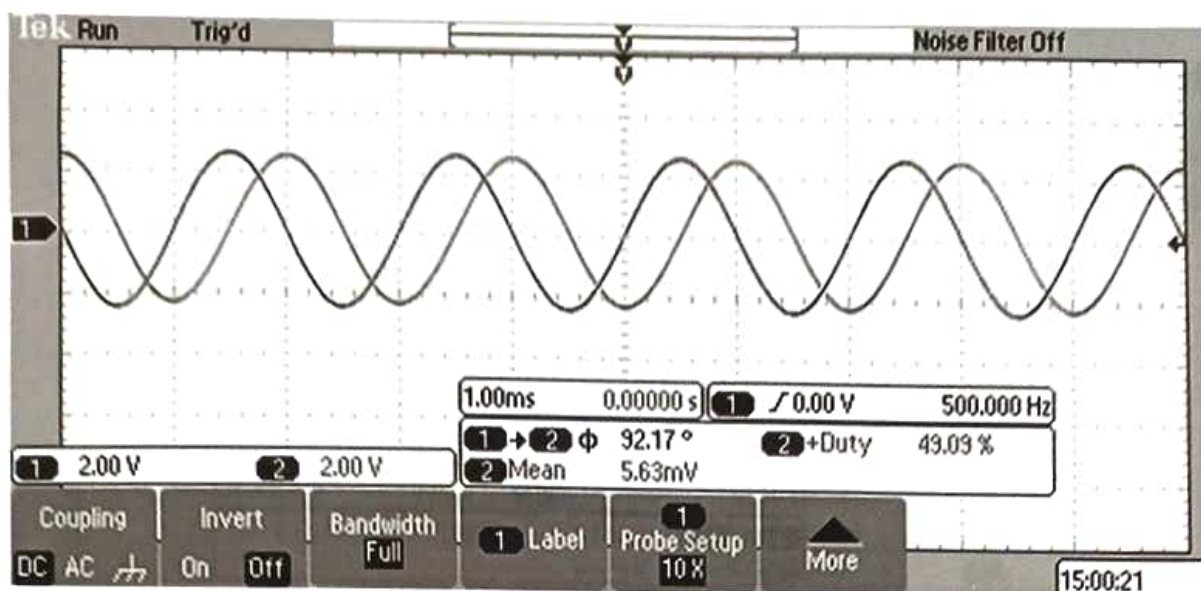

Phase shift =  $120^\circ$

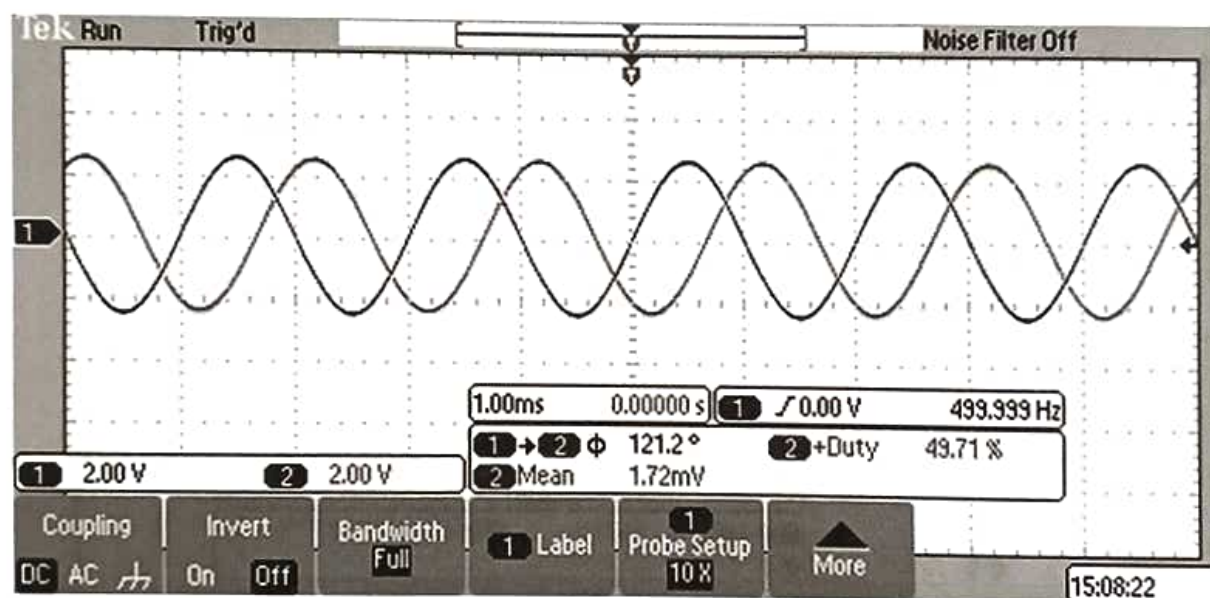

Phase shift =  $150^\circ$

