



परिपथविश्लेषणम्

NETWORK ANALYSIS

NETWORK ANALYSIS

Agenda:

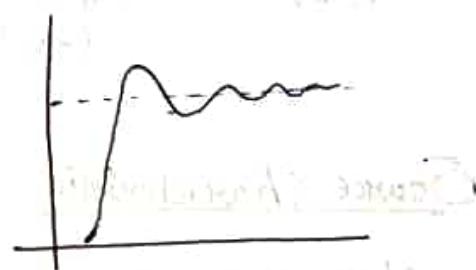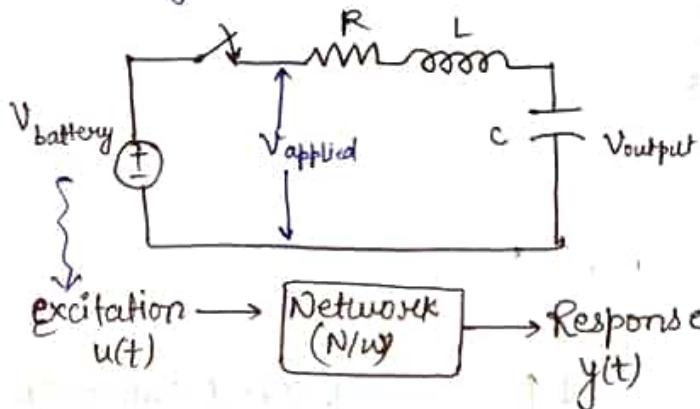
- ① what is Network Analysis (NA) all about?
- ② Reference directions and conventions.
- ③ Source characteristics & transformations / rules.
- ④ Signals and some elementary definition / ideas.



Network Analysis: Analysis of response from a n/w for given excitation.

N/w Design: Designing of N/w to get desired response for given excitation.




Reference Directions

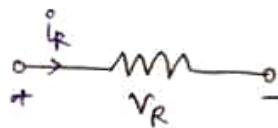

→ Load convention
comes from
Instantaneous power $P_R(t)$

$$P_R(t) = V_R(t) \cdot i_R(t)$$

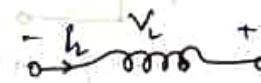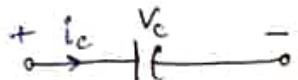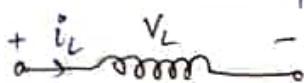
↳ is considered +ve, when load consumes power



↳ also correct; but needs to be consistent

$$V_L = V_m \cos \omega t$$
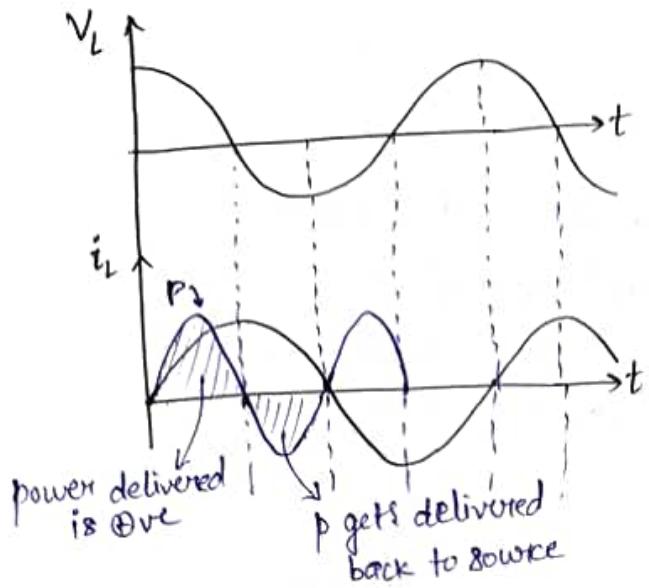
$$i_L (\text{in steady state}) = I_m \sin \omega t$$




Datasheet



Source Characteristic

Voltage source:

Ideal:

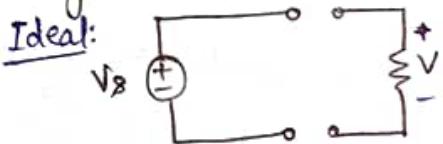


Practical:

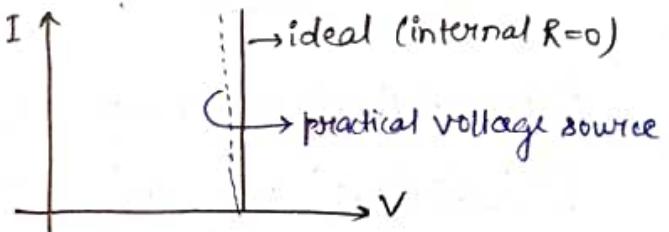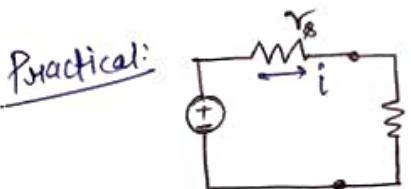



Current source:

Ideal:

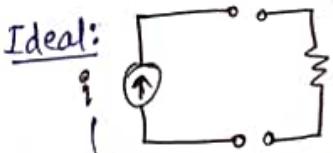


Keeps on sourcing current irrespective of voltage across it.


Practical:

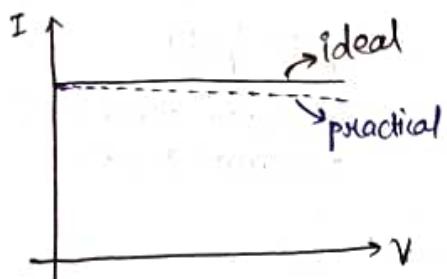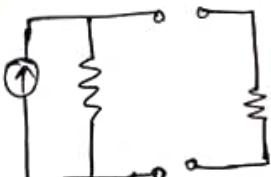

Dependent Sources

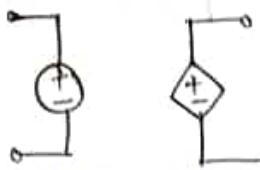


Voltage-controlled voltage source (VCCS)

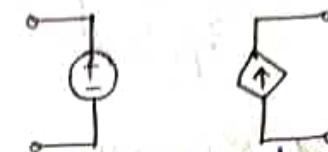

voltage-controlled current source (VCCS)




current-controlled current source (CCCS)

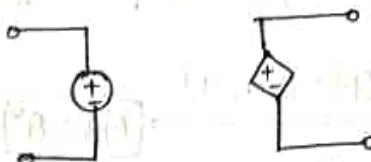



current-controlled voltage source (CCVS)

Transformation:

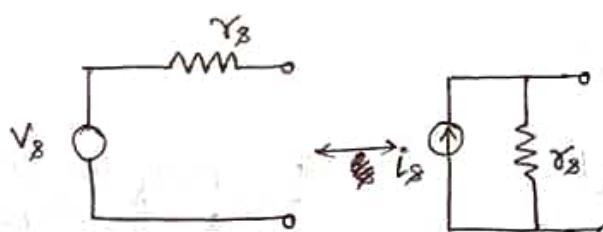

CARDINAL RULES:

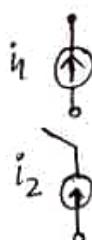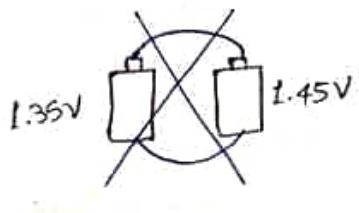- Never connect two V sources in parallel.
- Never connect two I sources in series.




Signals

↳ Excitation and responses of a network are functions of time — these are known as signals.

Linear Network

↪ A network is linear if the principles of superposition and proportionality are applicable.

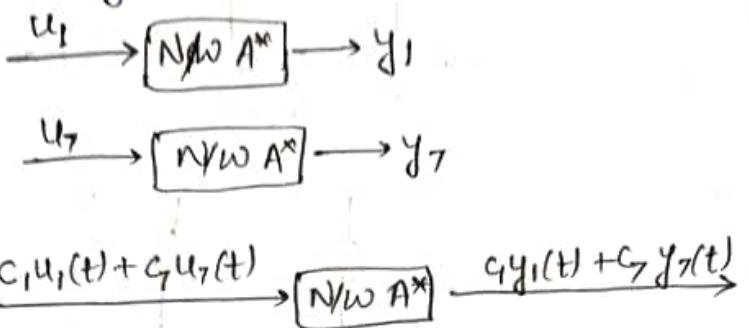Passive Network

↪ Network which doesn't contain active energy sources.

4-08-2023

signals: $v(t), i(t)$
 $q(t), \psi(t)$

Causal System

↪ Response system anticipated

↳ doesn't depend on future excitation

↳ practically all systems are causal.

we'll deal with such systems only.

→ If there's no excitation, there's no response.
 → Response doesn't depend on future excitation.

Idea of Complex Frequency


$$s = \sigma + j\omega$$

for LCR and RLC circuit, this approach is far more appropriate than differential equations

TIME DOMAIN ANALYSIS OF 1ST ORDER LINEAR NETWORK

1ST Order Linear Network or Linear System

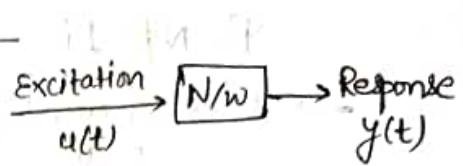↳ where $y(t)$ and $u(t)$ can be related by 1st order linear ODEs.



$$a_0 y + a_1 \frac{dy}{dt} = u \quad \text{--- (1)} \quad (\text{Variables are time dependent})$$

$$\Rightarrow a_0 y + a_1 y' = u$$


For eqn. 1 to be linear, a_0 & a_1 should either be constant or functions of independent variable (in this case, t) only.

$$\text{Eqn. 1} \Rightarrow A_0 y(t) + A_1 y'(t) = u(t)$$

↳ Linear Time Invariant system (LTI system)

$$\rightarrow a_0(t)y(t) + a_1(t)y'(t) = u(t)$$

LTIV

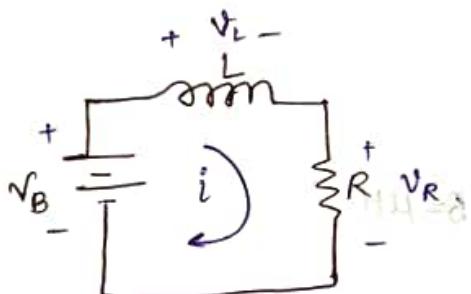



$$V_B = V_L + V_R$$

$$= L \frac{di}{dt} + Ri \quad \rightsquigarrow \text{Linear system!} \quad (\text{If } L \text{ & } R \text{ are current independent}).$$

Brief Note on L and C

Inductance parameter:

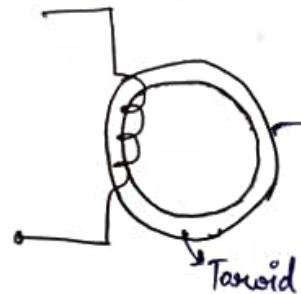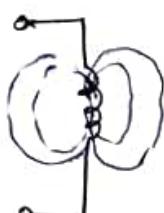↳ Magnetic field chooses path of low inductance.




high $M \gg M_0$
(high permeability)


$$V_L = \frac{d\Psi}{dt} = \frac{d}{dt}(Li) = L \frac{di}{dt}$$

$$\Psi = N\phi = Li$$

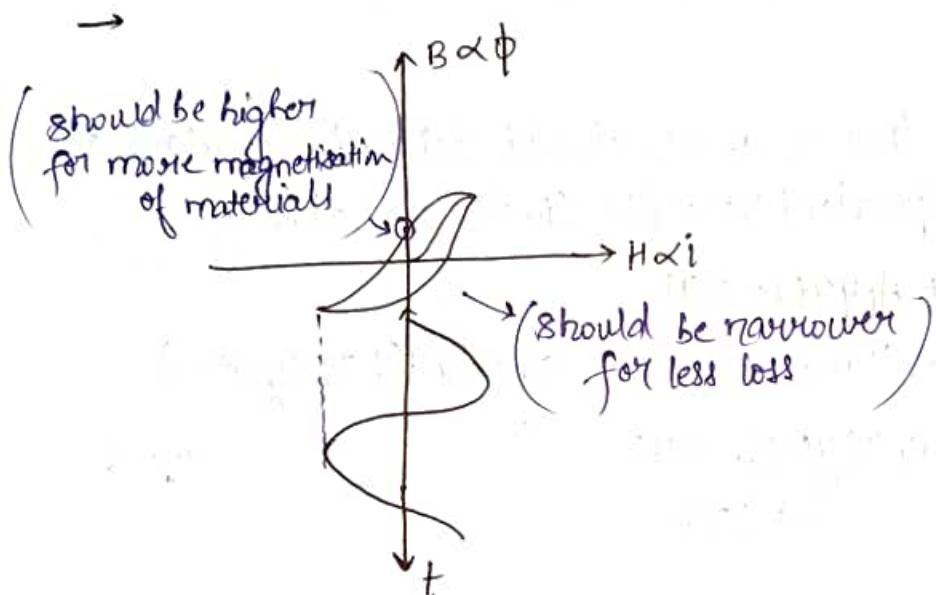→ L is constant if the magnetic field is linear
 ↳ Assumption for AV213 course.




→ In linear system, μ is constant.

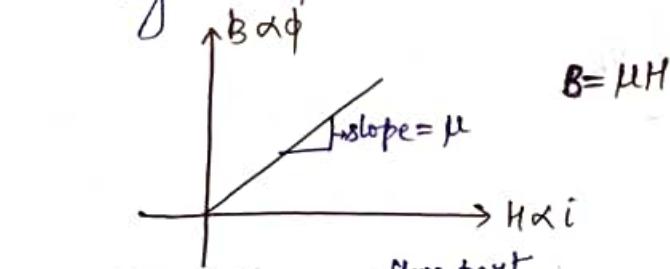


$$L = \frac{N^2}{R}; R = \frac{l}{\mu A} \rightarrow \begin{array}{l} \text{flux part} \\ \text{area of core seen by flux} \end{array}$$

$$= \underbrace{\mu A}_{\text{geometry is fixed}} N^2$$


(of no. of turns)

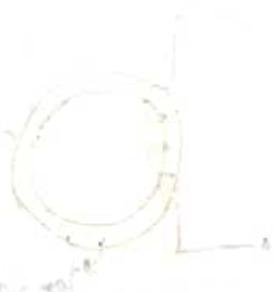

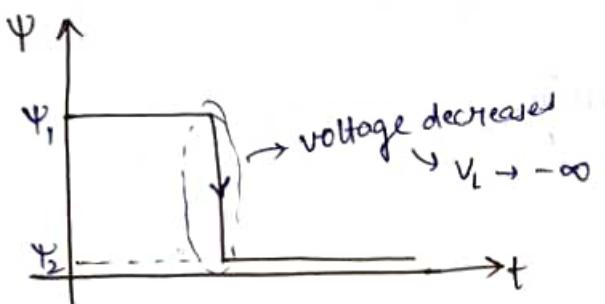

(i) Inductance

If suddenly we cut the wire,

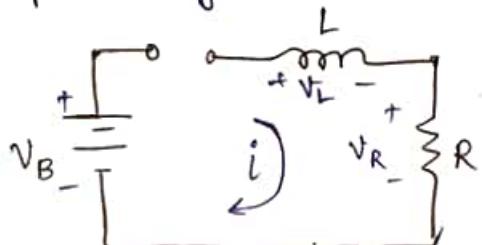

→ voltage across L would be ∞
↓ produces spark.

→ Φ cannot collapse/change significantly instantaneously.

current through an inductor cannot change suddenly.

conservation of flux


efflux and self inductance for simplicity consider small time interval




initially current in L is zero so self inductance is zero
current in C is zero so capacitor voltage is zero

Inductance (L)

- ↳ i_L cannot change instantaneously.
- ↳ V stiff element

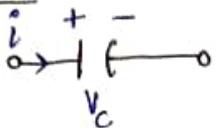Capacitance (C)
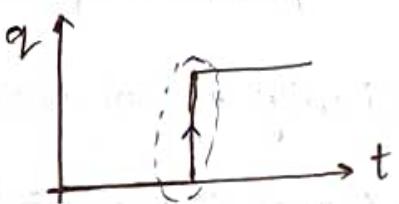
$$q = CV \Rightarrow i = \frac{dq}{dt} = C \frac{dv}{dt}$$




$\Rightarrow \frac{dq}{dt} \rightarrow \infty \Rightarrow i_{\text{charging}} \rightarrow \infty$
 ↓
 not a possibility
 by design

$q \rightarrow$ cannot change suddenly
 $\Rightarrow Cv$ cannot change suddenly.

$C \rightarrow V$ stiff element.


Time Domain Analysis of 1st Order RL N/W with DC Excitation

($t=0$ w/ switch is closed)

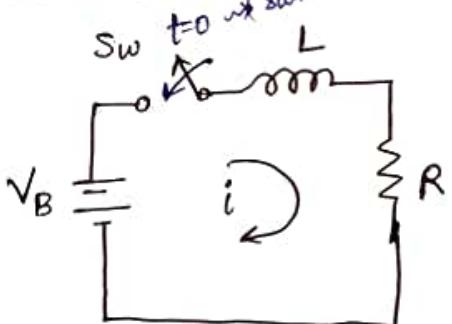


Initially relaxed (no energy stored)

ideal switch

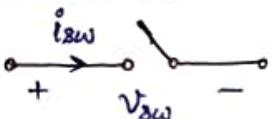

$i_{sw}=0$, when sw is open
 $v_{sw}=0$, when sw is closed.

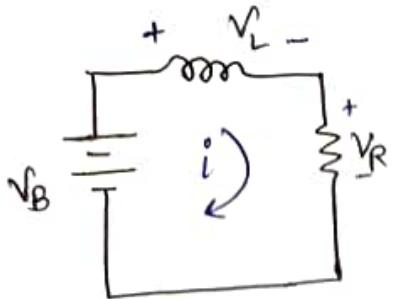Once switch is closed at $t=0$, the current circuit becomes



$$i(0) = 0$$

$$i(0+) = 0$$

KVL:

$$V_B = V_L + V_R$$

$$= L \frac{di}{dt} + iR$$

$$= Li' + iR$$

Objective: find and then plot i .

$$\Rightarrow \frac{V_B}{L} = i' + \frac{1}{LR} i = i' + \frac{1}{\tau} i \dots (e1)$$

where $\boxed{\tau \triangleq L/R}$ defn

Let $f: \text{IF}$.

$$f \frac{V_B}{L} = f i' + \frac{f}{\tau} i = (fi)'$$

$$\text{So, } f' = f/\tau \Rightarrow \frac{df}{f} = \frac{dt}{\tau} \Rightarrow f = k e^{t/\tau}$$

$$\therefore fi = \int f \frac{V_B}{L} dt$$

$$\text{or, } ke^{t/\tau} i = \int ke^{t/\tau} \cdot \frac{V_B}{L} dt$$

$$\Rightarrow i = \frac{V_B}{L} e^{-t/\tau} \int e^{t/\tau} dt + K_1 e^{-t/\tau}$$

$$= \frac{V_B}{L} e^{-t/\tau} \cdot \tau e^{t/\tau} + K_1 e^{-t/\tau}$$

$$= \frac{V_B}{R} + K_1 e^{-t/\tau}$$

Applying initial condition, $i(0) = 0$

$$\Rightarrow K_1 = -\frac{V_B}{R}$$


$$\therefore i(t) = \frac{V_B}{R} (1 - e^{-t/\tau})$$

$$\therefore V_L = V_B e^{-t/\tau}$$

$$(\because V_L = L \frac{di}{dt})$$

$$(\because L = \tau R)$$

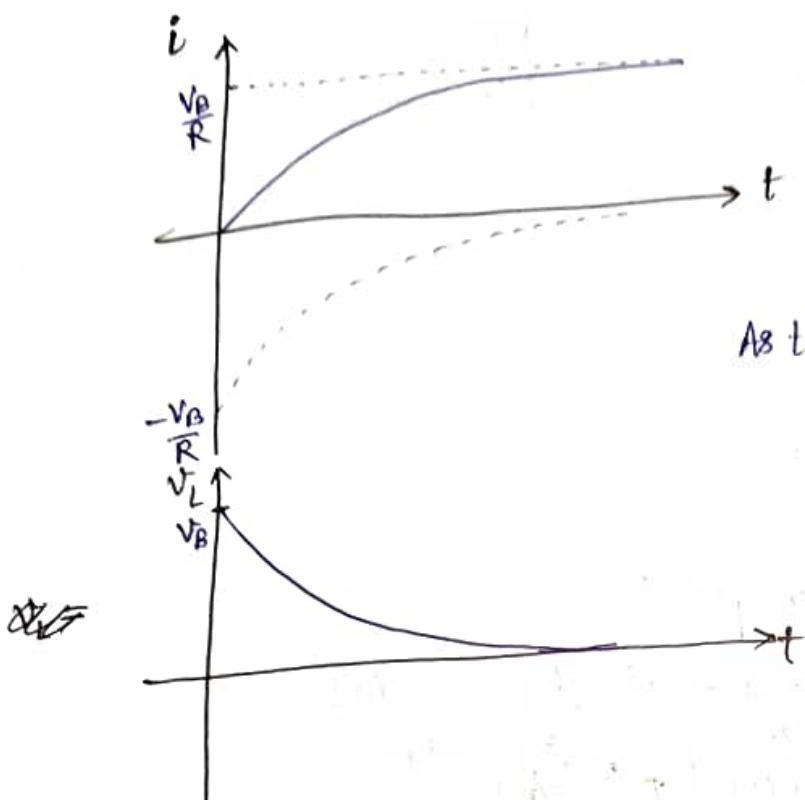
$$i(t) = \frac{V_B}{R} (1 - e^{-t/\tau}) = \frac{V_B}{R} - \frac{V_B}{R} e^{-t/\tau}$$





$$\text{As } t \rightarrow \infty, i_{\text{steady state}} = \frac{V_B}{R}$$

$$v_L = V_B e^{-t/\tau}$$

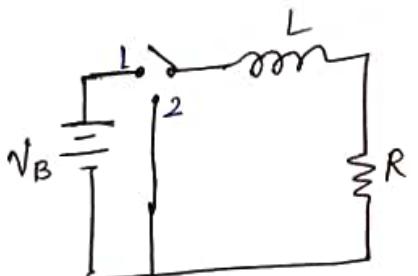$v_L \rightarrow 0$ in steady state
for DC excitation.



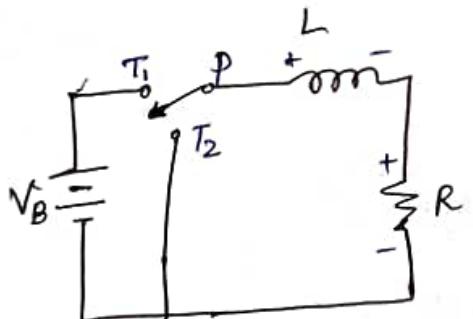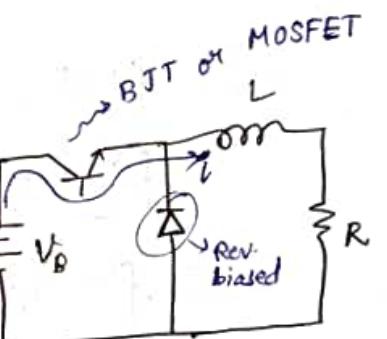\Rightarrow we want to change to pos(2),
before disconnecting pole pos(1) &
without short-circuiting.




SS was ~~not~~ reached

with Pole pos(1).

Then it is toggled to (2).

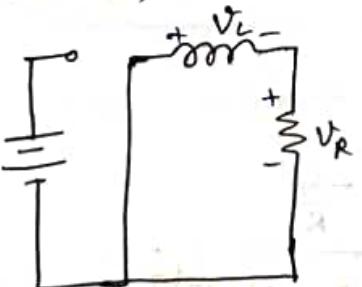
Once $S_w \rightarrow 2$, ~~rel.~~ circuit becomes



$$i(0) = \frac{V_B}{R}$$

$$0 = v_L + v_R \\ = L \dot{i} + R i$$

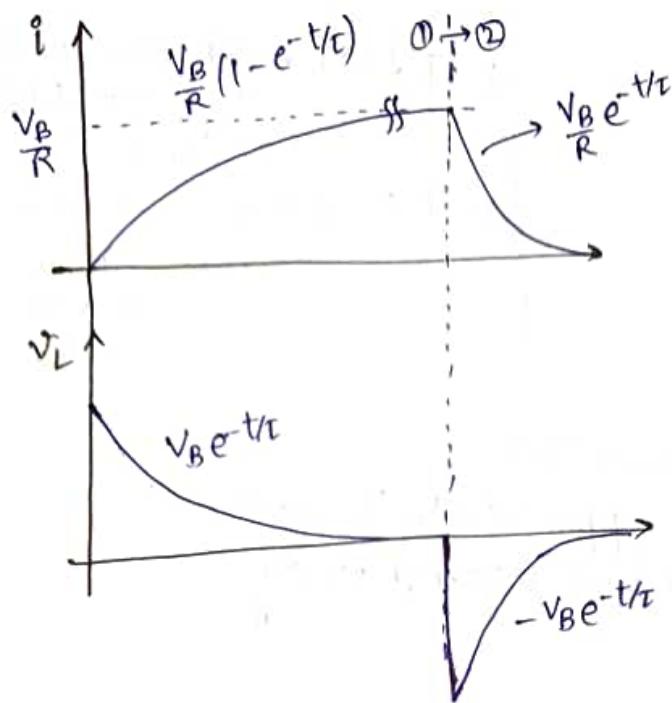
$$\Rightarrow i = \frac{V_B}{R} e^{-t/\tau}$$




10-08-2023

→ we can couple voltage source with i stiff element.

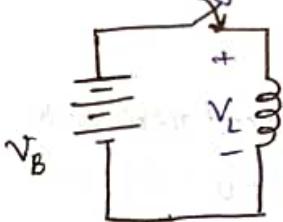↳ But we typically don't apply DC voltage source across L .




$$V_B = V_L = L \frac{di}{dt}$$

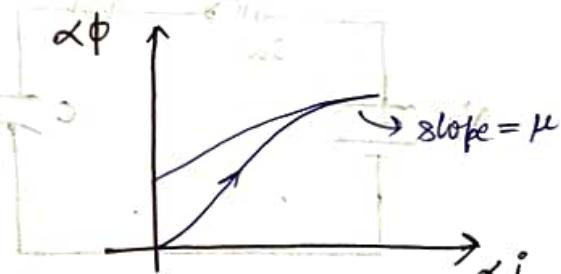

↳ Inductor constitutes magnetic material (around a core).

↳ i keeps on increasing as $V = \text{const.}$

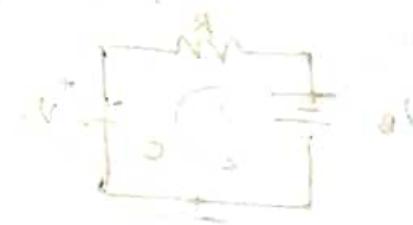↳ As saturation is reached, μ becomes zero.



$$i_L = \frac{V_B}{R} (1 - e^{-t/\tau}) \quad \text{in pos. ①}$$

$$= \frac{V_B}{R} e^{-t/\tau} \quad \text{in pos. ②}$$

where, $\tau \triangleq L/R$.

$\tau \rightarrow$ decides the rate of decay or rise of i .

τ : Time constant of the system.

$$\begin{aligned} i_L &= I e^{-t/\tau} \\ i_L(1) &= I e^{-1/\tau} \\ \# \tau \uparrow &\Rightarrow \text{Decay slower} \\ \# I e^{-1/\tau} &\sim 0.3I \quad I e^{-1/2} \sim 0.6I \end{aligned}$$

$$i_L = I e^{-t/\tau}$$


$$i_L = I e^{-t/\tau}$$

t/τ	i_L/I
0	1
1	~ 0.37
2	~ 0.14
3	~ 0.05
4	~ 0.018


- # $\tau \downarrow \Rightarrow L \downarrow \Rightarrow$ Resistive nature \uparrow
 \Rightarrow current following $v \uparrow$
 \Rightarrow lag b/w I & $v \downarrow$
- # $\tau \uparrow \Rightarrow L \uparrow \Rightarrow$ Lag b/w I & $v \uparrow$
 \Rightarrow More time to reach steady state.

\hookrightarrow settling time $= (4\tau)$
 For all practical applications, the system is assumed to have reached steady state at 4τ .

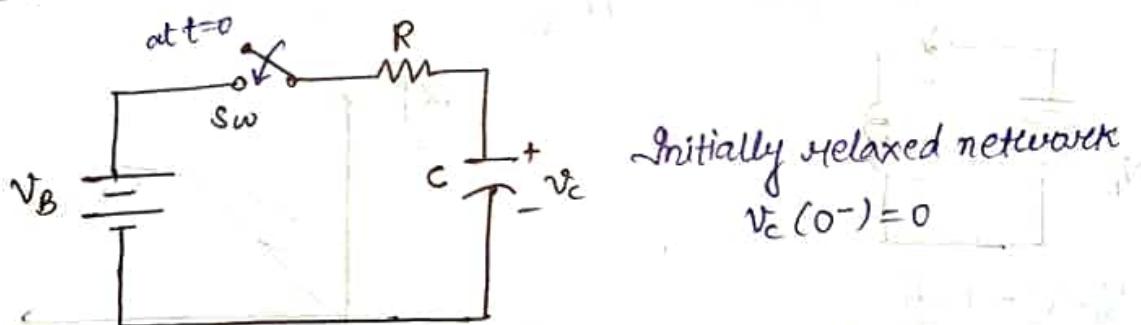RC Circuit - 1st Order with DC excitation



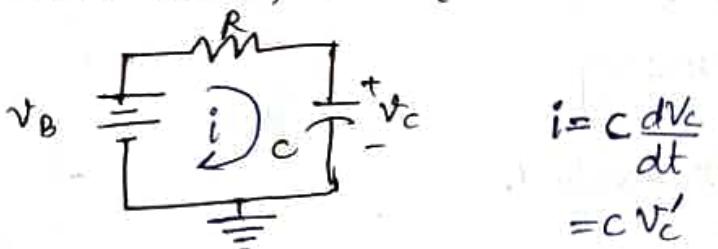Objective of Analysis: finding $V_C(t)$ for $t \geq 0$.
 Once SW is closed, the equivalent circuit becomes



$$V_B = iR + V'_C$$

$$\Rightarrow 0 = i'R + i'C \Rightarrow i' + \frac{1}{RC}i = 0$$


$$\tau \triangleq RC \text{ for RC N/W.}$$

$$\Rightarrow i = Ke^{-t/\tau}$$

$$\text{At } t=0, i(0) = \frac{V_B - V_C(0)}{R} = \frac{V_B}{R}$$

$$\therefore i = \frac{V_B}{R} e^{-t/\tau}$$
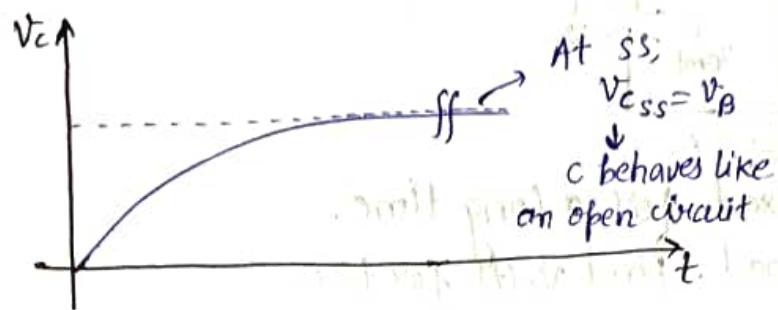
$$\therefore V_c = V_B - IR = V_B(1 - e^{-t/\tau})$$




At steady state,

$$V_c = V_B$$

- no charging current

- open circuit.

Discharging:

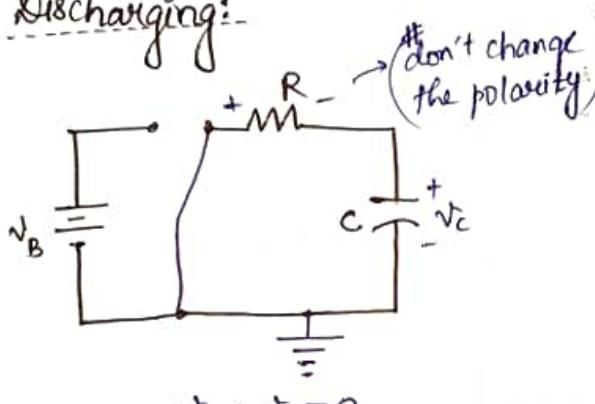

$$V_R + V_C = 0$$

$$\Rightarrow IR + V_C = 0$$

$$\Rightarrow RC V'_C + V_C = 0$$


$$\Rightarrow V_C = Ke^{-t/\tau}$$

: Normal capacitor

- ↳ can be charged in both dirn
- ↳ can be used with ac as well as dc voltage.


: Polarised capacitor

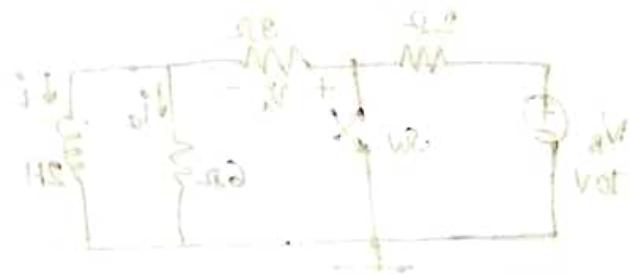- ↳ can be charged in one dirn only (only dc)
- ↳ stores large charge in less space.



out to break w. swift final o wif maf pulation low w
act ref sv & ai, g knif


Q1

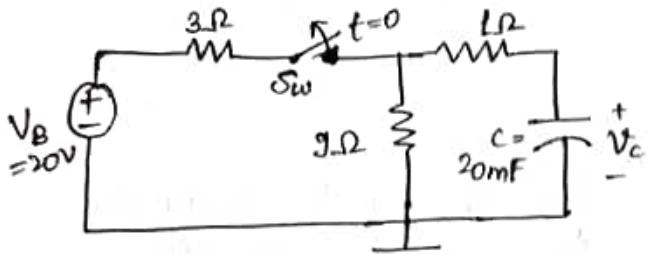


Initially S_W was closed for a long time.

At $t=0$, S_W was opened. Find $V_c(t)$ for $t \geq 0$.

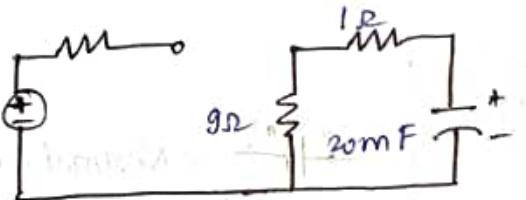Soln: For $t \geq 0$, relevant eqv. ckt. is



Initially, the eqv. ckt. was

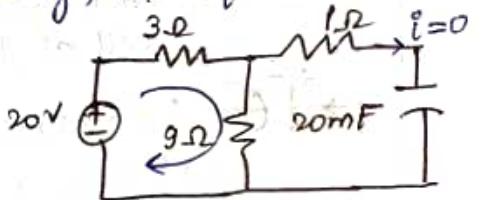

$$V_c(0^-) = \frac{9}{12} \times 20 \\ = 15V$$

For $t \geq 0$

$$V_c(0^-) \approx V_c(0^+)$$


$$V_c(t) = K e^{-t/\tau},$$

$$\text{where } K = V_c(0^-) = 15V$$

$$\tau = RC = 10 \times 20 \times 10^{-3} \\ = 0.2$$


$$\therefore V_c(t) = 15 e^{-st} V.$$

Q1

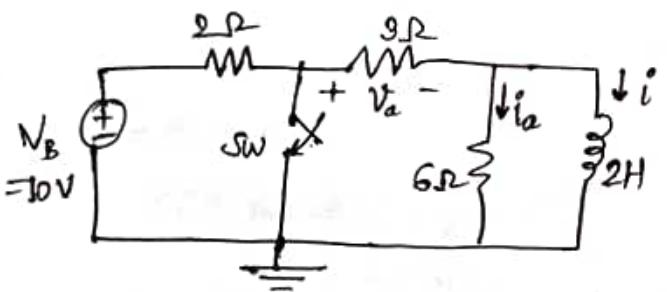


S_W was initially open for a long time. S_W closed at $t=0$. Find i , i_a & V_a for $t \geq 0$.

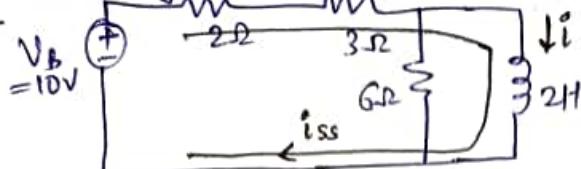Soln: Initially, at SS with S_w open, the relevant ckt. of interest is:



$$i_{ss} = \frac{10}{5} A = 2A$$

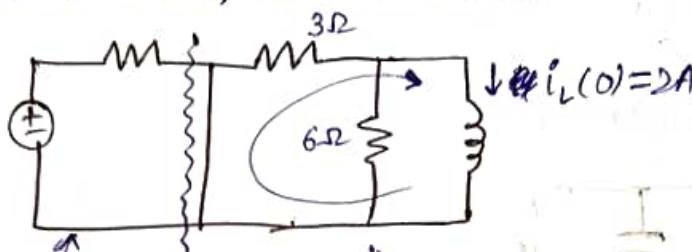When S_w is closed, the relevant ckt. becomes:



Not relevant anymore



$$V_L + V_R = 0$$

$$\Rightarrow L\dot{i}' + iR = 0$$


$$\Rightarrow i = K e^{-t/\tau}, \quad \tau = 1, \quad K = 2$$

$$\Rightarrow i = 2e^{-t} A$$

$$\therefore i_a = -\frac{3}{9} \times 2e^{-t} = -\frac{2}{3}e^{-t} A$$

$$\text{and, } V_a = V_L = -L\dot{i} = -2 \times 2(-\frac{1}{1})e^{-t}$$
$$\Rightarrow V_a = 4e^{-t} V$$

Q1

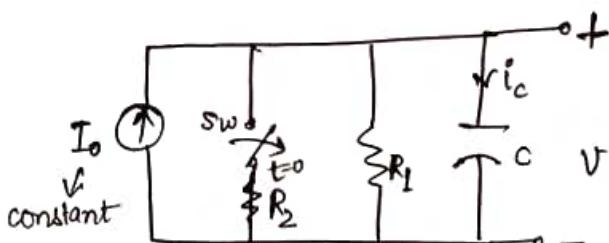


$$R_1 = 1\Omega, \quad R_2 = 0.5\Omega, \quad C = 0.5F$$

SS was reached with S_w closed.

Find $V_a(t)$ for $t \geq 0$.

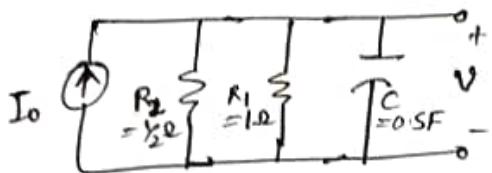
Qn: Initially when S_2 was closed, ckt. of interest was:



$$R_1 \parallel R_2 = \frac{1}{\frac{1}{2} + 1} = \frac{1}{3}$$

$$V_c(0^-) = I_o \times \frac{1}{3} V = \frac{I_o}{3} V$$

When switch is opened,

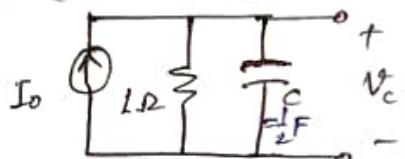

$$V_c(0) = \frac{I_o}{3} V$$

$$I_o = \frac{V_c}{1} + C V_c' = V_c + \frac{1}{2} V_c'$$

$$\Rightarrow V_c' + 2V_c = 2I_o$$

If f be the IF,

$$fV_c' + 2fV_c = 2fI_o$$

$$\Rightarrow f' = 2f \Rightarrow \frac{df}{f} = 2dt$$
$$\Rightarrow f = Ke^{2t}$$

$$\therefore (fV_c)' = 2fI_o$$

$$\Rightarrow fV_c = 2I_o \int f dt + K$$

$$\Rightarrow V_c = 2I_o e^{-2t} \int e^{2t} dt + Ke^{-2t}$$
$$= I_o + Ke^{-2t}$$


$$\text{At } t=0, V_c = I_o/3 = I_o + K$$

$$\Rightarrow K = -2I_o/3$$

$$\therefore V_c = I_o \left(1 - \frac{2}{3} e^{-2t} \right) V$$



Q) For $t \geq 0$

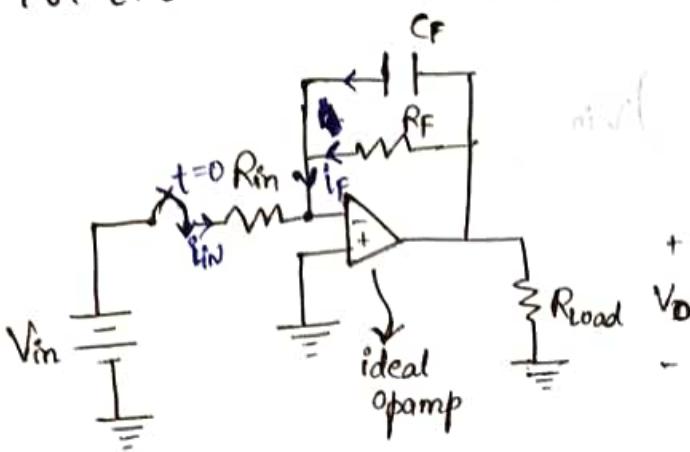

$$V_o(0) = 0$$

$$V_o(0^+) = 0$$

$V^+ = V^-$ only when we put the negative feedback, i.e., connecting output with 0vcc side

Soln: $V_+ = V_- \quad \text{--- (1)}$

$$\dot{I}_{in} + \dot{I}_F = 0 \quad \text{--- (2)}$$

$$\left\{ \begin{array}{l} \dot{I}_{in} = \frac{V_{in} - 0}{R_{in}} \\ \dot{I}_F = \frac{V_o}{R_F} + C_F \frac{dV_o}{dt} \end{array} \right. \quad \text{--- (3)}$$

Using (3) in (2),

$$\frac{V_{in}}{R_{in}} + \frac{V_o}{R_F} + C_F V'_o = 0$$

$$\Rightarrow V'_o + \frac{1}{R_F C_F} V_o = - \frac{1}{R_{in} C_F} V_{in} \quad \text{--- (4)}$$

Let f be the integrating factor.

$$- f \frac{1}{R_{in} C_F} V_{in} = f V'_o + \frac{f}{R_F C_F} V_o = (f V_o)'$$

$$\therefore \frac{df}{dt} = \frac{f}{R_F C_F} \Rightarrow f = k e^{t/T_F}$$

where $T_F \triangleq R_F C_F$

$$\text{Then, } (k e^{t/T_F} V_o)' = - k e^{t/T_F} \frac{1}{R_F C_F} V_{in}$$


$$\Rightarrow e^{t/T_F} V_o = - \frac{V_{in}}{R_{in} C_F} \int e^{t/T_F} dt + k_2$$

$$\Rightarrow V_o = - \frac{V_{in}}{R_{in} C_F} \cdot T_F + k_2 e^{-t/T_F}$$

$$\text{At } t=0, k_2 = \frac{R_F}{R_{in}} V_{in}$$

$$\therefore V_o = -\frac{R_F}{R_{in}} (1 - e^{-t/T_F}) V_{in}$$

RL with AC Excitation

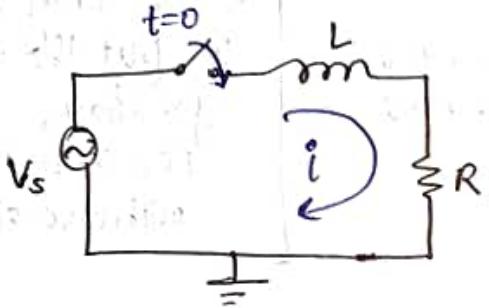


- Initially relaxed w/w.

- Sw closes at $t=0$.

- Objective of analysis: find $i(t)$ for $t \geq 0$.

Given $V_s = V_m \sin(\omega t + \alpha)$

For $t=0$, the relevant circuit is:

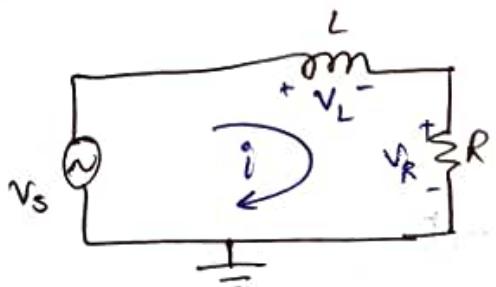

Applying KVL, $V_s = L i' + R i$

$$\Rightarrow V_m \sin(\omega t + \alpha) = L i' + R i$$

$$\Rightarrow i' + \frac{1}{L} i = \frac{V_m}{L} \sin(\omega t + \alpha) \quad \text{--- (1)}$$

If $f = k e^{t/T_F} \leftrightarrow \text{Int. factor}$

$$\Rightarrow (if)' = \frac{V_m}{L} k e^{t/T_F} \sin(\omega t + \alpha)$$

$$\Rightarrow i = \underbrace{\frac{V_m}{L} \int e^{t/T_F} \sin(\omega t + \alpha) dt}_{I_{ng}} + k_0 e^{-t/T_F} \quad \text{--- (2)}$$

$$\begin{aligned}
 I_{ng} &= \int_{t_0}^{t_0+T_F} e^{t/T_F} \sin(\omega t + \alpha) dt \\
 &= \int_{t_0}^{t_0+T_F} \sin(\omega t + \alpha) d(e^{t/T_F}) \\
 &= T_F \left[e^{t/T_F} \sin(\omega t + \alpha) - \int e^{t/T_F} d\{\sin(\omega t + \alpha)\} dt \right] \\
 &\quad \text{using } \int u dv = uv - \int v du \\
 &= T_F \left[e^{t/T_F} \sin(\omega t + \alpha) - \omega \int e^{t/T_F} \cos(\omega t + \alpha) dt \right] \\
 &= T_F \left[e^{t/T_F} \sin(\omega t + \alpha) - \omega T_F \int \cos(\omega t + \alpha) d(e^{t/T_F}) \right] \\
 &= T_F \left[e^{t/T_F} \sin(\omega t + \alpha) - \omega T_F \left\{ e^{t/T_F} \cos(\omega t + \alpha) - \int e^{t/T_F} d\{\cos(\omega t + \alpha)\} dt \right\} \right] \\
 &= T_F e^{t/T_F} \left[\sin(\omega t + \alpha) - \omega T_F \cos(\omega t + \alpha) \right. \\
 &\quad \left. - \omega^2 T_F^2 \int e^{t/T_F} \sin(\omega t + \alpha) dt \right] \\
 &\Rightarrow (1 + \omega^2 T_F^2) I_{ng} = T_F e^{t/T_F} \left[\sin(\omega t + \alpha) - \omega T_F \cos(\omega t + \alpha) \right] \\
 &\Rightarrow I_{ng} = \frac{1}{1 + \omega^2 T_F^2} T_F e^{t/T_F} \left[\sin(\omega t + \alpha) - \omega T_F \cos(\omega t + \alpha) \right] \quad \text{---(3)}
 \end{aligned}$$

Using (3) in (2),

$$i(t) = e^{-t/T_F} \frac{V_m}{K} \cdot \frac{1}{1 + \frac{\omega^2 T_F^2}{R^2}} \frac{L}{R} e^{t/T_F} \left[\sin(\omega t + \alpha) - \omega T_F \cos(\omega t + \alpha) \right] + k_0 e^{-t/T_F}.$$

$$\Rightarrow p(t) = \frac{V_m}{R} \frac{R^2}{\omega^2 L^2 + R^2} \left[\sin(\omega t + \alpha) - \omega T_F \cos(\omega t + \alpha) \right] + k_0 e^{-t/T_F}$$

$$\text{Let } Z \triangleq \sqrt{R^2 + \omega^2 L^2}$$

$$\theta \triangleq \tan^{-1} \left(\frac{\omega L}{R} \right) \rightarrow \text{Impedance angle}$$

$$\omega L \triangleq X$$

Then,

$$i(t) = \frac{V_m}{Z} \left[\underbrace{\frac{R}{Z} \sin(\omega t + \alpha)}_{X/Z} - \frac{R}{Z} \cdot \frac{\omega L}{R} \cos(\omega t + \alpha) \right] + k_0 e^{-t/\tau_F}$$

$$\Rightarrow i(t) = \frac{V_m}{Z} \left[\cos\theta \sin(\omega t + \alpha) - \sin\theta \cos(\omega t + \alpha) \right] + k_0 e^{-t/\tau_F}$$

$$\Rightarrow i(t) = \frac{V_m}{Z} \sin(\omega t - \theta) + k_0 e^{-t/\tau_F}$$

TD Analysis of Linear 2nd Order Network

2nd order ODE: $a_2(t)y''(t) + a_1(t)y'(t) + a_0(t)y(t) = r(t)$... (e1)

For (e1) to be linear,

$a_2, a_1, a_0 \rightarrow$ are either constants or functions of t only.

(e1) ~~Swapping the~~ $\xrightarrow{(t)} y'' + b_1 y' + b_0 y = r_1(t)$... (e2)


$$y(t) = y_h(t) + y_p(t)$$

For y_h , $y = k e^{\lambda t}$ trial form

$$\text{Characteristic eq.} : \lambda^2 + b_1 \lambda + b_0 = 0.$$


$[\lambda] \rightarrow$ unit of frequency.

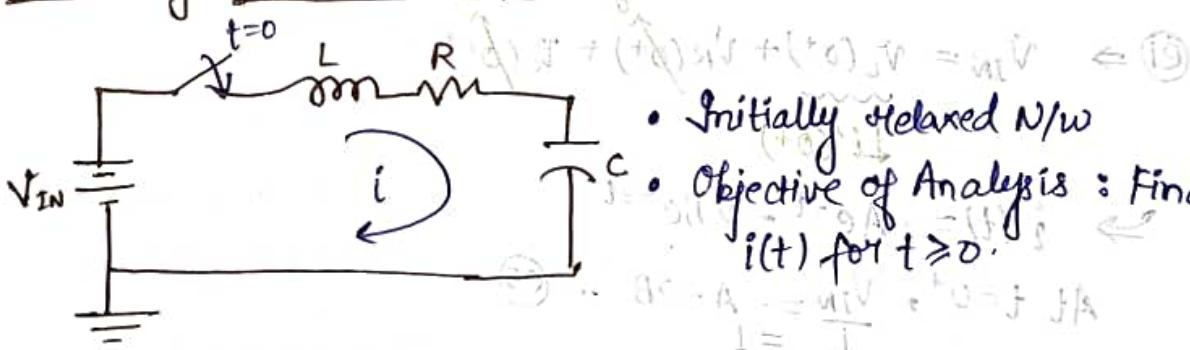Case Study: Series RLC with DC Excitation



- Initially relaxed N/W
- Objective of Analysis: Find & plot $i(t)$ for $t \geq 0$.

For $t \geq 0$, initial cond. is,

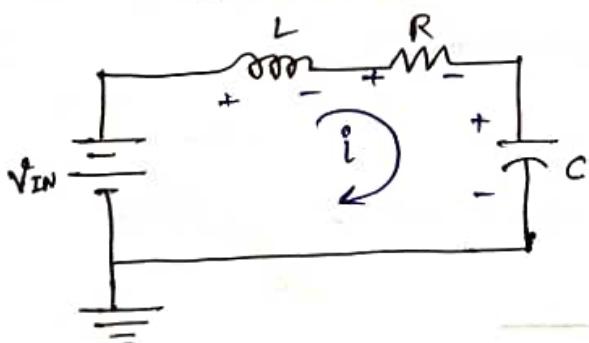

$$\text{Using KVL: } V_{IN} = V_L + V_R + V_C \quad \dots (e1)$$


Differentiating both sides of (e1)

$$0 = V_L' + V_R' + V_C'$$

$$\Rightarrow 0 = L i'' + R i' + \frac{1}{C} i$$

$$L = 8, R = 8 \quad \dots (e2), (e3)$$
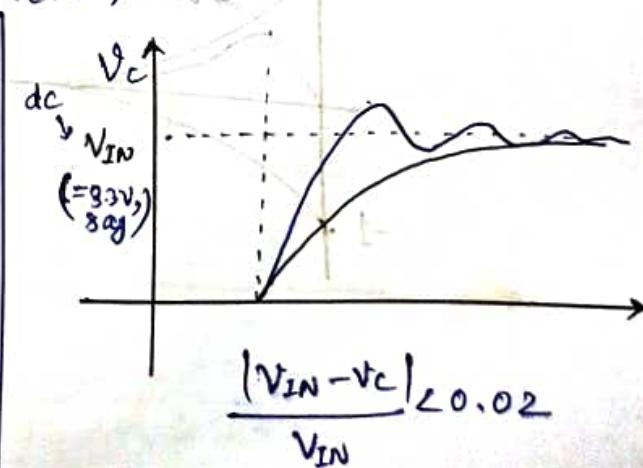
$$\begin{aligned} i(0-) &= 0, \quad V_{c,ss} = V_{IN} \\ v_c(0-) &= 0 \\ i(0+) &= 0 \\ v_c(0+) &= 0 \end{aligned}$$



$$\Rightarrow i'' + \frac{R}{L}i' + \frac{1}{LC}i = 0 \quad \text{... (2)}$$

Let $i = ke^{\lambda t}$ be a trial soln, then the corresponding auxilliary eqn is,

$$\lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0$$

Note: Notion of T (R/L or R_C) as in 1st order systems is not directly applicable here.

$$\lambda = \frac{1}{2} \left\{ -\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} \right\} \quad \text{... (3)}$$

Eg. $\text{V}_{IN} = 1 \text{ V}, R = 3 \Omega, L = 1 \text{ H}, C = \frac{1}{2} \text{ F}$.

$$\lambda = \frac{1}{2} \left\{ -3 \pm \sqrt{9 - 8} \right\}$$

$$= -1, -2$$

Then, $i(t) = Ae^{-t} + Be^{-2t}$

$$i(0^+) = 0 \Rightarrow 0 = A + B \quad \text{... (4)}$$



(2) $\Rightarrow V_{IN} = V_L(0^+) + V_R(0^+) + V_C(0^+)$

$$\Rightarrow i'(t) = -Ae^{-t} - 2Be^{-2t}$$

$$\text{At } t=0^+, \frac{V_{IN}}{L} = -A - 2B \quad \text{... (5)}$$

(4), (5) $\Rightarrow A = 1, B = -1$


$$i(t) = e^{-t} - e^{-2t} \quad A$$

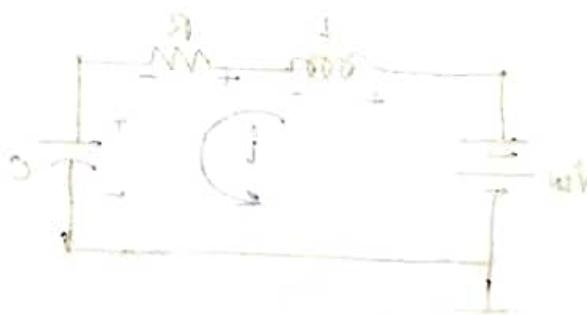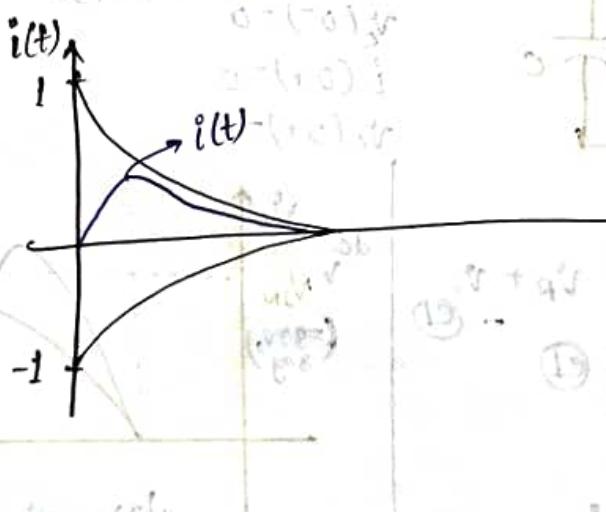

$$V_L + V_R + V_C = V_{IN} \quad \text{... (6)}$$

$$iL + RI + \frac{1}{C} \int i dt = 0 \quad \Leftarrow$$

RLC (Series) with DC Excitation

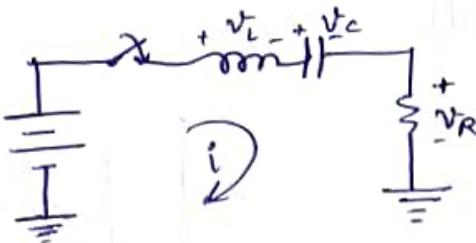

$$V_{IN} = V_L + V_R + V_C \quad \dots \text{eqn 1}$$

$$0 = i'' + \frac{R}{L} i' + \frac{1}{C} i \quad \dots \text{eqn 2}$$

↓ Characteristic Eqn / Auxiliary Eqn

$$\lambda = \frac{1}{2} \left\{ -\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} \right\}$$

Eg ① $V_{IN} = 1V, R = 2\Omega, L = 1H, C = 0.5F$.

$$\lambda = -1 \pm j$$

$$i(t) = e^{-t} (A \cos t + B \sin t)$$

$$i(0+) = 0, V_L(0+) = V_{IN}$$



$$i'(0+) = \frac{V_{IN}}{L}$$

$$i(t) = B e^{-t} \sin t$$

$$\Rightarrow i(t) = e^{-t} \sin t$$


Eg ①: $i(t) = e^{-t} - e^{-2t}$

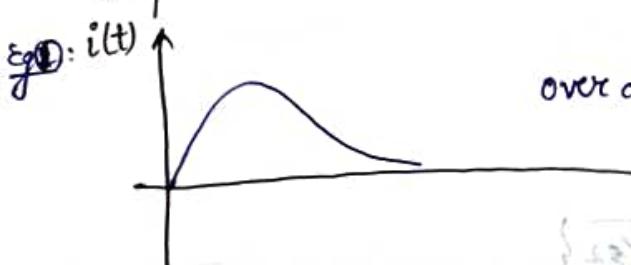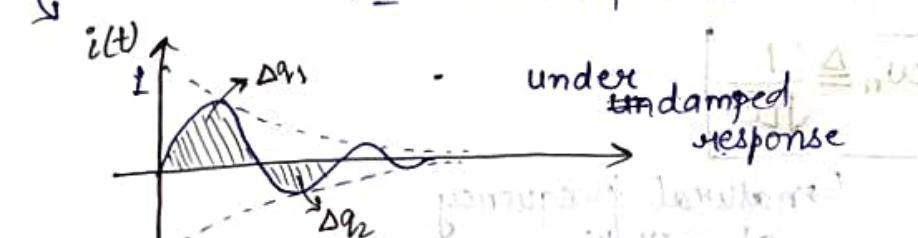Eg ②: $i(t) = e^{-t} \sin t \rightarrow \leq e^{-t} \rightarrow \text{damped sine}$



over damped response

\Rightarrow

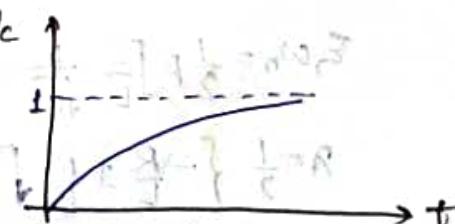


$$(s^2 + 1) \omega^2 = \omega^2 \left(1 + \frac{R^2}{L^2} \right) \Rightarrow \omega = \frac{1}{L} \sqrt{1 + \frac{R^2}{L^2}}$$

EQ@:

$$\begin{aligned}
 V_c(t) &= V_{IN} - [R - i'L] \\
 &= 1 - 2e^{-t\sqrt{\frac{1}{LC}}} - 1 \left\{ e^{-t\sqrt{\frac{1}{LC}}} - e^{-t\sqrt{\frac{1}{LC}}} \right\} \\
 &= 1 - e^{-t\sqrt{\frac{1}{LC}}} \{ 2\sin(\sqrt{\frac{1}{LC}}t + \pi/4) \}
 \end{aligned}$$

↳ can be over
 ↳ means V_c can be $> V_{IN}$.

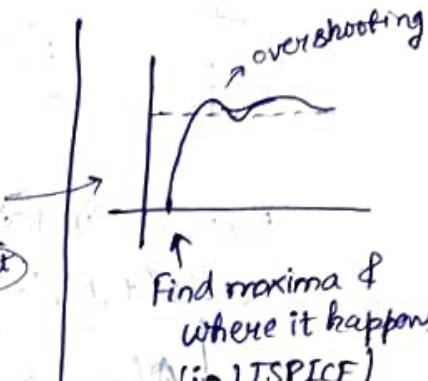$\rightarrow \lambda = \frac{1}{2} \left\{ -\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} \right\}$



overshooting

Find maxima & where it happens (in LTSPICE)

Hence whether $\frac{R}{L} > \omega_0 = \omega < \frac{2}{\sqrt{LC}}$, that decides the nature of transient.

if $\frac{R}{L} \geq \frac{2}{\sqrt{LC}}$ \rightarrow damped

$$\hookrightarrow \frac{1}{2} R \sqrt{\frac{C}{L}} > / = / < 1$$

$$\xi \triangleq \frac{1}{2} R \sqrt{\frac{C}{L}}$$

↳ damping ratio/damping factor
for series RLC.

ξ	nature of Response
> 1	overdamped
< 1	underdamped
$= 1$	critically damped
$= 0$	undamped

We also define, $\omega_n \triangleq \frac{1}{\sqrt{LC}}$

↳ natural frequency
of oscillation.

$$\xi \omega_n = \frac{1}{2} R \sqrt{\frac{C}{L}} \frac{1}{\sqrt{LC}} = \frac{1}{2} \frac{R}{L}$$

$$\lambda = \frac{1}{2} \left\{ -\frac{R}{L} \pm \frac{R}{L} \sqrt{1 - \frac{4}{R^2 C}} \right\}$$

$$= \frac{1}{2} \left\{ -2\xi \omega_n \pm 2\xi \omega_n \sqrt{1 - \frac{1}{\xi^2}} \right\}$$

$$\Rightarrow \lambda = -\xi \omega_n \pm j \omega_n \sqrt{1 - \xi^2}$$

$$\therefore \lambda = -\xi w_n \pm jw_n \sqrt{1-\xi^2}$$

allow 218 bytes in :2 photo

[ʌ] → frequency

Complex frequency,

$$s = \sigma + j\omega$$

$$\sigma^2 + \omega^2 = \omega_n^2 \rightarrow \text{circle}$$

$$\sigma = -\xi w_n$$

卷之三

$$v \rightarrow -\frac{1}{2} \sin x$$

$$\rightarrow \operatorname{Re}(\gamma) = \sigma$$

$$\sigma = \Theta \nu \xi \Rightarrow \xi = \Theta \nu \epsilon$$

$\hookrightarrow \Theta \nu \epsilon$ damped




Bags & Box Transport soft	
1	100
2	100
3	100
100	100

$$③ \quad -2 + \frac{1}{3x} + x \frac{1}{3x} = R$$

$$3x + 4y = 6 \leftarrow$$

perfect with respect to ω ; ω is called a σ -ideal if $\{x \in X : \omega(x) = 0\}$ is a σ -ideal.

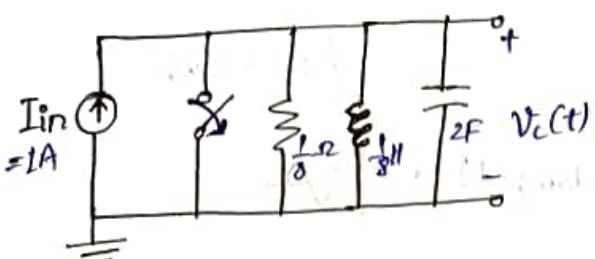Case Study 2: Parallel RLC with a Current Source




- Initially relaxed N/W.
- Find $V_c(t)$ for $t \geq 0$.

- Voltage source shouldn't be short-circuited.
- Current source should never be open-circuited.

$$I_{IN} = 1A, R = \frac{1}{8} \Omega, L = \frac{1}{8} H, C = 2F$$

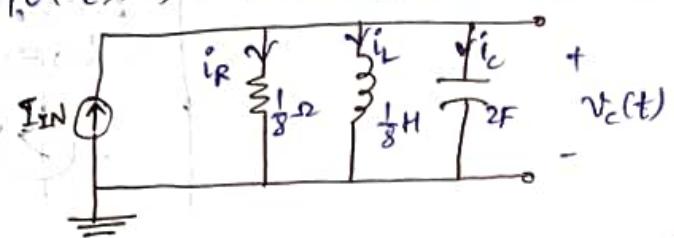For $t \geq 0$, the relevant ckt. becomes



$$\text{Using KCL: } I_{IN} = i_R + i_L + i_C \quad \dots \textcircled{1}$$

$$= \frac{V_c}{R} + \frac{1}{L} \int V_c dt + C \frac{dV_c}{dt}$$

Differentiating both sides of $\textcircled{1}$,

$$0 = \frac{1}{R} V_c' + \frac{1}{L} V_c + C V_c''$$

$$\Rightarrow V_c'' + \frac{1}{RC} V_c' + \frac{1}{LC} V_c = 0 \quad \dots \textcircled{2}$$

$$\downarrow \text{Ch. Eqn} \quad v = ke^{\lambda t}$$

$$\lambda^2 + \frac{1}{RC} \lambda + \frac{1}{LC} = 0 \quad \dots \textcircled{3}$$

$$\Rightarrow \lambda = \frac{1}{2} \left\{ -\frac{1}{RC} \pm \sqrt{\frac{1}{R^2 C^2} - \frac{4}{LC}} \right\}$$

$$= \frac{1}{2} \left\{ -\frac{1}{RC} \pm \frac{1}{RC} \sqrt{1 - \frac{4R^2 C}{L}} \right\}$$

$$\boxed{\xi \triangleq \frac{1}{2R} \sqrt{\frac{L}{C}}} \\ w_n = \frac{1}{\sqrt{LC}}$$

$$\left. \right\} \Rightarrow \xi w_n = \frac{1}{2RC}$$

$$\Rightarrow \lambda = -\xi w_n \pm \xi w_n \sqrt{1 - \xi^2}$$

$$\Rightarrow \boxed{\lambda = -\xi w_n \pm j w_n \sqrt{1 - \xi^2}}$$

Useful format for N/W designing
not useful for problem solving

$R=0 \rightarrow$ nothing happens
 $R \rightarrow \infty \rightarrow$ under damping

$\propto R$ for series RLC
 $\propto \frac{1}{R}$ for parallel RLC

$$\lambda_{1,2} = \frac{1}{2} \left\{ -\frac{1}{18 \times 2} \pm \sqrt{\left(\frac{1}{18 \times 2}\right)^2 - \frac{4}{18 \times 2}} \right\}$$

$$= \frac{1}{2} \left\{ -4 \pm \sqrt{16 - 16} \right\}$$

$$= -2$$

Now,

$$v_c(t) = (A + Bt)e^{-2t}$$

$$v_c(0+) = 0 \Rightarrow A = 0$$

$$\therefore v_c(t) = Bte^{-2t}$$

$$I_c(0+) = I_{in} = 1 = CV'_c(0+) \quad (\because I_R(0+) = I_L(0+) = 0)$$

$$V'_c(t) = B(e^{-2t} - 2te^{-2t})$$

$$V'_c(0+) = B = I_{in}/C = 0.5$$


$$\therefore v_c(t) = 0.5te^{-2t} V.$$

- Current through an L cannot change instant.
- Voltage across a C cannot change instant.

$$i_L(t) = 0$$

$i_R(0+) = 0$ as, if $i_R \neq 0$, it will change the $v_c(0+)$.

Series RLC with AC excitation

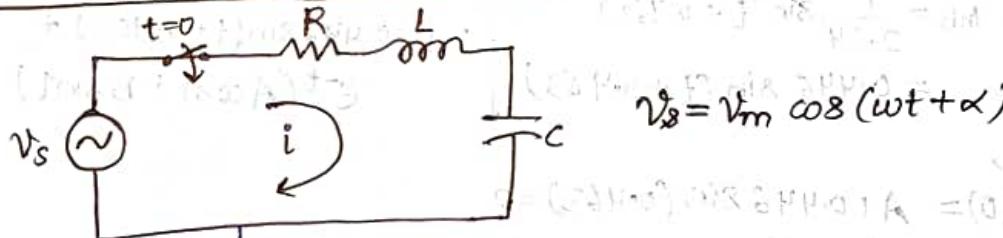

$$\text{For } t \geq 0, \quad v_s = v_R + v_L + v_C$$

$$\Rightarrow v_m \cos(\omega t + \alpha) = iR + Li' + \frac{1}{C} \int idt$$

Differentiating both sides,

$$\Rightarrow -v_m \omega \sin(\omega t + \alpha) = i'' + \frac{R}{L} i' + \frac{1}{LC} i$$

$$\text{Solution: } i = i_h + i_nh$$

$i_nh = \frac{v_m}{Z} \cos(\omega t + \alpha - \theta)$ can lag or lead depending on the reactive impedance.

$$\theta = \tan^{-1}\left(\frac{X}{R}\right)$$

$$(v_m \cos(\omega t + \alpha - \theta)) \cdot X = wL - \frac{1}{\omega C} \quad (ESP 1) \quad (1)j$$

Take $R = 2\Omega$, $L = 1H$, $C = 0.5F$, $v_s = 8\sin t$

$\cancel{R \neq 1 \Omega}$

$$\text{ch. eqn: } \lambda^2 + \frac{R}{L} \lambda + \frac{1}{LC} = 0$$

$$\Rightarrow \lambda = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}$$

$$\Rightarrow \lambda = -\frac{2}{2 \times 1} \pm \sqrt{\frac{4}{1} - \frac{4}{1 \times 1}}$$

$$= -1 \pm j1$$

$$\therefore i_h = e^{-t} (A \cos t + B \sin t)$$

$$\therefore i = \frac{1}{Z} \sin(t - \theta) + e^{-t} (A \cos t + B \sin t)$$

where

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \sqrt{4 + (1-2)^2}$$

$$= \sqrt{5} \approx 2.24$$

$$X = L - 2 = -1$$

$$\theta = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{-1}{2}\right) = -0.463$$

$$\therefore i_h = \frac{1}{2.24} \sin(t + 0.463)$$

$$= 0.446 \sin(t + 0.463)$$

$$\therefore i = 0.446 \sin(t + 0.463) + e^{-t} (A \cos t + B \sin t)$$

and,

$$i(0) = A + 0.446 \sin(0.463) = 0$$

$$\Rightarrow A \approx -0.2$$

$$V_L(0+) = V_B(0+) = 0 = \dot{i}(0+)$$

$$\therefore i(1) = e^{-1} (-0.2 \cos(1) + B \sin(1)) + 0.446 \sin(1 + 0.463)$$

$$\Rightarrow 1 [0.446 \cos(1 + 0.463) + \cancel{e^{-1}}(-A \sin(0) + B \cos(0)) = 0 \\ - \cancel{e^{-1}}(A \cos(0) + B \sin(0))]$$

$$\therefore 0.446 \cos(0.463) + B = 0$$

$$\Rightarrow B = A - 0.446 \cos(0.463) \Rightarrow B = -0.6$$


$$\therefore i(t) = 0.446 \sin(t + 0.463) - e^{-t} (0.2 \cos t + 0.6 \sin t).$$

$$\Rightarrow i(1) = 0.446 \sin(1.463) - \cancel{e^{-1}} (0.2 \cos 1 + 0.6 \sin 1)$$

$$= 0.4434 - 0.2255$$

$$= 0.2179 A$$


$$\approx 0.22 A$$

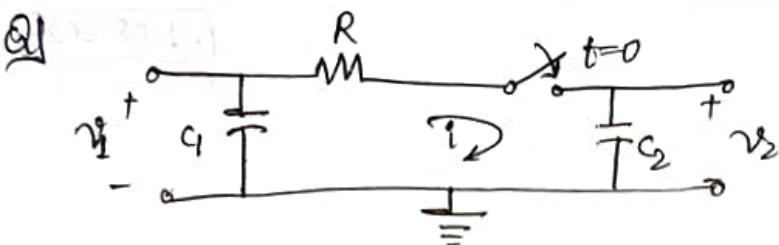

$$v_1(0-) = v_1 \quad \text{and} \quad v_2(0-) = v_2$$

Find $i(t)$, $v_1(t)$ & $v_2(t)$ for $t \geq 0$.

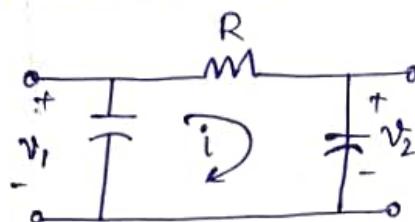Soln: Once switch is closed, the relevant ckt. becomes



Using KVL,

$$v_1 = iR + v_2 \quad \dots \textcircled{e1}$$

where, $\frac{C_1 dv_1}{dt} = -i \rightarrow$ discharging

$C_2 dv_2/dt = i \rightarrow$ charging

diff. $\textcircled{e1}$,

$$v_1' = i'R + v_2' \quad \dots \textcircled{e1}'$$

Using $\textcircled{e1}'$ and $\textcircled{e2}$,

$$\frac{-i}{C_1} = i'R + \frac{1}{C_2} i$$

$$\Rightarrow 0 = i'R + \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2}\right)}_{1/C_{eq}} i$$

$$\Rightarrow 0 = i' + \frac{1}{T} i, \text{ where } T = R C_{eq}$$


$$\Rightarrow i = K e^{-t/T}$$

$$\text{As } i(0) = \frac{v_1 - v_2}{R} = k,$$

(Assuming $v_1 > v_2$)

$$\therefore i = \frac{v_1 - v_2}{R} e^{-t/T}.$$
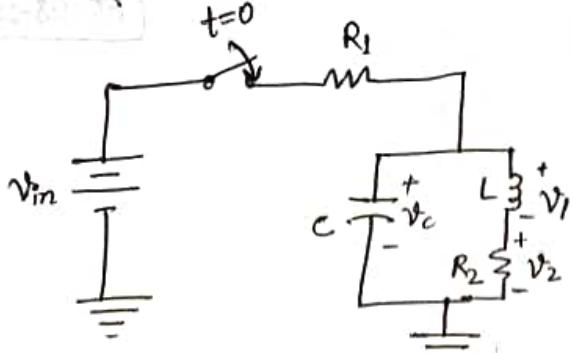
$$\frac{v_1 - v_2}{R} = (+0)^+ \frac{1}{R} + 0 = (+0)^+ \frac{1}{R} \therefore$$



Solve for:

$$\textcircled{a} \quad v_1 \text{ and } v_2 \text{ at } t=0^+$$


$$\textcircled{b} \quad v_1 \text{ and } v_2 \text{ as } t \rightarrow \infty$$

$$\textcircled{c} \quad v'_1(0^+), v'_2(0^+)$$

$$\textcircled{d} \quad v''_2(0^+).$$

Valkenburg
Exercise
Prob. 5-13


Soln: \textcircled{a}

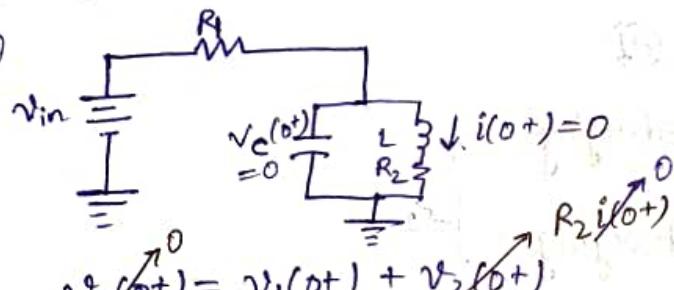

$$v_c(0^+) = v_1(0^+) + v_2(0^+)$$

$$\Rightarrow v_1(0^+) = v_2(0^+) = 0$$

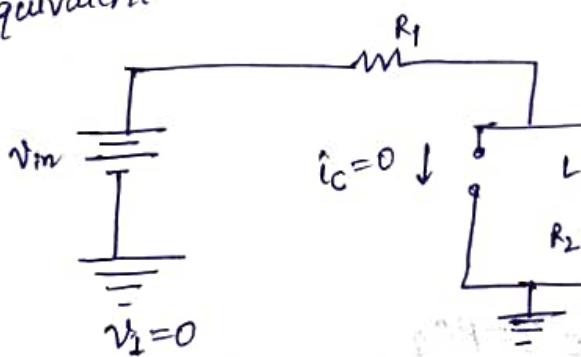\textcircled{b} Effective circuit as $t \rightarrow \infty$
equivalent



$$v_2 = \frac{R_2}{R_1 + R_2} v_{in}$$

$$\textcircled{c} \quad v_c(t) = v_1(t) + v_2(t)$$

$$\Rightarrow v'_c(t) = v'_1(t) + v'_2(t)$$

$$\Rightarrow v'_c(0^+) = v'_1(0^+) + v'_2(0^+)$$

$$\frac{1}{C} i_c(0^+)$$


$$\frac{1}{C} \frac{v_{in}}{R_1}$$

$$R_2 v'_1(0^+)$$

$$\therefore v'_2(0^+) = 0 \quad \text{and} \quad v'_1(0^+) = \frac{V_{IN}}{R_1 C}$$

$$\textcircled{d} \quad v_2''(0+) = i'' R_2 \\ = \frac{1}{L} v_1' R_2 \quad (\because i' = \frac{v_1}{L})$$
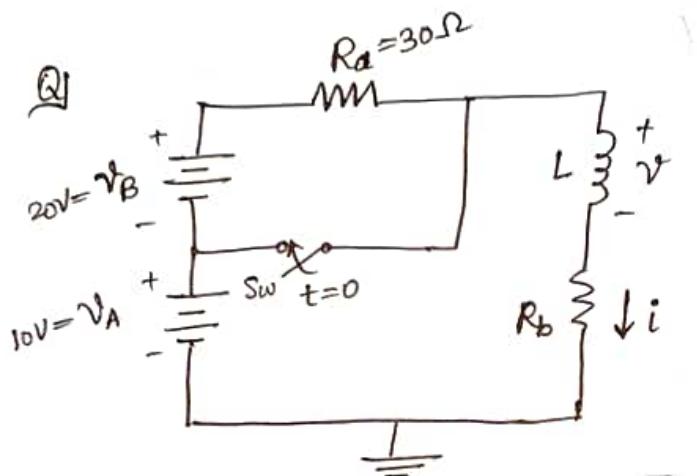
$$= \frac{R_2}{L R_1 C} v_{IN} \quad (\because v_1'(0+) = \frac{V_{IN}}{R_1 C})$$




$$L = 0.5 \text{ H}$$

$$R_b = 20 \Omega$$


Find and plot $v(t)$ & $i(t)$ for $t \geq 0$.

Q5: Initially,

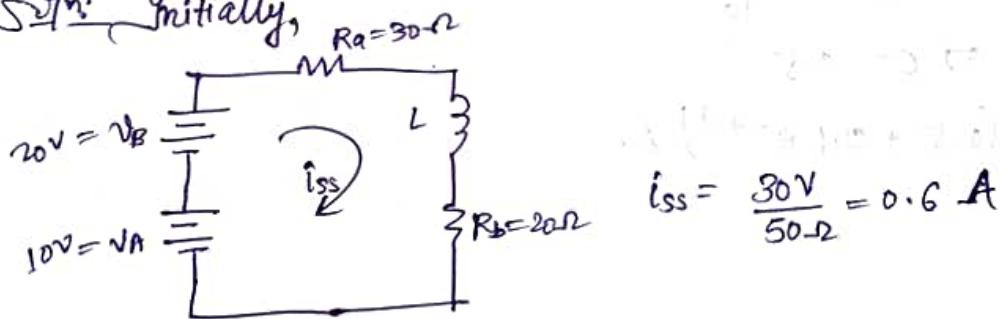

$$i_{ss} = \frac{30V}{50\Omega} = 0.6 \text{ A}$$

The relevant ckt. for $t \geq 0$:

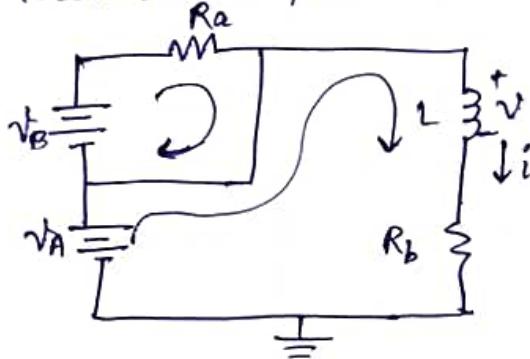

$$v_A = i' R_b + R_b i'$$

$$\Rightarrow 0 = L i'' + R_b i'$$

$$\Rightarrow 0 = v' + \frac{R_b}{L} v$$

$$\Rightarrow \int \frac{dv}{v} = -\frac{R_b}{L} \int dt$$

$$\Rightarrow v = K e^{-t/\tau}, \quad \tau = \frac{L}{R_b}$$

$$\text{At } t=0^+, v(0^+) = v_A - i(0^+) R_b$$

$$= 10 - 0.6 \times 20$$

$$= -2 \text{ V}$$

$$\therefore v = -2 e^{-t/2}$$

$$= -2 e^{-40t} \text{ V.}$$

$$\text{and, } \text{given LCR circuit } i(t) = \int \frac{v}{L} dt$$

$$= \frac{1}{0.5} \int -2 e^{-40t} dt$$

$$i(t) = -4 \left[\frac{e^{-40t}}{-40} \right] + C$$

$$= \frac{e^{-40t}}{10} + C$$

$$\text{At } t=0^+, i(0^+) = 0.6 \text{ A}$$


$$\Rightarrow 0.6 = \frac{1}{10} + C$$

$$\Rightarrow C = 0.5$$

$$\therefore i(t) = (0.5 + 0.1 e^{-40t}) \text{ A.}$$

MAGNETIC CIRCUITS REVIEW

Background

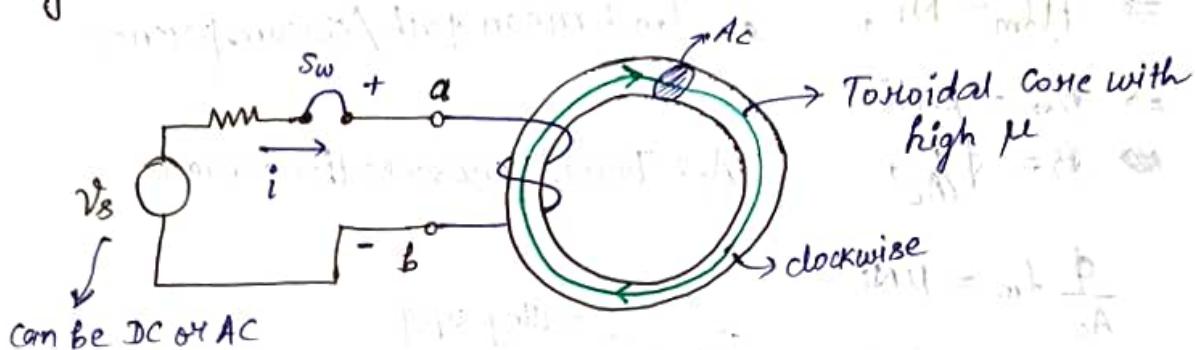

Once S_w is connected, $V_{ab} \approx v_s$

$i \xrightarrow[\text{up}]{\text{sets}}$ Magnetic field, ϕ

$$\phi = \Psi/N, \quad \Psi: \text{total flux linkage of coil}$$

$$\Psi = \int V_{ab} dt \leftarrow \text{Faraday's law}$$

$$= N \phi$$


Review of L, Ni, ϕ

$$L \stackrel{\Delta}{=} \Psi/i$$

Assumptions:

#1. Effect of electromagnetic radiation is negligible.

#2.

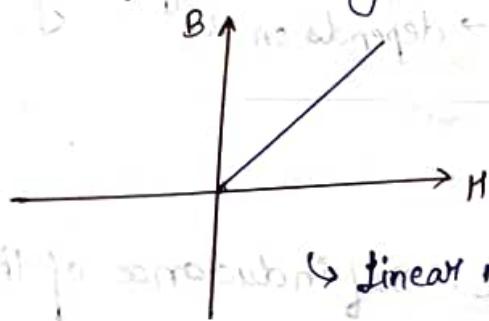

$$B = \mu H \quad \text{constant}$$

↳ linear magnetic field

#3. Magnetic ϕ path is well-defined.

Ampere's Circuital Law:

$$\oint \vec{H} \cdot d\vec{l} = i_{\text{enclosed}} = Ni$$

$$\Rightarrow Hl_m = Ni, \quad l_m: \text{mean path/circumference}$$

$$\Rightarrow Bl_m = \mu Ni$$

$$\Rightarrow B = \frac{\phi}{A_c}, \quad A_c: \text{Toroid cross-sectional area}$$

$$\frac{\phi}{A_c} l_m = \mu Ni \quad \xrightarrow{\text{setting up } \phi}$$

$$\Rightarrow \phi = Ni \frac{\mu A_c}{l_m} = \frac{Ni}{\left(\frac{l_m}{\mu A_c}\right)} \quad \begin{matrix} \text{setting up } R \\ \left(\frac{l_m}{\mu A_c}\right) \xrightarrow{\text{reluctance}} R \end{matrix}$$

Resistance

$$\# \quad \phi \xleftrightarrow[\text{to}]{\text{analogous}} i$$

$$Ni \xleftrightarrow{} e$$

$$R \xleftrightarrow{} R$$

Inductance,

$$L = \frac{\psi}{i} = \frac{Ni}{i}$$

$$= \frac{N}{i} \frac{Ni}{R}$$

$$= \frac{N^2}{R}$$


$$= \frac{N^2 A_c \cdot \mu}{l_m} \quad \begin{matrix} \rightarrow N, l, A_c \text{ are fixed by design/geometry} \\ \rightarrow \text{depends on } \mu \end{matrix}$$

$$V_s = V_{ab} = \frac{d\psi}{dt} = \frac{d}{dt}(Li)$$

$$\cong L \frac{di}{dt}, \quad L: \text{self-inductance of the coil}$$

Magnetically Coupled Circuits (MCC)

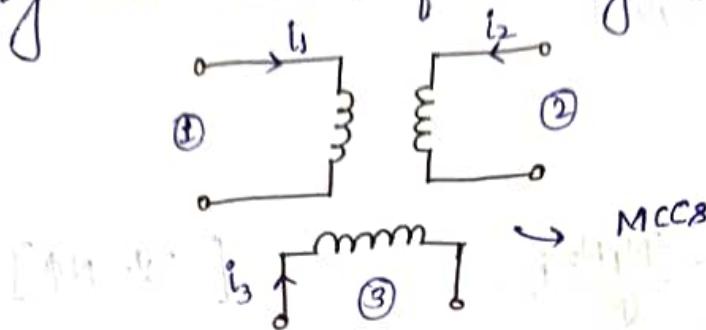→ Circuits/coils are said to be magnetically coupled, if 'i' flowing through one leads to flux linkage in another coil.




In such case,

ψ_1 : total flux linkage with coil 1

$$= \underbrace{L_{11} i_1}_{\Psi_{11}} + \underbrace{M_{12} i_2}_{\Psi_{12}} + \underbrace{M_{13} i_3}_{\Psi_{13}},$$

M₁₂: Mutual inductance b/w ① & ②
due to current in ②.

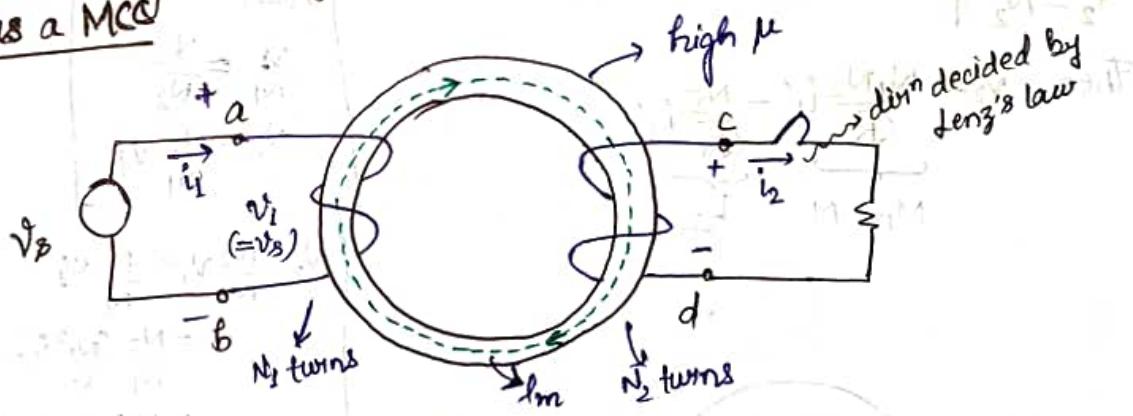2 Winding Transformer (2 wdg. T/f):
as a MCC \rightarrow high μ



ϕ → affected by i_1 and i_2

$$\oint \vec{H} \cdot d\vec{l} = N_1 i_1 - N_2 i_2 \\ = H l m$$

$$\Rightarrow H = \frac{N_1 i_1 - N_2 i_2}{l}$$

$$\Rightarrow \phi = BA_c = \mu H A_c = \frac{N_1 i_1 - N_2 i_2}{\text{lm}} \cdot \mu A_c$$

$$= \frac{N_1 i_1 - N_2 i_2}{(\text{lm}/\mu A_c)}$$

$$\Rightarrow \phi = \frac{N_1}{R} i_1 - \frac{N_2}{R} i_2$$

$$\text{Then, } \Psi_1 = N_1 \phi = \frac{N_1^2}{R} i_1 - \frac{N_1 N_2}{R} i_2. \quad [\Psi = N \phi]$$

$$L_{11} \triangleq \frac{N_1^2}{R} \rightarrow \text{Self inductance of } ①$$

$$\mu_{12} \triangleq \frac{N_1 N_2}{R} \rightarrow \text{Mutual inductance b/w coil 1 & 2.}$$

Then,


$$\Psi_1 = L_{11} i_1 - M_{12} i_2$$

$$V_1 = \Psi_1' = L_{11} i_1' - M_{12} i_2'$$

$$\Psi_2 = N_2 \phi$$

$$\text{Then, } V_2 = \frac{N_1 N_2}{R} i_1' - \frac{N_2^2}{R} i_2'$$
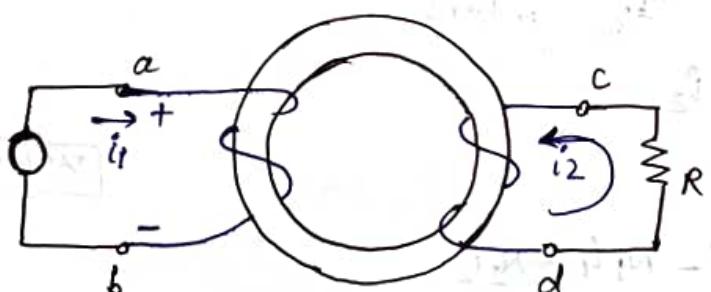
$$\underbrace{}_{M_{12}=M} \quad \underbrace{}_{L_{22}}$$




Also,

$$\frac{V_1}{N_1} = \frac{\Psi_2}{N_2}$$



$$V_2 = \frac{N_2}{N_1} V_1$$
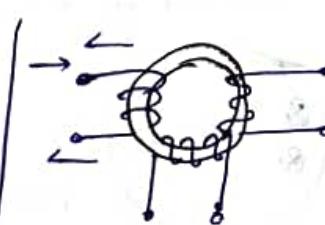
$$\left[\begin{aligned} N_2 &= \frac{N_2}{N_1} V_1 = \frac{N_2}{N_1} \Psi_1' \\ &= \frac{N_2}{N_1} \left(\frac{N_1^2}{R} i_1' - \frac{N_1 N_2}{R} i_2' \right) \\ &= \frac{N_1 N_2}{R} i_1' - \frac{N_2^2}{R} i_2' \end{aligned} \right]$$





Dot Convention

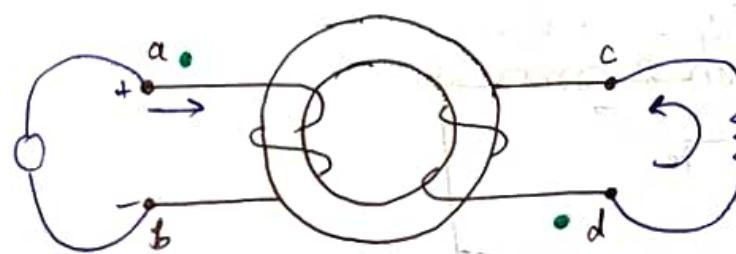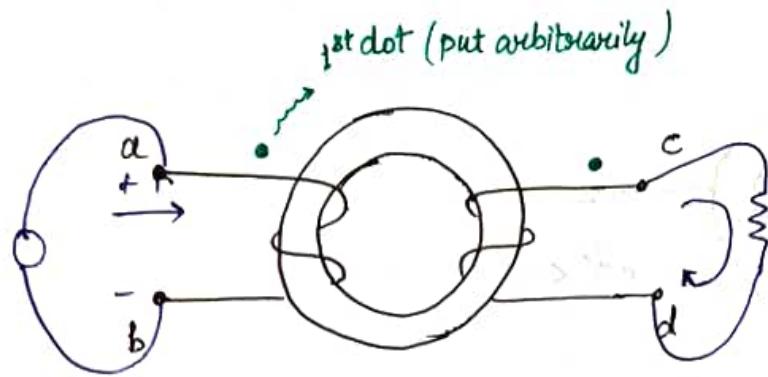→ Current flowing into 'dot' terminals leads to additive flux.



Eg.

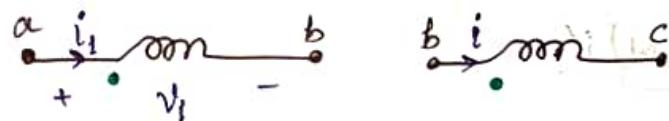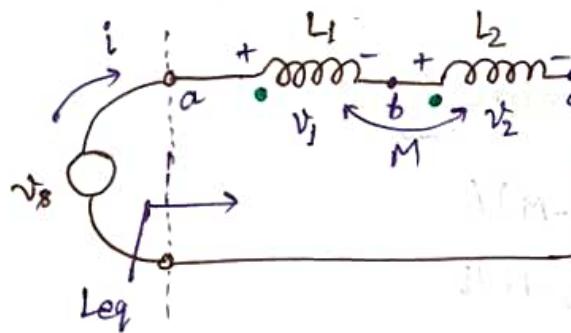

$$v_1 = \Psi_1' , \quad \Psi_1 = L_1 i_1 + M i_2 \\ = (L_1 + M) i_1$$

$$\therefore v_1 = (L_1 + M) i_1'$$

$$\Psi_2 = L_2 i + M i_1 \\ = (L_2 + M) i$$


$$\Rightarrow v_2 = (L_2 + M) i_2'$$

Then,

$$v_s = v_1 + v_2 = (L_1 + M) i_1' + (L_2 + M) i_2' = nV$$

$$\Rightarrow v_s = \underbrace{(L_1 + L_2 + 2M)}_{\text{Leg}} i' + (n - 1) i_2' +$$
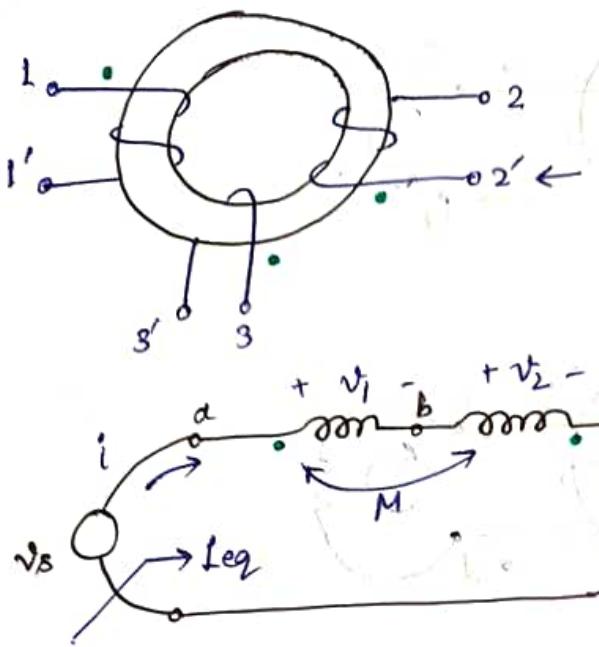
$$\begin{aligned} & v_s = (L_1 + L_2 + 2M) i' + (n - 1) i_2' + (1 - n) i_1' \\ & \quad \{ (n - 1) M + 2M \} i' + \end{aligned}$$




$$v_1 = \psi_1' ; \quad \psi_1 = L_1 i - Mi = (L_1 - M)i$$

$$v_2 = \psi_2' ; \quad \psi_2 = L_2 i - Mi = (L_2 - M)i$$

$$v_B = v_1 + v_2$$

$$= \underbrace{(L_1 + L_2 - 2M)}_{L_{eq}} i'$$

Q) Valkenburg, ch-5, Q.22.

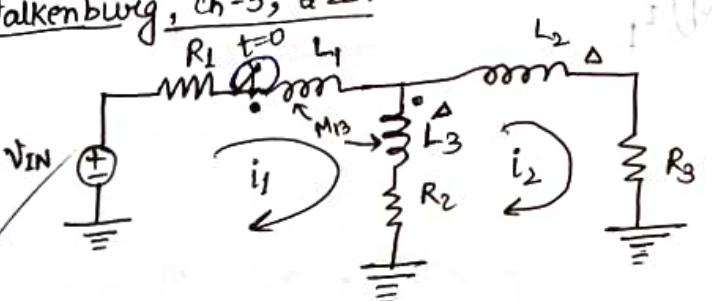

Find $i_1'(0+)$ and $i_2'(0+)$.

Soln:

$$V_{IN} = R_1 i_1 + R_2 (i_1 - i_2) + \{ L_1 i_1 + M_{13} (i_1 - i_2) \}' + \{ L_3 (i_1 - i_2) + M_{13} i_1 - M_{23} i_2 \}'$$

$$0 = R_2 (i_2 - i_1) + R_3 i_2 + \{ L_3 (i_2 - i_1) - M_{13} i_1 + M_{23} i_2 \}' + \{ L_2 i_2 + M_{23} (i_2 - i_1) \}'$$

$$i_1(i_1 - i_2) =$$

$$i_2(i_2 - i_1) =$$

$$M_{13}$$

$$M_{23}$$

$\rightarrow 1 \& 2$ are not coupled

$$\Rightarrow V_{IN} = (R_1 + R_2) i'_1 - R_2 i'_2 + \{L_1 + 2M_{13} + L_3\} i'_1 \\ + \{-M_{13} - L_3 - M_{13}\} i'_2 \dots \textcircled{e1}$$

$$0 = -R_2 i'_1 + (R_3 + R_2) i'_2 + \{L_3 - M_{13} - M_{23}\} i'_1 \\ + \{L_3 + M_{23} + L_2 + M_{23}\} i'_2 \dots \textcircled{e2}$$

As $i'_1(0+) = i'_2(0+) = 0$,

$$\textcircled{e2} \Rightarrow V_{IN} = \{L_1 + L_3 + 2M_{13}\} i'_1(0+) - \{M_{13} + L_3 + M_{23}\} (i'_2(0+)) \dots \textcircled{e3}$$


$$\textcircled{e3} \Rightarrow 0 = -\{L_3 + M_{13} + M_{23}\} i'_1(0+) + (L_3 + L_2 + 2M_{23}) i'_2(0+) \\ \Rightarrow (L_3 + M_{13} + M_{23}) i'_1(0+) = (L_3 + L_2 + 2M_{23}) i'_2(0+) \dots \textcircled{e4}$$

Using $\textcircled{e4}$ in $\textcircled{e3}$,

$$V_{IN} = (L_1 + L_3 + 2M_{13}) i'_1(0+) - i'_1(0+) \frac{(M_{13} + L_3 + M_{23})(L_3 + M_{13} + M_{23})}{(L_3 + L_2 + 2M_{23})}$$

$$\Rightarrow i'_1(0+) = \frac{V_{IN}}{(L_1 + L_3 + 2M_{13}) - (M_{13} + L_3 + M_{23}) \frac{(L_3 + M_{13} + M_{23})}{(L_3 + L_2 + 2M_{23})}}$$

Q1 Valkenburg, ch-5, Prob. 24

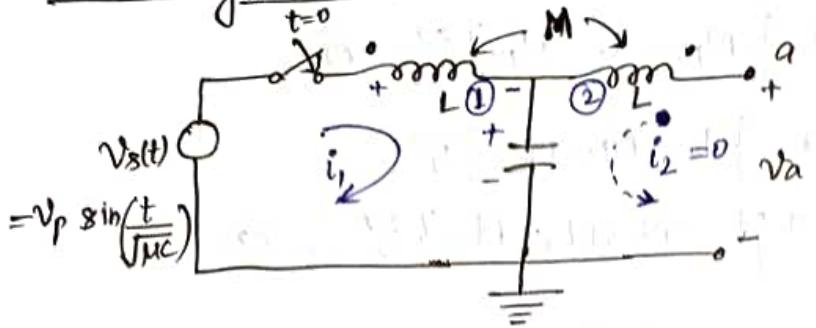

Initially relaxed N/w.

Find $V_a(0+)$, $V_a'(0+)$ and $V_a''(0+)$

Soln:

$$V_s = V_L + V_C; \quad i_1 = i_2 = 0$$

$$V_L = V_1' = L i_1' + M i_2' = 0$$

$$V_s = (L i_1' + M i_2') + V_C \quad \dots \textcircled{e1}$$

$$V_a = (L i_1' + M i_1') + V_C \quad \dots \textcircled{e2}$$

$$-V_C + V_{12} + V_a = 0$$

$$-V_C + \{L i_2 - M i_1\}' + V_a = 0$$

$$\Rightarrow V_s - L i_1' = V_a - M i_1'$$

$$\Rightarrow V_s = V_a + (1-M)i_1' \quad \dots \textcircled{e3}$$

13-09-2023

Initial conditions:

$$i_1(0+) = 0, \quad V_C(0+) = 0$$

$$V_L(0+) = 0 \Rightarrow i_1'(0+) = 0 \quad (\text{as } V_s(0+) = 0)$$

$$\therefore V_a(0+) = 0$$

$$\textcircled{e3} \Rightarrow V_s = V_a + (1-M)i_1''$$

$$\Rightarrow V_s(0+) = V_a(0+) + (1-M)\frac{V_L'(0+)}{L} \quad \dots \textcircled{e4} \quad (\because V_L = L i_1')$$

$$\textcircled{e5} \Rightarrow V_s = V_L + V_C$$

$$\Rightarrow V_s' = V_L' + V_C'$$

$$= V_L' + \frac{1}{C} i_1' \quad \dots \textcircled{e5}$$

$$\Rightarrow V_L'(0+) = V_s'(0+) - \frac{1}{C} i_1(0+)$$

$$= \frac{V_p}{\mu c} \quad \dots \textcircled{e6} \quad (\because V_s = V_p \sin(\frac{t}{\mu c}))$$

$$\textcircled{e4} \Rightarrow V_a'(0+) = \frac{V_p}{\mu c} - \frac{(1-M)}{L} \cdot \frac{V_p}{\mu c}$$

$$= \frac{\mu}{L} \cdot \frac{V_p}{\mu c} = \boxed{\frac{V_p}{L} \sqrt{\mu/c}}$$

LAPLACE TRANSFORM (LT)

↓
From a Network Analysis perspective

Agenda #1 Why study LT?

#2 The basic transform

#3 Some properties of LT (2 keys)

Time Domain (TD) $\xrightleftharpoons[\text{Inverse LT}]{\text{LT}}$

Frequency Domain (FD)


SISO

Single Input
Single Output

MIMO

Multiple Input
Multiput output

Advantage 1:

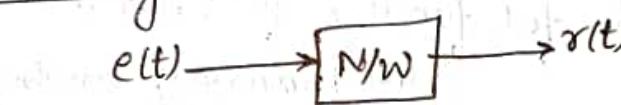

Apply
relevant
laws

ODEs, ICs
(Initial
conditions)

f domain
Series of
algebraic
equations



R(s)

Inv. LT


r(t)

Advantage 2:

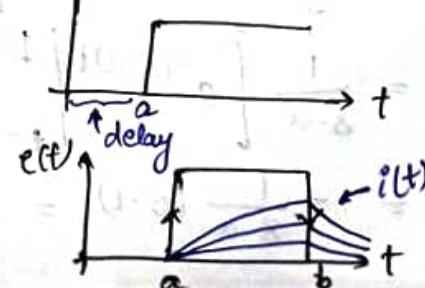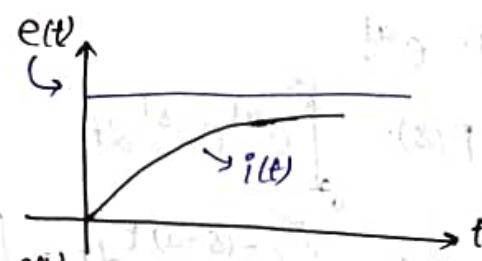LT handles ~~excitations~~ excitations like pulse, impulse very effectively.



The Basic Transform

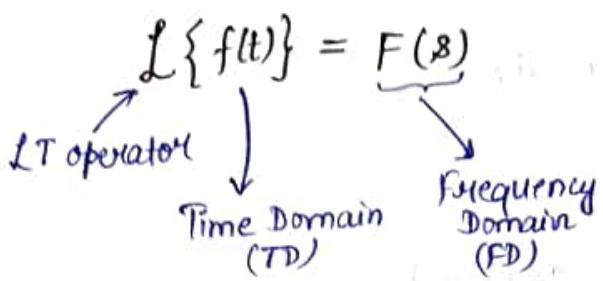

s : complex frequency

$$s = \sigma + j\omega$$

$$\mathcal{L}\{f(t)\} = F(s) \triangleq \int_{-\infty}^{\infty} e^{-st} f(t) dt$$

$$\hookrightarrow F(s) = \int_{-\infty}^{\infty} e^{-st} f(t) dt, \text{ for function for which } f(0-) \neq f(0+)$$

(like hammering something & lifting quickly)

Book
↓
Kreyszig

for $F(s)$ to exist,

$$\int_{-\infty}^{\infty} e^{-st} |f(t)| dt \rightarrow \text{finite}$$

if $f(t) = A$,

$$\begin{aligned} F(s) &= \int_{-\infty}^{\infty} A e^{-st} dt \\ &= A \left[-\frac{1}{s} e^{-st} \right]_{-\infty}^{\infty} \\ &= \frac{A}{s} \left\{ -e^{-st} \Big|_{\infty}^{\infty} + e^{-st} \Big|_{0-}^{0+} \right\} \end{aligned}$$

$$= A/s \text{ for } \operatorname{Re}\{s\} \geq 0.$$

if $f(t) = e^{at}$,

$$\begin{aligned} F(s) &= \int_{-\infty}^{\infty} e^{at} e^{-st} dt \\ &= \int_{-\infty}^{\infty} e^{-(s-a)t} dt = \left[-\frac{1}{s-a} e^{-(s-a)t} \right]_{-\infty}^{\infty} \\ &= \frac{1}{s-a} \left[e^{-(s-a)t} \Big|_{t=0}^1 - e^{-(s-a)t} \Big|_{t \rightarrow \infty} \right] \\ &= -\frac{1}{s-a} (0-1) = \frac{1}{s-a}, \text{ for } \operatorname{Re}\{s\} \geq a. \end{aligned}$$

a : abscissa of convergence

$$\xrightarrow{\text{LT}} f(t) \xleftarrow[\text{Inverse LT}]{\quad} F(s)$$

$$f(t) = \frac{1}{2\pi j} \int_{\sigma_1 - j\omega}^{\sigma_1 + j\omega} F(s) e^{st} ds$$

Properties:

① Uniqueness: $f(t) \xleftrightarrow[\text{unique}]{\text{mapping is}} F(s)$

② Linearity: $\mathcal{L}\{f(t)\} = F(s)$ and $\mathcal{L}\{g(t)\} = G(s)$

$$\text{Then, } k_1 \mathcal{L}\{f(t)\} + k_2 \mathcal{L}\{g(t)\} = k_1 F(s) + k_2 G(s)$$

22-09-2023


Laplace Transform (LT)

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^\infty e^{-st} f(t) dt$$

LT
 { Uniqueness
 Linearity }

$$\rightarrow \mathcal{L}\{1\} = \frac{1}{s}, \quad \mathcal{L}\{k_0\} = \frac{k_0}{s}$$
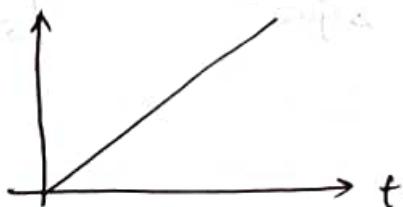
$$\mathcal{L}\{e^{at}\} = \frac{1}{s-a}$$



$f(t) = At \leftarrow \text{Ramp function}$

$$\text{Ex. } f(t) = t$$

$$\mathcal{L}\{f\} = \int_0^\infty t e^{-st} dt$$

$$= \int_0^\infty t \left(\frac{-1}{s}\right) \frac{d}{dt} (e^{-st}) dt = -\frac{1}{s} \int_0^\infty t d(e^{-st})$$

$$\begin{aligned}
 &= -\frac{1}{8} \left[t e^{-8t} - \int e^{-8t} dt \right]_{0^-}^{\infty} \\
 &= -\frac{1}{8} \left[\frac{1}{8} e^{-8t} + t e^{-8t} \right]_{0^-}^{\infty} \\
 &= -\frac{1}{8^2} e^{-8t} \Big|_{0^-}^{\infty} \rightarrow \frac{1}{8} \left[t e^{8t} \right]_{0^-}^{\infty} \\
 &= \frac{1}{8^2}
 \end{aligned}$$

So, $\mathcal{L}\{t\} = \frac{1}{8^2}$

$$\mathcal{L}\{t^n\} = \frac{n!}{s^{n+1}}$$

Eq. $f(t) = \cos \omega_0 t = \frac{1}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t})$

Then,

$$\begin{aligned}
 F(s) &= \int_0^\infty \cos \omega_0 t e^{-st} dt \\
 &= \frac{1}{2} \int_0^\infty (e^{j\omega_0 t} + e^{-j\omega_0 t}) e^{-st} dt \\
 &= \frac{1}{2} \int_0^\infty [e^{-(s-j\omega_0)t} + e^{-(s+j\omega_0)t}] dt \\
 &= \frac{1}{2} \left[-\frac{1}{s-j\omega_0} e^{-(s-j\omega_0)t} \Big|_{0^-}^\infty - \frac{1}{s+j\omega_0} e^{-(s+j\omega_0)t} \Big|_{0^-}^\infty \right] \\
 &= \frac{1}{2} \left[\frac{1}{s-j\omega_0} + \frac{1}{s+j\omega_0} \right] \\
 &= \frac{8}{s^2 + \omega_0^2}
 \end{aligned}$$

$$\therefore \mathcal{L}\{\cos \omega_0 t\} = \frac{8}{s^2 + \omega_0^2}$$

Similarly, $\mathcal{L}\{\sin \omega_0 t\} = \frac{\omega_0}{s^2 + \omega_0^2}$

$$\text{Eg, } f(t) = e^{at}$$

$$L\{1\} = \frac{1}{s}, L\{e^{at}\} = \frac{1}{s-a}$$

$$L\{K_0 e^{at}\} = \frac{K_0}{s-a}$$

$$L\left\{e^{at} \cdot \frac{1}{2}(e^{j\omega_0 t} + e^{-j\omega_0 t})\right\} = L\left\{e^{at} \cos \omega_0 t\right\}$$

$$= \int_{-\infty}^{\infty} \frac{e^{at}}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t}) dt$$

$$= \frac{1}{2} \int_{-\infty}^0 [e^{(a+j\omega_0)t} + e^{(a-j\omega_0)t}] dt$$

$$= \frac{1}{2} \left[\frac{e^{(a+j\omega_0)t}}{a+j\omega_0} + \frac{e^{(a-j\omega_0)t}}{a-j\omega_0} \right]_{-\infty}^0$$

$$= \frac{1}{2} \left[\frac{e^{-(a+j\omega_0)t}}{a+j\omega_0} + \frac{e^{-(a-j\omega_0)t}}{a-j\omega_0} \right]_{-\infty}^0$$

$$= \frac{1}{2} \left[\frac{1}{s-a-j\omega_0} + \frac{1}{s-a+j\omega_0} \right]$$

$$\therefore L\{e^{at} \cos \omega_0 t\} = \frac{s-a}{(s-a)^2 + \omega_0^2}$$

$$\text{Similarly, } L\{e^{at} \sin \omega_0 t\} = \frac{\omega_0}{(s-a)^2 + \omega_0^2}.$$

S-shifting Theorem

If $L\{f(t)\} = F(s)$, then

$$L\{e^{at} f(t)\} = F(s-a).$$

Q) find the laplace inverse of

$$F(s) = \frac{3s - 137}{s^2 + 2s + 401}$$

Soln: $F(s) = \frac{3(s+1) - 140}{(s+1)^2 + 20^2}$

$$= 3 \cdot \frac{(s+1)}{(s+1)^2 + 20^2} - 7 \cdot \frac{20}{(s+1)^2 + 20^2}$$

$$\begin{aligned} f(t) &= L^{-1}\{F(s)\} = 3 L^{-1}\left\{\frac{s+1}{(s+1)^2 + 20^2}\right\} - 7 L^{-1}\left\{\frac{20}{(s+1)^2 + 20^2}\right\} \\ &= 3e^{-t} \cos 20t - 7e^{-t} \sin 20t. \end{aligned}$$

Some commonly used transforms so far: $\rightarrow (s-3)^{-1} = \{f(t)\}$

$f(t)$	$L\{f(t)\}$
1	$\frac{1}{s}$
t	$\frac{1}{s^2}$
t^n	$\frac{n!}{s^{n+1}}$
e^{at}	$\frac{1}{s-a}$
$\cos \omega_0 t$	$\frac{s}{s^2 + \omega_0^2}$
$\sin \omega_0 t$	$\frac{\omega_0}{s^2 + \omega_0^2}$

- Shifting by s:

If $L\{f(t)\} = F(s)$,

then $L\{e^{at} f(t)\} = F(s-a)$.

$$\begin{aligned}
 L\left\{\frac{df(t)}{dt}\right\} &= \int_{0^-}^{\infty} e^{-st} \frac{df(t)}{dt} dt \\
 &= \int_{0^-}^{\infty} e^{-st} df \\
 &= \left[e^{-st} f(t) - \int f(t) d(e^{-st}) \right]_{0^-}^{\infty} \\
 &= \left[e^{-st} f(t) \right]_{0^-}^{\infty} + s \int_{0^-}^{\infty} f(t) e^{-st} dt - s \int f(t) e^{-st} dt \\
 &= e^{-st} f(t) \Big|_{t \rightarrow \infty} - e^{-st} f(t) \Big|_{t \rightarrow 0^-} + s F(s)
 \end{aligned}$$

$$\therefore L\left\{\frac{df(t)}{dt}\right\} = s F(s) - f(0^-)$$

$$\begin{aligned} L\{f''(t)\} &= sF(s) - f'(0) \\ \frac{df'(t)}{dt} &= s^2F(s) - sf(0) - f'(0). \end{aligned}$$

- $L\{f'(t)\} = sF(s) - f(0)$
- $L\{f''\} = s^2F(s) - sf(0) - f'(0)$

- $L\left\{\int_0^t f(t) dt\right\}$
Let $\int_0^t f(t) dt = g(t) \rightarrow f(t) dt = d\{g(t)\}$

Then, $L\left\{\int_0^t f(t) dt\right\}$

$$= \int_0^\infty g(t)e^{-st} dt = \int_0^\infty g(t) \left(-\frac{1}{s}\right) \frac{d}{dt}(e^{-st}) dt$$

$$= -\frac{1}{s} \int_0^\infty g(t) d(e^{-st})$$

$$= -\frac{1}{s} \left[g(t)e^{-st} - \int e^{-st} d\{g(t)\} \right]_0^\infty$$

$$= -\frac{1}{s} \left[g(t)e^{-st} - \int e^{-st} f(t) dt \right]_0^\infty$$

$$= -\frac{1}{s} \left[g(t)e^{-st} \right]_0^\infty + \frac{1}{s} \int_0^\infty e^{st} f(t) dt$$

$$= \frac{1}{s} g(0) + \frac{1}{s} \underbrace{\int_0^\infty e^{st} f(t) dt}_{F(s)}$$

$$\therefore L\left\{\int_0^t f(t) dt\right\} = \frac{1}{s} F(s)$$

Eg. ① Solving an ODE. (Find $y(t)$).

$$y'(t) + 40y(t) = 20 \rightarrow \text{e1}$$

$$\& y(0) = 0.6$$

Soln: Taking LT of e1,

$$\mathcal{L}\{y'(t) + 40y\} = \mathcal{L}\{20\}$$

$$\Rightarrow \mathcal{L}\{y'\} + 40\mathcal{L}\{y\} = \mathcal{L}\{20\}$$

$$\Rightarrow 8Y(s) - y(0) + 40Y(s) = \frac{20}{s}$$

$$\Rightarrow (8+40)Y(s) =$$

$$\Rightarrow 8Y(s) + y(0) + 40Y(s) = 20/s$$

$$\Rightarrow (8+40)Y(s) = 0.6 + 20/s$$

$$\Rightarrow Y(s) = \frac{0.6}{8+40} + \frac{20}{8(8+40)}$$

$$= \frac{0.6}{8+40} + 0.5 \frac{8+40-8}{8(8+40)} =$$

$$= \frac{0.6}{8+40} + \frac{0.5}{8} - \frac{0.5}{8+40}$$

$$= \frac{0.5}{8} + 0.1 \frac{1}{8+40}$$

$$\therefore y(t) = 0.5 + 0.1 e^{-40t}$$

Eg. ② Solving an ODE

$$y'' + 7y' + 12y = 21e^{3t} \dots \text{e2} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{solve for } y(t).$$

$$y(0) = 3.5, y'(0) = -10.$$


Soln: Taking LT of e2,

$$\mathcal{L}\{y''\} + 7\mathcal{L}\{y'\} + 12\mathcal{L}\{y\} = 21\mathcal{L}\{e^{3t}\}$$

$$\Rightarrow 8^2Y(s) - 8y(0) - y'(0) + 7\{8Y(s) - y(0)\} + 12Y(s) = \frac{21}{8-3}$$


$$\Rightarrow \underbrace{(s^2 + 7s + 12)}_{(s+3)(s+4)} y(s) - (8+7)y(0) - y'(0) = \frac{21}{s-3} \rightarrow \text{Pole}=3 \rightarrow \text{diverge}$$

$$\begin{aligned}
\Rightarrow y(s) &= \frac{8+7}{(s+3)(s+4)} y(0) + \frac{y'(0)}{(s+3)(s+4)} + \frac{21}{(s-3)(s+3)(s+4)} \\
&= \frac{8+7}{(s+3)(s+4)} \cdot \frac{7}{2} - \frac{10}{(s+3)(s+4)} + \frac{21}{(s-3)(s+3)(s+4)} \\
&= \frac{3.5s}{(s+3)(s+4)} + \frac{14.5}{(s+3)(s+4)} + \frac{21}{(s-3)(s+4)(s+3)} \\
&= 3.5s \cdot \frac{(s+4)-(s+3)}{(s+4)(s+3)} + 14.5 \cdot \frac{(s+4)-(s+3)}{(s+4)(s+3)} + \frac{21}{(s-3)(s+3)(s+4)} \\
&= \frac{3.5s}{(s+3)} - \frac{3.5s}{(s+4)} + \frac{14.5}{(s+3)} - \frac{14.5}{(s+4)} + \frac{21/12}{(s-3)} + \frac{(-7)_2}{(s+3)} + \frac{s}{(s+4)} \\
&= \frac{3.5s}{s+3} - \frac{3.5s}{s+4} + \frac{11}{s+3} - \frac{11.5}{s+4} + \frac{0.5}{s-3} \\
&= \left[3.5 - \frac{10.5}{(s+3)} \right] + \left[-3.5 + \frac{14}{(s+4)} \right] + \frac{11}{s+3} - \frac{11.5}{s+4} + \frac{0.5}{s-3} \\
&= \frac{0.5}{s+3} + \frac{2.5}{s+4} + \frac{0.5}{s-3} \\
\therefore y(t) &= 0.5e^{-3t} + 2.5e^{-4t} + 0.5e^{+3t}
\end{aligned}$$

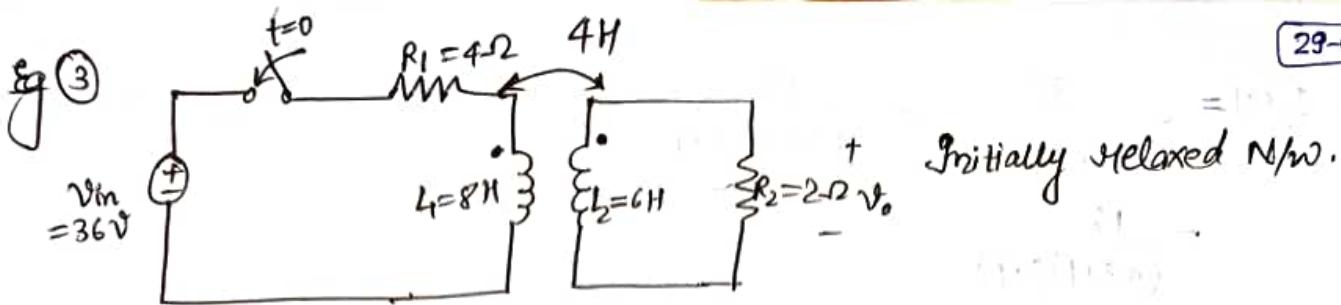

Find $V_0(t)$ for $t \geq 0$.

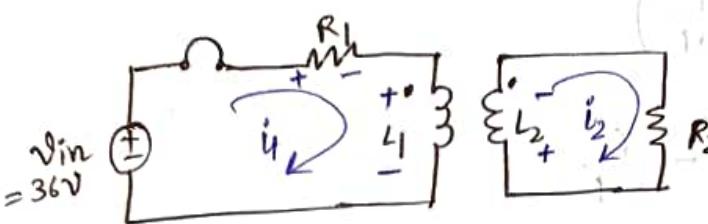Soln: For $t \geq 0$, the relevant circuit is,



$$V_{IN} = R_1 i_1 + L_1 i_1' - M i_2' \quad \dots (1)$$

$$0 = L_2 i_2' + M i_1' + i_2 R_2 \quad \dots (2)$$

OR

$$V_{IN} = R_1 i_1 + L_1 i_1' + M i_2' \dots (1)$$

$$V_{L2} = L_2 i_2' + M i_1'$$

$$V_o = -i_2 R_2$$

$$\therefore L_2 i_2' + M i_1' + i_2 R_2 = 0 \dots (2)$$

Taking LT of (1),

$$\frac{V_{IN}}{8} = R_1 I_1(s) + L_1 \{8 I_1(s) - i_1(0)\} - M \{8 I_2(s) - i_2(0)\}$$

$$\Rightarrow \frac{V_{IN}}{8} = R_1 I_1(s) + 8 L_1 I_1(s) - 8 M I_2(s) \dots (3)$$

Taking LT of (2),

$$0 = 8 L_2 I_2(s) - 8 M I_1(s) + I_2(s) R_2 \dots (4)$$

Using the parametric values,

$$0 = 68 I_2(s) - 48 I_1(s) + 2 I_2(s)$$

$$\Rightarrow I_1(s) = \frac{1}{48} [68 + 2] I_2(s) \dots (5)$$

$$(3) \Rightarrow \frac{36}{8} = 4 I_1(s) + 88 I_1(s) - 48 I_2(s)$$

$$= (4 + 88) I_1(s) - 48 I_2(s)$$

Substituting $I_1(s)$ from (5),

$$\frac{36}{8} = \left[(4 + 88) \cdot \frac{1}{48} (68 + 2) - 48 \right] I_2(s)$$

$$= \left[\frac{2 (1 + 28) (38 + 1)}{8} - 48 \right] I_2(s)$$

$$= \frac{128^2 + 108 + 2 - 48^2}{8} \cdot I_2(s)$$

$$\Rightarrow I_2(s) = \frac{36}{88^2 + 108 + 2} = \frac{18}{48^2 + 58 + 1}$$

$$= \frac{18}{(48+1)(8+1)}$$

$$= 6 \cdot \frac{4(8+1) - (48+1)}{(48+1)(8+1)}$$

$$= 6 \left(\frac{4}{8+1} - \frac{1}{8+1} \right)$$

$$= \cancel{6} \frac{6}{8+\frac{1}{4}} - \frac{6}{8+1}$$

$$\Rightarrow i_2(t) = 6e^{-t/4} - 6e^{-t}$$

$$= 6(e^{-t/4} - e^{-t})$$

$$\textcircled{25} \Rightarrow I_1(s) = \frac{1}{48} (68+2) \left[\frac{18}{(48+1)(8+1)} \right]$$

$$= \left(\frac{38+1}{8} \right) \left(\frac{9}{(48+1)(8+1)} \right)$$

$$= \left(3 + \frac{1}{8} \right) \left(\frac{9}{(48+1)(8+1)} \right)$$

$$= \frac{27}{(48+1)(8+1)} + \frac{9}{8(48+1)(8+1)}$$

$$= \frac{27/4}{3/4} \left[\frac{1}{(8+\frac{1}{4})} - \frac{1}{(8+1)} \right] + 9 \left[\frac{1}{8} + \left(\frac{-16}{3} \right) \frac{\frac{1}{4}}{(8+\frac{1}{4})} + \frac{1}{8+1} \right]$$




$$\Rightarrow i(t) = 9 \left[e^{-t/4} - e^{-t} \right] + 9 \left[1 - \frac{4}{3} e^{-t/4} + \frac{1}{3} e^{-t} \right]$$

$$= 9 - 3e^{-t/4} - 6e^{-t}$$

Unit Step

Unit step function,

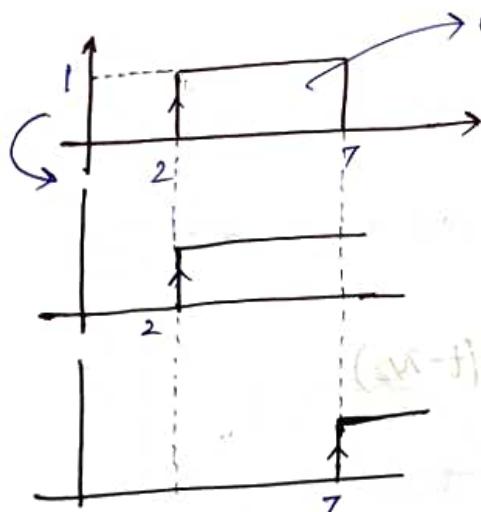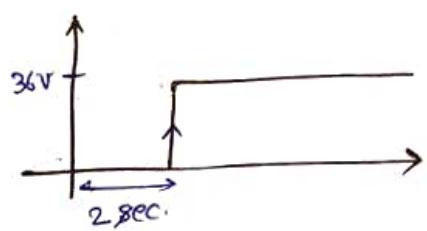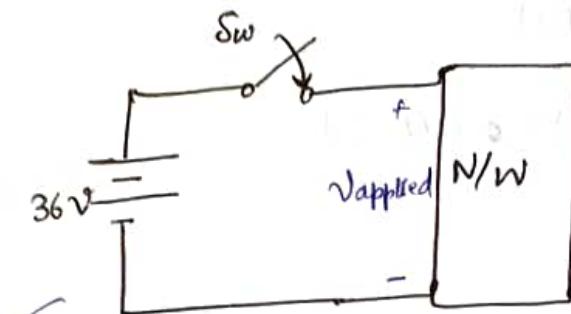
$$u(t) = \begin{cases} 1, & \text{for } t \geq 0 \\ 0, & \text{otherwise.} \end{cases}$$



$$v_{app} = 36u(t)V$$

$$u(t-2) = \begin{cases} 1, & \text{for } t \geq 2 \\ 0, & \text{otherwise.} \end{cases}$$

$$36u(t-2)V$$

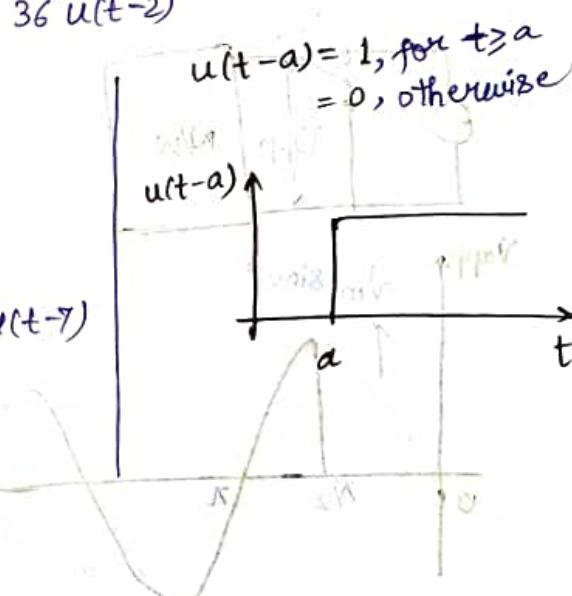

$$u(t-2) - u(t-7)$$

$$(x-t)u(x-t) \sin \omega t = (t)u(t)\sin \omega t$$


$$(R+L)u(x-t) \sin \omega t$$

$$(a-t)u(a-t) \int_0^t = 10 \cos \omega t$$






Unit Ramp
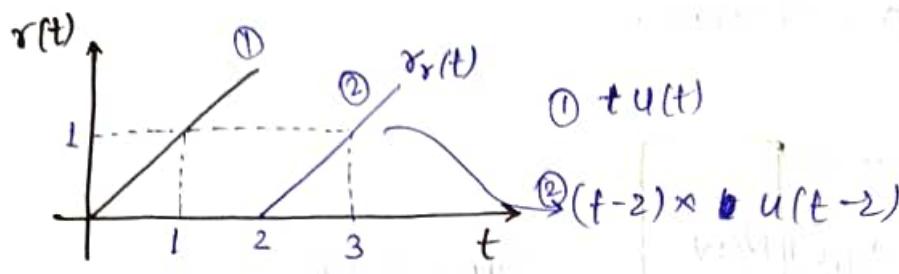
$$r(t) = t, \text{ for } t \geq 0 \\ = 0, \text{ otherwise}$$




04-10-2023

Delayed ramp:

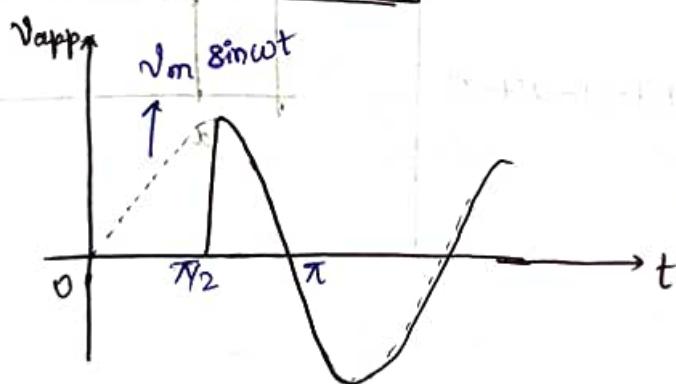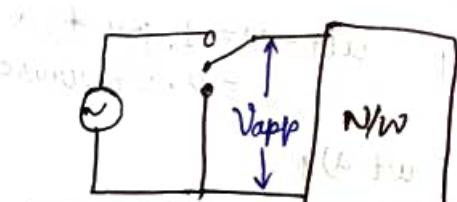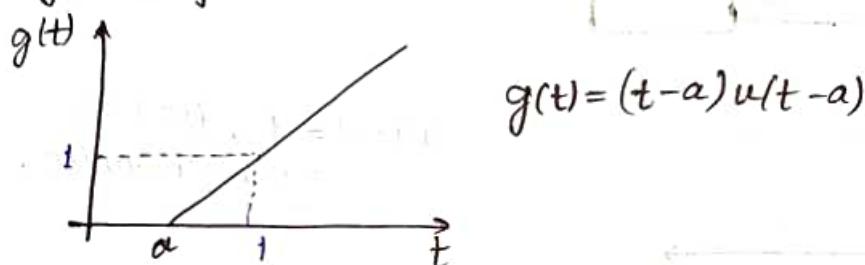
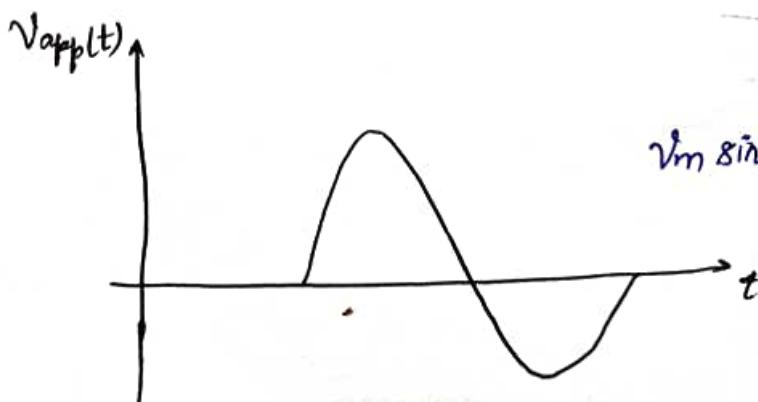
$$V_{app}(t) = V_m \sin \omega t u(t - \pi/2)$$



$$V_m \sin(\omega(t-\pi)) u(t-\pi)$$

General: $f(t-a)u(t-a)$

$$\mathcal{L}\{u(t)\} = \int_0^\infty 1 e^{-st} dt = \frac{1}{s}$$

$$\mathcal{L}\{u(t-a)\} = \int_a^\infty 1 \cdot e^{-st} dt = \frac{e^{-as}}{s}$$

$$\mathcal{L}\{f(t)\} = F(s)$$

$$\underbrace{\mathcal{L}\{u(t-a)f(t-a)\}}_{F_{sh}(s)} = \int_a^\infty f(t-a) e^{-st} dt$$

$$\text{Let } \theta = t-a \Rightarrow d\theta = dt$$

$$\text{when } t \rightarrow \infty, \theta \rightarrow \infty \\ t \rightarrow a, \theta \rightarrow 0.$$

$$F_{sh}(s) = \int_0^\infty f(\theta) e^{-s(\theta+a)} d\theta = e^{-as} F(s).$$


... s-shifting Theorem
(second-shifting theorem)

$$\therefore \mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$\mathcal{L}\{u(t-a)\} = e^{-as}/s$$


$$\mathcal{L}\{u(t-a)f(t-a)\} = e^{-as} F(s) \quad \text{where } \mathcal{L}\{f(t)\} = F(s).$$

Eg.

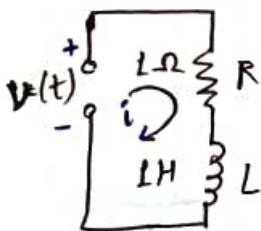

Initially relaxed NW.

Find $i(t)$ for $t \geq 0$.

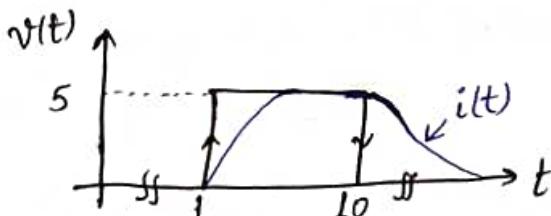

Soln: For $t \geq 0$,

$$\begin{aligned} V(t) &= Ri(t) + Li'(t) \\ &= i(t) + i'(t) \quad \dots \textcircled{1} \end{aligned}$$

$$V(t) = 5 \{u(t-1) - u(t-10)\} \quad \dots \textcircled{2}$$

Using \textcircled{1} & \textcircled{2},

$$5 \{u(t-1) - u(t-10)\} = i(t) + i'(t) \quad \dots \textcircled{3}$$

Taking LT for both sides of ③,

$$5 \left\{ \frac{e^{-8}}{s} - \frac{e^{-10s}}{s} \right\} = I(s) + 8I(s)$$

$$\Rightarrow I(s) = \frac{1}{s+8} \cdot 5 \left\{ \frac{e^{-8}}{s} - \frac{e^{-10s}}{s} \right\}$$

$$= 5 \left\{ e^{-8} \frac{1}{s} \frac{1}{s+8} - \frac{1}{s} \frac{1}{s+8} e^{-10s} \right\}$$

$$= 5 \left[\left(\frac{1}{s} - \frac{1}{s+8} \right) e^{-8} - \left(\frac{1}{s} - \frac{1}{s+8} \right) e^{-10s} \right]$$

$$\Rightarrow i(t) = 5 \left[L^{-1} \left\{ \frac{1}{s} e^{-8} \right\} - L^{-1} \left\{ \frac{1}{s+8} e^{-8} \right\} - L^{-1} \left\{ \frac{1}{s} e^{-10s} \right\} + L^{-1} \left\{ \frac{1}{s+8} e^{-10s} \right\} \right]$$

$$L^{-1} \left\{ \frac{1}{s} e^{-8} \right\} = u(t-8)$$


$$L^{-1} \left\{ \frac{1}{s+8} e^{-8} \right\} = u(t-8) e^{-t} \quad H(t) = e^{-t}$$

$$L^{-1} \left\{ \frac{1}{s} e^{-10s} \right\} = u(t-10)$$

$$L^{-1} \left\{ \frac{1}{s+10} e^{-10s} \right\} = e^{-t} u(t-10)$$

$$\therefore i(t) = 5 \left[u(t-8)(1-e^{-t}) - u(t-10)(1-e^{-t}) \right]$$



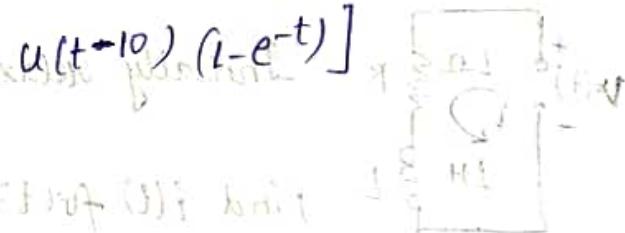
$$\begin{cases} e^{-(t-1)} \\ t=1, t=2 \\ \text{rule by} \\ G3 \end{cases}$$





$$\textcircled{2} \quad (B)i + (H)i =$$

$$\textcircled{2} \quad \{(a RD + (1-a)R) i\}^2 = 10V^2$$
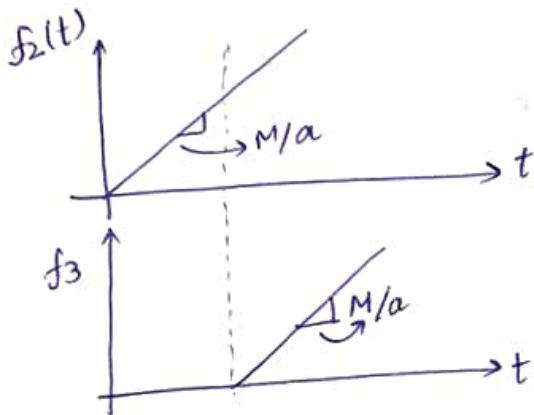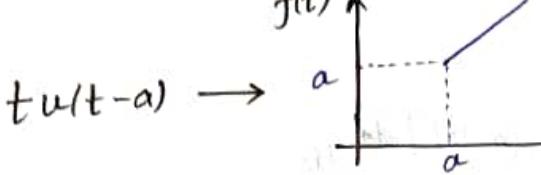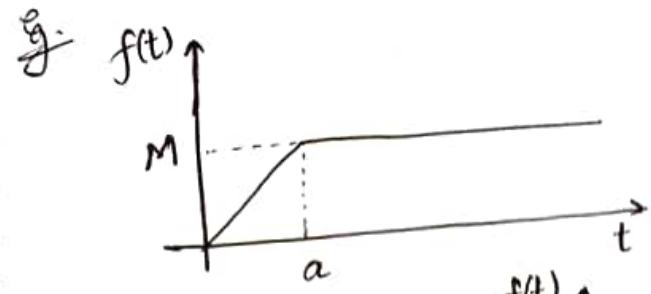
$$(B)i + (H)i = \{(a RD + (1-a)R) i\}^2$$


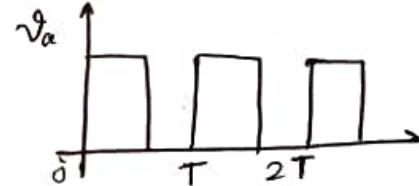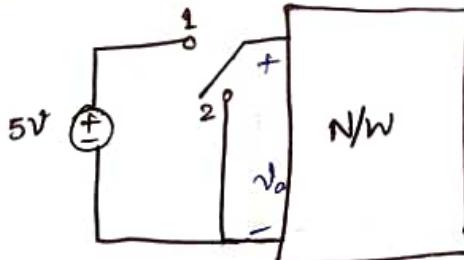
$$\begin{aligned}f(t) &= f_2(t) - f_3(t) \\&= \frac{M}{a} t + u(t) - \frac{M}{a}(t-a) u(t-a)\end{aligned}$$



if $f(t)$ is periodic with period T ,
then $f(t) = f(t+T)$.

LT of a periodic function $f(t)$

$$\mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} f(t) e^{-st} dt.$$

$$\begin{aligned}&= \int_{-\infty}^{0} f(t) e^{-st} dt + \int_{0}^{T} f(t) e^{-st} dt + \dots + \int_{(n-1)T}^{nT} f(t) e^{-st} dt \\&+ \dots = \sum_{n=1}^{\infty} I_n\end{aligned}$$

$$I_n = \int_{(n-1)T}^{nT} f(t) e^{-st} dt.$$

Let $\theta = t - (n-1)T$,

then $d\theta = dt$
and as $t \rightarrow (n-1)T$

$$\theta \rightarrow 0$$

and when $t = nT$, $\theta = T$.

$$\begin{aligned} \text{Then, } I_n &= \int_0^T f[\theta + (n-1)T] e^{-s[\theta + (n-1)T]} d\theta \\ &= \underbrace{\int_0^T f(\theta) e^{-s\theta} d\theta}_{\text{we consider } I_1} e^{-(n-1)T s} \\ &= e^{-(n-1)T s} I_1 \end{aligned}$$

$$\mathcal{L}\{f(t)\}$$

$$= I_1 + e^{-sT} I_1 + e^{-2sT} I_2 + \dots$$

$$\Rightarrow \boxed{\mathcal{L}\{f(t)\} = \frac{I_1}{1 - e^{-sT}}}$$



• Inverse of the shifting of (1) if
 $(f(t+T)) = (f(t))$ and


• Inverse of the shifting of $\mathcal{L}\{f(t)\}$

$$\mathcal{L}^{-1}\{e^{-sT} F(s)\} = f(t-T)$$

$$\begin{aligned} &\left[e^{-sT} f(s) \right] + \left[e^{-2sT} f(s) \right] + \left[e^{-3sT} f(s) \right] + \dots \\ &\quad \downarrow \text{shifting} \quad \downarrow \text{shifting} \quad \downarrow \text{shifting} \\ &\left[f(s) \right] + \left[f(s) \right] + \left[f(s) \right] + \dots \end{aligned}$$

Agenda:


- ① Impulse function and its LT
- ② Reln b/w unit step, unit impulse and unit ramp.
- ③ Final and Initial value Theorems.

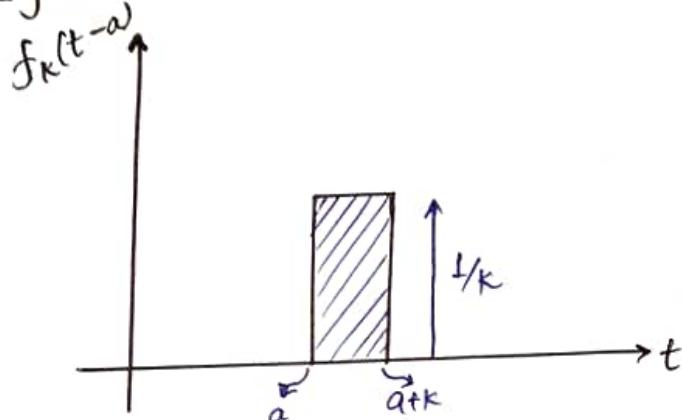Impulse function.

Let $f_k(t-a) = \frac{1}{k}$, for $a \leq t \leq a+k$ [$k \rightarrow a$ small +ve number]
 $= 0$, otherwise.

$$\int_{-\infty}^{\infty} f_k(t-a) dt = 1$$

As we reduce k ,

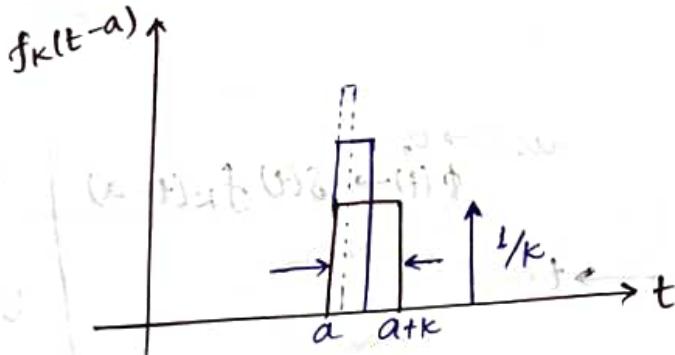

As $k \rightarrow 0$,

$$\lim_{k \rightarrow 0} f_k(t-a) \rightarrow \infty \text{ for } t=0$$

$\hookrightarrow = 0, \text{ otherwise}$
 $\triangleq \delta(t-a)$

Unit Impulse:

$$\triangleq \delta \rightarrow \infty, t=0 \\ = 0, \text{ otherwise.}$$

$$\int_0^\infty \delta(t) dt = 1$$


- If $g(t)$ is continuous,

$$\int_{0^-}^{\infty} g(t) \delta(t) dt = g(0).$$

LT of $\delta(t)$:

$$\mathcal{L}\{\delta(t)\} = \int_{0^-}^{\infty} e^{-st} \delta(t) dt \\ = \lim_{t \rightarrow 0^+} g(t) e^{-st} \\ = e^{-sa} \\ = 1.$$

$$\mathcal{L}\{\delta(t-a)\} = e^{-as}$$

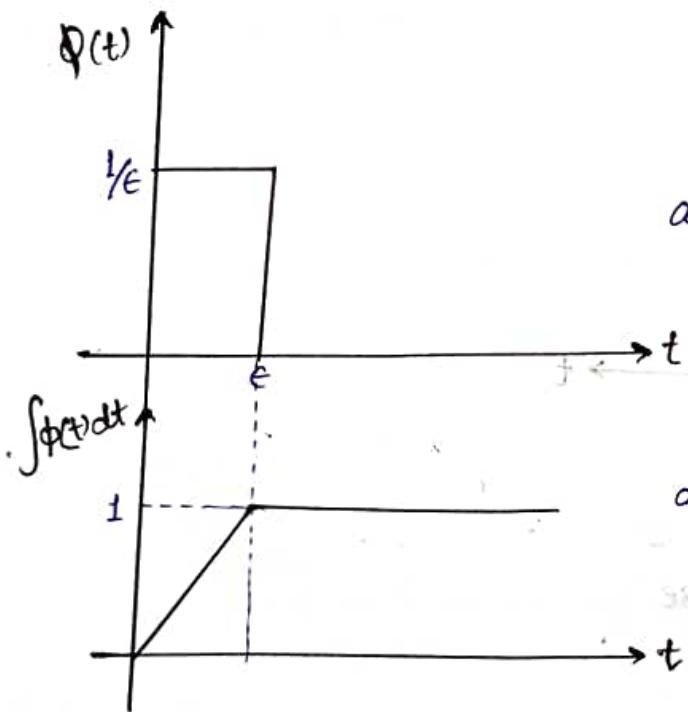

as $\epsilon \rightarrow 0$,
 $\phi(t) \rightarrow \delta(t) f_K(t-a)$

as $\epsilon \rightarrow 0$,
 $\int \phi(t) dt \rightarrow u(t)$

Unit Impulse fn
 \uparrow Diff.
 Unit Step fn
 \downarrow Integrate
 Unit Ramp fn

Initial and Final value Theorem

↳ Getting $f(0)$ and $\lim_{t \rightarrow \infty} f(t)$ directly from $F(s)$.

Initial value Theorem:

$$f(0) = \lim_{s \rightarrow \infty} s F(s)$$

$$\lim_{s \rightarrow \infty} \int_0^\infty e^{-st} f'(t) dt = \lim_{s \rightarrow \infty} s F(s) - f(0) \quad \left[L\left\{ \frac{df}{dt} \right\} = s F(s) - f(0) \right]$$

$$\Rightarrow \int_0^\infty \lim_{s \rightarrow \infty} e^{-st} f'(t) dt = \lim_{s \rightarrow \infty} s F(s) - f(0)$$

$$\Rightarrow 0 = \lim_{s \rightarrow \infty} s F(s) - f(0)$$

$$\Rightarrow \lim_{s \rightarrow \infty} s F(s) = f(0)$$

Final value Theorem:

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

$$L\{f'(s)\} = s F(s) - f(0)$$


$$\lim_{s \rightarrow 0} s F(s) = \lim_{s \rightarrow 0} (L\{f'(s)\} + f(0))$$

$$= \int_0^\infty f'(t) \lim_{s \rightarrow 0} e^{-st} dt + f(0)$$

$$= \int_0^\infty f'(t) dt + f(0)$$

$$= f(\infty) - f(0) + f(0)$$

$$= \lim_{t \rightarrow \infty} f(t)$$

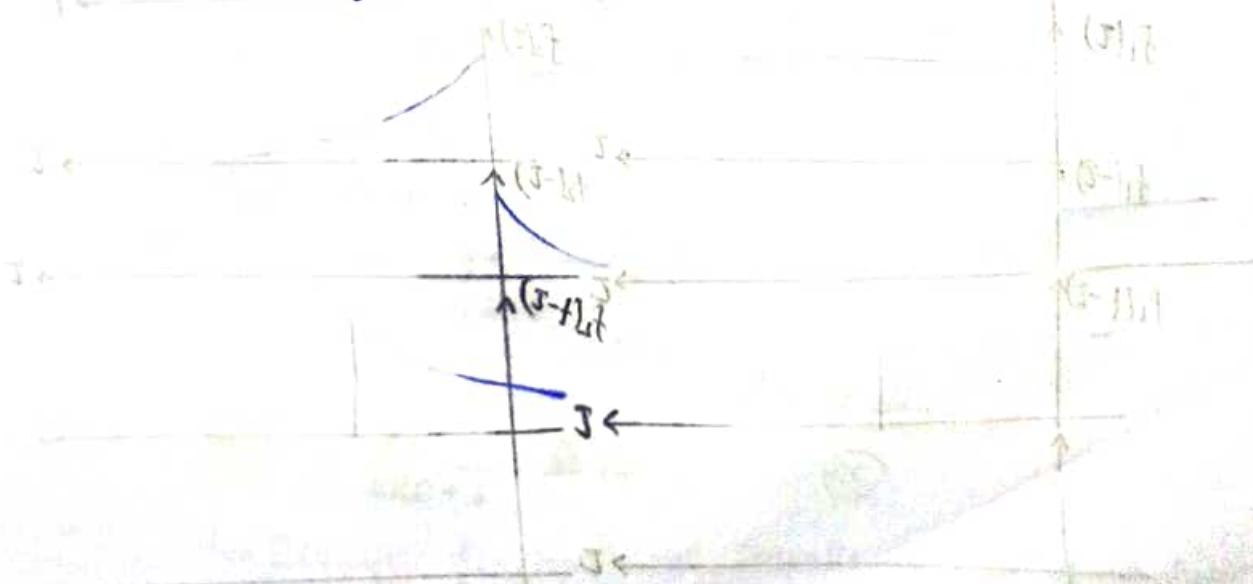

→ If $\mathcal{L}\{f(t)\}$, $\mathcal{L}\{f_1(t)\}$ and $\mathcal{L}\{f_2(t)\}$ are $F(s)$, $F_1(s)$ and $F_2(s)$, respectively, and

$$F(s) = F_1(s)F_2(s) \quad \dots \text{eq1}$$

$$\Rightarrow \mathcal{L}^{-1}\{F\} \neq \mathcal{L}^{-1}\{F_1\} \mathcal{L}^{-1}\{F_2\}$$

$$f(t) \neq f_1(t)f_2(t)$$

not necessarily

Then,

$$\begin{aligned} f(t) &= \int_0^t f_1(\tau) f_2(t-\tau) d\tau \rightarrow \text{convolution Integral} \\ &= \int_0^t f_1(t-\tau) f_2(\tau) d\tau \\ &= [f_1(t) * f_2(t)] \leftarrow \text{convolution} \end{aligned} \quad \dots \text{eq2 (CI)}$$

Convolution Integral

CI: Involves 4 steps.

① Reverse/fold one of the signals.


② Shift the folded signal.

③ Multiply 2 signals


④ Integration.

Eg. $f_1(t) = u(t) \rightarrow F_1(s) = \frac{1}{s}$.

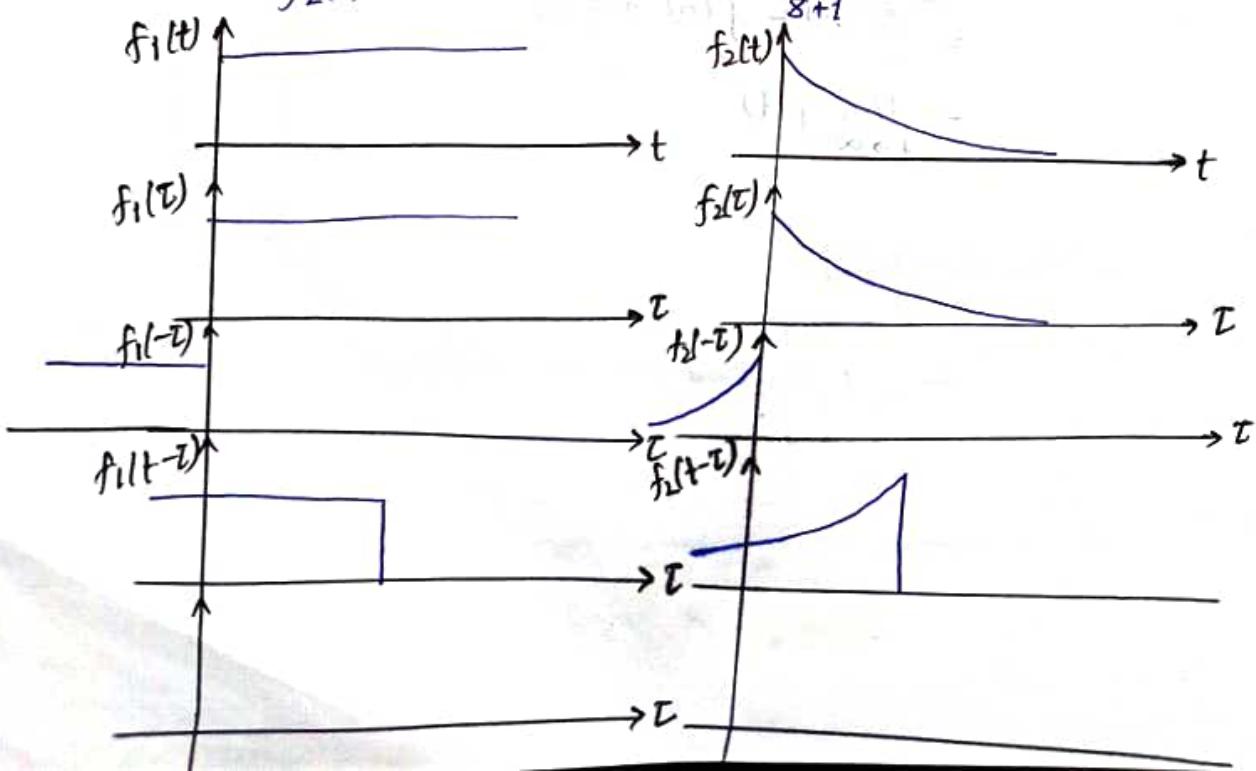
$$f_2(t) = e^{-t} u(t) \rightarrow F_2(s) = \frac{1}{s+1}.$$



$$f_1(t) * f_2(t)$$

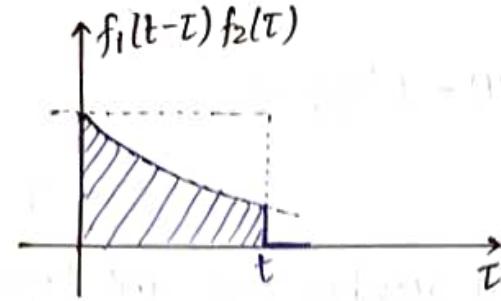


$$\begin{aligned} \int_0^t f_1(t-\tau) f_2(\tau) d\tau \\ = \int_0^t e^{-\tau} d\tau \\ = -e^{-\tau} \Big|_0^t \\ = \boxed{1 - e^{-t}} \end{aligned}$$

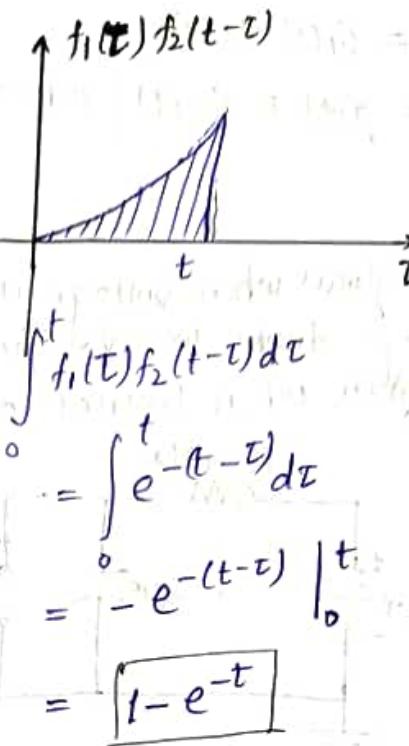

$$\begin{aligned} \int_0^t f_1(t) f_2(t-\tau) d\tau \\ = \int_0^t e^{-(t-\tau)} d\tau \\ = -e^{-(t-\tau)} \Big|_0^t \\ = \boxed{1 - e^{-t}} \end{aligned}$$

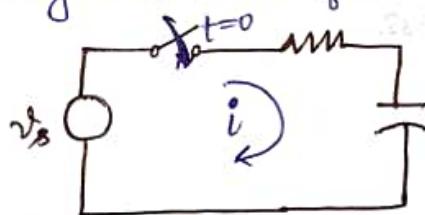→ CI allows us to compute the response of a N/W to any arbitrary excitation if the impulse response is known.



Initially relaxed system.

$$v_s(t) = Ri(t) + \frac{1}{C} \int i(t) dt$$

$$\text{LS} \Rightarrow v_s(s) = RI(s) + \frac{1}{sC} I(s)$$

$$v_s(s) = \frac{sCR + 1}{sC} \cdot I(s) + \text{Initial value}$$

$$\Rightarrow I(s) = \frac{sC}{sCR + 1} \cdot v_s(s) \quad \dots \textcircled{a}$$

$$\text{If } v_s(t) = \delta(t)$$

$$\text{then, } v_s(s) = 1$$

$$\text{Then, } I(s) = \frac{8C}{8CR + 1} \rightarrow G(s) \quad \dots \textcircled{b}$$

↓
Impulse response
of the system

$$\textcircled{a} \Rightarrow \frac{I(s)}{v_s(s)} = \frac{8C}{8CR + 1} \triangleq G(s) \quad \dots \textcircled{c}$$

Transfer function → Impulse response of the system


Using (a) & (c),

$$I(s) = G(s) V_s(s)$$
$$\Rightarrow i(t) = g(t) * v_s(t) \text{ where } g(t) = L^{-1}\{G(s)\}.$$

13-10-2023


- Q1 The lamp glows when voltage across it reaches 75V and turns off when the voltage drops to 30V. The lamp resistance is 120Ω when glowing and infinite when turned off. Initial transients while connecting the

Quiz-1
Q3

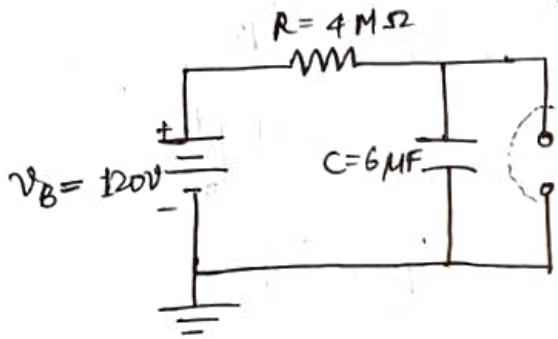

battery can be neglected. Find the time duration for which the lamp glows.

Soln: For $30V < V \leq 75V$,

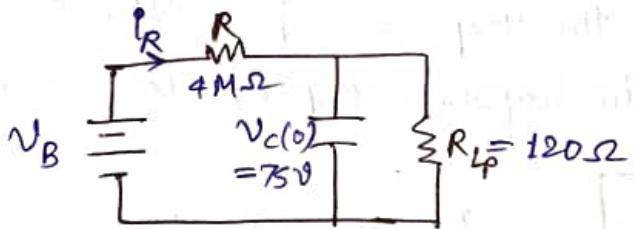

$$\begin{cases} V_B = R_i R + V_c \\ i_R = C V_c' + V_c / R_{lp} \end{cases}$$
$$\Rightarrow V_B = R C V_c' + \frac{R}{R_{lp}} V_c + V_c$$
$$= R C V_c' + \left(\frac{R}{R_{lp}} + 1 \right) V_c$$

$$\Rightarrow \frac{V_B}{RC} = V_c' + \frac{1}{C} \frac{R + R_{lp}}{R R_{lp}} V_c$$

$$= V_c' + \frac{1}{T_p} V_c, \quad T_p = C (R_{lp} \parallel R)$$

$$\Rightarrow V_c = \underbrace{\frac{V_B (R_{lp} \parallel R)}{R}}_{\ll 1} + k_0 e^{-t/T_p}$$

At $t=0$, $V_c(0) = 75V$, $75 \approx k_0$.

$$\therefore V_c = \frac{V_B (R_{lp} \parallel R)}{R} + 75 e^{-t/T_p}$$


Say, time taken for glowing is t_g ,

$$V_C(t_g) = 30V = V_B \frac{(R_{LP} \parallel R)}{R} + 75 e^{-t_g/\tau}$$

Transform Impedance


LT: 't' domain to 's' domain.

Resistance:

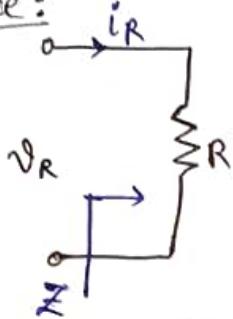


$$\begin{aligned} V_R(t) &= R i_R(t) \\ \Rightarrow V_R(s) &= R I_R(s) \\ \Rightarrow \frac{V_R(s)}{I_R(s)} &= R \end{aligned}$$

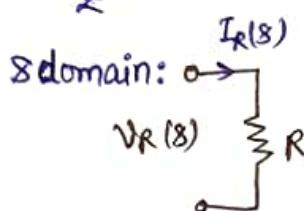(Terminal voltage and current must be retained)



Inductance:

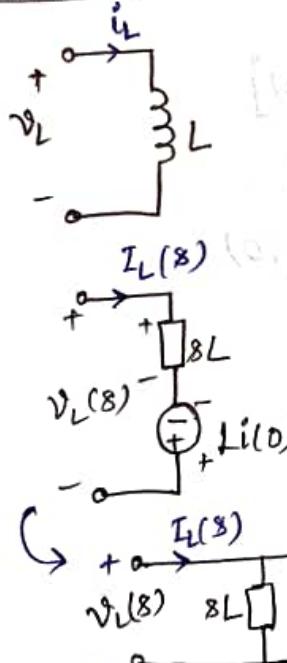


$$V_L(t) = L \frac{di}{dt} \quad \xrightarrow{\text{LT}} \text{Assumption: Magnetic field is linear. (even while designing)}$$


$$\begin{aligned} V_L(s) &= L \{ s I(s) - i(0) \} \\ &= s L I(s) - L i(0) \end{aligned}$$

$$\Rightarrow I_L(s) = \frac{V_L(s)}{sL} + \frac{i(0)}{s}$$

Capacitance:

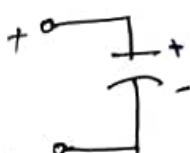

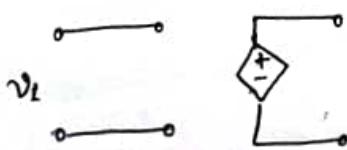
$$\begin{aligned} V_C(t) &= \alpha V_1(t) \\ \downarrow V_C(s) &= \alpha V_1(s) \end{aligned}$$



Valkenburg Prob. 7-42

Q1

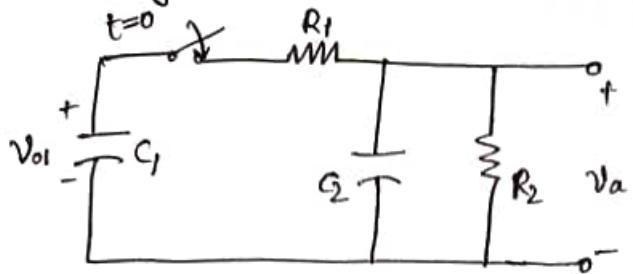


Find $v_a(t)$ for $t \geq 0$.

$$V_{01} = 10V$$


$$R_1 = 1\Omega, R_2 = 0.8\Omega$$

$$C_1 = \frac{1}{3}F, C_2 = \frac{3}{4}F.$$

Sgn:

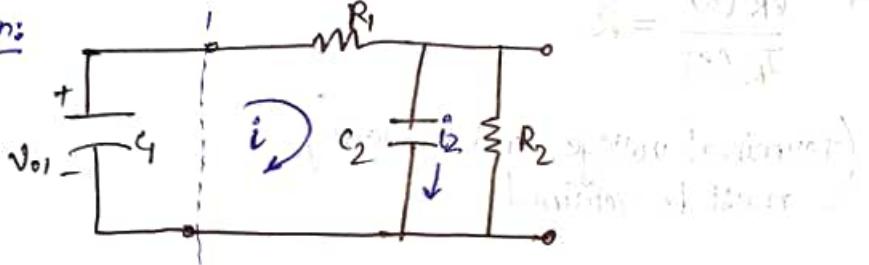
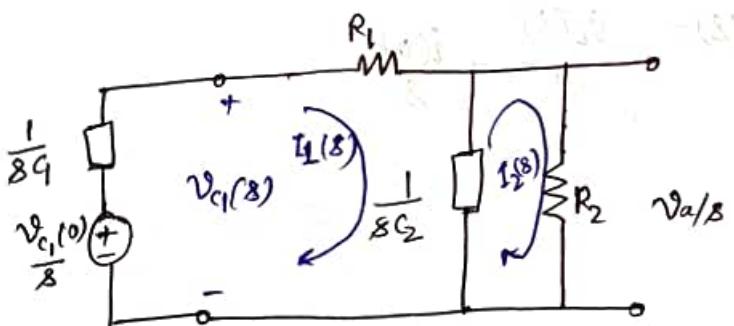
$$\begin{aligned} i_1 &= -C_1 \frac{dV_{C1}}{dt} \\ \Rightarrow I_1(8) &= -C_1 [8V_{C1}(8) - V_{C1}(0)] \\ \Rightarrow I_1(8) &= -8C_1 V_{C1}(8) + C_1 V_{C1}(0) \\ \Rightarrow V_{C1}(8) &= -\frac{1}{8C_1} I_1(8) + \frac{1}{8} V_{C1}(0) \end{aligned}$$




$$I_1: \frac{V_{C1}(0)}{8} = \frac{I_1}{8C_1} + R_1 i_1 + \frac{1}{8C_2} (I_1 - I_2) \quad \dots \textcircled{1}$$

$$I_2: \frac{1}{8C_2} (I_2 - I_1) + I_2 R_2 = 0 \quad \dots \textcircled{2}$$

$$\textcircled{1} + \textcircled{2} \Rightarrow \frac{I_1}{8C_1} + R_1 i_1 + I_2 R_2 + -\frac{V_{C1}(0)}{8} = 0.$$
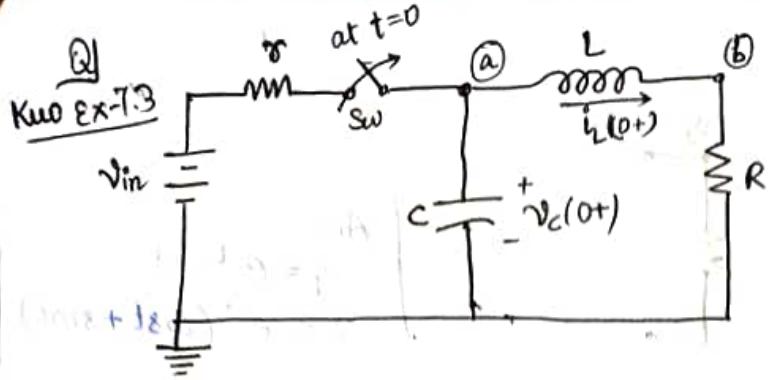
$$\Rightarrow I_2 = \frac{1}{R_2} \left[\frac{V_{C1}(0)}{8} - R_1 i_1 - \frac{I_1}{8C_1} \right]$$



Initially SS was heated with S_w closed.

Ans:


$$v_1 = e^{-t} \cos t$$

$$v_2 = e^{-t}(\cos t + 8\sin t)$$

$$V_{IN} = 1V, L = 0.5H, C = 1F, R = 1\Omega, \gamma = 0.01\Omega$$


Find $v_a(t)$ and $v_b(t)$ for $t \geq 0$.

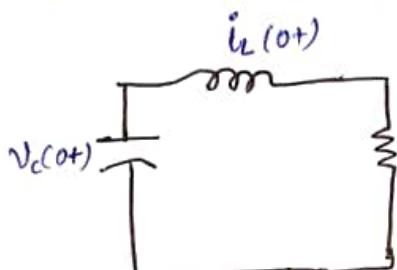Soln: For $t \geq 0$, the relevant circuit is



$$v_c(0+) \approx 1V$$
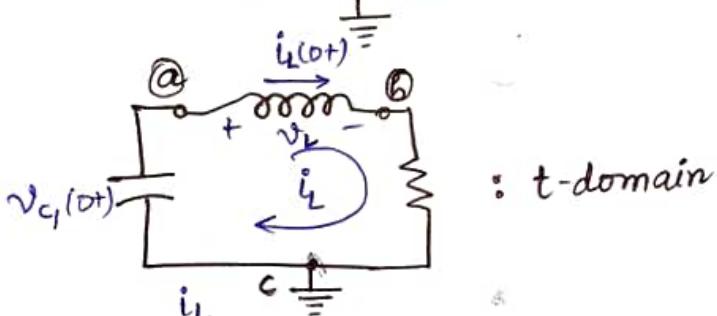
$$i_L(0+) \approx \frac{1}{L} = 1A \quad \left(\frac{V_{IN}}{\gamma + R} = \frac{1}{0.01 + 1} \approx 1 \right)$$




: s-domain

$$C_1 \frac{dV_Q}{dt} = -i_L$$

$$\int_C [8V_Q(s) - v_{c1}(0)] = -I_L(s)$$

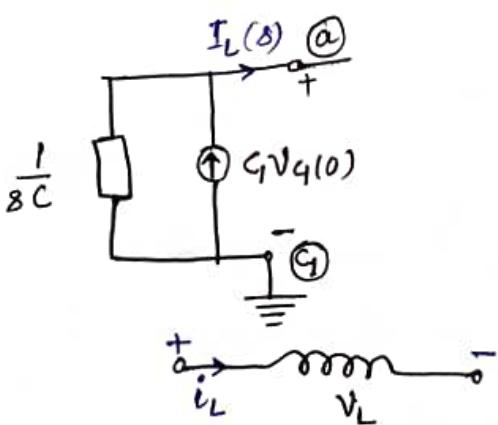
$$\Rightarrow I_L(s) = -8Cv_Q(s) + C_1v_{c1}(0)$$



Taking LT of $v_L = L \frac{di}{dt}$

$$V_L(s) = L \{ 8I_L(s) - i_L(0) \}$$
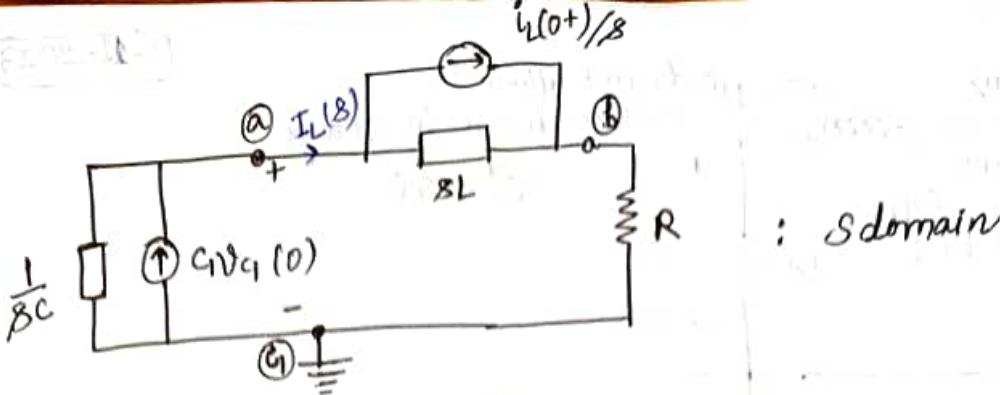
$$\Rightarrow I_L(s) = \frac{1}{8L} V_L(s) + \frac{i_L(0+)}{8}$$



Applying KCL at node @,

$$I_L(s) = -sCv_a(s) + C_1v_{C_1}(0+) = \frac{1}{sL} \{ v_a(s) - v_b(s) \} + i_L(0+)/s = \frac{v_b(s)}{R}$$

$$\text{Simplifying: } I_L(s) = -sV_a(s) + 1 = \frac{1}{s} \{ v_a(s) - v_b(s) \} + \frac{1}{s} \\ = v_b(s)$$

$$\Rightarrow v_b(s) + sV_a(s) = 1$$

$$- \frac{2}{s} \{ v_a(s) - v_b(s) \} + \frac{1}{s} = v_b(s) = \frac{1}{s}$$

$$\begin{bmatrix} s & 1 \\ -\frac{2}{s} & \frac{2+s}{s} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} 1 \\ \frac{1}{s} \end{bmatrix}$$

$$\begin{bmatrix} s & 1 & 1 \\ -\frac{2}{s} & \frac{2+s}{s} & \frac{1}{s} \end{bmatrix} \rightarrow \begin{bmatrix} 1 & \frac{1}{s} & \frac{1}{s} \\ -2 & 2+s & 1 \end{bmatrix}$$

$$\Rightarrow -2V_a(s) + (2+s)V_b(s) = 1$$

$$\Rightarrow -2sV_a(s) + (2s+8)V_b(s) = 8$$

$$\underline{2sV_a + 2V_b = 2}$$

$$\Rightarrow (8^2 + 2s + 2)V_b = 8 + 2$$

$$\Rightarrow V_b = \frac{8+2}{8^2 + 2s + 2}$$

$$\& 8V_a = 1 - \frac{8+2}{8^2 + 2s + 2} = \frac{8^2 + 8}{8^2 + 2s + 2}$$

$$\Rightarrow V_a = \frac{8+1}{8^2 + 2s + 2} = \frac{8+1}{(8+1)^2 + 1}$$


$$\Rightarrow V_a(t) = e^{-t} \cos t.$$

$$\text{and, } V_b(s) = \frac{8+1}{(8+1)^2 + 1} + \frac{1}{(8+1)^2 + 1}$$

$$\Rightarrow V_b(t) = e^{-t} \cos t + e^{-t} \sin t = e^{-t} (\cos t + 8 \sin t).$$

LTSpice

2-1-2023

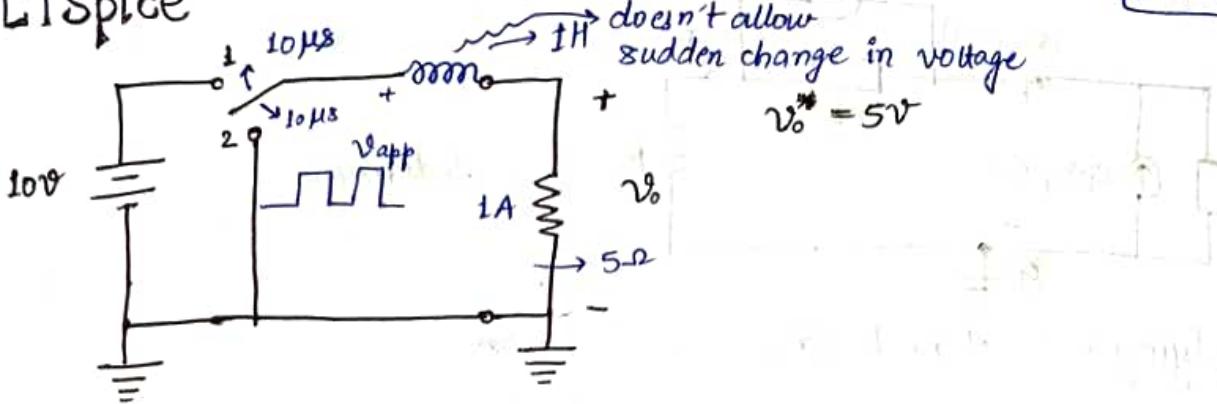

V_{app} (V_{app})



$$\langle V_{app} \rangle = \frac{1}{T} \int V_{app} dt = 5V.$$

50% duty cycle $\rightarrow 5V$

33% duty cycle $\rightarrow 3.3V$

If we don't use inductor, then around load we get pulsive current.

To avoid this, we can use inductor.

Start with L = 1H.

$$L = \frac{\Delta V}{\Delta I} = \frac{10V - 0V}{0.5A} = 20 \Omega$$

$$I = \frac{V}{R} = \frac{10V}{20 \Omega} = 0.5A$$

$$(10V + 10V) / 2 = 10V + 10V = 20V$$

Filter Design

- Specification
- Frequency component of excitation
- Network analysis + Frequency Response (FR).



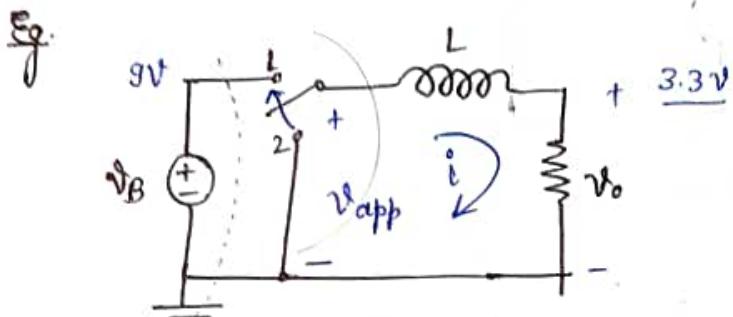



Fig. 1




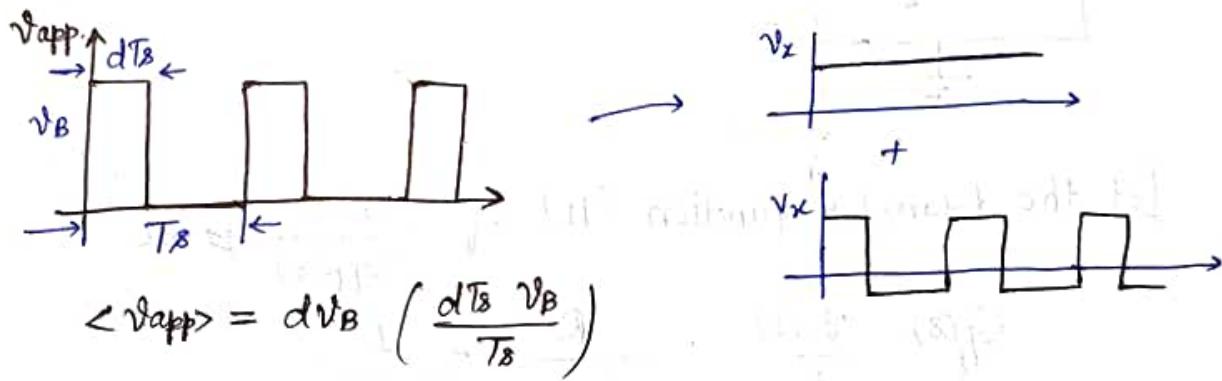


Equivalent circuit of Fig. 1:

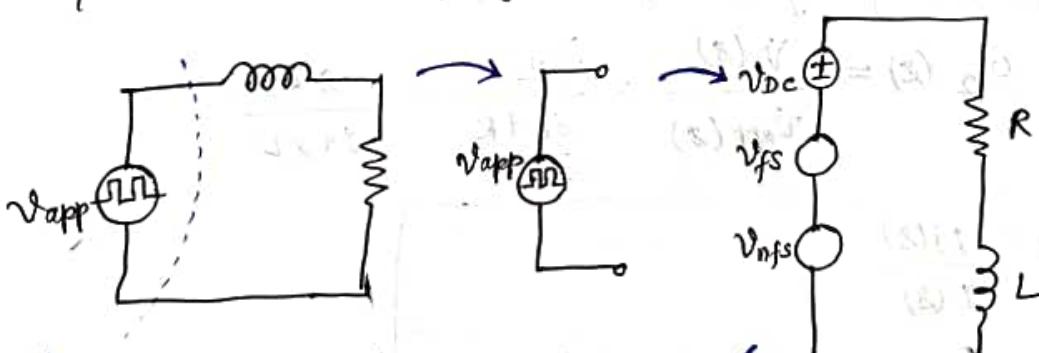

Applying superposition,

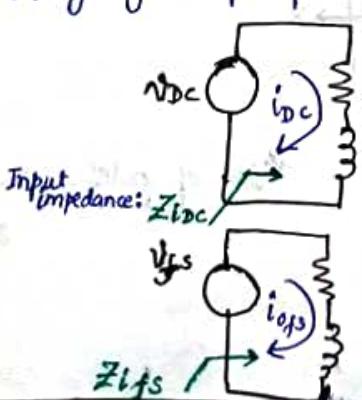

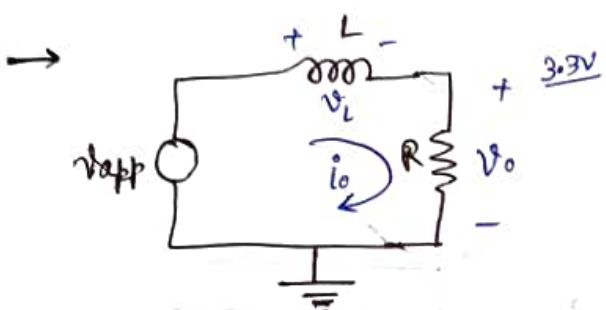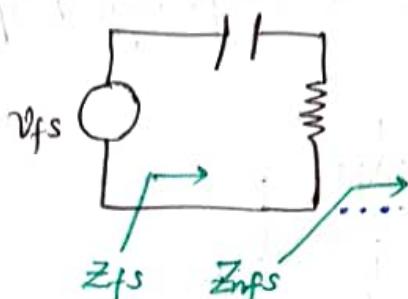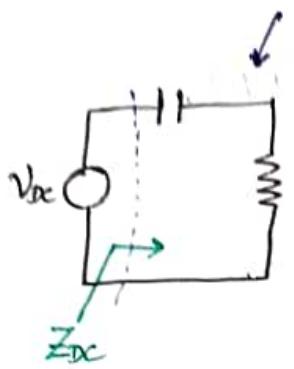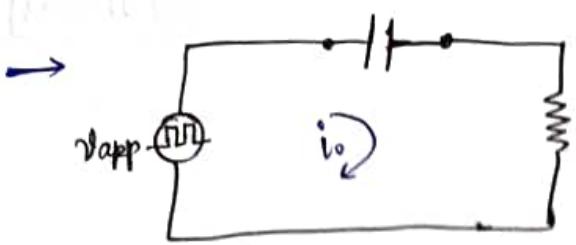

Let the transfer function (TF) of $\frac{V_o(s)}{V_{app}(s)}$ be

$$G_1(s) = \frac{V_o(s)}{V_{app}(s)} = \frac{R}{R+8L} = \frac{1}{1+8\tau}$$

Another transfer function,


$$G_2(s) = \frac{V_L(s)}{V_{app}(s)} = \frac{8L}{8L+R} = \frac{8\tau}{1+8\tau}$$


$$G(s) = \frac{N(s)}{D(s)}$$

$N(s)=0 \rightarrow$ roots represent zeroes $\rightarrow 0$


$D(s)=0 \rightarrow$ roots represent poles $\rightarrow x$

No. of poles = order of system

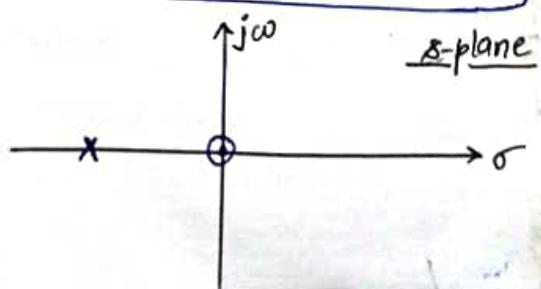

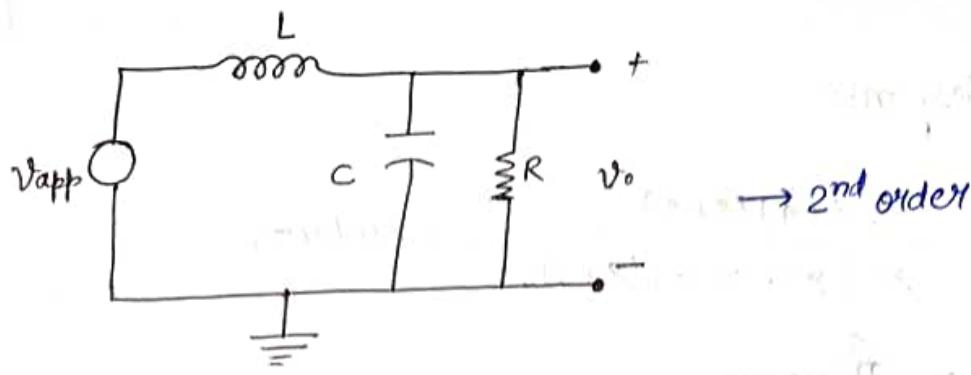
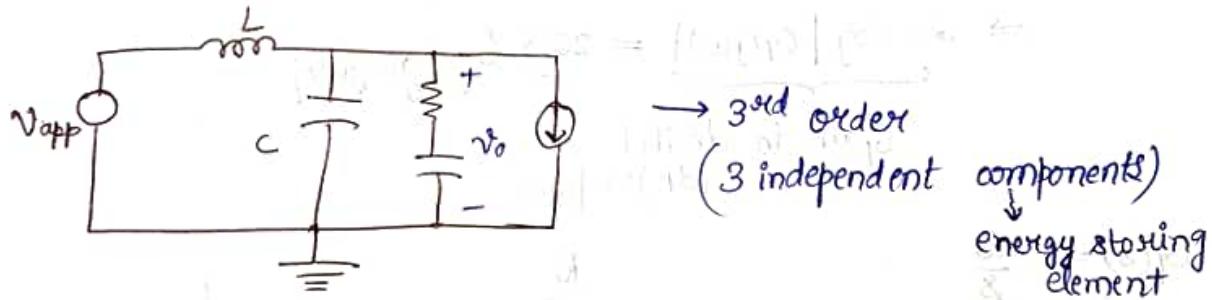
$$\begin{aligned}
 G_{13}(s) &= \frac{V_o(s)}{V_{app}(s)} = \frac{R \parallel L/sC}{sL + R \parallel 1/sC} \\
 &= \frac{R}{sRC + 1} \\
 &= \frac{R}{\frac{R}{sRC + 1} + sL} \\
 &= \frac{R}{R + s^2LCR + sL} \\
 &= \frac{1}{s^2LC + sL/R + 1}
 \end{aligned}$$



→ Any $G(s)$ can be represented as

$$\begin{aligned}
 G(s) &= K \frac{\prod (s+z_r) \prod (s^2+a_3s+b_3)}{s^m \prod (s+p_r) \prod (s^2+a_p s+b_p)} \rightarrow \boxed{\text{Pole-zero form}} \\
 &= K_T \frac{\prod (\tau_{zr}s+1) \prod (c_3s^2+b_3s+1)}{s^m \prod (\tau_{pr}s+1) \prod (c_ps^2+b_ps+1)}
 \end{aligned}$$

For filter, we only take $j\omega$ part of s . (Steady state) $\Rightarrow \underline{s=0}$.

$$G(j\omega) = K_T \frac{\prod (\tau_{zr}j\omega + 1) \prod (c_3(j\omega)^2 + b_3(j\omega) + 1)}{s^m \prod (\tau_{pr}j\omega + 1) \prod (c_p(j\omega)^2 + b_p(j\omega) + 1)}$$

$$\therefore G(s) = K G_{11}(s) G_{12}(s) \dots G_{1n}(s)$$

$$G(j\omega) = K_T G_{11}(j\omega) G_{12}(j\omega) \dots G_{1n}(j\omega)$$

Frequency Response

$$G(s) = \frac{(s+4)(s+5)}{s^2(s^2 + 2s + 2)(s+3)} \Rightarrow \text{order} = 5$$

$$= \prod_1^5 g_i(s)$$


Putting $\sigma=0$

$$G(j\omega) = \prod g_i(j\omega)$$

$$= |G(j\omega)| \angle G(j\omega)$$

$$= \underbrace{\prod |g_i(j\omega)|}_{G_1 \text{ magnitude}} \underbrace{\angle \sum g_i}_{\angle G}$$

$\downarrow |G(j\omega)|$

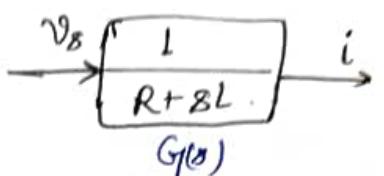

$$\text{Then, } \log |G(j\omega)| = \sum \log |g_i(j\omega)|$$

$$\Rightarrow 20 \log |G(j\omega)| = 20 \sum \log |g_i(j\omega)|$$

Gain in decibel
(dB) $\rightarrow |G|_{dB}$

$$G(s) = \frac{K}{s} \quad \frac{K}{s^2} \quad \frac{1}{s^n}$$

$$= 10 \cdot \frac{1}{s} \quad (\text{for } K=10)$$

\uparrow \uparrow

G_1 G_2

$$G_1(s) = 10 \Rightarrow |G_1|_{dB} = 20 \log 10 = 20 \text{ dB}$$

$$G_2(s) = \frac{1}{s} \Rightarrow G_2(j\omega) = \frac{1}{j\omega} = \frac{1}{\omega} \angle -90^\circ$$

$$|G_2|_{\omega=1} = 1 \Rightarrow |G_2|_{dB} = 0 \text{ dB}$$

At 'one decade above $\omega=1$ ' $\Rightarrow \omega=10$

$$|G_2|_{\omega=10} = 0.1 \Rightarrow |G_2|_{dB} = 20 \log (0.1) = -20 \text{ dB}$$





$Q/10$
 \uparrow 1 decade below
 Quantity, Q
 \downarrow 1 decade above
 $Q \times 10$

At, 'one decade below' $\omega=1$,

$$|G_2|_{\omega=0.1} = \frac{1}{0.1} = 10 \Rightarrow |G_2|_{dB} = 20 dB$$

$$|G_2|_{\omega=100} = 0.01 \Rightarrow |G_2|_{dB} = -40 dB \quad (2 \text{ decades above } \omega=1)$$

$$|G_2|_{0.01=\omega} = 100 \Rightarrow |G_2|_{dB} = 40 dB \quad (2 \text{ decades below } \omega=1)$$

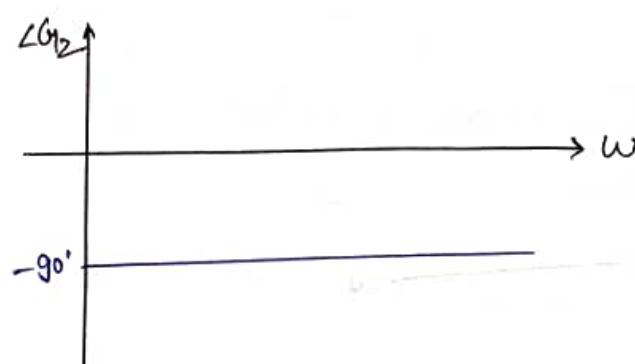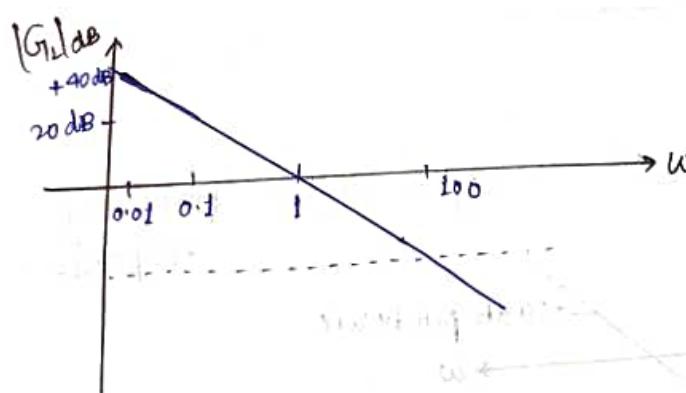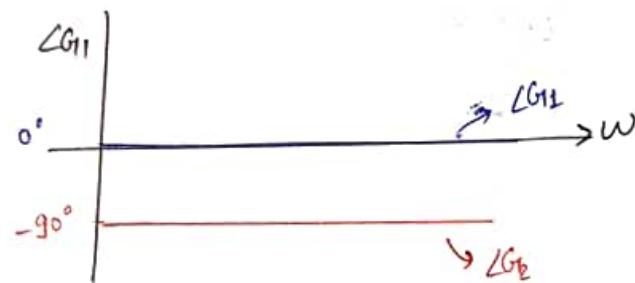
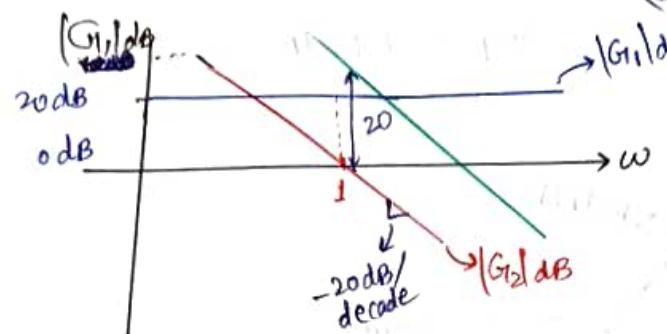


$$\rightarrow G(s) = \frac{1}{s^2} \Rightarrow G(j\omega) = -\frac{1}{\omega^2} = \frac{1}{\omega^2} \angle -180^\circ$$



$$|G_1|_{\omega=1} = 1 \Rightarrow G_{1dB} = 0 \text{ dB} \quad \left. \begin{array}{l} \\ \end{array} \right\} -40 \text{ dB per decade}$$

$$|G_1|_{\omega=10} = 0.01 \Rightarrow G_{1dB} = -40 \text{ dB}$$

$$|G_1|_{\omega=0.1} = 100 \Rightarrow G_{1dB} = +40 \text{ dB}$$

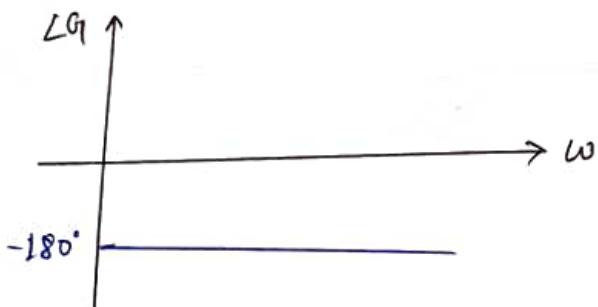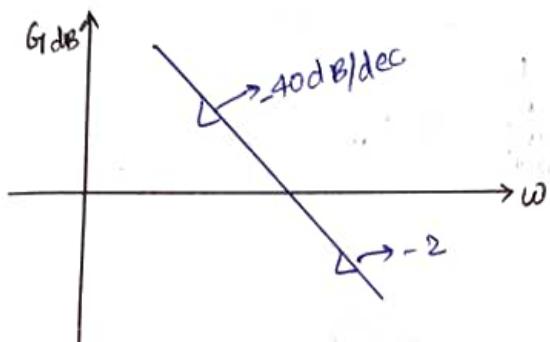
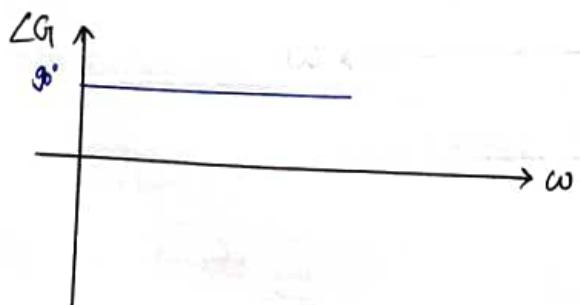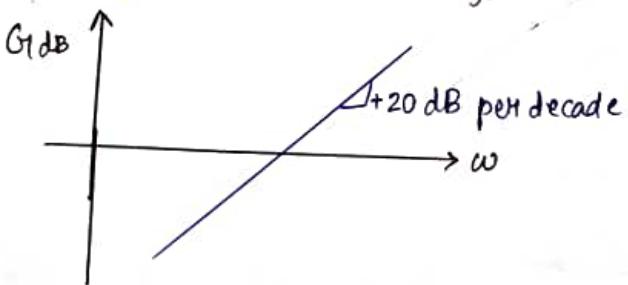
$$\rightarrow G(s) = s \Rightarrow G(j\omega) = \omega \angle 90^\circ : \text{Differentiator frequency response}$$



$$\rightarrow G(j\omega) = \frac{1}{1 + j\omega\tau}$$

$$\Rightarrow G(j\omega) = \frac{1}{1 + j\omega\tau} = \frac{1}{[1 + \omega^2\tau^2]^{1/2}} e^{-j\omega\tau} \quad \leftarrow -\tan^{-1}\omega\tau$$

At, $\omega\tau = 1$, $\omega = \frac{1}{\tau} \Rightarrow$ corner frequency (ω_c)

$$|G|_{dB} \Big|_{\omega=\frac{1}{\tau}} = 20 \log \frac{1}{(1+1)^{1/2}} \approx -3 \text{ dB}$$

$$\angle G \Big|_{\omega=\frac{1}{\tau}} = -45^\circ$$

At $\omega \ll \omega_c$, $|G| \approx 1$

$$|G|_{dB} = 0 \text{ dB}$$

$$\angle G \approx 0^\circ$$

At 1 decade below ω_c ,

$$|G|_{\omega=\frac{1}{10\tau}} = -0.995$$

$$\angle G \Big|_{\omega=\frac{1}{10\tau}} = -5.7^\circ$$

At 1 decade above ω_c ,

$$|G|_{\omega=\frac{10}{\tau}} = -20.04 \text{ dB}$$

$$\angle G \Big|_{\omega=\frac{10}{\tau}} = -84.9^\circ$$

At $\omega \gg \omega_c$, i.e., $\omega\tau \gg 1$

$$|G| \approx \frac{1}{\omega\tau} \rightarrow |G|_{\omega=\frac{10}{\tau}} = 0.1 \xrightarrow{G_{dB}} -20 \text{ dB}$$

$$\angle G \rightarrow -90^\circ$$

$$\rightarrow G(s) = \frac{1}{1+8\tau}$$

$$G_1(j\omega) = \frac{1}{1+j\omega\tau} = \frac{1}{[1+\omega^2\tau^2]^{1/2}} \angle -\tan^{-1}\omega\tau$$


$$G_L \text{dB} = 20 \log |G_1(j\omega)|$$

For $\omega \ll \omega_c$,

$$|G_1| \approx 1$$

for $\omega \gg \omega_c$,

$$|G_1| \approx \frac{1}{\omega\tau}$$

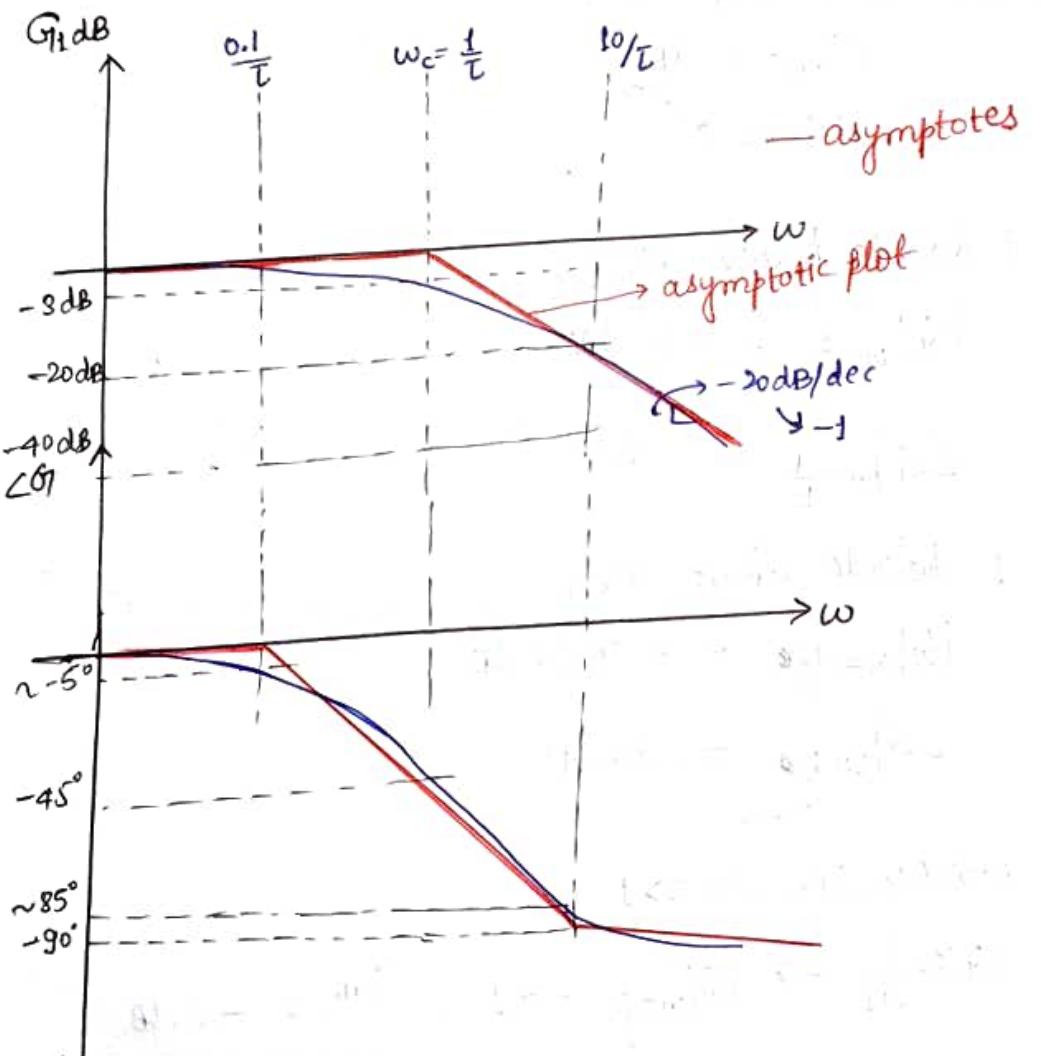

$$\rightarrow G(s) = 1 + \underbrace{Ts}_{\frac{1}{\omega_c}}$$

$$G(j\omega) = 1 + j\omega T$$


$$= [1 + \omega^2 T^2]^{1/2} \angle \tan^{-1} \omega T$$

$$\text{At } \omega = \frac{1}{T} = \omega_c, |G| \approx 1.414 \Rightarrow G_{dB} = 3 \text{ dB}$$

$\angle G = 45^\circ$


$$\text{For } \omega \ll \omega_c \Rightarrow \omega T \ll 1, G_{dB} = 0 \text{ dB} \quad (|G| \approx 1)$$




$$\text{For } \omega \gg \omega_c \Rightarrow \omega T \gg 1, |G| \approx \omega T$$

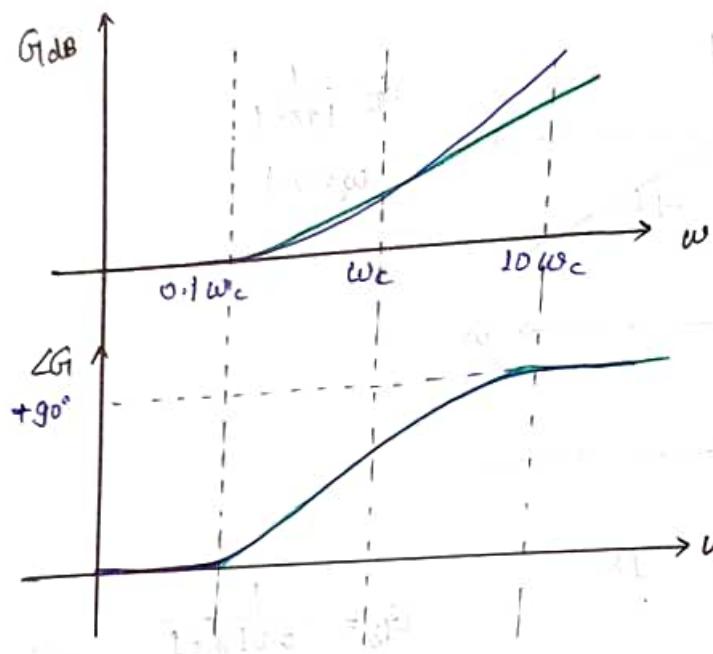


Eg. $G(s) = \frac{100}{8(10s+1)(0.01s+1)}$


Labels: g_1 , g_2 , g_3 , g_4

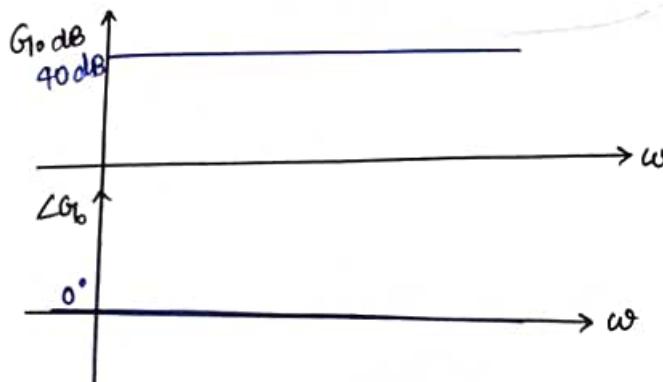

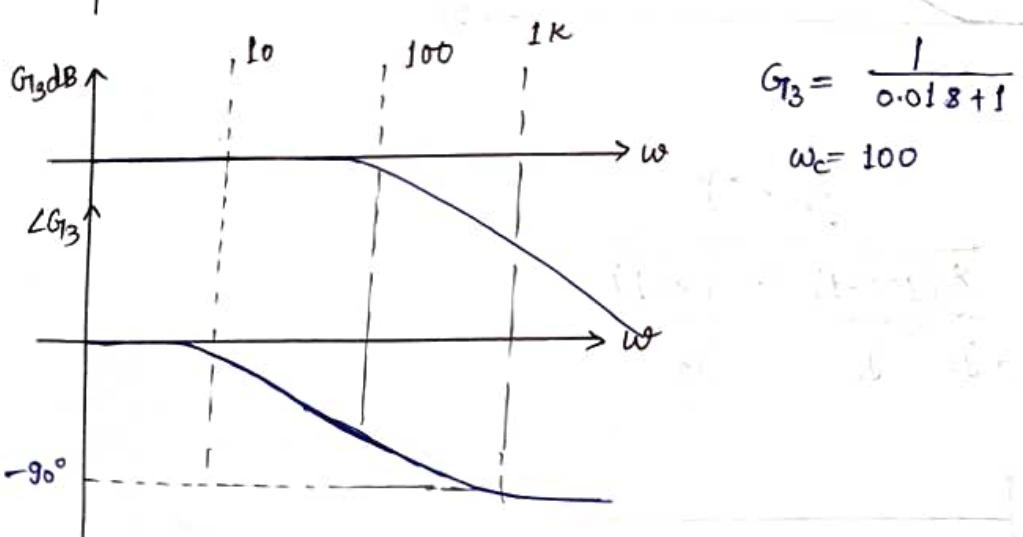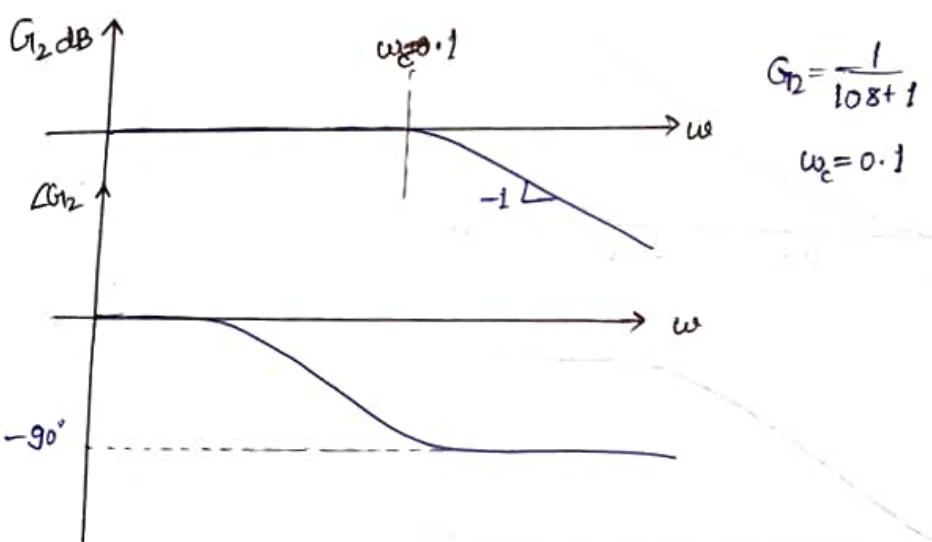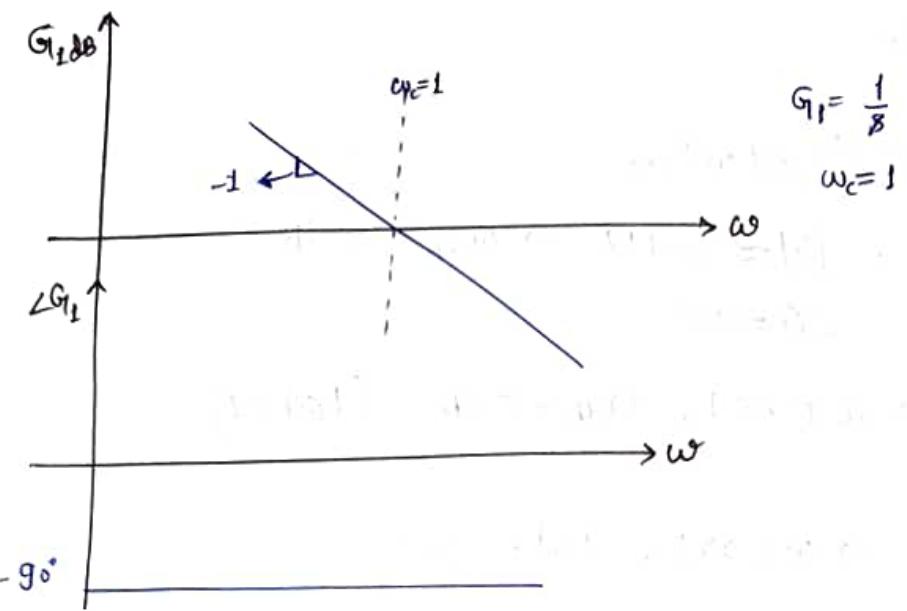

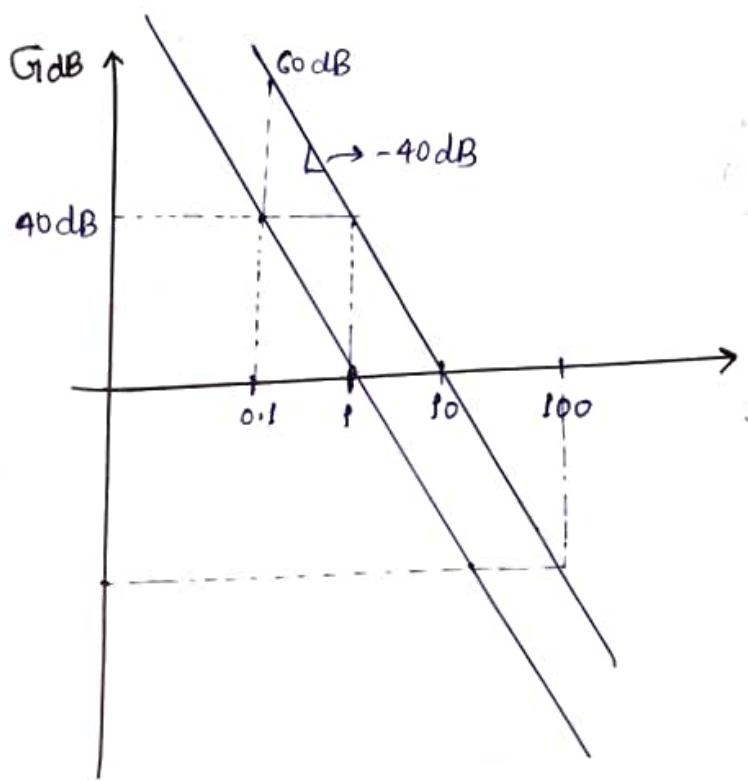

Eg.

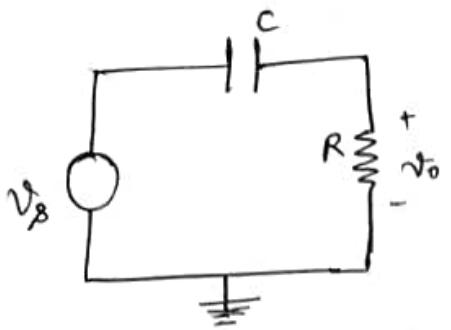


$$\frac{V_o(s)}{V_s(s)} = \frac{\frac{1}{sC}}{1 + \frac{1}{sL}}$$

$$= G_1(s)$$

$$G_1(j\omega) = \frac{j\omega L}{1 + j\omega L}$$

$$G_1(s) = \frac{8L}{s} \cdot \frac{1}{1 + \frac{s}{8L}}$$


$$G_1 \quad \quad \quad G_2$$

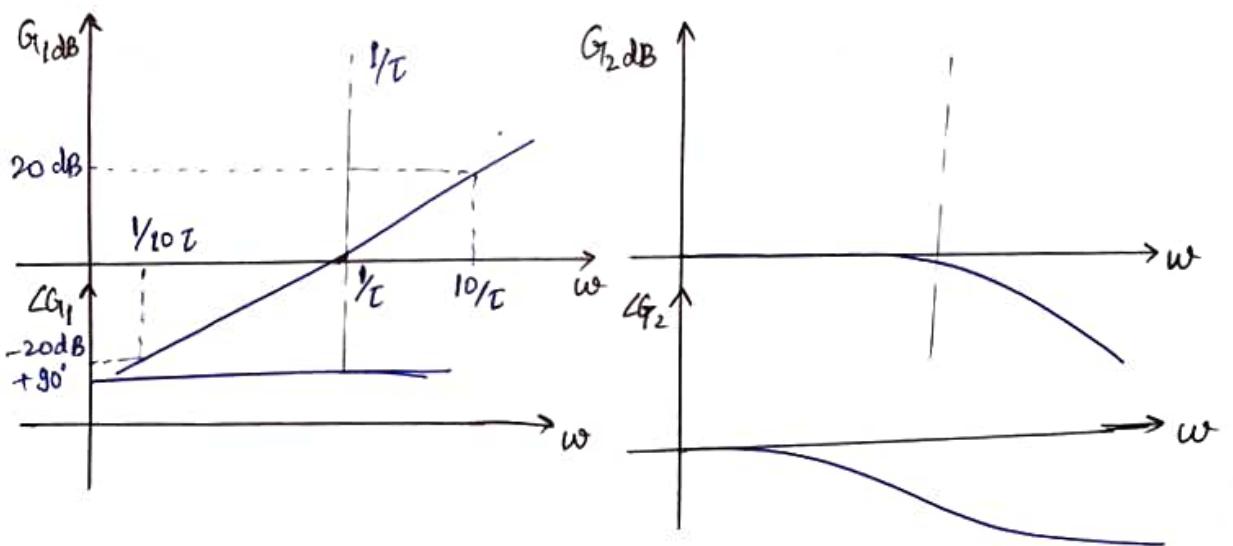

Eg. $G(s) = \frac{s+10}{(s+100)(s+0.1)}$

$$\rightarrow \frac{1}{s^m}, (1 + Ts)^{\pm m}, K$$





Case Study 1:

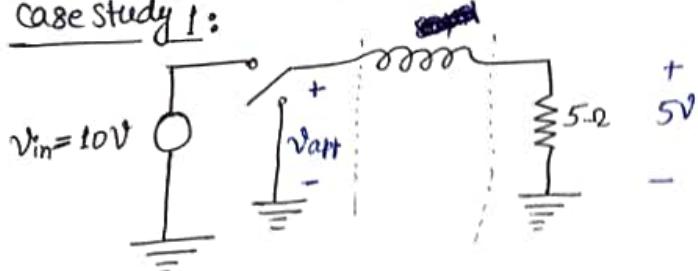


$$V_{in} = 10V, V_o^* = 5V, R = 5\Omega.$$

- All high f_s ($f_s = 100\text{Hz}$) in V_o should be attenuated by 20 dB.

$$A_t = \frac{1}{\text{gain}}$$

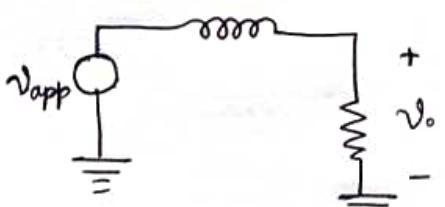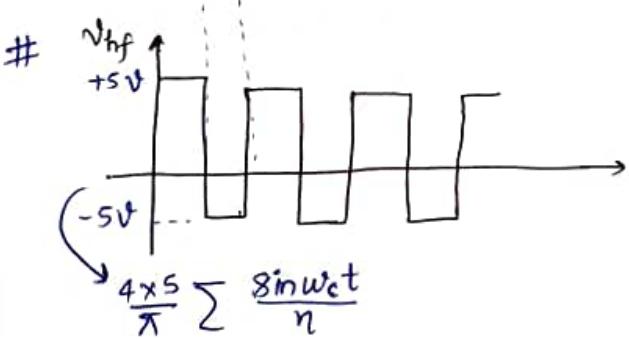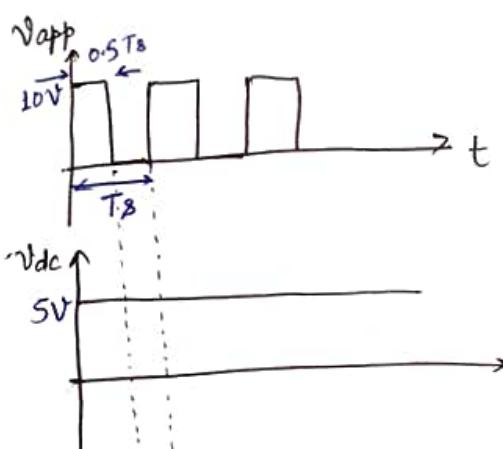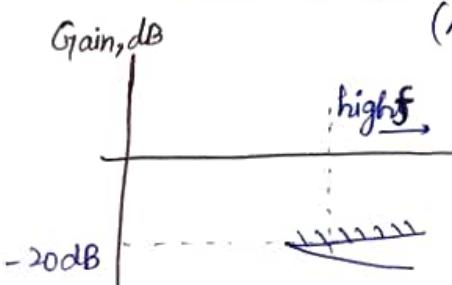
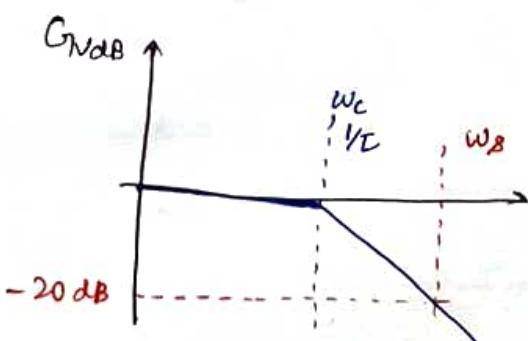
$$G_{V(8)} = \frac{V_o(8)}{V_{app}(8)} = \frac{1}{1 + 8\tau}$$



$$G_{V \text{ dB}} \Big|_{w \gg w_c} \approx \frac{1}{w\tau} = \frac{w_c}{w}$$

$G_{\text{gain at } \omega_s} \leq -20 \text{ dB}$

$$\Rightarrow 20 \log \frac{\omega_c}{\omega_s} \leq -20 \text{ dB}$$

$$\Rightarrow \frac{\omega_c}{\omega_s} \leq 1$$

$$\Rightarrow \omega_s \geq 10 \omega_c$$

$$\Rightarrow \omega_s \geq \frac{10}{T} \Rightarrow \omega_s \geq \frac{10R}{L} \text{ or } L \geq \frac{10 \times R}{2\pi f_s}$$


$$\Rightarrow L \geq \frac{10 \times 5}{2\pi \times 10^5}$$

$$\Rightarrow L \geq \frac{25 \times 10^{-5}}{\pi}$$


$$\Rightarrow L \sim 7.4 \times 10^{-5}$$


Case Study 2:

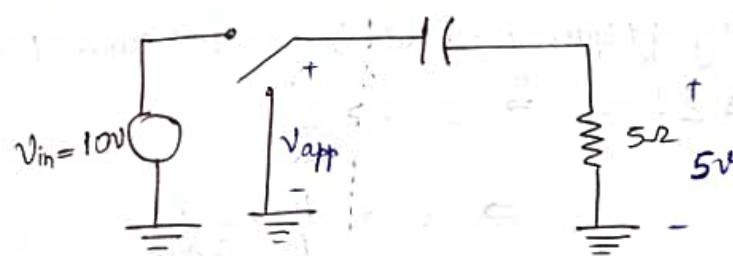Block the dc component and pass the high f components with a phase lag/lead $< 5^\circ$ by using minimum size of capacitance.


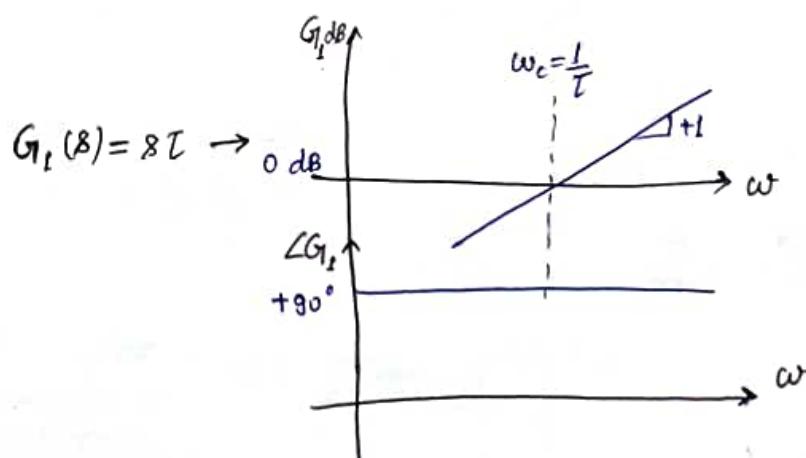
$$G_V(s) = \frac{V_o(s)}{V_{\text{app}}(s)} = \frac{8T}{1+sT}$$
$$= 8T \cdot \underbrace{\frac{1}{1+sT}}_{G_2}$$
$$\underbrace{G_1}_{G_1}$$



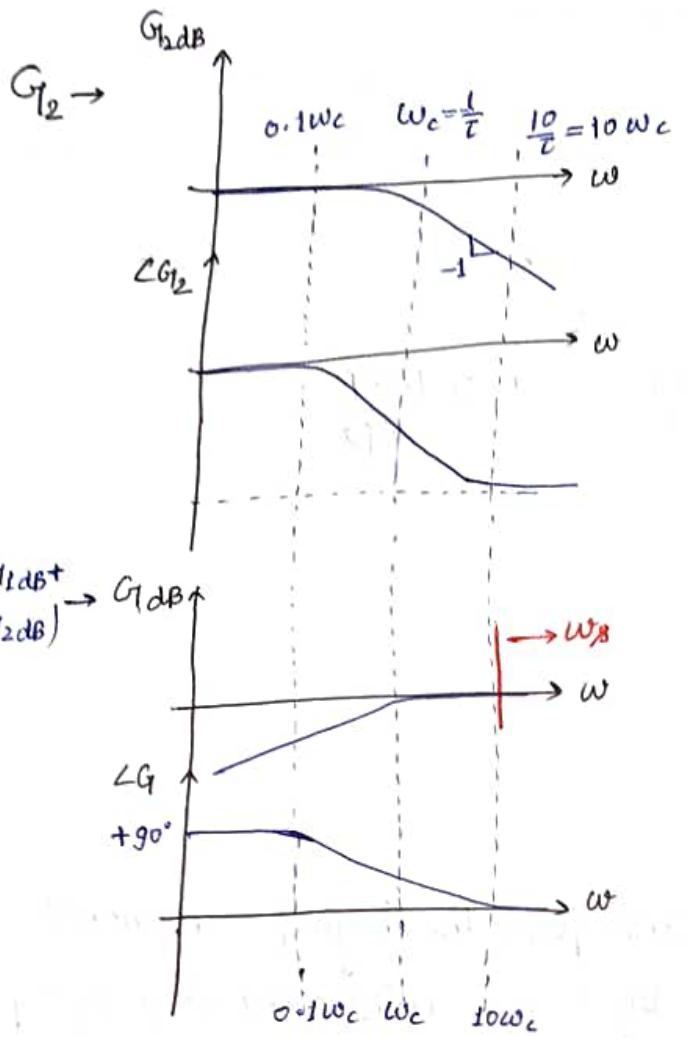

Switching frequency should be greater than 1 decade above ω_c .

$$\omega_8 \geq 10\omega_c \Rightarrow 2\pi f_8 \geq \frac{10}{RC}$$





$$\Rightarrow C \geq \frac{10}{R} \times \frac{1}{2\pi f_8}$$

$$\approx \frac{10}{5} \times \frac{1}{6 \times 10^5}$$

$$\Rightarrow C \geq 3.18 \times 10^{-6} F$$



$\leftarrow JX = (S)_1 R$

Pass Band Filter :

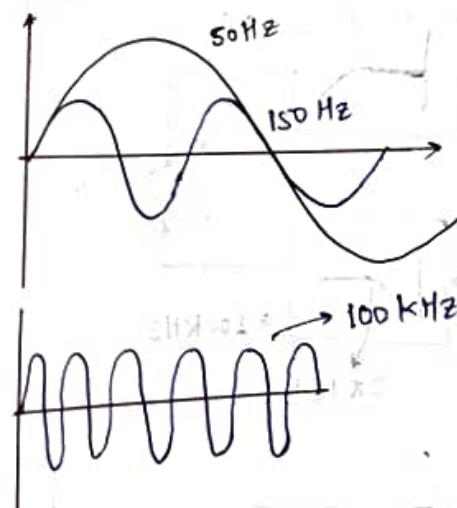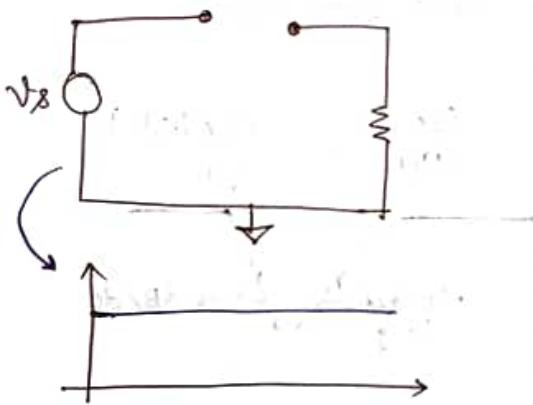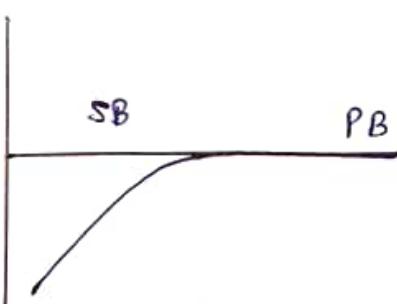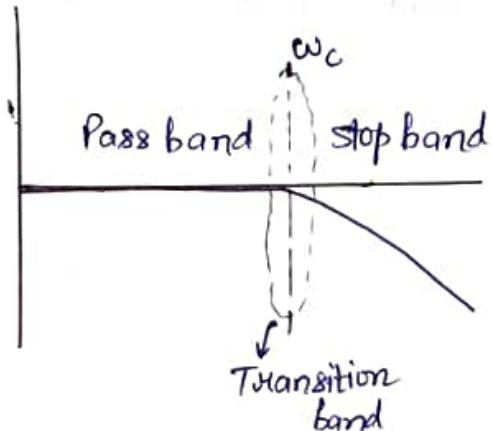


Q) Design a band pass filter that passes 50Hz and 150Hz components in V_B with unity gain and attenuates DC and 100 kHz components by atleast 20dB.
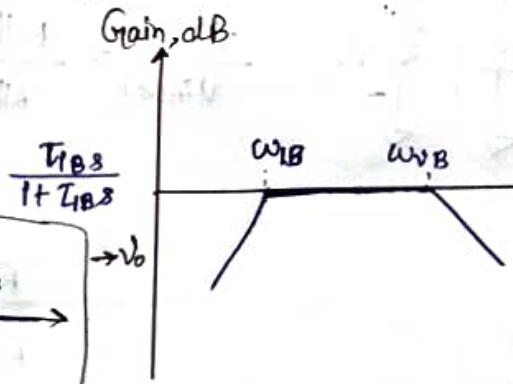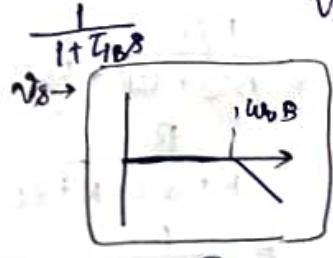
$$\text{Defn: } G(s) = \frac{V_o(s)}{V_B(s)}$$




Sequence doesn't matter

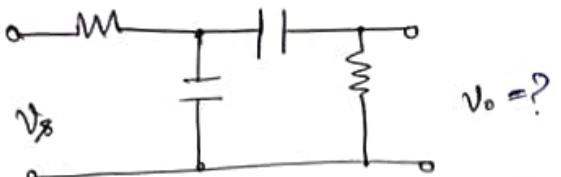



$\omega_{LB} \rightarrow 50\text{Hz} \rightarrow 5\text{kHz}$

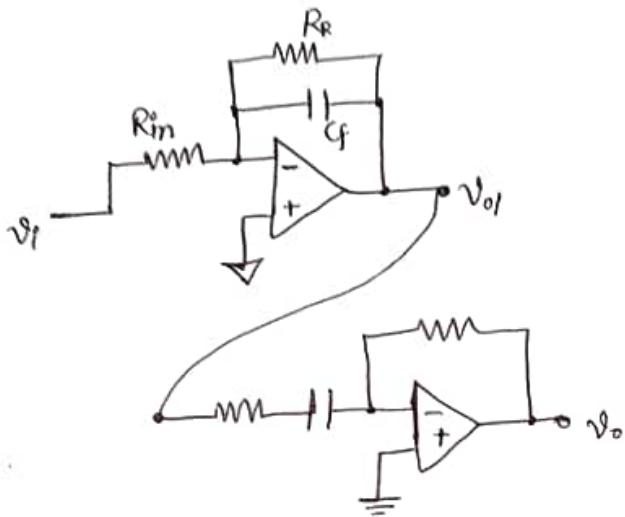At high frequency \rightarrow Output = 0
DC \rightarrow Output = 0




Eg Design a band stop filter that attenuates 50 Hz and 150 Hz components in V_s by atleast 20 dB and pass DC and 100 kHz.

Soln:

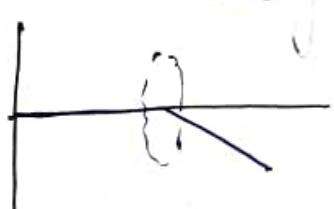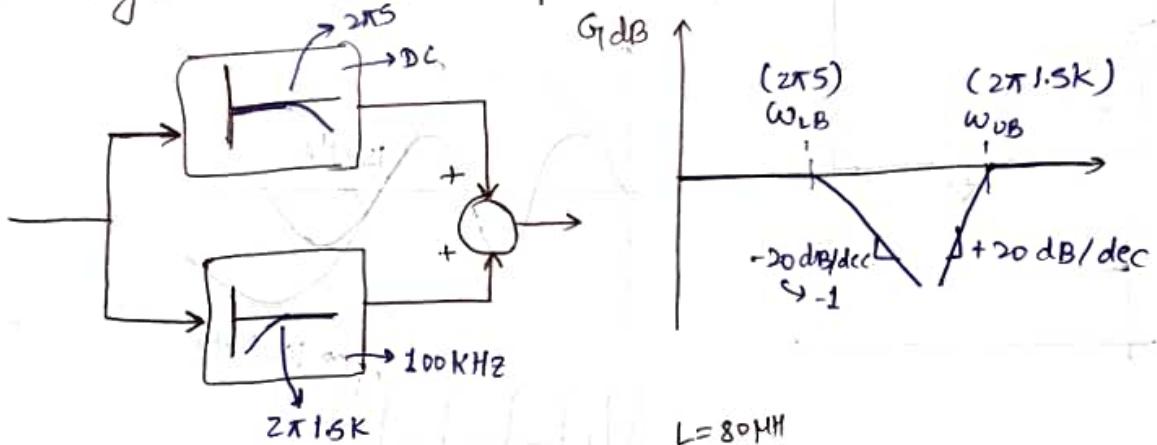

$$L = 80\mu\text{H}$$

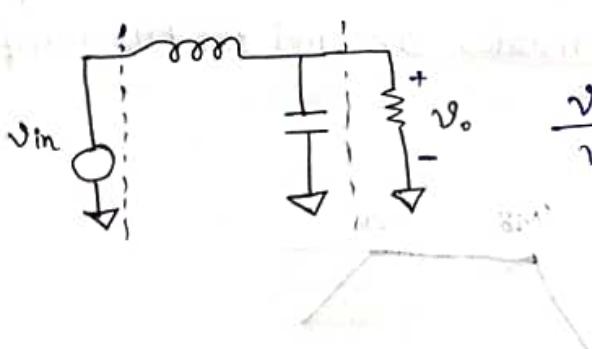
- 100 kHz and above to be attenuated by 20dB.



$$\frac{V_o(s)}{V_{in}(s)} = \frac{R \parallel \frac{1}{sC}}{R \parallel \frac{1}{sC} + 8L}$$



$$= \frac{\frac{R}{sC}}{\frac{R}{sC} + \frac{1}{8L}}$$
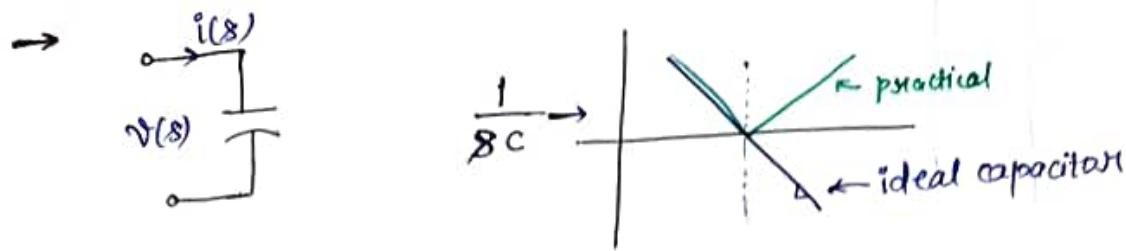
$$= \frac{R/8C}{R/8C + RLR + 4C} \\ = \frac{R}{R + 8^2 LCR + 8L} \\ = \frac{1}{8^2 C + 8^4 / R + 1}$$




$$V(s) = \frac{1}{sC} I(s)$$

$$\Rightarrow \frac{I(s)}{V(s)} = sC$$

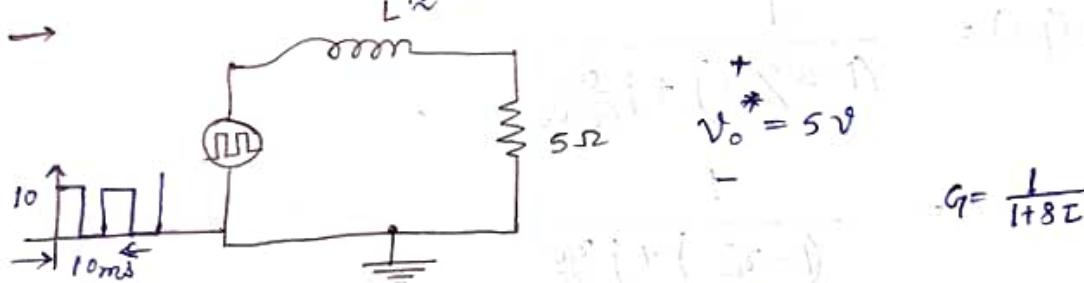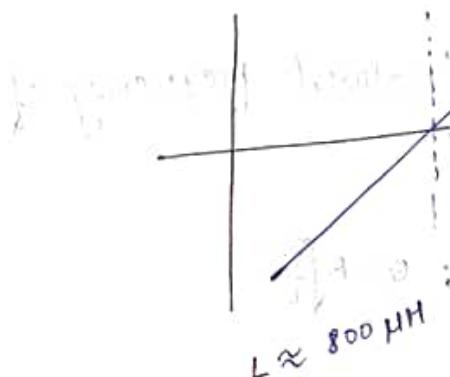

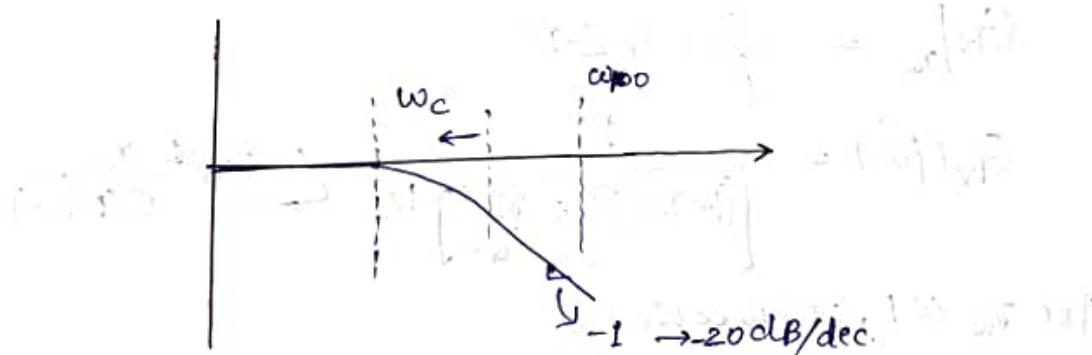
At least 40 dB attenuation to frequency
at 100 kHz and above.



$$w_c \leq \frac{1}{100} w_{100} \Rightarrow \frac{R}{L} \leq \frac{1}{100} \times 2\pi \times 100 \text{ K}$$

$$\Rightarrow L \geq \frac{100 \times 5}{2\pi \times 100 \text{ K}} = 7.96 \times 10^{-4} \text{ H}$$
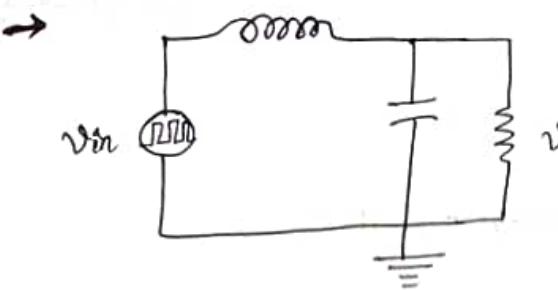
$$\Rightarrow L \approx 800 \mu\text{H}$$



$$\frac{v_o(s)}{v_{in}(s)} = \frac{1}{LCs^2 + \frac{R}{L}s + 1} = G_{Vv}(s)$$

Standardized form of representation :

$$G_{Vv}(s) = \frac{1}{s^2/\omega_c^2 + s/Q\omega_c + 1}$$

where,

ω_c : corner/resonant/natural frequency of oscillation

Q : Quality factor

$$\propto \frac{1}{\xi} \quad ; \quad Q = R \sqrt{\frac{C}{L}}$$

$$G_{Vv}(j\omega) = \frac{1}{(1 - \omega^2/\omega_c^2) + j\frac{\omega}{Q\omega_c}}$$

$$= \frac{1}{(1 - r_\omega^2) + j \frac{r_\omega}{Q}}$$

where, $r_\omega \triangleq \omega/\omega_c$.

$$G_{Vv}|_{r_\omega} = \frac{Q}{j} = Q \angle -90^\circ$$

$$G_{Vv}(j\omega) = \frac{1}{\left[(1 - r_\omega^2)^2 + \frac{r_\omega^2}{Q^2} \right]^{1/2}} \angle -\tan^{-1} \frac{r_\omega}{Q(1 - r_\omega^2)}$$

for $r_\omega \ll 1$, i.e., $\omega \ll \omega_c$,

$$|G_{Vv}| = \left[(1 - r_\omega^2)^2 + \frac{r_\omega^2}{Q^2} \right]^{1/2} \approx 1 \Rightarrow G_{Vv \text{dB}} = 0$$

$$\angle G_V = -\tan^{-1} \frac{r_\omega}{Q(1 - r_\omega^2)} \approx -\tan^{-1} \frac{r_\omega}{Q} \approx 0^\circ$$

for $\tau_\omega \ll 1$, i.e., $w \gg w_c$,

$$|G_{Vr}| = \frac{1}{[(1-\frac{\omega}{\omega_c})^2 + \frac{\omega^2}{Q\omega_c}]^{1/2}} \approx \frac{1}{\omega} = \frac{\omega_c^2}{\omega^2}$$


$$\angle G = \angle \tan^{-1} \frac{\omega}{Q(1-\frac{\omega}{\omega_c})} \approx \angle -\tan^{-1} \left(-\frac{1}{Q\omega_c} \right)$$

Suppose $Q=1$, $\tau_\omega=10$

$$\Rightarrow \angle G = 5.7^\circ$$

$$\omega_c=100 \Rightarrow \angle G = 0.57^\circ$$

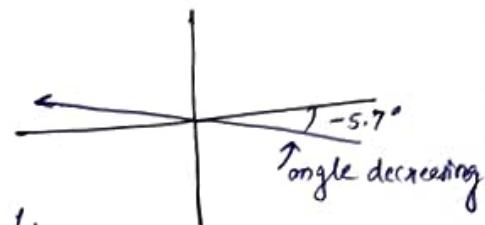
$\angle G$ approaches -180° as $\omega \gg 1$.
 (Refer to graph)



$$G_{Vr} \Big|_{\omega_c=10} = \frac{1}{100} \rightarrow 1 \text{ dec above } w_c : G_{VdB} = -40 \text{ dB}$$


$$G_{Vr} \Big|_{\omega_c=100} = \frac{1}{10^4} \rightarrow G_{VdB} = -80 \text{ dB}$$
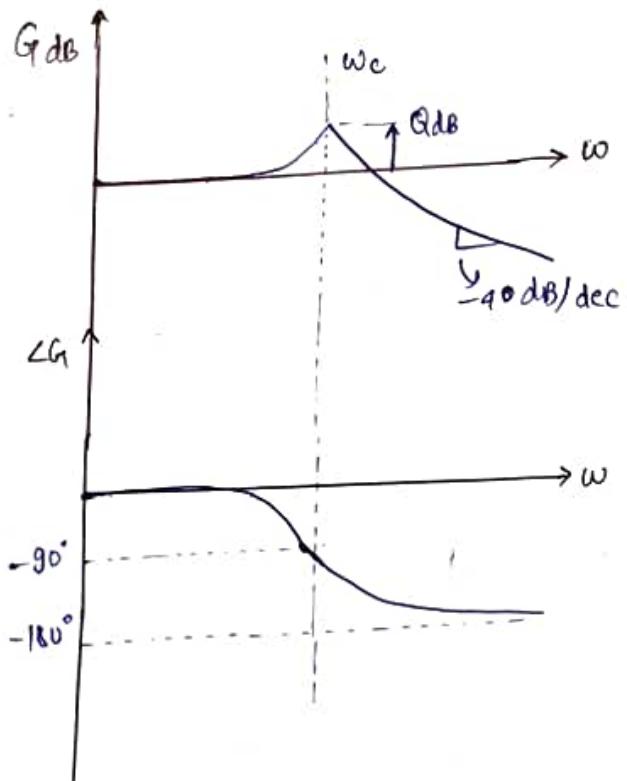
$$G(s) = \frac{1}{s^2/\omega_c^2 + s/Q\omega_c + 1}$$




Review:

20-11-2023


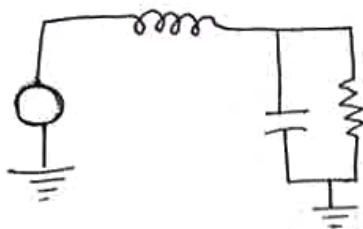


$$G(s) = \frac{1}{LCs^2 + sL/R + 1}$$
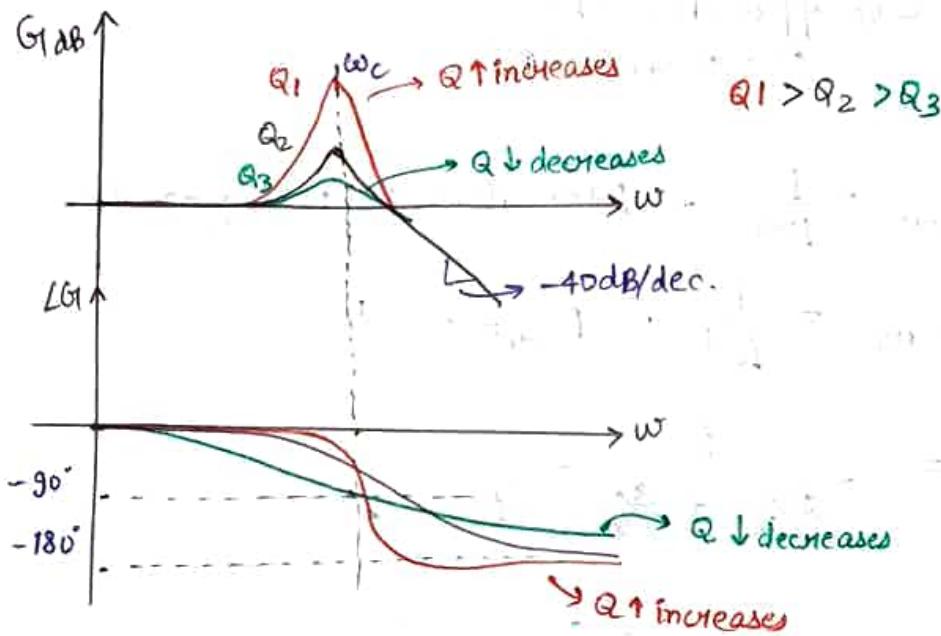
$$= \frac{1}{s^2/\omega_c^2 + s/Q\omega_c + 1}$$



Design

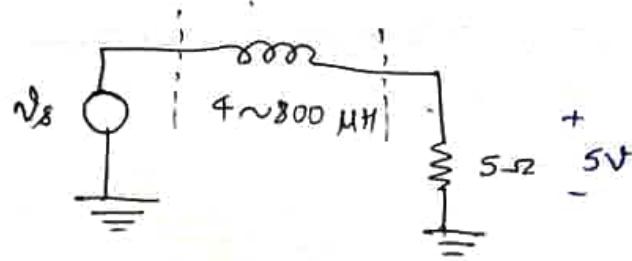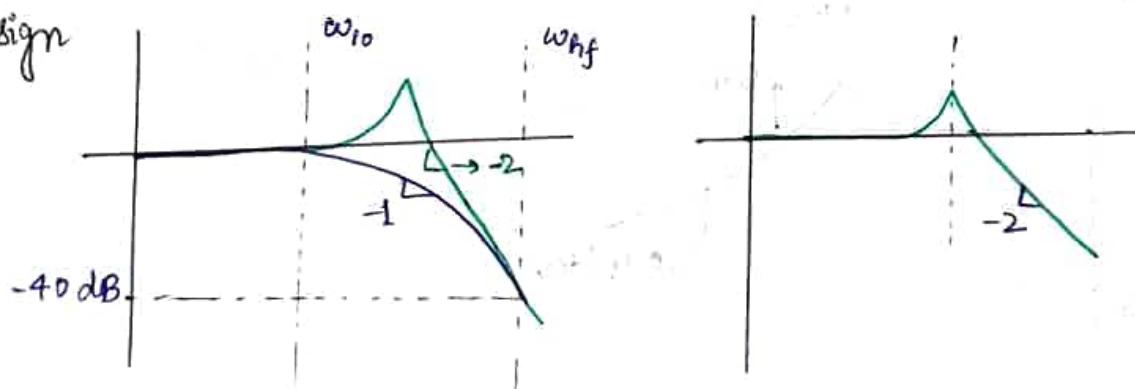

40 dB attenuation to 100 kHz.

At $\omega \gg \omega_c$,

$$|G| \underset{\omega \gg \omega_c}{\approx} \frac{\omega_c}{\omega^2}$$

$$20 \log \frac{\omega_c^2}{\omega^2} \leq -40 \text{ dB}$$

$$\Rightarrow \omega_c \leq 0.1 \omega_{00}$$

$$\Rightarrow \frac{1}{\sqrt{LC}} \leq \frac{1}{10} \times 2\pi \times 10^8$$

$$\Rightarrow LC \geq \left(\frac{1}{2\pi \times 10^8} \right)^2$$

$$\Rightarrow LC \geq \frac{1}{36 \times 10^8}$$

Let's choose $C = 10 \text{ nF}$ (63 V)

$$\text{then, } L \geq \frac{10^6}{10} \times \frac{1}{36 \times 10^8}$$


$$\Rightarrow L \geq 27 \mu\text{H}$$

Adding a zero at the origin to the transfer function,

$$G_1(s) = \frac{s/\omega_c}{s^2/\omega_c^2 + s/Q\omega_c + 1}$$

$$= \underbrace{\frac{s}{\omega_c}}_{G_1(s)} \cdot \underbrace{\frac{1}{s^2/\omega_c^2 + s/Q\omega_c + 1}}_{G_2(s)}$$


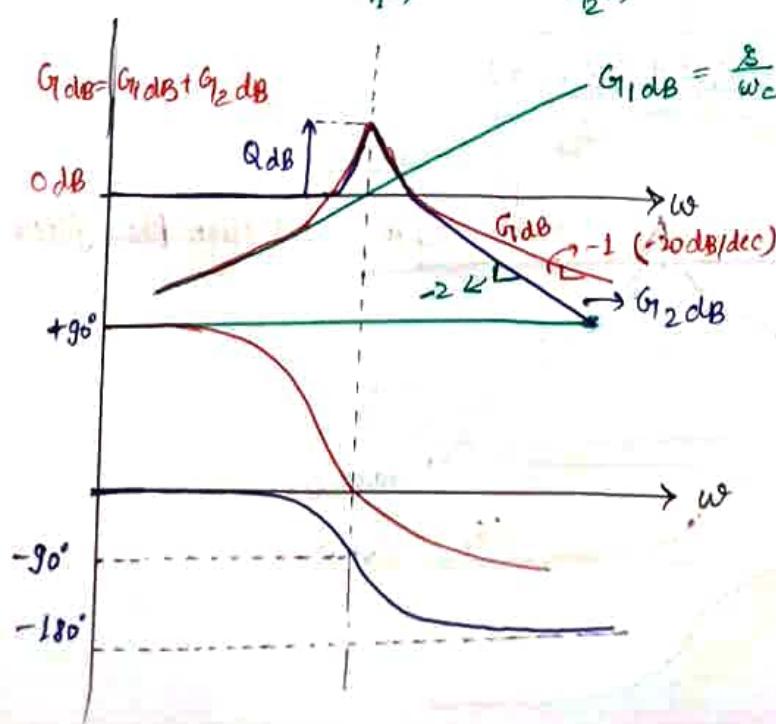
$$G_{1,\text{dB}} = G_{1,\text{dB}} + G_{2,\text{dB}} \quad G_{1,\text{dB}} = \frac{s}{\omega_c} \quad (\# \frac{j\omega}{\omega_c} = r \omega \angle 90^\circ)$$



$$G_3(s) = \frac{\frac{s}{Q\omega_c}}{s^2/\omega_c^2 + \frac{s}{Q\omega_c} + 1} \quad (\text{Introducing } \frac{1}{Q} \text{ factor})$$

$$= \frac{1}{Q} \cdot \frac{\frac{s}{\omega_c}}{s^2/\omega_c^2 + \frac{s}{Q\omega_c} + 1}$$

$\downarrow G_{dc}$ $\downarrow G_2$

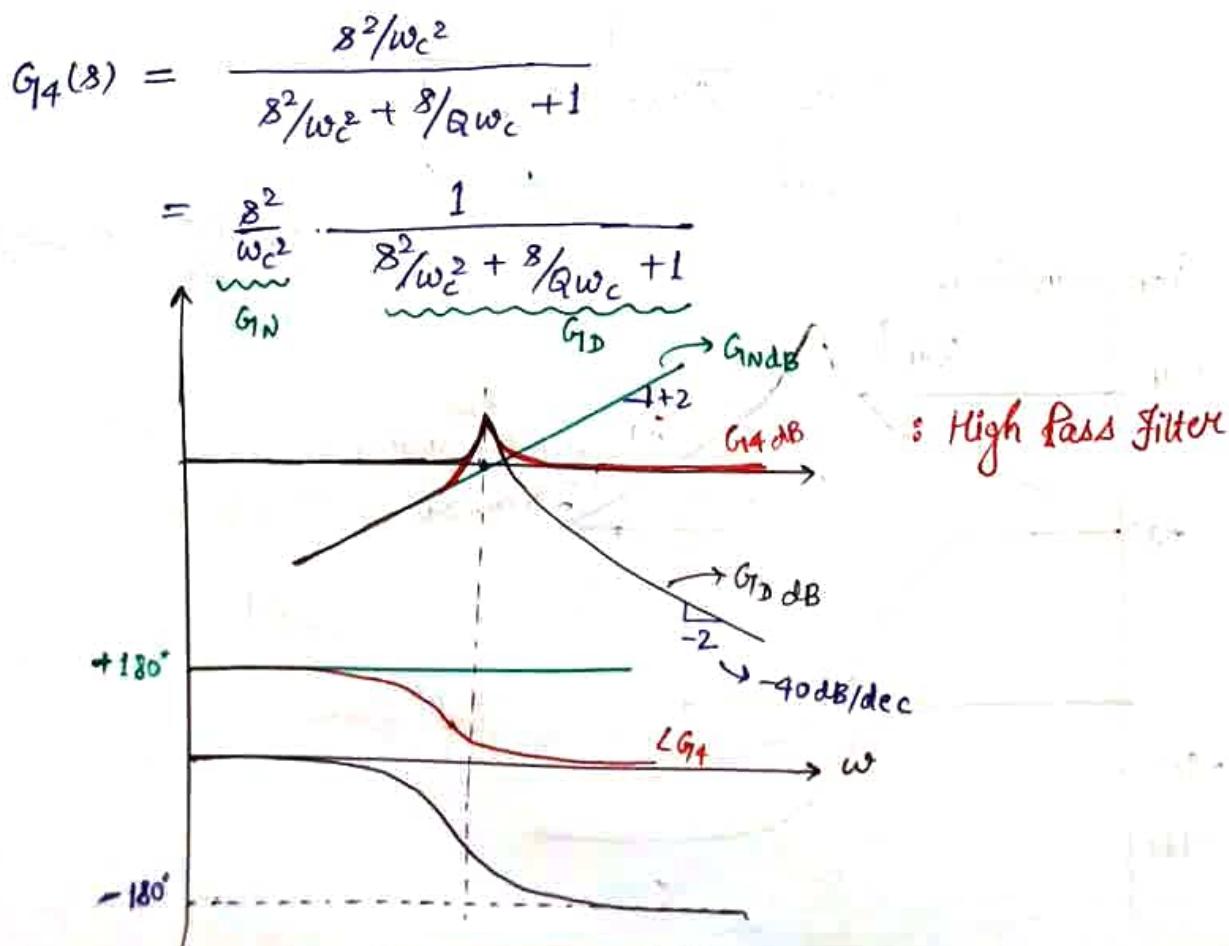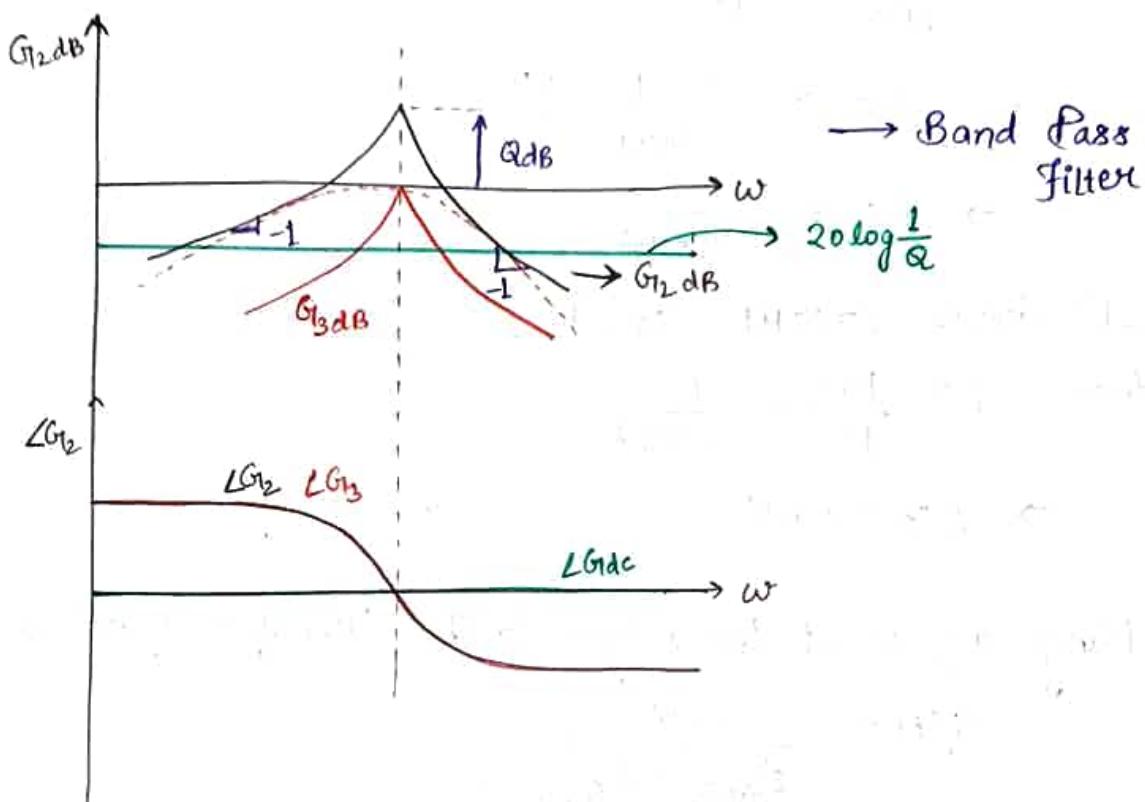


$$\text{Eq. } G(s) = \frac{s^2/\omega_c^2 + 1}{s^2/\omega_c^2 + s/Q\omega_c + 1}$$


$$G_N(s) = \frac{s^2/\omega_c^2 + 1}{s^2/\omega_c^2 + 1}$$

$$\begin{aligned} G_N(j\omega) &= 1 - \omega^2/\omega_c^2 \\ &= 1 - \gamma_\omega^2 \end{aligned}$$

$$G_N(j\omega) \Big|_{\omega=\omega_c} = 0$$

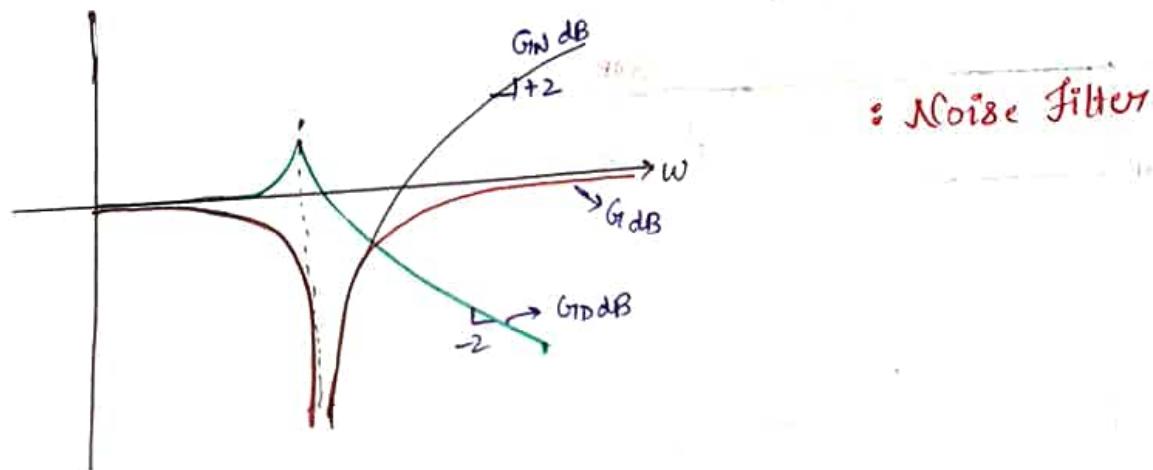

High Pass

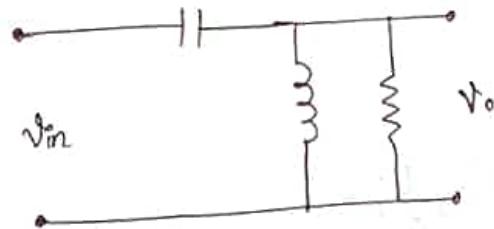


Eg. ~~D. P. ①(b)~~ ~~$\frac{8+1}{8+10}$~~ = $\frac{1}{10} \cdot \frac{8+1}{0.18+1}$ ($\frac{1+\frac{1}{18}}{1+\frac{1}{10}} \text{ form}$)

$$= \frac{1}{10} \cdot (8+1) \cdot \frac{1}{(0.18+1)}$$

$$\underbrace{G_1}_{w_c = \frac{1}{\tau} = 1} \quad \underbrace{G_2}_{w_c = 1} \quad \underbrace{G_3}_{w_c = 10}$$
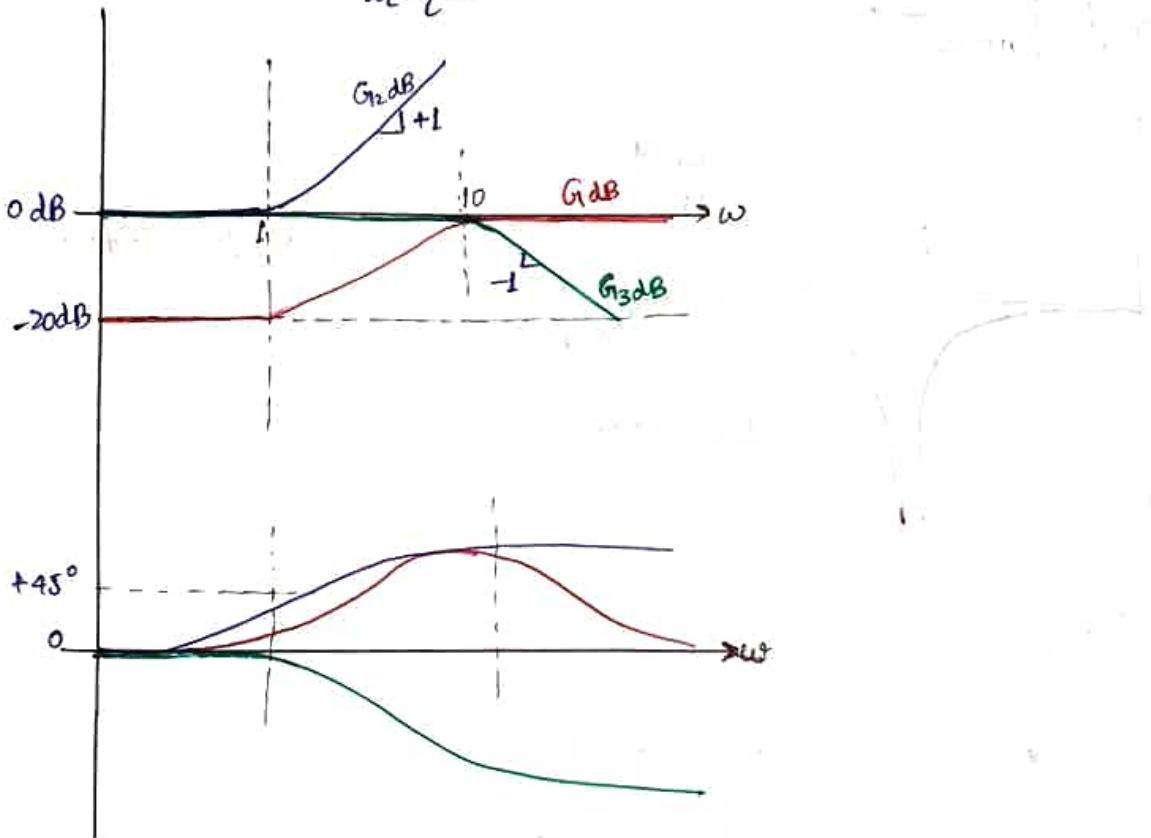
$$\rightarrow w_c = \frac{1}{\tau} = 10$$



Eg. D. P. ①(f) $\frac{s^2 + s + 1}{s} = \underbrace{(s^2 + s + 1)}_{\{ G_N \}} \cdot \underbrace{\left(\frac{1}{s}\right)}_{G_D}$

$$\downarrow$$


$$(s^2/w_c^2 + s/Qw_c + 1)$$

$$G_N(j\omega) = (1 - \omega^2) + j\omega$$

$$\text{for } \omega = 1, G_N(j\omega) = 1 \angle +90^\circ$$



$$\omega \gg 1, |G_N(j\omega)| \approx \omega^2$$

$$\omega \ll 1, |G_N(j\omega)| = 1$$


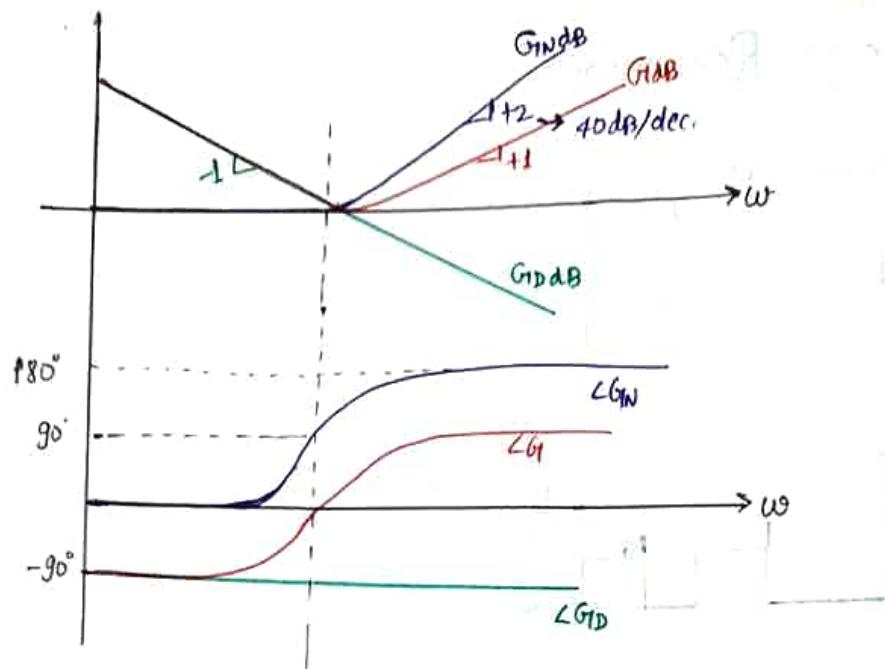


Q Design a passive and an active 1st order high pass filter which passes components $\geq 2 \text{ kHz}$ with a gain of 5.


D.P. set 2
④ Soln:

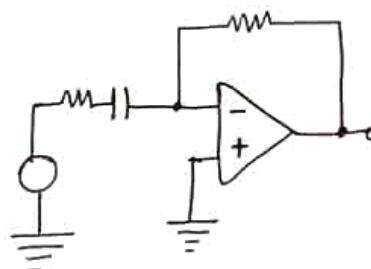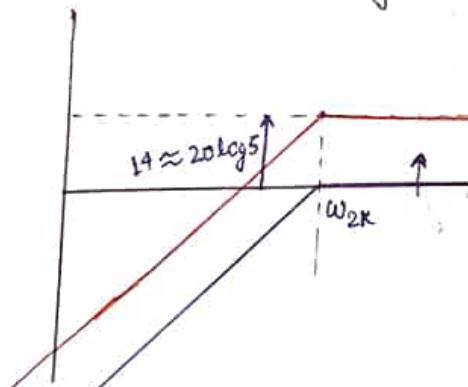

Brief Note on Resonance

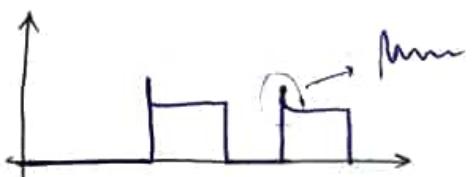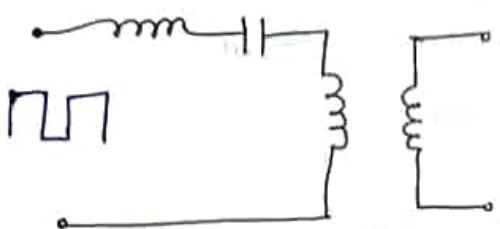

Series RLC

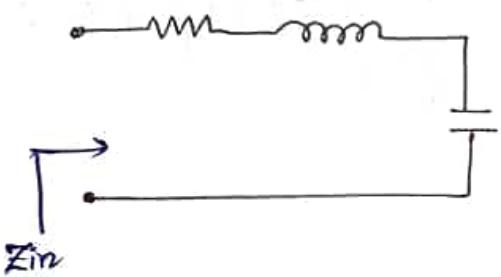

At $\omega = \omega_c$ (Resonance frequency)

$$Z_{in} = R$$


$$\Rightarrow \omega L = \frac{1}{\omega c}$$

$$\Rightarrow \omega_c = \frac{1}{\sqrt{LC}}$$

$$\xi \propto R$$


$$Q = \frac{\omega_c L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$
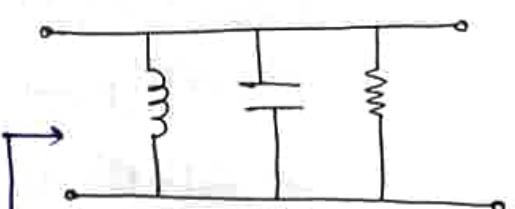
$$\frac{8^2}{\omega_c^2} + \frac{8}{Q\omega_c} + 1$$



$$\xi \propto \frac{1}{R}$$

Sallen-Key

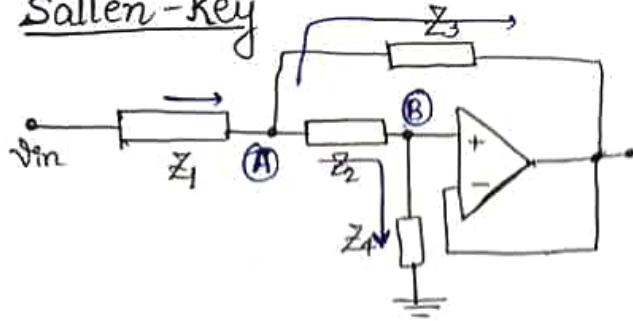

$$\frac{v_{in} - v_A}{Z_1} = \frac{v_A - v_o}{Z_2} + \frac{v_A - v_o}{Z_3}$$

and, $v_o = \frac{Z_4}{Z_2 + Z_4} v_A \Rightarrow v_A = \frac{Z_2 + Z_4}{Z_4} v_o$

$$\Rightarrow \frac{v_{in}}{Z_1} - \frac{Z_2 + Z_4}{Z_1 Z_4} v_o = \frac{Z_2 + Z_4}{Z_2 Z_4} v_o - \frac{v_o}{Z_2} + \frac{Z_2 + Z_4}{Z_3 Z_4} v_o - \frac{v_o}{Z_3}$$

$$\Rightarrow \frac{1}{Z_1} - \frac{Z_2 + Z_4}{Z_1 Z_4} G(s) = \frac{Z_2 + Z_4}{Z_2 Z_4} G(s) - \frac{G(s)}{Z_2} + \frac{Z_2 + Z_4}{Z_3 Z_4} G(s) - \frac{G(s)}{Z_3}$$

$$\Rightarrow \frac{\cancel{Z_1} \cancel{(Z_2 + Z_4)} G(s) \cancel{Z_2^2 Z_3 + Z_2 Z_3 Z_4}}{\cancel{Z_1 Z_4}} = \frac{\cancel{Z_2 Z_4} G(s)}{\cancel{Z_2}} - \frac{G(s)}{\cancel{Z_2}} + \frac{\cancel{Z_2 Z_4} G(s)}{\cancel{Z_3 Z_4}} - \frac{G(s)}{\cancel{Z_3}}$$


$$\Rightarrow \frac{Z_2 Z_3 + Z_3 Z_4 + Z_1 Z_3 + Z_1 Z_2}{Z_3 Z_4} G(s) = 1$$

$$\Rightarrow G(s) = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3 + Z_3 Z_4}$$

$$\frac{1}{s^2/w_c^2 + s/Qw_c + 1}$$

$$Z_3 Z_4 \rightarrow R_C$$

: High Pass

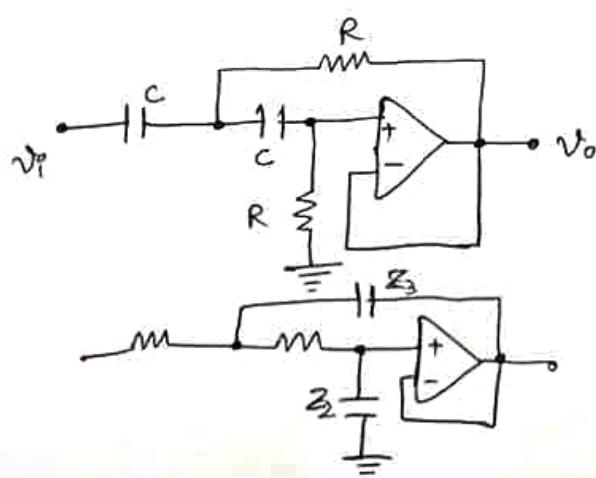



: Low Pass

Z₁Z₂

$$Z_1Z_2 + Z_2Z_3 + Z_3Z_4 + Z_4Z_1$$

$$= \frac{\frac{1}{8C_4} \cdot \frac{1}{8C_3}}{R_1R_2 + \frac{1}{8C_3}(R_1+R_2) + \frac{1}{8^2C_3C_4}}$$

Two Port Parameter

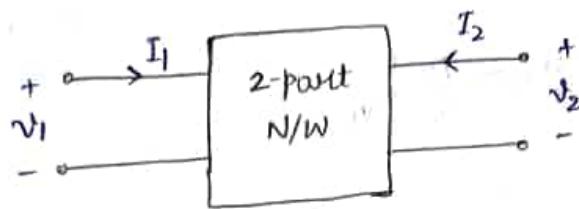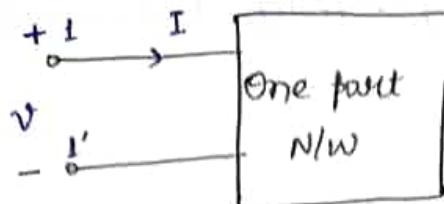


Z_{ab} parameters : (Impedance Parameters)

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \left. \begin{array}{l} I_1, I_2 : \text{independent} \\ V_1, V_2 : \text{dependent} \end{array} \right\}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \left. \begin{array}{l} I_1, I_2 : \text{independent} \\ V_1, V_2 : \text{dependent} \end{array} \right\}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}, \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}, \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

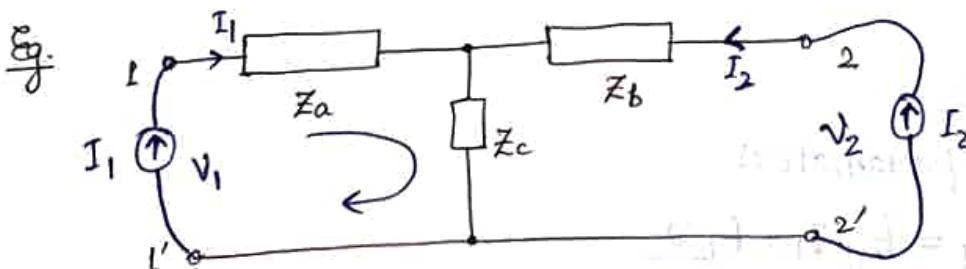

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = Z_a + Z_c$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = Z_c$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_b + Z_c$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = Z_c$$

\mathbf{Y} -Parameters: (Admittance Parameters)

$$\left. \begin{array}{l} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = V_{21} V_1 + Y_{22} V_2 \end{array} \right\} \quad V_1, V_2 : \text{independent variables}$$


$$\left. \begin{array}{l} Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}, \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \\ Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}, \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \end{array} \right\} \quad \text{Short-circuit parameters}$$

Eg.

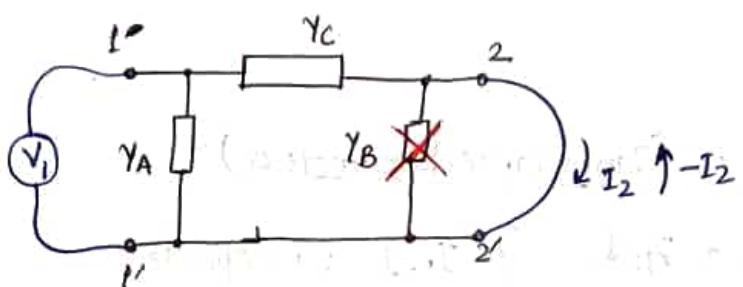

$$Y_{11} : V_1(Y_A + Y_c) = I_1 \Rightarrow Y_{11} = Y_A + Y_c$$
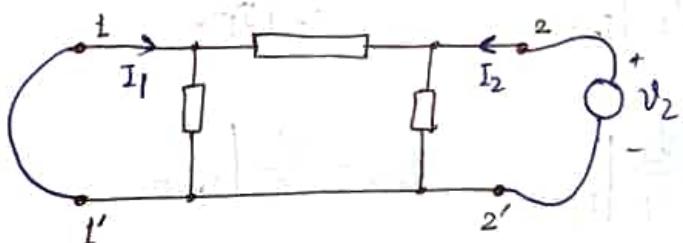
$$Y_{21} : V_1 Y_c = -I_2 \Rightarrow Y_{21} = -Y_c$$



\mathbf{h} -Parameters

↳ Hybrid-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

ABCD: Transmission line parameters

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$