

मौलिक वैद्युताभियन्त्रणम्
BASIC ELECTRICAL
ENGINEERING

CIRCUIT ELEMENTS

Active Elements

↳ Supply energy

Passive Elements

↳ Store/consume energy

① Resistor (R): Dissipates (consume) energy
convert to other forms

Resistance unit: Ohm (Ω)

② Inductor (L): Stores electrical energy
↳ Kinetic element ($E = \frac{1}{2} L i^2$)

Inductance unit: Henry

③ Capacitor (C): Stores electrical energy
↳ Potential element

Capacitance unit: Faraday (F), μF , nF

↳ Source of energy

↳ Load - energy consume

(Resistor can be used to represent load)

Element

Basic Relationship (voltage - current relationship)

Resistor

$$V = IR, I = V/R$$

Capacitor

$$q = CV$$

$$i_c = \frac{dq}{dt} = \frac{d}{dt}(CV_c) = C \frac{dV_c}{dt} \Rightarrow i_c = C \frac{dV_c}{dt}$$

$$\Rightarrow V_c = \frac{1}{C} \int i_c dt$$

Inductor

$$\Psi = Li$$

$$V_L = \frac{d\Psi}{dt} = \frac{d}{dt}(Li_L) = L \frac{di_L}{dt} \Rightarrow V_L = L \frac{di_L}{dt}$$

$$\Rightarrow i_L = \frac{1}{L} \int V_L dt$$

Resistor

$$V = IR$$



Scaling


Inductor

$$\phi = Li$$

$$V = \frac{d\phi}{dt} = \frac{d}{dt}(Li) = L \frac{di}{dt}$$

→ i mm


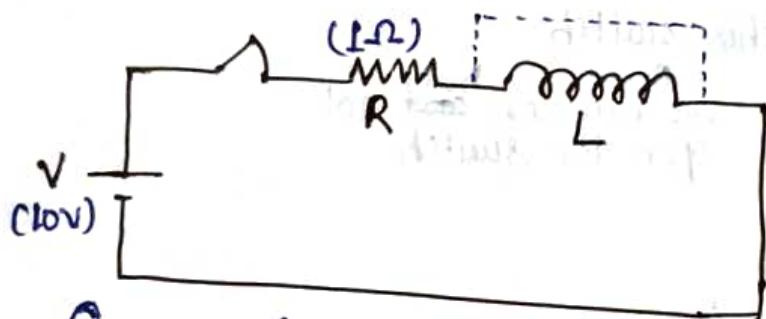
Current in a fixed inductor system cannot change abruptly
(as $dt \rightarrow 0$, $V \rightarrow \infty$)



$$\left(\frac{V}{R} = 10A \rightarrow \text{steady current} \right)$$


On opening switch,
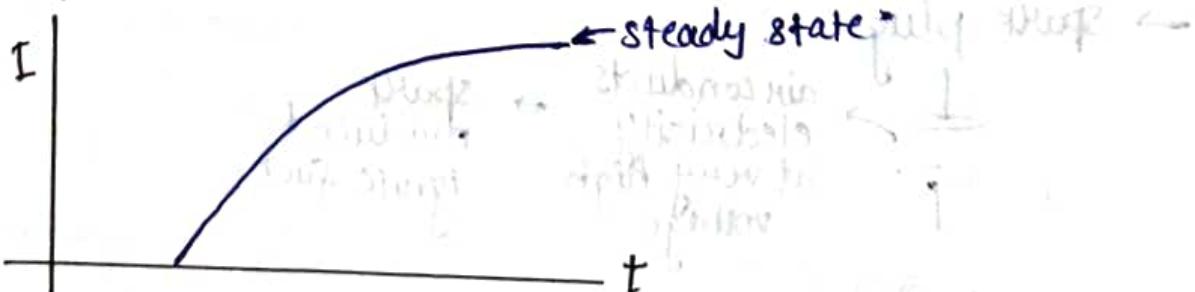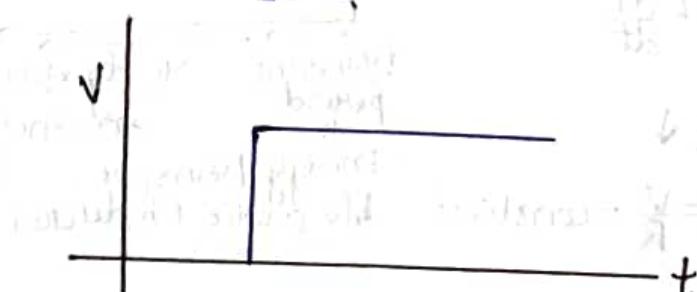
$$V = L \frac{di}{dt} = \frac{1 \times 10}{1 \times 10^{-6}} \quad \begin{matrix} (\downarrow \\ \text{Blast}) \end{matrix} \quad \begin{matrix} (dt = 10^{-6} \text{ for} \\ \text{electronic switch}) \end{matrix}$$



→ Inductor current shall not be interrupted

$$V = L \frac{di}{dt}$$

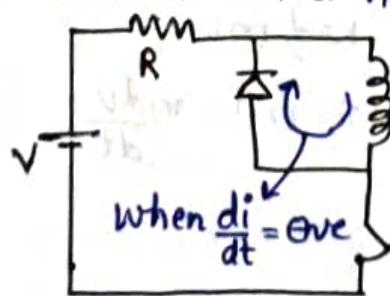


when $\frac{di}{dt} = +ve \Rightarrow V = +ve$


when $\frac{di}{dt} = -ve \Rightarrow V = -ve$

↳ diode → forward biased
(current circulates)

\rightarrow  $V_L = +ve$ (Absorbing power)

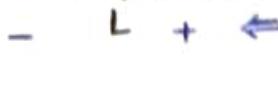
\rightarrow  $V_L = -ve$ (Releasing energy)

$$E = \frac{1}{2} L i^2$$

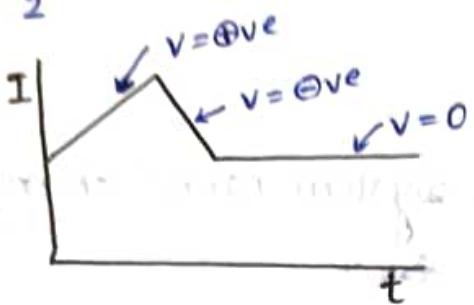


smoothens/stabilizes the current

14-03-2023

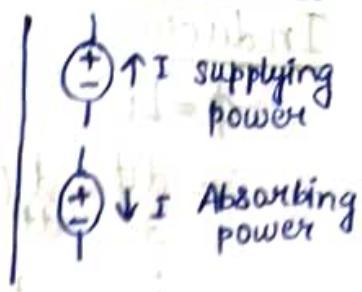

→ There is no use of this switch

we can close ~~but~~ not open the switch

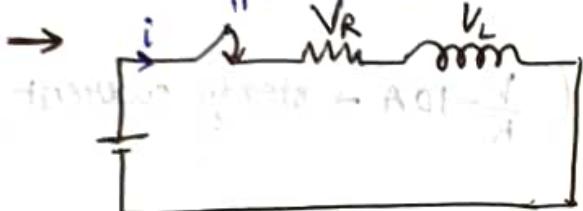

closing switch: $t=0$


At $t=0^+$, $i=0$

$$V_R = 0$$

$$V_L = V = L \frac{di}{dt}$$

After $t=0^+$, $V_R \uparrow$, $V_L \downarrow$

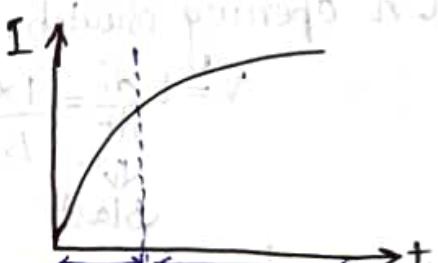
Finally ($t \rightarrow \infty$), $I = \frac{V}{R} = \text{constant}$. b/w source & inductor



↳ to energy transfer
↳ energy transfer

→ spark plug

 air conducts electricity at very high voltage \Rightarrow spark produced ignites fuel

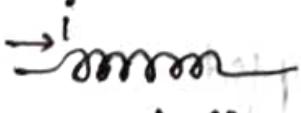
→  \Rightarrow inertial/kinetic element \Rightarrow exhibits inertia.

$$E = \frac{1}{2} L i^2$$

analogous to $K = \frac{1}{2} m v^2$


$$V = L \frac{di}{dt}$$

analogous to $F = m a = m \frac{dv}{dt}$

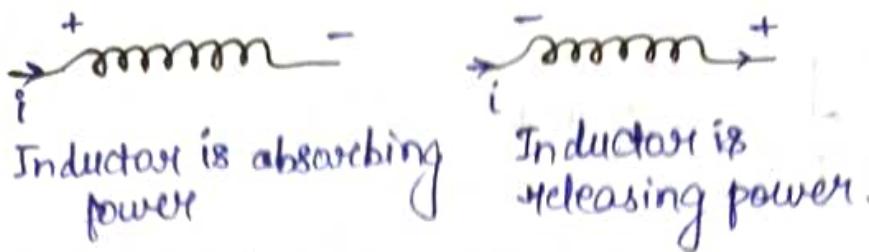

Capacitor

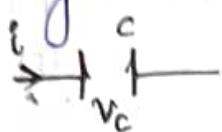↳ Makes its presence felt in the circuit if there is a change in voltage (otherwise, it'll behave like open circuit).




$$q = CV$$

$$i = \frac{dq}{dt} = \frac{d}{dt}(CV) = C \frac{dV}{dt}$$


↳ B/c of changing voltage
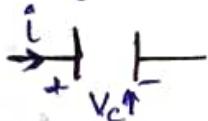
$$\frac{dV}{dt} = +ve \Rightarrow i = +ve$$



$$\frac{dV}{dt} = -ve \Rightarrow i = -ve$$

(put same polarity)

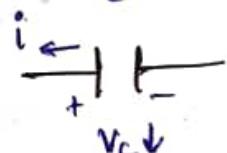


$\frac{V}{I} = \frac{+}{-}$ capacitor


$$VI \Rightarrow$$
 source is absorbing power

④ $VI \Rightarrow$ source is delivering power

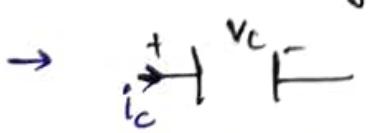$\theta VI \Rightarrow$ source is absorbing power



Absorbing/charging power

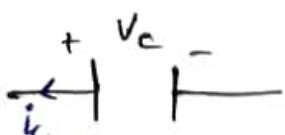

Releasing/discharging power


→ Voltage cannot change abruptly/instantaneously, as there will be infinite current.


$$i = \frac{dq}{dt} = C \frac{dV}{dt}$$

($i \rightarrow \infty$) ($dt \rightarrow 0$)

→ Capacitor stabilizes voltage in a circuit.

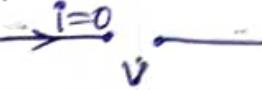There is a voltage, but no current: open circuit




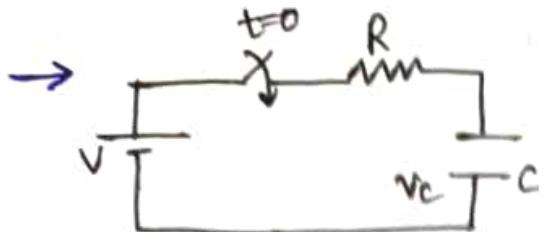


If at $t=0$, $V_C = 0$

$$t=0^+ \Rightarrow V_C = 0$$

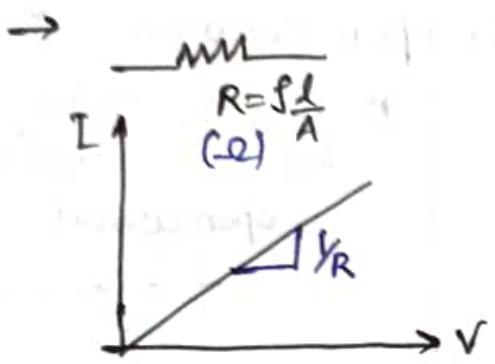
Uncharged capacitor will act like short circuit.
Source, capacitor, circuit will fail.




- $P = \int i^2 R dt$
- $V = IR$

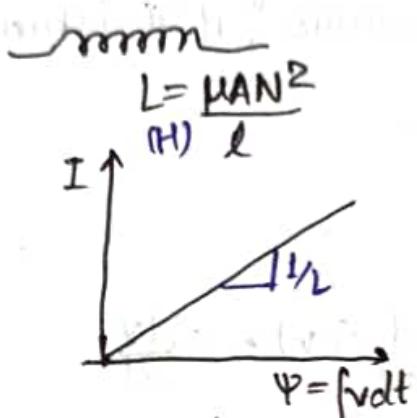

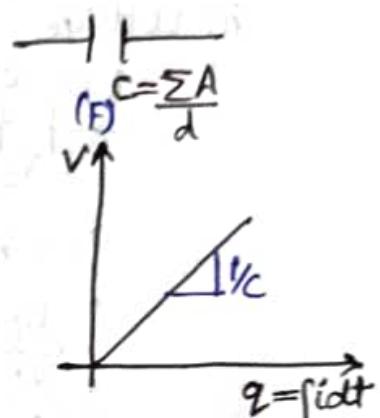
- $E = \frac{1}{2} Li^2$
- $V_L = \frac{L di}{dt}$
- $i_L = \frac{1}{L} \int V dt$



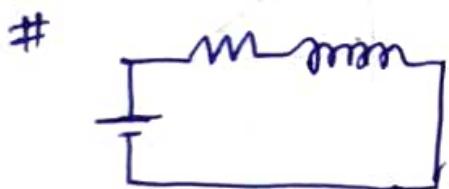- $E = \frac{1}{2} CV^2$
- $V_C = \frac{1}{C} \int i dt$
- $i_C = C \frac{dV}{dt}$





→ analogous to

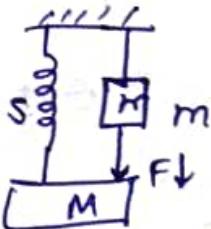




Mass
spring Damper

→ Element

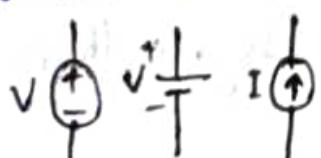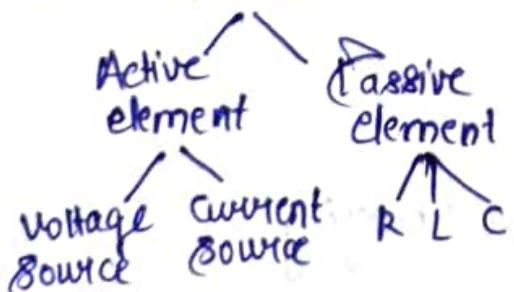


Voltage Source

↳ Terminal voltage remains constant.

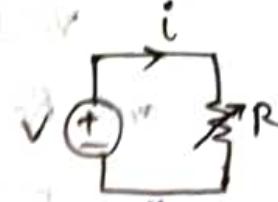
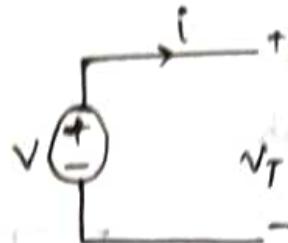
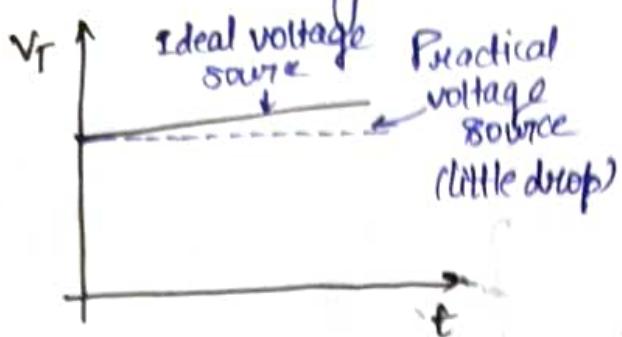


V : constant
 i : changes

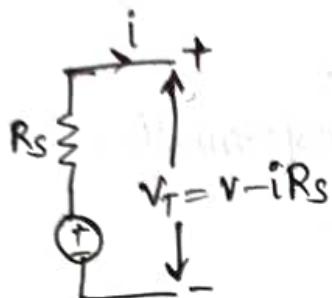


R_s : Internal resistance
(of source)
↳ $= 0$ (ideally)


Current Source

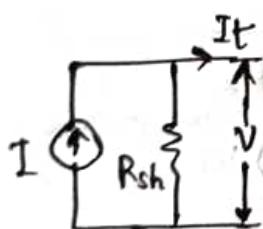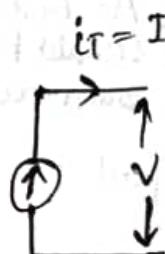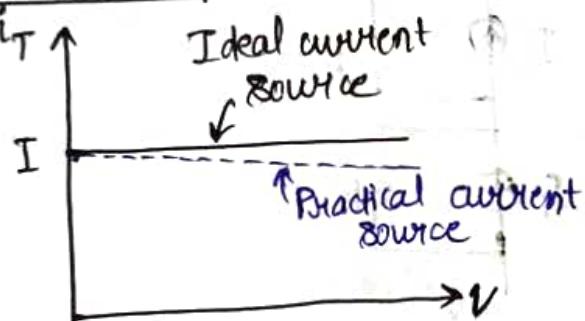

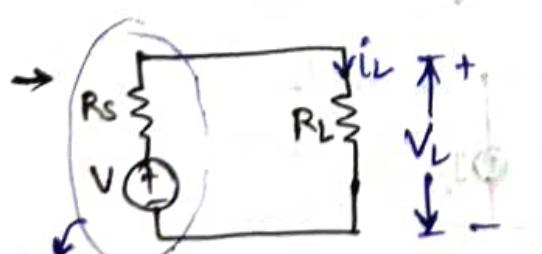$I_T = I - \frac{V}{R_{sh}}$, R_{sh} : internal resistance of the current source
↳ ∞ (ideally)


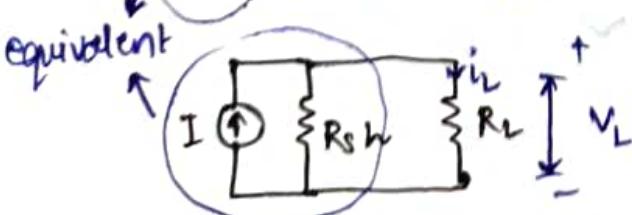
$$i_L = \frac{V}{R_s + R_L}, \quad V_L = \frac{V}{(R_s + R_L)} R_L = i_L R_L$$





$$i_L = \frac{I R_{sh}}{R_{sh} + R_L}, \quad V_L = i_L R_L = \frac{I R_{sh} \cdot R_L}{(R_s + R_L)}$$







→ The voltage source is equivalent to the given current source if

$$V = IR_{sh}$$


$$\text{and } R_s = R_{sh}$$

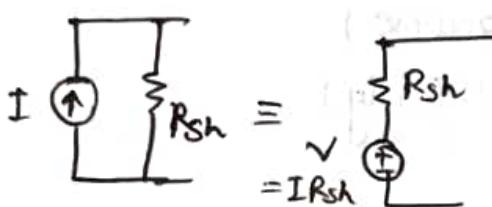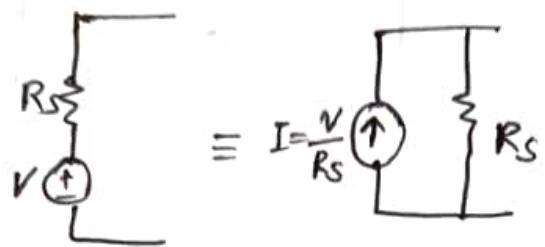

Source transformations

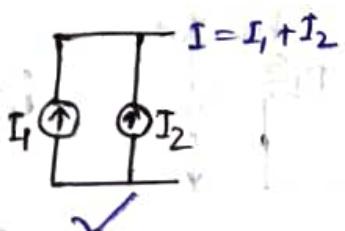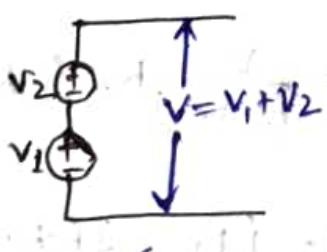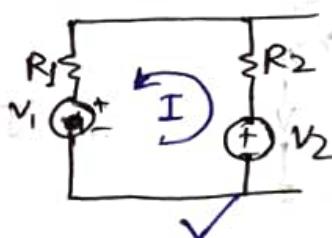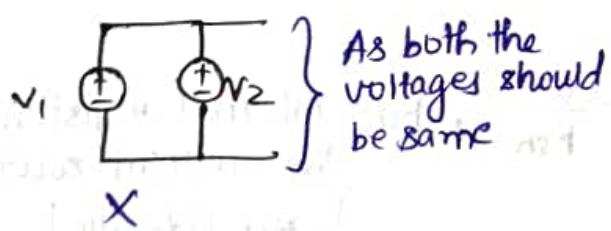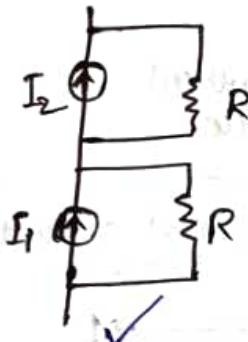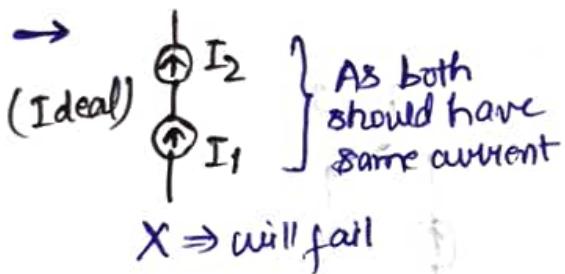


→ Turning on/off sources:

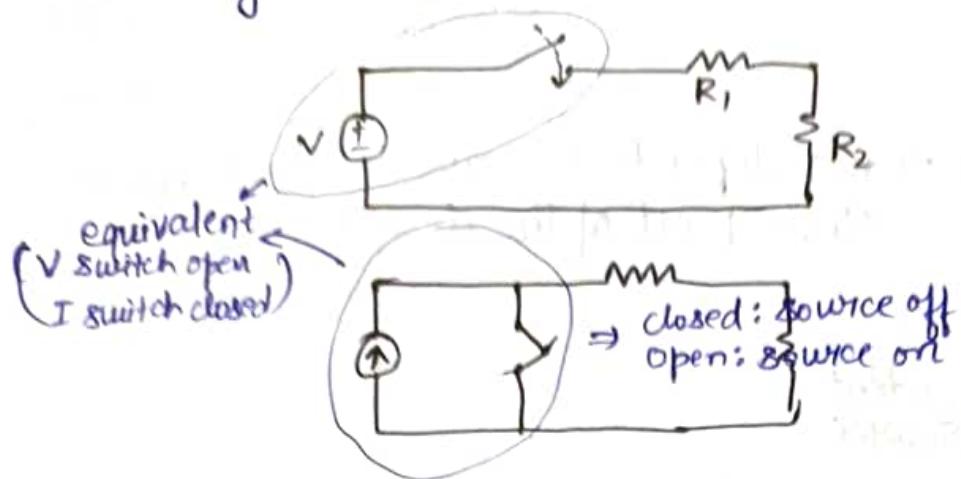


21-03-2023


→

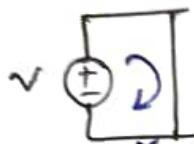

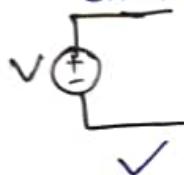↳ voltage source
shouldn't be
short-circuited



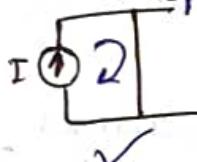↳ current source
shouldn't be
open-circuited



→



Source is
delivering power

$$P = V \times I$$

$$\Rightarrow \text{Power is +ve}$$




Source is
absorbing power


$$P = V \times (-I) = -VI$$

$$\Rightarrow \text{Power is -ve}$$

→

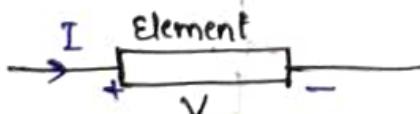


Element is absorbing power
-ve power

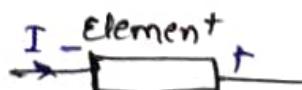


Delivering power
+ve power

→ Regenerative breaking: Load supplies power to the source to stop the vehicle.

→

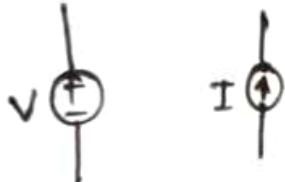


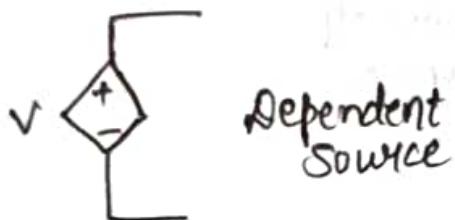Independent sources → not depends on current/voltages in other part of the circuit.




Dependent
Source

voltage Controlled Voltage Source (VCVS)

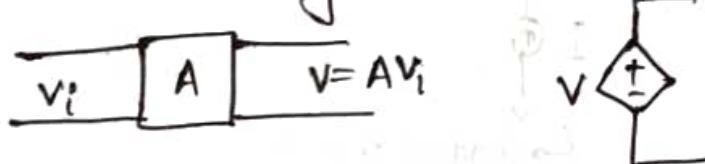

Current Controlled Voltage Source (CCVS)

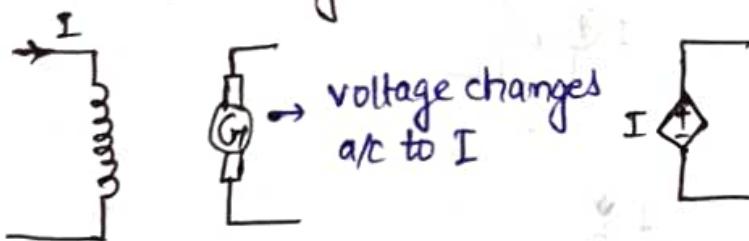


voltage Controlled Current Source (VCVS):

current controlled Current Source (CCCS):



AC CIRCUITS


Time Varying Signal

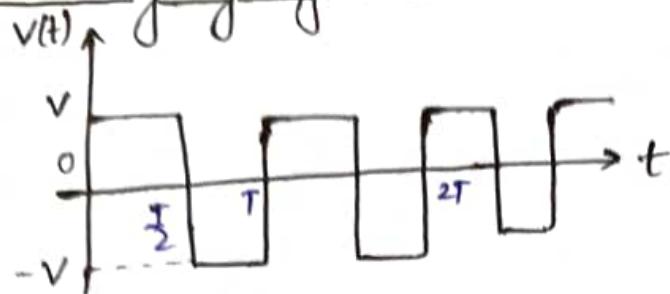


- Rectangular waveform
- Periodic waveforms

Periodic Signal

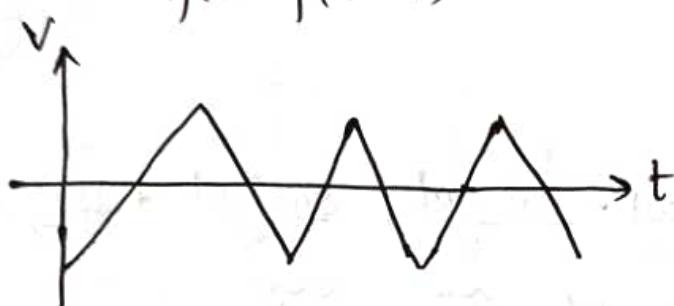$f(t)$ is a periodic function with period 'T' if
 $f(t) = f(t+T)$



- Triangular waveform

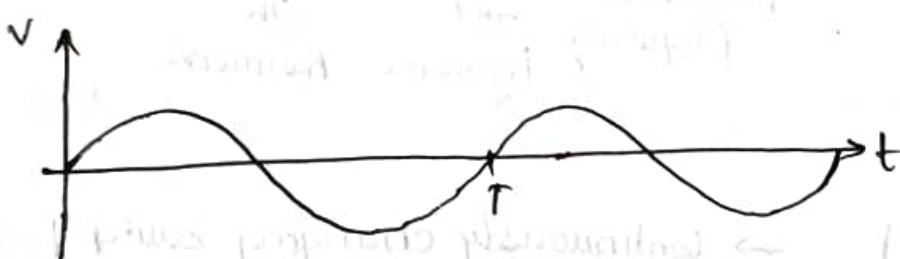



- Sinusoidal

frequency $= \frac{1}{T} \rightarrow$ no. of cycles per second

waveform: plot of magnitude vs. time

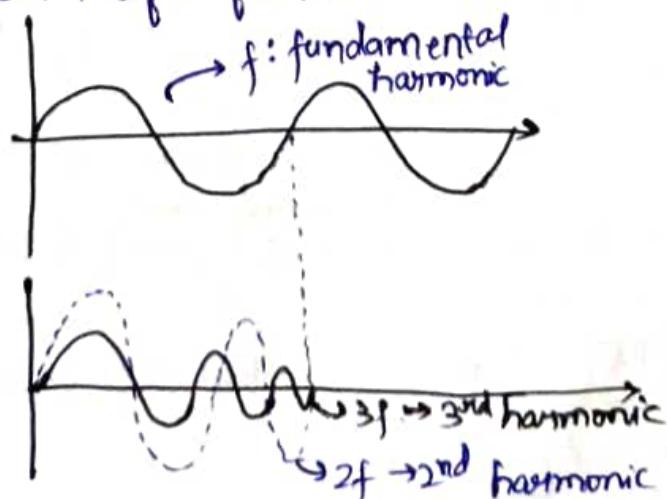Fourier Series: Any periodic waveform can be represented as the sum of infinite



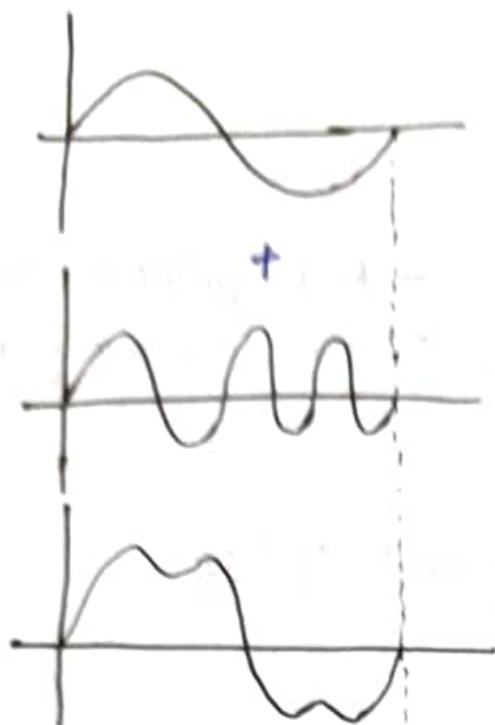


→ Resultant waveform

For square waveform:


$$v(t) = \frac{4V}{\pi} \left[\underbrace{\sin \omega t}_{\text{fundamental frequency}} + \underbrace{\frac{\sin 3\omega t}{3}}_{\text{3rd harmonic}} + \underbrace{\frac{\sin 5\omega t}{5}}_{\text{5th harmonic}} + \underbrace{\frac{\sin 7\omega t}{7}}_{\text{7th harmonic}} + \dots \right]$$

→ Inverter:

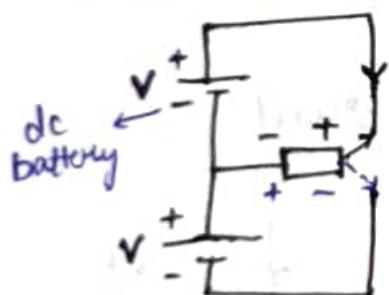


→ Continuously changing switch position will generate rectangular waveform/pulses

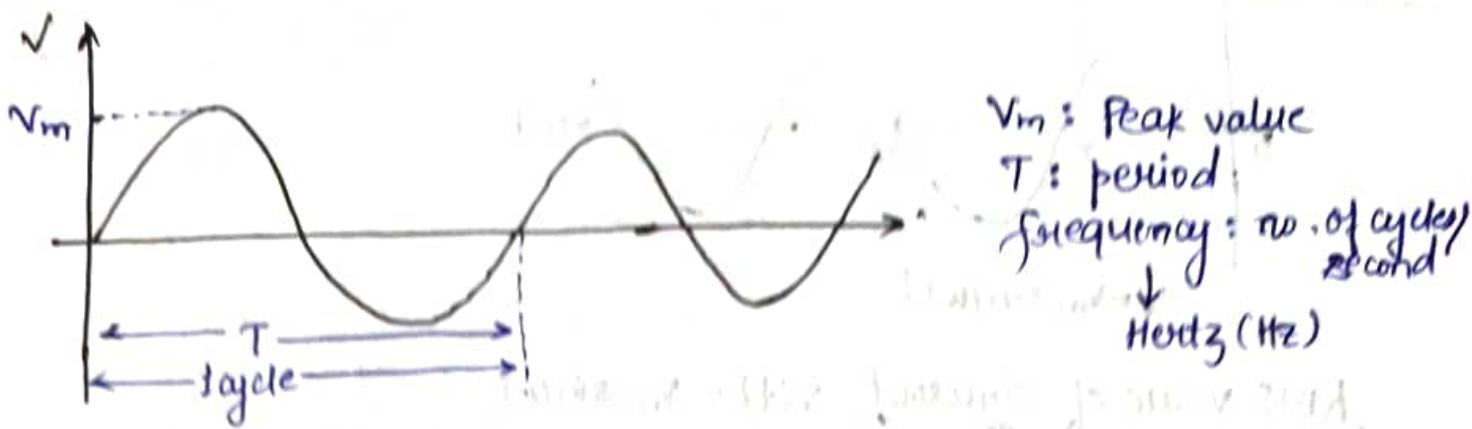Doing this 50 times a second will generate a 50 Hz AC current across the element.



Angular frequency, $\omega = 2\pi f \leftrightarrow \text{rad/sec.}$

$$= \frac{2\pi}{T}$$

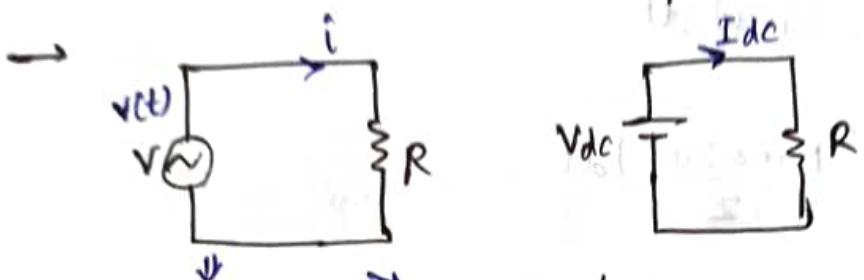

$$i = \frac{v(t)}{R}$$



If both R produce the same power/heat, effective value of i must be I_{dc} .

$$\text{For dc: } P = I_{dc}^2 R$$

If v and i are instantaneous values of voltages and current (in the ac),

$$\text{instantaneous power, } P = v \times i = i^2 R$$


$$\text{average power, } P_{av} = \frac{1}{T} \int_0^T i^2 R dt$$

$$\therefore I_{dc}^2 R = \frac{1}{T} \int_0^T i^2(t) R dt$$

$$\Rightarrow I_{dc}^2 = \frac{1}{T} \int_0^T i^2(t) dt$$

$$\Rightarrow I_{dc} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \rightarrow \text{Root Mean Square value (RMS)}$$
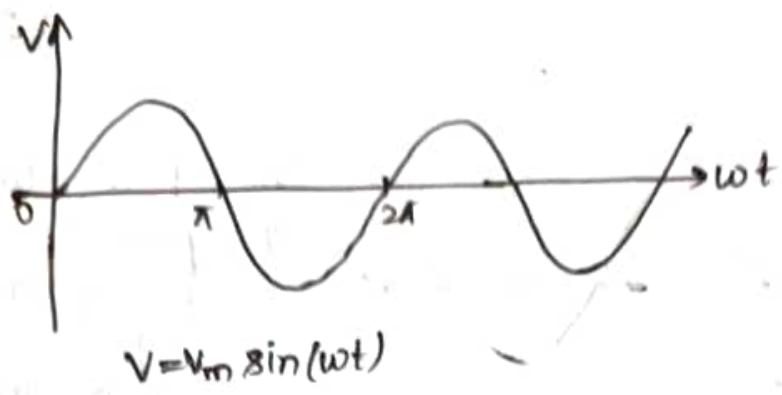
$$\rightarrow \text{RMS value of } f(t) \text{ with period } T: \sqrt{\frac{1}{T} \int_0^T f(t)^2 dt}$$




RMS value of sinusoid $v(t) = V_m \sin \omega t$:

$$\begin{aligned}
 V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T V_m^2 \sin^2 \omega t dt} \\
 &= \sqrt{\frac{V_m^2}{T} \int_0^T \frac{(1 - \cos 2\omega t)}{2} dt} \\
 &= \sqrt{\frac{V_m^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T} \\
 &= \sqrt{\frac{V_m^2}{2T} \left[T - \frac{\sin 2\frac{2\pi}{T} \cdot T}{2\omega} \right]} \quad (\because \omega = \frac{2\pi}{T}) \\
 &= \sqrt{\frac{V_m^2}{2}}
 \end{aligned}$$

$\therefore V_{\text{RMS}} = \frac{V_m}{\sqrt{2}} = \frac{\text{peak value}}{\sqrt{2}}$

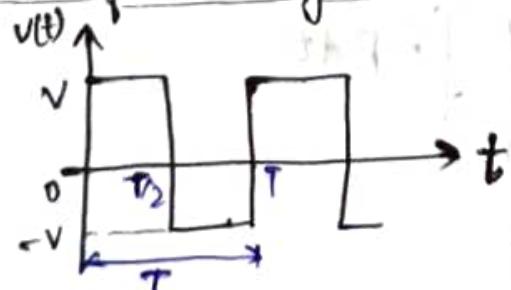→ RMS value of rectangular voltage waveform:




$$v(t) = \begin{cases} V, & \text{for } 0 < t \leq T_2 \\ -V, & \text{for } T_2 < t \leq T \end{cases}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} V^2 dt + \int_{T/2}^T (-V)^2 dt \right]} \\ = \sqrt{\frac{1}{T} \left[(V^2 t) \Big|_0^{T/2} + (V^2 t) \Big|_{T/2}^T \right]} = \sqrt{\frac{V^2}{T} \left[\frac{T}{2} + T - \frac{T}{2} \right]} \\ = \sqrt{\frac{V^2}{2}}$$

$$\therefore \boxed{V_{\text{rms}} = V}$$

→ Half-wave symmetry:


$$f(t) = -f(t - T/2)$$

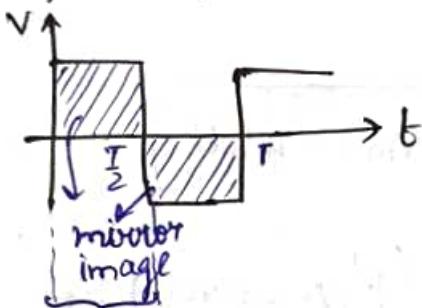



$$2 \times \overbrace{\text{RMS}}^{\text{(for } T/2\text{)}} = \overbrace{\text{RMS}}^{\text{(for } T\text{)}}$$

$$\rightarrow V = V_m \sin \omega t$$

→ Quarter wave symmetry:

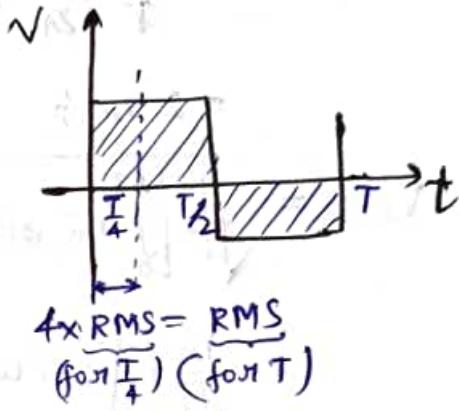


M1:

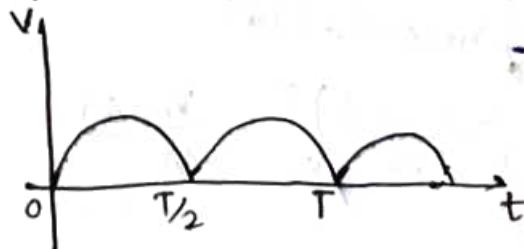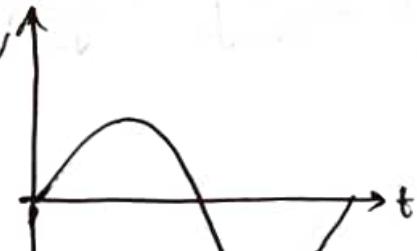

→ Full Wave Rectifier

$$\rightarrow \text{RMS value: } \frac{V_m}{\sqrt{2}}$$
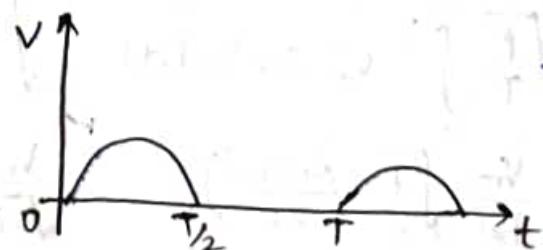
$$\rightarrow \text{Average value: } 2 \frac{V_m}{\pi}$$



→ Half Wave Rectifier

$$\rightarrow \text{RMS value: } \frac{V_m}{2}$$

$$\rightarrow \text{Average value: } \frac{V_m}{\pi}$$

Full Wave Rectifier:

$$\begin{aligned}
 V_{av} &= \frac{1}{T} \int_0^T f(t) dt \\
 &= \frac{1}{T} \left[\int_0^T V_m \sin(\omega t) dt + \int_{T/2}^T V_m (-\sin \omega t) dt \right] \\
 &= \frac{V_m}{T} \left[\left(-\frac{\cos \omega t}{\omega} \right)_0^{T/2} + \left(\frac{\cos \omega t}{\omega} \right)_{T/2}^T \right] \\
 &= \frac{V_m}{T} \cdot \frac{T}{2\pi} ((1+1)+(1+1)) \\
 &= 2 V_m / \pi
 \end{aligned}$$



$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{T} \left[\int_0^T V_m^2 \sin^2 \omega t dt + \int_{T/2}^T V_m^2 \sin^2 \omega t dt \right]} \\
 &= \frac{V_m}{\sqrt{T}} \left(\int_0^T \sin^2 \omega t dt \right)^{1/2} = \frac{V_m}{\sqrt{T}} \left(\int_0^T \left(\frac{1-\cos 2\omega t}{2} \right) dt \right)^{1/2} \\
 &= \frac{V_m}{\sqrt{2T}} \sqrt{\left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T} = \frac{V_m}{\sqrt{2T}} \sqrt{(T-0)} \\
 &= \frac{V_m}{\sqrt{2}}
 \end{aligned}$$

Half Wave Rectifier:

$$\begin{aligned}
 V_{av} &= \frac{1}{T} \int_0^{T/2} V_m \sin(\omega t) dt \\
 &= \frac{V_m}{T} \left(-\frac{\cos \omega t}{\omega} \right)_0^{T/2} = \frac{V_m}{2\pi} (1/2) \\
 &= \frac{V_m}{\pi}
 \end{aligned}$$

$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \omega t dt} = \sqrt{\frac{V_m^2}{T} \int_0^{T/2} \sin^2 \omega t dt} \\
 &= \frac{V_m}{\sqrt{2T}} \sqrt{\left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{T/2}} = \frac{V_m}{\sqrt{2T}} \sqrt{\frac{T}{2} - 0} \\
 &= \frac{V_m}{2}
 \end{aligned}$$

Q) Find RMS value:

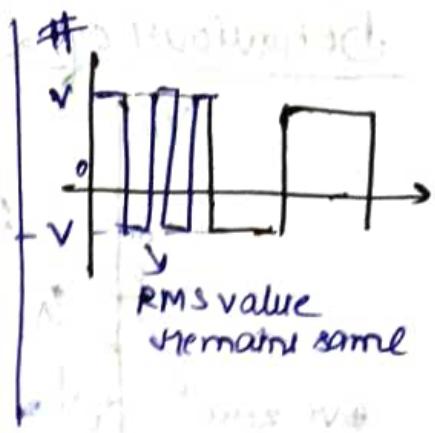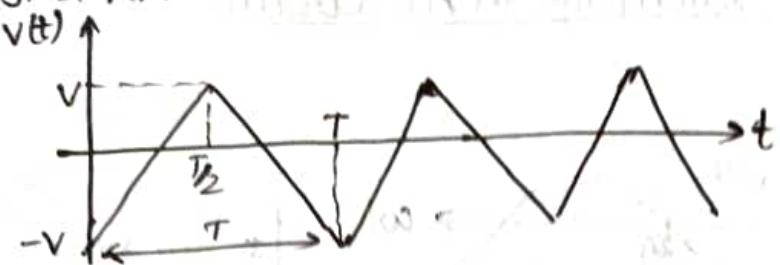

$$\text{Soln: } v(t) = \begin{cases} \left(\frac{4v}{T}\right)t - v, & 0 < t \leq T/2 \\ -\left(\frac{4v}{T}\right)t + 3v, & T/2 < t \leq T \end{cases}$$


$$\begin{aligned} V_{\text{avg.}} &= \frac{1}{T} \left[\int_0^{T/2} \left(\left(\frac{4v}{T}\right)t - v \right) dt + \int_{T/2}^T \left(-\left(\frac{4v}{T}\right)t + 3v \right) dt \right] \\ &= \frac{1}{T} \left[\left(\frac{4v}{T} \cdot \frac{t^2}{2} - vt \right) \Big|_0^{T/2} + \left(-\frac{4v}{T} \cdot \frac{t^2}{2} + 3vt \right) \Big|_{T/2}^T \right] \\ &= \frac{1}{T} \left[\left(\frac{4vT}{2} - \frac{vT}{2} \right) + \left(-2vT + \frac{vT}{2} + 3vT - \frac{3vT}{2} \right) \right] \\ &= v - 0v \end{aligned}$$

$$\begin{aligned} \therefore V_{\text{avg}} &= 0 \\ V_{\text{rms}}^2 &= \frac{1}{T} \int_0^{T/2} \left(\frac{4v}{T}t - v \right)^2 dt + \int_{T/2}^T \left(-\frac{4v}{T}t + 3v \right)^2 dt \\ &= \frac{1}{T} \int_0^{T/2} \left(\frac{16v^2}{T^2}t^2 + v^2 - \frac{8v^2t}{T} \right) dt + \frac{1}{T} \int_{T/2}^T \left(\frac{16v^2}{T^2}t^2 + 9v^2 - \frac{24v^2t}{T} \right) dt \\ &= \frac{1}{T} \left(\frac{16v^2}{T^2} \cdot \frac{t^3}{3} + v^2t - \frac{8v^2t^2}{T} \right) \Big|_0^{T/2} + \frac{1}{T} \left(\frac{16v^2}{T^2} \cdot \frac{t^3}{3} + 9v^2t - \frac{24v^2t^2}{T} \right) \Big|_{T/2}^T \\ &= \left(\frac{2v^2}{3} + \frac{v^2}{2} - v^2 \right) + \left(\frac{16}{3}v^2 + 9v^2 - 12v^2 \right) - \left(\frac{2v^2}{3} + \frac{9}{2}v^2 - \frac{3}{2}v^2 \right) \end{aligned}$$

$$= \left(\frac{16}{3} - 4 - 1 \right) v^2 = \left(\frac{16}{3} - 5 \right) v^2 = \frac{v^2}{3}$$

$$\Rightarrow V_{\text{rms}} = \frac{v}{\sqrt{3}}$$

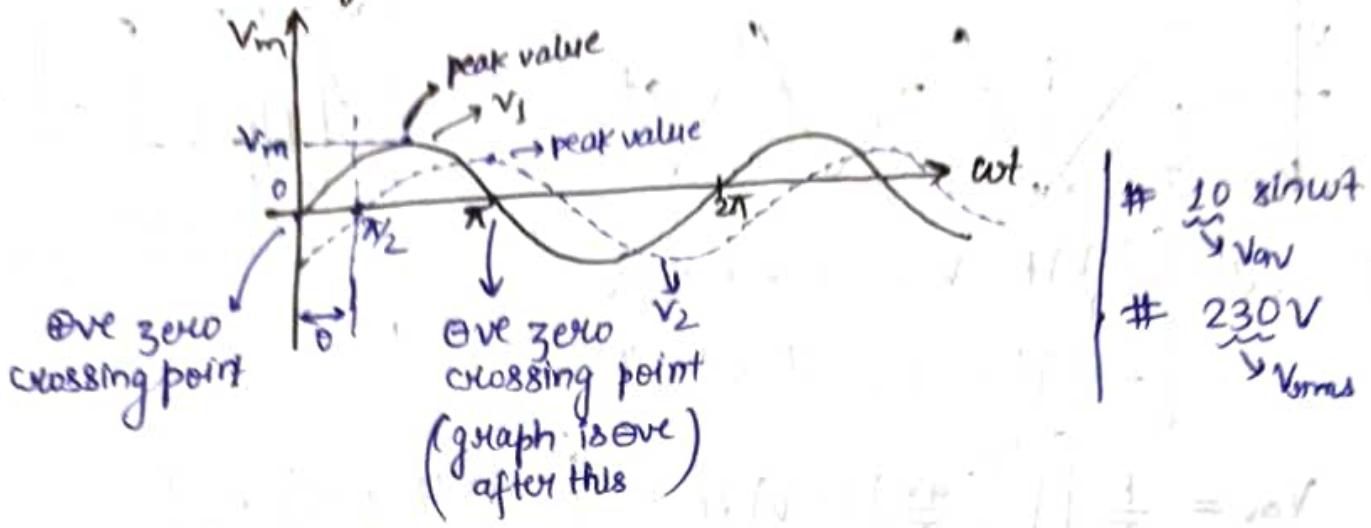Behaviour of different Elements in AC circuit



i) phase

ii) phase difference


→ There is a phase difference b/w the two waveforms V_1 and V_2 .
 (peak, ave zero crossing point, etc. of the two waveforms are happening at the different instant; similar points are not occurring simultaneously.)

→ V_2 is lagging behind V_1 ,
 or V_1 is leading ahead of V_2 .

$$\left. \begin{array}{l} \text{If } V_1 = V_{m1} \sin \omega t \\ V_2 = V_{m2} \sin(\omega t - \theta) \end{array} \right\} \begin{array}{l} \text{frequencies need to be same} \\ \text{for the two waveforms} \end{array}$$


$$\left. \begin{array}{l} \text{If } V_2 = V_{m2} \sin \omega t \\ V_1 = V_{m1} \sin(\omega t + \theta) \end{array} \right.$$

→

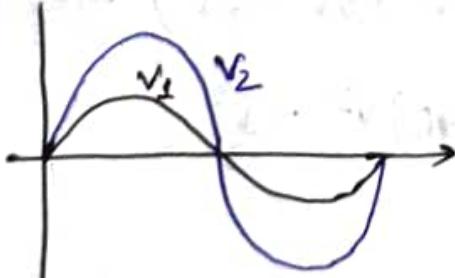

V_1 and V_2 are in phase.


Resistor (R):

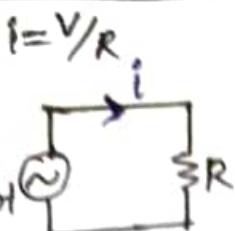

$$i = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$$



$$= \left(\frac{V_m}{R}\right) \sin \omega t$$

$$= I_m \sin \omega t$$

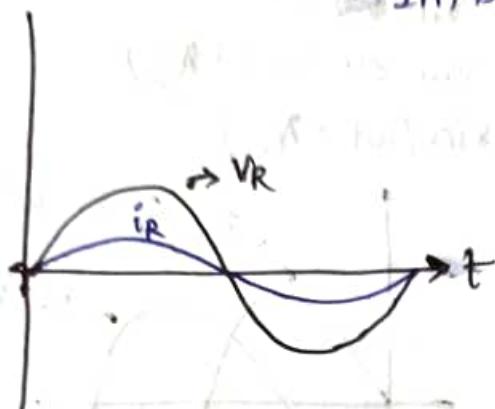


In a resistor, voltage and current are in phase.

Inductor (L):

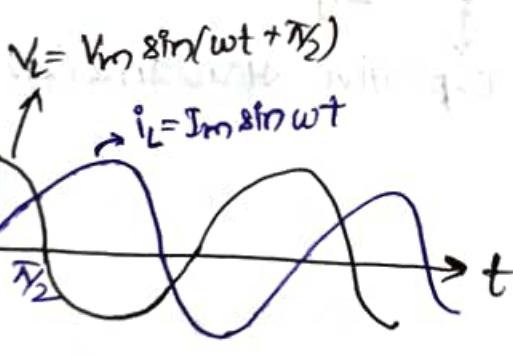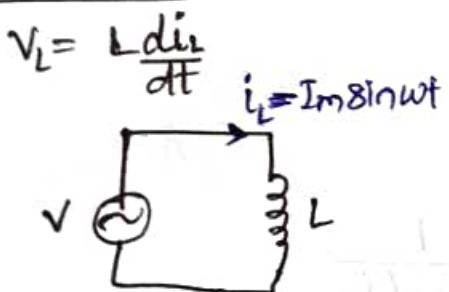

$$V_m = \omega L I_m$$
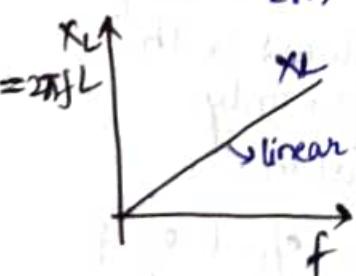
$$\frac{V_m}{I_m} = \omega L = 2\pi f L$$



- same dimension as R
- resists the flow of current like R
- but doesn't dissipate power

Inductive Resistance: $X_L = \omega L = 2\pi f L$

↳ frequency dependent opposition to the flow of current (unlike R)


$$v_L = L \frac{di_L}{dt}$$

$$= L \frac{d}{dt} I_m \sin \omega t$$

$$= \omega L I_m \cos \omega t$$

$$= \omega L I_m \sin(\omega t + \pi/2)$$


$$= V_m \sin(\omega t + \pi/2)$$

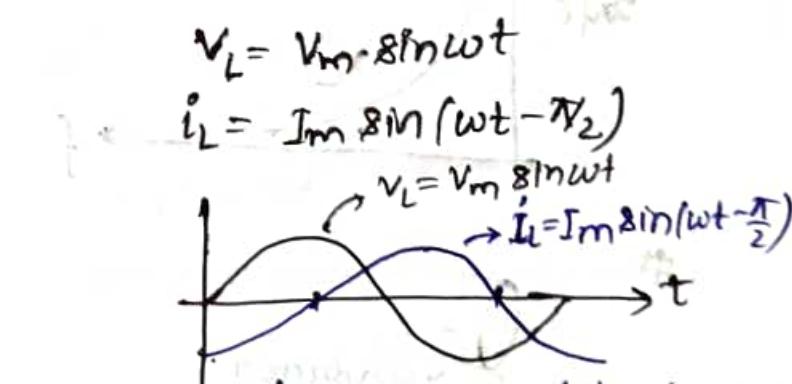

→ current lags behind voltage
or voltage leads ahead of current by an angle of $\pi/2$

Capacitor (C):

$$i = C \frac{dV}{dt}$$

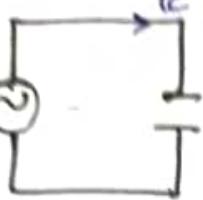

$$V = V_m \sin(\omega t)$$

$$i_c = C \frac{dV}{dt}$$


$$= C \frac{d}{dt} V_m \sin(\omega t)$$

$$= \omega C V_m \cos(\omega t)$$

$$= \omega C V_m \sin(\omega t + \pi/2)$$


$$= I_m \sin(\omega t + \pi/2)$$

$$i_c = I_m \sin(\omega t + \pi/2)$$

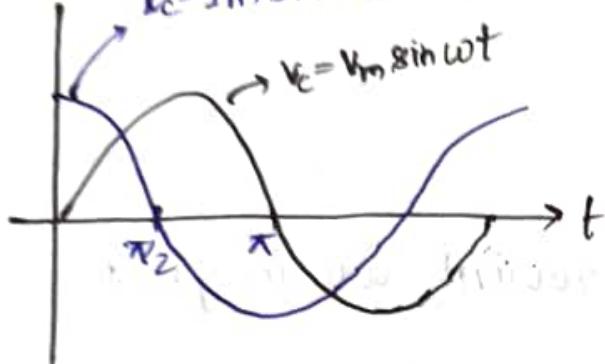

$$i_c = I_m \sin(\omega t)$$

$$V_c = V_m \sin(\omega t - \pi/2)$$

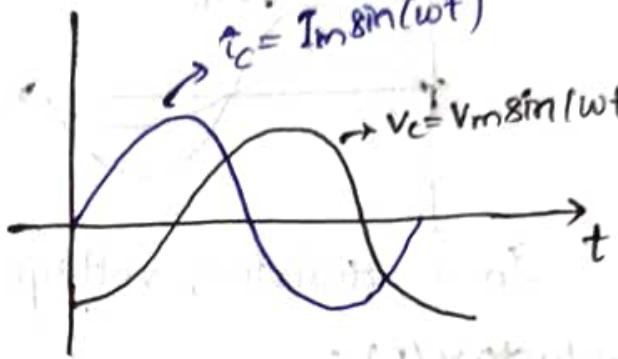


→ voltage lags behind current.
OR
→ current leads voltage by $\pi/2$.

$$I_m = \omega C V_m$$


$$\frac{V_m}{I_m} = \frac{1}{\omega C} = \frac{1}{2\pi f C} \Rightarrow$$

$$X_C = \frac{1}{2\pi f C}$$


↓ capacitive reactance (Ω)

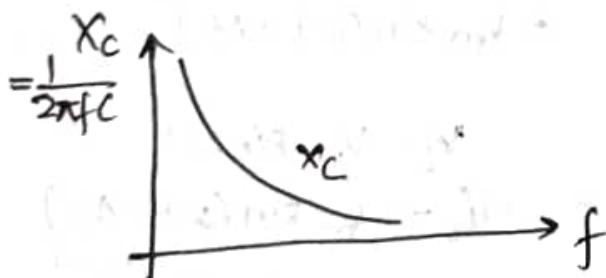

#

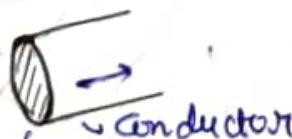

dc flows over the entire conductor

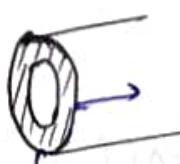

ac only flows on the surface


↳ $f \uparrow \Rightarrow$ ac flows on the surface only.

↳ skin resistance

negligible effect of f on resistance


Reactance

- Inductive Reactance: $X_L = 2\pi f L \rightarrow f=0 \rightarrow$ short circuit | $f=0 \rightarrow DC$
- Capacitive Reactance: $X_C = \frac{1}{2\pi f C} \rightarrow f=0 \rightarrow$ infinite resistance

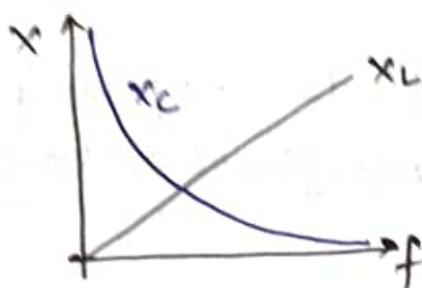


$$\left| \begin{array}{l} \omega = \text{rad/sec} \\ = \frac{\text{Angle}}{\text{time}} \end{array} \right.$$

$\omega = 2\pi f$ or $\omega = 2\pi / T$

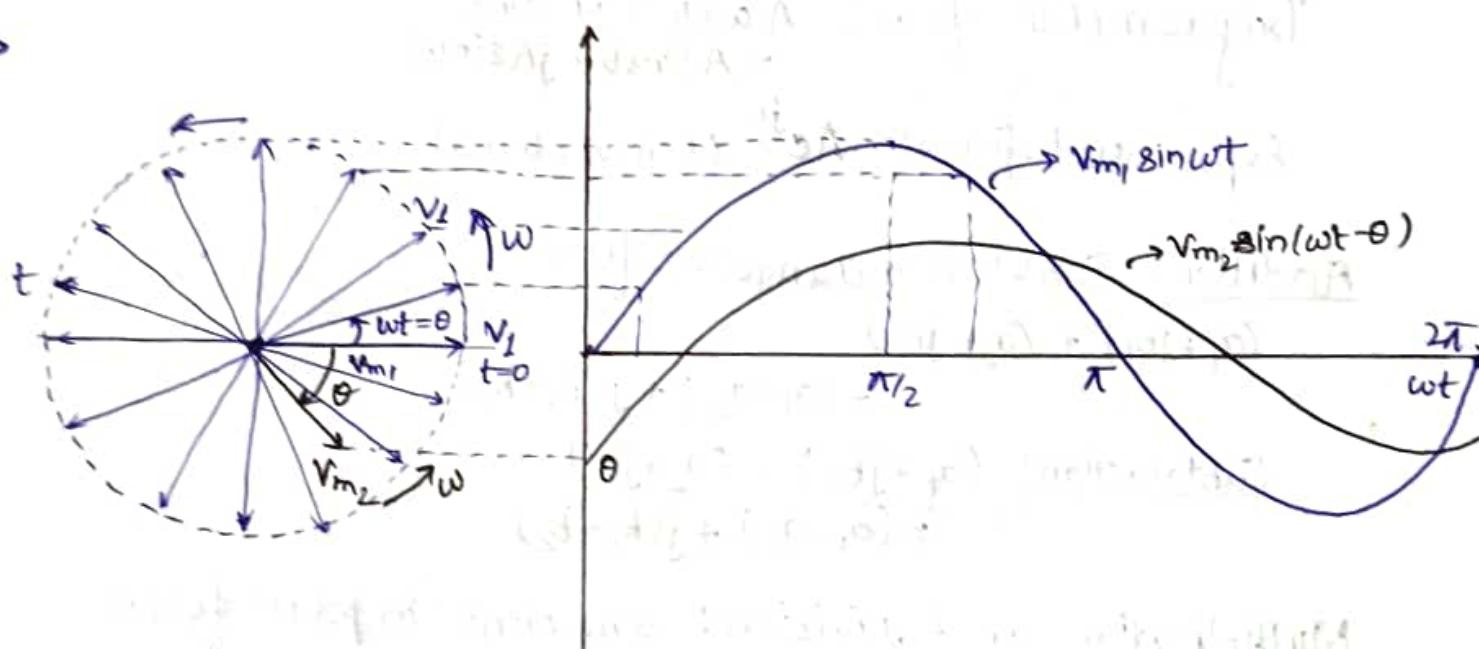Rotating Vector: Phasor

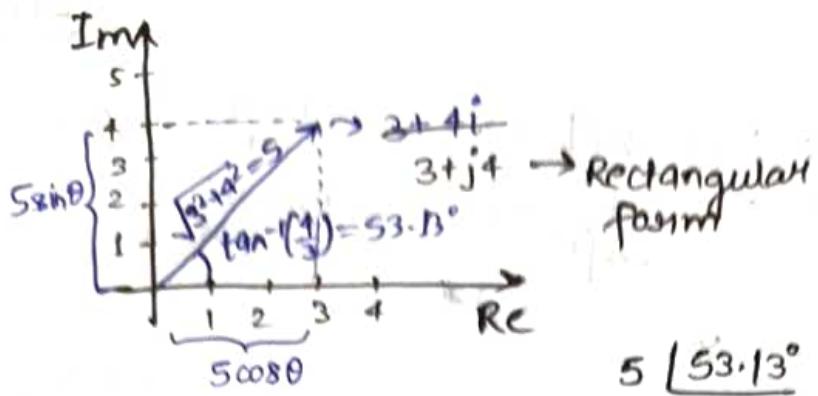- Represents only sinusoids
- Rotated
- Constant angular velocity
- can be represented using complex no.



$l \rightarrow$ reserved for current

$5 [53.13^\circ] \rightarrow$ polar form

$5cos\theta + j5sin\theta \rightarrow$ trigonometric form

Rectangular form: $a + jb$

Polar form: $A \angle \theta$

Trigonometric form: $A \cos\theta + jA \sin\theta$
 $= A(\cos\theta + j\sin\theta)$

Exponential form: $Ae^{j\theta}$ (θ in radians).

Addition: Easier in rectangular form


$$(a_1 + jb_1) + (a_2 + jb_2) \\ = (a_1 + a_2) + j(b_1 + b_2)$$

$$\begin{aligned} \text{Subtraction: } & (a_1 + jb_1) - (a_2 + jb_2) \\ & = (a_1 - a_2) + j(b_1 - b_2) \end{aligned}$$


Multiplication and Division: Convenient in polar form

$$A_1 \angle \theta_1 \times A_2 \angle \theta_2 = A_1 A_2 \angle (\theta_1 + \theta_2)$$
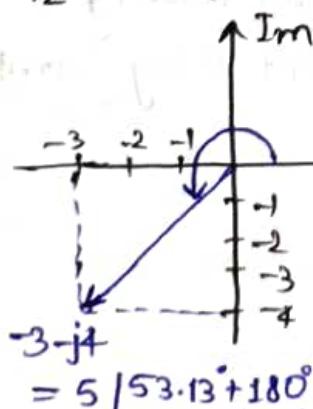
$$\frac{A_1 \angle \theta_1}{A_2 \angle \theta_2} = \left(\frac{A_1}{A_2} \right) \angle (\theta_1 - \theta_2)$$



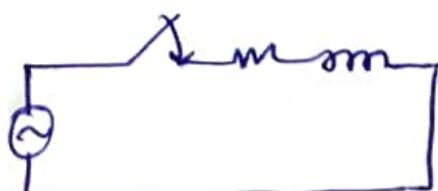Sinusoids
 \downarrow
 Represented using
 phasor, not vector



↳ After some time, sinusoidal steady state is achieved.

Eg: $3 \rightarrow 3+j0 \rightarrow 3 \angle 0^\circ$

$j3 \rightarrow 0+j3 \rightarrow 3 \angle 90^\circ$

$j = \sqrt{-1}$

$j \times j3 = -3 \rightarrow -3+j0 \rightarrow 3 \angle 180^\circ$

$\rightarrow a+jb \rightarrow A \angle \theta$

$\Rightarrow A = \sqrt{a^2+b^2}$

and $\theta = \tan^{-1}\left(\frac{b}{a}\right)$

Eg:

$-3 \rightarrow 3 \angle 180^\circ$


$-j3 \rightarrow 3 \angle 270^\circ$

$3 \rightarrow 3+j0 \rightarrow 3 \angle 0^\circ$


$j3 \rightarrow 0+j3 \rightarrow 3 \angle 90^\circ$

$-3 \rightarrow -3+j0 \rightarrow 3 \angle 180^\circ$

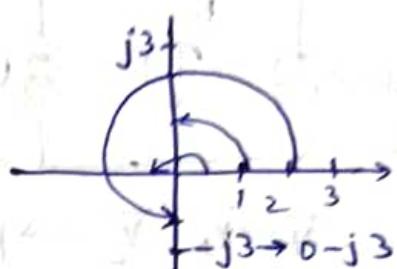$-3j \rightarrow 0-j3 \rightarrow 3 \angle -90^\circ$



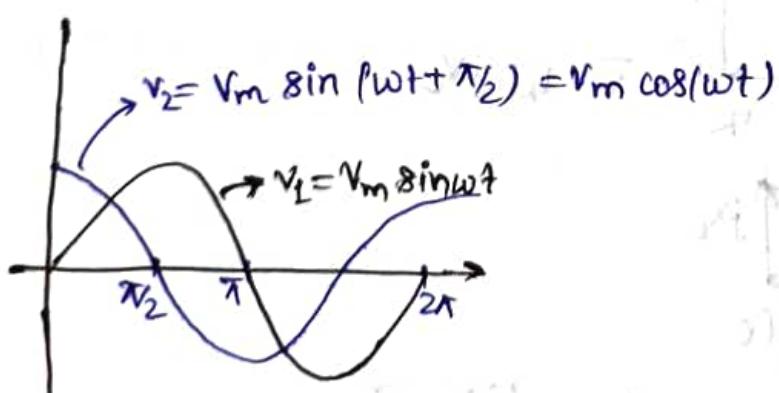SINUSOIDAL STEADY STATE ANALYSIS OF AC CIRCUIT




$$V_1 = V_m \sin \omega t$$

$$V_2 = V_m \cos \omega t = jV_1 = jV_m \sin \omega t$$

$$\frac{dV_1}{dt} = \frac{d}{dt} V_m \sin \omega t = \omega V_m \cos \omega t = \omega V_2 \\ = j\omega V_1$$

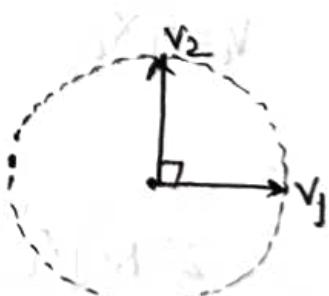
$$\therefore \boxed{\frac{dV_1}{dt} = j\omega V_1}$$



$$\rightarrow V_2 = jV_1 \Rightarrow V_1 = \frac{V_2}{j}$$

$$\int V_2 dt = \int V_m \cos \omega t dt = \frac{V_m}{\omega} \sin \omega t = \frac{V_1}{\omega} = \frac{V_2}{j\omega}$$
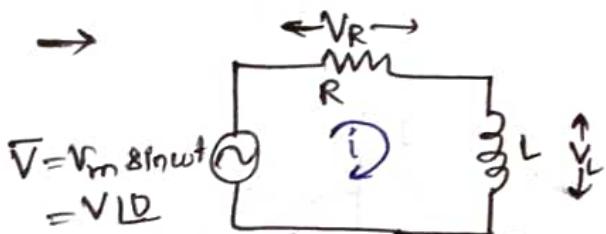
$$\therefore \boxed{\int V_2 dt = \frac{V_2}{j\omega}}$$



$$V = V_R + V_L \rightarrow \text{phases}$$

$$V = iR + L \frac{di}{dt}$$

Using sinusoidal steady state,

$$V = iR + j\omega L i = i(R + j\omega L)$$


$$V = iZ, Z \rightarrow \text{Impedance}$$

$$\omega L = 2\pi f L = X_L$$

↓
inductive reactance

$$V_R = iR$$

$$V_L = i j X_L$$

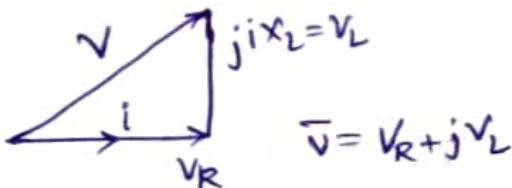

$$\bar{V} = V_R + jV_L$$


$$Z = R + jX_L$$

Impedance triangle

$$\text{Magnitude of Impedance, } |Z| = \sqrt{R^2 + X_L^2}$$

$$\text{Angle of impedance, } \theta = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$Z = R + jX_L = |Z| \angle \theta$$

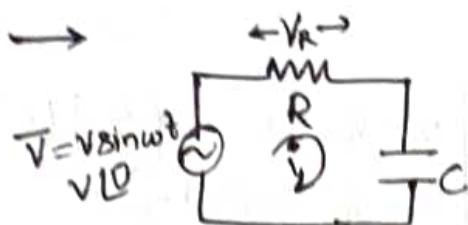

$$V = Ri + \frac{1}{C} \int i dt$$


Using sinusoidal steady state,

$$V = Ri + \frac{i}{j\omega C}$$

$$= Ri - jX_C i$$

$$= i(R - jX_C)$$


$$= iZ$$

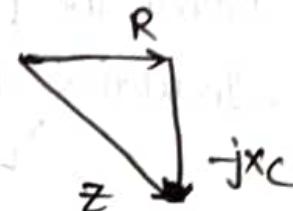

$$Z = R - jX_C$$

$$|Z| = \sqrt{R^2 + X_C^2}$$
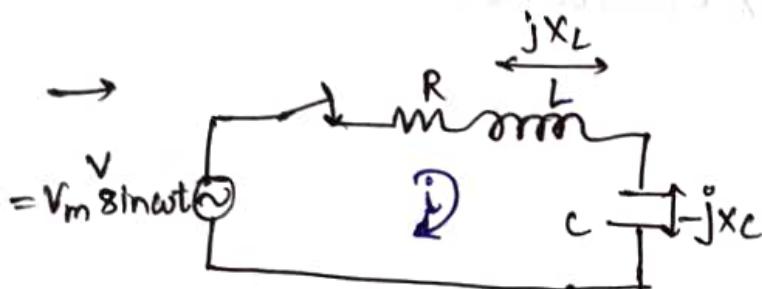
$$\angle Z = \theta = \tan^{-1} \left(-\frac{X_C}{R} \right)$$



Using KVL,

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Using sinusoidal steady state condition,


$$V = iR + j\omega L i + \frac{i}{j\omega C}$$

$$V = iR + jX_L i - jX_C i$$

$$= iR + ij(X_L - X_C)$$


$$\therefore V = i(R + jX)$$

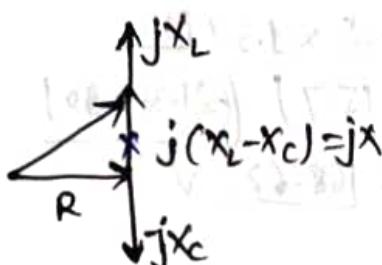
\rightarrow capacitor reactance opposes the inductive reactance.



At some time t,

$X_L = X_C \rightarrow$ at resonance

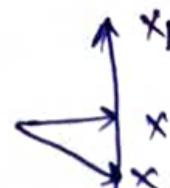

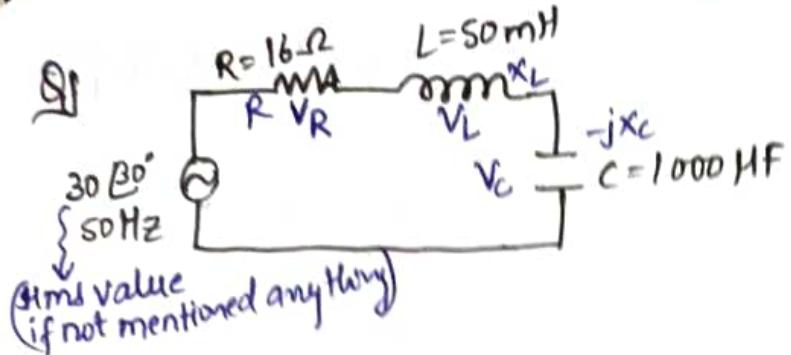

$$V_1 = V_m_1 \sin(\omega t - \left(\frac{V_m_1}{\sqrt{2}} \right) L \omega^\circ)$$

$$V_2 = V_m_2 \sin(\omega t - 60^\circ)$$

$$\left(\frac{V_m_2}{\sqrt{2}} \right) L \underline{-60^\circ}$$

① Determine the current 'i' in the circuit.


② Draw the phasor diagram representing i, V_R, V_L, V_C, V .

Sol: Inductive reactance,

$$X_L = 2\pi f L = 2\pi \times 50 \times 50 \times 10^{-3} \\ = 15.7\Omega$$

Capacitive reactance,
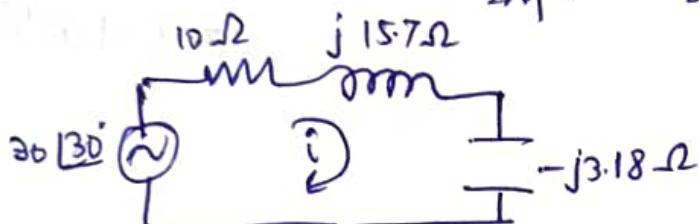
$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 1000 \times 10^{-9}} = 3.18\Omega$$



$$\text{Current, } i = \frac{V}{Z} = \frac{V}{R + jX_L - jX_C} = \frac{30 \angle 30^\circ}{10 + j15.7 - j3.18} \\ = \frac{30 \angle 30^\circ}{10 + j12.52} = \frac{30 \angle 30^\circ}{16.03 \angle 51.38^\circ} = 1.87 \angle -21.38^\circ \text{ A}$$

Voltage across R ,

$$V_R = iR = 1.80 \angle -21.38^\circ \times 10 \angle 0^\circ \\ = 18.7 \angle -21.38^\circ$$


$$10 + j12.52 \\ = \sqrt{10^2 + 12.52^2} \\ \tan^{-1}\left(\frac{12.52}{10}\right)$$

Voltage across the inductor,

$$V_L = i \times jX_L = 1.87 \angle -21.38^\circ \times j15.7 \\ = 1.87 \angle -21.38^\circ \times 1.57 \angle 90^\circ \\ = (1.87 \times 1.57) \angle (21.38 + 90)^\circ \\ = 29.36 \angle 68.62^\circ \text{ V}$$

Voltage across capacitor,
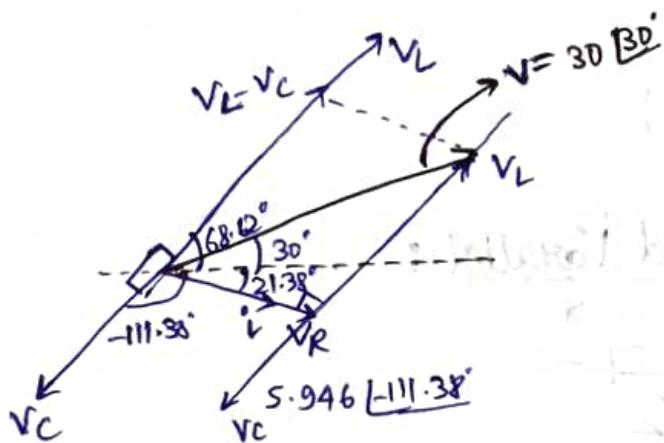
$$\begin{aligned} V_C &= i (-jX_C) = 1.87 \angle -21.38^\circ \times -j3.18 \\ &= 1.87 \angle 21.38^\circ \times 3.18 \angle -90^\circ \\ &= (1.87 \times 3.18) \angle -21.38 - 90^\circ \\ &= 5.946 \angle -111.38^\circ \text{ V} \end{aligned}$$



$$\begin{aligned} \bar{V}_R + \bar{V}_C + \bar{V}_L &= 18.7 \angle 21.38^\circ + 29.36 \angle 68.62^\circ + 5.946 \angle -111.38^\circ \\ &= 29.8 \angle 29.95^\circ \\ &\approx 30 \angle 30^\circ \end{aligned}$$



$$\frac{X_L}{X+X_L} = \frac{X_L}{(X+3)(X+4)} = \frac{1}{(X+3)(X+4)}$$

$$\frac{X_L}{X+X_L} = \frac{1}{X+4}$$


$$1 = \left| \frac{X_L}{X+4} \right|^2 \Rightarrow \frac{X_L^2}{X^2+16} = 1$$

$$1 = \frac{X_L^2}{X^2+16} \Rightarrow X_L^2 = X^2 + 16 \Rightarrow X_L = \sqrt{X^2 + 16}$$

$$\text{Impedance } Z = \frac{X_L}{X+4} = \frac{\sqrt{X^2 + 16}}{X+4} = 9$$

Impedance (Ω)

↳ complex

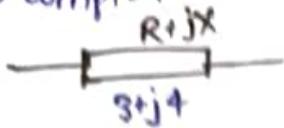


$$Z = R + jX$$


$$|Z| = \sqrt{R^2 + X^2}$$

$$\angle(Z) = \tan^{-1}\left(\frac{X}{R}\right)$$

$$R+jX = \sqrt{R^2+X^2} \quad \boxed{\tan^{-1}(X/R)}$$

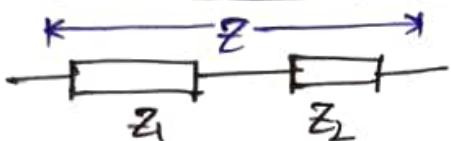→ Impedance in Series and Parallel:

$$Z_t = Z_1 + Z_2$$

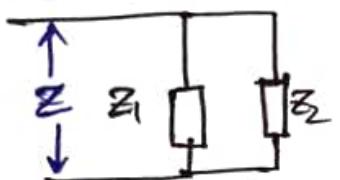

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\Rightarrow Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

~~$\rightarrow Z = R + jX$~~

$\frac{1}{R} \rightarrow$ Admittance (G)

$$\begin{aligned} \frac{1}{Z} &= \frac{1}{R+jX} = \frac{R-jX}{(R+jX)(R-jX)} = \frac{R-jX}{R^2+X^2} \\ &= \frac{R}{R^2+X^2} - \frac{jX}{R^2+X^2} \end{aligned}$$

$$\Rightarrow \boxed{\frac{1}{Z} = G - jB}$$

$$G = \frac{R}{R^2+X^2} \rightarrow \text{conductance}$$

$$B = \frac{X}{R^2+X^2} \rightarrow \text{susceptance}$$

POWER IN AC CIRCUITS

Instantaneous power = Inst. voltage × Inst. current

$$p = v \times i$$

Power in Resistor



$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R}$$

$$= \left(\frac{V_m}{R}\right) \sin \omega t$$

$$= I_m \sin \omega t$$

$$p = v \times i = V_m \sin \omega t \times I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$


$$\text{Average power, } P_{av.} = \frac{1}{T} \int_0^T p \, dt$$

$$= \frac{1}{T} \int_0^T \left(\frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2} \right) dt$$


$$= \frac{1}{T} \int_0^T \left(\frac{V_m I_m}{2} \right) dt \rightarrow \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos 2\omega t \, dt$$

$$= \frac{V_m I_m}{2} = \frac{V_m I_m}{\sqrt{2} \sqrt{2}} \Rightarrow = V_{rms} I_{rms}$$
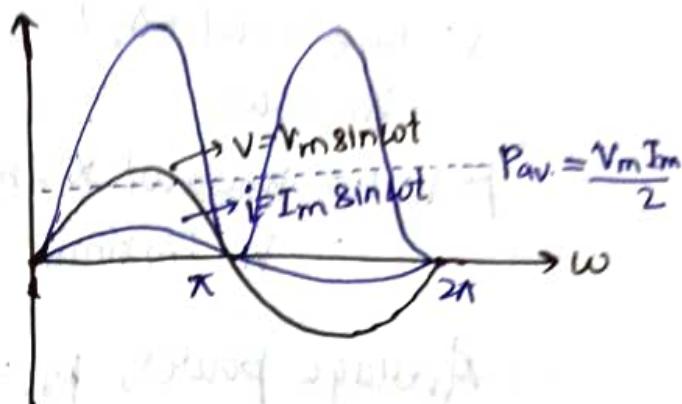
$$\therefore P_{av} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$



Power in Inductor

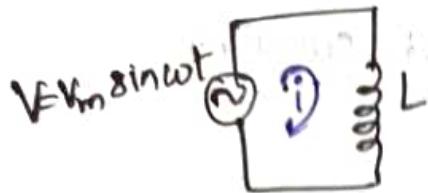

$$i = I_m \sin \omega t$$


$$V = V_m \sin(\omega t + \pi/2)$$

$$= V_m \cos \omega t$$

$$P = V \times i = V_m \cos \omega t \times I_m \sin \omega t$$


$$= V_m I_m \sin \omega t \cos \omega t = \frac{V_m I_m}{2} \sin 2\omega t$$
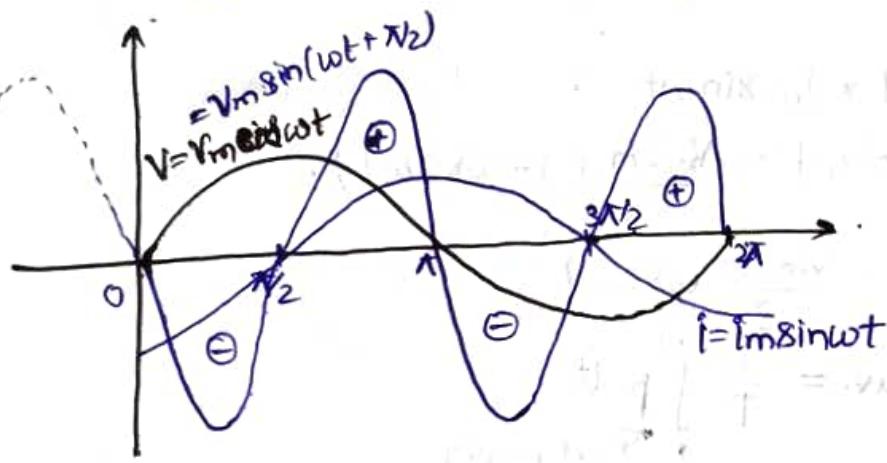
$$\text{Average power, } P_{av} = \frac{1}{T} \int_0^T P dt = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \sin 2\omega t dt = 0$$



- ⊖ P \Rightarrow Inductor is releasing power
- ⊕ P \Rightarrow Inductor is absorbing power
↓
Doesn't consume power

Power in Capacitor

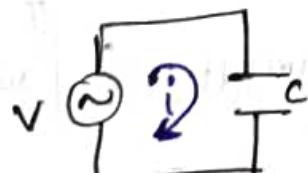

$$V = V_m \sin \omega t$$


$$i = I_m \sin(\omega t + \pi/2)$$

$$= I_m \cos \omega t$$

$$P = V \times i = V_m \sin \omega t \times I_m \cos \omega t$$



$$= V_m I_m \sin \omega t \cos \omega t = \frac{V_m I_m}{2} \sin 2\omega t$$
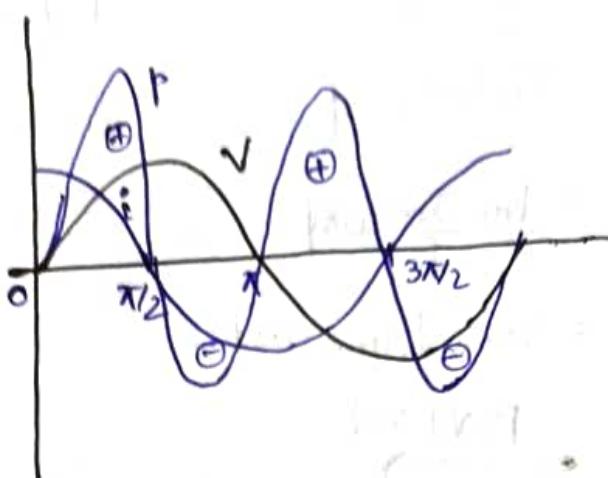
$$\text{Average power, } P_{\text{av}} = \frac{1}{T} \int_0^T P dt = \frac{1}{T} \int_0^T \frac{I_m V_m}{2} \sin 2\omega t dt = 0$$



12-04-2023

$\rightarrow R-L$

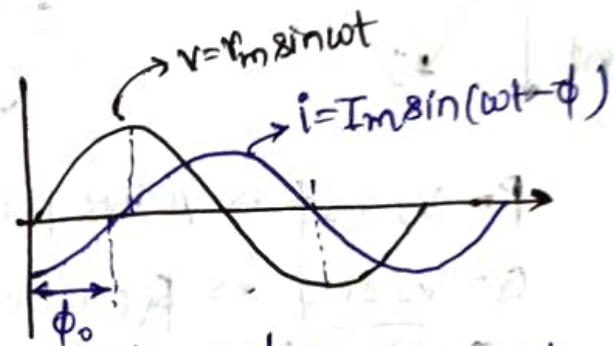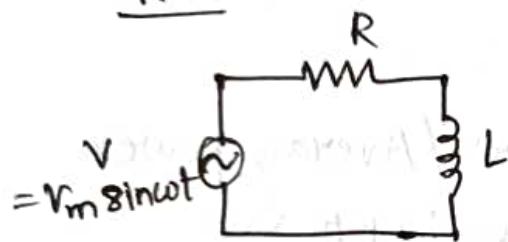

Inst. power = Inst. voltage \times inst. current

$$\Rightarrow P = v \cdot i$$

$$\Rightarrow P = V_m \sin \omega t \times \sin(\omega t - \phi)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$= V_m I_m \sin \omega t [\sin \omega t \cos \phi - \cos \omega t \sin \phi]$$

$$= V_m I_m [\sin^2 \omega t \cos \phi - \sin \omega t \cos \omega t \sin \phi]$$

$$= V_m I_m \left[\left(\frac{1 - \cos 2\omega t}{2} \right) \cos \phi - \frac{\sin 2\omega t}{2} \sin \phi \right]$$

$$= \frac{V_m I_m}{2} [\cos \phi - (\cos 2\omega t \cos \phi + \sin 2\omega t \sin \phi)]$$

$$\Phi = V_m \frac{I_m}{2} \cos \phi - \frac{V_m I_m}{2} (\cos(2\omega t + \phi))$$


Average power,

$$P_{av.} = \frac{1}{T} \int_0^T P dt = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos \phi dt - \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \omega x (\sin \omega t - \phi) dt$$

$$= \frac{V_m I_m}{2} \cos \phi$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$
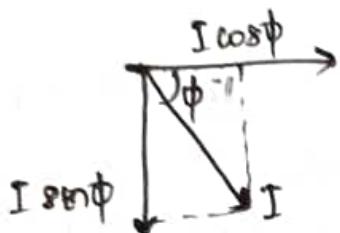
$$\therefore P_{av.} = V_{rms} I_{rms} \cos \phi$$



$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

$$S = VI$$

$$I = I_{rms}$$

$$V = V_{rms}$$

$P = VI \cos \phi \Rightarrow$ Active power / Real power / Average power

$Q = VI \sin \phi \Rightarrow$ Reactive power \rightarrow flows back to source (circulates)

$S = \sqrt{P^2 + Q^2} \Rightarrow$ Apparent power

$$P^2 + Q^2 = (VI \cos \phi)^2 + (VI \sin \phi)^2$$

$$= (VI)^2 [\cos^2 \phi + \sin^2 \phi]$$

$$= (VI)^2 = S^2$$

$$\therefore S = \sqrt{P^2 + Q^2}$$

\rightarrow Complex power, $\bar{S} = P + jQ$

$$|\bar{S}| = \sqrt{P^2 + Q^2} = S$$

\rightarrow Apparent power is the magnitude of the complex power.

\rightarrow Active power, $P = S \cos \phi \rightarrow$ Watts, kW, MW

Reactive power, $Q = S \sin \phi \rightarrow$ Volt-Ampere Reactive (VAR, kVAR, MVAR)


Apparent power, $S = \sqrt{P^2 + Q^2} \rightarrow$ Volt-Ampere (VA, kVA, MVA)

$$\rightarrow \text{Power factor (pf)} = \frac{\text{Active power}}{\text{Apparent power}} = \frac{P}{S} = \cos\phi$$


↳ Best pf = 1 when $\cos\phi = 1$ or $\phi = 0 \rightarrow$ purely resistive.

↳ Unity power factor: $\cos\phi = 1, \phi = 0$


18-04-2023

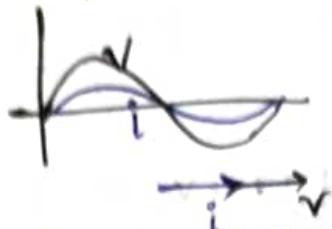

↳ current is lagging behind the voltage

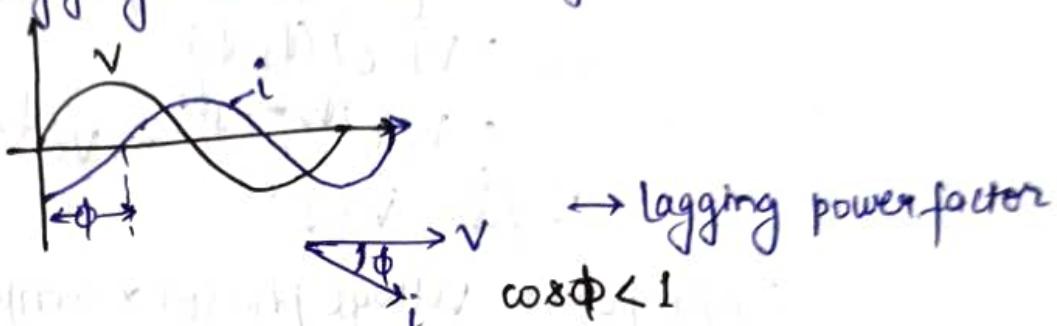

↳ current is leading ahead of voltage

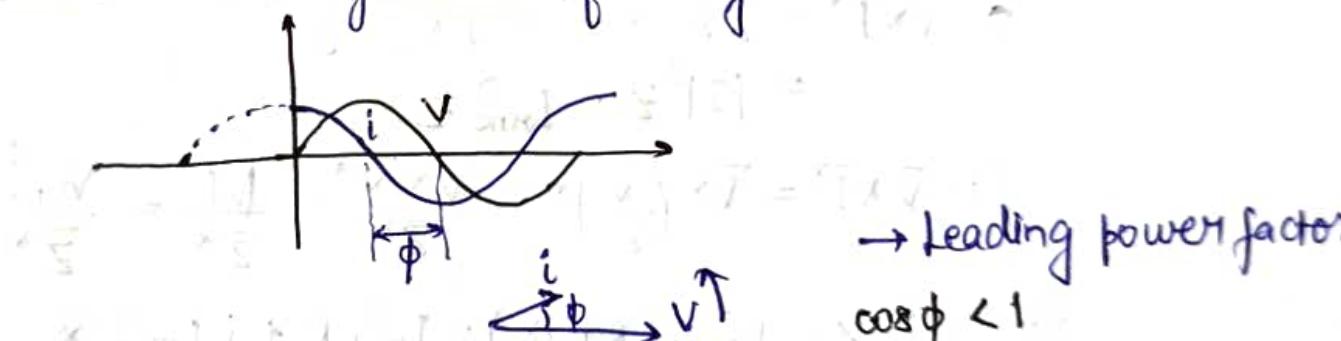

e.g. 0.8 lag } power
 0.8 lead } factor

$$\rightarrow S = P + jQ$$

Polar form

Rectangular form

$$V = V_m \sin(\omega t + \phi_v) \rightarrow V [\phi_v] \rightarrow V e^{j\phi_v}$$

$$I = I_m \sin(\omega t + \phi_i) \rightarrow I [\phi_i] \rightarrow I e^{j\phi_i}$$

$V \rightarrow$ rms value
 $I \rightarrow$ rms value
 $\phi_v, \phi_i \rightarrow$ in radians

$$\text{Active power, } P = VI \cos(\phi_v - \phi_i)$$

$$\text{Reactive power, } Q = VI \sin(\phi_v - \phi_i)$$

#

Complex Conjugate

$$3+j4 \rightarrow 3-j4$$

$$5|\tan^{-1}(4/3) \rightarrow 5|\tan^{-1}(-4/3)$$

$$A\angle\theta \rightarrow A\angle\theta$$

$$Ae^{j\theta} \rightarrow Ae^{-j\theta}$$

Complex power, $\bar{S} = P + jQ$

$$= VI \cos(\phi_v - \phi_i) + j VI \sin(\phi_v - \phi_i)$$

$$= VI [\cos(\phi_v - \phi_i) + j \sin(\phi_v - \phi_i)]$$

$$= VI e^{j(\phi_v - \phi_i)}$$

$$= VI e^{j\phi_v} e^{-j\phi_i} = V e^{\phi_v} \times I e^{-j\phi_i}$$

$$\therefore \boxed{\bar{S} = \bar{V} \times \bar{I}^*}$$

Complex power = voltage phasor \times complex conjugate of the current phasor

$$\bar{S} = \bar{V} \times \bar{I}^* = \bar{I} \bar{Z} \times \bar{I}^* = \bar{I} \times \bar{I}^* \bar{Z}$$

$$= |I|^2 \bar{Z} = I_{\text{rms}}^2 \bar{Z}$$


$$\bar{S} = \bar{V} \times \bar{I}^* = \bar{V} \times \left(\frac{\bar{V}}{\bar{Z}} \right)^* = \frac{\bar{V} \times \bar{V}^*}{\bar{Z}^*} = \frac{|V|^2}{\bar{Z}^*} = \frac{V_{\text{rms}}^2}{\bar{Z}^*}$$


$$\bar{S} = I_{\text{rms}}^2 \bar{Z} = I_{\text{rms}}^2 (R + jX) = I_{\text{rms}}^2 R + j I_{\text{rms}}^2 X$$

$$\bar{S} = P + jQ$$

Active power, $P = I_{\text{rms}}^2 R$

Reactive power, $Q = I_{\text{rms}}^2 X$

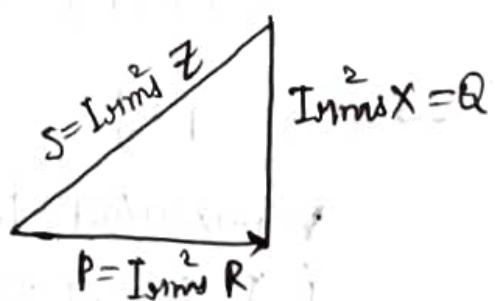

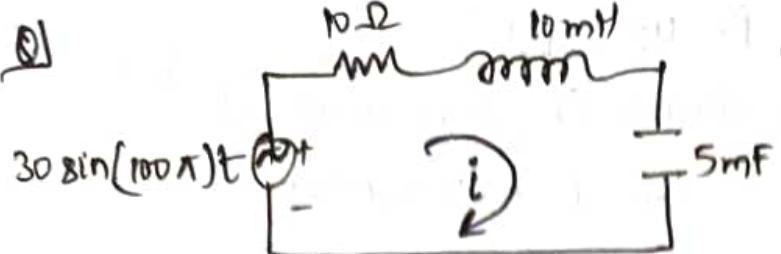

① Determine the current i .

② Evaluate the complex power delivered by the source.

③ Prove that:

ⓐ Active power delivered by the source is equal to the active power consumed by the circuit.

ⓑ Reactive power delivered by the source is equal to the reactive power absorbed by the circuit.

Soln:

$$V = V_m \sin \omega t = V_m \sin(2\pi f)t$$

$$\Rightarrow V = 30 \sin(100\pi)t$$

$$V_m = 30, V_{rms} = 30/\sqrt{2}$$

$$2\pi f = 100\pi \Rightarrow f = 50 \text{ Hz}$$

$$X_L = 2\pi f L = 2\pi \times 50 \times 10 \times 10^{-3} = 3.14 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 10^{-3} \times 5} = 0.6366$$

$$\text{Total impedance, } Z = 10 + j3.14 - j0.6366 \\ = (10 + j2.51) \Omega$$

$$\text{Current, } i = \frac{V}{Z} = \frac{30/\sqrt{2} \text{ } \Omega}{10 + j2.51} = 2.057 \angle -14.09^\circ \text{ A}$$

Complex power delivered by the source,

$$\bar{S} = V \times I \bar{I}^*, \bar{I} = 2.057 \angle -14.09^\circ$$


$$|\bar{I}|^* = 2.057 \angle +14.09^\circ \text{ A}$$

$$\text{Q81 } \bar{S} = \frac{30}{\sqrt{2}} \Omega \times 2.057 \angle 14.09^\circ$$

$$= 43.6462 \angle 14.09^\circ \text{ VA}$$

$$= 42.33 + j10.625 \text{ VA}$$

$$\hookrightarrow P + jQ$$

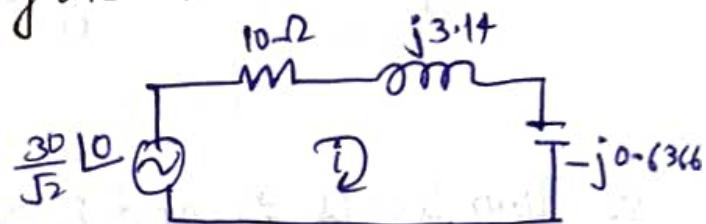

A.p. delivered by the source, $P = 42.33 \text{ W}$

A.p. delivered consumed in the circuit (by 10Ω resistor)

$$= I_{\text{rms}}^2 R = (2.057)^2 \times 10$$

$$= 42.31 \text{ W}$$

R.P. supplied by the source, $Q = 10.625 \text{ VAR}$

R.P. absorbed by the inductor $= I_{\text{rms}}^2 \times X_L$

$$= (2.057)^2 \times 3.14 = 13.28 \text{ VAR}$$

R.P. absorbed by the capacitor $= (I_{\text{rms}})^2 (-X_C)$

$$= -(2.057)^2 (0.6366)$$


$$= -2.69 \text{ VAR}$$

Net R.P. absorbed by $L \& C = 13.28 - 2.69$

$$= 10.59 \text{ VAR}$$

19-04-2023

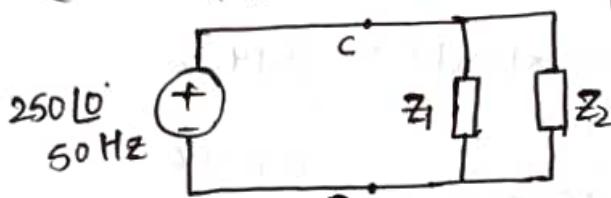Q) Two loads Z_1 and Z_2 are connected in parallel across an AC voltage source (G_1) as shown in fig.



$Z_1 = 4 \text{ kW}$ at a pf of 0.75 lag

$Z_2 = 2 \text{ kW}$ at a pf of 0.95 lead.
↓ active power

- Evaluate the complex power drawn from the source.
- Evaluate the pf at load terminals (C-D).
- Evaluate the current drawn from the source (G_1).

Soln: Load $Z_1 = 4 \text{ kW}$ at a pf 0.75 lag $\rightarrow P_1$

$$\cos \phi_1 = 0.75 \Rightarrow \phi_1 = 41.4096$$

$$\text{Apparent power of } Z_1 (S_1) = \frac{4000}{0.75} = 5333.33 \text{ VA}$$

$$\text{Reactive power of } Z_1 = S_1 \cos \phi$$

$$= 5333.33 \sin(41.4096) = 3527.668 \text{ VAr}$$


(Q)

Complex power of $Z_1 = P_1 + jQ_1 = 4000 + j3527.668 \text{ VA}$

Load $Z = 2\text{kW}$ at pf of 0.95 lead $\rightarrow P_2$

$$\cos\phi_2 = 0.95 \Rightarrow \phi_2 = 18.195^\circ$$
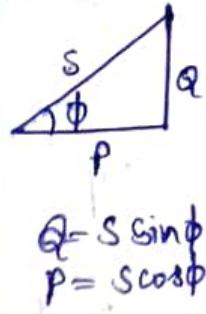
$$\text{Apparent power of } Z_2 (S_2) = \frac{P_2}{\cos\phi_2} = \frac{2000}{0.95} = 2105.26 \text{ VA}$$



$$\text{R.P. of } Z_2 (Q_2) = S_2 \sin\phi_2 = 2105.26 \sin 18.195^\circ = 657.367 \text{ VAR}$$

$$\text{C.P. of } Z_2 = \bar{S}_2 = 2000 - j657.367 \text{ VA}$$

$$\text{Total C.P. drawn from the source} = \bar{S}_1 + \bar{S}_2$$

$$= 4000 + j3527.668 + 2000 - j657.367$$

$$= 6000 + j2870.3$$

$$= 6651.2 \angle 25.56^\circ$$

$$\text{P.f. at terminal (C-D)} = \frac{\text{Ac.P.}}{\text{App.P.}}$$

$$= \frac{6000}{6651.2} = 0.90209 \text{ lag}$$



$$\text{Or, } \cos\phi = \cos(25.56) = 0.902$$

$$\text{Or, } \cos(\tan^{-1}(\frac{Q}{P})) = \cos(\tan^{-1}(\frac{2870.3}{6000})) = 0.902$$

$$\text{App.P.} = V_{\text{rms}} \times I_{\text{rms}} = 6651.2$$

$$\text{Current drawn from the source} = \frac{6651.2}{250} = 26.6 \text{ A}$$

Q1

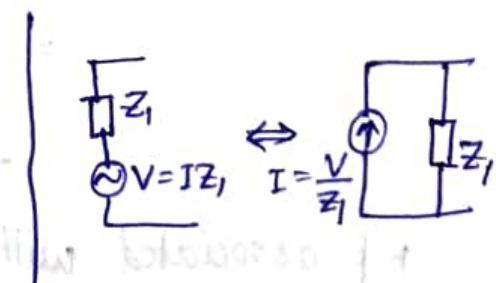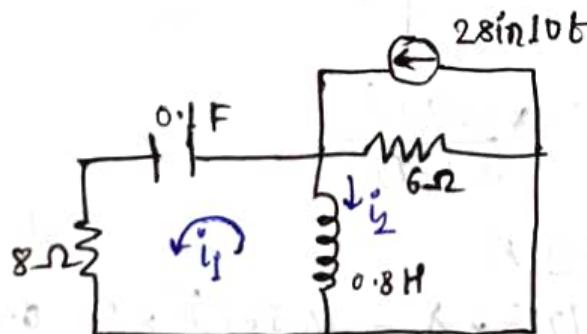


- ① Evaluate the R.P. associated with 0.1 F capacitor.
- ② Evaluate the p. consumed by 8 ohm resistor.

$$\text{Soln: } I_m \sin \omega t = 2.8 \sin 10t$$

$$\omega = 10 \text{ rad/s}, I_m = 2A, I_{\text{rms}} = \frac{2}{\sqrt{2}} = \frac{2}{\sqrt{2}} 10^{\circ} A$$

$$\text{Capacitive reactance of } 0.1 \text{ F cap.} = \frac{1}{j\omega C} = \frac{1}{j10 \times 0.1} = -j10 \Omega$$

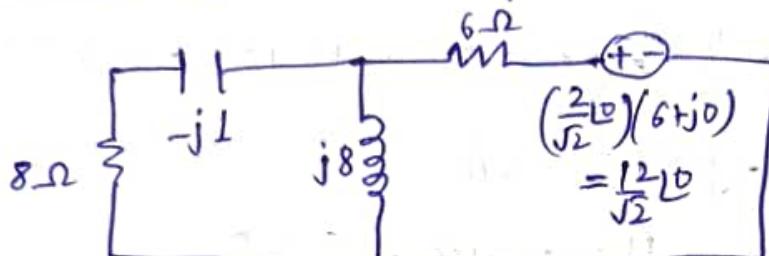
$$\text{Inductive reactance of } 0.5 \text{ H Ind.} = j\omega L = j \times 10 \times 0.8 = j8 \Omega$$



Eff. impedance of $(8-j1) \parallel (j8)$,

$$Z_{\text{eq}} = \frac{(8-j1)(j8)}{(8-j1)+j8} = 6.07 \angle 41.69^\circ \Omega$$

$$= (4.533 + j4.037) \Omega$$

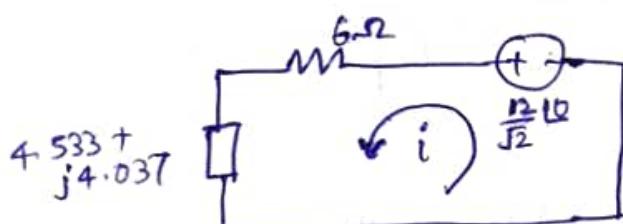

$$\text{Total current supplied by } \left(\frac{12}{\sqrt{2}}\right) \Omega \text{ source}$$

$$i = \frac{\frac{12}{\sqrt{2}} \Omega}{(6+j0) + 4.533 + j4.037}$$

$$= \frac{\frac{12}{\sqrt{2}} \Omega}{10.533 + j4.037}$$

$$= 0.752 \angle -20.97^\circ$$

current flowing through 0.1 F cap.


$$i_1 = i \times \frac{j8}{(8-j1+j8)}$$

$$= 0.752 \angle -20.97^\circ \times \frac{0+j8}{(8+j7)}$$

$$= 0.565 \angle 27.9^\circ A$$

$$\text{R.P. associated with } 0.1 \text{ F cap.} = |I|^2 \times X_C = (0.565)^2 \times 1 = 0.32 \text{ VAR}$$


$$\text{Power consumed by } 8\Omega \text{ resistor} = |I|^2 \times R = (0.565)^2 \times 8 = 2.56 \text{ W.}$$

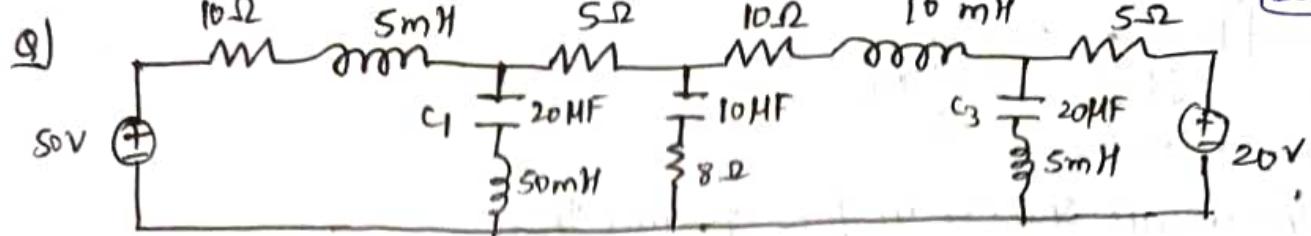

In the circuit shown in fig., evaluate at steady state,

- energy stored in the circuit.
- power dispersed in the circuit.

Soln: @ Steady state eq. circuit:

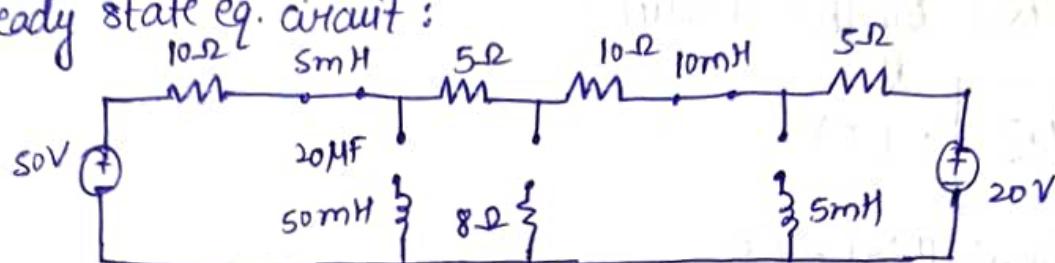

Applying KVL,

$$50 - 10I - 5I - 10I - 5I - 20 = 0$$

$$\Rightarrow I = 30/30 = 1A$$

$$\text{Voltage across } C_1 \rightarrow (20\mu F) \Rightarrow 50 - 10 = 40V$$

$$\text{,,} \quad C_2 \rightarrow (10\mu F) \Rightarrow 50 - 10 \times 1 - 5 \times 1 = 35V$$

$$\text{,,} \quad C_3 \rightarrow (20\mu F) \Rightarrow 50 - 10 \times 1 - 5 \times 1 - 10 \times 1 = 25V$$

$$\begin{aligned} \text{Total energy stored in capacitor } C_1, C_2 \text{ & } C_3 &\Rightarrow \frac{1}{2} \times 20 \times 10^{-6} \times 40^2 \\ &\quad + \frac{1}{2} \times 10 \times 10^{-6} \times 35^2 \\ &\quad \therefore E = \frac{1}{2} CV^2 \end{aligned}$$


$$\text{Total energy stored in inductor} = \frac{1}{2} \times 5 \times 10^{-3} \times 1^2 + \frac{1}{2} \times 10 \times 10^{-3} \times 1^2$$

$$\therefore \text{Energy stored in circuit} = 35 \text{ mJ.}$$

② At steady state,

Power dissipated in the circuit (Resistor)
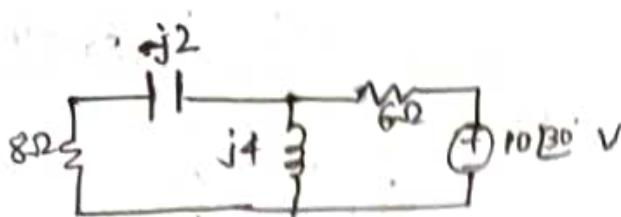
$$\begin{aligned} &= 1^2 \times 10 + 1^2 \times 5 + 1^2 \times 10 + 1^2 \times 5 \\ &= 30W \end{aligned}$$



In the circuit shown in fig, prove that

- ① total active power supplied by the source is equal to the total active power consumed.
- ② total s.p. supplied by the source is equal to the total s.p. absorbed by the circuit.

Soln:



$$Z_{eq} = [(8-j2) || j4] + 6\Omega$$

$$= 6 + \frac{(8-j2) \times j4}{8-j2 + j4} = 7.8826 + j3.53 = 8.632 \angle 24.13^\circ \Omega$$

$$\text{Current supplied by the source} = \frac{V}{Z_{eq}} = \frac{10 \angle 30^\circ}{8.632 \angle 24.13^\circ} = 1.1581 \angle 5.87^\circ \text{ A}$$

$$\begin{aligned} \text{Complex power delivered by } 10 \angle 30^\circ \text{ V source} &= V \times I^* \\ &= 10 \angle 30^\circ \times 1.1581 \angle -5.87^\circ \\ &= 11.581 \angle 24.13^\circ \text{ VA} \\ &= \underbrace{10.569}_{P} + \underbrace{j4.73}_{Q} \text{ V} \end{aligned}$$

Current through $(8-j2)\Omega$ impedance.

$$= 1.1581 \angle 5.87^\circ \times \frac{j4}{8-j2+j4} = 0.562 \angle 81.84^\circ \text{ A}$$

$(j4)\Omega$ impedance

$$\begin{aligned} &= \frac{1.1581 \angle 5.87^\circ \times (8-j2)}{8-j2+j4} \\ &= 1.1581 \angle -22.2^\circ \text{ A} \end{aligned}$$

$$\text{Total active power absorbed} = 1.1581^2 \times 6 + 0.562^2 \times 8 = 10.57$$

$$\text{Total reactive power consumed} = 0.562^2 (-2) + 1.1581 \times 4 = 4.73$$

Hence proved.

Power in AC Circuit

① Active Power (P) or Real Power/Average Power


② Reactive Power (Q)

③ Apparent Power (S)

$$\text{Complex Power, } \bar{S} = \bar{P} + j\bar{Q}$$


Apparent Power = $|S| \rightarrow$ Magnitude of complex power

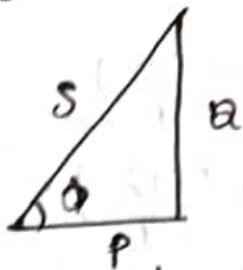Power factor, $\cos \phi = \frac{\text{Active Power}}{\text{Apparent Power}}$




$$\left| \begin{array}{l} P = S \cos \phi \\ Q = S \sin \phi \\ \phi = \tan^{-1}(Q/P) \end{array} \right.$$

Schematic representation:

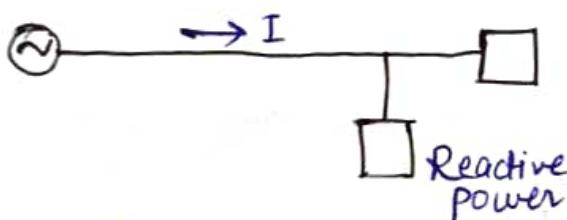

Circuit diagram:

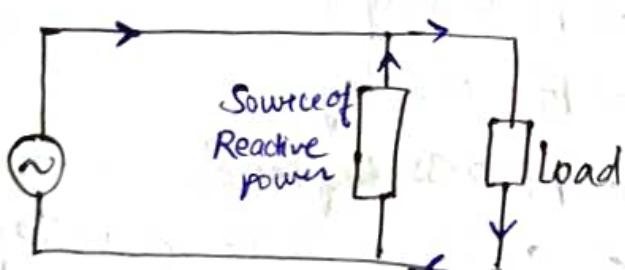


Devices needing magnetic field will need the circulation of some current in the circuit
 \rightarrow Needed a reactive power/current.

lag 0.8 $\rightarrow \cos\phi$,

lag 0.9 $\rightarrow \cos\phi_B$

$$\phi_1 = \tan^{-1}\left(\frac{Q_1}{P}\right)$$
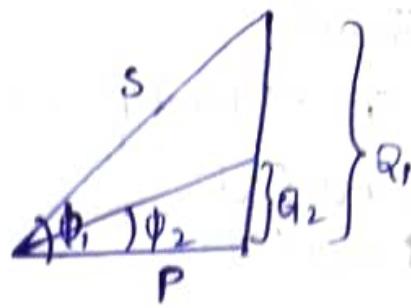
$$\phi_2 = \tan^{-1}\left(\frac{Q_2}{P}\right)$$



Reactive power to be compensated,


$$Q_1 - Q_2 \rightarrow Q = I^2 X_C = \frac{V^2}{X_C} = \frac{V^2}{\frac{1}{2\pi f C}} = 2\pi f C V^2$$

$$C = \frac{Q}{2\pi f V^2}$$

$$(\because X_C = \frac{1}{2\pi f C})$$

Value needs to
compensate the
reactive power
of value Q

Q1

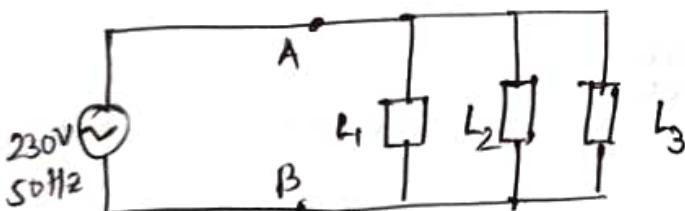

Three loads, $L_1 = 10 \text{ kW}$ at pf 0.8 lag,

$L_2 = 15 \text{ kW}$ at pf 0.6 lag,

$L_3 = 10 \text{ kW}$ at pf 0.95 lead,

are connected across a 230V, 50Hz AC voltage source
as shown in figure.

- ① Determine the power factor at load terminals A-B.
- ② Evaluate the capacitance of the capacitor required to be connected across the load terminals (A-B) for improving the power factor to 0.98 lag.
- ③ Calculate the current drawn from the source before and after improving the power factor.

~~Soln:~~ $L_1 \rightarrow 10 \text{ kW at pf } 0.8 \text{ lag} \rightarrow S_1 = \frac{10}{0.8} = 12.5 \text{ kVA}, Q = 5.8 \sin \phi$,
 complex power of $L_1(S_1)$, $\phi = \cos^{-1}(0.8)$, $\bar{S}_1 = 10 + j 5.8 \sin \phi$
 $= (10 + j 7.5) \text{ kVA}$

$L_2 \rightarrow 15 \text{ kW at pf } 0.6 \text{ lag} \rightarrow S_2 = \frac{15}{0.6} = 25 \text{ kVA}$

complex power of L_2 , $\bar{S}_2 = 15 + j 20$

$L_3 \rightarrow 10 \text{ kW at pf } 0.95 \text{ lead}, S_3 = \frac{10}{0.95} = 10.52 \text{ kVA}$

complex power of L_3 , $\bar{S}_3 = 10 - j 3.28$

Total complex power supplied by the source,

$$\bar{S} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \\ = 35 + j 24.213 \text{ kVA}$$


Power factor at load terminals

$$= \cos \left(\tan^{-1} \left(\frac{24.215}{35} \right) \right) = 0.822 \text{ lag}$$



Total apparent power supplied

$$(\text{before connecting capacitor}) = |\bar{S}| = \sqrt{35^2 + 24.213^2}$$

$$= 42.55 \text{ kVA}$$

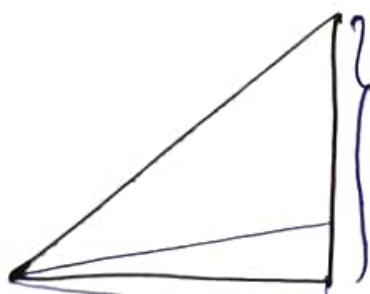
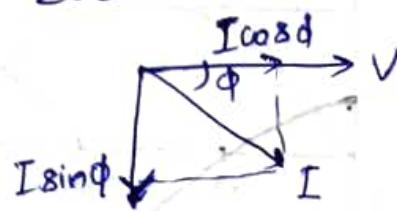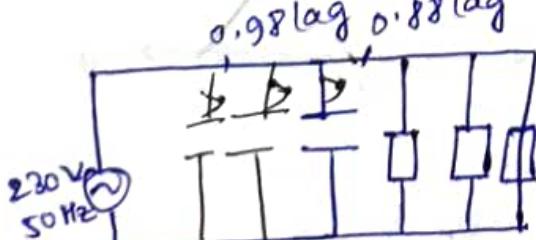
$$\text{current drawn at pf } 0.822 \text{ lag} = \frac{S}{V} = \frac{42.55 \times 1000}{230} = 185.4$$





$$\text{Apparent power drawn at pf } 0.98 \text{ lag (after connecting capacitor)} = \sqrt{35^2 + 7.127^2} \\ = 35.7 \text{ kVA}$$

$$\text{current drawn from the source at pf } 0.98 \text{ lag} = \frac{35.7 \times 1000}{230} = 155.2 \text{ A}$$

APFC: Active Power Factor Correction
Static VAR Compensator

THREE PHASE AC SYSTEM

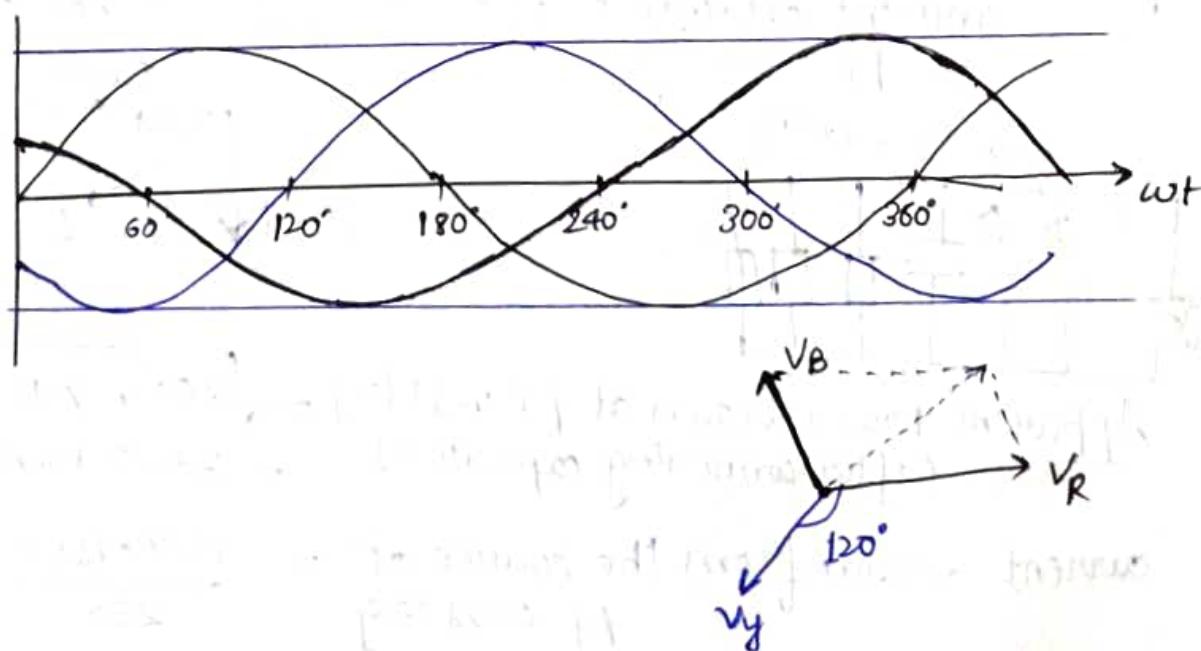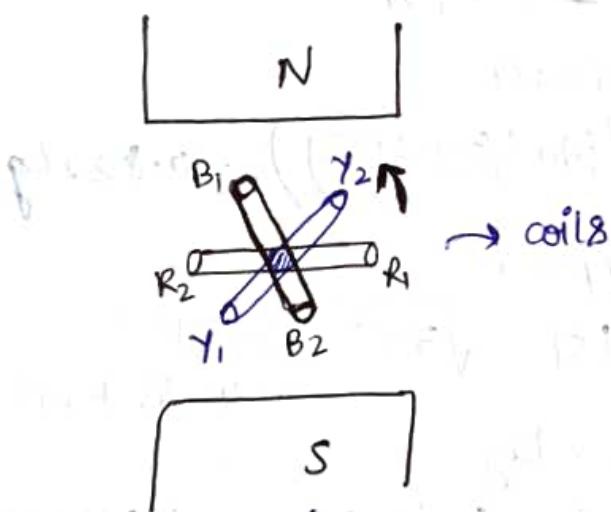- High power factor
- High power density
- Constant power
- Reliable
- Provides rotating magnetic field
- Transmission is cheaper



$$V_R = V_m \sin \omega t$$

$$V_y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ)$$

$$\Rightarrow V_B = V_m \sin(\omega t + 120^\circ)$$

$$V_R = V \underline{10^\circ}$$

$$V_y = V \underline{-120^\circ}$$

$$V_B = V \underline{-240^\circ} = V \underline{120^\circ}$$

→ Actual



→ Magnets rotate instead of the coils

→ Phase sequence: order in which waveforms attain their peak values.

RYB } Possible phase sequences
RBY }

RYBR YBYRB

RBY RBY RBY


$$V_R + V_y + V_B$$

$$= V_m \sin \omega t + V_m \sin(\omega t - 120^\circ) + V_m \sin(\omega t - 240^\circ)$$



$$= V_m [\sin \omega t + \sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ + \sin \omega t \cos 240^\circ - \cos \omega t \sin 240^\circ]$$

$$= V_m [\sin \omega t - \frac{1}{2} \sin \omega t - \frac{\sqrt{3}}{2} \cos \omega t - \frac{1}{2} \sin \omega t + \frac{\sqrt{3}}{2} \cos \omega t]$$



$$= 0$$

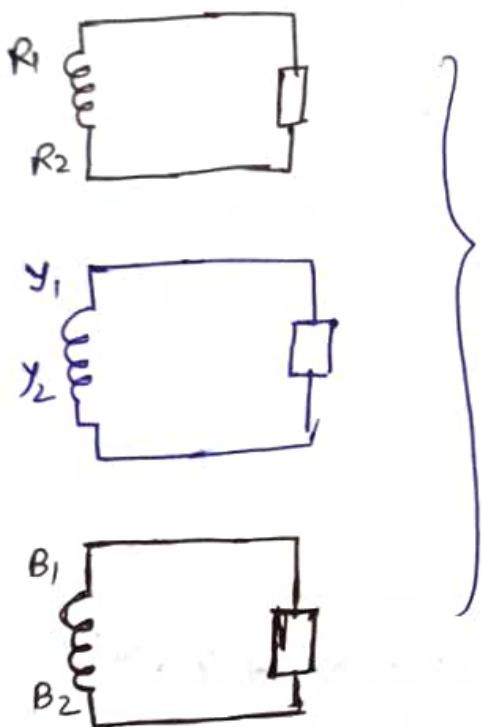

will be interconnected

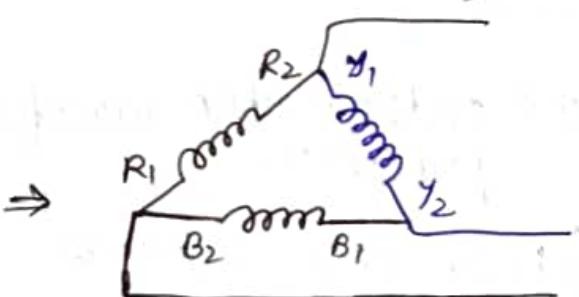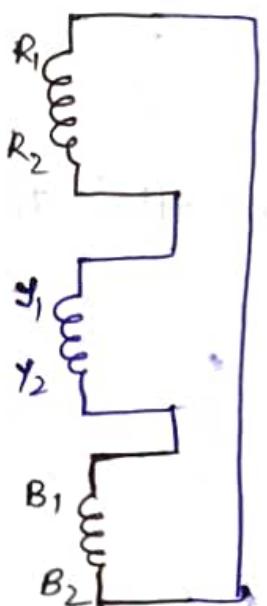


Delta Connection
(Mesh Connection)

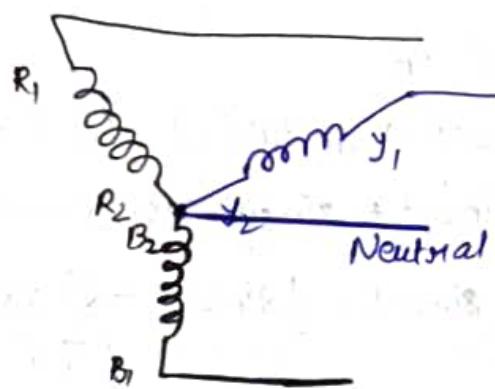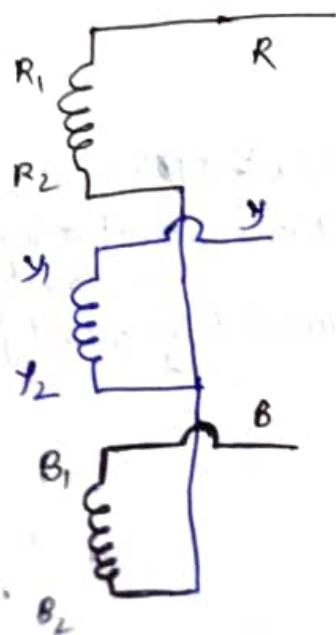

Star Connection
(Y-connection)

Star Connection → 3Phase 4 wire system

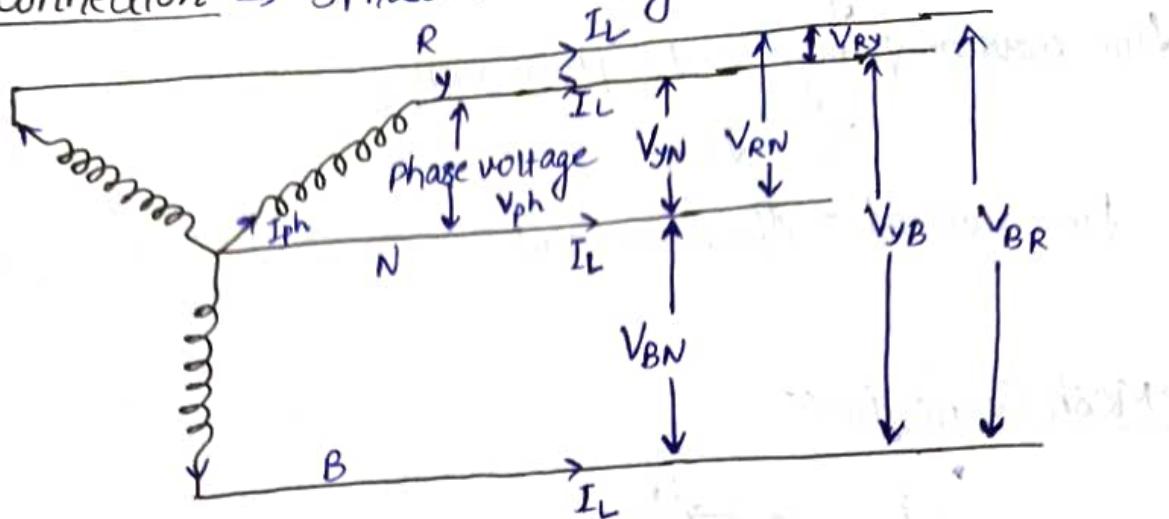

Phase voltages: V_{RN}, V_{YN}, V_{BN}

Line voltages: V_{RY}, V_{YB}, V_{BR}

Line voltage leads the corresponding ph voltage by angle 30°.

$$|V_{RN}| = |V_{YN}| = |V_{BN}| = V_{ph}$$

$$|V_{RY}| = |V_{YB}| = |V_{BR}| = V_L$$

$$\begin{aligned} \bar{V}_{RY} &= \bar{V}_{RN} + \bar{V}_{NY} \\ &= \bar{V}_{RN} - \bar{V}_{YN} \end{aligned}$$

$$\begin{aligned} \bar{V}_{YB} &= \bar{V}_{RN} - \bar{V}_{BN} \\ V_{BR} &= \bar{V}_{BN} - \bar{V}_{RN} \end{aligned}$$

$$\begin{aligned} |V_{RY}| &= \sqrt{|V_{RN}|^2 + (V_{YN})^2 + 2V_{RN}V_{YN}\cos60^\circ} \\ &= \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph} \cdot V_{ph} \times 0.5} \end{aligned}$$

$$\therefore V_L = \sqrt{3} V_{ph}$$

440V, 3ph, 50 Hz

↓
Line voltage

→ Line Current and Phase current

$$I_L = I_{ph}$$


Star (Y)- Connected System:

Line current = $\sqrt{3}$ phase voltage

$$V_L = \sqrt{3} V_{ph}$$

Line current = Phase current

Delta-Mesh Connection

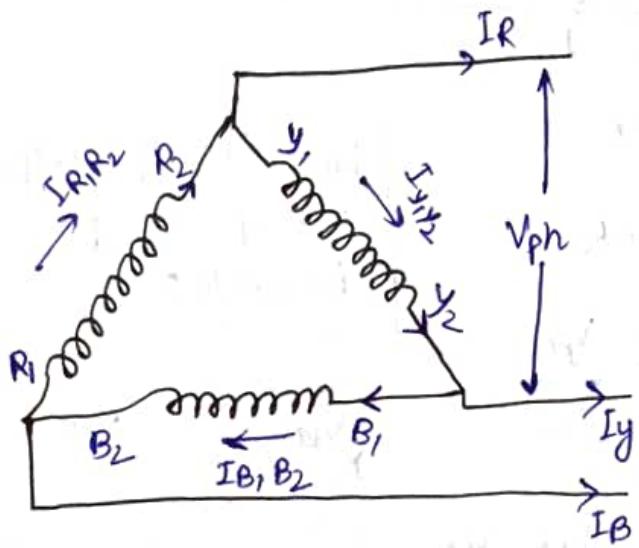

$$I_R = I_{R1, R2} - I_{y1, y2}$$

$$I_y = I_{y1, y2} - I_{B1, B2}$$

$$I_B = I_{B1, B2} - I_{R1, R2}$$

Δ-connected System:

Line voltage = Phase voltage


For a balanced system,

$$|I_{RR_2}| = |I_{y1, y2}| = |I_{B1, B2}| = I_{ph}$$


$$I_R = I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph} \cos 60^\circ}$$

$$= \sqrt{3} I_{ph}$$

$$\therefore I_L = \sqrt{3} I_{ph}$$



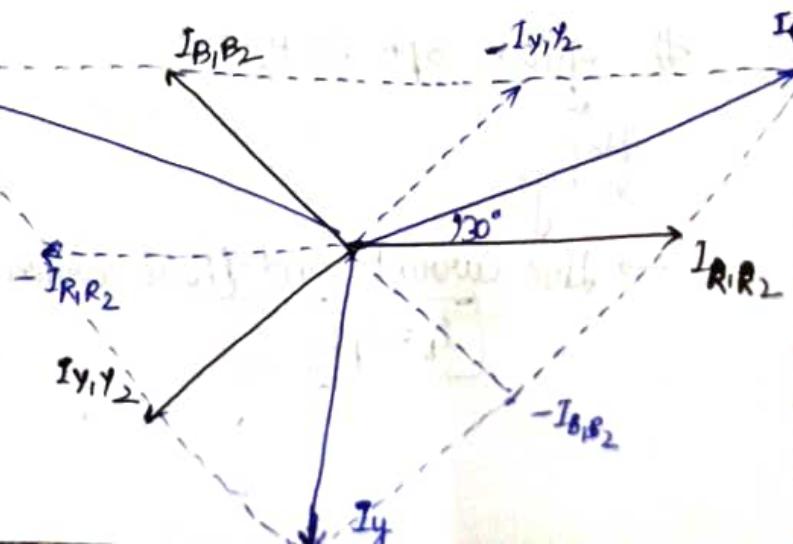


3-phase Transformer

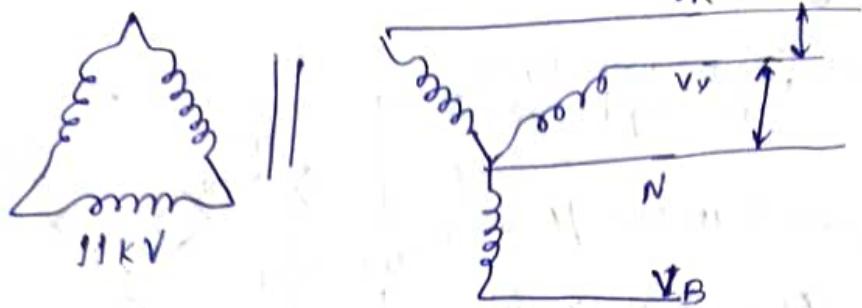

→ Vector phase: Dyn 11

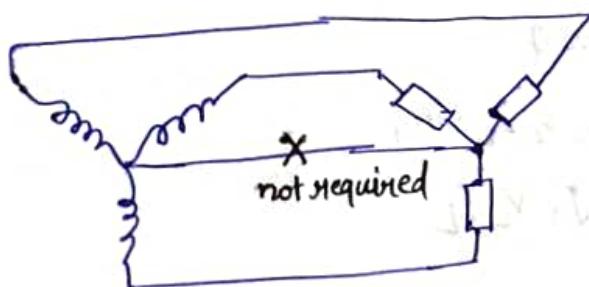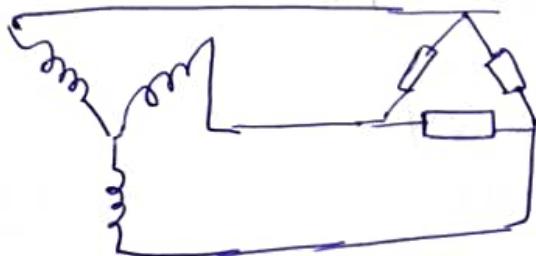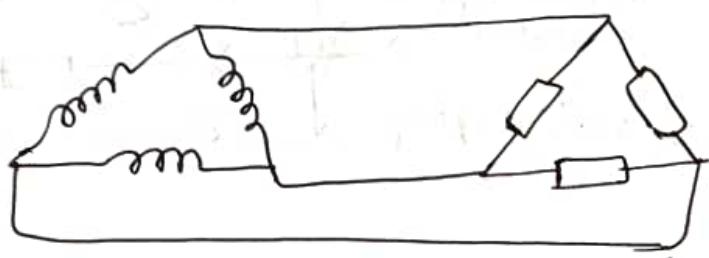Δ Y N phase shift b/w primary & secondary voltages




Power in 3-phase System

For balanced system (same impedance in all phases, z)

3-phase power = $3 \times$ power in one phase

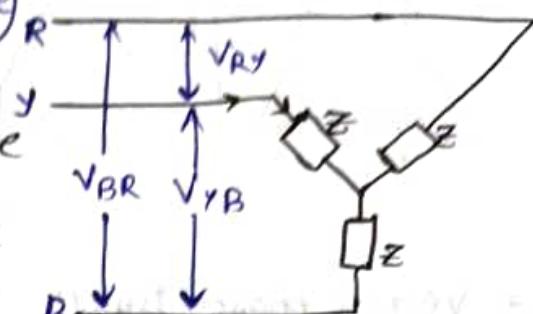3-phase active power (P) = $3 \times$ single phase active power




$$P = 3V_{ph} \cdot I_{ph} \cos\phi, \phi: \text{phase diff.}$$

Star connected system:

Line voltage, $V_L = \sqrt{3} \times \text{phase voltage (}V_{ph}\text{)}$

$$V_L = \sqrt{3} V_{ph}$$

$$\Rightarrow V_{ph} = V_L / \sqrt{3}$$

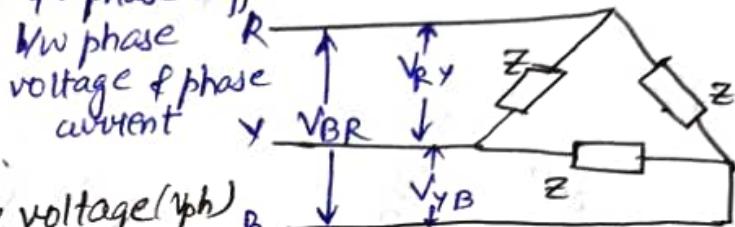

Line current, $I_L = \text{phase current (}I_{ph}\text{)}$

$$I_L = I_{ph}$$

Active power, $P = 3 \cdot V_{ph} \cdot I_{ph} \cos\phi$

$$= 3 \cdot \frac{V_L}{\sqrt{3}} \cdot I_L \cos\phi$$

$$\therefore P = \sqrt{3} V_L I_L \cos\phi$$

Reactive power, $Q = \sqrt{3} V_L I_L \sin\phi$

Apparent power, $S = \sqrt{3} V_L I_L$

Δ -connected System:

Line voltage (V_L) = phase voltage (V_{ph})

Line current, $I_L = \sqrt{3} \times \text{phase current}$

$$I_{ph} = I_L / \sqrt{3}$$

3-phase active power, $P = 3 \cdot V_{ph} \cdot I_{ph} \cos\phi$

$$= 3 \cdot V_L \cdot \frac{I_L \cos\phi}{\sqrt{3}}$$

$$\therefore P = \sqrt{3} I_L V_L \cos\phi$$



Reactive power, $Q = \sqrt{3} V_L I_L \sin \phi$

Apparent power, $S = \sqrt{3} V_L I_L$

Complex power, $\bar{S} = P + jQ$

Power factor = $\frac{\text{Active power}}{\text{Apparent power}}$

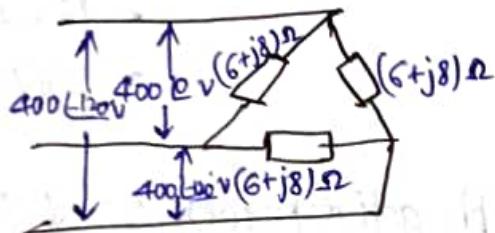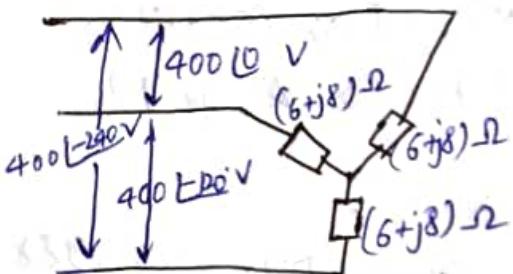- Q) A balanced star connected load of $(6+j8)\Omega$ impedance/phase is supplied from a $400V$, 3 ph, 50Hz supply.
- @ calculate the active power, reactive power and apparent power drawn from the supply.
- ② if the same load is connected in delta, calculate the active power, reactive power, apparent power and power factor.



Star connected load:

Active power, $P = \sqrt{3} V_L I_L \cos \phi$

$$V_L = 400\text{V}, I_{ph} = I_L$$

$$\text{Phase current, } I_L = \frac{\text{Phase voltage}}{\text{Impedance}} = \frac{V_{ph}}{Z_{ph}} = \frac{V_L / \sqrt{3}}{Z_{ph}}$$

$$= \frac{400/\sqrt{3}}{(6+j8)} = 23.09 \angle -53.13^\circ = I_L$$

$$3\text{-phase active power, } P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 23.09 \cos(53.13^\circ)$$

$$= 9598.35 \text{ W}$$

$$3\text{-phase reactive power, } Q = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} \times 400 \times 23.09 \sin(53.13^\circ)$$

$$= 12797.75 \text{ VAR}$$

$$\text{Apparent power, } S = \sqrt{3} \times V_L I_C$$

$$= \sqrt{3} \times 400 \times 23.09 = 15997.22 \text{ VA}$$

$$\text{Power factor} = \frac{\text{Active power}}{\text{Apparent power}} = \frac{9598.35}{15997.22} = 0.6 \text{ lag}$$

when the same load is connected in Δ :

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{im}} = \frac{400}{6+j8} = 40 \angle -53.13^\circ$$

$$|I_L| = \sqrt{3} I_{ph} = 40\sqrt{3} = 69.28$$

$$\text{3-ph active power, } P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 69.28 \cos(-53.13^\circ)$$

$$= \underline{28799.2 \text{ W}} \quad (\gg \star \text{ 3-ph P})$$

$$\text{3-ph active power, } Q = \sqrt{3} V_L I_L \sin \phi$$



$$= \sqrt{3} \times 400 \times 69.28 \sin(53.13^\circ) = -383988 \text{ VAR}$$


$$\text{Apparent power, } S = \sqrt{3} V_L I_L = \sqrt{3} \times 400 \times 69.28$$

$$= 47998.6 \text{ VA}$$

$$\text{Power factor} = \frac{\text{Active power}}{\text{Apparent power}} = \frac{28799.2}{47998.6} = 0.6 \text{ lag}$$


Improving power factor:

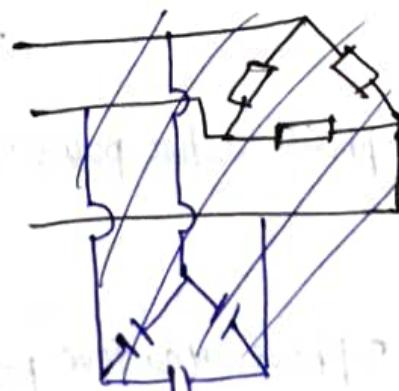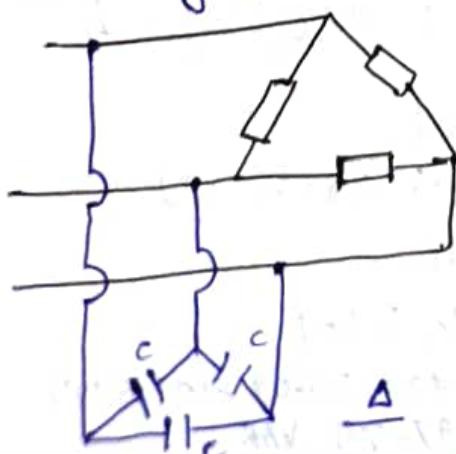

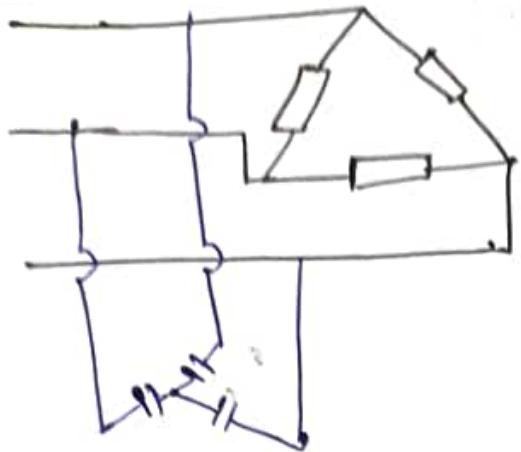

Reactive power supplied by the capacitor = $\frac{V^2}{X_C}$


$$X_C = \frac{1}{2\pi f C}$$

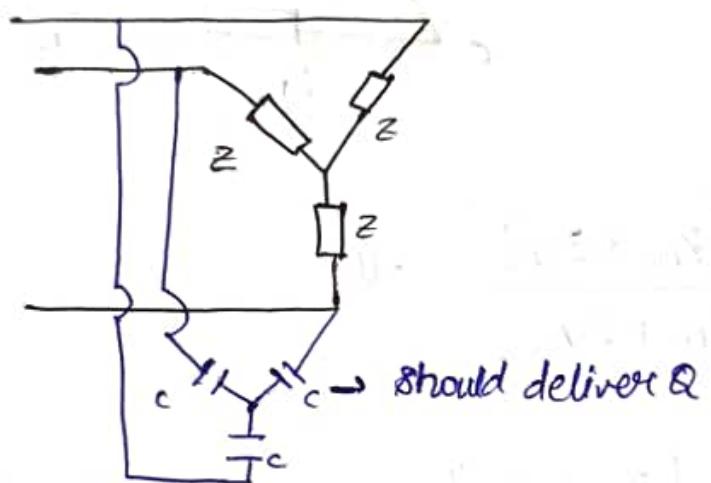

Electrical Machines:

TRANSFORMER

26-06-2023

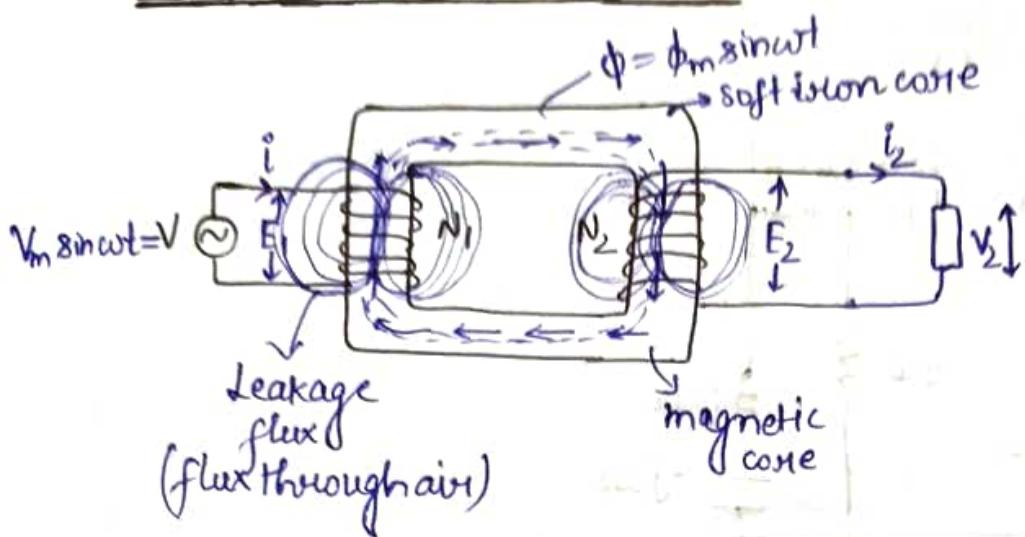

$$\text{Flux} = \frac{\text{MMF}}{\text{Reluctance}} \rightarrow \text{Ohm's law of magnetic circuit}$$

(MMF: Magneto-motive force)

$$\phi = \frac{NI}{S} = \frac{\Phi_m \sin \omega t}{\text{Reluctance}}$$

By Faraday's Law,

$$\text{EMF (E)} = N \frac{d\phi}{dt}$$

$$E_1 = N_1 \frac{d\phi}{dt}; E_2 = N_2 \frac{d\phi}{dt}$$

$$\Rightarrow \boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2}} \rightarrow \text{Twin's ratio}$$

If $E_2 > E_1 \Rightarrow N_2 > N_1 \rightarrow$ step-up transformer

$E_2 < E_1 \Rightarrow N_2 < N_1 \rightarrow$ step-down transformer

$$\rightarrow \frac{E_2}{N_2} = \frac{E_1}{N_1} \rightarrow \text{voltage induced per turn}$$

→ Frequency doesn't change.

→ Power transfer through magnetic medium.

→ Dirn of i_2 is such that it opposes the flux through secondary (Lenz's Law).

→ As a result, the flux inside core reduces $\Rightarrow E_1$ reduces.

→ As a result, diff b/w V & E_1 increases, thus more current (i_1) flows. The increase in current nullifies flux due to i_2 , hence again original flux is established.

Magnetising current (I_M) \rightarrow Reactive current (as does not constitute to power, ideally)

$$\bar{i}_1 = \bar{i}_0 + \bar{i}'_2$$

\hookrightarrow current reflected from secondary

(ie, the increase in current i_1 , as discussed above).

Instantaneous power at primary = $E_1 i_1$

$$E_1 i_1 = E_2 i_2 \text{ (ideally)} \quad \left[\Rightarrow i_1 = (N_2 E_1 / N_1) i_2 \Rightarrow N_1 i_1 = N_2 i_2 \right]$$

$$\boxed{\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{E_2}{E_1}}$$

\hookrightarrow Ampere turns are equal for both ~~side~~ coils

→ $i N$ = Ampere turn = const.

→ $\frac{E}{N}$ = voltage/turn = const.

Power Loss in Transformer



→ Core loss: due to { Eddy currents in core \rightarrow thin laminating done. Hysteresis loss \rightarrow many small loops of currents are formed. Both depends on B & frequency

$$\rightarrow \text{Flux density} = \frac{\phi}{A} = B \quad (\text{weber/m}^2)$$

$$M \propto NI$$



→ Copper loss: Power loss in windings.

→ Hysteresis loss:

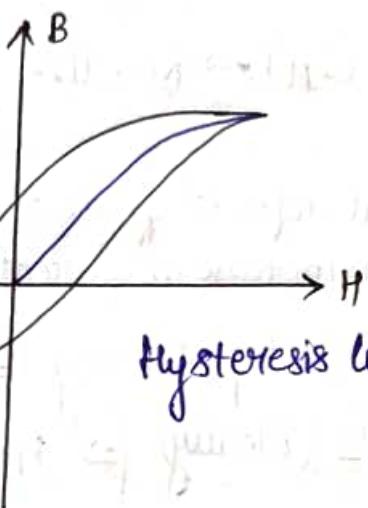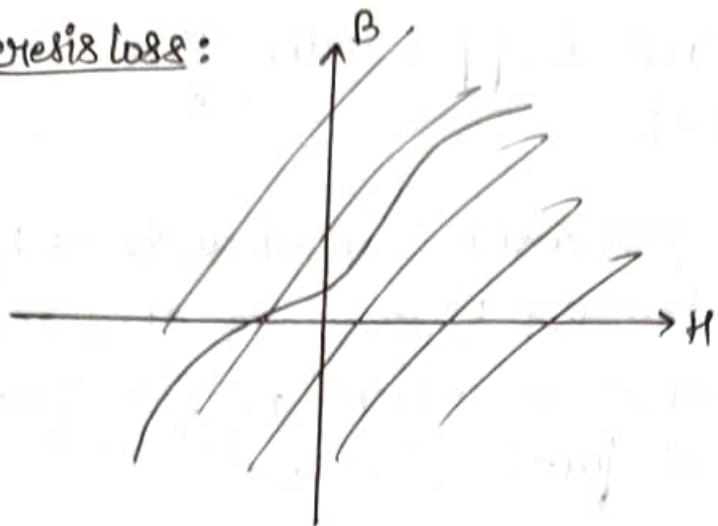

Hysteresis loop

Equivalent Circuit of Transformer:

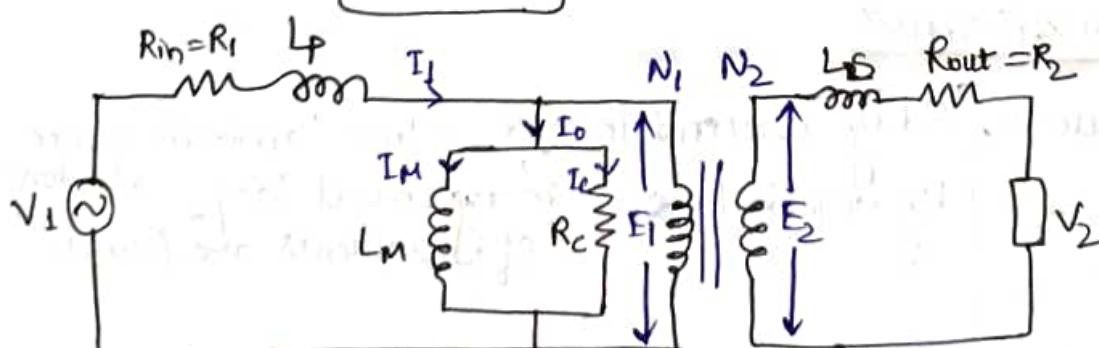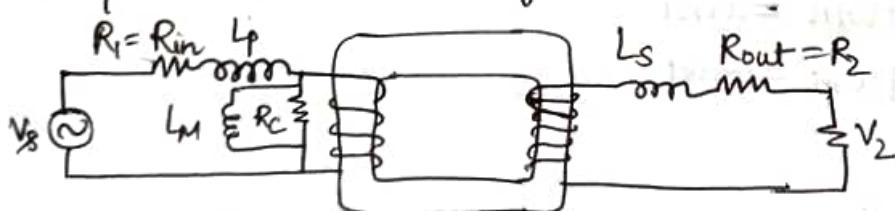

R_{in} & R_{out} : Copper resistance of 1° & 2° coils

L_p & L_S : Leakage inductance of 1° & 2° coils

L_M : Magnetizing inductance (Hysteresis loss) \rightarrow represents flux in core

R_C : Resistance of core

↓
 connected in parallel b/c core loss is constant, current through R_c in parallel will be constant if V_1 is constant & does not depend on induced voltage/current due to θ

- Even if load is not there, core losses exist. That's why input to chokes having transformers should be switched off.
- We don't use capacitor b/c it creates electric field whereas inductor creates magnetic field.

$$\bar{I}_1 = \bar{I}'_2 + \bar{I}_o$$

Now, replacing transformer,



$$I_2^2 R_2 = I'^2 R'_2 \Rightarrow R'_2 = \frac{I_2^2}{I'^2} R_2 = \left(\frac{N_1}{N_2}\right)^2 R_2 \rightarrow \text{Add this to } 1^\circ \text{ side}$$

$$\& X'_2 = \left(\frac{N_1}{N_2}\right)^2 X_2$$


$$I_2^2 X_2 = I'^2 (X'_2)$$

$$X'_2 = \frac{I_2^2 X_2}{I'^2} = \left(\frac{N_1}{N_2}\right)^2 X_2$$

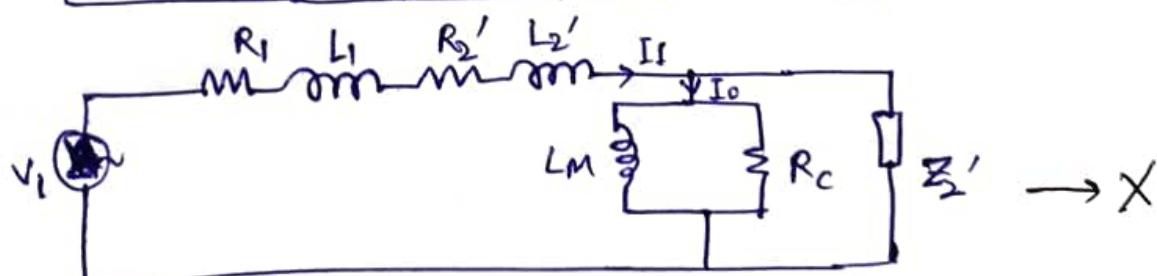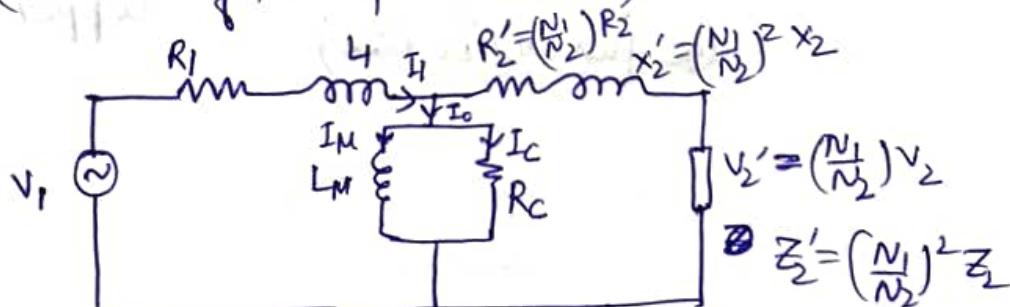So, equivalent circuit:
 (no need of transformer now)



Now, I_o is very small

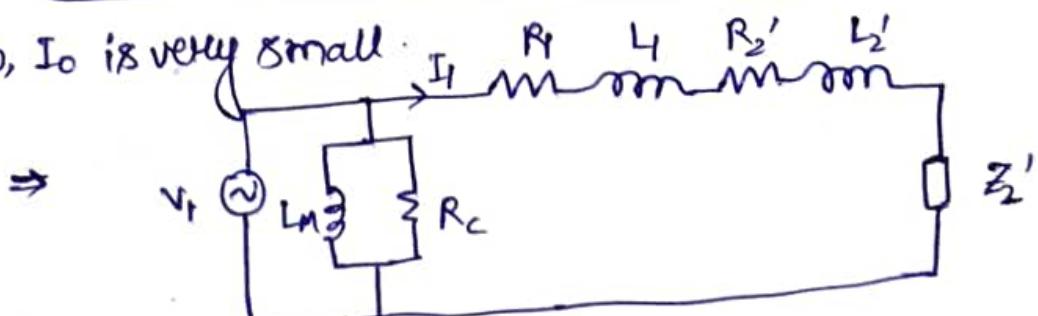


Further,

$$= \left(R_1 + \left(\frac{N_1}{N_2}\right)^2 R_2 \right)$$

$$R_1 + R_2' = R_{01}$$
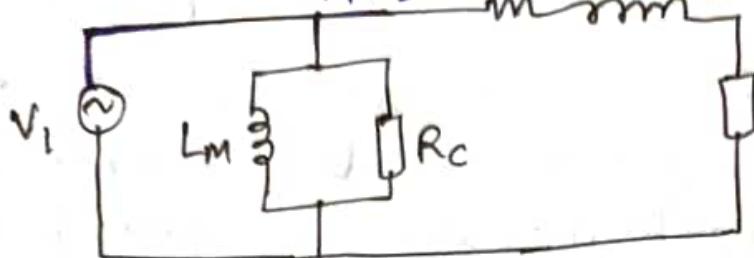
$$jX_{01} = j(X_1 + X_2') = j\left(X_1 + \left(\frac{N_1}{N_2}\right)^2 X_2\right)$$



← Equivalent circuit w.r.t. Primary

↳ We can construct equivalent circuit w.r.t. Secondary also.

→ To determine transformer properties:




① No load test: Whole I_1 will be in the form of I_0 . So, we can (copper loss negligible) measure L_m and R_c . (Core loss)

② Short circuit test: Short circuit the load.

(core loss
negligible)

Voltage supply to them be very less.
Core loss is negligible; & we can measure
(b/c flux will be less) copper loss.

Δ/Δ and Δ/Y Transformations

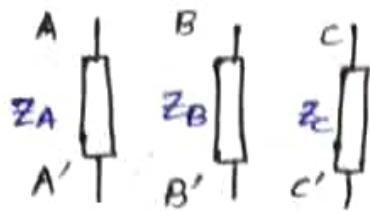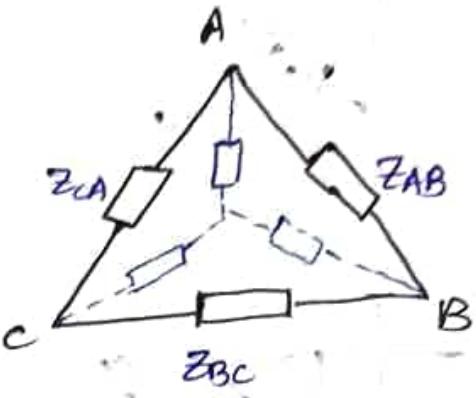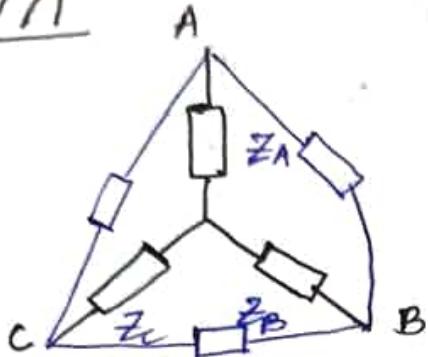 Δ/Y 

Between A and B,

$$Z_A + Z_B = \frac{Z_{AB} [Z_{BC} + Z_{CA}]}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (1)}$$

Between B and C,

$$Z_B + Z_C = \frac{Z_{BC} [Z_{AB} + Z_{CA}]}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (2)}$$

Between C and A,

$$Z_C + Z_A = \frac{Z_{CA} [Z_{AB} + Z_{BC}]}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (3)}$$

Δ/Y Transformation:

 $Z_{AB}, Z_{BC}, Z_{CA} \rightarrow$ Known $Z_A, Z_B, Z_C \rightarrow$ to be found

$$\textcircled{1} + \textcircled{2} + \textcircled{3} \Rightarrow$$

$$Z_A + Z_B + Z_C = \frac{Z_{AB} Z_{CA} + Z_{BC} Z_{AB} + Z_{CA} Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}} \quad \text{--- (4)}$$

$$\textcircled{4} - \textcircled{2} \Rightarrow Z_A = \frac{Z_{AB} Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_A = \frac{Z_{AB} Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}} \quad - \textcircled{5}$$

Similarly,

$$Z_B = \frac{Z_{BC} Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}} \quad - \textcircled{6}$$

$$Z_C = \frac{Z_{CA} Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}} \quad - \textcircled{7}$$

Y / Δ transformation:

$Z_A, Z_B, Z_C \rightarrow$ Known

$Z_{AB}, Z_{BC}, Z_{CA} \rightarrow$ to be found

$$\textcircled{5} \times \textcircled{6} + \textcircled{6} \times \textcircled{7} + \textcircled{7} \times \textcircled{5} \Rightarrow$$

$$Z_A Z_B + Z_B Z_C + Z_C Z_A = \frac{Z_{AB} Z_{BC} Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}} \quad - \textcircled{8}$$


$$\frac{\textcircled{8}}{\textcircled{5}} \Rightarrow Z_A + Z_B + \frac{Z_A Z_B}{Z_C} = Z_{AB}$$

Similarly,


$$Z_{BC} = Z_B + Z_C + \frac{Z_B Z_C}{Z_A}$$

$$Z_{CA} = Z_C + Z_A + \frac{Z_C Z_A}{Z_B}$$

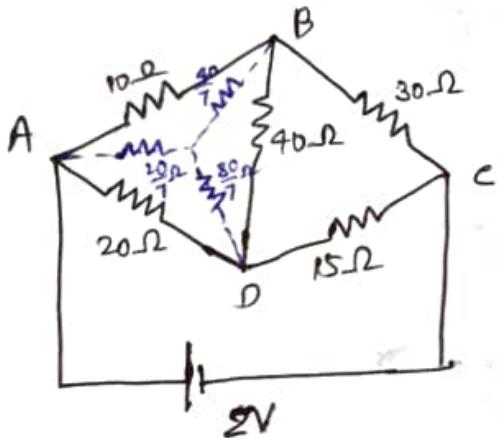Q) Find the equivalent resistance across the terminals A and C.




Soln:

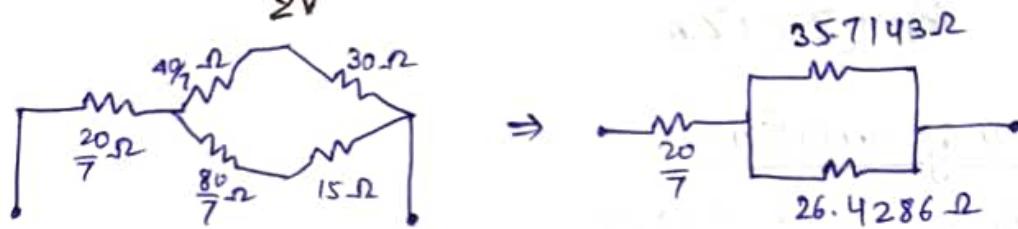



$$\Rightarrow \frac{20}{7} \parallel 26.4286 \Omega$$

$$R_{eq} = 18.046 \Omega$$

Q) Calculate eq. resistance b/w A & B.

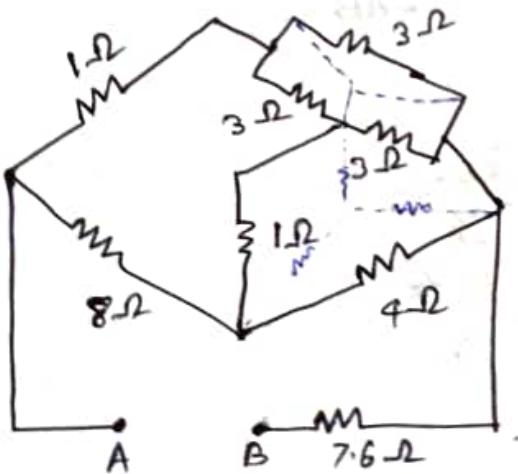


Soln:


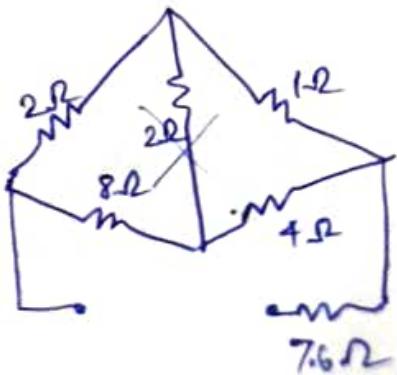
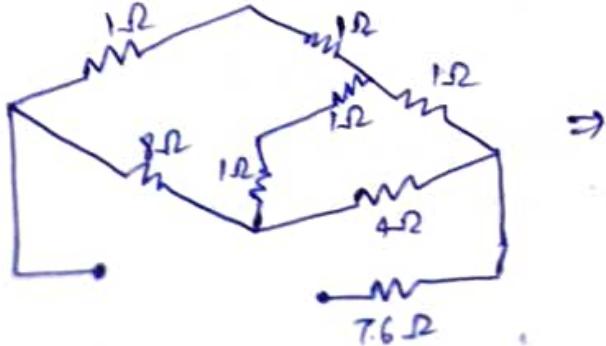


$$R_{eq} = 11.7 \Omega$$

Q1 Find the current i .

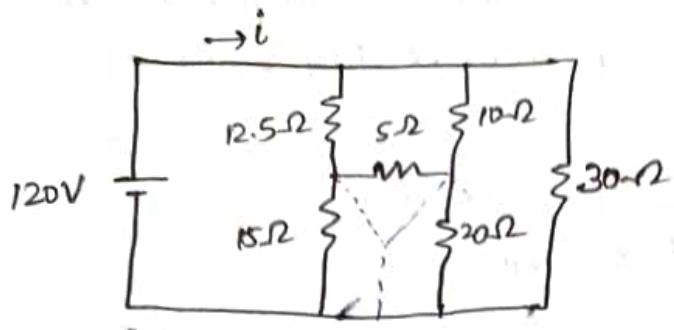

Soln:

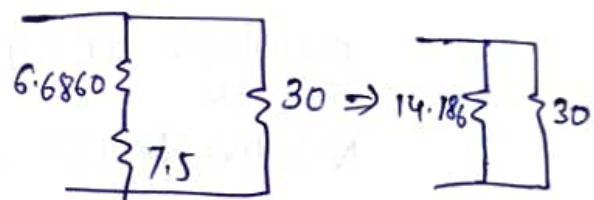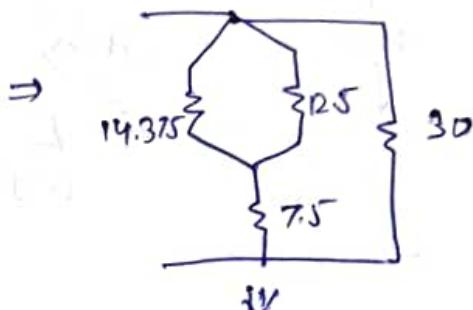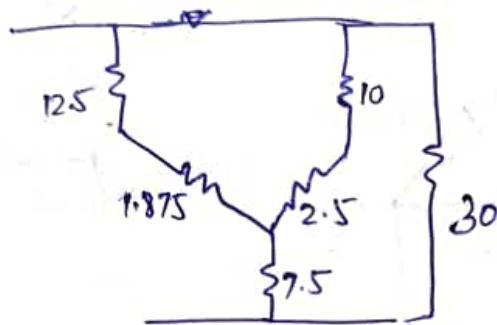


$$R_{eq} = 9.6316 \Omega$$


$$i = \frac{120 \text{ V}}{9.6316 \Omega} = 12.459 \text{ A.}$$

Q2 Find the Resistance b/w A and B.

(a)

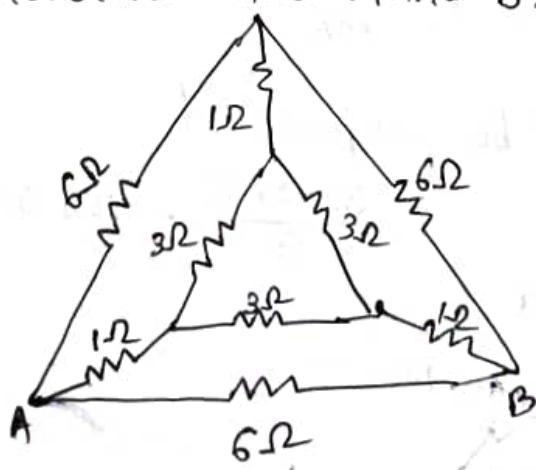


$$\text{Ans: } R_{AB} = 2\Omega$$

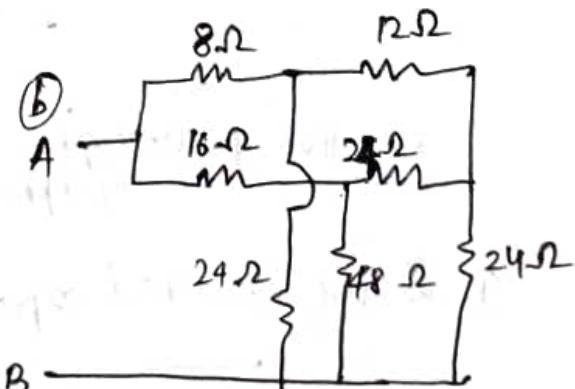

$$R_{eq} = 16\Omega$$

Mesh/Loop Current Method

② Network containing independent voltage sources and impedances

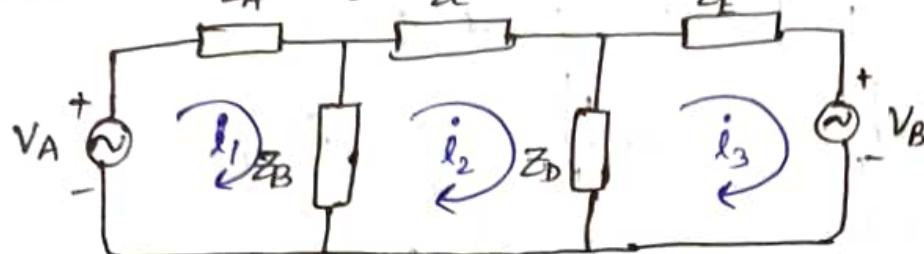

Loop 1:

$$V_A = Z_A i_1 + Z_B (i_1 - i_2) = i_1 (Z_A + Z_B) + i_2 (-Z_B)$$

Loop 2:

$$0 = Z_C i_2 + Z_D (i_2 - i_3) + Z_B (i_2 - i_1) = i_2 (-Z_B) + i_2 (Z_B + Z_C + Z_D) + i_3 (-Z_D)$$

Loop 3:

$$-V_B = (i_3 - i_2) Z_D + i_3 Z_E$$

$$\Rightarrow -V_B = i_2 (-Z_D) + i_3 (Z_D + Z_E)$$

$$\begin{bmatrix} V_A \\ 0 \\ -V_B \end{bmatrix} = \begin{bmatrix} Z_A + Z_B & -Z_B & 0 \\ -Z_B & Z_B + Z_C + Z_D & -Z_D \\ 0 & -Z_D & Z_D + Z_E \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$Z_{ii} \rightarrow$ sum of all impedances through which loop current i_i is flowing.

$Z_{ij} \rightarrow$ sum of all impedances common to i_i and i_j (+ve if both are in same direction, else -ve)


$V_i \rightarrow$ +ve if voltage source drives the current in the same direction as the loop current, else negative.

$$I_1 = \frac{\Delta_1}{\Delta}, I_2 = \frac{\Delta_2}{\Delta}, I_3 = \frac{\Delta_3}{\Delta} \text{ where}$$

$$\Delta = \begin{vmatrix} (Z_A + Z_B) & -Z_B & 0 \\ -Z_B & (Z_B + Z_C + Z_D) & -Z_D \\ 0 & -Z_D & Z_D + Z_E \end{vmatrix}, \quad \Delta_1 = \begin{vmatrix} V_A & -Z_B & 0 \\ 0 & (Z_B + Z_C + Z_D) & -Z_D \\ -V_B & -Z_D & Z_D + Z_E \end{vmatrix}, \quad \Delta_2 = \begin{vmatrix} Z_A + Z_B & V_A & 0 \\ -Z_B & 0 & -Z_D \\ 0 & -V_B & (Z_D + Z_E) \end{vmatrix},$$

$$\Delta_3 = \begin{vmatrix} Z_A + Z_B & -Z_B & V_A \\ -Z_B & (Z_B + Z_C + Z_D) & 0 \\ 0 & -Z_D & -V_B \end{vmatrix}$$


Super Mesh / Super Loop:

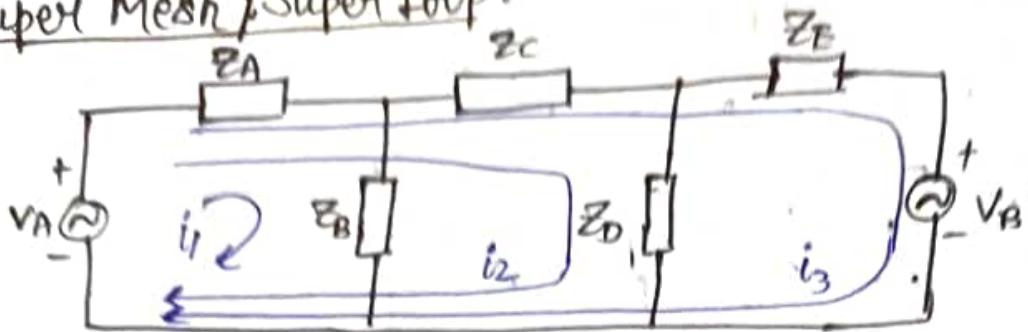

$$\text{Loop 1: } V_A = [i_1 + i_2 + i_3] Z_A + i_1 Z_B$$

$$\text{Loop 2: } V_A = [i_1 + i_2 + i_3] Z_A + [i_2 + i_3] Z_C + i_2 Z_D$$
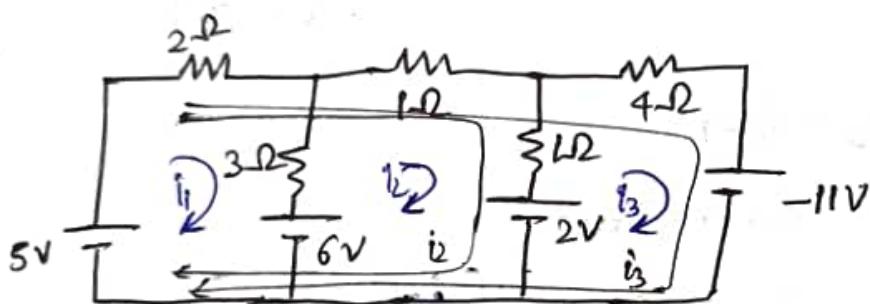
$$\text{Loop 3: } V_A - V_B = [i_1 + i_2 + i_3] Z_A + [i_2 + i_3] Z_C + i_3 Z_E$$



$$\text{Sdn: } \begin{bmatrix} -1 \\ 4 \\ 13 \end{bmatrix} = \begin{bmatrix} 5 & -3 & 0 \\ -3 & 5 & -1 \\ 0 & -1 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5 & -3 & 0 \\ -3 & 5 & -1 \\ 0 & -1 & 5 \end{vmatrix} = 24(5) + 3(-15) = 120 - 45 = 75$$

$$\Delta_1 = \begin{vmatrix} -1 & -3 & 0 \\ 4 & 5 & -1 \\ 13 & -1 & 5 \end{vmatrix} = -24 + 99 = 75$$

$$\Delta_2 = \begin{vmatrix} 5 & -1 & 0 \\ 3 & 4 & -1 \\ 0 & 13 & 0 \end{vmatrix} = -165 + 15 = 150$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{75}{75} = 1 \text{ A}$$

$$\Delta_3 = \begin{vmatrix} 5 & -3 & -1 \\ -3 & 5 & 4 \\ 0 & -1 & 13 \end{vmatrix} = 345 - 117 \cdot 3 = 225$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{150}{75} = 2 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{225}{75} = 3 \text{ A}$$

By super mesh,

$$\begin{bmatrix} -1 \\ 3 \\ 16 \end{bmatrix} = \begin{bmatrix} 5 & 2 & 2 \\ 2 & 4 & 3 \\ 2 & 3 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$


$$\Rightarrow i_1 = -1 \text{ A}$$

$$i_2 = -1 \text{ A}$$

$$i_3 = 3 \text{ A}$$

Q obtain the voltage using mesh method.
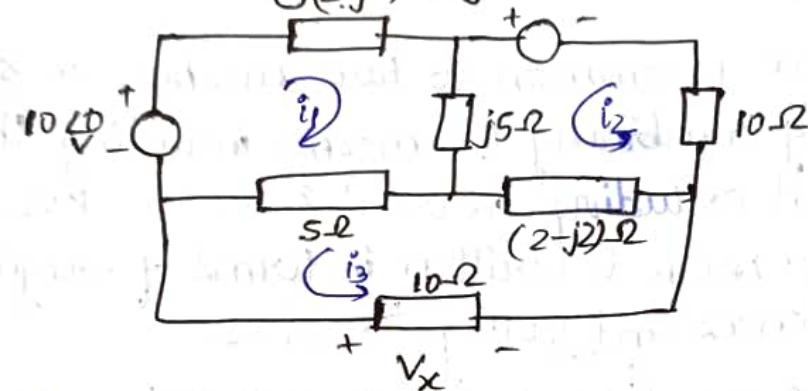
$$(2-j2) \cdot 2 \quad 5 \angle 30^\circ V = 4 \cdot 33 + j25$$



Soln:

$$\begin{bmatrix} 10 \\ 4.33 + j2.5 \\ 0 \end{bmatrix} = \begin{bmatrix} 7 + j3 & j5 & 5 \\ j5 & 12 + j3 & -(2-j2) \\ 5 & -(2-j2) & 17 - j2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$$\Rightarrow i_3 = 0.4353 \angle 165.87^\circ \text{ A}$$


$$V_x = 10 i_3$$

$$= 4.353 \angle 165.87^\circ \text{ A}$$

- ⑥ Network of independent current and voltage source and impedances
- if possible, convert the current source into voltage source.
 - if the current source is common only to one mesh, then the mesh current is given by the source current.
 - otherwise, define voltage across current source and write the mesh equations as if these source voltages were known.
 - Augment the set of equations with one equation for each current source expressed as difference b/w two mesh currents, or
- or If a current source is common to two meshes, a super mesh is obtained by combining the meshes including the current source but excluding current source. KVL equation around the super mesh is written in terms of original mesh currents, impedances and voltage sources.

Augment with one equation for each current sources, expressed as difference b/w two mesh current.

Q1

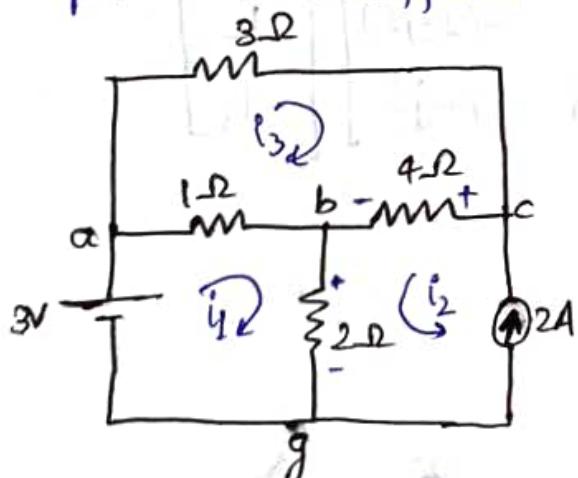

Find I_{ab} and V_{cg} .

$$\text{Solt: } i_2 = 2A$$

$$3 = 1(i_1 - i_3) + 2(i_1 + i_2)$$

$$0 = 3i_3 + 4(i_3 + i_2) + 1(i_3 - i_1)$$

Solving,

$$3i_1 + i_3 + 2(i_1 + i_2) = 0$$

$$0 = 3i_3 + 4(i_3 + i_2) + 1(i_3 - i_2)$$

$$3 = i_1 - i_3 + 2i_1 + 4$$

$$-1 = 3i_1 - i_3$$

$$0 = 3i_3 + 4i_3 + 8 + i_3 - 4$$

$$-8 = 8i_3 - i_1$$

$$-25 = 23i_3$$


$$\Rightarrow i_3 = \frac{-25}{23} = -1.0869A$$

$$i_1 = \frac{i_3 - 1}{3} = -0.6956A$$

$$i_{ab} = 0.3913A$$


$$\begin{aligned}\therefore V_{cg} &= 2(i_1 + i_2) + 4(i_2 + i_3) \\ &= 2(2 - 0.6956) + 4(2 - 1.0869) \\ &= 6.2612V\end{aligned}$$

Q1

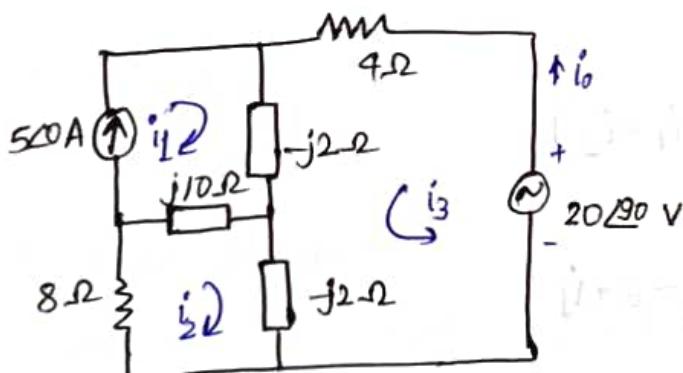

An8:
 $i_o = 6.1201$ [144.78 A]

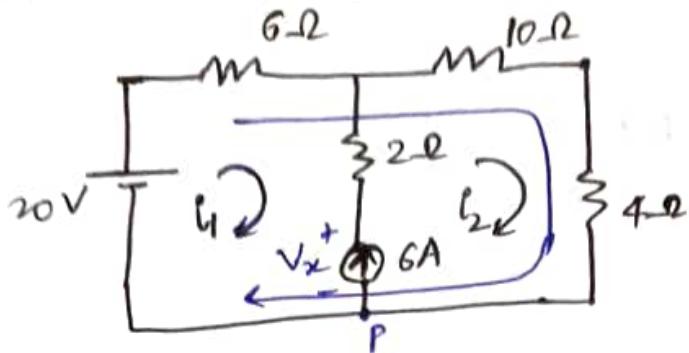Q) Using mesh current method, obtain i_1 and i_2 .



$$\text{Sqn: } 20 - V_x = 6i_1 + 2[i_1 - i_2] \quad \text{--- (1)}$$

$$V_x = 10i_2 + 4i_2 + 2[i_2 - i_1] \quad \text{--- (2)}$$

Using KCL at P,

$$i_2 = 6 + i_1 \quad \text{--- (3)}$$

Put (3) & (2) in (1)

$$20 - 6i_1 - 2i_1 + 2(6 + i_1) = 10(6 + i_1) + 4(6 + i_1) + 2(6 + i_1) - 2i_1$$

$$\Rightarrow 20 - 6i_1 = 60 + 24 + 12 + 14i_1$$

$$\Rightarrow 20i_1 = -64 \Rightarrow i_1 = -\frac{64}{20} = -\frac{32}{10} = -3.2 \text{ A}$$

$$\text{and, } i_2 = 6 + i_1 = 2.8 \text{ A}$$


Using super mesh,

$$20 - V_x = 6i_1 + 2(i_1 - i_2)$$

$$20 = 6i_1 + 14i_2$$

$$\text{and using KCL, } i_2 = 6 + i_1$$

Q

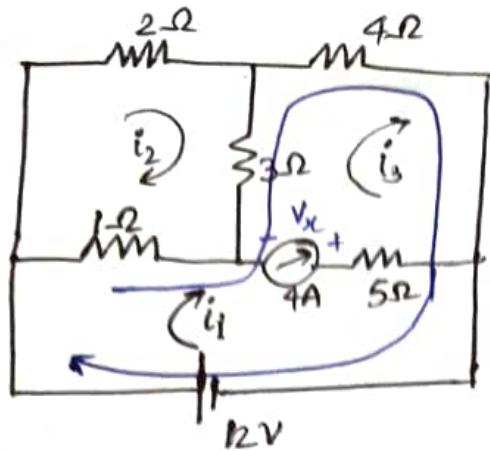

$$0 = 2i_2 + 3(i_2 - i_3) + 1(i_2 - i_1) \quad \text{---} ①$$

$$-V_x = 4i_3 + 5(i_3 - i_1) + 3(i_3 - i_2) \quad \text{---} ②$$

$$V_x + 12 = 1(i_1 - i_2) + 5(i_1 - i_3) \quad \text{---} ③$$

and using KCL, $i_1 = 4 + i_3$

$$① \Rightarrow 6i_2 = i_1 + 3i_3$$

$$② \Rightarrow V_x + 12i_3 = 5i_1 + 3i_2$$

$$③ \Rightarrow V_x + 12 + i_2 = 6i_1 - 5i_3$$

$$\Rightarrow i_1 = 6A$$

$$i_2 = 2A$$

$$i_3 = 2A$$


Using super mesh

~~$$-12 = 12i_3 + 2i_2 + 8i_1 \quad 6i_2 = i_1 + 3i_3 \quad \text{---} ①$$~~

$$12 = 1[i_1 - i_2] + 3[i_3 - i_2] + 4i_3 \quad \text{---} ②$$

$$\text{KCL: } i_1 = 4 + i_3 \quad \text{---} ③$$

Q) Find the mesh current.

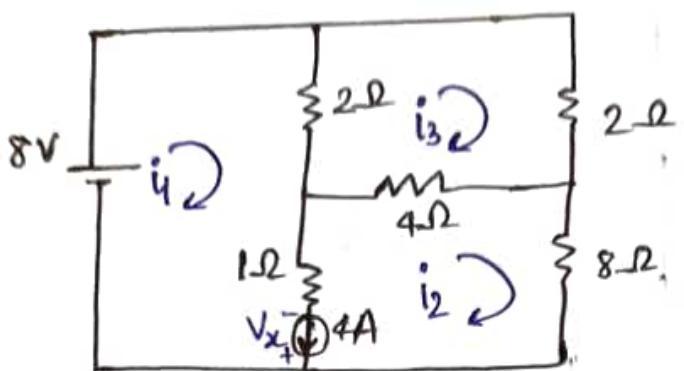

Soln: Loop 1: $2(i_1 - i_3) + 1(i_1 - i_2) = 8 + V_x$

Loop 2: $-V_x = 1(i_2 - i_1) + 4(i_2 - i_3) + 8i_2$


Loop 3: $0 = 2(i_3 - i_1) + 2i_3 + 4(i_3 - i_2)$

and, $i_4 = i_1 - i_2$

$$\Rightarrow i_4 = \frac{88}{19} \text{ A}, i_2 = \frac{12}{19} \text{ A}, i_3 = \frac{28}{19} \text{ A}, V_x = -\frac{28}{19} \text{ V.}$$

Mesh/Loop Analysis

Q1 Find I.

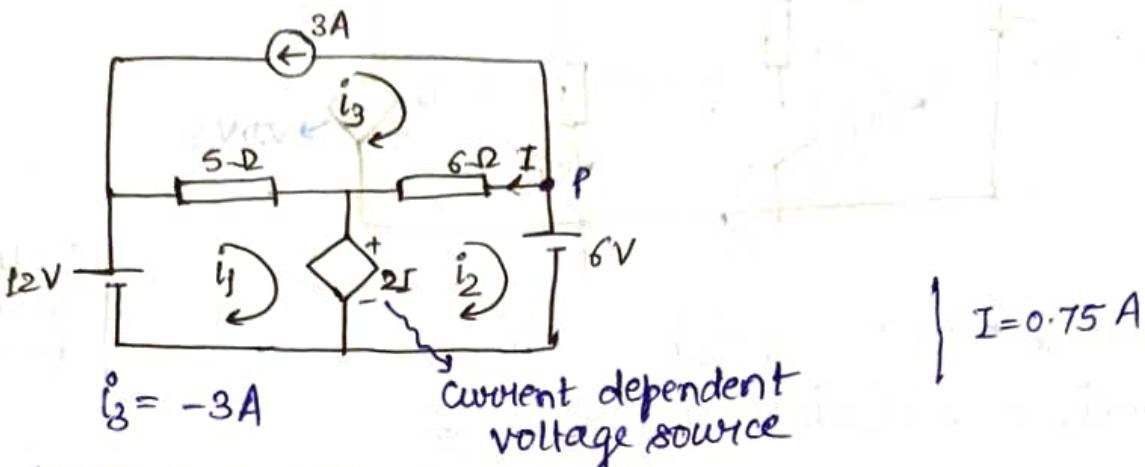

Soln: $i_3 = -3 \text{ A}$ current dependent voltage source

$$\text{Loop 1} \Rightarrow 12 - 2I = 5 [i_1 - i_3]$$

$$\text{Loop 2} \Rightarrow -6 + 2I = 6(i_2 + i_3)$$

$$\text{Loop 3} \Rightarrow i_3 = 3 \text{ A}$$

$$\text{KCL} \Rightarrow I = i_3 - i_2 \text{ (at P)}$$

$$i_1 = -0.9 \text{ A}$$

$$i_2 = -(15/4) \text{ A}$$


$$I = 0.75 \text{ A}$$

② Network containing DEPENDENT sources

When a network contains a dependent source, the mesh equations are written in the usual way.

A dependent source is treated exactly like an independent source in obtaining the mesh eq's. Then an eq for each dependent source is written in terms of one or more mesh currents. These values are substituted into the main mesh eq's from which mesh currents can be obtained.

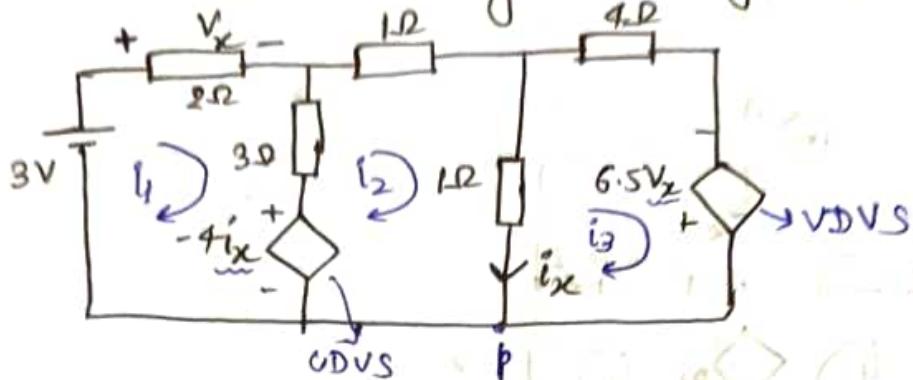Q) Obtain the current i_x and voltage V_x using mesh current method.



$$\begin{cases} i_1 = 1A \\ i_2 = 2A \\ i_3 = 3A \end{cases}$$

$$3 + 4i_x - V_x = 3(i_1 - i_2) \quad \text{---(1)}$$

$$-4i_x = 3(i_2 - i_1) + 1(i_2 - i_3) \quad \text{---(2)}$$

$$6.5V_x = 1(i_3 - i_2) + 4i_3 \quad \text{---(3)} = 15 - 5i_2 \quad \leftarrow \text{Eqn 1}$$

$$\begin{aligned} \text{KCL: } i_x &= i_2 - i_3 & \text{---(4)} \Rightarrow i_3 &= i_2 - i_x & \text{---(4)} \\ (\text{at } p) \quad 2i_1 &= V_x & \text{---(5)} \Rightarrow i_1 &= \frac{V_x}{2} & \text{---(5)} \end{aligned}$$

$$\text{---(1)} \Rightarrow 3 + 4i_x - V_x = 3i_1 - 3i_2 \Rightarrow 3 + 4i_x = 5i_1 - 3i_2 \Rightarrow 3 + 7i_2 = 5i_1 + 4i_x \quad \text{---(i)}$$

$$\text{---(2)} \Rightarrow -4i_x = 4i_2 - 3i_1 + i_x - i_2 \quad \text{---(ii)} \Rightarrow 4i_x = 3i_1 - 3i_2 - i_x \quad \text{---(iii)}$$

$$\Rightarrow 5i_x = 3i_1 - 3i_2 \Rightarrow 8i_2 - 5i_3 = 3i_1 \quad \text{---(ii)}$$

$$\text{---(3)} \Rightarrow 6.5V_x = 5i_2 - 5i_x - i_2$$

$$\Rightarrow 6.5V_x = 4i_2 - 5i_x \Rightarrow 13i_1 = 4i_2 - 5i_x + 5i_3$$


$$\Rightarrow i_1 = 1A, i_2 = 2A, i_3 = 3A \quad \boxed{\Rightarrow 13i_1 + i_2 = 5i_3} \quad \text{---(iii)}$$

$$\Rightarrow i_x = i_2 - i_3 = -1A$$

$$V_x = 2i_1 = 2V$$

NODE VOLTAGE METHOD

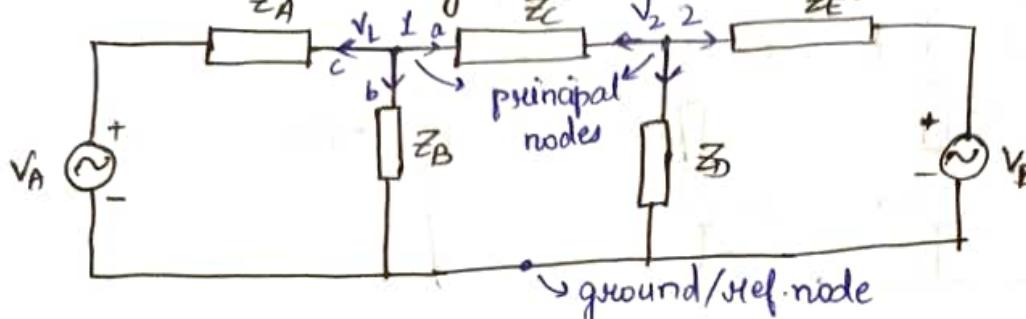① Network containing independent voltage sources and impedances



- 3 total nodes
- ↳ 2 principal nodes
- ↳ 1 reference node
- Node generally means principal nodes.

$$\text{KCL at node 1} \Rightarrow \frac{V_1 - V_A}{Z_A} + \frac{V_1 - V_2}{Z_C} + \frac{V_1 - V_2}{Z_B} = 0 \quad | \# \text{Node: junction of 3 or more branches.}$$

$$\Rightarrow \left[\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right] V_1 + \left[-\frac{1}{Z_C} \right] V_2 = \frac{V_A}{Z_A}$$

$$\text{KCL at node 2} \Rightarrow \frac{V_2 - V_A}{Z_C} + \frac{V_2 - V_B}{Z_E} + \frac{V_2 - V_B}{Z_D} = 0 \Rightarrow \left[-\frac{1}{Z_C} \right] V_1 + \left[\frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right] V_2 = \frac{V_B}{Z_E}$$

$$\Rightarrow \begin{bmatrix} \left(\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right) & -\frac{1}{Z_C} \\ -\frac{1}{Z_C} & \frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_A}{Z_A} \\ \frac{V_B}{Z_E} \end{bmatrix}$$

$| \frac{1}{Z} = y : \text{Admittance}$

$\frac{1}{Z_{ii}} = y_{ii} \rightarrow \text{sum of all admittances connected to node } i$

$\frac{1}{Z_{ij}} = y_{ij} \rightarrow \text{negative of sum of all admittances connected b/w nodes } i \text{ and } j$

$I_i \rightarrow +ve, \text{if the source drives the current into node } i,$
 $\text{else, } -ve.$


→ If $n = \text{total no. of nodes (including ref. node)}, (n-1)$ equations have to be solved.

$$\therefore V_1 = \frac{\Delta_1}{\Delta}; V_2 = \frac{\Delta_2}{\Delta} \text{ where }$$

replaced by current

$$\Delta = \begin{vmatrix} \left(\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right) & -\frac{1}{Z_C} \\ -\frac{1}{Z_C} & \left(\frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right) \end{vmatrix}, \Delta_1 = \begin{vmatrix} \frac{V_A}{Z_A} & -\frac{1}{Z_C} \\ \frac{V_B}{Z_E} & \left(\frac{1}{Z_C} + \frac{1}{Z_D} + \frac{1}{Z_E} \right) \end{vmatrix}, \Delta_2 = \begin{vmatrix} \frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} & \frac{V_A}{Z_A} \\ -\frac{1}{Z_C} & \frac{V_B}{Z_E} \end{vmatrix}$$

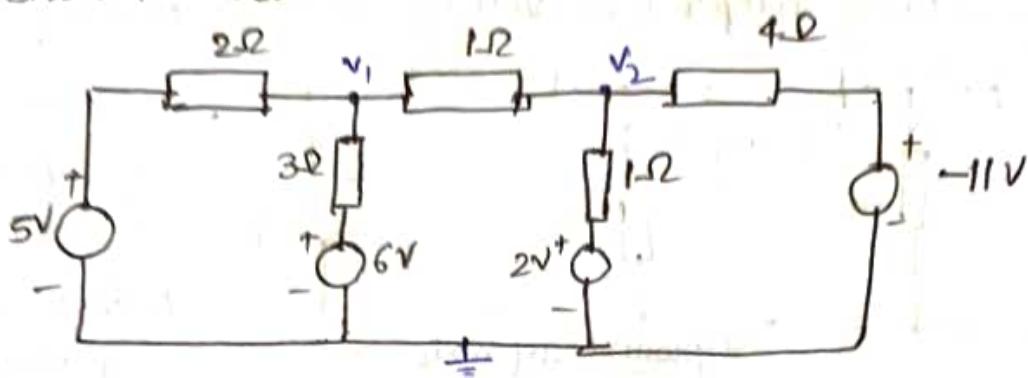Using node voltage method, obtain the branch currents for the circuit shown below.



Soln:

$$\begin{bmatrix} \frac{1}{2} + \frac{1}{3} + \frac{1}{1} & -\frac{1}{1} \\ \frac{1}{1} & \frac{1}{1} + \frac{1}{1} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \frac{5}{2} + \frac{6}{3} \\ -\frac{11}{4} + \frac{2}{1} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \frac{11}{6} & -1 \\ -1 & \frac{9}{4} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} \frac{9}{2} \\ -\frac{3}{4} \end{bmatrix}$$

(1) ~~$\Delta = 3 \cdot 125$~~

$$\frac{11}{6}v_1 - v_2 = \frac{9}{2}$$

$$-v_1 + \frac{9}{4}v_2 = -\frac{3}{4}$$

$$\frac{(-1 + \frac{33}{8})v_2}{(-1 + \frac{33}{8})v_2} = -\frac{11}{8} + \frac{9 \times 4}{2 \times 4} = \frac{25}{8}$$

$$\Rightarrow v_2 = \frac{-25}{25} = 1V$$

$$\Delta = 3 \cdot 125$$

$$\Delta_1 = 9 \cdot 375$$


$$\Delta_2 = 3 \cdot 125$$

$$v_1 = \frac{\Delta_1}{\Delta} = 3V$$

$$v_2 = \frac{\Delta_2}{\Delta} = 1V$$

$$\text{and, } v_1 = \frac{9}{4}v_2 + \frac{3}{4} = \frac{12}{4} = 3V$$

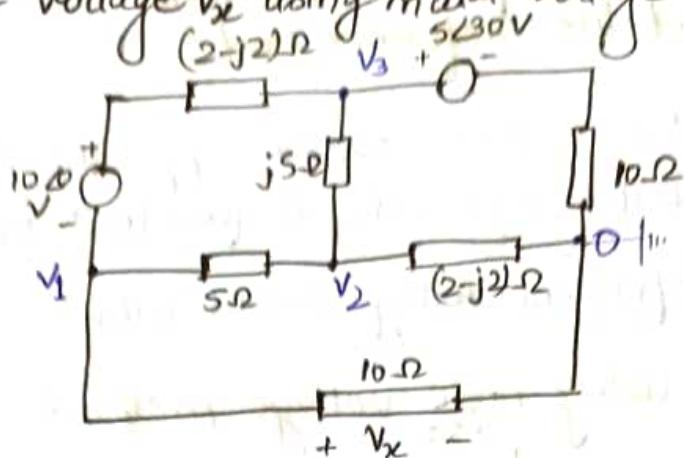Q) Obtain the voltage V_x using modal voltage method.



$$\text{Node 1: } \frac{V_1 - V_2}{5} + \frac{V_1 + 10 \angle 0 - V_3}{2-j2} + \frac{V_1}{10} = 0$$

$$\text{Node 2: } \frac{V_2 - V_1}{5} + \frac{V_2 - 0}{2-j2} + \frac{V_2 - V_3}{j5} = 0$$

$$\text{Node 3: } \frac{V_3 - 10 \angle 0 - V_1}{2-j2} + \frac{V_3 - V_2}{j5} + \frac{V_3 - 5L30 - 0}{10} = 0$$

$$\Rightarrow \begin{cases} \left(\frac{1}{5} + \frac{1}{2-j2} + \frac{1}{10}\right)V_1 + \left(-\frac{1}{5}\right)V_2 + \left(\frac{1}{2-j2}\right)V_3 = -\frac{10 \angle 0}{2-j2} \\ \left(-\frac{1}{5}\right)V_1 + \left(\frac{1}{5} + \frac{1}{2-j2} + \frac{1}{j5}\right)V_2 + \left(-\frac{1}{j5}\right)V_3 = 0 \\ \left(-\frac{1}{2-j2}\right)V_1 + \left(-\frac{1}{j5}\right)V_2 + \left(\frac{1}{2-j2} + \frac{1+j}{j5-10}\right)V_3 = \frac{10 \angle 0}{2-j2} + \frac{5L30}{10} \end{cases}$$

$$\Rightarrow \begin{bmatrix} \left(\frac{1}{5} + \frac{1}{2-j2} + \frac{1}{10}\right) & -\left(\frac{1}{5}\right) & \left(\frac{1}{2-j2}\right) \\ \left(-\frac{1}{5}\right) & \left(\frac{1}{5} + \frac{1}{2-j2} + \frac{1}{j5}\right) & \frac{1}{j5} \\ \left(-\frac{1}{2-j2}\right) & \left(-\frac{1}{j5}\right) & \left(\frac{1}{2-j2} + \frac{1}{j5} + \frac{1}{10}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -\frac{10 \angle 0}{2-j2} \\ 0 \\ \frac{10 \angle 0}{2-j2} + \frac{5L30}{10} \end{bmatrix}$$


$$\Delta = 0.0694 + j0.0324 ; \Delta_1 = -0.3276 - j0.0633$$

$$\therefore \Delta_{12} = \therefore V_x = V_1 = \frac{\Delta_1}{\Delta} = 4.3564 \angle 165.91^\circ$$

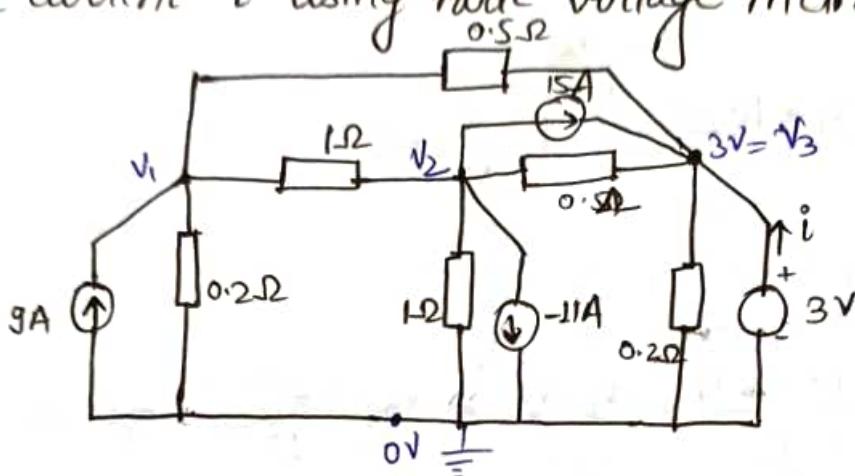
b) Network containing an independent VOLTAGE source directly b/w a principal node and the reference node

When an independent voltage source appears directly b/w a principal node & the ref. node, it fixes that node voltage to be at the independent voltage source value.

Q) Find the current 'i' using node voltage method -



Soln:

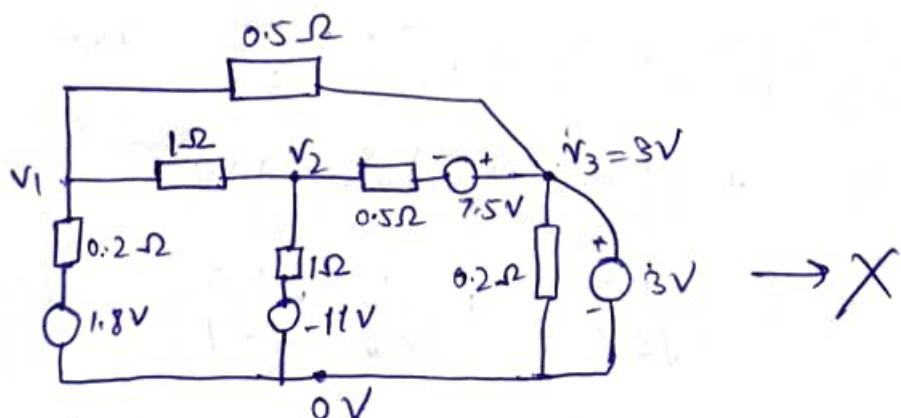

$$\begin{cases} V_3 = 3V \\ V_1 = 2V \\ V_2 = 1V \\ i = 6A \end{cases}$$

$$\text{Node 1: } \frac{V_1 - 0}{0.2} + g + \frac{V_1 - 3}{0.5} + \frac{V_1 - V_2}{1} = 0$$

$$\text{Node 2: } \frac{V_2 - V_1}{1} + \frac{V_2 - 3}{0.5} + 11A + 15A + \frac{V_2 - 3}{0.2} = 0$$

$$\text{Node 3: } \frac{3 - V_1}{0.5} + \frac{3 - V_2}{0.5} + \frac{3 - V_3}{0.2} + \frac{3 - V_3}{0.2} = 0$$

$$V_3 = 3V$$

$$\Rightarrow \begin{cases} (5+2+1)v_1 - v_2 = 9+6 \\ -v_1 + 4v_2 = 2 \end{cases}$$

$$\Rightarrow \begin{bmatrix} 8 & -1 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 15 \\ 2 \end{bmatrix}$$

$$\Rightarrow \begin{cases} 8v_1 - v_2 = 15 \\ -v_1 + 4v_2 = 2 \end{cases} \times 4$$

$$31v_1 = 62$$

$$\Rightarrow v_1 = 2 \text{ V}$$

$$v_2 = 8v_1 - 15 = 16 - 15 = 1 \text{ V}$$

At node 3:

$$-i + \frac{3}{0.2} + \frac{3-v_2}{0.5} - 15 + \frac{3-v_1}{0.5} = 0$$

$$\Rightarrow i = 15 + 6 - 2 - 15 + 6 - 4 \\ = 6 \text{ A}$$


② Network containing an independent VOLTAGE source directly b/w principal nodes

When an independent voltage source appears directly b/w two principal nodes, the voltage at one node will be fixed above the other by the independent voltage source. Both KCL and KVL are applied to find the node voltages.

• Define a current through the voltage source and write the nodal eqns as if this source is known.

OR The 2 principal nodes b/w which the indep. voltage source is connected form a SUPERNODE. A supernode is formed by enclosing the dep. / indep. voltage source connected directly in b/w the principal nodes & any elements connected in || with it. The KCL for the supernode is written in terms of original node voltages and impedances.

Q) Find the node voltages. supernode

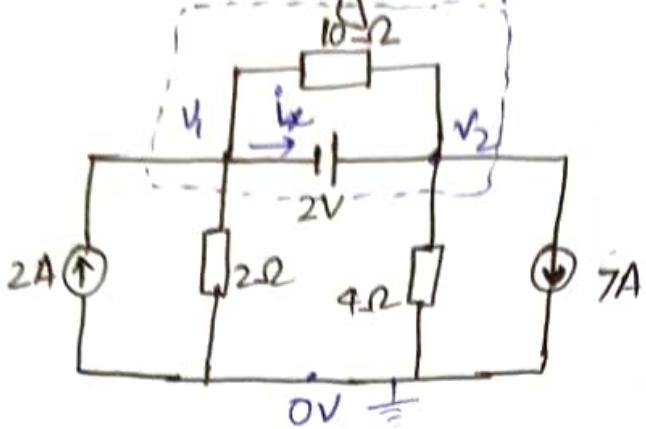

Soln: $V_1 + 2 = V_2$ (KVL)

Node 1: $-2 + \frac{V_1}{2} + i_x + \frac{V_1 - V_2}{10} = 0 \quad \text{---(1)}$

Node 2: $7 + \frac{V_2}{4} - i_x + \frac{V_2 - V_1}{10} = 0 \quad \text{---(2)}$

$$\Rightarrow 6V_1 - V_2 + 10i_x = 20,$$

$$-2V_1 + 7V_2 - 20i_x = 140$$

$$5 + \left(\frac{6V_1}{10} - \frac{V_1}{10}\right) + \left(\frac{i_x}{10} + \frac{7}{20}\right)V_2 = 0$$

$$\Rightarrow 5 + \frac{V_1}{2} + \frac{V_2}{4} = 0$$

and optional $\Rightarrow \frac{5 \times 4}{4} \frac{V_1 \times 2}{2} + \frac{V_1 + 2}{4} = 0$

$$\Rightarrow \frac{3}{4}V_1 + \frac{22}{4} = 0$$

$$\Rightarrow V_1 = -\frac{22}{3} = -7.333 \text{ V}$$

$$\text{then } V_2 = V_1 + 2 = -5.333 \text{ V}$$

OR


At the supernode,

$$2 = \frac{V_1}{2} + \frac{V_2}{4} + 7 \rightarrow \text{supernode eqn}$$

(we can get by adding (1) & (2))

KVL: $V_2 = 2 + V_1$

Q) Determine the node voltages.

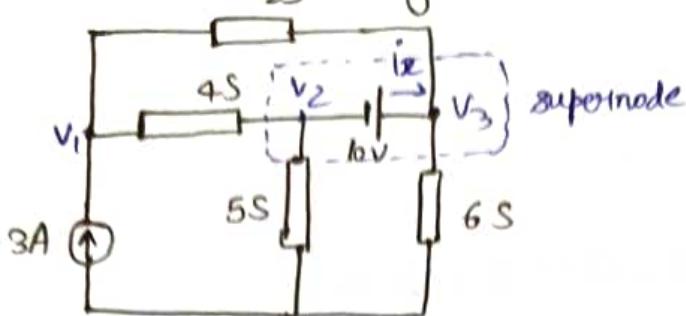

Soln: At node 1:

$$3 = (V_1 - V_2) \cdot 4 + (V_1 - V_3) \cdot 2$$

$$\text{node } 2: (V_2 - V_1) \cdot 4 + V_2 \cdot 5 + i_x = 0 \quad \text{---} ①$$

$$\text{node } 3: i_x = V_3 \cdot 6 + (V_3 - V_1) \cdot 2 \quad \text{---} ②$$

$S = \text{Siemens} = \frac{1}{\Omega}$
unit of admittance

$$\text{KVL: } V_2 + 10 = V_3$$

$$\Rightarrow V_2 = -5.1818 \text{ V}, V_3 = 4.8182 \text{ V}$$

$$V_1 = -1.3485 \text{ V}$$

By supernode


$$\text{node 1: } 3 = (V_1 - V_2) \cdot 4 + (V_1 - V_3) \cdot 2$$

$$\text{at supernode: } V_2 \cdot 5 + V_3 \cdot 6 + (V_3 - V_1) \cdot 2 + (V_2 - V_1) \cdot 4 = 0 \\ \Rightarrow -6V_1 + 9V_2 + 8V_3 = 0$$

$$\text{KVL: } V_2 + 10 = V_3$$

$$\Rightarrow V_1 = -1.3485 \text{ V}, V_2 = -5.1818 \text{ V}, V_3 = 4.8182 \text{ V.}$$

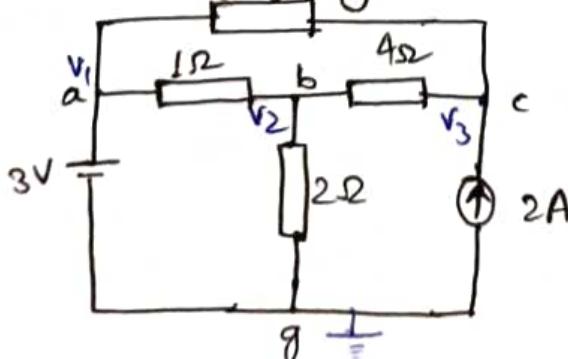Q) Find I_{ab} and V_{cg} using nodal method.



$$\text{Soln: Node 1: } V_1 = 3 \text{ V}$$

$$\text{Node 2: } (V_2 - V_1) + \frac{V_2}{2} + \frac{V_2 - V_3}{4} = 0$$

$$\text{Node 3: } 2 = \frac{(V_3 - V_2)}{4} + \frac{(V_3 - V_1)}{3}$$

$$\Rightarrow V_2 = 2.6088 \text{ V}$$


$$V_3 = 6.2617 \text{ V}$$

$$V_{cg} = V_3 = 6.2617 \text{ V}$$

$$I_{ab} = \frac{(V_1 - V_2)}{1} = 3 - 2.6088 = 0.3912 \text{ A}$$

\rightarrow No supernode (b/c we don't have a voltage source connected directly b/w 2 principal nodes).

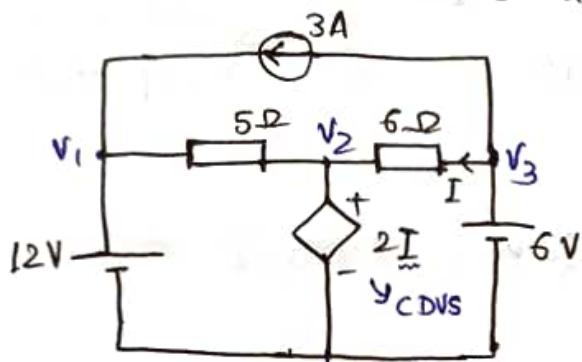Q) Determine the current I using nodal method.



Soln:

$$V_1 = 12 \text{ V} \quad (\text{at node 1})$$

$$V_3 = 6 \text{ V} \quad (\text{at node 3})$$

$$\text{At node 2: } \cancel{\frac{V_1 - V_2}{5}} + \cancel{\frac{V_3 - V_2}{6}} V_2 = 2I$$

$$I = \frac{V_3 - V_2}{6} = \frac{6 - 2I}{6}$$

$$\Rightarrow 8I = 6$$

$$\Rightarrow I = \frac{3}{4} = 0.75 \text{ A}$$

Superposition Theorem

The response in any element of a linear active bilateral network containing multiple independent sources is the algebraic sum of the individual responses due to each independent source acting alone with all other sources replaced by their respective internal impedances, i.e., voltage sources are replaced by short circuits and current sources are replaced by open circuits.

(2) Obtain the voltage

Linear → Superposition principle
→ Homogeneity property

$$v_1(t) \rightarrow [G(\cdot)] \rightarrow y_1(t)$$

$$v_2(t) \rightarrow [G(\cdot)] \rightarrow y_2(t)$$

$$v_1(t) + v_2(t) \rightarrow [G(\cdot)] \rightarrow y_1(t) + y_2(t)$$


$$v_1(t) \rightarrow [] \rightarrow y_1(t)$$

$$\alpha v(t) \rightarrow [] \rightarrow \alpha y(t) \rightarrow \text{Homogeneity property}$$


Bilateral : ~~opposite~~ property remains same in both the
Element polarities (e.g., resistor)

Unilateral : Opposite to bilateral (e.g., diode)
Element

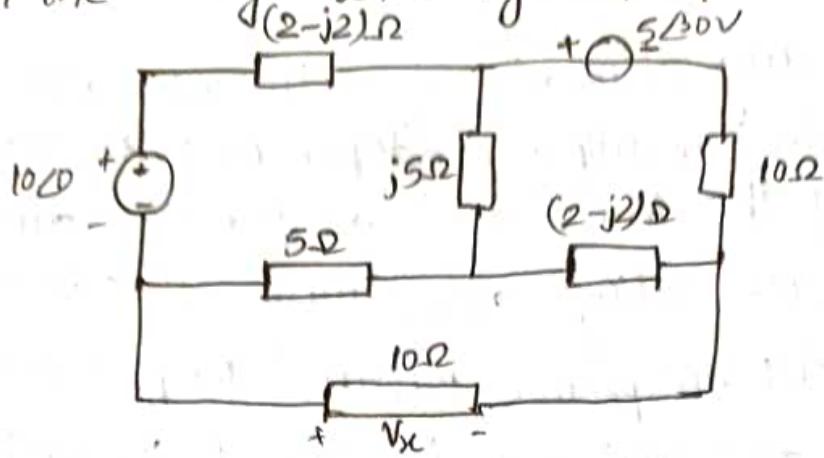Q) Obtain the voltage V_{xc} , using Superposition theorem.



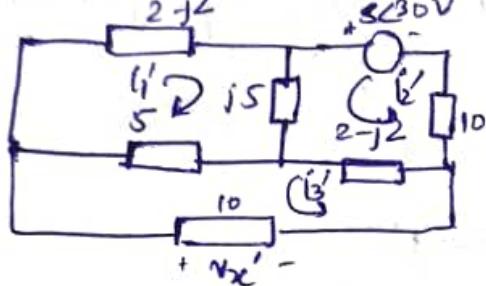
Soln @ When $5\angle 30^\circ$ source alone is acting



$$\begin{bmatrix} (7+j3) & j5 & 5 \\ j5 & (12+j3) & (-2+j2) \\ 5 & (-2+j2) & (17-j2) \end{bmatrix} \begin{bmatrix} i_1' \\ i_2' \\ i_3' \end{bmatrix} = \begin{bmatrix} 0 \\ 5\angle 30^\circ \\ 0 \end{bmatrix}$$

$$\therefore i_3' = \frac{\Delta_3'}{\Delta} = 0.0855 \angle 45.31^\circ \text{ A} \Rightarrow V_{xc}' = 10 \times i_3' = 0.855 \angle 45.31^\circ \text{ V}$$

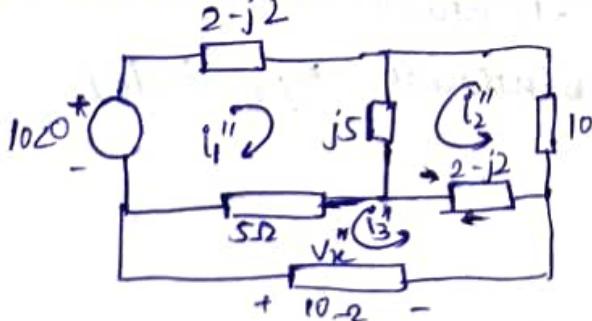(b) Now, when 10V source alone is acting.



$$\begin{bmatrix} (7+j3) & j5 & 5 \\ j5 & (12+j3) & (-2+j2) \\ 5 & (-2+j2) & (17-j2) \end{bmatrix} \begin{bmatrix} i_1'' \\ i_2'' \\ i_3'' \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$


$$\therefore i_3'' = \frac{\Delta_3''}{\Delta} = 0.4844 \angle 74.61^\circ A \Rightarrow V_x'' = 10 \times i_3'' = 4.844 \angle 74.61^\circ V$$

$$i_b = i_3' + i_3'' = 0.0855 \angle 45.31^\circ A + 0.4844 \angle 74.61^\circ A \\ = 0.4353 \angle 165.86^\circ A$$

$$\therefore V_x = 10 \times i_3 = 4.353 \angle 165.86^\circ V$$


OR $V_x = V_x' + V_x'' = 0.855 \angle 45.3 + 4.844 \angle 74.61 = 4.353 \angle 165.86 V$

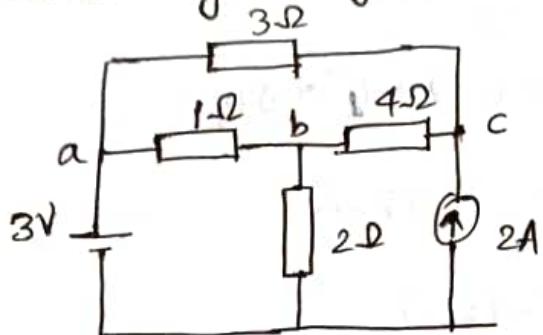Q Find I_{ab} and V_{cg} using superposition theorem.



- Voltage source
↳ short-circuit
- Current source
↳ open circuit
- Short circuit

@ When 3V alone is acting

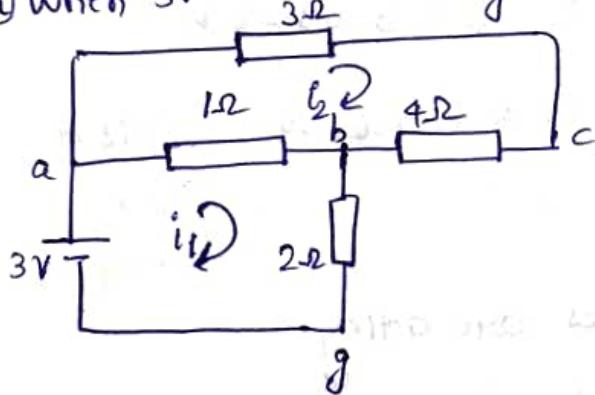

$$\begin{bmatrix} 3 \\ 0 \end{bmatrix} = \begin{bmatrix} 3 & -1 \\ -1 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


$$\Delta = 23, \Delta_1 = 24, \Delta_2 = 3$$

$$\therefore i_1 = \frac{\Delta_1}{\Delta} = 1.0435 A, i_2 = \frac{\Delta_2}{\Delta} = 0.1304 A$$

$$\Rightarrow i_{ab}' = i_1 - i_2 = 0.9131 A$$

$$V_{cg}' = +4(i_2) + 2(i_1) \\ = 2.6086 V$$

⑥ Now, when ~~2A along~~ alone is acting

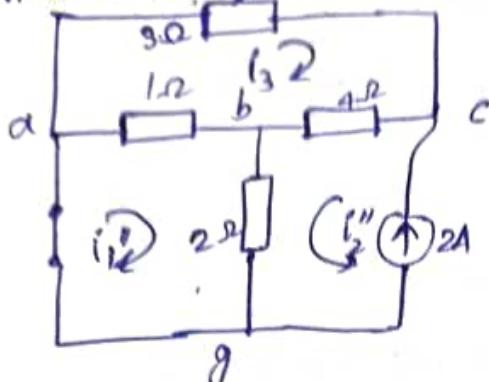

$$\text{Loop 2: } i_2'' = 2A$$

$$\text{Loop 1: } 3i_1'' + 2i_2'' - i_3 = 0 \Rightarrow 3i_1'' - i_3 = -4$$

$$\text{Loop 3: } -i_1'' + 4i_2'' + 8i_3 = 0 \Rightarrow -i_1'' + 8i_3 = -8$$

$$\Rightarrow i_1'' = -1.7391A; i_3 = -1.2173A$$


$$\therefore i_{ab}'' = i_1'' - i_3 = -0.5218A$$

$$V_{cg}'' = +2(i_1'' + i_2'') + 4(i_2'' + i_3) = 3.6526V$$

$$\therefore i_{ab} = i_{ab}'' + i_{ab}' = 0.9131A \cancel{-0.5218A}$$

$$V_{cg} = V_{cg}' + V_{cg}'' = 2.6086 + 3.6526 = 6.2612V$$

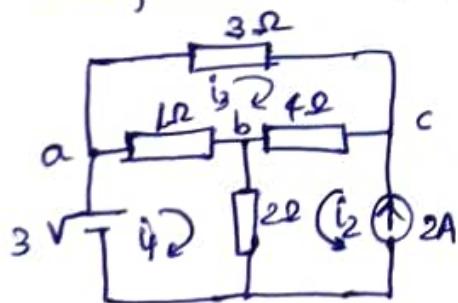Verification: When both sources are acting.



$$\text{Loop 2} \Rightarrow i_2 = 2A$$

$$\text{Loop 1} \Rightarrow 3 = 1 \times (i_1 - i_3) + 2 \times (i_1 + i_2)$$



$$\text{Loop 3} \Rightarrow 0 = 1 \times (i_3 - i_1) + 4 \times (i_3 + i_2) + 3 \times i_3$$

$$\Rightarrow i_1 = -0.6956A, i_3 = -1.0869A$$

$$\therefore i_{ab} = i_1 - i_3 = 0.3913A$$

$$V_{cg} = 2 \times (i_2 + i_1) + 4 \times (i_2 + i_3) \\ = 6.2612V.$$

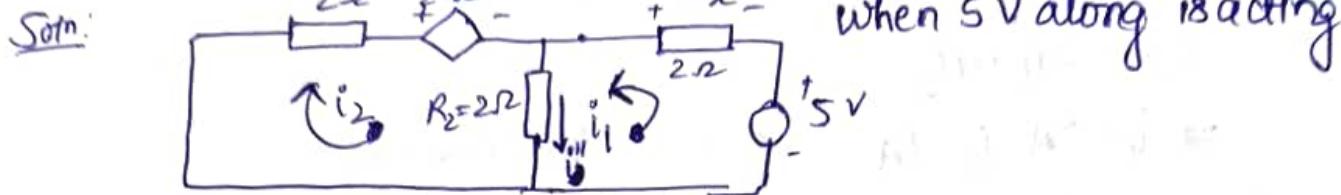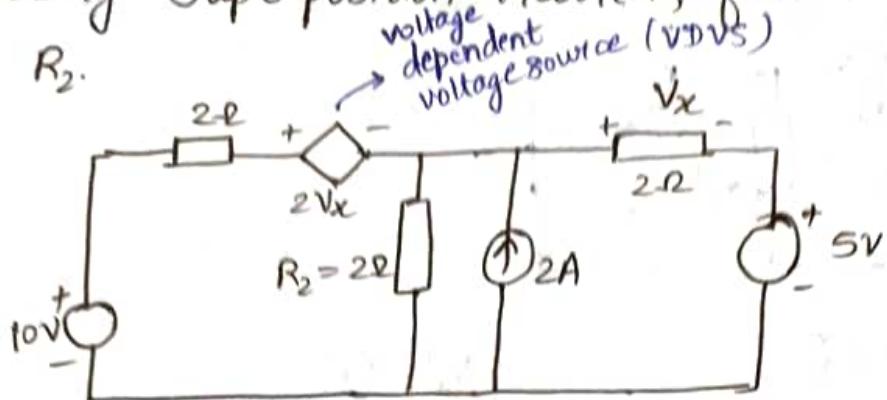Q) Using Superposition theorem, find the power dissipated in R_2 .



$$\text{Mesh method: } 5 = 4i_1 + 2i_2 \quad (\text{Loop 1})$$


$$-2V_x = 4i_2 + 2i_1 \quad (\text{Loop 2})$$

$$V_x''' = 2i_1$$

$$\Rightarrow i_1 = 1A, i_2 = 0.5A$$

$$\therefore i''' = i_1 + i_2 = 0.5A$$

When 2A along is acting

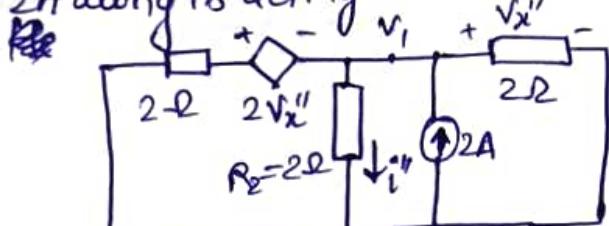


$$\text{Nodal method: } 2 = \frac{(V_1 + 2V_x'')}{2} + \frac{V_1}{2} + \frac{V_1}{2}$$

$$\Rightarrow \frac{(V_1 + 2V_x)}{2} + V_1 = 2$$

$$\Rightarrow V_1 = 0.8V$$

$$\therefore i'' = \frac{V_1}{2} = 0.4A$$

When 10V alone is acting

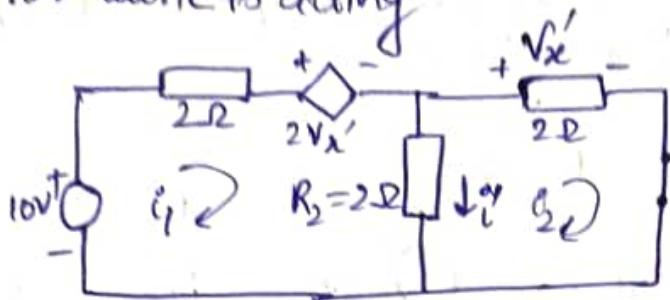

$$10 - 2V_x = 4i_1 - 2i_2$$

$$V_x = 2i_2$$

$$0 = -2i_1 + 4i_2$$

$$\Rightarrow i_1 = 2A, i_2 = 1A$$

$$\therefore i' = i_1 - i_2 = 1A$$

$$V_x' = 2i_2$$

Hence, total current (i) through $R_2 = 2\Omega = i' + i'' + i''' = 2.9A$


Therefore, power dissipated by $R_2 = i^2 R_2 = 16.82W$.

THEVENIN THEOREM

Thevenin theorem states that any linear active network can be replaced by single voltage source (V_{Th}) in series with a single impedance (Z_{Th}).


The Thevenin voltage (V_{Th}) is the open circuit voltage measured across the load terminals.

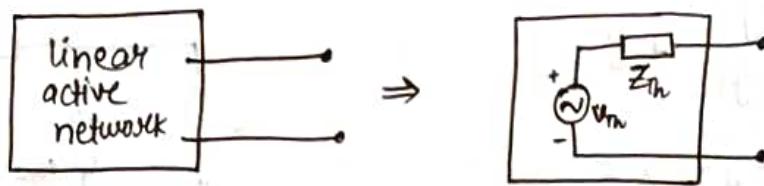Thevenin impedance (Z_{Th}) is the impedance of the network at the load terminals when all the sources are replaced by their respective internal impedances.



Thevenin Equivalent Circuit

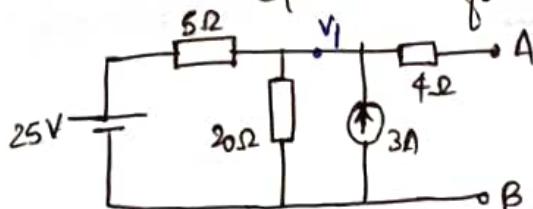Q) Obtain the Thevenin equivalent for the given network.




Soln: To find V_{Th} :


$$\frac{V_1 - 25}{5} + \frac{V_1}{20} = 3 \Rightarrow V_1 = 32V$$

To find R_{Th} :

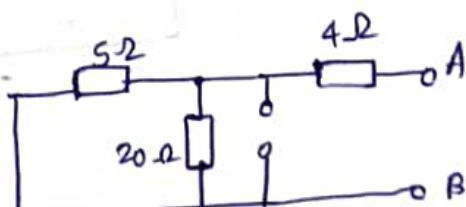
$$R_{Th} = \frac{20 \times 5}{20 + 5} + 4 = \frac{100}{25} + 4 = 8\Omega$$



Thevenin Eq.:

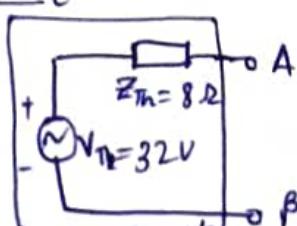

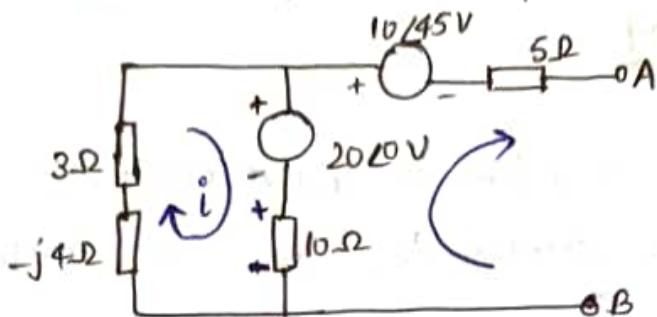Q1 Obtain the Thevenin equivalent for the network given below.




Soln: To find Thevenin voltage $V_{Th} = V_{AB}$


$$i = \frac{-20\angle 0}{13-j4} = 1.4704 \angle -162.89^\circ A$$

$$\begin{aligned} V_{Th} &= +10(1.4704 \angle -162.89) + (20\angle 0) - (10\angle 45) \\ &= 11.4524 \angle -95.63^\circ V \end{aligned}$$

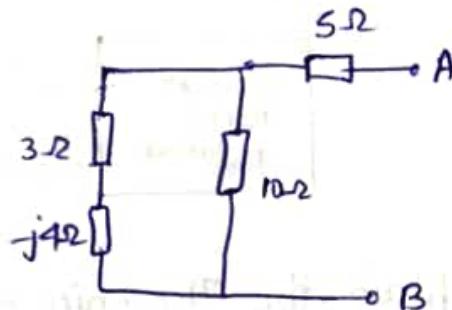
$$\begin{aligned} Z_{Th} &= \frac{10(3-j4)}{10+3-j4} + 5 \\ &= \frac{30-j40}{13-j4} + 5 \\ &= 7.9730 - j2.1622 \end{aligned}$$



Thevenin eq.:

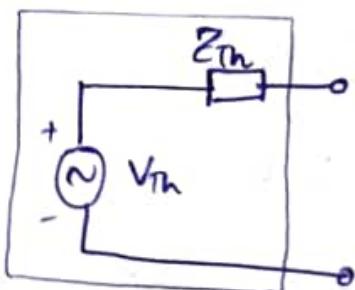

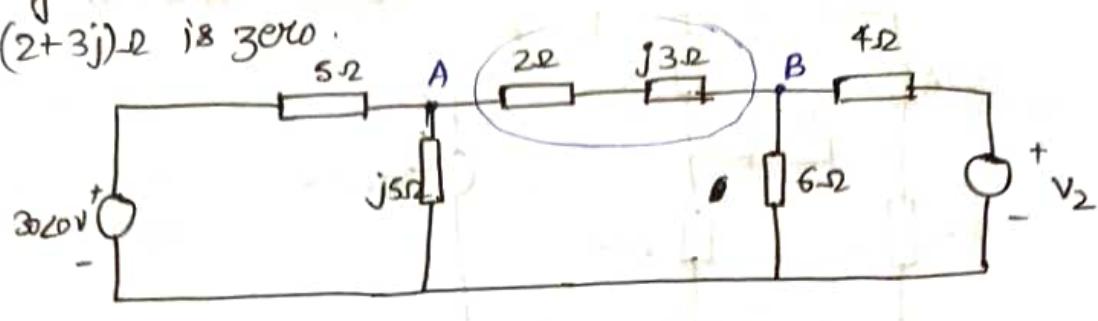Q Using Thevenin theorem, find v_2 such that current through $(2+3j)\Omega$ is zero.




Soh To find Thevenin voltage V_{Th} :

$$i_1 = \frac{30∠0}{5+j5} = 4.2426∠-45^\circ A$$



$$i_2 = -\frac{v_2}{6+4} = -\frac{v_2}{10}$$
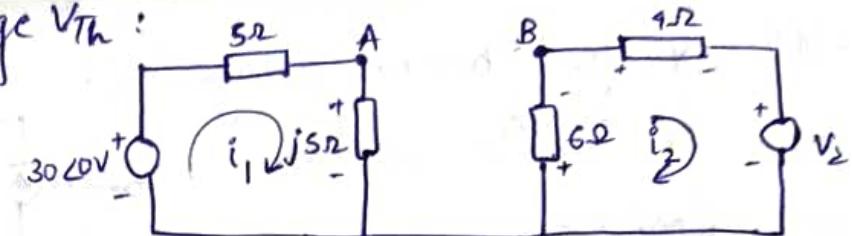
$$\begin{aligned} V_{Th} &= V_{AB} = + (6i_2) + (j5 i_1) \\ &= -0.6v_2 + 21.213∠45^\circ \end{aligned}$$



To find Thevenin impedance Z_{Th} :
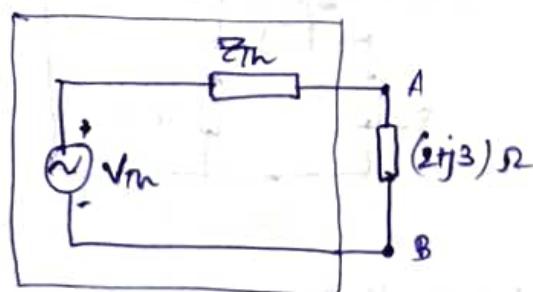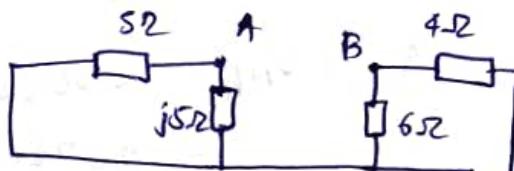
$$\begin{aligned} Z_{Th} &= \frac{6 \times 4}{6+4} + \frac{j25 \times 5}{5+j5} \\ &= 2.4 + \frac{j25}{5+j5} \\ &= (4.9 + j2.5) \Omega \end{aligned}$$




$$\text{For } i_{AB} = 0, V_{Th} = 0$$

$$\Rightarrow -0.6v_2 + 21.213∠45^\circ = 0$$

$$\Rightarrow v_2 = 35.355∠45^\circ V.$$

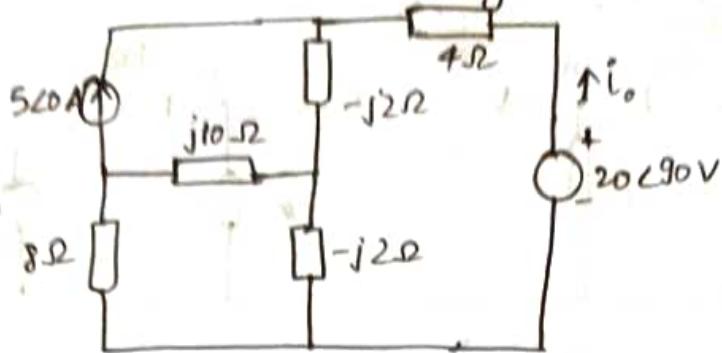Q) Determine the current i_o using Thevenin Theorem.




Sol:

To find Thevenin voltage V_{Th} :

$$i = 5 \angle 90^\circ A$$

Loop 2 \Rightarrow
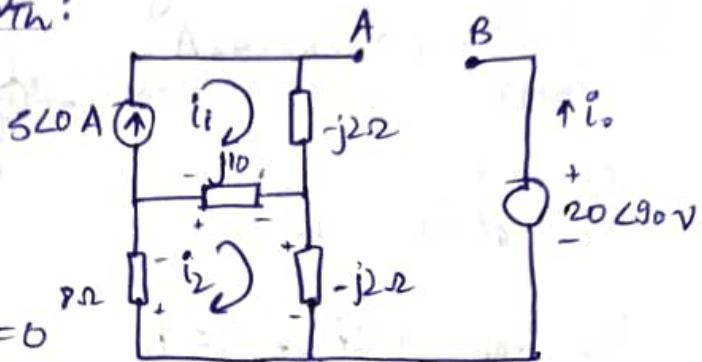
$$(-j2)i_2 + (8)i_2 + (j10)i_2 - (j10)i_1 = 0$$




$$\Rightarrow j8i_2 + 8i_2 = (-j10)5 \angle 90^\circ = (5 \angle 0^\circ) * (10 \angle 90^\circ)$$

$$\Rightarrow i_2 = \frac{50 \angle 90^\circ}{8+j8} = 4.4194 \angle 45^\circ A$$

$$V_{Th} = V_{AB} = -20 \angle 90^\circ + (-j2)4.4194 \angle 45^\circ + (-j2)5 \angle 90^\circ \\ = 36.7848 \angle -80.21^\circ V$$

To find Thevenin impedance Z_{Th} :
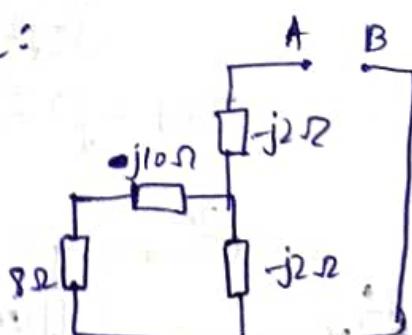
$$Z_{Th} = -j2 + \frac{(8+j10)(-j2)}{(8+j8)} \\ = 4.2573 \angle -86.63^\circ \Omega$$




Current through 4Ω ,

$$I_o = \frac{V_{Th}}{4 + Z_{Th}} = 6.1201 \angle -35.21^\circ A$$

NORTON THEOREM


Norton theorem states that any linear active network can be replaced by single current source (I_N) in parallel with a single impedance (Z_N).

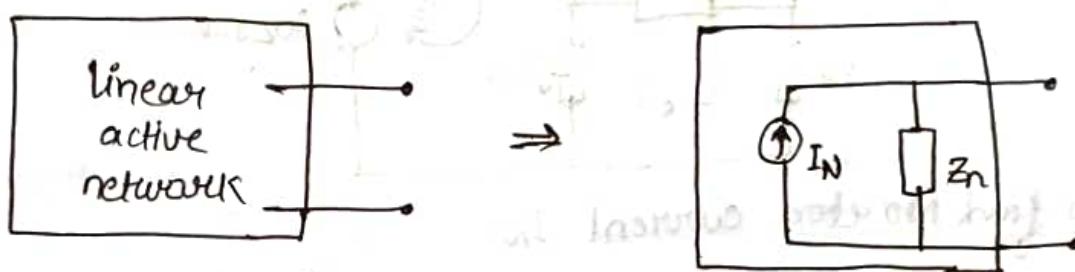The Norton current (I_N) is the short circuit current measured at the load terminals and the Norton impedance (Z_N) is the impedance of the network at the load terminals when all the sources are replaced by their respective internal impedances.



Norton equivalent circuit.

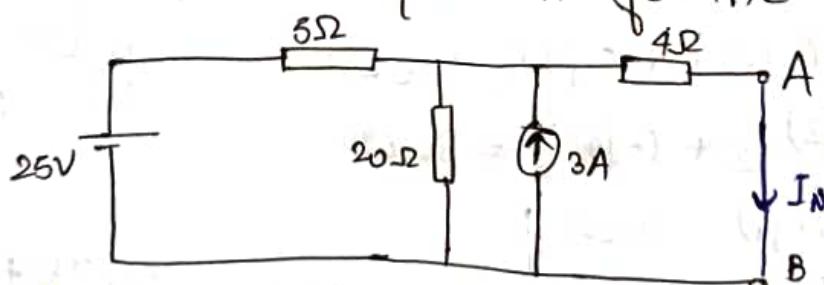Q] Obtain the Norton equivalent for the network given.



Soln: To find Norton current I_N :

By nodal method,

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + \frac{V_1}{4} = 3$$


$$\Rightarrow V_1 = 16V$$

$$\therefore I_{sc} = I_N = \frac{16}{4} = 4A$$


To find Norton Resistance, R_N :

$$R_N = \frac{20 \times 5}{25} + 4 = 8\Omega$$

Norton Equivalent:

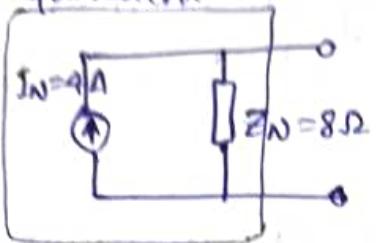

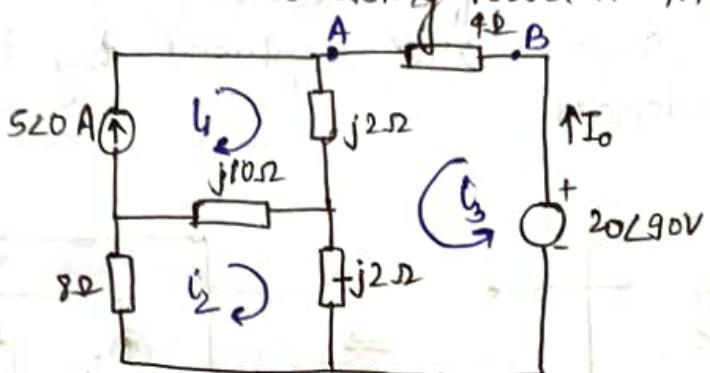Q) Determine the current I_o using Norton theorem.



Soln: To find Norton current I_N :

$$(8+j8)i_2 - j10i_1 - j2i_3 = 0 \quad ; \quad i_1 = 5∠0° A$$

$$\Rightarrow (8+j8)i_2 - j2i_3 = 50∠90°$$

$$(-j2)i_2 + (-j2)i_1 + (-j4)i_3 = 20∠90°$$

$$\Rightarrow (-j2)i_2 + (-j4)i_3 = 30∠90°$$


$$i_3 = \frac{(8+j8) \begin{vmatrix} 50∠90 \\ -j2 \end{vmatrix} - \begin{vmatrix} 30∠90 \\ -j2 \end{vmatrix}}{\begin{vmatrix} (8+j8) & -j2 \\ -j2 & -j4 \end{vmatrix}} = \frac{416 \cdot 1730 \angle 44.7824^\circ}{48 \cdot 1663 \angle -41.6335^\circ}$$

$$\therefore I_N = I_{sc} = i_3 = 8.6403 \angle 186.41^\circ A$$


To find Norton impedance Z_N :

$$Z_N = -j2 + \frac{(8+j10)(-j2)}{(8+j8)}$$

$$= 4.2573 \angle -86.63^\circ \Omega$$

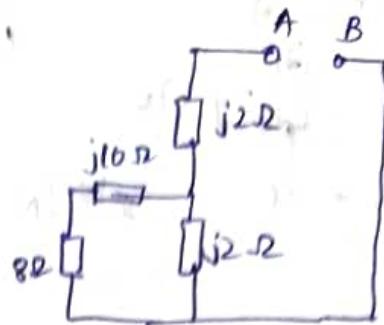


Norton Equivalent:

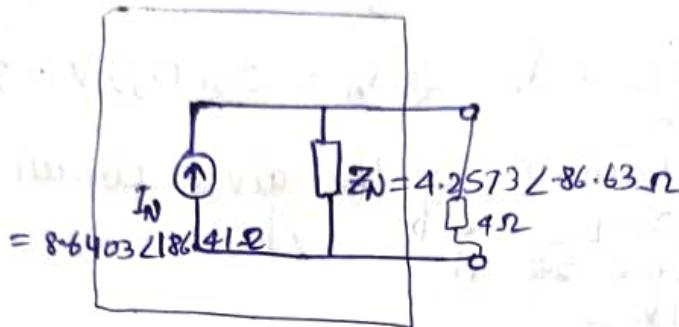

$$\text{Current through } 4\Omega = I_N \times \frac{Z_N}{(Z_N + 4)}$$

$$= 6.1199 \angle 144.77^\circ A$$

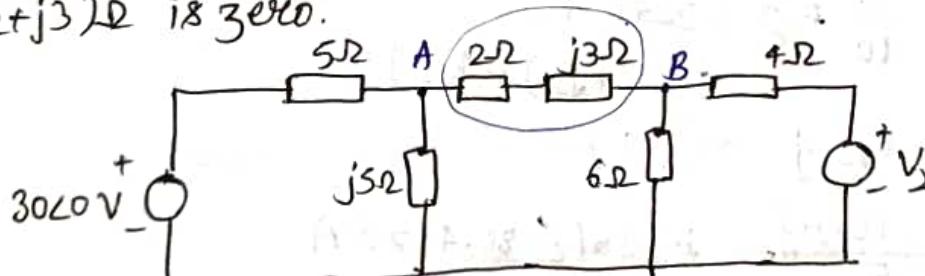Q1 Using Norton theorem, find V_2 , such that current through $(2+j3)\Omega$ is zero.



Soln: To find I_N :



$$\frac{V_A - 30}{5} + \frac{V_A}{5j} + \frac{V_A}{6} + \frac{V_A - V_2}{4} = 0$$

$$\Rightarrow I_N = \frac{V_A}{6} + \frac{V_A - V_2}{4}$$


To find Z_N :

$$Z_N = \frac{5 \times j5}{5+j5} + \frac{4 \times 6}{4+6}$$

$$= (4.9 + j2.5) \Omega$$

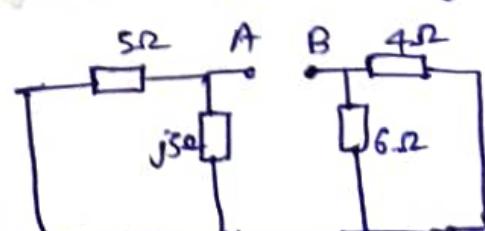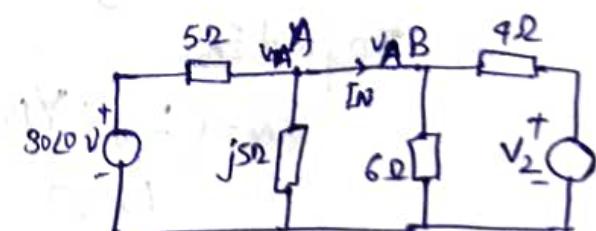

Norton Eqn:

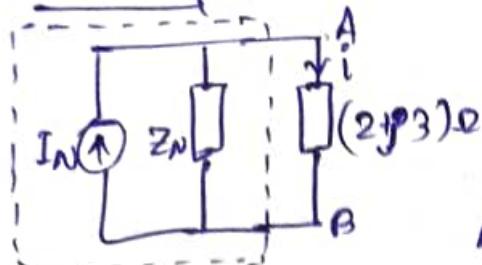


$$i = \frac{I_N \times Z_N}{Z_N + (2+j3)} = 0$$

$$\text{As } I_N = 0 \Rightarrow \frac{V_A - V_2}{4} + \frac{V_A}{6} = 0 \Leftarrow -\left(\frac{V_A - 30}{5} + \frac{V_A}{5}\right)$$

$$\Rightarrow \frac{V_A(1-j)}{5} = 6 \Rightarrow V_A = 15(1+j) V$$


$$10V_A = 6V_2 \Rightarrow V_2 = \frac{5}{3} V_A = 25(1+j) V = 35.3553 \angle 45^\circ V$$

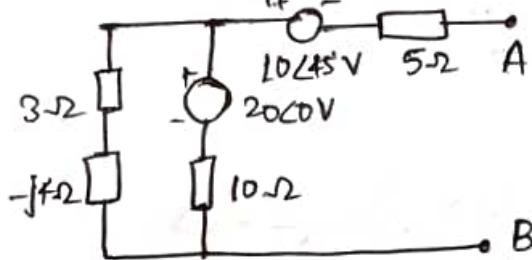Q1 Obtain Norton equivalent of the given circuit.



Soln: To find I_N :
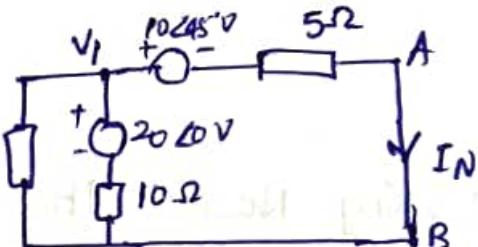
$$\frac{V_1}{3-j4} + \frac{V_1 - 20}{10} + \frac{V_1 - 10 \angle 45^\circ}{5} = 0 \quad (3\Omega - j4\Omega)$$



$$\Rightarrow \frac{V_1(3+j4)}{25} + \frac{V_1}{10} + \frac{V_1}{5} = 2 \angle 45^\circ + 2$$

$$= (2 + j2) + (j\sqrt{2})$$


$$\Rightarrow V_1 = (8.2190 + j0.2361) V$$

$$I_N = \frac{V_1 - 10 \angle 45^\circ}{5} = 1.3861 \angle -80.4659^\circ A$$

To find Z_N :

$$Z_N = \frac{(3-j4)(10)}{13-j4} + 5$$
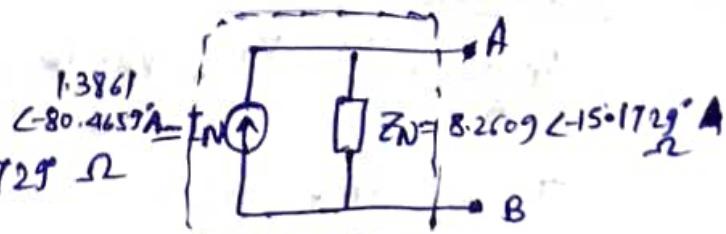
$$= 8.2609 \angle -15.1729^\circ \Omega$$




Norton Eqn.

MAXIMUM POWER TRANSFER THEOREM

In a linear bilateral active network, the maximum power is transferred from the source to the load if the load impedance is complex conjugate of source impedance.

$$Z_s = R_s + jX_s$$

~~Explaination~~

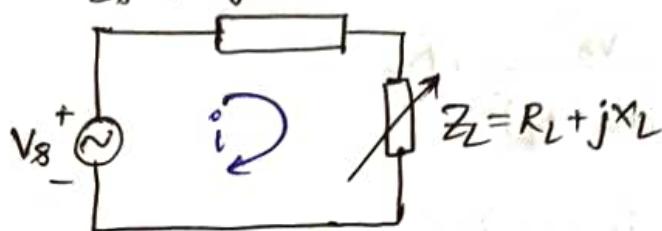

$$i = \frac{V_s}{Z_s + Z_L} = \frac{V_s}{(R_s + jX_s) + (R_L + jX_L)}$$

$$= \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$|i| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

Since no power is consumed by the load reactance, the power dissipated in the load is due to the resistive part ~~part~~ (R_L) of the load impedance. Hence, the power will be dissipated by R_L only.

$$P_L = \frac{V_s^2}{(R_s + R_L)^2 + (X_s + X_L)^2} \cdot R_L \quad \text{--- (1)}$$

- ① Let R_L be fixed and X_L be variable.

$$\frac{d}{dx_L} [P_L] = 0$$

\Rightarrow

$$\Rightarrow x_S + x_L = 0$$

$$\Rightarrow x_L = -x_S$$

$$\therefore P_L = \frac{V_S^2}{(R_S + R_L)^2} \cdot R_L$$

② ~~But~~ when R_L is varied:

$$\frac{d}{dR_L} [P_L] = 0$$


$$\Rightarrow R_S = R_L$$

$$Z_L = Z_S^* \\ = R_S - jx_S$$

$$\text{efficiency, } \eta = \frac{\text{Output}}{\text{Input}}$$

$$= \frac{i^2 R_L}{i^2 (R_L + R_S)}$$
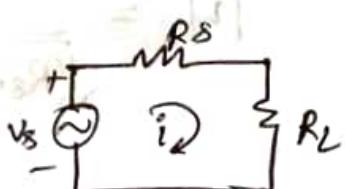
$$= \frac{R_L}{R_S + R_L} = \frac{1}{\left(\frac{R_S}{R_L} + 1\right)}$$




$$\text{if } R_L = R_S, \quad \eta = \frac{1}{2} = 50\%$$

$$\text{if } R_L \rightarrow \infty, \quad \eta = 1 = 100\% \\ \text{or } R_S \rightarrow 0$$


$$\text{if } R_L \rightarrow 0, \quad \eta = 0$$

→ Efficiency is only 50% when maximum power transfer is achieved, but approaches 100% as $R_L \rightarrow \infty$ or $R_B \rightarrow 0$. Efficiency is 0% if $R_L \rightarrow 0$.

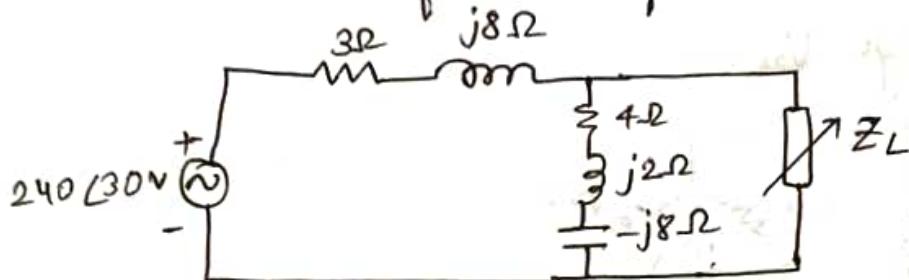Q Determine the load impedance Z_L that absorbs max^m power and hence find this power.




Soln: To find V_{Th} :

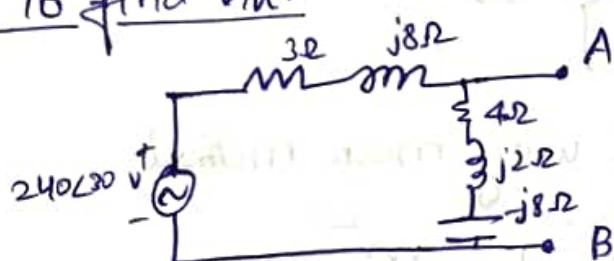

$$V_{Th} = \frac{240(30)(4-j6)}{(7+j2)} \\ = 237.7248 \angle -42.25^\circ V$$

$$Z_{Th} = \frac{(3+j8)(4-j6)}{(7+j2)} = 8.463(-2.8113) \Omega \\ = (8.4528 - j0.415) \Omega$$

$$Z_L = (8.4528 + j0.415) \Omega$$

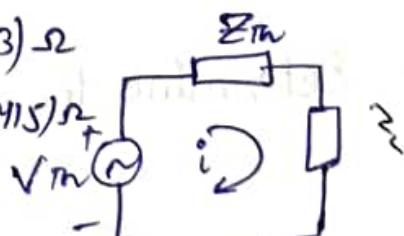

$$i = \frac{V_{Th}}{2R_{Th}} = \cancel{\frac{128.1689}{2}} \angle \cancel{-47.3844387^\circ} / \Omega$$


$$\boxed{P_{max} = 167.4307 W}$$

$$P_{max} = I^2 R = \frac{V_{Th}^2}{4R_{Th}} \quad R' = \frac{V_{Th}^2}{4R}$$


Assignment

20-06-2023

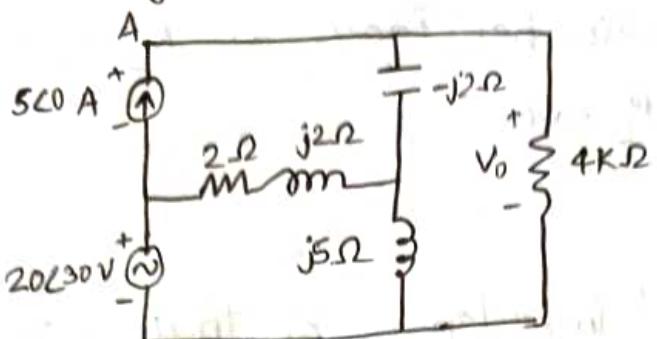
- Q1 ① Find V_o using mesh and nodal method.




- ② Find the voltage V_{ab} .

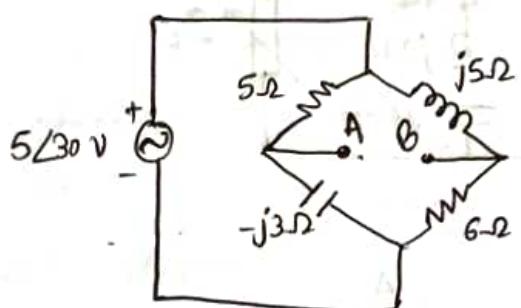

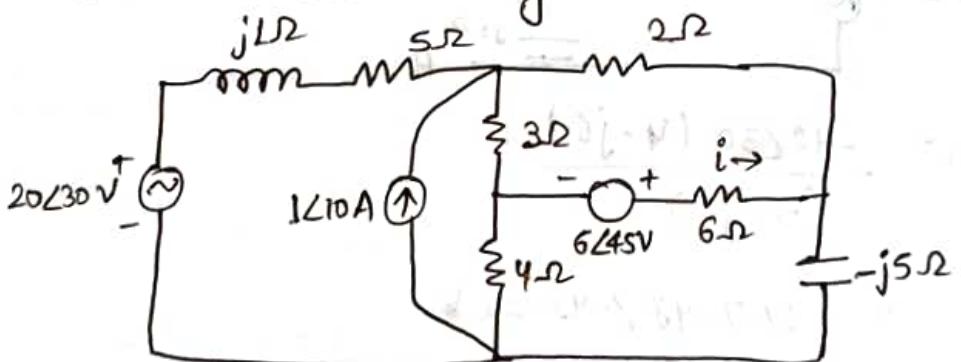- ③ Determine current I using mesh method.



- ④ Determine the node voltages.

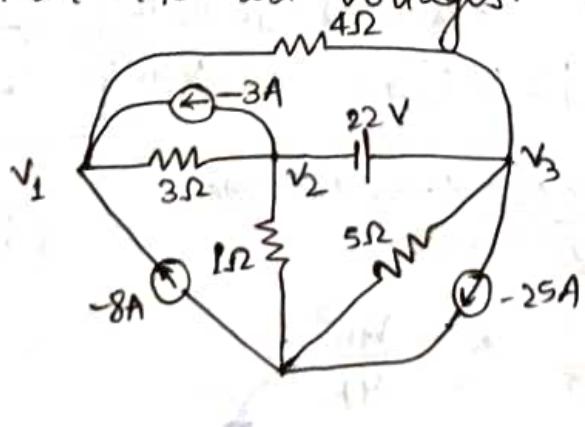

⑤ Using TT and NT, find V_o .

