
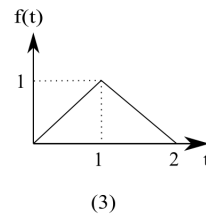
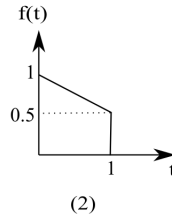


AVP 213 Drill Problems - Set 1

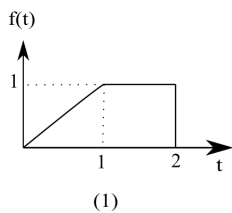Q. Find Laplace Transform of the following:



Q. Solve for $y(t)$ using Laplace Transform for the following:

(4) $y'' + 0.04y = 0.02t^2$; $y(0) = -25$; $y'(0) = 0$

(5) $y'' + 3y' + 2.25y = 9t^3 + 64$; $y(0) = 1$; $y'(0) = 31.5$

(6) $y'' + 2y' + 5y = 50t - 100$; $y(2) = -4$; $y'(2) = 14$


(7) $y'' + 3y' + 2y = 4t$ if $0 \leq t < 1$, $y(0) = 0$
 $= 8$ if $t \geq 1$, $y'(0) = 0$

(8) $y'' + 2y' + 5y = 10\sin t$ if $0 \leq t < 2\pi$, $y(\pi) = 1$
 $= 0$ if $t \geq 2\pi$, $y'(\pi) = 2e^{-\pi} - 2$


(9) $y'' + 4y = \delta(t - \pi)$; $y(0) = 8$; $y'(0) = 0$

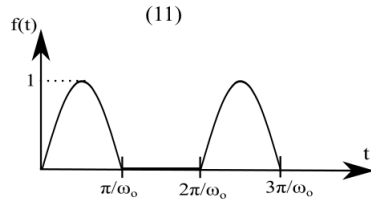(10) $y'' + 3y' + 2y = 10[\sin t + \delta(t - 1)]$; $y(0) = 1$; $y'(0) = -1$



Q. Find $F(s)$ for the periodic waveforms $f(t)$ in the problems (11) to (14)



Half Wave Rectified sinusoids

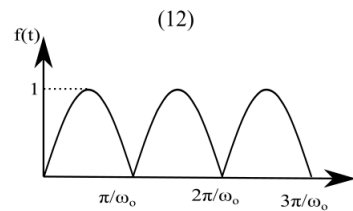


Full Wave Rectified sinusoids

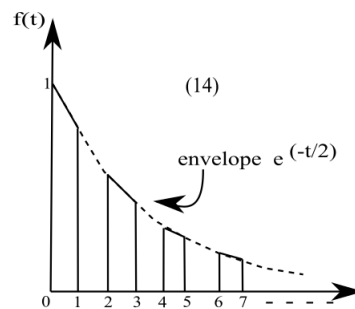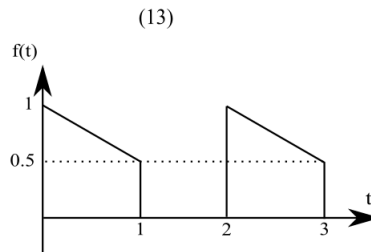


Q. Analyse and solve for problems (15) to (29) by methods applicable in time domain.

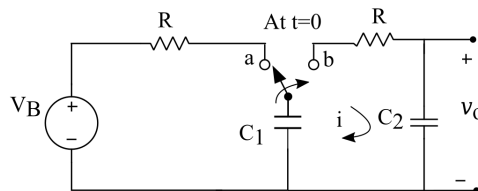
- (15) Switch moves from 'a' to 'b' at $t = 0$. Steady state was initially reached at position 'a'. Given $v_0(0^-) = 0$. Find $i(t)$ and $v_0(t)$ for $t > 0$.



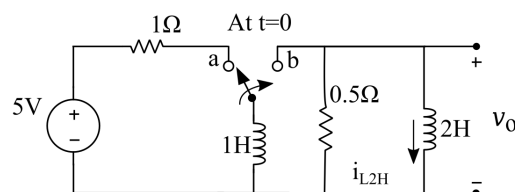
- (16) Solve for $v_0(t)$, given $i_{L2H}(0^-) = 0$. Steady state was initially reached at position 'a'.



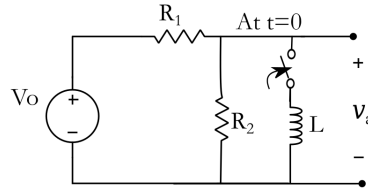
- (17) $V_0 = 3V$, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $L = 0.5H$ at $t = 0$, switch is closed. Find $v_a(t)$ for $t > 0$



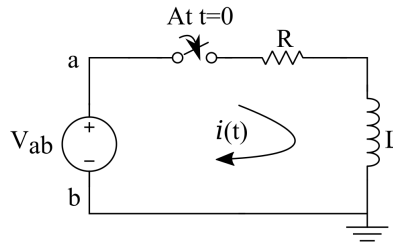
- (18) $v_{ab} = V_m \sin \omega_0 t$, solve for $i(t)$



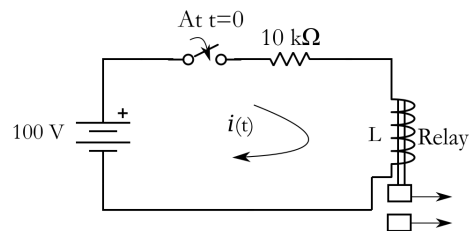
- (19) Relay is an electromagnetic switch which constitute of a coil inductance 'L' is having movable parts. The relay is designed and constructed in such a manner that it is activated when current through the coil is $0.008A$. After the switch is closed at $t = 0$, it is observed that the relay gets activated when $t = 0.1sec$. Find the inductance (L) of the coil.



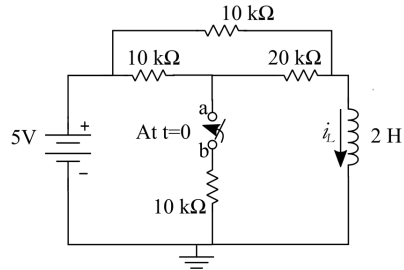
- (20) Initially the switch was open with the network reaching steady state. At $t = 0$, the switch is closed. Find and plot $i_L(t)$ for $t > 0$.



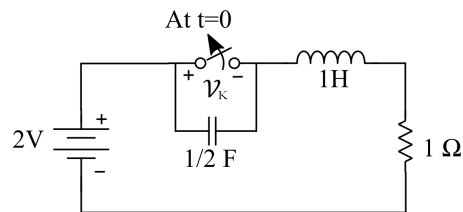
- (21) Network was at steady state with switch Sw closed. At $t = 0$, Sw is opened. Determine v_k and $\frac{dv_k}{dt}$ at $t = 0^+$



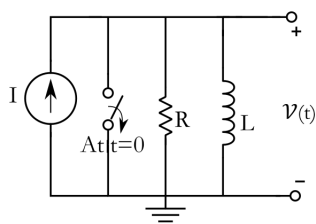
- (22) If $I = 1A$, $R = 100\Omega$, $L = 1H$, solve for v , $\frac{dv}{dt}$, $\frac{d^2v}{dt^2}$ at $t = 0^+$



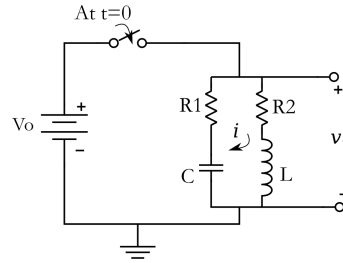
- (23) Network unenergized before $t = 0$, Determine v_1 , $\frac{dv_1}{dt}$, $\frac{d^2v_1}{dt^2}$ at $t = 0^+$



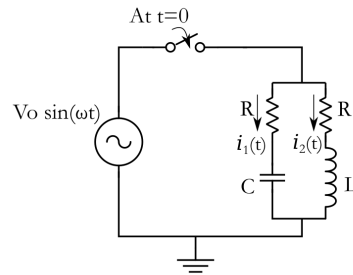- (24) Find $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t = 0^+$



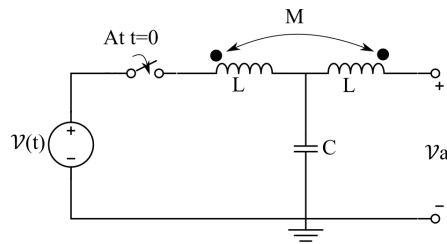
- (25) Network initially relaxed $v(t) = V_m \sin(\frac{t}{\sqrt{MC}})$.




Show that,

- (a) $v_a(0^+) = 0$,
 (b) $\frac{dv_a}{dt}(0^+) = \frac{V\sqrt{M}}{L\sqrt{C}}$

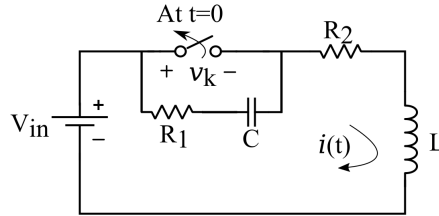
- (26) Network initially reached steady state with switch closed. At $t = 0$, it is opened.



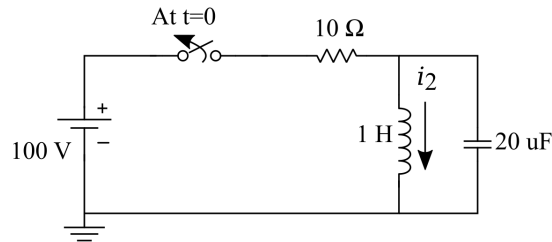
- (a) Find an expression for the voltage across the switch v_k at $t = 0^+$
- (b) If the parameters are adjusted such that $i(0^+) = 1$ and $\frac{di}{dt}(0^+) = -1$, what is the value of $\frac{dv_k}{dt}$ at $t = 0^+$?
- (27) Initially switch was closed and steady state was reached in the network. At $t = 0$, the switch is opened. Find expression for $i_2(t)$.



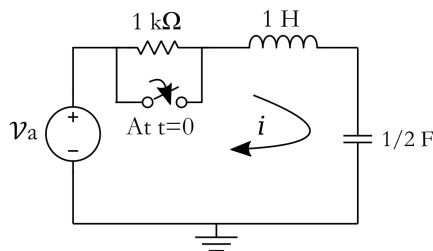
- (28) Steady state was reached with switch open. $v_a = 100\sin 377t$. At $t = 0$, switch is closed. Determine $i(t)$ for $t \geq 0$



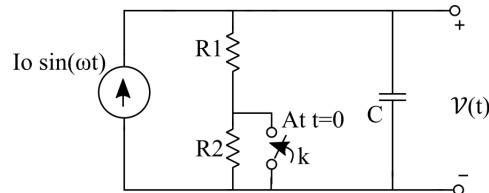
- (29) Network initially was operating in steady state with 'k' opened. At $t = 0$, 'k' is closed. Find expression for $v(t)$ for $t \geq 0$.



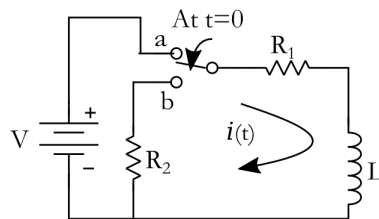
- (30) Steady state was initially reached with switch at position 'a'. Solve for $i(t)$ using Laplace transform method.



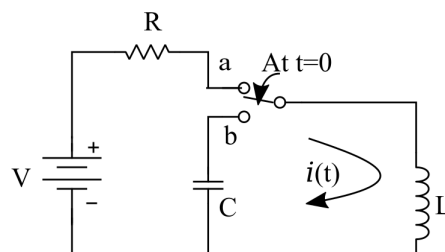
- (31) Steady state was initially reached at position 'a'. Solve for $i(t)$ using Laplace transform method.



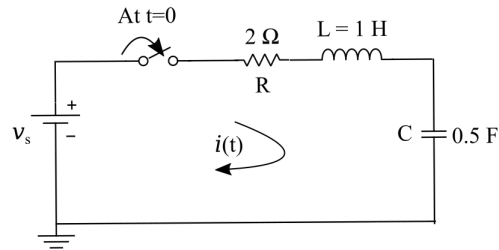
- (32) $v_s = \sin t$, Initially relaxed network. Find $i(t)$ for $t > 0$.



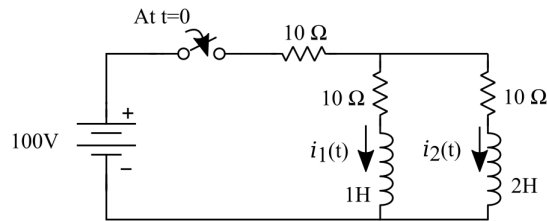
- (33) Initially unenergized network. Find $i_1(t)$, $i_2(t)$ for $t > 0$



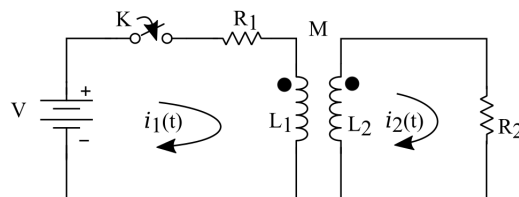
- (34) Initially unenergized network. $L_1 = 1H, L_2 = 4H, M = 2H, R_1 = R_2 = 1\Omega, V = 1V$. Find $i_1(t)$, $i_2(t)$



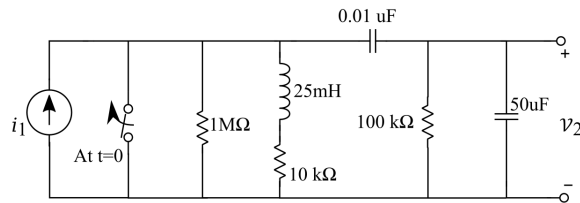
- (35) Initially unenergized network. Switch opened at $t = 0$ If $i_1(t) = 10^{-3}e^{-t}u(t)A$, find and plot $v_2(t)$ for $t \geq 0$



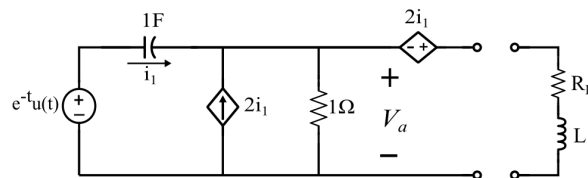
- (36) With respect to the load consisting of R_L and L determine the Thevenin equivalent network.



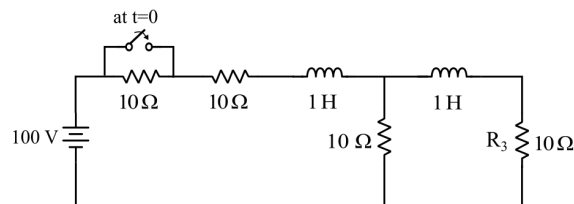
- (37) Find the current in R_3 using (a) Thevenin's theorem (b) Norton's theorem



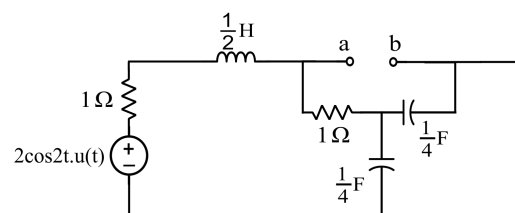- (38) Find both Thevenin's and Norton's equivalent network for the terminals a-b in the figure for zero initial conditions.



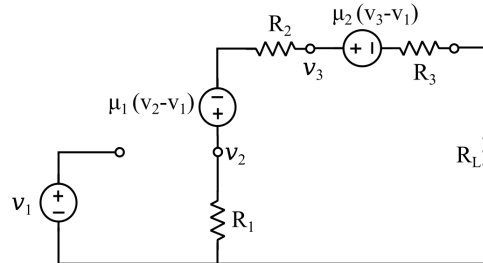- (39) R_L is the load. Determine the equivalent Thevenin Network to find the current in load R_L .



- (40) $v_s = \sqrt{2}V_1 \sin 2\pi ft$, where $V_1 = 230 \text{ V}$ and $f = 50 \text{ Hz}$.

- (a) Design an appropriate filter which passes the DC component in $v_o(t)$ and attenuates (reduces/seals down) all AC components having frequency 50Hz or more by atleast 100 times.
Note : Remember for this problem as well as subsequent problems, the best designed filter is the one which is simplest yet meets all it's specifications.
- (b) Design an appropriate filter which attenuates the DC component in $v_o(t)$ by atleast 100^2 times and passes all the AC components having frequency 50 Hz or more with phase error (if any) less than 2° .
- (c) Repeat problem (a) and (b) by re-designing the filters with op-amps.

