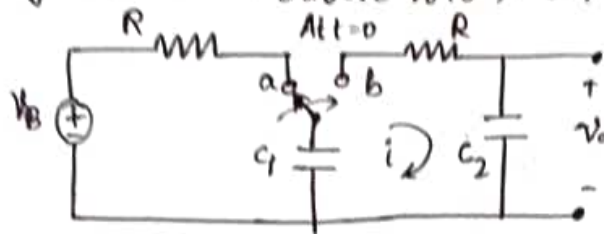



Assignment -1
AV213 - Network Analysis
(Solved Problems Set-1)

SAURABH KUMAR ①
 SC22BL46
 (ECE)

- ⑬ Switch moves from 'a' to 'b' at $t=0$. Steady state was initially reached at position 'a'. Given $v_o(0^-)=0$. Find $i(t)$ and $v_o(t)$ for $t>0$.




Soln: Initial equivalent circuit:

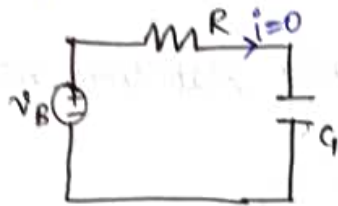

$$v_{C_1}(0^+) = v_{C_1}(0^-) = v_B = v_1(0^+)$$

For $t \geq 0$.

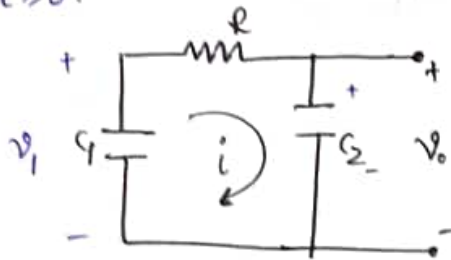

Using KVL,

$$v_1 = iR + v_2$$

$$\Rightarrow v_1' = i'R + v_2'$$

$$\Rightarrow -\frac{i}{C_1} = i'R + \frac{i}{C_2}$$

$$(C \frac{dv}{dt} = i)$$

$$\Rightarrow 0 = i'R + \left(\frac{1}{C_1} + \frac{1}{C_2}\right)i = i'R + \left(\frac{1}{C_{eq}}\right)i$$

$$\Rightarrow 0 = i' + \frac{1}{\tau}i, \quad \tau = RC_{eq}$$

$$\Rightarrow \frac{di}{dt} = -\frac{1}{\tau}i \Rightarrow \int \frac{di}{i} = -\frac{1}{\tau} \int dt \Rightarrow i = Ke^{-t/\tau}$$

$$\text{As } i(0) = \frac{v_1 - v_2}{R} = K$$

$$\therefore i = \frac{v_1 - v_2}{R} e^{-t/\tau}$$

$$\Rightarrow i = \frac{v_B}{R} e^{-t/\tau}$$

$$(\because v_1(0) = v_B, v_2(0) = 0)$$

$$\text{As } C_2 \frac{dv_o}{dt} = i = \frac{v_B}{R} e^{-t/\tau}$$

$$\Rightarrow v_o = -\frac{v_B}{RC_2} \frac{e^{-t/\tau}}{1/\tau} + K_1$$


$$= -\frac{v_B C_{eq}}{C_2} e^{-t/\tau} + K_1$$

$$\text{As } v_o(0+) = 0,$$


$$K_1 = \frac{v_B C_{eq}}{C_2}$$

$$\therefore v_o = \frac{v_B C_{eq}}{C_2} (1 - e^{-t/\tau})$$

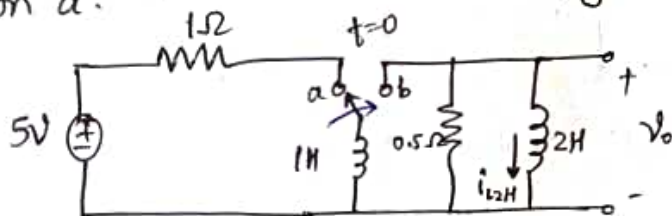(16) Solve for $v_o(t)$, given $i_{L2H}(0^-) = 0$. Steady state was reached initially at position 'a'.




Soln: Initially,

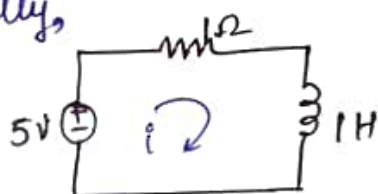

$$i(0+) = i(0-) = \frac{5V}{1\Omega} = 5A$$

For $t > 0$,

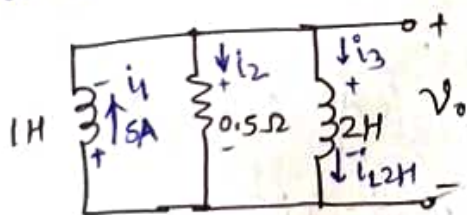

$$i_1 = i_2 + i_3$$

$$\Rightarrow i_1' = i_2' + i_3'$$

$$\Rightarrow -\frac{v_o}{1} = \frac{v_o'}{0.5} + \frac{v_o}{2}$$

$$\Rightarrow 0 = 2v_o' + 3\frac{v_o}{2}$$

$$\Rightarrow 0 = 4v_o' + 3v_o \quad \text{--- (i)}$$

$$\Rightarrow 0 = 4\frac{dv_o}{dt} + 3v_o \Rightarrow 4\frac{dv_o}{v_o} = -3dt$$

$$\Rightarrow v_o = k e^{-3/4 t}$$

③

Sum (i)


$$0 = 4 v_o' + 3 v_o$$

$$\Rightarrow 0 =$$


$$\text{As } v_o(0+) = i \times R = -5 \times 0.5 = -2.5 \text{ V}$$

$$\therefore v_o = -2.5 e^{-3/4 t}$$

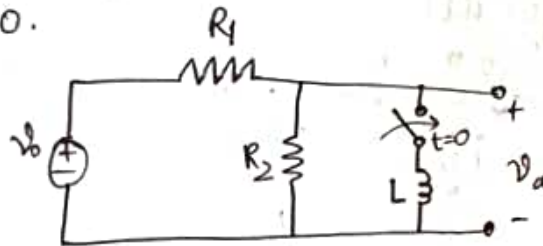
- ⑪ $v_o = 3 \text{ V}$, $R_1 = 10 \Omega$, $R_2 = 5 \Omega$, $L = 0.5 \text{ H}$ at $t = 0$, switch is closed. Find $v_a(t)$ for $t > 0$.



Soln: Initial equivalent circuit:

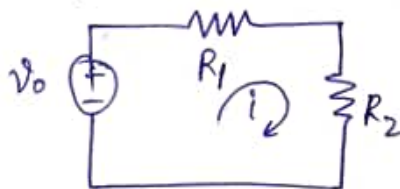
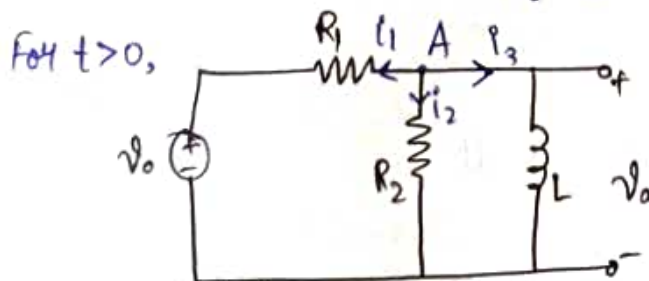
$$i(0+) = i(0-) = \frac{v_o}{R_1 + R_2} = \frac{3}{15} \text{ A} \Rightarrow v_a = \frac{3}{15} \times 5 = 1 \text{ V}$$



At point A,

$$i_1 + i_2 + i_3 = 0$$

$$\Rightarrow \frac{v_a - v_o}{R_1} + \frac{v_a}{R_2} + i_3 = 0$$

$$\Rightarrow \frac{v_o'}{R_1} + \frac{v_a'}{R_2} + \frac{v_a}{L} = 0 \quad (\text{differentiating wrt } t)$$

$$\Rightarrow V_a' \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = - \frac{V_a}{L}$$

$$\Rightarrow \frac{V_a'}{V_a} = - \frac{1}{L} \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\Rightarrow V_a = K e^{-\frac{1}{L} \left(\frac{R_1 R_2}{R_1 + R_2} \right) t}$$


As $V_a(0^+) = 1V$

$$\Rightarrow K = 1$$

$$\therefore V_a(t) = e^{-\frac{2}{0.5 \left(\frac{10 \times 5}{3} \right)} t}$$

$$= e^{-\frac{20}{3} t} V$$

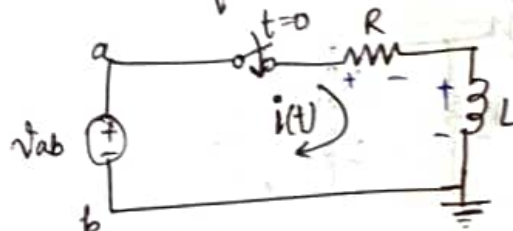⑮ $V_{ab} = V_m \sin \omega t$, solve for $i(t)$.



Soln: Applying KVL (for $t > 0$),

$$V_{ab} = iR + L i'$$

$$\Rightarrow V_m \sin \omega t = iR + L i'$$

$$\Rightarrow \frac{di}{dt} + \frac{i}{T_F} = \frac{V_m}{L} \sin \omega t$$

$$IF = e^{\int \frac{1}{T_F} dt} = e^{t/T_F}$$

$$\therefore i e^{t/T_F} = \int e^{t/T_F} \frac{V_m}{L} \sin \omega t dt$$

$$= \frac{V_m}{L} \int e^{t/T_F} \sin \omega t dt$$

Let $I = \int e^{t/T_F} \sin \omega t dt$

$$= -\frac{e^{t/T_F}}{\omega} \cos \omega t + \int \frac{e^{t/T_F} \cos \omega t}{\omega T_F} dt$$

$$= -\frac{e^{t/T_F}}{\omega} \cos \omega t + \frac{1}{\omega T_F} \left[e^{t/T_F} \sin \omega t - \underbrace{\int \frac{e^{t/T_F} \sin \omega t}{T_F \omega} dt}_{I/T_F} \right]$$

(5)

$$\Rightarrow I \left(1 + \frac{1}{\omega_0^2 T_F^2} \right) = -\frac{e^{t/T_F} \cos \omega_0 t}{\omega_0} + \frac{e^{t/T_F} \sin \omega_0 t}{\omega_0 T_F}$$

$$\Rightarrow I = \frac{\omega_0^2 T_F^2}{1 + T_F^2 \omega_0^2} e^{t/T_F} \left[\sin \omega_0 t - T_F \cos \omega_0 t \right]$$

$$= \frac{T_F e^{t/T_F}}{1 + T_F^2 \omega_0^2} \left[\sin(\omega_0 t) - T_F \cos \omega_0 t \right]$$


$$\therefore i = \frac{T_F}{1 + T_F^2 \omega_0^2} \left[\sin \omega_0 t - T_F \cos \omega_0 t \right] + K_0 e^{-t/T_F}$$

At $t \rightarrow 0^+$, $i = 0$.

$$0 = \frac{-T_F^2}{1 + T_F^2 \omega_0^2} + K_0 \Rightarrow K_0 = \frac{T_F^2}{1 + T_F^2 \omega_0^2}$$

$$\therefore i(t) = \frac{T_F}{1 + T_F^2 \omega_0^2} \left[\sin \omega_0 t - T_F \cos \omega_0 t + T_F e^{-t/T_F} \right]$$

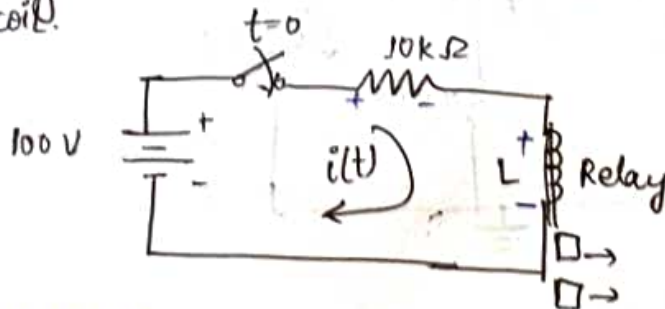- (19) Relay is an EM switch which constitute of a coil inductance 'L' is having movable parts. The relay is designed and constructed in such a manner that it is activated when current through the coil is 0.008A. After the switch is closed at $t=0$, it is observed that the relay gets activated when $t=0.1$ sec. Find the inductance (L) of the coil.



Soln: Using KVL ($t > 0$),

$$100 = 10Ki + Li'$$

$$\Rightarrow i' + \frac{i}{10K} = 100$$

$$IF = e^{\int \frac{10K}{L} dt} = e^{10Kt/L}$$

$$\therefore i e^{10Kt/L} = \int e^{10Kt/L} \cdot 100 dt$$

$$= \frac{e^{10Kt/L}}{10K/L} + K$$

$$\Rightarrow i = \frac{L}{10K} + Ke^{-10Kt/L}$$

As $i(0+) = 0$,

$$0 = \frac{L}{10K} + K \Rightarrow K = -\frac{L}{10K}$$

$$\therefore i(t) = \frac{L}{10K} \left[1 - e^{-10Kt/L} \right]$$

Given that $i = 0.008A$ when $t = 0.1 \text{ sec}$.


$$\Rightarrow 0.008 = \frac{L}{10K} (1 - e^{-10K \times 0.1/L})$$

$$\Rightarrow 80 = L - L e^{-K/L}$$

$$\Rightarrow \ln 80 = \ln(L - L e^{-K/L})$$


$$\Rightarrow L \approx 621.35 \text{ H}$$

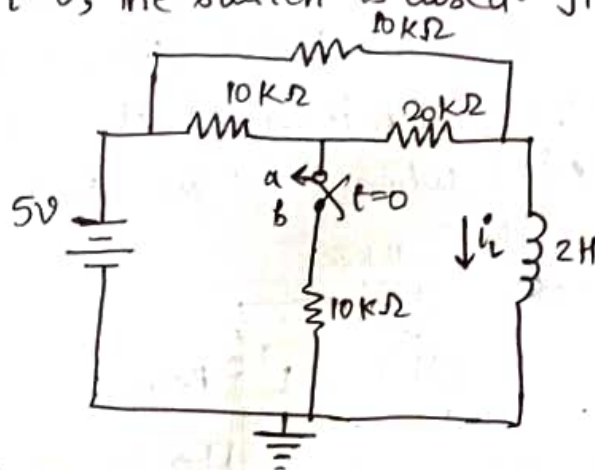② Initially the switch was open with the network reaching steady state. At $t=0$, the switch is closed. Find and plot $i_L(t)$ for $t > 0$.




Soln:

Initial equivalent ckt.,

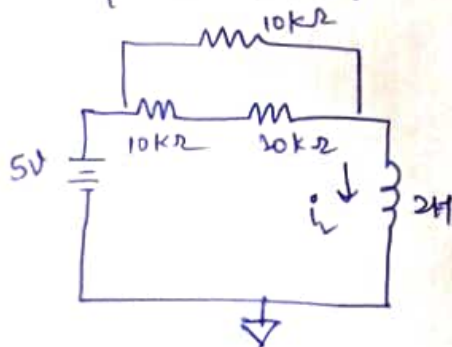

\Rightarrow

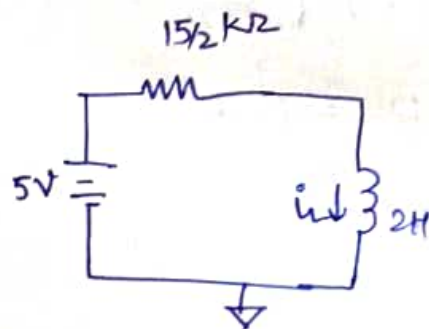

Using KVL and $i(0) = 0$,


$$i(t) = \frac{V}{R} (1 - e^{-t/\tau})$$

$$= \frac{5}{7.5k} (1 - e^{-t/\tau})$$

For $t \rightarrow 0^+$,

$$i_L = \frac{5}{7.5k} A = \frac{2}{3} A$$

For $t > 0$, Thevenin's theorem:

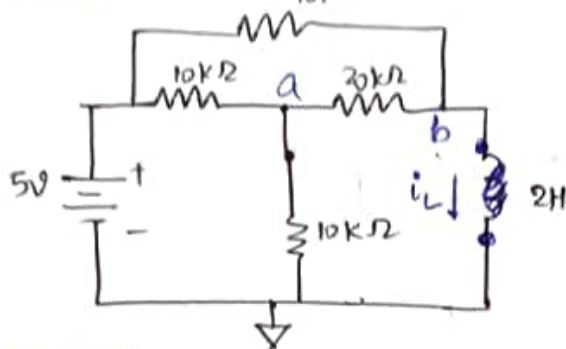

Equivalent

$$\text{At } a: \frac{a-5}{10} + \frac{a}{10} + \frac{a-b}{20} = 0 \Rightarrow 2a-10+2a+a-b \Rightarrow b = 5a-10$$

$$\text{At } b: \frac{b-5}{10} + \frac{b-a}{20} = 0 \Rightarrow 2b-10+b-a=0$$

$$\Rightarrow 3b-10-a=0$$

$$\Rightarrow 14a-40=0 \Rightarrow a = \frac{20}{7}$$

$$\Rightarrow b = 5 \times \frac{20}{7} - 10 = \frac{30}{7}$$

$$\therefore \text{Thevenin voltage} = \frac{30}{7} = 4.28 V$$

Thevenin impedance,

$$Z_{th} = 10k\Omega \parallel 25k\Omega$$

$$= \frac{10 \times 25}{35} k = \frac{50}{7} k\Omega$$

Now,

$$\frac{30}{7} = i' \times \frac{50}{7} + Li' \Rightarrow 2i' + \frac{50}{7}i = \frac{30}{7}$$


$$i' = \frac{15}{7} e^{-\frac{25}{7}t}$$

$$\therefore i e^{\frac{25}{7}t} = \int \frac{15}{7} e^{-\frac{25}{7}t} dt$$


$$= \frac{15}{7} \frac{e^{-\frac{25}{7}t}}{-\frac{25}{7}} = -\frac{3}{5} e^{-\frac{25}{7}t} \Rightarrow i = \frac{3}{5} + c e^{-\frac{25}{7}t}$$

$$i(0^-) = \frac{2}{3} A$$
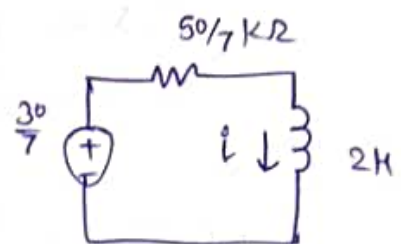
$$\Rightarrow \frac{2}{3} = \frac{3}{5} + c \Rightarrow c = \frac{1}{15} \Rightarrow i = \frac{1}{15} (9 + e^{-\frac{25}{7}t})$$



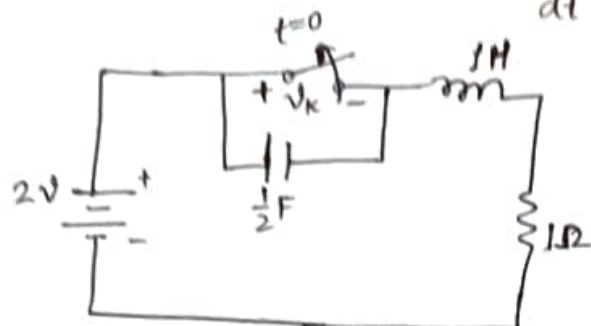② Network was at steady state with switch S_w closed. At $t=0$, S_w is opened. Determine v_k and $\frac{dv_k}{dt}$ at $t=0^+$.




Soln: Initial equivalent ckt.:



for $t \rightarrow 0^+$, $i = \frac{2V}{1\Omega} = 2A$.

for $t > 0$:

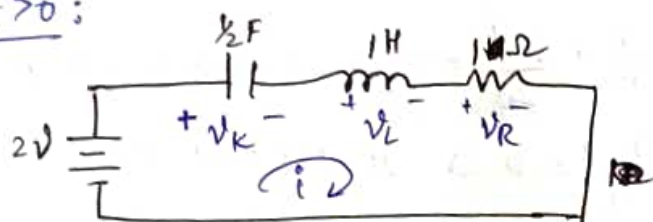

Using KVL,

$$2 = v_k + v_L + v_R$$

$$\Rightarrow v_k = 2 - i' - i \quad \text{--- (1)}$$

$$\Rightarrow 0 = v_k' + v_L' + v_R'$$

$$\Rightarrow 0 = \frac{i}{\frac{1}{2}} + i'' + i'$$

$$\boxed{v_k(0^+) = v_k(0^-) = 0 \text{ V}}$$

$$\Rightarrow 0 = 2i' + i'' + i'$$

$$\Rightarrow i''(0^+) + i'(0^+) = -2i(0^+) = -2 \times 2 = -4A$$


$$\textcircled{i} \Rightarrow v_k' = -(i'' + i')$$

$$\Rightarrow v_k'(0^+) = -(i''(0^+) + i'(0^+))$$


$$\Rightarrow \boxed{v_k'(0^+) = 4 \text{ V sec}^{-1}}$$

22) If $I = 2A$, $R = 100\Omega$, $L = 1H$, solve for v , $\frac{dv}{dt}$, $\frac{d^2v}{dt^2}$ at $t = 0^+$.

9

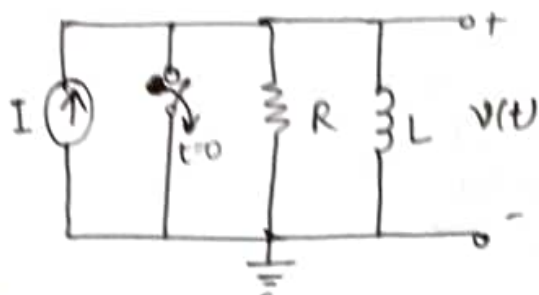

Soln: For $t \geq 0$,

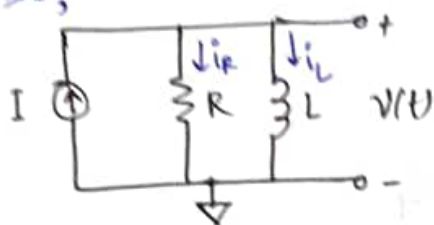

Using KCL,

$$I = i_R + i_L \quad \text{--- (i)}$$

$$\Rightarrow 2 = \frac{v}{R} + \frac{1}{L} \int v dt$$

$$\Rightarrow 0 = \frac{v'}{100} + v \quad \text{--- (ii)}$$

$$v(0^+) = 0$$

$$\Rightarrow v'(0^+) = 0$$

$$\text{(i)} \Rightarrow I(0^+) = i_R(0^+) + i_L(0^+)$$

$$\Rightarrow 2 = \frac{v(0^+)}{100} + 0$$

$$\Rightarrow v(0^+) = 200 \text{ V}$$


$$\text{(ii)} \Rightarrow 0 = v'(0^+) + 100 \times 200$$

$$\Rightarrow v'(0^+) = -20 \text{ K V/sec}$$


$$\text{(i)} \Rightarrow 0 = v'' + 100 v'$$

$$\Rightarrow v''(0^+) = -2 \text{ M/sec}^2$$

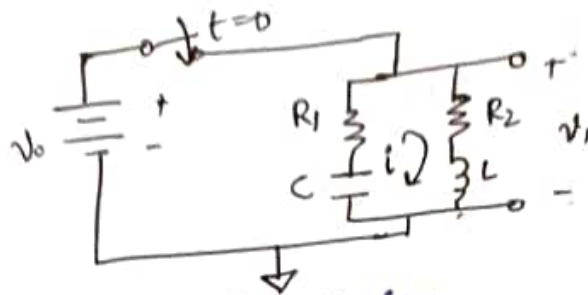②③ Network unenergized before $t=0$, determine v_1 , v_1' , v_1'' at $t=0^+$. ⑩



Soln: At $t=0^+$, equivalent circuit is:

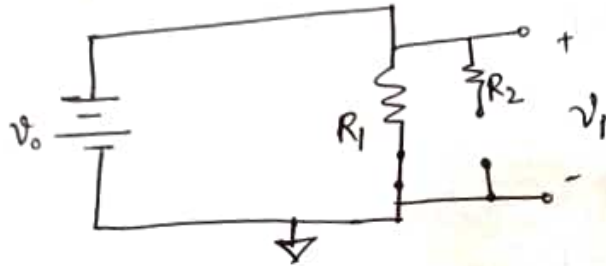


$$v_1 = v_0$$

$$\Rightarrow v_1(0^+) = v_0$$


$$\Rightarrow v_1'(0^+) = 0$$

$$\Rightarrow v_1''(0^+) = 0$$

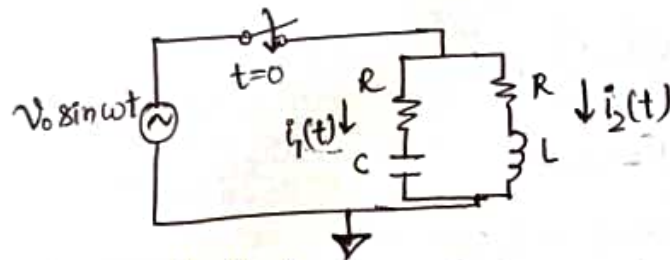②④ Find $\frac{di_1}{dt}$ and $\frac{di_2}{dt}$ at $t=0^+$.



Soln: At $t=0^+$, equivalent ckt. is:

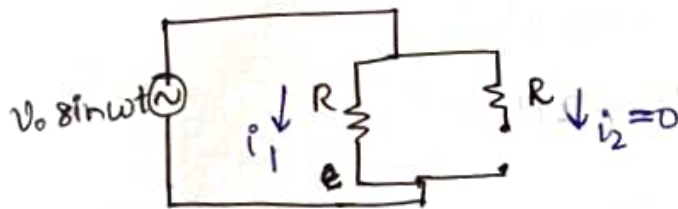

$$i_1 = \frac{v_0}{R} \sin wt$$

$$\Rightarrow i_1' = \frac{v_0 \omega \cos wt}{R}$$


$$\Rightarrow i_1'(0^+) = \frac{v_0 \omega}{R}$$

$$i_2 = 0$$

$$\Rightarrow i_2' = 0$$

$$\Rightarrow i_2'(0^+) = 0$$

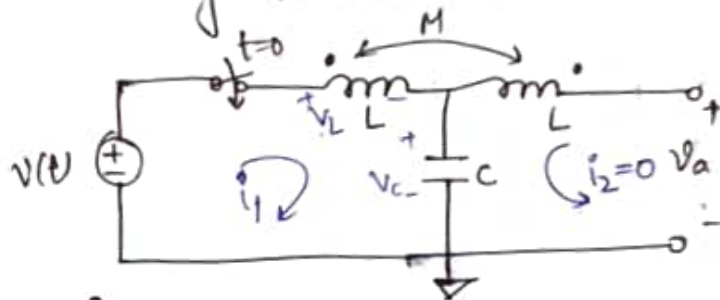25) Network initially relaxed $v(t) = v_m \sin\left(\frac{t}{\sqrt{LC}}\right)$.



Show that,

(a) $v_a(0+) = 0$

(b) $\frac{dv_a}{dt}(0+) = \frac{v_m M}{L\sqrt{C}}$

Soln: (a) Using KVL,

$$v = v_L + v_C$$

$$= (L i_1' + M i_2') + v_C \quad \text{--- (i)}$$

and, $v_a = L i_2' + M i_1' + v_C \quad \text{--- (ii)}$

$$\text{(i) \& (ii)} \Rightarrow v - L i_1' = v_a - M i_1'$$

$$\Rightarrow v = v_a + (L - M) i_1' \quad \text{--- (iii)}$$

At $t=0+$,

$$i_1 = 0, v_C = 0$$

$$v_L = 0, v_a = 0 \Rightarrow i_1' = 0$$

$$\therefore \boxed{v_a(0+) = 0}$$

(b) (ii) $\Rightarrow v_a = v - (L - M) i_1'$

$$v_a' = v' - (L - M) i_1''$$

$$= v_L' + v_C' - (L - M) i_1''$$

$$= v_L' + v_C' - (L - M) \frac{v_L'}{L} \quad \text{--- (iv)}$$

As $v_L = v - v_C$

$$v_L' = v' - v_C'$$


$$= v' - \frac{i_1}{C}$$

$$v_L'(0+) = v'(0+) - \frac{i_1(0+)}{C}$$

$$= \frac{v_m}{\sqrt{LC}}$$

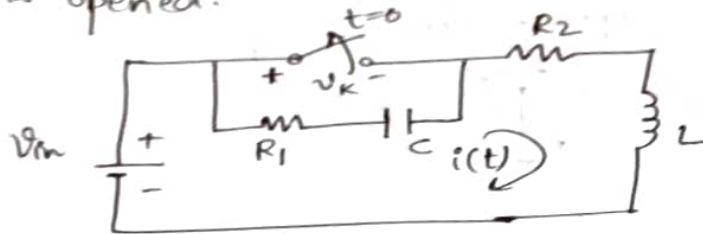
(iv) $\Rightarrow v_a'(0+) = \frac{v_m}{\sqrt{LC}} - \left(\frac{L-M}{L}\right) \frac{v_m}{\sqrt{LC}} = \frac{v_m}{\sqrt{LC}} \cdot \frac{M}{L} = \boxed{\frac{v_m M}{L\sqrt{C}}}$

- 26 Network initially reached steady state with closed switch. At $t=0$, it is opened.




- (a) Find an expression for the voltage across the switch v_K at $t=0^+$.
 (b) If the parameters are adjusted such that $i(0^+)=1$ and $\frac{di}{dt}(0^+)=-1$, what is the value of $\frac{dv_K}{dt}$ at $t=0^+$?

Soln: (a) Initial equivalent circuit:

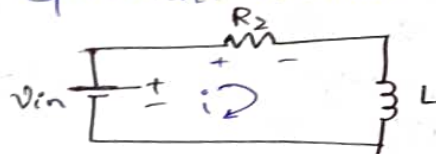

$$i(0^+) = \frac{v_{in}}{R_2}$$

For $t \geq 0$:

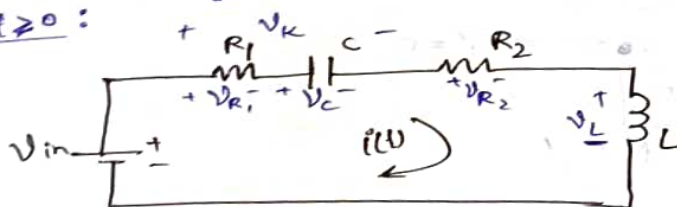

Using KVL,

$$v_{in} = v_{R_1} + v_C + v_{R_2} + v_L$$

$$\Rightarrow v_{in}(0^+) = v_{R_1}(0^+) + v_C(0^+) + v_{R_2}(0^+) + v_L(0^+)$$

$$\Rightarrow v_{in} = i(0^+)R_1 + i(0^+)R_2 + L i'(0^+)$$

$$v_K(0^+) = v_{R_1}(0^+) + v_C(0^+)$$


$$= i(0^+)R_1 + 0$$

$$\therefore \boxed{v_K(0^+) = \frac{v_{in} \cdot R_1}{R_2}}$$


② $v_k'(0+) = v_{R_1}'(0+) + v_C'(0+)$
 $= i'(0+) R_1 + \frac{i_1'(0+)}{C}$
 $= (-1) R_2 + \frac{1}{C}$

$\therefore \boxed{v_k'(0+) = -R_2 + \frac{1}{C}}$

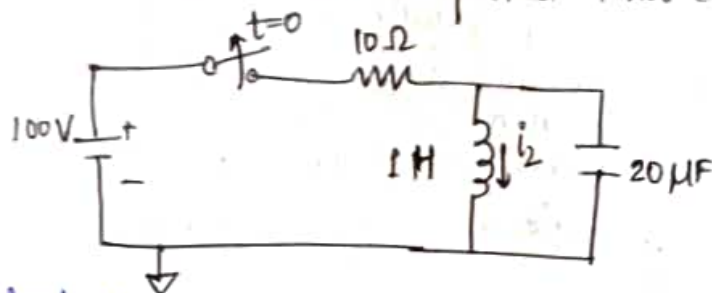② Initially switch was closed and steady state was reached in the network. At $t=0$, the switch is opened. And expression for $i_2(t)$.



Soln: Initial equivalent circuit:

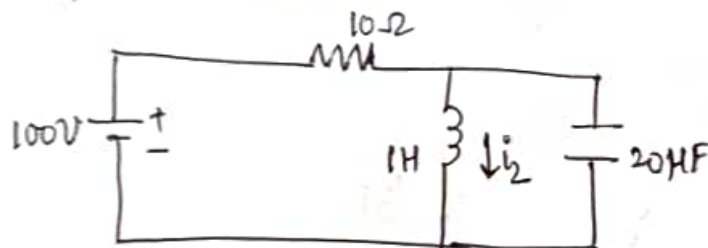

$i_2 = \frac{100}{10} = 10 \text{ A}$


$\therefore i_2(0+) = 10 \text{ A}$

For $t \geq 0$,

$v_C = 100 - 10 \times 10 = 0 \text{ V}$

$\Rightarrow v_L = v_C = 0 \Rightarrow v_L' = 0 \Rightarrow i_2' = 0$

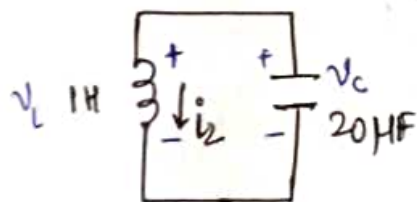$\Rightarrow i_2'(0+) = 0 \Rightarrow i_2'(0+) = 0$



$v_L = v_C$

$\Rightarrow i_2' = \frac{1}{C} \int i_2 dt$

$\Rightarrow i_2 = C i_2'' \Rightarrow i_2'' - \frac{1}{C} i_2 = 0$

characteristic eqn: $\lambda^2 - \frac{1}{C} = 0$

$\Rightarrow \lambda = \pm \frac{1}{\sqrt{C}}$

$\therefore i_2(t) = e^{k_1 e^{1/\sqrt{C}t}} + k_2 e^{-1/\sqrt{C}t}$

$$\Rightarrow i_2' = \frac{K_1}{\sqrt{c}} e^{\frac{1}{\sqrt{c}}t} - \frac{K_2}{\sqrt{c}} e^{-\frac{1}{\sqrt{c}}t}$$

$$i_2'(0) = 0 \Rightarrow 0 = \frac{K_1}{\sqrt{c}} - \frac{K_2}{\sqrt{c}} \Rightarrow K_1 - K_2 = 0$$

and,


$$i_2(0) = 10$$

$$\Rightarrow K_1 = K_2$$


$$\Rightarrow 10 = K_1 + K_1 \Rightarrow K_1 = 5 A.$$

$$\therefore i_2 = 5e^{\frac{1}{\sqrt{c}}t} + 5e^{-\frac{1}{\sqrt{c}}t}.$$

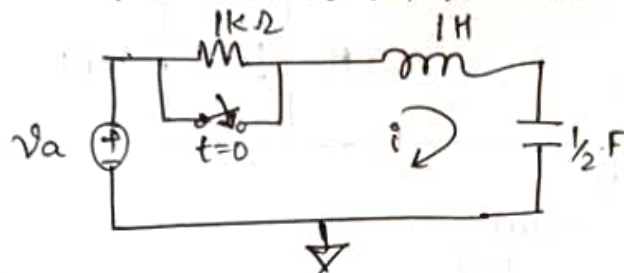②⑧ Steady state was reached with switch open. $v_a = 100 \sin 377t$.
At $t=0$, switch is closed. Determine $i(t)$ for $t \geq 0$.




Soln: Initial equivalent ckt.:

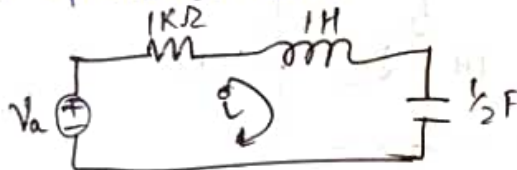

$$i(0^+) = 0, v_L(0^+) = 0 \Rightarrow Li' = 0 \Rightarrow i'(0^+) = 0.$$

For $t \geq 0$:

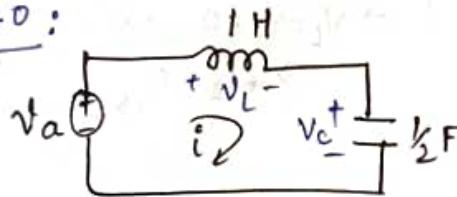

Using KVL,

$$v_a = v_L + v_C$$

$$\Rightarrow v_a = Li' + \frac{1}{c} \int i dt$$

$$\Rightarrow Li'' + \frac{i}{c} = 100(\cos 377t) 377 = 37700 \cos 377t$$

$$\Rightarrow i'' + \frac{i}{LC} = 37700 \cos 377t$$

$$\text{Char. eqn: } \lambda^2 + \frac{1}{LC} = 0 \Rightarrow \lambda^2 = -2$$

$$\Rightarrow \lambda = \pm \frac{1}{\sqrt{LC}} = \pm \sqrt{2}i$$

$$\therefore i(t) = K_1 e^{\frac{1}{\sqrt{LC}}t} + K_2 e^{-\frac{1}{\sqrt{LC}}t}.$$

$$i'(0) = 0 \Rightarrow 0 = \frac{K_1}{\sqrt{LC}} - \frac{K_2}{\sqrt{LC}} \Rightarrow K_1 = K_2$$

$$i(0) = 0 \Rightarrow 0 = 2K_1 \Rightarrow K_1 = 0$$

$$\therefore i_h(t) = 0$$

and,

$$y_p(t) = A \sin 377t + B \cos 377t$$

$$\Rightarrow 377^2 A \sin(377t) + (377)^2 \cos(377t) + A$$

$$i_{inh} = \frac{100}{377} \sin(377t - \pi/2)$$

$$\therefore i = C_1 \cos \sqrt{2}t + C_2 \sin \sqrt{2}t + \frac{100}{377} \sin(377t - \pi/2)$$

$$\text{As } i(0) = i(0+) = 0.066\sqrt{2} \sin(-0.360)$$

$$V_L = iX_L = 0.66\sqrt{2} \angle -0.360 \quad (377 \angle \pi/2)$$

$$= 351.88 \angle 1.210$$

$$\therefore V_L(0+) = 351.88 \angle 1.210 = 351.88 \sin(1.210)$$

$$\therefore i(0+) = -0.66\sqrt{2} \sin(0.36)$$

$$C_1 + \frac{100}{377}(-1) = -0.328$$

$$\Rightarrow C_1 = -0.062$$

For Q:

$$V_L = Li' = -C_1\sqrt{2} \sin \sqrt{2}t + C_2\sqrt{2} \cos \sqrt{2}t + 100 \cos(377t - \pi/2)$$


$$V_L(0+) = C_2\sqrt{2} = 329.224$$

$$C_2 = 232.796$$


$$\therefore i(t) = -0.062 \cos \sqrt{2}t + 232.796 \sin \sqrt{2}t$$

$$+ 0.2652 \sin(377t - \pi/2)$$

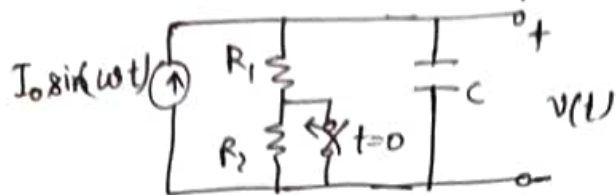- (29) Network initially was operating in steady state with 'k' opened. At $t=0$, 'k' is closed. Find expression for $v(t)$ for $t \geq 0$.




Sol: Initial equivalent circuit:

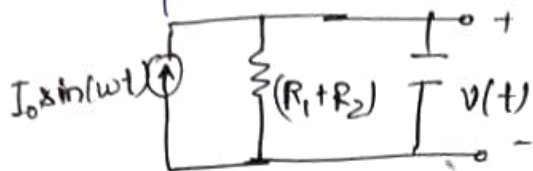

$$v(t) = I_0 \sin(\omega t) \left[(R_1 + R_2) \parallel \frac{j}{\omega C} \right]$$

$$v(0^-) = 0, v(0^+) = 0$$

for $t \geq 0$:

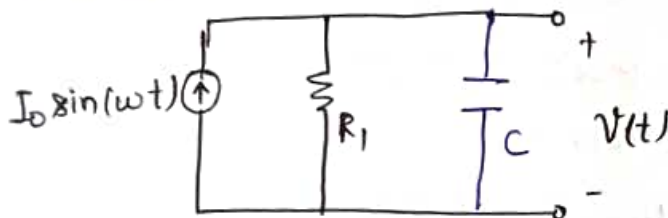

$$I_0 \sin \omega t = \frac{v(t)}{R} + i_c$$

$$\Rightarrow \frac{I_0}{C} \sin \omega t = \frac{v}{R} + v'$$

$$IF = e^{t/\tau C}$$

$$\therefore v \cdot e^{t/\tau C} = \int \frac{I_0}{C} \sin \omega t \cdot e^{t/\tau C} dt = \frac{I_0}{C} \int \sin(\omega t) e^{t/\tau C} dt$$

$$I = \tau \sin \omega t e^{t/\tau C} - \int \omega \cos \omega t \cdot e^{t/\tau C} \tau dt$$

$$= \tau \sin \omega t e^{t/\tau C} - \tau \omega \int \cos \omega t e^{t/\tau C} \tau dt - \int \sin \omega t \cdot \omega e^{t/\tau C} \tau dt$$

$$= \tau \sin \omega t e^{t/\tau C} - \tau^2 \omega \cos(\omega t) e^{t/\tau C} + \omega^2 \tau^2 \int \sin \omega t e^{t/\tau C} dt$$

$$\Rightarrow I = \frac{\tau e^{t/\tau C}}{1 + \omega^2 \tau^2} [\sin \omega t - \omega \tau \cos \omega t]$$

and, $v_L(0^+) = 0$

$$\therefore v = \frac{\tau}{1 + \omega^2 \tau^2} [\sin \omega t - \omega \tau \cos \omega t] + \frac{\omega \tau^2}{1 + \omega^2 \tau^2} e^{-t/\tau C}$$