

## Digital Electronics Verilog Lab 7

### Submitted By:

Saurabh Kumar

SC ID: SC22B146

Course: DIGITAL ELECTRONICS AND VLSI DESIGN LAB (AV232)

### LAB SHEET

**Question No. 1.** Instantiate a block random access memory (BRAM) of FPGA to store 25 contents of the last lab sheet. Provide input to BRAM using:

- i) test bench.
- ii) Assignment: Read the data using \$readmemb or \$readmemh from a text file.
- iii) Assignment: Initialize the BRAM with the data.

### Sol: Code:

```
module RAM (clk,add,din,en,we,dout);
    input wire clk;
    input wire[4:0] add;
    input wire[7:0] din;
    input wire en;
    input wire[0:0] we;
    output wire[7:0] dout;

    // Block Memory Generator Instantiation
    blk_mem_gen_0 your_instance_name (
        .clk(clk),
        .en(en),
        .we(we),
        .addr(addr),
        .din(din),
        .dout(dout));
endmodule
```

### Testbench Code:

```
module tb_RAM();
    reg t_clk, t_cs, t_we;
    reg [4:0] t_address;
    reg [7:0] t_data;
    integer i;
    RAM DUT(t_clk, t_address, t_data, t_cs, t_we);
    initial begin
        t_clk = 0;
        t_cs = 0;
        t_we = 0;
        end

    initial begin
        forever #5 t_clk = ~t_clk;
        end

    initial begin
        t_data = 8'b00000000;
        t_address = 5'b00000;
        #10 t_cs = 1;
        t_we = 1;
        for (i = 0; i < 25; i = i + 1) begin
            #10 t_data = t_data + 8'b00000001;
            t_address = t_address + 5'b00001;
            end
        #10 t_cs = 1;
```

```

t_re = 1;
t_we = 0;
t_address = 5'b00000;
for (i = 0; i < 25; i = i + 1) begin
#10 t_address = t_address + 5'b00001;
end
end
endmodule

```


#### Constraint File:

```


set_property PACKAGE_PIN H16 [get_ports clka_0]
set_property IOSTANDARD LVCMOS33 [get_ports clka_0]
set_property C_CLK_INPUT_FREQ_HZ 300000000 [get_debug_cores dbg_hub]
set_property C_ENABLE_CLK_DIVIDER false [get_debug_cores dbg_hub]
set_property C_USER_SCAN_CHAIN 1 [get_debug_cores dbg_hub]
connect_debug_port dbg_hub/clk [get_nets clka_0_IBUF]

```


#### Schematic:

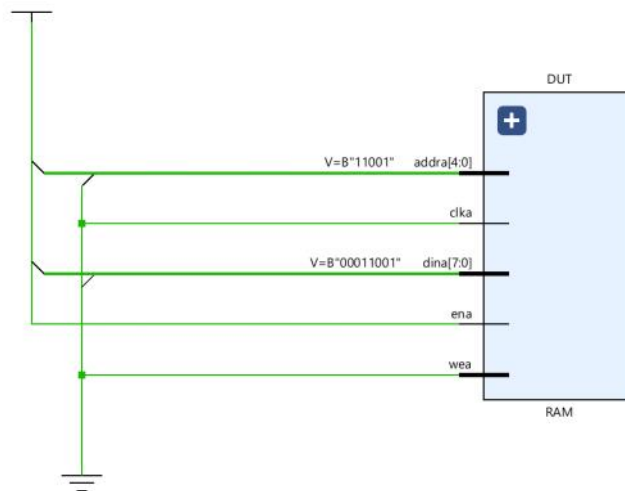


#### Simulation:

 

#### Block Design:

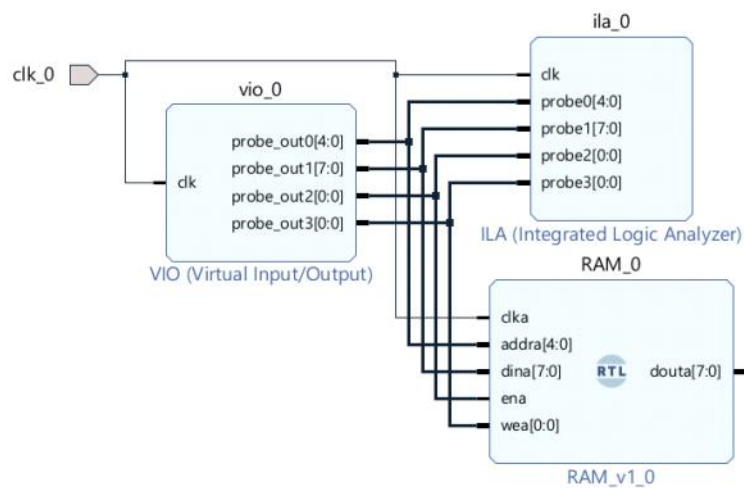

### Synthesis:

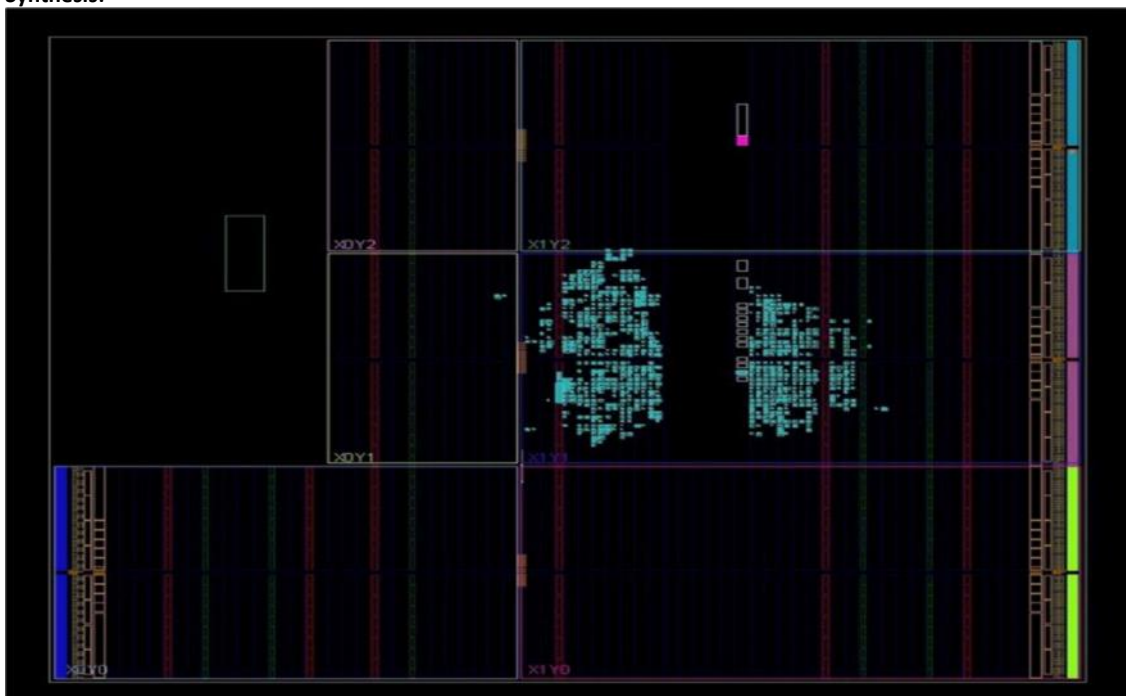

Question No. 2. Design a 4-bit Ring counter with [7:0]q bits. Perform behavioural simulations and follow the steps:

- Open block diagram.
- Right click -> Import module -> add the counter module to the diagram.
- Add Virtual Input-Output (VIO) and Integrated Logic Analyser (ILA) IP from IP catalogue.
- Follow the tutorial.

Provide inputs reset and clear through VIO and use system clock H16 for the design.

Sol: Code:

```
// Ring Counter
module counter(clk,reset,en,Q);
    input clk,reset,en;
    output reg [0:7]Q;

    //assign Q[0] = 1;
```

```

initial begin
    Q[0] <= 1;
    Q[1] <= 0;
    Q[2] <= 0;
    Q[3] <= 0;
    Q[4] <= 0;
    Q[5] <= 0;
    Q[6] <= 0;
    Q[7] <= 0;
end

always@(posedge clk)
begin
    if(en)
    begin
        if(reset)
        begin
            Q = 0;
        end
        else
        begin
            //    Q[0] = 1;
            Q[1] <= Q[0];
            Q[2] <= Q[1];
            Q[3] <= Q[2];
            Q[4] <= Q[3];
            Q[5] <= Q[4];
            Q[6] <= Q[5];
            Q[7] <= Q[6];
            Q[0] <= Q[7];
        end
    end
end
endmodule

```

#### **Testbench Code:**

```

module tb_counter();
    reg enable,reset,clk;
    wire [7:0]q;
    counter c1(clk,reset,enable,q);
    initial
    begin
        reset = 0;
        enable = 0; clk = 0;
    end
    always forever begin
        #5 clk = ~clk;
    end
    initial begin
        #5 reset = 1;
        #20 reset = 0;
        enable = 1;
    end
endmodule

```


#### **Constraint File:**

```


set_property IOSTANDARD LVCMOS33 [get_ports clk_0]
set_property PACKAGE_PIN H16 [get_ports clk_0]
set_property C_CLK_INPUT_FREQ_HZ 300000000 [get_debug_cores dbg_hub]
set_property C_ENABLE_CLK_DIVIDER false [get_debug_cores dbg_hub]
set_property C_USER_SCAN_CHAIN 1 [get_debug_cores dbg_hub]
connect_debug_port dbg_hub/clk [get_nets clk_0_IBUF]

```


#### **Schematic:**

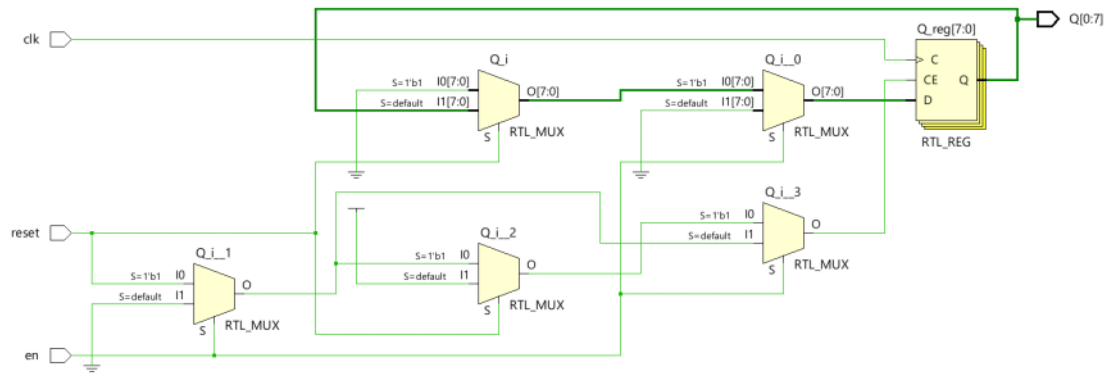


### Simulation:

 

### Block Diagram:

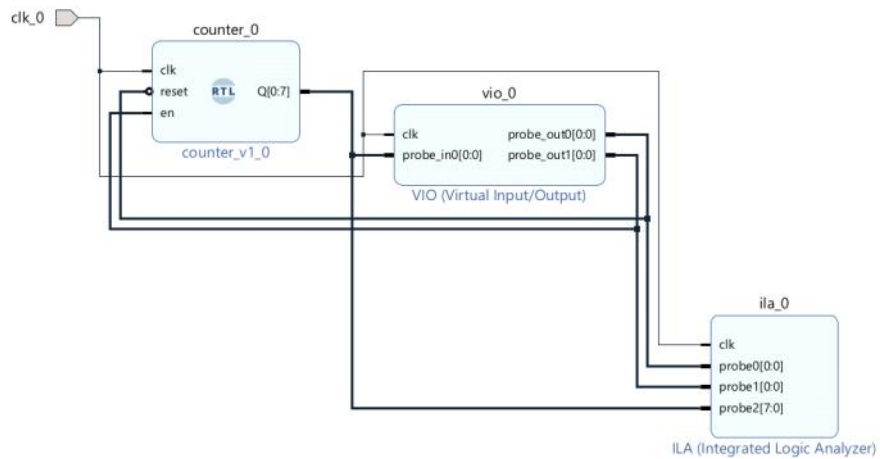

### Synthesized Schematic:

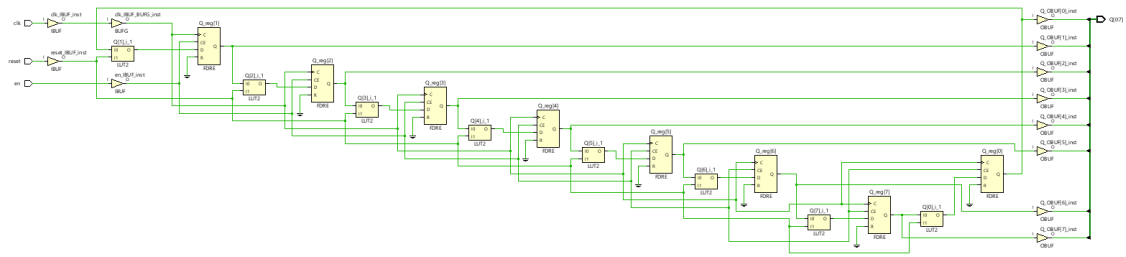

Synthesis:

