

Tutorial-4

B.Tech, 7th Sem

① @ Input signal,

$$V_{in} = 5 \sin(200\pi t)$$

$$V_{sig}^2 = V_{rms}^2 = \left(\frac{5}{\sqrt{2}}\right)^2 = \frac{25}{2} = 12.5 \text{ V}^2$$

Noise,

$$V_{noise}^2 = \frac{q^2}{12}, \quad \text{where } q = \frac{V_R}{2^{n-1}} \text{ for bipolar ADC}$$

$$= 1.27 \times 10^{-4} \text{ V}^2 \quad = \frac{5}{2^7} = 0.039$$

$$\therefore SNR_{max} = 10 \log \left(\frac{V_{sig}^2}{V_{noise}^2} \right)$$

$$= 10 \log \left(\frac{12.5}{1.27 \times 10^{-4}} \right)$$

$$= 10 \log(96,337.92)$$

$$\approx 49.838 \text{ dB}$$

⑥ $V_{rms}^2 = \left(\frac{2.5}{\sqrt{2}}\right)^2 \text{ V}^2 = \frac{6.25}{2} \text{ V}^2$

$$\therefore SNR_{max} = 10 \log \left(\frac{6.25/2}{1.27 \times 10^{-4}} \right)$$

$$= 10 \log(24,606.3)$$

$$\approx 43.91 \text{ dB}$$

② For triangular wave,


$$V_{sig}^2 = V_{rms}^2 = \left(\frac{V_R}{\sqrt{3}}\right)^2 = \left(\frac{5}{\sqrt{3}}\right)^2 = 8.33 \text{ V}^2$$

$$V_{noise}^2 = \frac{q^2}{12} = \left(\frac{V_R}{2^{n-1}}\right) \cdot \frac{1}{12} = \left(\frac{5}{2^7}\right)^2 \cdot \frac{1}{12} = 1.27 \times 10^{-4} \text{ V}^2$$

$$\therefore SNR_{max} = 10 \log \left(\frac{8.33}{1.27 \times 10^{-4}} \right)$$

$$\approx 48.17 \text{ dB}$$

③ 10-bit dual-slope ADC;

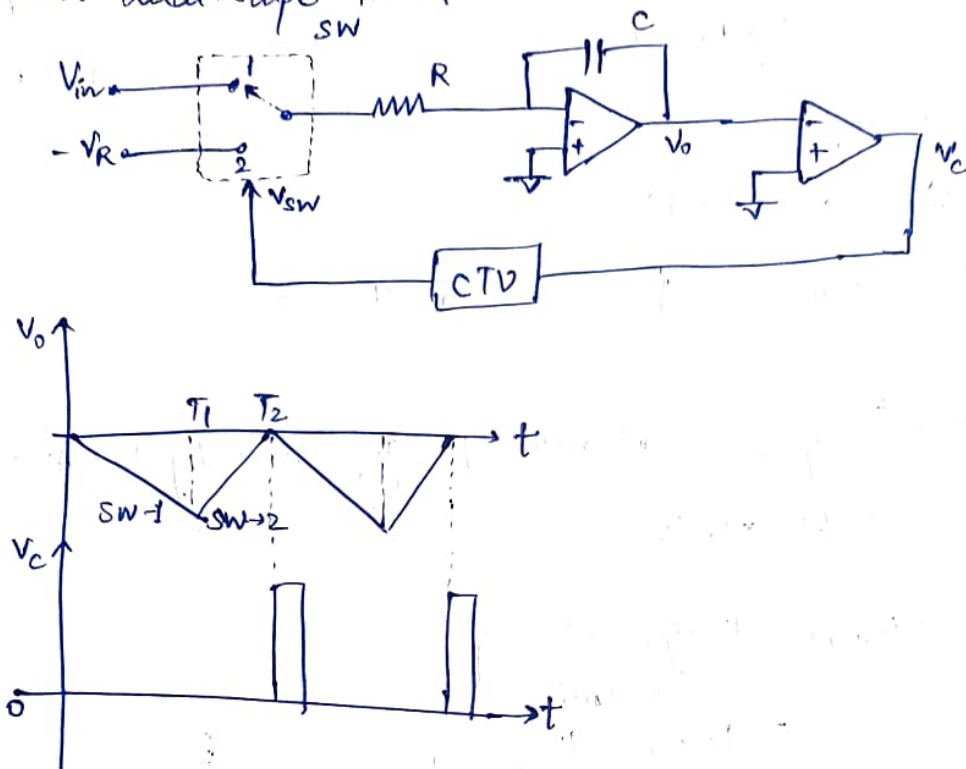

④ $f_{clk} = 1 \text{ MHz} \Rightarrow T_{clk} = \frac{1}{f_{clk}} = 1 \mu\text{s}$

For 10-bit dual-slope ADC,


integration time, $T_1 = 2^n \cdot T_{clk}$
 $= 2^{10} \cdot 1 \mu\text{s}$
 $= 1024 \mu\text{s}$
 $= 1.024 \text{ ms}$

max^m conversion time $= 2 T_1$
 $= 2.048 \text{ ms}$

$T_{interference} = \frac{1}{f_{interference}}$
 $= 0.02 \text{ s}$

Here, T_1 is not integral multiple of $T_{interference}$.

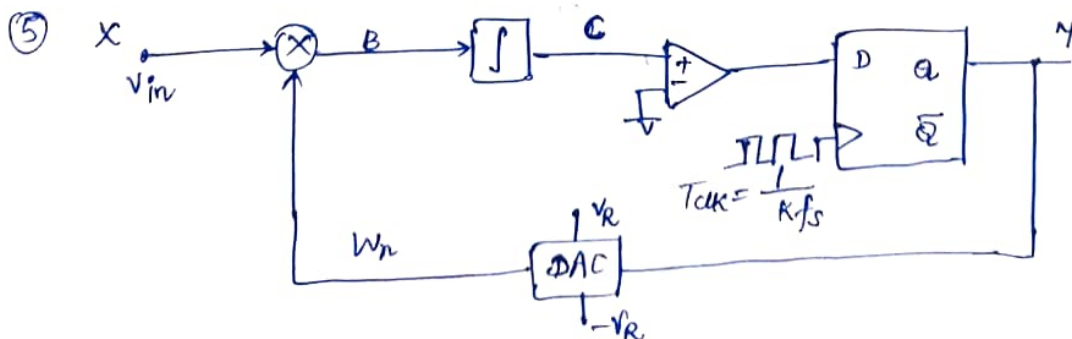\therefore Dual-slope ADC does not reject 50 Hz interference, hence o/p of ADC is not independent from 50 Hz interference.



$$X \in (-V_R, V_R), V_R = 1V$$

$$\in (-1V, 1V)$$

$$X = V_{in} = 0.25V$$

$$C_n = C_{n-1} + B_n, \quad n: \text{Sampling instance}$$

$$Y_n = \begin{cases} \text{High}(1), & C_n \geq 0 \\ \text{Low}(0), & C_n < 0 \end{cases}$$

$$W_n = \begin{cases} V_R, & Y_n = 1 \\ -V_R, & Y_n = 0 \end{cases}$$

$$B_n = X_n - W_{n-1}$$

$= X - W_{n-1}$, X should be constant for atleast few clock cycles.

n	X	B	C	Y	W_n
1	0.25	0.25	0.25	1	1
2	0.25	-0.75	-0.5	0	-1
3	0.25	1.25	+0.75	1	1
4	0.25	-0.75	0	1	1
5	0.25	-0.75	0.75	0	-1
6	0.25	1.25	0.5	1	1
7	0.25	-0.75	-0.25	0	-1
8	0.25	1.25	0	1	1


$\overline{Y} = \frac{5}{8}$

For 3-bit ADC,

X	D_2	D_1	D_0	
$(-1, -0.75)$	0	0	0	1/8
$(-0.75, -0.5)$	0	0	1	2/8
$(-0.5, -0.25)$	0	1	0	3/8
$(-0.25, 0)$	0	1	1	4/8
$(0, 0.25)$	1	0	0	5/8
$0.25 \in (0.25, 0.5)$	1	0	1	6/8 $\rightarrow \checkmark$
$(0.5, 0.75)$	1	1	0	7/8
$(0.75, 1)$	1	1	1	8/8

Digital o/p of the ADC $\equiv 101$.

(6)

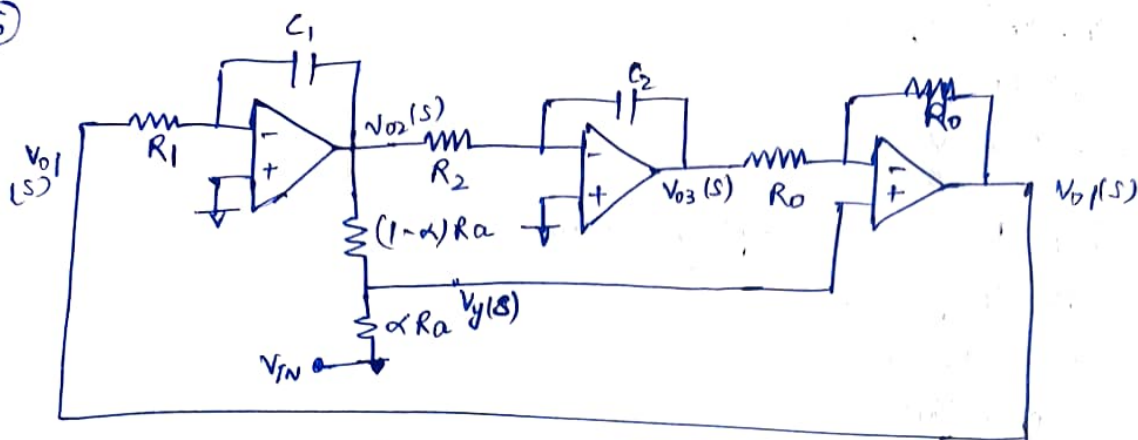

$$V_{02}(s) = -\frac{1}{sR_1C_1} V_{01}(s)$$

$$V_{03}(s) = -\frac{1}{sR_2C_2} V_{02}(s) = \frac{1}{s^2 R_1 R_2 C_1 C_2} V_{01}(s)$$

$$V_y(s) = (1-\alpha) V_{IN}(s) + \alpha V_{02}(s)$$

$$\text{Also, } V_{01}(s) = -V_{03}(s) + 2V_y(s)$$

$$\Rightarrow V_{01}(s) = \frac{V_{01}(s)}{s^2 R_1 R_2 C_1 C_2} + 2(1-\alpha) V_{IN}(s) - \frac{2\alpha V_{01}(s)}{sR_1C_1}$$

$$\Rightarrow V_{01}(s) \left[1 + \frac{2\alpha}{sR_1C_1} + \frac{1}{s^2 R_1 R_2 C_1 C_2} \right] = 2(1-\alpha) V_{IN}(s)$$

$$\Rightarrow V_{01}(s) \left[\frac{s^2 R_1 R_2 C_1 C_2 + 2\alpha R_2 C_2 s + 1}{s^2 R_1 R_2 C_1 C_2} \right] = 2(1-\alpha) V_{IN}(s)$$

$$\Rightarrow \frac{V_{01}}{V_{IN}}(s) = \frac{2(1-\alpha)s^2}{s^2 + \frac{2\alpha s}{R_1 C_1} + \frac{1}{R_1 R_2 C_1 C_2}} \quad \text{: HPF}$$

$$\frac{V_{02}}{V_{IN}}(s) = \frac{-2(1-\alpha)\frac{s}{R_1 C_1}}{s^2 + \frac{2\alpha s}{R_1 C_1} + \frac{1}{R_1 R_2 C_1 C_2}} \quad \text{: BPF}$$

$$\text{Comparing with } \frac{2K\xi\omega_0 s}{s^2 + 2\xi\omega_0 s + \omega_0^2} = \frac{K\left(\frac{\omega_0}{Q}\right) s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2},$$

$$\omega_0 = 2\pi f = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 2\pi \times 2000 = 12,560 \text{ rad/s.}$$

$$BW = \frac{f_0}{Q} = 5 \text{ Hz}$$

$$\Rightarrow Q = \frac{2K}{s} = 400.$$

$$\text{Take } R_1 = R_2 = R, C_1 = C_2 = C.$$

$$\Rightarrow \omega_0 = \frac{1}{RC}$$

Take $C = 1 \text{ nF}$.

$$R = \frac{1}{(12560)(1 \times 10^{-9})} \approx 79.62 \text{ k}\Omega.$$

Now, $\frac{W_0}{Q} = \frac{2\alpha}{RC}$

$$\Rightarrow \alpha = \frac{W_0 RC}{2Q} = \frac{12560 \times 79.62 \times 10^{-9} \times 10^3}{2 \times 400} = 1.25 \times 10^3.$$


$$K = \frac{1}{\alpha} - 1 = \frac{10^3}{1.25} - 1 = 799 \rightarrow 20 \log 799 \approx 58.05 \text{ dB}$$

Take $R_a = 200 \text{ k}\Omega$.

$$\alpha R_a = 250 \Omega.$$

$$(1-\alpha)R_a \approx 199.75 \text{ k}\Omega.$$

Take $R_b = 100 \text{ k}\Omega$.

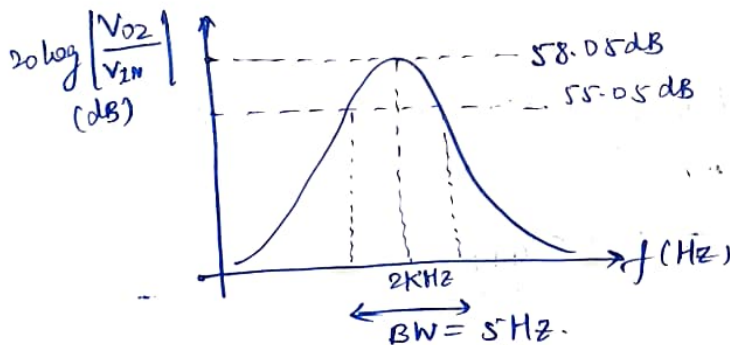

$$\textcircled{7} \quad \frac{V_{O3}}{V_{IN}}(s) = \frac{2(1-\alpha)}{s^2 + \frac{2\alpha s}{R_1 C_1} + \frac{1}{R_1 R_2 C_1 C_2}} \quad ; \text{LPF}$$

$$\begin{aligned} \text{Notch filter : } \frac{V_{O1}}{V_{IN}}(s) + \frac{V_{O3}}{V_{IN}}(s) \\ \equiv \frac{2(1-\alpha)s^2 + 2(1-\alpha)}{s^2 + \frac{2\alpha s}{R_1 C_1} + \frac{1}{R_1 R_2 C_1 C_2}} \end{aligned}$$

comparing with $\frac{K(s^2 + \omega_0^2)}{s^2 + 2\xi\omega_0 s + \omega_0^2}$,

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 2\pi \times 500 \approx 3140 \text{ rad/s}$$

$$K = 2(1-\alpha) = 1 \Rightarrow \alpha = 1/2.$$

$$BW = \frac{f}{Q} = \frac{2\alpha}{R_1 C_1} \quad (\alpha = 2\zeta_p \omega_0)$$

$$Q = \frac{f_0}{BW} = \frac{500}{10} = 50.$$

Take $C_1 = 10 \text{ nF}$.

$$R_1 = \frac{2 \left(\frac{1}{2} \right) 500}{10 \times 10^{-6} \times \frac{500}{10}} = 10^4 = 10 \text{ k}\Omega.$$

Take $C_2 = 10 \text{ nF}$.

$$\omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\Rightarrow R_2 = \frac{1}{R_1 C_1 C_2 \omega_0^2}$$


$$= \frac{1}{(3140)^2 (10 \times 10^3) (10 \times 10^{-6})^2}$$

$$= 0.10 \Omega.$$


Instead Take $C_2 = 1 \text{ nF}$.

$$R_2 = 1 \Omega.$$

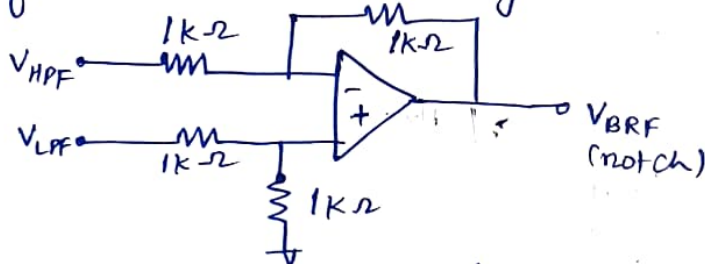Notch filter can be obtained using notch summing amplifier.



(8) (a)

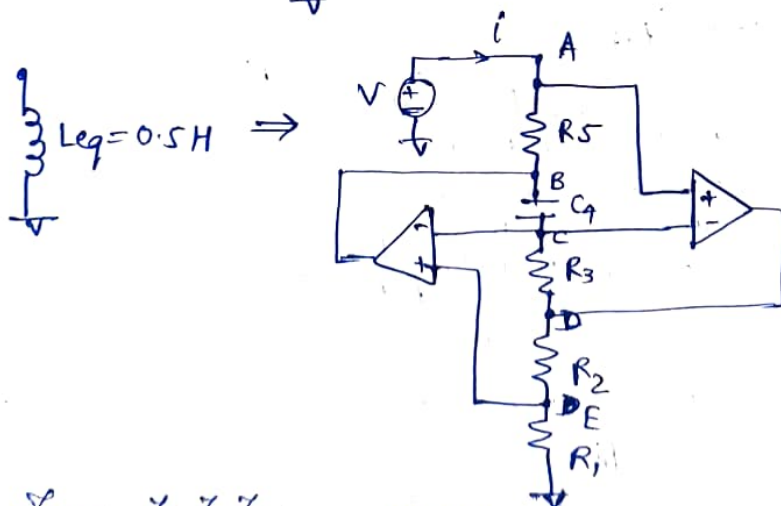

$$Z_{eq} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} = \frac{R_1 R_3 R_5}{R_2 \left(\frac{1}{sC_4} \right)} = s \left(\frac{R_1 R_3 R_5 C_4}{R_2} \right)$$


$$Z_{eq} = \frac{R_1 R_3 R_5 C_4}{R_2} = 0.5 \text{ H}$$

Given that $C_4 = 10 \text{ nF}$, $R_1 = R_3 = R_5 = R_2$.

$$\therefore \frac{R^3 C_4}{R} = 0.5 \Rightarrow R^2 (10 \times 10^{-9}) = 0.5$$

$$\Rightarrow R^2 = 0.05 \times 10^9 = 5 \times 10^7$$
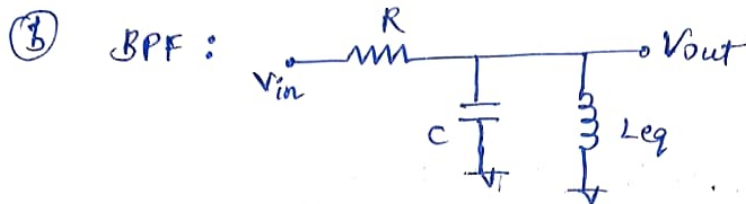
$$\Rightarrow R \approx 7 \text{ k}\Omega$$




$$\omega_0 = \frac{1}{\sqrt{L_{eq} C}} = 2\pi \times 5 \times 10^3 = 10000\pi$$

$$Q = R \sqrt{\frac{C}{L_{eq}}} = 25$$

$$\Rightarrow R = 25 \sqrt{\frac{0.5}{2 \times 10^{-9}}} \approx 15.8 \text{ k}\Omega \times 25 \approx 395.3 \text{ k}\Omega$$
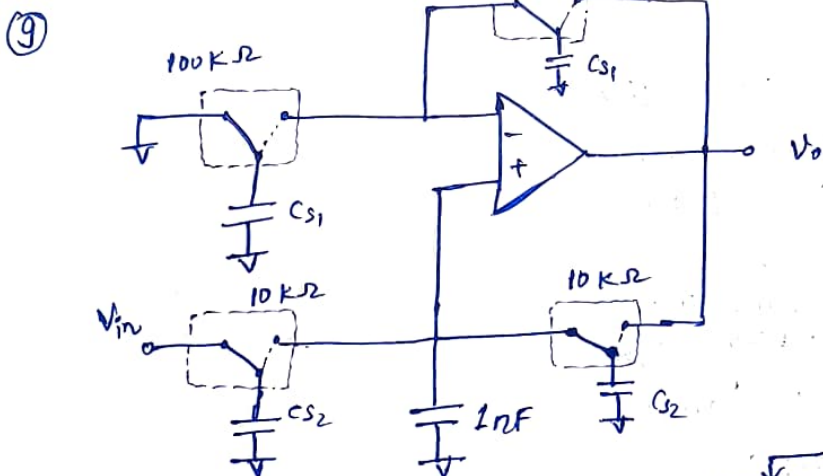
$$C = \frac{1}{L_{eq} (31400)^2} \approx 2 \text{ nF}$$




$$R_{eq} = \frac{1}{f_c C_s}$$

$$C_{s1} = \frac{1}{R_{eq} f_c}$$

$$= \frac{1}{100 \times 10^3 \times 10^6} = 0.01 \text{ nF}$$
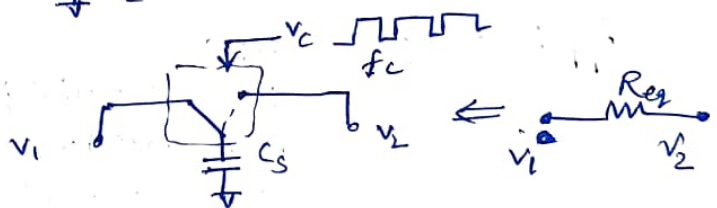
$$C_{s2} = \frac{1}{10 \times 10^3 \times 10^6} = 0.1 \text{ nF}$$



- ⑩ LF398 is a precision sample-and-hold amplifier. It captures (samples) an analog input voltage and stores (holds) it on a capacitor, providing a constant output voltage even when the input changes.

Modes of operation:

① Sample Mode:

- The control (sample/hold) pin is ^{logic} high.
- The circuit tracks the input signal, the output follows the ip signal.

② Hold Mode:

- The control pin is logic low.
- The switch opens, isolating the hold capacitor.
- The output remains constant at the last sampled value.

Specifications:

Supply voltage: $\pm 5V$ to $\pm 18V$

I/p offset voltage: $\sim 2mV$

Acquisition time: $< 10\mu s$

Hold step: $0.5mV$

Drift rate: $0.01mV/ms$


I/p impedance: very high

Output current: $\pm 10mA$

Applications:

- ADC
- Data acquisition and multiplexing systems
- Peak detector
- Digital control system.

⑪ ①

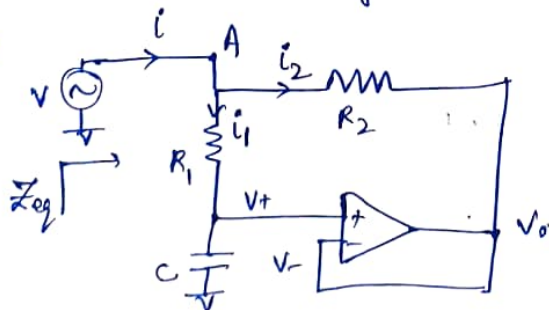

$$V^+ = \frac{1/sC}{R_1 + 1/sC} V = V^- = V_0$$


$$i_1 = \frac{V}{R_1 + 1/sC}$$

$$\begin{aligned}
 i_2 &= \frac{V - V_0}{R_2} = \left[V - \frac{1/s_c V}{R_1 + 1/s_c} \right] \frac{1}{R_2} \\
 &= \frac{V(R_1 + 1/s_c) - V/s_c}{R_2(R_1 + 1/s_c)} \\
 &= \frac{V R_1 + V/s_c - V/s_c}{R_2 + 1/s_c} = \frac{V R_1}{R_2(R_1 + 1/s_c)}
 \end{aligned}$$

$$\begin{aligned}
 i &= i_1 + i_2 \\
 &= V \left[\frac{1}{R_1 + 1/s_c} + \frac{R_1}{R_2(R_1 + 1/s_c)} \right] \\
 &= V \left[\frac{R_2 + R_1}{R_2(R_1 + 1/s_c)} \right]
 \end{aligned}$$

$$\therefore Z_{eq} = \frac{V}{i} = \frac{R_2(R_1 + 1/s_c)}{R_1 + R_2}$$

⑤

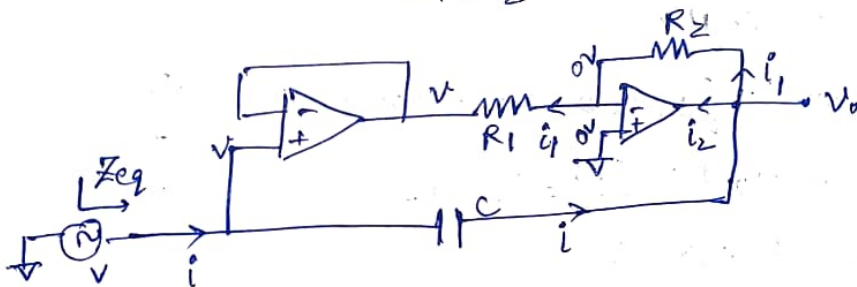

$$i = \frac{V - V_0}{1/s_c}, \quad i_1 = \frac{V_0}{R_2} = -\frac{V}{R_1} \Rightarrow V_0 = -\frac{R_2}{R_1} V$$

$$\begin{aligned}
 \Rightarrow i &= (V - V_0) s_c \\
 &= s_c \left(V + \frac{R_2}{R_1} V \right) \\
 &= s_c V \left(\frac{R_1 + R_2}{R_1} \right)
 \end{aligned}$$

$$\Rightarrow \frac{V}{i} = Z_{eq} = \frac{1}{s_c \left(\frac{R_1 + R_2}{R_1} \right)} = \frac{R_1}{s_c (R_1 + R_2)}$$

AV491-Advanced Sensors and Interface Electronics

Tutorial - 2

① Input voltage noise;

$$\begin{aligned} \textcircled{a} \quad E_N^2 &= \int_{f_L}^{f_H} e_n^2 df \\ &= \int_{0.1}^{100} e_{nw}^2 \left[1 + \frac{f_{CE}}{f} \right] df \\ &= e_{nw}^2 \left[f + f_{CE} \ln f \right] \Big|_{0.1}^{100} \\ &= (20 \times 10^{-9})^2 \left[(100 - 0.1) + 200 \ln \left(\frac{100}{0.1} \right) \right] \\ &= (20 \times 10^{-9})^2 [1481.45] \\ &= 5.9258 \times 10^{-13} \text{ V} \end{aligned}$$

$$\therefore E_N = 0.7698 \mu\text{V}.$$

$$\begin{aligned} \textcircled{b} \quad E_N^2 &= (20 \times 10^{-9})^2 \left[(20000 - 20) + 200 \ln \left(\frac{20000}{20} \right) \right] \\ &= (20 \times 10^{-9})^2 [21361.55] \\ &= 8.545 \times 10^{-12} \text{ V} \end{aligned}$$

$$\therefore E_N = 2.923 \mu\text{V}.$$

$$\begin{aligned} \textcircled{c} \quad E_N^2 &= (20 \times 10^{-9})^2 \left[(10^6 - 0.1) + 200 \ln \left(\frac{10^6}{0.1} \right) \right] \\ &= (20 \times 10^{-9})^2 [1003223.5] \\ &= 4.012 \times 10^{-10} \text{ V} \end{aligned}$$

$$\therefore E_N \approx 20 \mu\text{V}.$$

② Thermal noise;

$$\begin{aligned} E_T &= \sqrt{4kTB R} \\ &= \sqrt{4 \times 1.38 \times 10^{-23} \times 298 \times 1 \times 10^3} \\ &\approx 4 \text{ nV}. \end{aligned}$$

$$\begin{aligned} \textcircled{b} \quad E_T &= \sqrt{4 \times 1.38 \times 10^{-23} \times 77 \times 1 \times 10^3} \\ &= 2.06 \text{ nV} \end{aligned}$$

$$\begin{aligned} \textcircled{c} \quad E_T &= \sqrt{4 \times 1.38 \times 10^{-23} \times 4.2 \times 1 \times 10^3} \\ &= 0.481 \text{ nV} \end{aligned}$$

③ Shot noise, $i_{SH}^2 = 2q I_{DC}$

$$= 2 \times 1.6 \times 10^{-19} \times 10 \times 10^3$$

$$= 3.2 \times 10^{-21}$$

$$P_{DSH} = I_{SH}^2 = \cancel{(3.2 \times 10^{-21})} \times B \times i_{SH}^2$$

$$= 3.2 \times 10^{-21} \times 10 \times 10^3$$

$$= 3.2 \times 10^{-16} \Rightarrow I_{SH} = 1.788 \times 10^{-8} \text{ A}$$

B-E resistance, $r_e = \frac{V_T}{I_E} = \frac{26 \text{ mV}}{10 \text{ mA}} = 2.6 \Omega$

\therefore voltage noise, $v_{SH} = I_{SH} r_e$

$$= 1.788 \times 10^{-8} \times 2.6$$

$$= 46.48 \text{ nV}$$

④ Thermal noise,

$$E_T = \sqrt{4KTBR}$$

$$= \sqrt{4 \times 1.38 \times 10^{-23} \times 300 \times 10 \times 10^3 \times 2.6}$$

$$= 2.07 \times 10^{-8} \text{ V}$$

$$= 20.7 \text{ nV}$$

⑤ (a) Voltage spectral density, $e_T = \sqrt{4KTR}$

$$= 4 \times 1.38 \times 10^{-23} \times 300 \times 10 \times 10^3$$

$$= 1.656 \times 10^{-16} \text{ V}/\sqrt{\text{Hz}}$$

Current spectral density, $i_T = \frac{\sqrt{4KT}}{R}$

$$= \frac{4 \times 1.38 \times 10^{-23} \times 300}{10 \times 10^3}$$

$$= 1.656 \times 10^{-24} \text{ A}/\sqrt{\text{Hz}}$$

⑥ RMS voltage noise,

$$e_T = \sqrt{4KTBR}$$

$$= \sqrt{4 \times 1.38 \times 10^{-23} \times 300 \times 19980 \times 10 \times 10^3}$$

$$= 1.818 \mu\text{V}$$

⑥ (a) $I_{SH}^2 = 2q I_{DC} B$

$$= 2 \times 1.6 \times 10^{-19} \times 10^6 \times 10^6$$

$$= 3.2 \times 10^{-19} \text{ A}^2$$

$$I_{DC}^2 = 10^{-12} \text{ A}^2$$

$$\therefore \text{SNR} = 10 \log \left(\frac{I_{DC}^2}{I_{SH}^2} \right) = 10 \log \left(\frac{10^{-12}}{3.2 \times 10^{-19}} \right)$$

$$\approx 64.95 \text{ dB}$$

$$\textcircled{6} \quad I_{SH}^2 = 2 \times 1.6 \times 10^{-19} \times 10^{-9} \times 10^6$$

$$= 3.2 \times 10^{-22} \text{ A}^2$$

$$I_{Dc}^2 = 10^{-18}$$

$$\therefore \text{SNR}_{(dB)} = 10 \log \left(\frac{10^{-18}}{3.2 \times 10^{-22}} \right)$$

$$\approx 34.95 \text{ dB}$$

$$\textcircled{7} \quad \text{2nd order LPF: } H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\text{Noise BW, } B = \frac{1}{|H(0)|^2} \int_0^\infty |H(jf)|^2 df$$

$$= 1 \cdot \int_0^\infty \frac{f_c^2}{f^2 + j2\zeta f f_c + f_c^2} df$$

$$= \frac{f_c}{4\zeta} (4\zeta^2 + 1)$$

$$\textcircled{i} \quad \zeta = 1 \Rightarrow B = \frac{f_c}{4} (5) = 1.25 f_c$$

$$\textcircled{ii} \quad \zeta = 2 \Rightarrow B = \frac{f_c}{8} (17) = 2.125 f_c$$

$$|H(j\omega)| = \frac{f_c^2}{f_c^2 + j2\zeta f f_c + f^2}$$


$$|H(0)| = \frac{f_c^2}{f_c^2} = 1$$

$$H(jf) = \frac{f_c^2}{f_c^2 + j2\zeta f f_c + f^2}$$


$$|H(jf)|^2 = \frac{f_c^4}{(f_c^2 + f^2)^2 + 4\zeta^2 f^2 f_c^2}$$

$$|H(0)|^2 = 1$$


BJT Noise model:

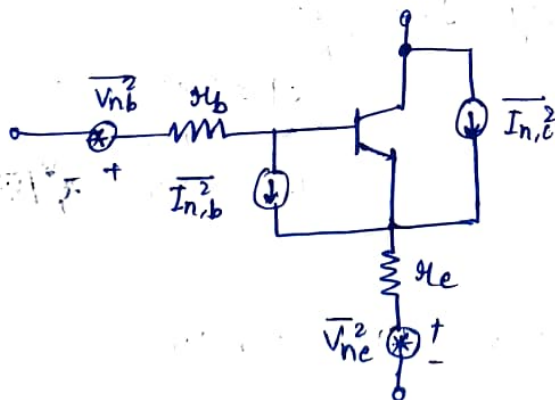


JFET Noise model:

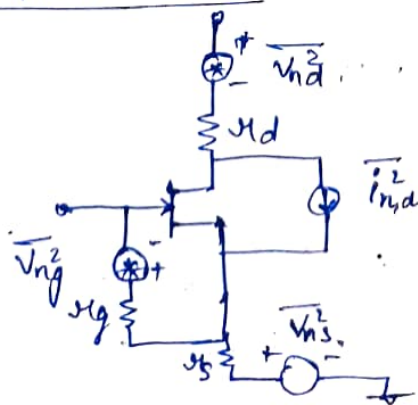

MOSFET Noise model:

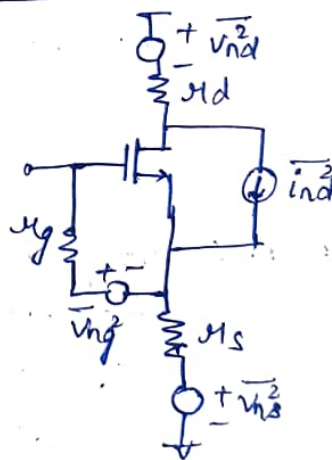

⑨

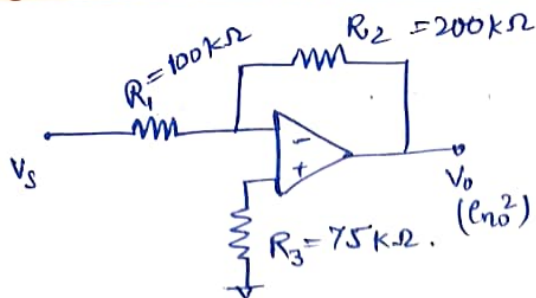

$$G = 2 \quad \left| \quad f_N = \frac{A_0 f_B}{G_N} = \frac{1\text{ MHz}}{3} \right.$$

$$e_{ni}^2 = e_{nw}^2 \left(1 + \frac{f_{CE}}{f} \right)$$

$$i_n^2 = i_{nw}^2 \left(1 + \frac{f_{CE}}{f} \right)$$

$$e_{ni}^2 = e_n^2 + 8kTR_3 + 2i_n^2 R_3^2$$

As \$R_3\$ is very large,

$$e_{ni}^2 \approx 2i_n^2 R_3^2$$

$$= 2i_{nw}^2 \left(1 + \frac{f_{CE}}{f} \right) R_3^2$$

$$e_{no}^2 = \frac{G_N^2}{\left(1 + \left(\frac{f}{f_N} \right)^2 \right)} e_{ni}^2$$

$$\Rightarrow E_{no}^2 = \int_0^{f_H} e_o^2 df = 2G_N^2 i_{nw}^2 R_3^2 \int_{0.1}^{\infty} \frac{\left(1 + \frac{f_{CE}}{f} \right)}{\left(1 + \left(\frac{f}{f_N} \right)^2 \right)} df$$

$$= 2G_N^2 i_{nw}^2 R_3^2 \left[f_N \tan^{-1} \left(\frac{f}{f_N} \right) + \frac{f_{CE}}{2} \ln \left(\frac{f^2}{f^2 + f_N^2} \right) \right]_{0.1}^{\infty}$$

$$= 2 \times 3^2 \times (500 \times 10^{-15})^2 \times (75 \times 10^3)^2 \times$$

$$\left[\frac{10^6}{3} \tan^{-1} \left(\frac{\pi}{2} \right) + \frac{2 \times 10^3}{2} \ln(1) - \frac{10^6}{3} \left(\frac{0.1}{10^6} \right) - \frac{2 \times 10^3}{2} \ln \left(\frac{0.1}{10^6} \right) \right]$$

$$\approx 18 \times 25 \times 10^{-26} \times 75^2 \times 10^6 \times \left[\frac{\pi}{2} \times \frac{10^6}{3} - 0.1 + 10^3 (-15.02) \right]$$

$$= 2531250 \times 10^{-20} [0.52 \times 10^6 - 0.1 - 15.02 \times 10^3]$$

$$= 1.32 \times 10^{-8} \text{ V}^2$$

$$\Rightarrow E_{no} = 1.14 \times 10^{-4} = 114 \mu\text{V}$$

$$V_{rms} = \frac{1}{\sqrt{2}} \Rightarrow G V_{rms} = \sqrt{2}$$

$$\therefore \text{SNR} = 20 \log \left(\frac{G V_{rms}}{E_{no}} \right)$$

$$= 20 \log \left(\frac{\sqrt{2}}{114 \times 10^{-6}} \right) \approx 81.87 \text{ dB}$$

⑩ For low effect of bias current, R_3 has to be very low.

$$e_{ni}^2 = e_n^2 + 8KT R_3 + 2i_{nw}^2 R_3^2$$

$$\approx e_n^2 = i_{nw}^2 \left(1 + \frac{f_{CE}}{f} \right)$$

$$e_o^2 = \frac{G_N^2 e_{ni}^2}{1 + f^2/f_N^2} \cdot (1 + f_{CE}/f) = \frac{G_N^2 e_{nw}^2}{4kf} \left(\frac{1}{1 + f^2/f_N^2} + \frac{f_{CE}/f}{1 + f^2/f_N^2} \right)$$

$$\Rightarrow E_{No}^2 = \int_{f_L}^{f_H} e_o^2 df = G_N^2 e_{nw}^2 \left[\frac{\pi}{2} f_N + f_L - \frac{f_{CE}}{2} \cdot 2 \ln \left(\frac{f_H}{f_{NL}} \right) \right]$$

$$= 3^2 \times (20 \times 10^{-9})^2 \left[\frac{\pi}{2} (10^6) - 0.1 - 200 \ln \left(\frac{10^6}{\frac{10^6}{3 \times 0.1}} \right) \right]$$

$$= 36 \times 10^{-16} \left[0.52 \times 10^6 - 0.1 - 200 \ln(15.02) \right]$$

$$= 18.72 \times 10^{-10} \text{ V}^2$$

$$E_o = 4.32 \times 10^{-5} \text{ V} = 43.2 \mu\text{V}$$

$$\therefore \text{SNR} = 20 \log \left(\frac{\sqrt{2}}{4.32 \times 10^{-5}} \right) \approx 90.3 \text{ dB}$$

$$e_{ni}^2 = 2i_{nw}^2 R_3^2 = 2i_{nw}^2 \left(1 + \frac{f_{CE}}{f} \right) R_3^2$$

$$e_o^2 = \frac{G_N^2}{1 + f^2/f_N^2} e_{ni}^2$$

$$\therefore E_{No}^2 = \int_{f_L}^{f_H} e_o^2 df = 2G_N^2 i_{nw}^2 R_3^2 \int_{0.1}^{\infty} \frac{1 + f_{CE}/f}{1 + f^2/f_N^2} df$$

$$= 2G_N^2 i_{nw}^2 R_3^2 \left[f_N \tan^{-1} \left(\frac{f}{f_N} \right) + \frac{f_{CE}}{2} \ln \left(\frac{f^2}{f^2 + f_N^2} \right) \right]_{0.1}^{\infty}$$

$$\approx 2G_N^2 i_{nw}^2 R_3^2 \frac{\pi}{2} f_N$$

$$\text{For } E_{No}^2 = (50 \times 10^{-6})^2,$$

$$(50 \times 10^{-6})^2 = 2 \times 9 \times (500 \times 10^{-15})^2 \times R_3^2 \times \frac{\pi}{2} \times \frac{10^6}{3}$$

$$\Rightarrow 25 \times 10^{-10} = 3 \times 25 \times 10^{-26} \times R_3^2 \times \pi \times 10^6$$

$$\Rightarrow R_3^2 = \frac{10^{-10}}{3 \times 10^{-20} \times \pi} = 0.106 \times 10^{10}$$

$$\Rightarrow R_3 = 0.326 \times 10^5 \Rightarrow R_3 = 326 \text{ K}\Omega$$

Let $R_1 = 400 \text{ K}\Omega$.

Then, $R_3 = R_1 \parallel R_2$

$$\Rightarrow 326 \text{ K} = \frac{(400 \text{ K}) R_2}{R_2 + 400 \text{ K}}$$

$$\Rightarrow 326 \text{ K} R_2 + \cancel{326000} \text{ M} = 400 \text{ K} R_2$$

$$\Rightarrow 74 \text{ K} R_2 = 130400 \text{ M}$$

$$\Rightarrow R_2 = \frac{130400}{74} \text{ K}$$

$$= 1.76 \text{ M}\Omega$$

$$\text{SNR} = 20 \log \frac{\sqrt{2}}{50 \times 10^{-6}}$$

$$\approx 89 \text{ dB}$$

(11) $R_3 \rightarrow$ very large.

$$e_{ni}^2 \approx 2 i_n^2 R_3^2$$

$$\therefore E_{n0}^2 \approx 2 G_n^2 i_n^2 R_3^2 \frac{\pi}{2} f_n$$

$$= 9 \times 9 \times (170 \times 10^{-15})^2 \times (75 \times 10^3)^2 \times \frac{\pi}{2} \times \frac{0.6 \times 10^6}{2}$$

$$= 9 \times 17^2 \times 10^{-28} \times 75^2 \times 10^6 \times \frac{\pi}{2} \times 0.6 \times 10^6$$

$$= 13786,437.94 \times 10^{-16}$$

$$= 13.79 \mu\text{V}^2$$

$$\therefore E_{n0} = 3.71 \text{ mV}$$

As $E_{n0} \propto R$, to reduce the noise by half, take $R_3 = \frac{75}{2} \text{ K}\Omega$.

(12) $e_n^2 = e_{nw}^2 \left(1 + \frac{f_{CE}}{f}\right)$

$$= A_1 + \frac{A_2}{f}$$

$$\left| \begin{array}{l} f_1 = 10 \text{ Hz} \\ f_2 \gg f_{CE} \end{array} \right.$$

$$e_n^2(f_1) = 20^2 \times 10^{-18} \text{ V}^2/\text{Hz}$$

$$e_n^2(f_2) = 36 \times 10^{-18} \text{ V}^2/\text{Hz}$$

At $f = f_2$, $e_n^2 = A_1 + \frac{A_2}{f_2} \approx A_1 = 36 \times 10^{-18} \text{ V}^2/\text{Hz}$

At $f = f_1$, $e_n^2 = 20^2 \times 10^{-18} = 36 \times 10^{-18} + \frac{A_2}{10}$

$$\Rightarrow A_2 = 364 \times 10^{-18} \times 10$$

$$= 364 \times 10^{-17} \text{ V}^2$$

RMS o/p noise, 1M

$$E_{N_o}^2 = \int_{1\text{m}}^{1\text{M}} n^2 df = \int_{1\text{m}}^{1\text{M}} \left(A_1 + \frac{A_2}{f} \right) df$$

$$= A_1 (10^6 - 10^{-3}) + A_2 \ln \left(\frac{10^6}{10^{-3}} \right)$$

$$\approx A_1 \times 10^6 + A_2 \ln 10^9$$

$$= 36 \times 10^{-18} \times 10^6 + 364 \times 10^{-17} \times 20.72$$

$$= 36 \times 10^{-12} + 7543.27 \times 10^{-17}$$

$$\approx 36 \times 10^{-12} \text{ V}^2$$

$$\Rightarrow E_N \approx 6 \mu\text{V} / \sqrt{\text{Hz}}$$

(13) TF of amplifier, $H_1(f) = H_2(f) = \frac{A_0}{1+jf/f_B} = \frac{1}{1+jf/f_B}$

$$\therefore \text{BW} = \int_0^\infty |H_1(f)|^2 |H_2(f)|^2 df$$

$$= \int_0^\infty \frac{1}{(1+f^2/f_B^2)^2} df$$

$$\text{Take } f/f_B = x \Rightarrow df = f_B dx$$

$$\Rightarrow \text{BW} = \int_0^\infty \frac{1}{(1+x^2)^2} f_B dx$$

$$\text{Take } x = \tan \theta \quad \left| \begin{array}{l} x=0 \Rightarrow \tan \theta = 0 \Rightarrow \theta = 0 \\ x=\infty \Rightarrow \tan \theta = \infty \Rightarrow \theta = \pi/2 \end{array} \right.$$


$$\Rightarrow dx = \sec^2 \theta d\theta$$

$$\Rightarrow \text{BW} = f_B \int_0^{\pi/2} \frac{1}{(1+\tan^2 \theta)^2} \sec^2 \theta d\theta$$

$$= f_B \int_0^{\pi/2} \frac{1}{\sec^2 \theta} d\theta = f_B \int_0^{\pi/2} \cos^2 \theta d\theta = f_B \int_0^{\pi/2} \left(\frac{1+\cos 2\theta}{2} \right) d\theta$$

$$= \frac{f_B}{2} [0 + \sin 2\theta]_0^{\pi/2}$$
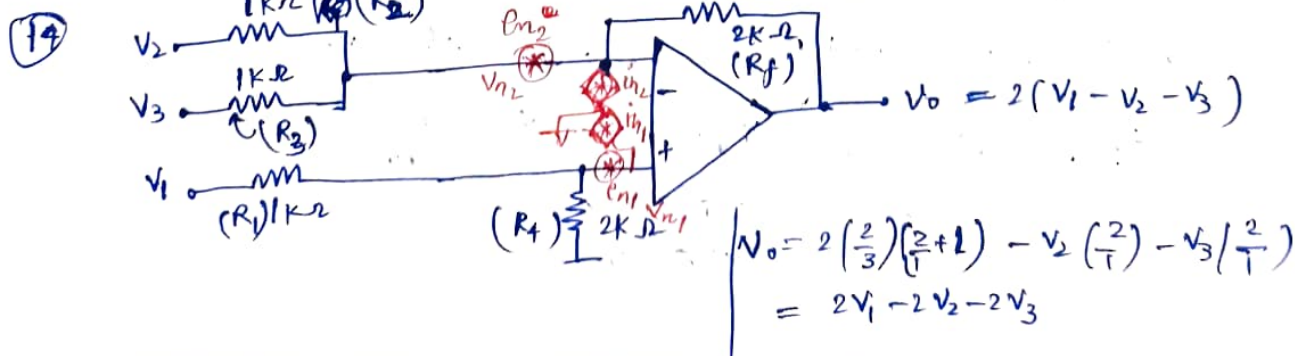
$$= f_B/2 (\pi/2) = \boxed{\frac{f_B \pi}{4}}$$



$$V_o = \left(1 + \frac{R_f}{R_2 \parallel R_3}\right) [V_{n1} - V_{n2} + I_{n1}(R_1 \parallel R_4) + I_{n2}(R_1 \parallel R_2 \parallel R_f)]$$

$$G_N = 1 + \frac{R_f}{R_2 \parallel R_3}$$

$$e_o^2 = G_N^2 \cdot e_{ni}^2$$


$$E_o^2 = \int_{f_L}^{f_H} e_o^2 \cdot df = \int_{f_L}^{f_H} G_N^2 \cdot e_{ni}^2 \cdot df$$

$$e_{ni}^2 = V_{n1}^2 + i_{n1}^2 [R_1 \parallel R_4 + R_3 \parallel R_2 \parallel R_f]$$

$$e_{ni}^2 = e_{n\omega}^2 \left(1 + \frac{f_{CE}}{f}\right) + i_{n\omega}^2 \left(1 + \frac{f_{CE}}{f}\right) (R_1 \parallel R_4 + R_3 \parallel R_2 \parallel R_f)$$

$$\therefore E_o^2 = \int_{f_L}^{f_H} \left(1 + \frac{R_f}{R_2 \parallel R_3}\right)^2 \left[\frac{e_{n\omega}^2 \left(1 + \frac{f_{CE}}{f}\right) + i_{n\omega}^2 \left(1 + \frac{f_{CE}}{f}\right) \times (R_1 \parallel R_4 + R_3 \parallel R_2 \parallel R_f)}{(1 + f^2/f_B^2)} \right] df$$

(15) @ Difference amplifier:

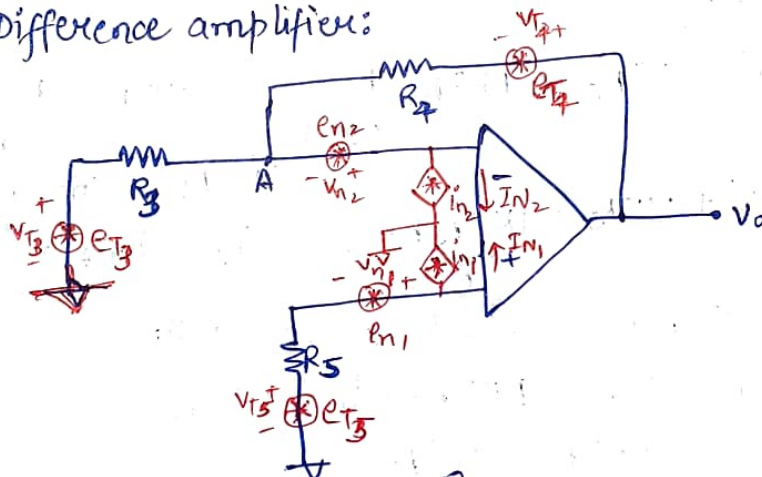

$$V_p = V_{n1} + V_{T5} - I_{n1} R_5 \quad \text{--- (1)}$$

$$V_n = V_{n2} + V_A \quad \text{--- (2)}$$

KCL at node A:

$$\frac{V_A - V_{T3}}{R_3} + \frac{V_A - V_o + V_{T4}}{R_4} + I_{N2} = 0$$

$$\Rightarrow V_A \left[\frac{1}{R_3} + \frac{1}{R_4} \right] - \frac{V_{T3}}{R_3} + \frac{V_{T4}}{R_4} - \frac{V_o}{R_4} + I_{N2} = 0$$

$$\text{As } V_A = V_n - V_{n2},$$

$$\Rightarrow (V_n - V_{n2}) \left(\frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{V_{T3}}{R_3} + \frac{V_{T4}}{R_4} - \frac{V_o}{R_4} + I_{N2} = 0$$

$$V_n = V_{n2} + \left(\frac{V_{T3}}{R_3} - \frac{V_{T4}}{R_4} \right) \left(\frac{R_3 R_4}{R_3 + R_4} \right) + \left(\frac{V_o}{R_4} - I_{N2} \right) \frac{R_3 R_4}{R_3 + R_4}$$

$$= V_{n2} + \frac{V_{T3}}{R_3} - \frac{V_{T4}}{R_4} + \frac{V_o R_3}{R_3 + R_4} - I_{N2} \frac{R_3 R_4}{R_3 + R_4} \quad \text{--- (3)}$$

Now, $V_o = A(V_p - V_n) \Rightarrow V_o/A = V_p - V_n$

If $A \rightarrow \text{very large } (\infty)$, $V_o/A \rightarrow 0 \Rightarrow V_p = V_n$

$$\therefore V_{n1} + V_{T5} - I_{N1} R_5 = V_{n2} + \frac{V_{T3} R_1}{R_3 + R_4} - \frac{V_{T4} R_3}{R_3 + R_4} + \frac{V_o R_3}{R_3 + R_4} - I_{N2} (R_3 \parallel R_4)$$

$$\frac{V_o R_3}{R_3 + R_4} = V_{n1} - V_{n2} + V_{T5} - \frac{V_{T3} R_1}{R_3 + R_4} + \frac{V_{T4} R_3}{R_3 + R_4} - I_{N2} (R_3 \parallel R_4) - I_{N1} R_5$$

At $V_o = 0$, $\frac{V_o}{1 + R_4/R_3} = V_{ni}$

Noise gain, $G_N = 1 + R_3/R_4$

$\Rightarrow V_o = G_N V_{ni}$

$e_o^2 = G_N^2 e_{ni}^2$

$$e_{ni}^2 = e_{n1}^2 + e_{n2}^2 + e_{T5}^2 + e_{T3}^2 \left(\frac{R_1}{R_3 + R_4} \right)^2 + e_{T4}^2 \left(\frac{R_3}{R_3 + R_4} \right)^2 + i_{n1}^2 R_5^2 + i_{n2}^2 (R_3 \parallel R_4)^2$$

Take $e_n^2 = e_{n1}^2 + e_{n2}^2$

$i_n^2 = i_{n1}^2 + i_{n2}^2$

$$\Rightarrow e_{ni}^2 = e_n^2 + 4KTR_5 + 4KTR_3 \frac{R_1^2}{(R_3 + R_4)^2} + 4KTR_4 \frac{R_3^2}{(R_3 + R_4)^2} + i_n^2 [R_5^2 + (R_3 \parallel R_4)^2]$$

$$= e_n^2 + 4KTR_5 + 4KTR_3 \frac{R_1^2}{R_3 + R_4} + i_n^2 [R_5^2 + (R_3 \parallel R_4)^2]$$

For V_p current bias compensation, $R_5 = R_3 \parallel R_4$

$$\Rightarrow e_{ni}^2 = e_n^2 + 4KTR_5 + 4KTR_5 + i_n^2 (R_5^2 + R_5^2)$$


$$= e_n^2 + 8KTR_5 + 2i_n^2 R_5^2$$

Now, $e_o^2 = e_{ni}^2 G_N^2$

$$= G_N^2 [e_n^2 + 8KTR_5 + 2i_n^2 R_5^2]$$

$$E_{No}^2 = \int_{f_L}^{f_H} e_o^2 df$$

⑥ Voltage buffer:

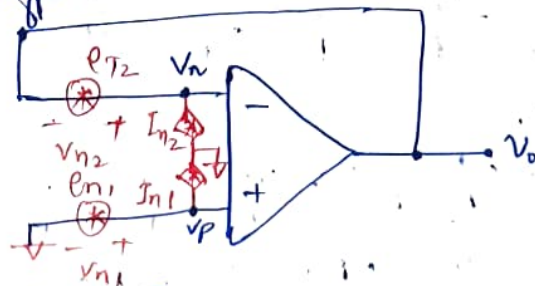

$V_p = V_{n1} \quad \text{--- (1)}$

$V_n = V_{n2} + V_o \quad \text{--- (2)}$

$V_o = A(V_p - V_n)$

$A \rightarrow \infty, \frac{V_o}{A} \rightarrow 0 \Rightarrow V_p = V_n$

$$\Rightarrow V_{n1} = V_{n2} + V_o$$

$$\Rightarrow V_o = V_{n1} - V_{n2}$$

$$G_N = 1$$

$$V_o = G_N V_{ni}$$

$$e_o^2 = G_N^2 e_{ni}^2$$

$$e_{ni}^2 = e_n^2 = e_{nw}^2 \left(1 + \frac{f_{CE}}{f}\right)$$


$$e_o^2 = G_N^2 e_n^2$$

$$E_{no}^2 = \int_{f_L}^{f_H} e_o^2 df = \int_{f_L}^{f_H} G_N^2 e_{nw}^2 \left(1 + \frac{f_{CE}}{f}\right) df$$

$$= G_N^2 e_{nw}^2 \int_{f_L}^{f_H} \left(1 + \frac{f_{CE}}{f}\right) df$$

$$= G_N^2 e_{nw}^2 \left[(f_H - f_L) + f_{CE} \ln\left(\frac{f_H}{f_L}\right) \right]$$

② Trans-impedance amplifier:

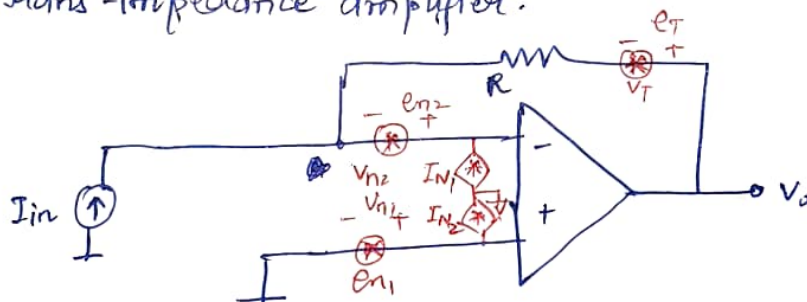

$$V_p = V_{n1} \quad - (1)$$

$$V_n = V_{n2} + V_A \quad - (2)$$

$$\text{KCL at } (A) \Rightarrow \frac{V_A - V_o + V_T}{R} + I_{N2} = 0$$

$$\Rightarrow \frac{V_A}{R} - \frac{V_o}{R} + \frac{V_T}{R} + I_{N2} = 0$$

$$\Rightarrow \frac{V_n - V_{n2} - V_o}{R} + \frac{V_T}{R} + I_{N2} = 0$$

$$[V_A = V_n - V_{n2} \text{ from } (2)]$$

$$\Rightarrow V_n = V_{n2} + V_o - V_T + I_{N2} R$$

$$\text{If } A \rightarrow \infty \Rightarrow \frac{V_o}{A} \rightarrow 0$$

$$\Rightarrow V_p = V_n$$

$$\Rightarrow V_{n1} = V_{n2} + V_o - V_T + I_{N1} R$$

$$e_o^2 = G_N^2 e_{ni}^2, \quad G_N = 1$$

$$e_{ni}^2 = e_{n1}^2 + e_{n2}^2 + e_T^2 + i_{n2}^2 R^2$$

$$\text{Take } e_{n1}^2 + e_{n2}^2 = e_n^2; \quad i_n^2 = i_n^2$$

$$\Rightarrow e_{ni}^2 = e_n^2 + 4KTR + i_n^2 R^2$$

$$E_o^2 = \int_{f_L}^{f_H} e_o^2 df = \int_{f_L}^{f_H} G_N^2 \left[e_{nw}^2 \left(1 + \frac{f_{CE}}{f}\right) + 4KTR + i_n^2 R^2 \left(1 + \frac{f_{CE}}{f}\right) \right] df$$