




Indian Institute of Space Science and Technology
Department of Avionics
AV 211 Analog Electronic Circuits
Quiz 1

Time: 1 hour

Max. marks: 15

Answer all the questions

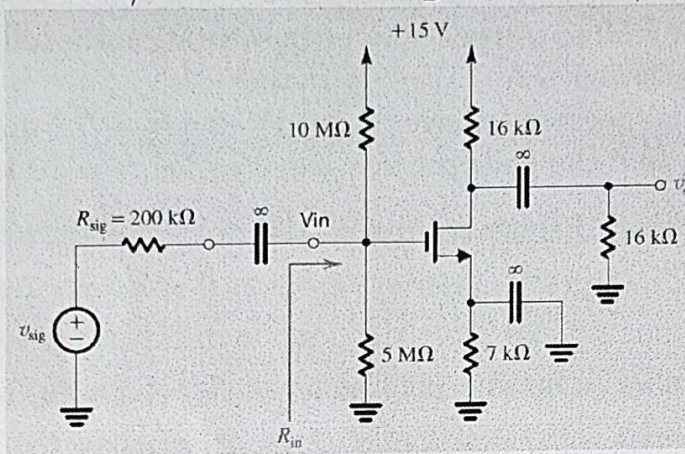1. For the circuit given below, the transistor $V_{TH} = 1V$, $k_n = \mu_n C_{ox} W/L = 4 \text{ mA/V}^2$. The current $I_D = 0.5 \text{ mA}$. (7 marks)



- What is the V_{GS} required by the transistor? (1 mark)
 - What is the transconductance of the transistor (g_m)? (1 mark)
 - What is the input impedance of the amplifier R_{in} ? (1 mark)
 - Draw the complete small signal equivalent circuit for the given amplifier (1 mark)
 - Derive and calculate the small signal voltage gain $\frac{v_o}{v_{in}}$ (2 marks)
 - Derive and calculate the small signal overall voltage gain $\frac{v_o}{v_{sig}}$ (1 mark)
2. You are required to design a common base amplifier. The circuit is given a unipolar supply of +15 V and GND (0V). The amplifier is required to match a TV cable of characteristic impedance 75Ω . In other words, the input impedance of the amplifier is required to be equal to that of the characteristic impedance of the TV cable. (5 marks)
- Draw the full circuit of your amplifier, including biasing arrangements. You do not need to provide the resistor values at this point. (1 mark)

- (b) Draw the small signal equivalent circuit and derive the small signal input impedance of your amplifier (take necessary approximations with justification). (1.5 marks)
 - (c) What is the value of DC collector current that is required to ensure that the required input impedance is achieved? You can take $V_T = 25 \text{ mV}$. (1 mark)
 - (d) If the collector resistor is $20 \text{ K } \Omega$, what is the small signal voltage gain? (1.5 mark)
3. For the circuit shown below, (3 marks)
- (a) Show that for the PMOS transistor to be in saturation the following condition must be satisfied: $IR \leq |V_{tp}|$. (1 mark)
 - (b) If the transistor is specified to have $|V_{tp}| = 1 \text{ V}$ and $k_p = 0.2 \text{ mA/V}^2$, and for $I = 0.1 \text{ mA}$, find the voltages V_{SD} and V_{SG} for $R = 10 \text{ k}\Omega$. (2 marks)

