

Indian Institute of Space Science and Technology (IIST)  
Quiz I Question Paper, September, 2022  
ECE(Avionics), Electromagnetic and Wave Propagation (AV214), 3rd Semester

Marks: 15

Time: 1 Hr.

**Answer all the questions. Make suitable assumptions if necessary.**

1. A  $50 \Omega$  lossless transmission line is terminated with a load impedance  $Z_L = (30 - j50) \Omega$ . The wavelength is 8 cm. Find

- the reflection coefficient at the load end
- the standing wave ratio on the line
- the position of voltage maximum nearest to the load
- the position of current maximum nearest to the load

$$1\frac{1}{2} + 1\frac{1}{2} + 2 + 2$$

2. For the transmission line network shown in Fig.1, calculate the time average power dissipated in the load resistor  $R_L$ .

4

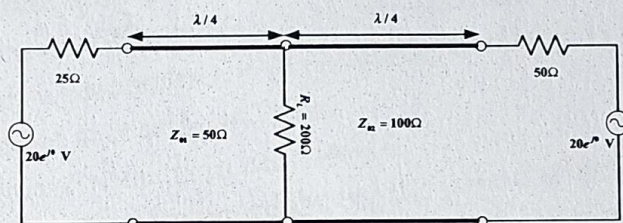


Figure 1: Q. No. 2

3. A transmission line with characteristic impedance of  $150 \Omega$  is terminated with a  $50 \Omega$  load. A distance  $l = 0.375\lambda$  away from the load, an element with  $jB = -j0.003 \text{ S}$  is connected in parallel as shown in Fig. 2. Using Smith chart only, find (a) the load impedance just to the right of  $jB$  ( $Z_1$ ) (b) VSWR on the line to the right of  $jB$  (c) the impedance seen from the left of  $jB$  ( $Z_2$ ) and (d) the VSWR on the line to the left of  $jB$ . Clearly show the points on the Smith chart.

4

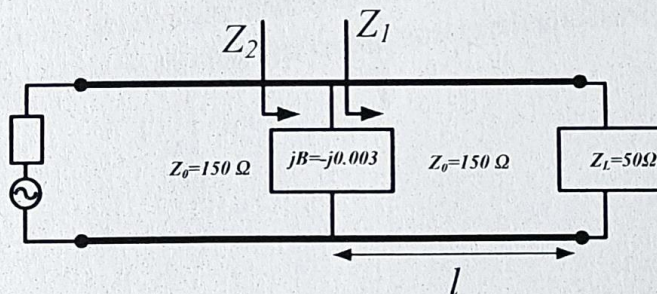


Figure 2: Q. No 3