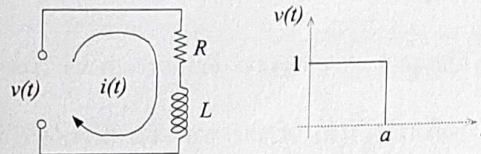


AV 213: Network Analysis

Instructions: Be relaxed. Notations used have their usual meanings unless specified otherwise. There are nine questions. Answer them all. All the best.

- 1) For the network and the input as shown in Figure 1, find the expression of $i(t)$ for $t \geq a$ and then plot its waveform. R , L and a are 1Ω , $4H$ and 2 sec respectively. (5)

Figure 1: $R-L$ network with pulse input.

- 2) For the network shown in Figure 2, find Z and Y parameters in s domain. Values of L , C and R are $1H$, $1F$ and 1Ω respectively (6)

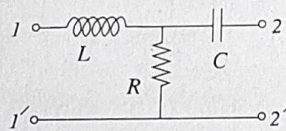


Figure 2: 2 port network.

- 3) For the network shown in Figure 3, derive the expression and the value of resonance frequency ω . Given that $L_1 = 2H$, $L_2 = 10H$, $M = 2H$ and $C = 0.25F$. (5)

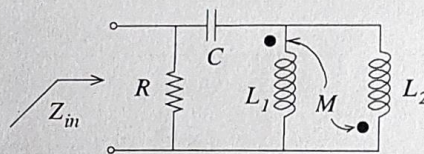


Figure 3: Resonance in network.

- 4) Use Laplace Transformation to find $y(t)$ for the following

$$y'(t) - 6y(t) = 0.$$

It is given that $y(-1) = 4$. (6)

- 5) Design an active 1st order high pass filter which passes frequencies $\geq 2\text{ kHz}$ without any change to gain and phase and attenuates frequencies $\leq 2\text{ Hz}$ by at least 20 dB . Choose the highest possible corner frequency for this application. (6)

- 6) In Figure 4, switch Sw is closed at $t = 0$, the network had previously reached steady state. All the resistors shown are 10Ω resistors and the inductors are $1H$ inductors. Find the current in R_3 applying (a) Thevenin and (b) Norton Theorem. (4 + 3 = 7)

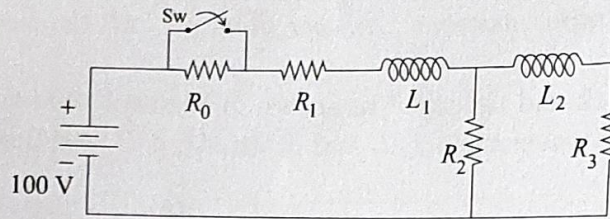
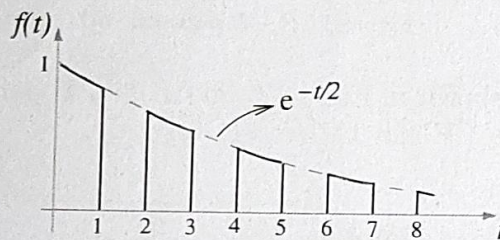


Figure 4: Application of Thevenin and Norton Theorems.

- 7) Find Laplace Transform $F(s)$ of the waveform shown in Figure 5. (5)

Figure 5: Exponentially decaying $f(t)$

- 8) The network shown in Figure 7 had initially reached steady state with the switch Sw open. At $t = 0$, Sw is closed. Find $v_o(t)$ for $t \geq 0$. Given that $I_o = 3A$, $C_o = 2F$, $R_1 = R_2 = 4\Omega$ and $V_B = 24V$. (5)

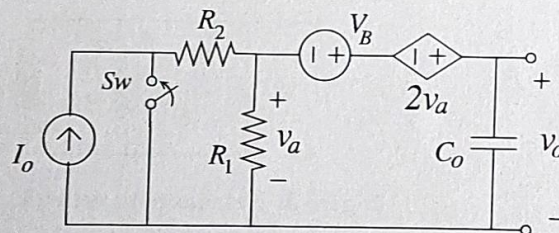


Figure 6: Dual fed network.

- 9) For the network shown in Figure 7, the capacitor was charged to $200kV$ and then the Sw was closed. Let that instant of closure be $t = 0$. Find out v_T for $t \geq 0$ and the time taken to reach the maximum value of v_T . (2 + 3 = 5)

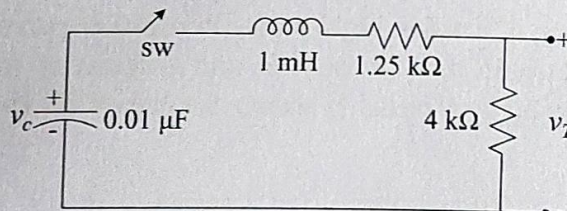


Figure 7: Dual fed network.

end of question paper